




**ACE**

**GATE | PSUs**

ELECTRONICS &

COMMUNICATION ENGINEERING

 

# ELECTRONICS & COMMUNICATION ENGINEERING

## DIGITAL CIRCUITS & MICROPROCESSORS

Volume-1 : Study Material with Classroom Practice Questions

01. Ans: (d)

Sol:  $135_x + 144_x = 323_x$

$$(1 \times x^2 + 3 \times x^1 + 5 \times x^0) + (1 \times x^2 + 4 \times x^1 + 4 \times x^0) = 3x^2 + 2x^1 + 3x^0$$

$$\Rightarrow x^2 + 3x + 5 + x^2 + 4x + 4 = 3x^2 + 2x + 3$$

$$x^2 - 5x - 6 = 0$$

$$(x-6)(x+1) = 0 \quad (\text{Base cannot be negative})$$

Hence  $x = 6$ .

(OR)

As per the given number  $x$  must be greater than 5. Let consider  $x = 6$

$$(135)_6 = (59)_{10}$$

$$(144)_6 = (64)_{10}$$

$$(323)_6 = (123)_{10}$$

$$(59)_{10} + (64)_{10} = (123)_{10}$$

So that  $x = 6$

02. Ans: (a)

Sol: 8-bit representation of

$$+127_{10} = 01111111_{(2)}$$

1's complement representation of

$$-127 = 10000000.$$

2's complement representation of

$$-127 = 10000001.$$

No. of 1's in 2's complement of

$$-127 = m = 2$$

No. of 1's in 1's complement of

$$-127 = n = 1$$

$$\therefore m : n = 2 : 1$$

03. Ans: (c)

Sol: In 2's complement representation the sign bit can be extended towards left any number of times without changing the value. In given number the sign bit is 'X<sub>3</sub>', hence it can be extended left any number of times.

04. Ans: (c)

Sol: Binary representation of  $+(539)_{10}$ :

2	539	
2	269 -1	
2	134 -1	
2	67 -0	
2	33 -1	
2	16 -1	
2	8 -0	
2	4 -0	
2	2 -0	
1	-0	

$$(+539)_{10} = (10000 11 0 11)_2 = (00100 0011011)_2$$

$$2'S \text{ complement} \rightarrow 110111100101$$

$$\text{Hexadecimal equivalent} \rightarrow (DE5)_H$$

05. Ans: 5

Sol: Symbols used in this equation are 0,1,2,3 Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0)(x+3x^0+x^{-1})$$

$$3x^2 + x + 2 = (2x) \left( x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$x(x-5) = 0$$

$$x = 0(\text{or}) x = 5$$

$$x \text{ must be } x > 3, \text{ So } x = 5$$



**06. Ans: 3**

**Sol:**  $123_5 = x8_y$

$$1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0 = x.y^1 + 8 \times y^0$$

$$25 + 10 + 3 = xy + 8$$

$$\therefore xy = 30$$

Possible solutions:

i.  $x = 1, y = 30$

ii.  $x = 2, y = 15$

iii.  $x = 3, y = 10$

$\therefore$  3 possible solutions exists.

**07. Ans: 1**

**Sol:** The range (or) distinct values

$$\text{For 2's complement} \Rightarrow -(2^{n-1}) \text{ to } +(2^{n-1}-1)$$

For sign magnitude

$$\Rightarrow -(2^{n-1}-1) \text{ to } +(2^{n-1}-1)$$


Let  $n = 2 \Rightarrow$  in 2's complement

$$-(2^{2-1}) \text{ to } +(2^{2-1}-1)$$

$$-2 \text{ to } +1 \Rightarrow -2, -1, 0, +1 \Rightarrow X = 4$$

$n = 2$  in sign magnitude  $\Rightarrow -1 \text{ to } +1 \Rightarrow Y = 3$

$$X - Y = 1$$

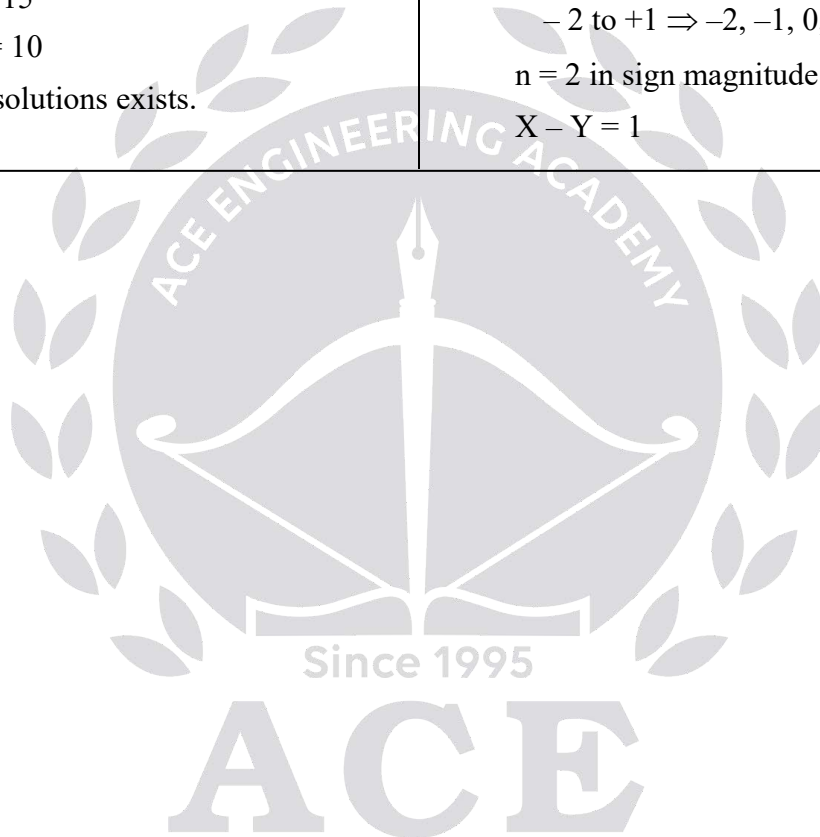

# Chapter 2 Logic Gates & Boolean Algebra

01. Ans: (c)

**Sol:** Given 2's complement numbers of sign bits are x & y. z is the sign bit obtained by adding above two numbers. ∴ Overflow is indicated by  $= \bar{x}\bar{y}z + x y \bar{z}$

**Examples**

1. A = +7    0111  
    B = +7    0111  
       14    1110 ⇒  $\bar{x}\bar{y}z$
2. A = +7    0111  
    B = +5    0101  
       12    1100 ⇒  $\bar{x}\bar{y}z$
3. A = -7    1001  
    B = -7    1001  
       -14   10010 ⇒  $x y \bar{z}$
4. A = -7    1001  
    B = -5    1011  
       -12   10100 ⇒  $x y \bar{z}$

02. Ans: (b)

**Sol:** Truth table of XOR

A	B	o/p
0	0	0
0	1	1
1	0	1
1	1	0

**Stage 1:**

Given one i/p = 1 Always.

1	X	o/p	
1	0	1	= $\bar{X}$
1	1	0	= $X$

For First XOR gate o/p =  $\bar{X}$


**Stage 2:**

$\bar{X}$	X	o/p
0	1	1
1	0	1

For second XOR gate o/p = 1.  
 Similarly for third XOR gate o/p =  $\bar{X}$  & for fourth o/p = 1  
 For Even number of XOR gates o/p = 1  
 For 20 XOR gates cascaded o/p = 1.


03. Ans: (b)

**Sol:**

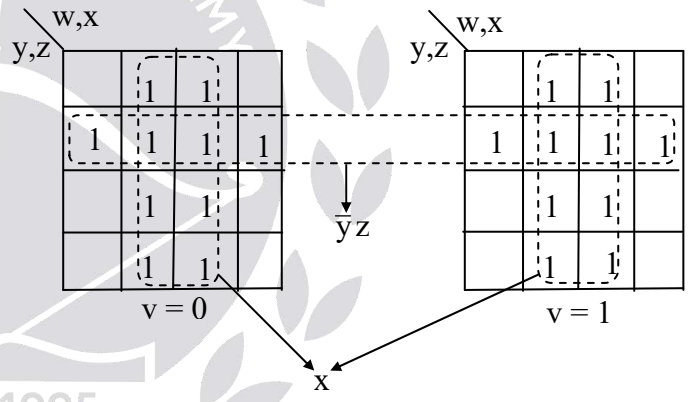

04. Ans: (c)

**Sol:**

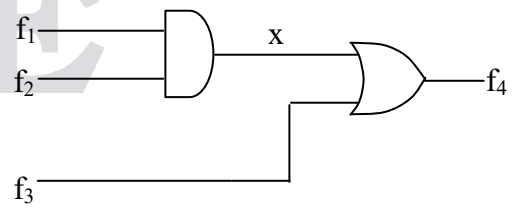



$$x = f_1 f_2$$

$$f_4 = f_1 \cdot f_2 + f_3$$

05. Ans: (d)

**Sol:**

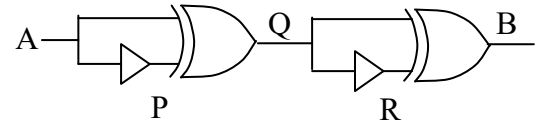

 

**06. Ans: (c)**

**Sol:**  $\overline{x_1} \oplus \overline{x_3} = \overline{x_1 x_3} + \overline{x_1 \overline{x_3}} = y$

$\overline{x_2} \oplus \overline{x_4} = \overline{x_2 x_4} + \overline{x_2 \overline{x_4}} = z$

$(\overline{x_1} \oplus \overline{x_3}) \oplus (\overline{x_2} \oplus \overline{x_4})$

$= y \oplus z = 0$ , when  $y = z$

$\therefore$  option (c) is true

For all cases option A, B, D not satisfy.

**07. Ans: (b)**

**Sol:**  $M(a,b,c) = ab + bc + ca$

$\overline{M(a,b,c)} = \overline{bc} + \overline{ab} + \overline{ac}$

$M(a,b,\overline{c}) = ab + b\overline{c} + \overline{c}a$

$M(\overline{M(a,b,c)}, M(a,b,\overline{c}), c)$

$= (\overline{bc} + \overline{ab} + \overline{ac})(ab + b\overline{c} + ac)$   
 $+ (ab + b\overline{c} + ca)c + (\overline{bc} + \overline{ab} + \overline{ac})c$

$= (\overline{bc} + \overline{ab} + \overline{ac})(ab + b\overline{c} + ac)$   
 $+ (\overline{bc} + \overline{ab} + \overline{ac})c + abc$

$= a\overline{b}\overline{c} + \overline{a}b\overline{c} + abc + \overline{a}\overline{b}c$

$= c[a\overline{b} + \overline{a}b] + c[ab + \overline{a}\overline{b}]$


$= \sum m(1, 2, 4, 7)$

$\therefore M(x, y, z) = a \oplus b \oplus c$

Where  $x = \overline{M(a,b,c)}$ ,  $y = M(a,b,\overline{c})$ ,  $z = c$

**08. Ans: 40**

**Sol:**

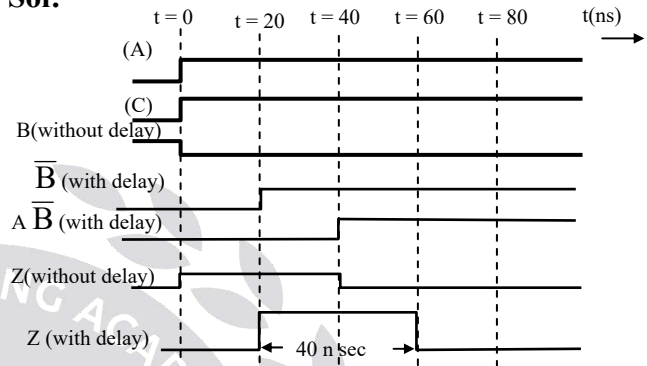

$\therefore Z$  is 1 for 40 nsec

**09. Ans: (c)**


**Sol:** Logic gates  $\overline{X} + Y = \overline{X\overline{Y}} = \overline{X}Y_1$

Where  $Y_1 = \overline{Y}$

It is a NAND gate and thus the gate is 'Universal gate'.

01. Ans: (b)


Sol:

 

$$f = \bar{x}z + x\bar{z}$$

02. Ans: (b)


Sol:

 


$$f = \bar{b} \bar{d} + \bar{b} \bar{c}$$

03.

Sol:

 

$$= y(x+w)$$

 

$$\text{SOP: } x y + y w$$

$$\text{POS: } y(x + w)$$

04. Ans: (a)

Sol: For n-variable Boolean expression,


$$\text{Maximum number of minterms} = 2^n$$

$$\text{Maximum number of implicants} = 2^n$$

$$\begin{aligned} \text{Maximum number of prime implicants} &= \frac{2^n}{2} \\ &= 2^{n-1} \end{aligned}$$

05. Ans: (c)

Sol:

 

$$F(A, B, C) = \bar{A}\bar{C} + BC$$

06. Ans: 1

$$\text{Sol: After minimization} = (\overline{A + B + C + D})$$

$$= ABCD$$

∴ only one minterm.



07. Ans: 3

Sol:  $\bar{w}\bar{z} + \bar{w}x\bar{y} + \bar{x}y\bar{z}$

wx \ yz	00	01	11	10
00	1			1
01	1	1		1
11				
10				1



01. Ans: (d)

Sol: Let the output of first MUX is “F<sub>1</sub>”

$$F_1 = AI_0 + \bar{A}I_1$$

Where A is selection line, I<sub>0</sub>, I<sub>1</sub> = MUX Inputs

$$F_1 = \bar{S}_1 \cdot W + S_1 \cdot \bar{W} = S_1 \oplus W$$

Output of second MUX is

$$F = \bar{A} \cdot I_0 + A \cdot I_1$$

$$F = \bar{S}_2 \cdot F_1 + S_2 \cdot \bar{F}_1$$

$$F = S_2 \oplus F_1$$


$$\text{But } F_1 = S_1 \oplus W$$

$$F = S_2 \oplus S_1 \oplus W$$

$$\text{i.e., } F = W \oplus S_1 \oplus S_2$$

02. Ans: 50





Sol:

 

Initially all the output values are '0', at  $t = 0$ , the inputs to the 4-bit adder are changed to  $X_3X_2X_1X_0 = 1100$ ,  $Y_3Y_2Y_1Y_0 = 0100$

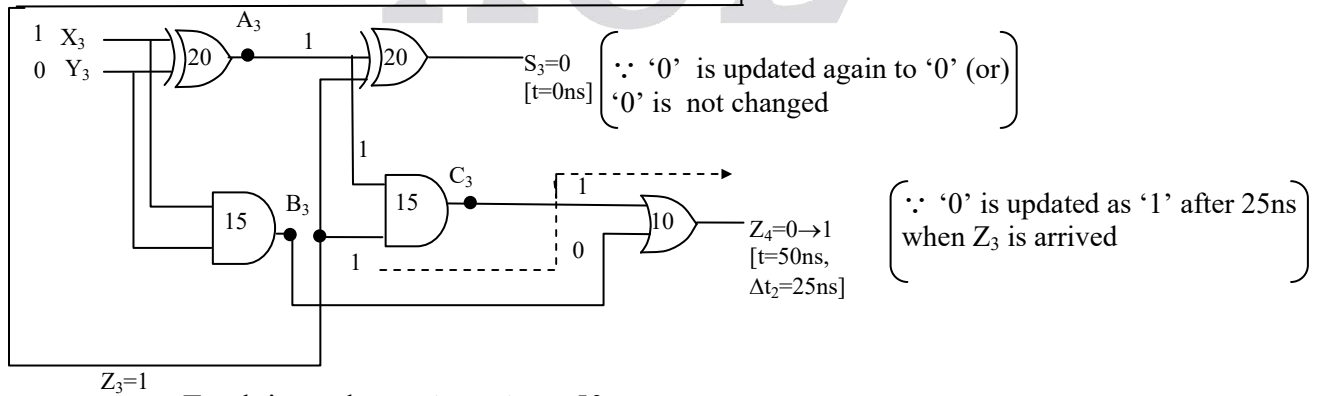 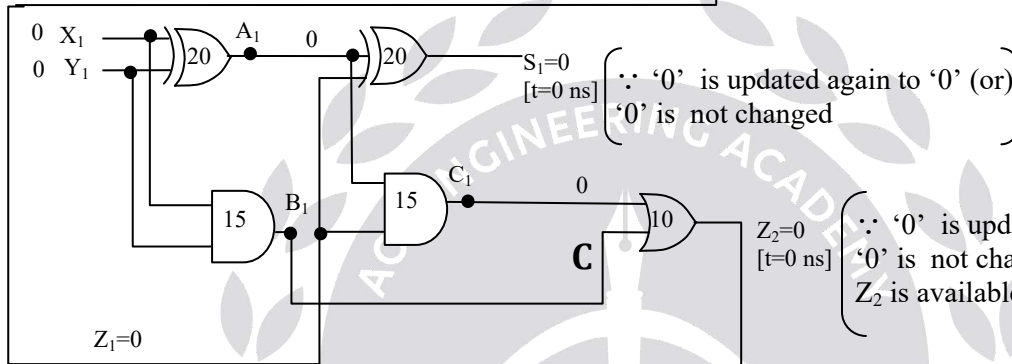 ----- indicates critical path delay to get the output





Total time taken =  $\Delta t_1 + \Delta t_2 = 50$  ns

i.e. critical time (or) maximum time is taken for  $Z_4$  to get final output as '1'



**03. Ans: (a)**

**Sol:** The given circuit is binary parallel adder/subtractor circuit. It performs A+B, A-B but not A + 1 operations.

K	C <sub>0</sub>	Operation
0	0	A+B (addition)
0	1	A+B+1(addition with carry)
1	0	A+ $\bar{B}$ (1's complement addition)
1	1	A+ $\bar{B}$ +1(2's complement subtraction)

**04. Ans: (d)**

**Sol:** It is expansion of 2:4 decoders to 1:8 demultiplexer A<sub>1</sub>, A<sub>0</sub> must be connected to S<sub>1</sub>, S<sub>0</sub> i.e.,  
R = S<sub>0</sub>, S = S<sub>1</sub>

Q must be connected to S<sub>2</sub> i.e., Q = S<sub>2</sub>

P is serial input must be connected to D<sub>in</sub>

**05. Ans: 6**

**Sol:** T = 0 → NOR → MUX 1 → MUX 2  
           2ns       1.5ns       1.5ns

Delay = 2ns + 1.5ns + 1.5ns = 5ns

T = 1 → NOT → MUX 1 → NOR → MUX 2  
           1ns     1.5ns     2ns     1.5ns

Delay = 1ns + 1.5ns + 2ns + 1.5ns = 6ns

Hence, the maximum delay of the circuit is 6ns

**06. Ans: -1**

**Sol:** When all bits in 'B' register is '1', then only it gives highest delay.


∴ '-1' in 8 bit notation of 2's complement is 1111 1111

01. Ans: (c)

Sol: Given Clk,  $X_1, X_2$

Output of First D-FF is  $Q_1$

Output of Second D-FF is  $Q_2$

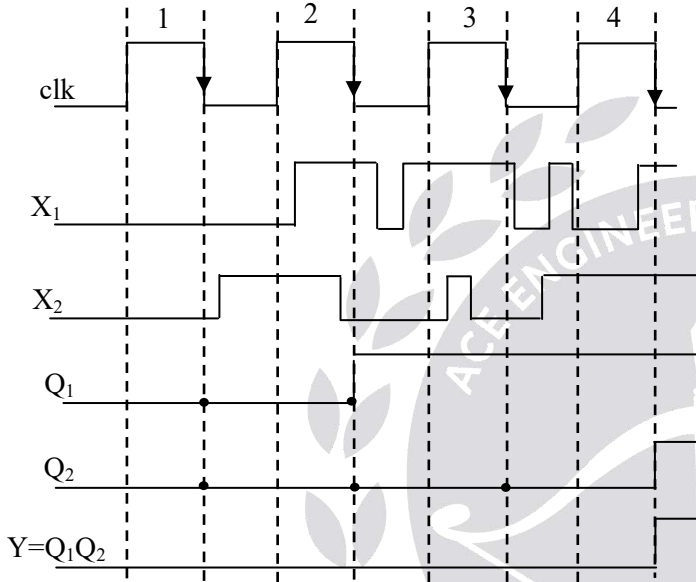

02. Ans: 4

Sol: In the given first loop of states, zero has repeated 3 times. So, minimum 4 number of Flip-flops are needed.

03. Ans: 7

Sol: The counter is cleared when

$$Q_D Q_C Q_B Q_A = 0110$$

Clk	$Q_D$	$Q_C$	$Q_B$	$Q_A$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	0	0	0

As the clear input is given to be synchronous so it waits upto the next clock pulse to clear the counter & hence the counter get's cleared during the 7<sup>th</sup> clock pulse.

$$\therefore \text{mod of counter} = 7$$


04. Ans: (b)

Sol: The given circuit is a mod 4 ripple down counter.  $Q_1$  is coming to 1 after the delay of  $2\Delta t$ .

CLK	$Q_1$	$Q_0$
	0	0
1	1	1
2	1	0
3	0	1
4	0	0

05. Ans: (c)

Sol: Assume  $n = 2$

 

Outputs of counter is connected to inputs of decoder

Counter outputs		Decoder inputs		Decoder outputs			
$Q_1$	$Q_0$	a	b	$d_3$	$d_2$	$d_1$	$d_0$
0	0	0	0	0	0	0	1
0	1	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0

The overall circuit acts as 4-bit ring counter  $n = 2$

$$\therefore k = 2^2 = 4, \text{ k-bit ring counter}$$



06. Ans: (b)

Sol:

CLK	Serial in= $B \oplus C \oplus D$	A B C D
0		1 0 1 0
1	1 →	1 1 0 1
2	0 →	0 1 1 0
3	0 →	0 0 1 1
4	0 →	0 0 0 1
5	1 →	1 0 0 0
6	0 →	0 1 0 0
7	1 →	1 0 1 0

∴ After 7 clock pulses content of shift register become 1010 again

07. Ans: (b)

Sol:

J	K	Q	$\bar{Q}_n$	$T = (J + Q_n)(K + \bar{Q}_n)$	$Q_{n+1}$
0	0	0	1	$0.1 = 0$	0
0	0	1	0	$1.0 = 0$	1
0	1	0	1	$0.1 = 0$	0
0	1	1	0	$1.1 = 1$	0
1	0	0	1	$1.1 = 1$	1
1	0	1	0	$1.0 = 0$	1
1	1	0	1	$1.1 = 1$	1
1	1	1	0	$1.1 = 1$	0

J	$\bar{K}Q_n$	00	01	11	10
0				1	
1		1		1	1


$$T = J \bar{Q}_n + KQ_n = (J + Q_n)(K + \bar{Q}_n)$$

08. Ans: 1.5

Sol:

Clk	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>	Q <sub>5</sub>	Y = Q <sub>3</sub> + Q <sub>5</sub>
0	0	1	0	1	0	0
1	0	0	1	0	1	1
2	1	0	0	1	0	0
3	0	1	0	0	1	1
4	1	0	1	0	0	1
5	0	1	0	1	0	0

 The waveform at OR gate output, Y is [A = +5V]



Average power

$$P = \frac{V_{Ao}^2}{R} = \frac{1}{R} \left[ \frac{1}{T_1} \int_0^{T_1} y^2(t) dt \right] = \frac{1}{RT_1} \left[ \int_T^{2T} A^2 dt + \int_{3T}^{4T} A^2 dt \right]$$

$$= \frac{A^2}{RT_1} [(2T - T) + (4T - 3T)] = \frac{A^2 \cdot 3T}{R(5T)} = \frac{5^2 \cdot 3}{10 \times 5} = 1.5 \text{ mw}$$



09. Ans: (b)

Sol:

Present State	Next State		Output (Y)	
	X = 0	X = 1	X = 0	X = 1
A	A	E	0	0
B	C	A	1	0
C	B	A	1	0
D	A	B	0	1
E	A	C	0	1

Step (1):

By replacing state B as state C then state B, C are equal.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
B	B	A
D	A	B
E	A	B

Step (2):

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
D	A	B
E	A	B

State D, E are equal, remove state E and replace E with D in next state.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B
D	A	B

Finally reduced state table is

Reduced state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B

∴ 3 states are present in the reduced state table

10. Ans: (c)

Sol: State table for the given state diagram

State	Input	Output
S <sub>0</sub>	0	1
S <sub>0</sub>	1	0
S <sub>1</sub>	0	1
S <sub>1</sub>	1	0

Output is 1's complement of input.

11. Ans: (c)

Sol: In state (C), when XYZ = 111, then Ambiguity occurs

Because, from state (C)

⇒ When X = 1, Z = 1

⇒ N.S is (A)

When Y = 1, Z = 1 ⇒ N.S is (B)

# 6

# Logic Gate Families

## Chapter

01. Ans: (D)

Sol:  $V_{OH}(\min)$ :-

(High level output voltage)

The minimum voltage level at a Logic circuit output in the logic '1' state under defined load conditions.

$V_{OL}(\max)$ :-

(Low level output voltage)

The maximum voltage level at a logic circuit output in the Logical '0' state under defined load conditions.

$V_{IL}(\max)$ :- (Low level input voltage)

The maximum voltage level required for a logic '0' at an input. Any voltage above this level will not be accepted as a Low by the logic circuit.

$V_{IH}(\min)$  :- (High level Input voltage)

The minimum voltage level required for logic '1' at an input. Any voltage below this level will not be accepted as a HIGH by the Logic circuit.

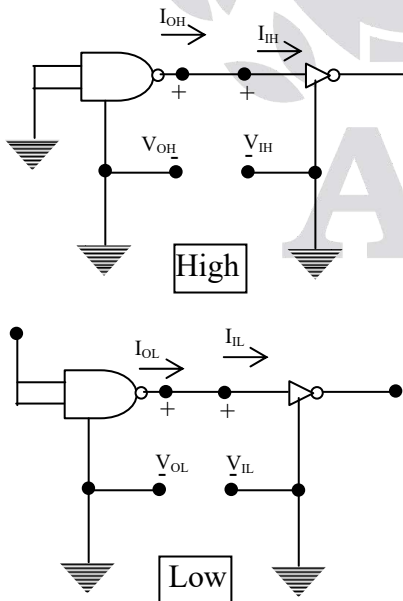


Fig: currents and voltages in the two logic states.

02. Ans: (b)

Sol: Fan out is minimum in DTL

(High Fan-out = CMOS)

Power consumption is minimum in CMOS.  
Propagation delay is minimum in ECL  
(fastest = ECL)

03. Ans: (b)

Sol: When  $V_1 = 2.5V$ ,

$Q_1$  is in reverse active region


$Q_2$  is in saturation region

$Q_3$  is in saturation region

$Q_4$  is in cut-off region

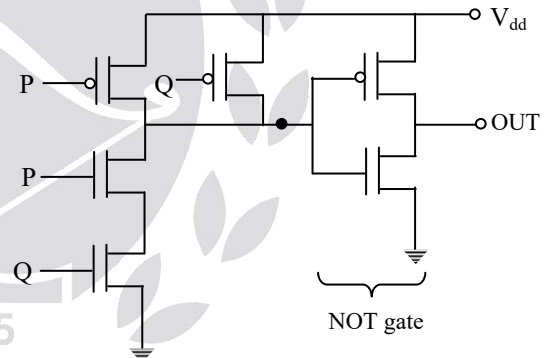04. Ans: (d)

Sol: The given circuit can be redrawn as below:



$$\begin{aligned} \text{OUT} &= \overline{(\overline{PQ})} = PQ \\ &= P \text{ AND } Q \end{aligned}$$

05. Ans: (b)

Sol: As per the description of the question, when the transistor  $Q_1$  and diode both are OFF then only output  $z = 1$ .

X	Y	Z	Remarks
0	0	0	$Q_1$ is OFF, Diode is ON
0	1	1	$Q_1$ is OFF, Diode is OFF
1	0	0	$Q_1$ is ON, Diode is OFF
1	1	0	$Q_1$ is ON, Diode is OFF

$$\text{Hence } Z = \overline{XY}$$

# Chapter 7

## Semiconductor Memories

01. Ans: (b)

Sol: Square of a 4 - bit number can be at most 8 - bit number.

$$\{ \text{i.e. } (1111)_2 = (15)_{10} \\ [(15)_{10}]^2 = (225)_{10} \}$$

Therefore ROM requires 8 data lines.

Data is with size of 4 bits

ROM must require 4 address lines and 8 data lines

$$\text{ROM} = 2^n \times m$$

n = inputs (address lines),

m = output lines

$$n = 4, m = 8.$$

02. Ans: (a)

Sol: ROM is used to design a combinational circuit. The number of address lines of the ROM is equal to the number of input variables in the truth table.

ROM is represented as  $2^n \times m$  where  $2^n$  inputs and m output lines.

[Where n = address bits]

03. Ans: (b)


Sol:

8	4	2	1	2	4	2	1	
i/p s				o/p s				
X <sub>3</sub>	X <sub>2</sub>	X <sub>1</sub>	X <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>	
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	0	2
0	0	1	1	0	0	1	1	3
0	1	0	0	0	1	0	0	4
0	1	0	1	1	0	1	1	5
0	1	1	0	1	1	0	0	6
0	1	1	1	1	1	0	1	7
1	0	0	0	1	1	1	0	8
1	0	0	1	1	1	1	1	9
1	0	1	0	x	x	x	x	
1	0	1	1	x	x	x	x	
1	1	0	0	x	x	x	x	
1	1	0	1	x	x	x	x	
1	1	1	0	x	x	x	x	
1	1	1	1	x	x	x	x	

The outputs are in 2 4 2 1 BCD number

04. Ans: (c)


Sol:

 

At the rising edge of the First clock pulse the content of location  $(0110)_2 = 6 \Rightarrow 1010$  appears on the data bus, at the rising of the second clock pulse the content of location  $(1010)_2 = 10_2 \Rightarrow 1000$  appears on the data bus.

05. Ans: (b)

Sol: 1-bit SRAM memory cell is

 

In 2 Inverters, output of the 1<sup>st</sup> Inverter is connected to Gate Input of 2<sup>nd</sup> Inverter and vice versa.

# 8

## A/D & D/A Converters

### Chapter


01. Ans: (b)

Sol:

CLK	Counter			Decoder				V <sub>0</sub>
	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	
1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	1
3	0	1	0	0	0	1	0	2
4	0	1	1	0	0	1	1	3
5	1	0	0	1	0	0	0	8
6	1	0	1	1	0	0	1	9
7	1	1	0	1	0	1	0	10
8	1	1	1	1	0	1	1	11

02. Ans: (b)

Sol:

 

$$R_{\text{equ}} = (((((2R \parallel 2R) + R) \parallel 2R) + R) \parallel 2R) + R \parallel 2R$$

$$R_{\text{equ}} = R = 10\text{k}\Omega.$$

$$I = \frac{V_R}{R} = \frac{10\text{V}}{10\text{k}} = 1\text{mA}.$$

$$\begin{aligned} \text{Current division at } \frac{I}{16} \\ = \frac{1 \times 10^{-3}}{16} = 62.5 \mu\text{A} \end{aligned}$$

03. Ans: (c)

Sol: Net current at inverting terminal,

$$I_i = \frac{I}{4} + \frac{I}{16} = \frac{5I}{16}$$

$$\begin{aligned} V_0 &= -I_i R = -\frac{5I}{16} \times 10\text{k}\Omega \\ &= \frac{-5 \times 1 \times 10^{-3} \times 10 \times 10^3}{16} = -3.125\text{V} \end{aligned}$$

04. Ans: (d)

Sol: Given that  $V_{\text{DAC}} = \sum_{n=0}^3 2^{n-1} b_n$  Volts

$$V_{\text{DAC}} = 2^{-1} b_0 + 2^0 b_1 + 2^1 b_2 + 2^2 b_3$$

$$\Rightarrow V_{\text{DAC}} = 0.5b_0 + b_1 + 2b_2 + 4b_3$$

Initially counter is in 0000 state

Up counter o/p	V <sub>DAC</sub> (V)	o/p of comparator
0 0 0 0	0	1
0 0 0 1	0.5	1
0 0 1 0	1	1
0 0 1 1	1.5	1
0 1 0 0	2	1
0 1 0 1	2.5	1
0 1 1 0	3	1
0 1 1 1	3.5	1
1 0 0 0	4	1
1 0 0 1	4.5	1
1 0 1 0	5	1
1 0 1 1	5.5	1
1 1 0 0	6	1
1 1 0 1	6.5	0

When  $V_{\text{DAC}} = 6.5\text{V}$ , the o/p of comparator is '0'. At this instant, the clock pulses to the counter are stopped and the counter remains in 1101 state.

$\therefore$  The stable reading of the LED display is 13.





**05. Ans: (b)**

**Sol:** The magnitude of error between  $V_{DAC}$  &  $V_{in}$  at steady state is  $|V_{DAC} - V_{in}| = |6.5 - 6.2|$   
 $= 0.3 \text{ V}$

**06. Ans: (a)**

**Sol:** In Dual slope

$$\text{ADC} \Rightarrow V_{in} T_1 = V_R \cdot T_2$$

$$\Rightarrow V_{in} = \frac{V_R T_2}{T_1}$$

$$= \frac{100 \text{ mV} \times 370.2 \text{ ms}}{300 \text{ ms}}$$

DVM indicates = 123.4

**07. Ans: (d)**

**Sol:** Ex:  $f_{in} = 1 \text{ kHz} \rightarrow f_s = 2 \text{ kHz}$

$$f_{in} = 25 \text{ kHz} \leftarrow f_s = 50 \text{ kHz}$$

$$1. \text{ Max conversion time} = 2^{N+1} T = 2^{11} \cdot 1 \mu\text{s} \\ = 2048 \mu\text{s}$$


$$2. \text{ Sampling period} = T_s \geq \text{maximum} \\ \text{conversion time}$$

$$T_s \geq 2048 \mu\text{s}$$

$$3. \text{ Sampling rate } f_s = \frac{1}{T_s} \leq \frac{1}{2048 \times 10^{-6}}$$

$$f_s \leq 488 \quad f_s \leq 500 \text{ Hz}$$
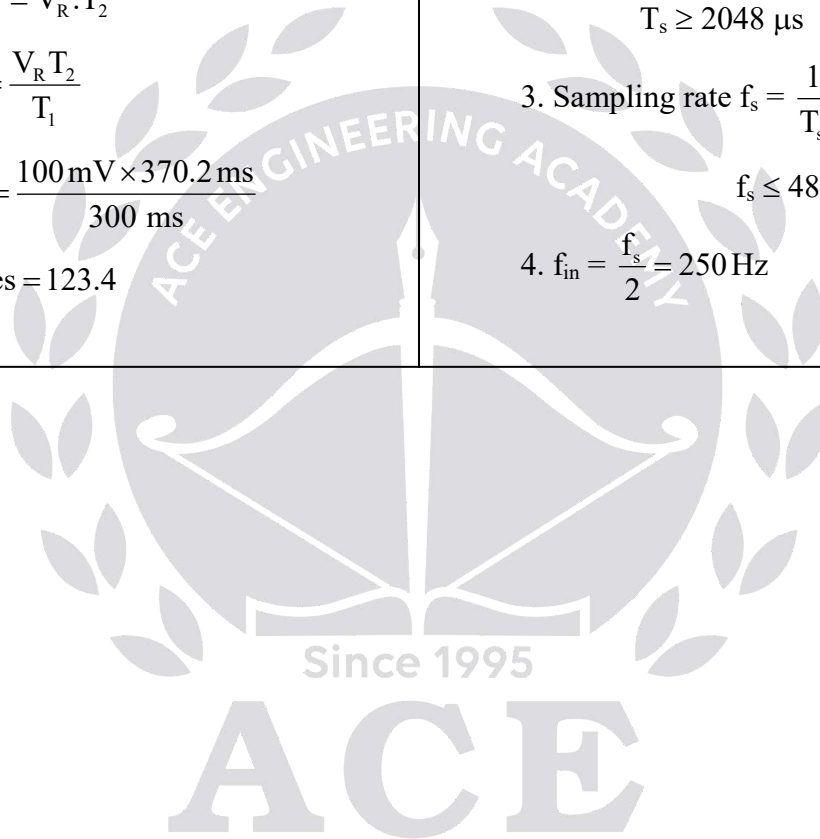
$$4. f_{in} = \frac{f_s}{2} = 250 \text{ Hz}$$



# Chapter 9

## Architecture, Pin Details of 8085 & Interfacing with 8085

01. Ans: (a)

Sol: chip select is an active low signal for  $\text{chipselect} = 0$ ; the inputs for NAND gate must be let us see all possible cases for  $\text{chipselect} = 0$  condition


A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	X	X
0	0	1	1	0	0	X	X
0	1	0	1	0	0	X	X
0	1	1	0	0	0	X	X
1	0	0	1	0	0	X	X
1	0	1	0	0	0	X	X
0	0	0	0	1	1	X	X
0	0	1	1	1	1	X	X
0	1	0	1	0	0	X	X
0	1	1	0	0	0	X	X
1	0	0	1	0	0	X	X
1	0	0	0	0	0	X	X

→ 60H (A<sub>1</sub>A<sub>0</sub>=00)  
→ 63H (A<sub>1</sub>A<sub>0</sub>=11)

The only option that suits here is option(a)

A<sub>0</sub> & A<sub>1</sub> are used for line selection

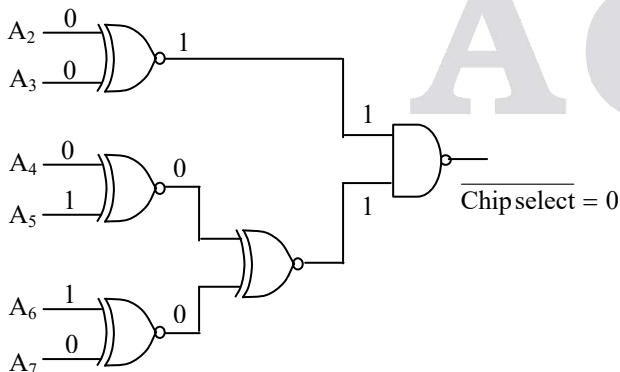A<sub>2</sub> to A<sub>7</sub> are used for chip selection



∴ Address space is 60H to 63H

A<sub>0</sub> to A<sub>11</sub> are used for line selection

A<sub>12</sub> to A<sub>15</sub> are used for chip selection

A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub> -----A <sub>0</sub>
1	1	1	0	0-----0 =E000H
1	1	1	0	1-----1 =EFFFH

02. Ans: (d)

Sol:

- Both the chips have active high chip select inputs.
- Chip 1 is selected when A<sub>8</sub> = 1, A<sub>9</sub> = 0
- Chip 2 is selected when A<sub>8</sub> = 0, A<sub>9</sub> = 1
- Chips are not selected for combination of 00 & 11 of A<sub>8</sub> & A<sub>9</sub>
- Upon observing A<sub>8</sub> & A<sub>9</sub> of given address Ranges, F800 to F9FF is not represented

03. Ans: (d)

Sol: The I/O device is interfaced using “Memory Mapped I/O” technique.

The address of the Input device is

A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub>	A <sub>10</sub>	A <sub>9</sub>	A <sub>8</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
1	1	1	1	1	0	0	0	1	1	1	1	1	0	0	0

=F8F8<sub>H</sub>

The Instruction for correct data transfer is = LDA F8F8H

04. Ans: (b)

Sol:

- Out put 2 of 3×8 Decoder is used for selecting the output port. ∴ Select code is 010

$$\begin{array}{cccccccc} \underline{A_{15}} & \underline{A_{14}} & \underline{A_{13}} & \underline{A_{12}} & \underline{A_{11}} & \underline{A_{10}} & \text{---} & \underline{A_0} \\ 0 & 1 & 0 & 1 & 0 & 0 & \text{---} & 0 \\ \Rightarrow & 5000\text{H} & & & & & & \end{array}$$

- This mapping is memory mapped I/O




05. Ans: (d)

Sol:

A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub>	A <sub>10</sub>	A <sub>9</sub> ----	A <sub>0</sub>	
0	0	0	0	1	0	0	----	0 =0800H
			⋮					⋮
0	0	0	0	1	0	1	----	1 =0BFFH
			⋮					⋮
0	0	0	1	1	0	0	----	0 =1800H
			⋮					⋮
0	0	0	1	1	0	1	----	1 =1BFFH
			⋮					⋮
0	0	1	0	1	0	0	----	0 =2800H
			⋮					⋮
0	0	1	0	1	0	1	----	1 =2BFFH
			⋮					⋮
0	0	1	1	1	0	0	----	0 =3800H
			⋮					⋮
0	0	1	1	1	0	1	----	1 =3BFFH

06. Ans: (a)

Sol: Address Range given is

 

	A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub>	A <sub>10</sub>	A <sub>9</sub>	A <sub>8</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
1000H →	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
2FFFH →	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1

To provide  $\overline{CS}$  as low, The condition is

$$A_{15} = A_{14} = 0 \text{ and } A_{13} A_{12} = 01 \text{ (or) } (10)$$


i.e  $A_{15} = A_{14} = 0$  and  $A_{13} A_{12}$  shouldn't be 00, 11.

$$\text{Thus it is } A_{15} + A_{14} + [A_{13}A_{12} + \overline{A_{13}}\overline{A_{12}}]$$



07. Ans: (a)

Sol:

 


$A_{15}, A_{14}$  are used for chip selection

$A_{13}, A_{12}, A_{11}$  are used for input of decoder

$A_{15}$	$A_{14}$	$A_{13}$	$A_{12}$	$A_{11}$	$A_{10}$ ----- $A_0$
Enable of decoder		Input of decoder			Address of chip

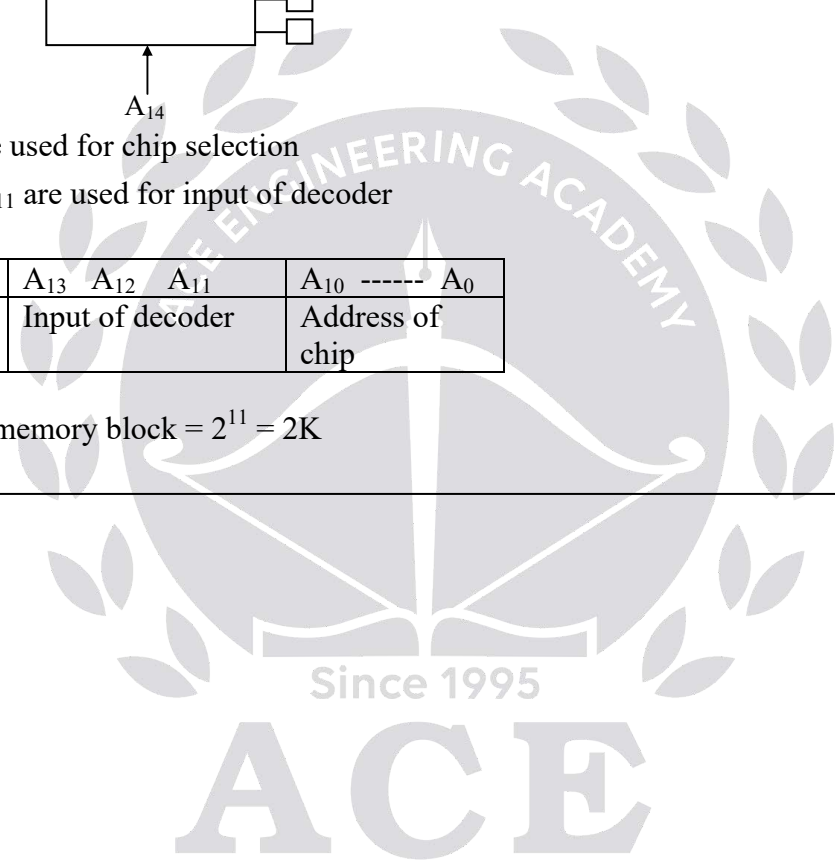Size of each memory block =  $2^{11} = 2K$



**01. Ans: (c)**

**Sol:**

6010H : LXI H,8A79H ; (HL) = 8A79H  
 6013H : MOV A, L ; (A)←(L) = 79  
 6014H : ADD H ; (A) = 0111 1001  
           +  
           ; (H) = 1000 1010  
           ; (A) = 0000 0011  
           CY = 1, AC = 1  
 6015H : DAA ; 66 Added to (A)  
                   since CY=1 &  
                   AC=1  
           ; (A) = 69H  
 6016H : MOV H,A ; (H)←(A) =69H  
 6017H : PCHL ; (PC)←(HL) = 6979H

**02. Ans: (c)**

**Sol:** 0100H : LXI SP, 00FFH ; (SP) = 00FFH  
 0103H : LXI H, 0107 H ; (HL) = 0107H  
 0106H : MVI A, 20H ; (A) = 20H  
 0108H : SUB M ; (A)←(A)-(0107)  
           ; (0107) = 20H  
           ; (A) = 00H

The contents of Accumulator is 00H

**03. Ans: (c)**

**Sol:** SUB1 : MVI A, 00H   A← 00H  
           CALL SUB2 → program will shifted to  
                   SUB 2 address location  
   A  
 SUB 2 : INR A →

01H

RET → returned to the main program

∴ The contents of Accumulator after execution of the above SUB2 is 02H

**04. Ans: (c)**

**Sol:** The loop will be executed until the value in register equals to zero, then,

Execution time

$$= 9(7T+4T+4T+10T) + (7T+4T+4T+7T) + 7T$$

$$= 254T$$

**05. Ans: (d)**

**Sol:** H=255 : L = 255, 254, 253, ----0

H=254 : L = 0, 255, 254, -----0

H=1 : L = 0,255,254,253,---0

H=0 : —

→ In first iteration (with H=255), the value in L is decremented from 255 to 0 i.e., 255 times

→ In further remaining 254 iterations, the value in L is decremented from 0 to 0 i.e., 256 times

∴ 'DCRL' instruction gets executed for

$$\Rightarrow [255 + (254 \times 256)]$$

$$\Rightarrow 65279 \text{ times}$$

**06. Ans: (a)**

**Sol:** "STA 1234H" is a 3-Byte Instruction and it requires 4 Machine cycles (Opcode fetch, Operand1 Read, Operand2 Read, Memory write). The Higher order Address (A<sub>15</sub> - A<sub>8</sub>) sent in 4 machine cycles is as follows

Given "STA 1234" is stored at 1FFEh



i.e.,            Address            Instruction  
  
                  1FFE, 1FFF, 2000 : STA 1234H

Machine cycle	Address (A <sub>15</sub> -A <sub>0</sub> )	Higher order address (A <sub>15</sub> -A <sub>8</sub> )
1. Opcode fetch	1FFE <sub>H</sub>	1F <sub>H</sub>
2. Operand1 Read	1FFF <sub>H</sub>	1F <sub>H</sub>
3. Operand2 Read	2000 <sub>H</sub>	20 <sub>H</sub>
4. Memory Write	1234 <sub>H</sub>	12 <sub>H</sub>

i.e. Higher order Address sent on A<sub>15</sub>-A<sub>8</sub> for 4 Machine Cycles are 1F<sub>H</sub>, 1F<sub>H</sub>, 20<sub>H</sub>, 12<sub>H</sub>.

**07. Ans: (d)**

**Sol:** The operation SBI BE<sub>H</sub> indicates A-BE → A where A indicates accumulator  
Thus the result of the subtraction operation is stored in the accumulator and the contents of accumulator are changed.

**08. Ans: (c)**

**Sol:** If the content in register B is to be multiplied with the content in register C, the contents of register B is added to the accumulator (initial value of accumulator is 0) for C times.

