 




ACE
GATE | PSUs

ELECTRICAL

ENGINEERING



ELECTRICAL ENGINEERING

DIGITAL ELECTRONICS & MICROPROCESSORS

Volume-1 : Study Material with Classroom Practice Questions

Digital & Microprocessors

(Solutions for Volume-1 Class Room Practice Questions)

01. Number System

01. Ans: (d)

Sol: $135_x + 144_x = 323_x$

$$(1 \times x^2 + 3 \times x^1 + 5 \times x^0) + (1 \times x^2 + 4 \times x^1 + 4 \times x^0) = 3x^2 + 2x^1 + 3x^0$$

$$\Rightarrow x^2 + 3x + 5 + x^2 + 4x + 4 = 3x^2 + 2x + 3$$

$$x^2 - 5x - 6 = 0$$

$$(x-6)(x+1) = 0 \quad (\text{Base cannot be negative})$$

Hence $x = 6$.

(OR)

As per the given number x must be greater than 5. Let consider $x = 6$

$$(135)_6 = (59)_{10}$$

$$(144)_6 = (64)_{10}$$

$$(323)_6 = (123)_{10}$$

$$(59)_{10} + (64)_{10} = (123)_{10}$$

So that $x = 6$

02. Ans: (a)

Sol: 8-bit representation of

$$+127_{10} = 01111111_{(2)}$$

1's complement representation of

$$-127 = 10000000.$$

2's complement representation of

$$-127 = 10000001.$$

No. of 1's in 2's complement of

$$-127 = m = 2$$

No. of 1's in 1's complement of

$$-127 = n = 1$$

$$\therefore m:n = 2:1$$

03. Ans: (c)

Sol: In 2's complement representation the sign bit can be extended towards left any number of times without changing the value. In given number the sign bit is ' X_3 ', hence it can be extended left any number of times.

04. Ans: (c)

Sol: Binary representation of $+(539)_{10}$:

$$\begin{array}{r} 2 \overline{) 539} \\ 2 \overline{) 269} -1 \\ 2 \overline{) 134} -1 \\ 2 \overline{) 67} -0 \\ 2 \overline{) 33} -1 \\ 2 \overline{) 16} -1 \\ 2 \overline{) 8} -0 \\ 2 \overline{) 4} -0 \\ 2 \overline{) 2} -0 \\ 1 \overline{) 1} -0 \end{array}$$

$$(+539)_{10} = (10000 \ 11 \ 0 \ 11)_2 = (00100 \ 0011011)_2$$

$$2\text{'S complement} \rightarrow 110111100101$$

$$\text{Hexadecimal equivalent} \rightarrow (DE5)_H$$

05. Ans: 5

Sol: Symbols used in this equation are 0,1,2,3

Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0)(x+3x^0+x^{-1})$$

$$3x^2 + x + 2 = (2x) \left(x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$x(x-5) = 0$$

$$x = 0(\text{or}) x = 5$$



x must be $x > 3$, So $x = 5$

06. Ans: 3

Sol: $123_5 = x8_y$

$$1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0 = x.y^1 + 8 \times y^0$$

$$25 + 10 + 3 = xy + 8$$

$$\therefore xy = 30$$

Possible solutions:

i. $x = 1, y = 30$

ii. $x = 2, y = 15$

iii. $x = 3, y = 10$

\therefore 3 possible solutions exists.

07. Ans: 1

Sol: The range (or) distinct values

For 2's complement $\Rightarrow -(2^{n-1})$ to $+(2^{n-1}-1)$

For sign magnitude

$$\Rightarrow -(2^{n-1}-1) \text{ to } +(2^{n-1}-1)$$

Let $n = 2 \Rightarrow$ in 2's complement

$$-(2^{2-1}) \text{ to } +(2^{2-1}-1)$$

$$-2 \text{ to } +1 \Rightarrow -2, -1, 0, +1 \Rightarrow X = 4$$

$n = 2$ in sign magnitude $\Rightarrow -1$ to $+1$

$$\Rightarrow Y = 3$$

$$X - Y = 1$$

02. Logic Gates & Boolean Algebra

01. Ans: (c)

Sol: Given 2's complement numbers of sign bits are x & y. z is the sign bit obtained by adding above two numbers. \therefore Overflow is indicated by $= \bar{x}\bar{y}z + x y \bar{z}$

Examples

1. $A = +7$ 0111

$B = +7$ 0111

14 1110 $\Rightarrow \bar{x}\bar{y}z$

2. $A = +7$ 0111

$B = +5$ 0101

12 1100 $\Rightarrow \bar{x}\bar{y}z$

3. $A = -7$ 1001

$B = -7$ 1001

-14 10010 $\Rightarrow x y \bar{z}$

4. $A = -7$ 1001

$B = -5$ 1011

-12 10100 $\Rightarrow x y \bar{z}$

02. Ans: (b)

Sol: Truth table of XOR

A	B	o/p
0	0	0
0	1	1
1	0	1
1	1	0

Stage 1:

Given one i/p = 1 Always.

$$1 \quad X \quad \text{o/p}$$

$$1 \quad 0 \quad 1 = \bar{X}$$

$$1 \quad 1 \quad 0 = \bar{X}$$

For First XOR gate o/p = \bar{X}

Stage 2:

$$\bar{X} \quad X \quad \text{o/p}$$

$$0 \quad 1 \quad 1$$

$$1 \quad 0 \quad 1$$



For second XOR gate o/p = 1.


Similarly for third XOR gate o/p = \bar{X} & for fourth o/p = 1

For Even number of XOR gates o/p = 1

For 20 XOR gates cascaded o/p = 1.


03. Ans: (b)

Sol:

 

04. Ans: (c)

Sol:


 


$$x = f_1 f_2$$

$$f_4 = f_1 \cdot f_2 + f_3$$

05. Ans: (d)

Sol:

  

06. Ans: (c)

$$\text{Sol: } \bar{x}_1 \oplus \bar{x}_3 = \bar{x}_1 x_3 + x_1 \bar{x}_3 = y$$

$$\bar{x}_2 \oplus \bar{x}_4 = \bar{x}_2 x_4 + x_2 \bar{x}_4 = z$$

$$(\bar{x}_1 \oplus \bar{x}_3) \oplus (\bar{x}_2 \oplus \bar{x}_4)$$

$$= y \oplus z = 0, \text{ when } y = z$$

\therefore option (c) is true

For all cases option A, B, D not satisfy.

07. Ans: (b)

$$\text{Sol: } M(a,b,c) = ab + bc + ca$$

$$\overline{M(a,b,c)} = \bar{b}\bar{c} + \bar{a}\bar{b} + \bar{a}\bar{c}$$

$$M(a,b,\bar{c}) = ab + b\bar{c} + \bar{c}a$$

$$M(\overline{M(a,b,c)}, M(a,b,\bar{c}), c)$$

$$= (\bar{b}\bar{c} + \bar{a}\bar{b} + \bar{a}\bar{c})(ab + b\bar{c} + \bar{c}a)$$

$$+ (ab + \bar{b}\bar{c} + \bar{c}a)c + (\bar{b}\bar{c} + \bar{a}\bar{b} + \bar{a}\bar{c})c$$

$$= (\bar{b}\bar{c} + \bar{a}\bar{b} + \bar{a}\bar{c})(ab + b\bar{c} + \bar{c}a)$$

$$+ (\bar{b}\bar{c} + \bar{a}\bar{b} + \bar{a}\bar{c})c + abc$$

$$= \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + ab\bar{c} + \bar{a}\bar{b}c$$

$$= \bar{c}[ab + \bar{a}b] + c[ab + \bar{a}b]$$

$$= \sum m(1, 2, 4, 7)$$


$$\therefore M(x, y, z) = a \oplus b \oplus c$$



Where $x = M(a, b, c)$, $y = M(a, b, \bar{c})$, $z = c$

08. Ans: 40

Sol:

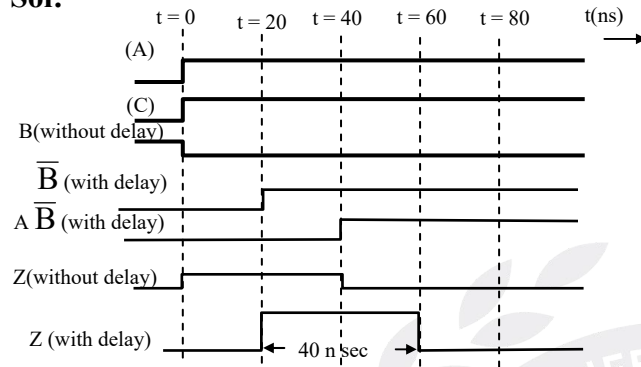

$\therefore Z$ is 1 for 40 nsec

09. Ans: (c)

Sol: Logic gates $\bar{X} + Y = \overline{XY} = \overline{XY_1}$


Where $Y_1 = \bar{Y}$

It is a NAND gate and thus the gate is 'Universal gate'.

03. K-Maps

01. Ans: (b)


Sol:

 

$$f = \bar{x}z + x\bar{z}$$

02. Ans: (b)


Sol:

 


$$f = \bar{b}\bar{d} + \bar{b}\bar{c}$$

03.

Sol:

 

$$= y(x+w)$$

 

$$= xy + yw$$

$$\text{SOP: } x y + y w$$

$$\text{POS: } y(x + w)$$

04. Ans: (a)

Sol: For n -variable Boolean expression,

Maximum number of minterms = 2^n



Maximum number of implicants = 2^n

Maximum number of prime implicants = $\frac{2^n}{2}$
= 2^{n-1}

05. Ans: (c)

Sol:

AB \ C	00	01	11	10
0	1	1	0	0
1	0	1	1	0

$$F(A, B, C) = \bar{A}\bar{C} + BC$$

06. Ans: 1

Sol: After minimization = $(\bar{A} + \bar{B} + \bar{C} + \bar{D})$
= ABCD


∴ only one minterm.

07. Ans: 3

Sol: $\bar{w}\bar{z} + \bar{w}xy + \bar{x}y\bar{z}$

02. Ans: 50

Sol:

 

Initially all the output values are '0', at $t = 0$, the inputs to the 4-bit adder are changed to $X_3X_2X_1X_0 = 1100$, $Y_3Y_2Y_1Y_0 = 0100$

----- indicates critical path delay to get the output

yz \ wx	00	01	11	10
00	1			1
01	1	1		1
11				
10				1

04. Combinational Circuits

01. Ans: (d)

Sol: Let the output of first MUX is "F₁"

$$F_1 = AI_0 + AI_1$$

Where A is selection line, I_0, I_1 = MUX

Inputs

$$F_1 = \bar{S}_1 \cdot W + S_1 \cdot \bar{W} = S_1 \oplus W$$

Output of second MUX is

$$F = \bar{A} \cdot I_0 + A \cdot I_1$$


$$F = \bar{S}_2 \cdot F_1 + S_2 \cdot \bar{F}_1$$

$$F = S_2 \oplus F_1$$

$$\text{But } F_1 = S_1 \oplus W$$

$$F = S_2 \oplus S_1 \oplus W$$
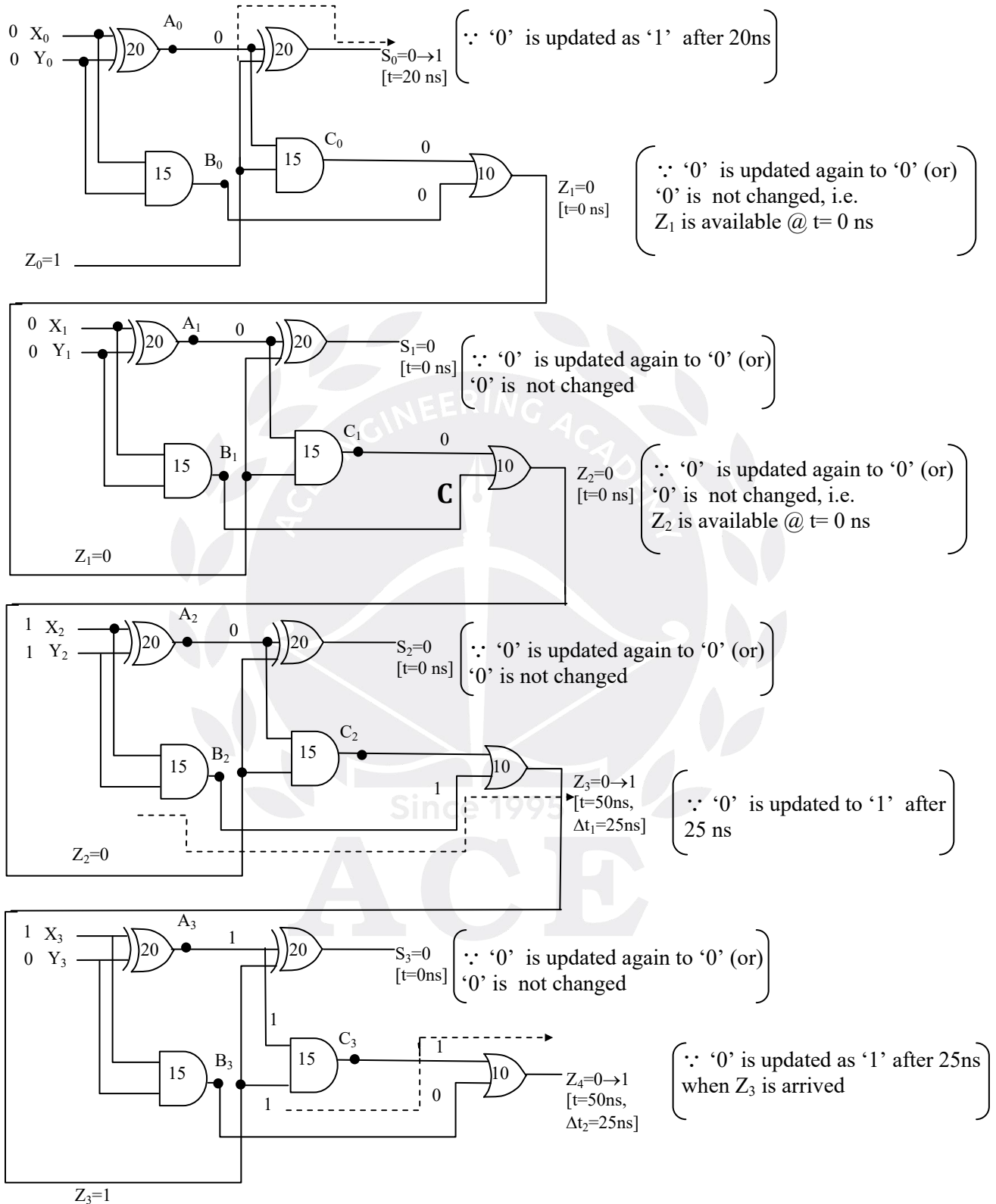
$$\text{i.e., } F = W \oplus S_1 \oplus S_2$$



Total time taken = $\Delta t_1 + \Delta t_2 = 50 \text{ ns}$

i.e. critical time (or) maximum time is taken for Z_4 to get final output as '1'



03. Ans: (a)

Sol: The given circuit is binary parallel adder/subtractor circuit. It performs $A+B$, $A-B$ but not $A+1$ operations.

K	C ₀	Operation
0	0	$A+B$ (addition)
0	1	$A+B+1$ (addition with carry)
1	0	$A+\overline{B}$ (1's complement addition)
1	1	$A+\overline{B}+1$ (2's complement subtraction)

04. Ans: (d)

Sol: It is expansion of 2:4 decoders to 1:8 demultiplexer A_1, A_0 must be connected to S_1, S_0 i.e., $R = S_0, S = S_1$
 Q must be connected to S_2 i.e., $Q = S_2$
 P is serial input must be connected to D_{in}

05. Ans: 6

Sol: $T = 0 \rightarrow \text{NOR} \rightarrow \text{MUX 1} \rightarrow \text{MUX 2}$
 2ns 1.5ns 1.5ns

Delay = $2\text{ns} + 1.5\text{ns} + 1.5\text{ns} = 5\text{ns}$

$T = 1 \rightarrow \text{NOT} \rightarrow \text{MUX 1} \rightarrow \text{NOR} \rightarrow \text{MUX 2}$
 1ns 1.5ns 2ns 1.5ns

Delay = $1\text{ns} + 1.5\text{ns} + 2\text{ns} + 1.5\text{ns} = 6\text{ns}$

Hence, the maximum delay of the circuit is 6ns

06. Ans: -1

Sol: When all bits in 'B' register is '1', then only it gives highest delay.

\therefore '-1' in 8 bit notation of 2's complement is 1111 1111


05. Sequential Circuits

01. Ans: (c)

Sol: Given Clk, X_1, X_2

Output of First D-FF is Q_1

Output of Second D-FF is Q_2

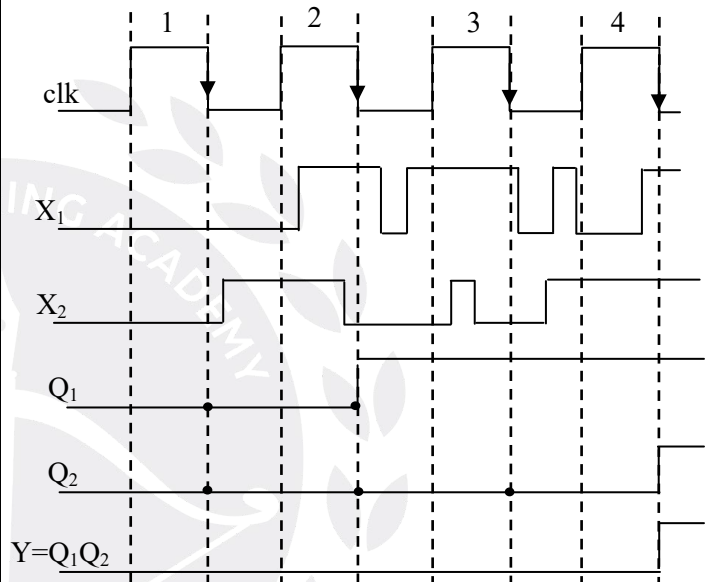

02. Ans: 4

Sol: In the given first loop of states, zero has repeated 3 times. So, minimum 4 number of Flip-flops are needed.

03. Ans: 7

Sol: The counter is cleared when

$$Q_D Q_C Q_B Q_A = 0110$$

Clk	Q _D	Q _C	Q _B	Q _A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1



4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	0	0	0

As the clear input is given to be synchronous so it waits upto the next clock pulse to clear the counter & hence the counter get's cleared during the 7th clock pulse.

\therefore mod of counter = 7


04. Ans: (b)

Sol: The given circuit is a mod 4 ripple down counter. Q_1 is coming to 1 after the delay of $2\Delta t$.

CLK	Q_1	Q_0
	0	0
1	1	1
2	1	0
3	0	1
4	0	0

05. Ans: (c)

Sol: Assume $n = 2$

 

Outputs of counter is connected to inputs of decoder

Counter outputs		Decoder inputs		Decoder outputs			
Q_1	Q_0	a	b	d_3	d_2	d_1	d_0
0	0	0	0	0	0	0	1
0	1	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0

The overall circuit acts as 4-bit ring counter
 $n = 2$

$\therefore k = 2^2 = 4$, k-bit ring counter

06. Ans: (b)

Sol:

CLK	Serial in= $B \oplus C \oplus D$	A B C D
0		1 0 1 0
1	1 \rightarrow	1 1 0 1
2	0 \rightarrow	0 1 1 0
3	0 \rightarrow	0 0 1 1
4	0 \rightarrow	0 0 0 1
5	1 \rightarrow	1 0 0 0
6	0 \rightarrow	0 1 0 0
7	1 \rightarrow	1 0 1 0

\therefore After 7 clock pulses content of shift register become 1010 again

07. Ans: (b)

Sol:

J	K	Q	\bar{Q}_n	$T = (J + Q_n) (K + \bar{Q}_n)$	Q_{n+1}
0	0	0	1	$0.1 = 0$	0 } Q_n
0	0	1	0	$1.0 = 0$	
0	1	0	1	$0.1 = 0$	0 } 0
0	1	1	0	$1.1 = 1$	
1	0	0	1	$1.1 = 1$	1 } 1
1	0	1	0	$1.0 = 0$	
1	1	0	1	$1.1 = 1$	1 } \bar{Q}_n
1	1	1	0	$1.1 = 1$	



J \ KQ _n	00	01	11	10
0			1	
1	1		1	1


$$T = J \overline{Q_n} + KQ_n = (J + Q_n)(K + \overline{Q_n})$$

08. Ans: 1.5

Sol:

C/k	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Y = Q ₃ + Q ₅
0	0	1	0	1	0	0
1	0	0	1	0	1	1
2	1	0	0	1	0	0
3	0	1	0	0	1	1
4	1	0	1	0	0	1
5	0	1	0	1	0	0

 The waveform at OR gate output, Y is [A = +5V]



Average power

$$\begin{aligned}
 P &= \frac{V_{Ao}^2}{R} = \frac{1}{R} \left[\int_0^{T_1} y^2(t) dt \right] \\
 &= \frac{1}{RT_1} \left[\int_T^{2T} A^2 dt + \int_{3T}^{4T} A^2 dt \right] \\
 &= \frac{A^2}{RT_1} [(2T - T) + (4T - 3T)] \\
 &= \frac{A^2 \cdot 3T}{R(5T)} = \frac{5^2 \cdot 3}{10 \times 5} = 1.5 \text{ mW}
 \end{aligned}$$

09. Ans: (b)

Sol:

Present State	Next State		Output (Y)	
	X = 0	X = 1	X = 0	X = 1
A	A	E	0	0
B	C	A	1	0
C	B	A	1	0
D	A	B	0	1
E	A	C	0	1

Step (1):

By replacing state B as state C then state B, C are equal.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
B	B	A
D	A	B
E	A	B

Step (2):

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
D	A	B
E	A	B

State D, E are equal, remove state E and replace E with D in next state.



Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B
D	A	B

Finally reduced state table is

Reduced state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B

∴ 3 states are present in the reduced state table

10. Ans: (c)

Sol: State table for the given state diagram

State	Input	Output
S ₀	0	1
S ₀	1	0
S ₁	0	1
S ₁	1	0

Output is 1's complement of input.

11. Ans: (c)

Sol: In state (C), when XYZ = 111, then

Ambiguity occurs

Because, from state (C)

⇒ When X = 1, Z = 1

⇒ N.S is (A)

When Y = 1, Z = 1 ⇒ N.S is (B)

06. AD and DA Converters


01. Ans: (b)

Sol:

CLK	Counter			Decoder				V ₀
	Q ₂	Q ₁	Q ₀	D ₃	D ₂	D ₁	D ₀	
1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	1
3	0	1	0	0	0	1	0	2
4	0	1	1	0	0	1	1	3
5	1	0	0	1	0	0	0	8
6	1	0	1	1	0	0	1	9
7	1	1	0	1	0	1	0	10
8	1	1	1	1	0	1	1	11

02. Ans: (b)

Sol:

 

$$R_{\text{equ}} = (((((2R \parallel 2R) + R) \parallel 2R) + R) \parallel 2R) + R) \parallel 2R$$

$$R_{\text{equ}} = R = 10k\Omega$$

$$I = \frac{V_R}{R} = \frac{10V}{10k} = 1mA$$

$$\text{Current division at } \frac{I}{16}$$

$$= \frac{1 \times 10^{-3}}{16} = 62.5 \mu A$$

03. Ans: (c)

Sol: Net current at inverting terminal,

$$I_i = \frac{I}{4} + \frac{I}{16} = \frac{5I}{16}$$



$$V_0 = -I_i R = -\frac{5I}{16} \times 10k\Omega$$

$$= \frac{-5 \times 1 \times 10^{-3} \times 10 \times 10^3}{16} = -3.125V$$

04. Ans: (d)

Sol: Given that $V_{DAC} = \sum_{n=0}^3 2^{n-1} b_n$ Volts

$$V_{DAC} = 2^{-1}b_0 + 2^0b_1 + 2^1b_2 + 2^2b_3$$

$$\Rightarrow V_{DAC} = 0.5b_0 + b_1 + 2b_2 + 4b_3$$

Initially counter is in 0000 state

Up counter o/p	$V_{DAC}(V)$	o/p of comparator
$b_3 b_2 b_1 b_0$		
0 0 0 0	0	1
0 0 0 1	0.5	1
0 0 1 0	1	1
0 0 1 1	1.5	1
0 1 0 0	2	1
0 1 0 1	2.5	1
0 1 1 0	3	1
0 1 1 1	3.5	1
1 0 0 0	4	1
1 0 0 1	4.5	1
1 0 1 0	5	1
1 0 1 1	5.5	1
1 1 0 0	6	1
1 1 0 1	6.5	0

When $V_{DAC} = 6.5 V$, the o/p of comparator is '0'. At this instant, the clock pulses to the counter are stopped and the counter remains in 1101 state.

\therefore The stable reading of the LED display is 13.

05. Ans: (b)

Sol: The magnitude of error between V_{DAC} & V_{in} at steady state is $|V_{DAC} - V_{in}| = |6.5 - 6.2|$
 $= 0.3 V$

06. Ans: (a)

Sol: In Dual slope

$$ADC \Rightarrow V_{in} T_1 = V_R \cdot T_2$$

$$\Rightarrow V_{in} = \frac{V_R T_2}{T_1}$$

$$= \frac{100mV \times 370.2ms}{300ms}$$

DVM indicates = 123.4

07. Ans: (d)

Sol: Ex: $f_{in} = 1 kHz \rightarrow f_s = 2 kHz$

$$f_{in} = 25 kHz \leftarrow f_s = 50 kHz$$

$$1. \text{ Max conversion time} = 2^{N+1}T = 2^{11} \cdot 1 \mu s$$

$$= 2048 \mu s$$

$$2. \text{ Sampling period} = T_s \geq \text{maximum conversion time}$$

$$T_s \geq 2048 \mu s$$

$$3. \text{ Sampling rate } f_s = \frac{1}{T_s} \leq \frac{1}{2048 \times 10^{-6}}$$

$$f_s \leq 488 \quad f_s \leq 500 Hz$$

$$4. f_{in} = \frac{f_s}{2} = 250 Hz$$

08. Ans: (d)

Sol: In an ADC along with S-H circuit (sample and hold) circuit, to avoid error at output, voltage across capacitor should not drop by more than $\pm \Delta/2$, where Δ is step size.



Here, $\Delta = \frac{10-0}{(2^{10}-1)} = 9.775 \times 10^{-3} \text{ V}$

Hence $\frac{\Delta}{2} = 4.8875 \times 10^{-3} \text{ V}$

So conversion time (maximum) should be such that the drop across capacitor voltage must reach maximum value $\Delta/2$.

Hence, time taken for this

$$t = \frac{\Delta/2}{\text{droprate}} = \frac{4.8875 \times 10^{-3}}{10^{-4} \text{ V/msec}}$$

$$t \approx 49 \text{ msec}$$

07. Architecture, Pin Details of 8085 & Interfacing with 8085

01. Ans: (a)


Sol: chip select is an active low signal for $\overline{\text{chipselect}} = 0$; the inputs for NAND gate must be let us see all possible cases for $\overline{\text{chipselect}} = 0$ condition

A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	
0	0	0	0	0	0	X	X	
0	0	1	1	0	0	X	X	
0	1	0	1	0	0	X	X	
0	1	1	0	0	0	X	X	→ 60H (A ₁ A ₀ =00)
1	0	0	1	0	0	X	X	
1	0	1	0	0	0	X	X	
0	0	0	0	1	1	X	X	
0	0	1	1	1	1	X	X	
0	1	0	1	0	0	X	X	
0	1	1	0	0	0	X	X	→ 63H (A ₁ A ₀ =11)
1	0	0	1	0	0	X	X	
1	0	0	0	0	0	X	X	

The only option that suits here is option(a)

A₀ & A₁ are used for line selection

A₂ to A₇ are used for chip selection

 

∴ Address space is 60H to 63H

A₀ to A₁₁ are used for line selection

A₁₂ to A₁₅ are used for chip selection

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	=E000H
1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	=EFFFH

02. Ans: (d)

- Sol:**
- Both the chips have active high chip select inputs.
 - Chip 1 is selected when A₈ = 1, A₉ = 0
 - Chip 2 is selected when A₈ = 0, A₉ = 1
 - Chips are not selected for combination of 00 & 11 of A₈ & A₉
 - Upon observing A₈ & A₉ of given address Ranges, F800 to F9FF is not represented

03. Ans: (d)

Sol: The I/O device is interfaced using “Memory Mapped I/O” technique.



The address of the Input device is

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
1	1	1	1	1	0	0	0	1	1	1	1	1	0	0	0

=F8F8_H

The Instruction for correct data transfer is
= LDA F8F8H

04. Ans: (b)

- Out put 2 of 3×8 Decoder is used for selecting the output port. ∴ Select code is 010

$$\begin{array}{ccccccc} \underline{A_{15}} & \underline{A_{14}} & \underline{A_{13}} & \underline{A_{12}} & \underline{A_{11}} & \underline{A_{10}} & \text{---} & \underline{A_0} \\ 0 & 1 & 0 & 1 & 0 & 0 & \text{---} & 0 \\ \Rightarrow & 5000\text{H} \end{array}$$

- This mapping is memory mapped I/O


05. Ans: (d)

Sol:

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉ ----	A ₀	
0	0	0	0	1	0	0	----	0 =0800H
			⋮					⋮
0	0	0	0	1	0	1	----	1 =0BFFH
			⋮					⋮
0	0	0	1	1	0	0	----	0 =1800H
			⋮					⋮
0	0	0	1	1	0	1	----	1 =1BFFH
			⋮					⋮
0	0	1	0	1	0	0	----	0 =2800H
			⋮					⋮
0	0	1	0	1	0	1	----	1 =2BFFH
			⋮					⋮
0	0	1	1	1	0	0	----	0 =3800H
			⋮					⋮
0	0	1	1	1	0	1	----	1 =3BFFH

06. Ans: (a)

Sol: Address Range given is

 

	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
1000H →	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
2FFFH →	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1

To provide $\overline{\text{CS}}$ as low, The condition is


$$A_{15} = A_{14} = 0 \text{ and } A_{13} A_{12} = 01 \text{ (or) } (10)$$

i.e $A_{15} = A_{14} = 0$ and $A_{13} A_{12}$ shouldn't be 00, 11.

$$\text{Thus it is } A_{15} + A_{14} + [A_{13}A_{12} + \overline{A_{13}}\overline{A_{12}}]$$

07. Ans: (a)

Sol:

 

A_{15}, A_{14} are used for chip selection

A_{13}, A_{12}, A_{11} are used for input of decoder

A ₁₅ A ₁₄	A ₁₃ A ₁₂ A ₁₁	A ₁₀ ----- A ₀
Enable of decoder	Input of decoder	Address of chip

Size of each memory block = $2^{11} = 2K$

08. Instruction set of 8085 & Programming with 8085

01. Ans: (c)

Sol:

6010H : LXI H,8A79H ; (HL) = 8A79H

6013H : MOV A, L ; (A) \leftarrow (L) = 79

6014H : ADD H ; (A) = 0111 1001

+

$$; (H) = 1000 \ 1010$$
$$\overline{; (A)} = 0000 \ 0011$$

CY = 1, AC = 1

6015H : DAA ; 66 Added to (A)
since CY=1 &

AC=1

; (A) = 69H

6016H : MOV H,A ; (H) \leftarrow (A) =69H

6017H : PCHL ; (PC) \leftarrow (HL) = 6979H

02. Ans: (c)

Sol: 0100H : LXI SP, 00FFH ; (SP) = 00FFH

0103H : LXI H, 0107 H ; (HL) = 0107H

0106H : MVI A, 20H ; (A) = 20H

0108H: SUB M; (A) \leftarrow (A)-(0107)

$$; (0107) = 20H$$

```
; (A) = 00H
```

The contents of Accumulator is 00H

03. Ans: (c)

Sol: SUB1 : MVI A, 00H A ← 00H

CALL SUB2 → program will shifted to SUB 2 address location

SUB 2 : INR $A \rightarrow \overline{A}$

01H

RET → returned to the main program

∴ The contents of Accumulator after execution of the above SUB2 is 02H

04. Ans: (c)

Sol: The loop will be executed until the value in register equals to zero, then,

Execution time

$$=9(7T+4T+4T+10T)+(7T+4T+4T+7T)+7T$$
$$= 254T$$

05. Ans: (d)

Sol: H=255 : L = 255, 254, 253, ---0

H=254 : L = 0, 255, 254, -----0



H=1 : L = 0,255,254,253,---0

H=0 : —

→ In first iteration (with H=255), the value in L is decremented from 255 to 0 i.e., 255 times

→ In further remaining 254 iterations, the value in L is decremented from 0 to 0 i.e., 256 times

∴ 'DCRL' instruction gets executed for

⇒ [255 + (254 × 256)]

⇒ 65279 times

06. Ans: (a)

Sol: "STA 1234H" is a 3-Byte Instruction and it requires 4 Machine cycles (Opcode fetch, Operand1 Read, Operand2 Read, Memory write). The Higher order Address ($A_{15} - A_8$) sent in 4 machine cycles is as follows

Given "STA 1234" is stored at 1FFE_H

i.e., Address Instruction

1FFE, 1FFF, 2000 : STA 1234H

Machine cycle	Address ($A_{15}-A_0$)	Higher order address ($A_{15}-A_8$)
1. Opcode fetch	1FFE _H	1F _H
2. Operand1 Read	1FFF _H	1F _H
3. Operand2 Read	2000 _H	20 _H
4. Memory Write	1234 _H	12 _H

i.e. Higher order Address sent on $A_{15}-A_8$ for

4 Machine Cycles are 1F_H, 1F_H, 20_H, 12_H.

07. Ans: (d)

Sol: The operation SBI BE_H indicates A-BE → A where A indicates accumulator

Thus the result of the subtraction operation is stored in the accumulator and the contents of accumulator are changed.

08. Ans: (c)

Sol: If the content in register B is to be multiplied with the content in register C, the contents of register B is added to the accumulator (initial value of accumulator is 0) for C times.