 




ELECTRONICS & COMMUNICATION ENGINEERING



GATE I PSUs

DIGITAL CIRCUITS & MICROPROCESSORS

Volume - I : Study Material with Classroom Practice Questions

Study Material with Classroom Practice solutions*To****Digital Circuits & Microprocessors******CONTENTS***

<i>Chapter No.</i>	<i>Name of the Chapter</i>	<i>Page No.</i>
01	Number Systems	03 – 04
02	Logic Gates and Boolean Algebra	05 – 06
03	K – Maps	07 – 07
04	Combinational Circuits	08 – 10
05	Sequential Circuits	11 – 13
06	Logic Gate Families	14 – 14
07	Semiconductor Memories	15 – 16
08	A/D & D/A Converters	17 – 18
09	Architecture, Pin Details of 8085 & Interfacing with 8085	19 – 20
10	Instruction Set of 8085 & Programming with 8085	21 – 22

Chapter 1 Number Systems

Class Room Practice Solutions

01. Ans: (d)

Sol: $135_x + 144_x = 323_x$

$$(1 \times x^2 + 3 \times x^1 + 5 \times x^0) + (1 \times x^2 + 4 \times x^1 + 4 \times x^0) = 3x^2 + 2x^1 + 3x^0$$

$$\Rightarrow x^2 + 3x + 5 + x^2 + 4x + 4 = 3x^2 + 2x + 3$$

$$x^2 - 5x - 6 = 0$$

$$(x-6)(x+1) = 0 \quad (\text{Base cannot be negative})$$

Hence $x = 6$.

(OR)

As per the given number x must be greater than 5. Let consider $x = 6$

$$(135)_6 = (59)_{10}$$

$$(144)_6 = (64)_{10}$$

$$(323)_6 = (123)_{10}$$

$$(59)_{10} + (64)_{10} = (123)_{10}$$

So that $x = 6$

02. Ans: (a)

Sol: 8-bit representation of $+127_{10}$

$$= 01111111_{(2)}$$

1's complement representation of

$$-127 = 10000000.$$

2's complement representation of

$$-127 = 10000001.$$

No. of 1's in 2's complement of

$$-127 = m = 2$$

No. of 1's in 1's complement of

$$-127 = n = 1$$

$$\therefore m : n = 2 : 1$$

03. Ans: (c)

Sol: In 2's complement representation the sign bit can be extended towards left any number of times without changing the value. In given number the sign bit is 'X₃', hence it can be extended left any no. of times.

04. Ans: (c)

05. Ans: 5

Sol: Symbols used in this equation are 0,1,2,3
Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0)(x+3x^0+x^{-1})$$

$$3x^2 + x + 2 = (2x) \left(x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$x(x-5) = 0$$

$$x = 0(\text{or}) x = 5$$

x must be $x > 3$, So $x = 5$

06. Ans: 3 possible solutions

Sol: $123_5 = x8_y$

$$1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0 = x.y^1 + 8 \times y^0$$

$$25 + 10 + 3 = xy + 8$$

$$\therefore xy = 30$$

Possible solutions:

i. $x = 1, y = 30$

ii. $x = 2, y = 15$

iii. $x = 3, y = 10$

3 possible solutions



07. Ans: (1)

Sol: The range (or) distinct values

For 2's complement $\Rightarrow -(2^{n-1})$ to $+(2^{n-1}-1)$

For sign magnitude

$\Rightarrow -(2^{n-1}-1)$ to $+(2^{n-1}-1)$

Let $n = 2 \Rightarrow$ in 2's complement

$-(2^{2-1})$ to $+(2^{2-1}-1)$

-2 to $+1 \Rightarrow -2, -1, 0, +1 \Rightarrow x = 4$

$n = 2$ in sign magnitude $\Rightarrow -1$ to $+1 \Rightarrow y = 3$

$x - y = 1$

Class Room Practice Solutions

01. Ans: (c)

Sol: Given 2's complement numbers of sign bits are x & y. z is the sign bit obtained by adding above two numbers. \therefore Overflow is indicated by $= \bar{x}\bar{y}z + x y \bar{z}$

Examples

1. A = +7 0111
B = +7 0111
14 1110 $\Rightarrow \bar{x}\bar{y}z$
2. A = +7 0111
B = +5 0101
12 1100 $\Rightarrow \bar{x}\bar{y}z$
3. A = -7 1001
B = -7 1001
-14 10010 $\Rightarrow x y \bar{z}$
4. A = -7 0111
B = -5 0101
-12 10100 $\Rightarrow x y \bar{z}$

02. Ans: (b)

Sol: Truth table of XOR

A	B	o/p
0	0	0
0	1	1
1	0	1
1	1	0

Stage 1:

Given one i/p = 1 Always.

1 X o/p

1 0 1 = \bar{X}
1 1 0 = \bar{X}

For First XOR gate o/p = \bar{X}

Stage 2:

\bar{X}	X	o/p
0	1	1
1	0	1

For second XOR gate o/p = 1.


Similarly for third XOR gate o/p = \bar{X} & for fourth o/p = 1

For Even number of XOR gates o/p = 1

For 20 XOR gates cascaded o/p = 1.

03. Ans: (b)

Sol:

 



04. Ans: (c)

Sol: $f = f_1 f_2 + f_3$

05. Ans: (d)

Sol:

 

 

06. Ans: (c)

Sol: For all cases option A, B, D not satisfy.

07. Ans: (b)

Sol: $M(a,b,c) = ab + bc + ca$

$$\overline{M(a,b,c)} = \overline{bc} + \overline{ab} + \overline{ac}$$

$$M(a, b, \overline{c}) = ab + b\overline{c} + \overline{c}a$$

$$\begin{aligned} M(\overline{M(a,b,c)}, M(a,b,\overline{c}), c) &= (\overline{bc} + \overline{ab} + \overline{ac})(ab + b\overline{c} + ac) \\ &\quad + (ab + b\overline{c} + ca)c + (\overline{bc} + \overline{ab} + \overline{ac})c \end{aligned}$$

$$= (\overline{bc} + \overline{ab} + \overline{ac})(ab + b\overline{c} + ac) + (\overline{bc} + \overline{ab} + \overline{ac})c + abc$$

$$= ab\overline{c} + \overline{ab}c + abc + \overline{ab}c$$

$$= \overline{c}[a\overline{b} + \overline{a}b] + c[ab + \overline{a}b]$$


$$= \sum m(1, 2, 4, 7)$$

$$\therefore M(x, y, z) = a \oplus b \oplus c$$

$$\text{Where } x = \overline{M(a,b,c)}, y = M(a,b,\overline{c}), z = c$$

08. Ans: 40

Sol:

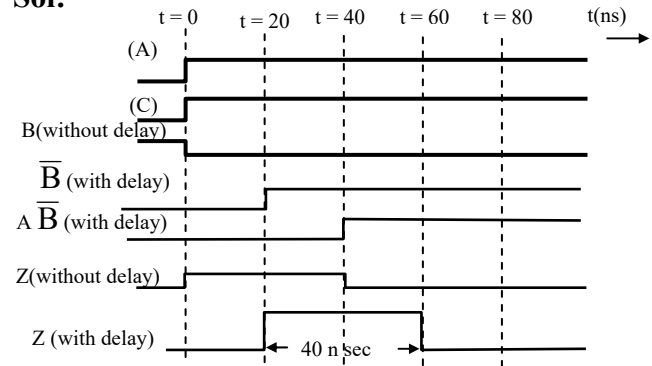

$\therefore Z$ is 1 for 40 nsec

09. Ans: (c)

Sol: Logic gates $\overline{X} + Y = \overline{X\overline{Y}} = \overline{XY_1}$

$$\text{Where } Y_1 = \overline{Y}$$


It is a NAND gate and thus the gate is

‘Universal gate’.

Class Room Practice Solutions


01. Ans: (b)

Sol:

 



02. Ans: (b)

Sol:

 

03.


Sol:

  SOP: $x y + y w$ POS: $y(x + w)$

04. Ans: (a)

05. Ans: (c)

Sol:

 


06. Ans: 1

Sol: After minimization $= \overline{(\bar{A} + \bar{B} + \bar{C} + \bar{D})}$
 $= ABCD$

 \therefore only one minterm.

07. Ans: 3

 Sol: $\bar{w}\bar{z} + \bar{w}x\bar{y} + \bar{x}y\bar{z}$ 

Class Room Practice Solutions

01. Ans: (d)

Sol: Let the output of first MUX is “F₁”

$$F_1 = AI_0 + AI_1$$

Where A is selection line, I₀, I₁ = MUX Inputs

$$F_1 = \bar{S}_1 \cdot W + S_1 \cdot \bar{W} = S_1 \oplus W$$

Output of second MUX is

$$F = \bar{A} \cdot I_0 + A \cdot I_1$$

$$F = \bar{S}_2 \cdot F_1 + S_2 \cdot \bar{F}_1$$

$$F = S_2 \oplus F_1$$


$$\text{But } F_1 = S_1 \oplus W$$

$$F = S_2 \oplus S_1 \oplus W$$

$$\text{i.e., } F = W \oplus S_1 \oplus S_2$$


02. Ans: 50

Sol:

 

Initially all the output values are '0', at $t = 0$, the inputs to the 4-bit adder are changed to $X_3X_2X_1X_0 = 1100$, $Y_3Y_2Y_1Y_0 = 0100$

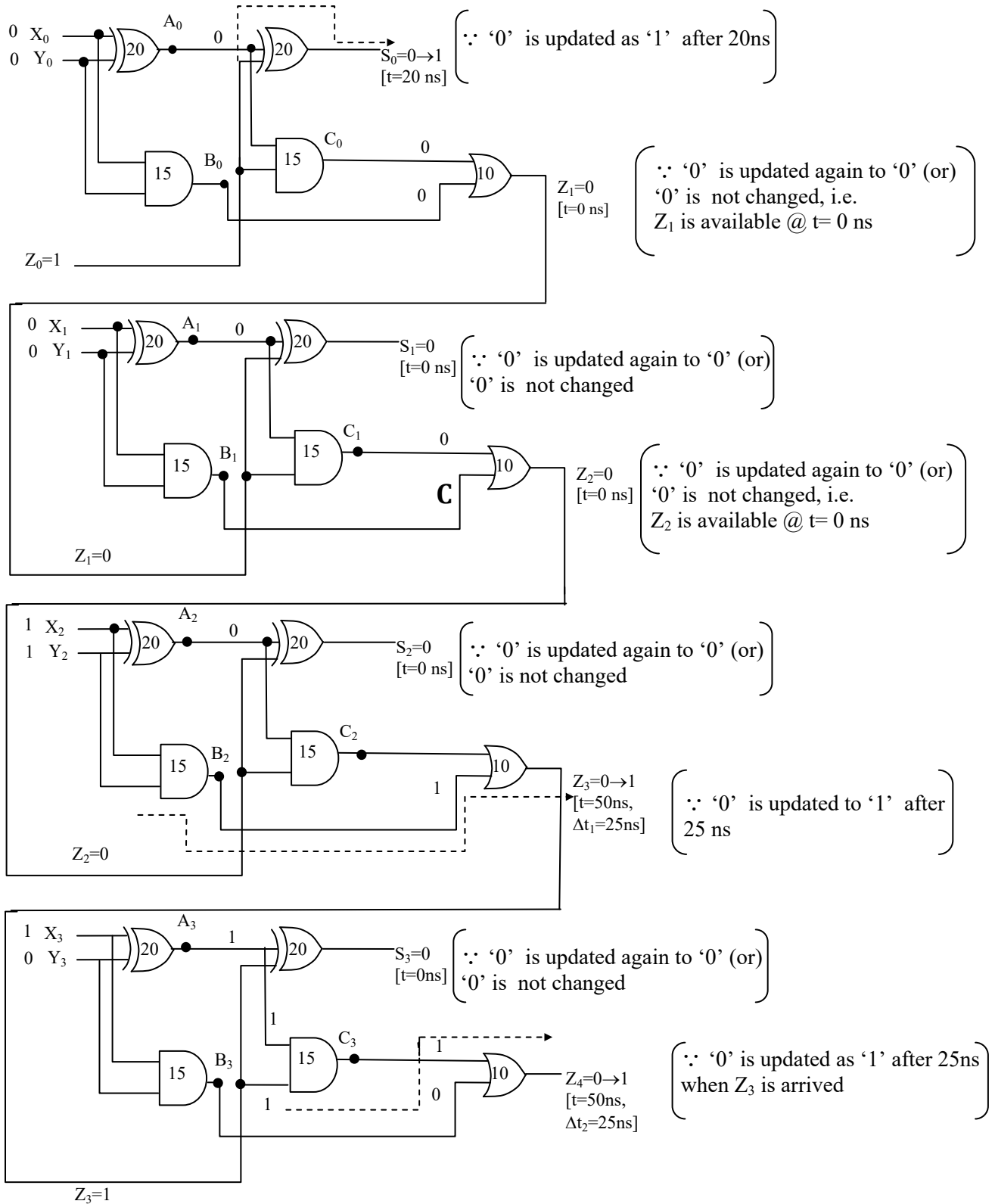----- indicates critical path delay to get the output



Total time taken = $\Delta t_1 + \Delta t_2 = 50\text{ ns}$

i.e. critical time (or) maximum time is taken for Z_4 to get final output as '1'



03. Ans: (a)

Sol: The given circuit is binary parallel adder/subtractor circuit. It performs $A+B$, $A-B$ but not $A + 1$ operations.

K	C_0	Operation
0	0	$A+B$ (addition)
0	1	$A+B+1$ (addition with carry)
1	0	$A+\overline{B}$ (1's complement addition)
1	1	$A+\overline{B}+1$ (2's complement subtraction)

04. Ans: (d)

Sol: It is expansion of 2:4 decoders to 1:8 demultiplexer A_1, A_0 must be connected to S_1, S_0 i.e.,
 $R = S_0, S = S_1$

Q must be connected to S_2 i.e., $Q = S_2$

P is serial input must be connected to D_{in}

05. Ans: 6

Sol: $T = 0 \rightarrow \underset{2ns}{\text{NOR}} \rightarrow \underset{1.5ns}{\text{MUX 1}} \rightarrow \underset{1.5ns}{\text{MUX 2}}$

Delay = $2ns + 1.5ns + 1.5ns = 5ns$

$T = 1 \rightarrow \underset{1ns}{\text{NOT}} \rightarrow \underset{1.5ns}{\text{MUX 1}} \rightarrow \underset{2ns}{\text{NOR}} \rightarrow \underset{1.5ns}{\text{MUX 2}}$

Delay = $1ns + 1.5ns + 2ns + 1.5ns = 6ns$

Hence, the maximum delay of the circuit is 6ns


06. Ans: -1

Sol: When all bits in 'B' register is '1', then only it gives highest delay.

\therefore '-1' in 8 bit notation of 2's complement is 1111 1111

Class Room Practice Solutions

01. Ans: (c)

 Sol: Given Clk, X_1 , X_2 Output of First D-FF is Q_1 Output of Second D-FF is Q_2 

02. Ans: 4

Sol: In the given first loop of states, zero has repeated 3 times. So, minimum 4 number of Flip-flops are needed.

03. Ans: 7

Sol: The counter is cleared when

$$Q_D Q_C Q_B Q_A = 0110$$

Clk	Q_D	Q_C	Q_B	Q_A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	0	0	0

As the clear input is given to be synchronous so it waits upto the next clock pulse to clear the counter & hence the counter get's cleared during the 7th clock pulse.


$$\therefore \text{mod of counter} = 7$$

04. Ans: (b)

Sol: The given circuit is a mod 4 ripple down counter. Q_1 is coming to 1 after the delay of $2\Delta t$.

CLK	Q_1	Q_0
	0	0
1	1	1
2	1	0
3	0	1
4	0	0

05. Ans: (c)

 Sol: Assume $n = 2$ 

Outputs of counter is connected to inputs of decoder

Counter outputs		Decoder inputs		Decoder outputs			
Q_1	Q_0	a	b	d_3	d_2	d_1	d_0
0	0	0	0	0	0	0	1
0	1	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0

The overall circuit acts as 4-bit ring counter
 $n = 2$

$$\therefore k = 2^2 = 4, \text{ k-bit ring counter}$$



06. Ans: (b)

Sol:

CLK	Serial in= $B \oplus C \oplus D$	A B C D
0		1 0 1 0
1	1 \longrightarrow	1 1 0 1
2	0 \longrightarrow	0 1 1 0
3	0 \longrightarrow	0 0 1 1
4	0 \longrightarrow	0 0 0 1
5	1 \longrightarrow	1 0 0 0
6	0 \longrightarrow	0 1 0 0
7	1 \longrightarrow	1 0 1 0

0	1	0	1	$0.1 = 0$	$0 \}$
0	1	1	0	$1.1 = 1$	$0 \}$ 0
1	0	0	1	$1.1 = 1$	$1 \}$
1	0	1	0	$1.0 = 0$	$1 \}$ 1
1	1	0	1	$1.1 = 1$	$1 \}$
1	1	1	0	$1.1 = 1$	$0 \}$ \bar{Q}_n

J \ K Q_n	00	01	11	10
0			1	
1	1		1	1

07. Ans: (b)

Sol:

J	K	Q	\bar{Q}_n	$T = (J + Q_n)(K + \bar{Q}_n)$	Q_{n+1}
0	0	0	1	$0.1 = 0$	$0 \}$
0	0	1	0	$1.0 = 0$	$1 \}$ Q_n


$$T = J \bar{Q}_n + K Q_n = (J + Q_n)(K + \bar{Q}_n)$$

08. Ans: 1.5

Sol:

C/k	Q_1	Q_2	Q_3	Q_4	Q_5	$Y = Q_3 + Q_5$
0	0	1	0	1	0	0
1	0	0	1	0	1	1
2	1	0	0	1	0	0
3	0	1	0	0	1	1
4	1	0	1	0	0	1
5	0	1	0	1	0	0

 The waveform at OR gate output, Y is $[A = +5V]$



Average power

$$\begin{aligned}
 P &= \frac{V_{Ao}^2}{R} = \frac{1}{R} \left[\lim_{T_1 \rightarrow \infty} \frac{1}{T_1} \int_0^{T_1} y^2(t) dt \right] = \frac{1}{RT_1} \left[\int_T^{2T} A^2 dt + \int_{3T}^{4T} A^2 dt + \int_{5T}^{6T} A^2 dt \right] \\
 &= \frac{A^2}{RT_1} [(2T - T) + (5T - 3T)] = \frac{A^2 \cdot 3T}{R(5T)} = \frac{5^2 \cdot 3}{10 \times 5} = 1.5 \text{ mw}
 \end{aligned}$$



09. Ans: (b)

Sol:

Present State	Next State		Output (Y)	
	X = 0	X = 1	X = 0	X = 1
A	A	E	0	0
B	C	A	1	0
C	B	A	1	0
D	A	B	0	1
E	A	C	0	1

Step (1):

By replacing state B as state C then state B, C are equal.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
B	B	A
D	A	B
E	A	B

Step (2):

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
D	A	B
E	A	B

State D, E are equal, remove state E and replace E with D in next state.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B
D	A	B

Finally reduced state table is

Reduced state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B

∴ 3 states are present in the reduced state table

10. Ans: (c)

Sol: State table for the given state diagram

State	Input	Output
S ₀	0	1
S ₀	1	0
S ₁	0	1
S ₁	1	0

Output is 1's complement of input.

11. Ans: (c)

Sol: In state (C), when XYZ = 111, then Ambiguity occurs

Because, from state (C)

⇒ When X = 1, Z = 1

⇒ N.S is (A)

When Y = 1, Z = 1 ⇒ N.S is (B)

6

Logic Gate Families

Class Room Practice Solutions

01. Ans: (b)

Sol: $V_{OH}(\text{min})$:-

(High level output voltage)

The minimum voltage level at a Logic circuit output in the logic '1' state under defined load conditions.

$V_{OL(max)}$:-

(Low level output voltage)

The maximum voltage level at a logic circuit output in the Logical '0' state under defined load conditions.

V_{IL}(max):- (Low level input voltage)

The maximum voltage level required for a logic '0' at an input. Any voltage above this level will not be accepted as a Low by the logic circuit.

V_{IH}(min) :- (High level Input voltage)

The minimum voltage level required for logic '1' at an input. Any voltage below this level will not be accepted as a HIGH by the Logic circuit.

 
 


Fig: currents and voltages in the two logic states.

02. Ans: (b)

Sol: Fan out is minimum in DTL

(High Fan-out = CMOS)

Power consumption is minimum in CMOS.
Propagation delay is minimum in ECL
(fastest = ECL)

03. Ans: (b)

04. Ans: (d)

05. Ans: (b)

Sol: As per the description of the question, when the transistor Q_1 and diode both are OFF then only output $z = 1$.

X	Y	Z	Remarks
0	0	0	Q ₁ is OFF, Diode is ON
0	1	1	Q ₁ is OFF, Diode is OFF
1	0	0	Q ₁ is ON, Diode is OFF
1	1	0	Q ₁ is ON, Diode is OFF

Hence $Z = \overline{X}Y$

Chapter 7 Semiconductor Memories

Class Room Practice Solutions

01. Ans: (b)

Sol: Square of a 4 – bit number can be at most 8 – bit number.

$$\{ \text{i.e } (1111)_2 = (15)_{10}$$

$$[(15)_{10}]^2 = (225)_{10} \}$$

Therefore ROM requires 8 data lines.

Data is with size of 4 bits

ROM must require 4 address lines and 8 data lines

$$\text{ROM} = 2^n \times m$$

$$n = \text{inputs(address lines),}$$

$$m = \text{output lines}$$

$$n = 4, m = 8.$$

02. Ans: (a)

Sol: ROM is used to design a combinational circuit. The number of address lines of the ROM is equal to the number of input variables in the truth table.

ROM is represented as $2^n \times m$ where 2^n inputs and m output lines.

[Where n = address bits]

03. Ans: (b)


Sol:

8	4	2	1	2	4	2	1	2421 Outputs
i/p s				o/p s				
X_3	X_2	X_1	X_0	Y_3	Y_2	Y_1	Y_0	
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	0	2
0	0	1	1	0	0	1	1	3
0	1	0	0	0	1	0	0	4
0	1	0	1	1	0	1	1	5
0	1	1	0	1	1	0	0	6
0	1	1	1	1	1	0	1	7
1	0	0	0	1	1	1	0	8
1	0	0	1	1	1	1	1	9
1	0	1	0	x	x	x	x	
1	0	1	1	x	x	x	x	
1	1	0	0	x	x	x	x	
1	1	0	1	x	x	x	x	
1	1	1	0	x	x	x	x	
1	1	1	1	x	x	x	x	

The outputs are in 2 4 2 1 BCD number

04. Ans: (c)

Sol:

 


At the rising edge of the First clock pulse the content of location $(0110)_2 = 6 \Rightarrow 1010$



appears on the data bus, at the rising of the second clock pulse the content of location $(1010)_2 = 10_2 \Rightarrow 1000$ appears on the data bus.

05. Ans: (b)


Sol: 1-bit SRAM memory cell is

 

In 2 Inverters, output of the 1st Inverter is connected to Gate Input of 2nd Inverter and vice versa.

Class Room Practice Solutions**01. Ans: (b)****Sol:**

CLK	Counter			Decoder				V ₀
	Q ₂	Q ₁	Q ₀	D ₃	D ₂	D ₁	D ₀	
1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	1
3	0	1	0	0	0	1	0	2
4	0	1	1	0	0	1	1	3
5	1	0	0	1	0	0	0	8
6	1	0	1	1	0	0	1	9
7	1	1	0	1	0	1	0	10
8	1	1	1	1	0	1	1	11

 02. Ans: (b)**Sol:**

$$R_{\text{equ}} = (((((2R \parallel 2R) + R) \parallel 2R) + R) \parallel 2R) + R$$

$$R_{\text{equ}} = R = 10\text{k}\Omega.$$

$$I = \frac{V_R}{R} = \frac{10\text{V}}{10\text{k}} = 1\text{mA}.$$

$$\begin{aligned} \text{Current division at } \frac{I}{16} \\ = \frac{1 \times 10^{-3}}{16} = 62.5 \mu\text{A} \end{aligned}$$

03. Ans: (c)**Sol:** Net current at inverting terminal,

$$I_i = \frac{I}{4} + \frac{I}{16} = \frac{5I}{16}$$

$$\begin{aligned} V_0 &= -I_i R = -\frac{5I}{16} \times 10\text{k}\Omega \\ &= \frac{-5 \times 1 \times 10^{-3} \times 10 \times 10^3}{16} = -3.125\text{V} \end{aligned}$$

04. Ans: (d)**Sol:** Given that $V_{\text{DAC}} = \sum_{n=0}^3 2^{n-1} b_n$ Volts

$$V_{\text{DAC}} = 2^{-1}b_0 + 2^0b_1 + 2^1b_2 + 2^2b_3$$

$$\Rightarrow V_{\text{DAC}} = 0.5b_0 + b_1 + 2b_2 + 4b_3$$

Initially counter is in 0000 state

Up counter o/p				V _{DAC} (V)	o/p of comparator
b ₃	b ₂	b ₁	b ₀		
0	0	0	0	0	1
0	0	0	1	0.5	1
0	0	1	0	1	1
0	0	1	1	1.5	1
0	1	0	0	2	1
0	1	0	1	2.5	1
0	1	1	0	3	1
0	1	1	1	3.5	1
1	0	0	0	4	1
1	0	0	1	4.5	1
1	0	1	0	5	1
1	0	1	1	5.5	1
1	1	0	0	6	1
1	1	0	1	6.5	0

When $V_{\text{DAC}} = 6.5\text{ V}$, the o/p of comparator is '0'. At this instant, the clock pulses to the counter are stopped and the counter remains in 1101 state.

\therefore The stable reading of the LED display is 13.



05. Ans: (b)

Sol: The magnitude of error between V_{DAC} & V_{in} at steady state is $|V_{DAC} - V_{in}| = |6.5 - 6.2|$
 $= 0.3 \text{ V}$

06. Ans: (a)

Sol: In Dual slope

$$ADC \Rightarrow V_{in} T_1 = V_R \cdot T_2$$

$$\Rightarrow V_{in} = \frac{V_R T_2}{T_1}$$

$$= \frac{100 \text{ mV} \times 370.2 \text{ ms}}{300 \text{ ms}}$$

DVM indicates = 123.4

07. Ans: (d)

Sol: Ex: $f_{in} = 1 \text{ kHz} \rightarrow f_s = 2 \text{ kHz}$

$$f_{in} = 25 \text{ kHz} \leftarrow f_s = 50 \text{ kHz}$$

$$1. \text{ Max conversion time} = 2^{N+1} T = 2^{11} \cdot 1 \mu\text{s} \\ = 2048 \mu\text{s}$$

$$2. \text{ Sampling period} = T_s \geq \text{maximum conversion time}$$

$$T_s \geq 2048 \mu\text{s}$$

$$3. \text{ Sampling rate } f_s = \frac{1}{T_s} \leq \frac{1}{2048 \times 10^{-6}}$$


$$f_s \leq 488 \quad f_s \leq 500 \text{ Hz}$$

$$4. f_{in} = \frac{f_s}{2} = 250 \text{ Hz}$$

Class Room Practice Solutions

 01. Ans: (a)

Sol: A_0 & A_1 are used for line selection
 A_2 to A_7 are used for chip selection



\therefore Address space is 60H to 63H
 A_0 to A_{11} are used for line selection
 A_{12} to A_{15} are used for chip selection

A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	-----	A_0	
1	1	1	0	0	-----	0	=E000H
⋮	⋮	⋮	⋮	⋮	-----	⋮	
1	1	1	0	1	-----	1	=EFFFH

02. Ans: (d)

Sol:

- Both the chips have active high chip select inputs.
- Chip 1 is selected when $A_8 = 1$, $A_9 = 0$
 Chip 2 is selected when $A_8 = 0$, $A_9 = 1$
- Chips are not selected for combination of 00 & 11 of A_8 & A_9
- Upon observing A_8 & A_9 of given address Ranges, F800 to F9FF is not represented

03. Ans: (d)

Sol: The I/O device is interfaced using “Memory Mapped I/O” technique.
 The address of the Input device is

A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	A_9	A_8	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0	
1	1	1	1	1	0	0	0	1	1	1	1	1	0	0	0	=F8F8H

The Instruction for correct data transfer is
 = LDA F8F8H

04. Ans: (b)

Sol:

- Output 2 of 3×8 Decoder is used for selecting the output port. \therefore Select code is 010

A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	---	A_0	
0	1	0	1	0	0	---	0	\Rightarrow 5000H

- This mapping is memory mapped I/O

05. Ans: (d)


Sol:

A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	A_9	---	A_0	
0	0	0	0	1	0	0	---	0	=0800H
			⋮			⋮		⋮	
0	0	0	0	1	0	1	---	1	=0BFFH
0	0	0	1	1	0	0	---	0	=1800H
			⋮			⋮		⋮	
0	0	0	1	1	0	1	---	1	=1BFFH
0	0	1	0	1	0	0	---	0	=2800H
		⋮				⋮		⋮	
0	0	1	0	1	0	1	---	1	=2BFFH
0	0	1	1	1	0	0	---	0	=3800H
		⋮				⋮		⋮	
0	0	1	1	1	0	1	---	1	=3BFFH



06. Ans: (a)

Sol: Address Range given is

 

	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
1000H →	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
2FFFH →	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1

To provide \overline{cs} as low, The condition is


$A_{15} = A_{14} = 0$ and $A_{13} A_{12} = 01$ (or) (10)

i.e $A_{15} = A_{14} = 0$ and $A_{13} A_{12}$ shouldn't be 00, 11.

Thus it is $A_{15} + A_{14} + [A_{13}A_{12} + \overline{A_{13}}\overline{A_{12}}]$

07. Ans: (a)

Sol:

 

A_{15}, A_{14} are used for chip selection

A_{13}, A_{12}, A_{11} are used for input of decoder

A ₁₅ A ₁₄	A ₁₃ A ₁₂ A ₁₁	A ₁₀ ----- A ₀
Enable of decoder	Input of decoder	Address of chip

Size of each memory block = $2^{11} = 2K$

Class Room Practice Solutions

01. Ans: (c)

Sol:

6010H : LXI H,8A79H ; (HL) = 8A79H
6013H : MOV A, L ; (A) ← (L) = 79
6014H : ADD H ; (A) = 0111 1001
+
; (H) = 1000 1010
; (A) = 0000 0011
CY = 1, AC = 1
6015H : DAA ; 66 Added to (A)
since CY=1 &
AC=1
; (A) = 69H
6016H : MOV H,A ; (H) ← (A) = 69H
6017H : PCHL ; (PC) ← (HL) = 6979H

02. Ans: (c)

Sol: 0100H : LXI SP, 00FFH ; (SP) = 00FFH
0103H : LXI H, 0107 H ; (HL) = 0107H
0106H : MVI A, 20H ; (A) = 20H
0108H : SUB M ; (A) ← (A) - (0107)
; (0107) = 20H
; (A) = 00H
The contents of Accumulator is 00H

03. Ans: (c)

Sol: SUB1 : MVI A, 00H A ← 00H
CALL SUB2 → program will shifted to
SUB 2 address location
SUB 2 : INR A → A

01H

RET → returned to the main program

∴ The contents of Accumulator after execution of the above SUB2 is 02H

04. Ans: (c)

Sol: The loop will be executed until the value in register equals to zero, then,

Execution time

$$= 9(7T+4T+4T+10T) + (7T+4T+4T+7T) + 7T$$
$$= 254T$$

05. Ans: (d)

Sol: H=255 : L = 255, 254, 253, ---0

H=254 : L = 0, 255, 254, -----0

H=1 : L = 0,255,254,253,---0

H=0 : —

→ In first iteration (with H=255), the value in L is decremented from 255 to 0 i.e., 255 times

→ In further remaining 254 iterations, the value in L is decremented from 0 to 0 i.e., 256 times

\therefore 'DCRL' instruction gets executed for

$$\Rightarrow [255 + (254 \times 256)]$$

$\Rightarrow 65279$ times

06. Ans: (a)

Sol: “STA 1234H” is a 3-Byte Instruction and it requires 4 Machine cycles (Opcode fetch, Operand1 Read, Operand2 Read, Memory write). The Higher order Address ($A_{15} - A_8$) sent in 4 machine cycles is as follows

Given “STA 1234” is stored at 1FFEh



i.e., Address Instruction

1FFE, 1FFF, 2000 : STA 1234H

Machine cycle	Address (A ₁₅ -A ₀)	Higher order address (A ₁₅ -A ₈)
1. Opcode fetch	1FFE _H	1F _H
2. Operand1 Read	1FFF _H	1F _H
3. Operand2 Read	2000 _H	20 _H
4. Memory Write	1234 _H	12 _H

i.e. Higher order Address sent on A₁₅-A₈ for
4 Machine Cycles are 1F_H, 1F_H, 20_H, 12_H.

07. Ans: (d)

Sol: The operation SBI BE_H indicates A-BE → A where A indicates accumulator
Thus the result of the subtraction operation is stored in the accumulator and the contents of accumulator are changed.

08. Ans: (c)

Sol: If the content in register B is to be multiplied with the content in register C, the contents of register B is added to the accumulator (initial value of accumulator is 0) for C times.