




ESE | GATE | PSUs

ELECTRICAL ENGINEERING

DIGITAL ELECTRONICS & MICROPROCESSORS

 Volume - 1 : Study Material with Classroom Practice Questions



Digital Electronics & Microprocessors

(Solutions for Volume-1 Class Room Practice Questions)

1. Number Systems

01. Ans: (d)

Sol: $135_x + 144_x = 323_x$

$$(1 \times x^2 + 3 \times x^1 + 5 \times x^0) + (1 \times x^2 + 4 \times x^1 + 4 \times x^0) = 3x^2 + 2x^1 + 3x^0$$

$$\Rightarrow x^2 + 3x + 5 + x^2 + 4x + 4 = 3x^2 + 2x + 3$$

$$x^2 - 5x - 6 = 0$$

$$(x-6)(x+1) = 0 \quad (\text{Base cannot be negative})$$

Hence $x = 6$.

(OR)

As per the given number x must be greater than 5. Let consider $x = 6$

$$(135)_6 = (59)_{10}$$

$$(144)_6 = (64)_{10}$$

$$(323)_6 = (123)_{10}$$

$$(59)_{10} + (64)_{10} = (123)_{10}$$

So that $x = 6$

02. Ans: (a)

Sol: 8-bit representation of

$$+127_{10} = 01111111_{(2)}$$

1's complement representation of

$$-127 = 10000000.$$

2's complement representation of

$$-127 = 10000001.$$

No. of 1's in 2's complement of

$$-127 = m = 2$$

No. of 1's in 1's complement of

$$-127 = n = 1$$

$$\therefore m:n = 2:1$$

03. Ans: (c)

Sol: In 2's complement representation the sign bit can be extended towards left any number of times without changing the value. In given number the sign bit is 'X₃', hence it can be extended left any number of times.

04. Ans: (c)

Sol: Binary representation of $+(539)_{10}$:

$$\begin{array}{r} 2 \overline{) 539} \\ 2 \overline{) 269} \quad -1 \\ 2 \overline{) 134} \quad -1 \\ 2 \overline{) 67} \quad -0 \\ 2 \overline{) 33} \quad -1 \\ 2 \overline{) 16} \quad -1 \\ 2 \overline{) 8} \quad -0 \\ 2 \overline{) 4} \quad -0 \\ 2 \overline{) 2} \quad -0 \\ 1 \quad -0 \end{array}$$

$$(+539)_{10} = (10000 \ 11 \ 0 \ 11)_2 = (00100 \ 0011011)_2$$

$$2'S \text{ complement} \rightarrow 110111100101$$

$$\text{Hexadecimal equivalent} \rightarrow (DE5)_H$$

05. Ans: 5

Sol: Symbols used in this equation are 0,1,2,3

Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0)(x+3x^0+x^{-1})$$

$$3x^2 + x + 2 = (2x) \left(x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$x(x-5) = 0$$

$$x = 0 \text{ (or) } x = 5$$

x must be $x > 3$, So $x = 5$



06. Ans: 3

Sol: $123_5 = x8_y$

$$1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0 = x \cdot y^1 + 8 \times y^0$$

$$25 + 10 + 3 = xy + 8$$

$$\therefore xy = 30$$

Possible solutions:

i. $x = 1, y = 30$

ii. $x = 2, y = 15$

iii. $x = 3, y = 10$

\therefore 3 possible solutions exists.

07. Ans: 1

Sol: The range (or) distinct values

For 2's complement $\Rightarrow -(2^{n-1})$ to $+(2^{n-1}-1)$

For sign magnitude

$$\Rightarrow -(2^{n-1}-1) \text{ to } +(2^{n-1}-1)$$

Let $n = 2 \Rightarrow$ in 2's complement

$$-(2^{2-1}) \text{ to } +(2^{2-1}-1)$$

$$-2 \text{ to } +1 \Rightarrow -2, -1, 0, +1 \Rightarrow X = 4$$

$n = 2$ in sign magnitude $\Rightarrow -1 \text{ to } +1 \Rightarrow Y = 3$

$$X - Y = 1$$

08. Ans: (c)

Sol: (a) $(68)_{16} = (001 \ 101 \ 000)_2$

$$\begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array}$$

$$= (1 \ 5 \ 0)_8$$

(b) $(8C)_{16} = (010 \ 001 \ 100)_2$

$$\begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array}$$

$$= (2 \ 1 \ 4)_8$$

(c) $(4F)_{16} = (001 \ 001 \ 111)_2$

$$\begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array}$$

$$= (1 \ 1 \ 7)_8$$

(d) $(5D)_{16} = (001 \ 011 \ 101)_2$

$$\begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array} \begin{array}{ccc} \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \\ \text{ } & \text{ } & \text{ } \end{array}$$

$$= (1 \ 3 \ 5)_8$$

09. Ans: (b)

Sol: A. $\begin{array}{cc} 7 & 5 \\ \downarrow & \downarrow \end{array}$

$$(111 \ 101)$$

C. $\begin{array}{cc} 3 & 7 \\ \downarrow & \downarrow \end{array}$

$$(011 \ 111)$$

B. $\begin{array}{cc} 6 & 5 \\ \downarrow & \downarrow \end{array}$

$$(110 \ 101)$$

D. $\begin{array}{cc} 2 & 6 \\ \downarrow & \downarrow \end{array}$

$$(010 \ 110)$$

10. Ans: (a)

Sol: 2's complement arithmetic is preferred in digital computers because it is efficient and one representation for zero.

11. Ans: (a)

Sol: $(11X1Y)_8 = (12C9)_{16}$

$$8^4 + 8^3 + 64X + 8 + Y$$

$$= 16^3 + (2 \times 16^2) + (12 \times 16) + 9$$

$$4096 + 512 + 64X + 8 + Y$$

$$= 4096 + 512 + 192 + 9$$

$$\therefore 4616 + 64X + Y = 4809$$

$$64X + Y = 193$$

By verification option (a) is correct

12. Ans: (d)

Sol: 2's comp no:

a_3	a_2	a_1	a_0
-------	-------	-------	-------

2's comp no. using 6 bits

$$\rightarrow \begin{array}{cccccc} a_3 & a_3 & a_3 & a_2 & a_1 & a_0 \end{array}$$

$$(2's \text{ comp no}) \times 2 + 1$$

$$\rightarrow \begin{array}{cccccc} a_3 & a_3 & a_2 & a_1 & a_0 & 1 \end{array}$$



2. Logic Gates & Boolean Algebra

01. Ans: (c)

Sol: Given 2's complement numbers of sign bits are x & y. z is the sign bit obtained by adding above two numbers. \therefore Overflow is indicated by $= \bar{x}\bar{y}z + x y \bar{z}$

Examples

1. A = +7 0111
 B = +7 0111
 14 1110 $\Rightarrow \bar{x}\bar{y}z$
2. A = +7 0111
 B = +5 0101
 12 1100 $\Rightarrow \bar{x}\bar{y}z$
3. A = -7 1001
 B = -7 1001
 -14 10010 $\Rightarrow x y \bar{z}$
4. A = -7 1001
 B = -5 1011
 -12 10100 $\Rightarrow x y \bar{z}$

02. Ans: (b)

Sol: Truth table of XOR

A	B	o/p
0	0	0
0	1	1
1	0	1
1	1	0

Stage 1:

Given one i/p = 1 Always.

1	X	o/p
1	0	1
1	1	0

For First XOR gate o/p = \bar{X}

Stage 2:

\bar{X}	X	o/p
0	1	1
1	0	1

For second XOR gate o/p = 1.


Similarly for third XOR gate o/p = \bar{X} & for fourth o/p = 1

For Even number of XOR gates o/p = 1

For 20 XOR gates cascaded o/p = 1.


03. Ans: (b)

Sol:

 

04. Ans: (c)

Sol:


 


$$x = f_1 f_2$$

$$f_4 = f_1 \cdot f_2 + f_3$$



05. Ans: (d)

  

06. Ans: (c)

Sol: $\overline{x_1} \oplus \overline{x_3} = \overline{x_1 x_3} + \overline{x_1 \overline{x_3}} = y$

$\overline{x_2} \oplus \overline{x_4} = \overline{x_2 x_4} + \overline{x_2 \overline{x_4}} = z$

$(\overline{x_1} \oplus \overline{x_3}) \oplus (\overline{x_2} \oplus \overline{x_4})$

$= y \oplus z = 0, \text{ when } y = z$

\therefore option (c) is true

For all cases option A, B, D not satisfy.

07. Ans: (b)

Sol: $M(a,b,c) = ab + bc + ca$

$\overline{M(a,b,c)} = \overline{ab + bc + ca} = \overline{ab} \overline{bc} + \overline{ab} \overline{ca} + \overline{bc} \overline{ca}$

$M(a,b,\overline{c}) = ab + b\overline{c} + \overline{c}a$

$M(\overline{M(a,b,c)}, M(a,b,\overline{c}), c)$

$= (\overline{ab} \overline{bc} + \overline{ab} \overline{ca} + \overline{bc} \overline{ca})(ab + b\overline{c} + \overline{c}a)$
 $+ (ab + b\overline{c} + \overline{c}a)c + (\overline{bc} \overline{ca} + \overline{ab} \overline{ca} + \overline{ab} \overline{bc})c$

$= (\overline{bc} \overline{ca} + \overline{ab} \overline{ca} + \overline{ab} \overline{bc})(ab + b\overline{c} + \overline{c}a)$
 $+ (\overline{bc} \overline{ca} + \overline{ab} \overline{ca} + \overline{ab} \overline{bc})c + abc$

$= \overline{ab} \overline{c} + \overline{ab} \overline{c} + abc + \overline{ab} \overline{c}$

$= \overline{c}[ab + \overline{ab}] + c[ab + \overline{ab}]$


$= \sum m(1, 2, 4, 7)$

$\therefore M(x, y, z) = a \oplus b \oplus c$

Where $x = \overline{M(a,b,c)}, y = M(a,b,\overline{c}), z = c$

08. Ans: 40

Sol:

 

$\therefore Z$ is 1 for 40 nsec

09. Ans: (c)

Sol: Logic gates $\overline{X} + Y = \overline{X \overline{Y}} = \overline{X Y_1}$

Where $Y_1 = \overline{Y}$

It is a NAND gate and thus the gate is 'Universal gate'.

10. Ans: (d)

Sol: A. $X = \overline{A} + \overline{B} = \overline{AB}$

B. $X = \overline{A + B}$

C. $X = \overline{\overline{A} + \overline{B}} = AB$

D. $X = \overline{\overline{A} \overline{B}} = A + B$



11. Ans: (a)

Sol: XOR gate is not a universal gate, because it is not possible to realize any Boolean function using only XOR gates.

12. Ans: (b)

Sol: (A) $A \oplus B = 0$ only when $A = B$

(B) $\overline{A+B} = \overline{A} \cdot \overline{B} = 0$ only when $A = 1$ and $B = 1$

(C) $\overline{A} \cdot B = 0$ only when $A = 1$ and $B = 0$

(D) $A \oplus B = 1$ only when $A \neq B$

13. Ans: (b)

Sol: (A) $ab + bc + ca + abc$

$$bc(1+a) + ca + ab$$

$$bc + ca + ab$$

$$\text{Inverse function } \overline{(ab + bc + ca)}$$

$$= \overline{a} \overline{b} + \overline{b} \overline{c} + \overline{c} \overline{a}$$

(B) $ab + \overline{a} \overline{b} + \overline{c}$

$$\text{Inverse function} = \overline{ab + \overline{a} \overline{b} + \overline{c}}$$

$$= (\overline{a} + \overline{b})(a + b)c$$

$$= (\overline{a}b + a\overline{b})c$$

$$= (a \oplus b)c$$

(C) $(a+bc)$

$$\text{Inverse function} = \overline{a+bc}$$

$$= \overline{a}(\overline{b} + \overline{c})$$

(D) $(\overline{a} + \overline{b} + \overline{c})(a + \overline{b} + \overline{c})(\overline{a} + \overline{b} + c)$

$$\text{Inverse function}$$

$$\overline{(\overline{a} + \overline{b} + \overline{c})(a + \overline{b} + \overline{c})(\overline{a} + \overline{b} + c)}$$

$$= abc + \overline{a}bc + ab\overline{c}$$

14. Ans: (c)

Sol: AND gate : Boolean multiplication

OR gate : Boolean addition

NOT gate : Boolean complementation

15. Ans: (a)

Sol: When all inputs of a NAND-gate are shorted to get a one input, one output gate, it becomes an inverter.

When all inputs of a NAND – gate are at logic ‘0’ level, the output is at logic ‘1’ level.

Both statements are true and statement-II is the correct explanation of statement-I

16. Ans: (c)

Sol: A NAND gate represents a universal logic family.

Only two NAND gates are sufficient to accomplish any of the basic gates.

Statement-I is true but statement-II is false.

3. K-Maps

01. Ans: (b)

Sol:

yz \ wx	00	01	11	10
00		1	1	
01	×			1
11	×			1
10		1	1	×

$$f = \overline{x}z + x\overline{z}$$



02. Ans: (b)

Sol:

ab \ cd	00	01	11	10
00	1	x	x	1
01	x			1
11				
10	1			x

$$f = \bar{b} \bar{d} + \bar{b} \bar{c}$$

03.

Sol:

POS

wz \ xy	00	01	11	10
00	0	x	0	0
01	0	x	1	1
11	1	1	1	1
10	0	x	0	0

$= y(x+w)$

SOP

wz \ xy	00	01	11	10
00	0	x	0	0
01	0	x	1	1
11	1	1	1	1
10	0	x	0	0

$= xy + yw$

SOP: $x y + y w$

POS: $y(x + w)$

04. Ans: (a)

Sol: For n-variable Boolean expression,

Maximum number of minterms = 2^n

Maximum number of implicants = 2^n

Maximum number of prime implicants = $\frac{2^n}{2}$
 $= 2^{n-1}$

05. Ans: (c)

Sol:

AB \ C	00	01	11	10
0	1	1	0	0
1	0	1	1	0

$$F(A, B, C) = \bar{A}\bar{C} + BC$$

06. Ans: 1

Sol: After minimization = $(\overline{A + B + C + D})$
 $= ABCD$

\therefore only one minterm.

07. Ans: 3

Sol: $\bar{w} \bar{z} + \bar{w} x \bar{y} + \bar{x} y \bar{z}$

yz \ wx	00	01	11	10
00	1			1
01	1	1		1
11				
10				1

08. Ans: (c)

Sol: Given K-map is


$X_1 X_2 \backslash X_3 X_4$	00	01	11	10
00	1		d	d
01		1	d	1
11		d	1	
10	1	d		d



$$\text{Output} = \overline{X_2} \overline{X_4} + X_1 \overline{X_3} + X_2 X_4$$

09. Ans: None

Sol:

 


The minimal form is

$$F = \overline{x} + y + \overline{z}$$

None of the options is correct

10. Ans: (a)

Sol: Given K-map

 

No. of essential prime implicants = 4.

4. Combinational Circuits

01. Ans: (d)

Sol: Let the output of first MUX is “F₁”

$$F_1 = AI_0 + \overline{A}I_1$$

Where A is selection line, I₀, I₁ = MUX

Inputs

$$F_1 = \overline{S_1} \cdot W + S_1 \cdot \overline{W} = S_1 \oplus W$$

Output of second MUX is

$$F = \overline{A} \cdot I_0 + A \cdot I_1$$

$$F = \overline{S_2} \cdot F_1 + S_2 \cdot \overline{F_1}$$

$$F = S_2 \oplus F_1$$

$$\text{But } F_1 = S_1 \oplus W$$

$$F = S_2 \oplus S_1 \oplus W$$


$$\text{i.e., } F = W \oplus S_1 \oplus S_2$$

02. Ans: 19.2

Sol: One AND/OR gate delay = 1.2 μs

One XOR gate delay = 2.4 μs

Full Adder with 2 Half Adder

 

In one F.A; Sum delay = 4.8 μs

Carry delay = 2.4 + 1.2 + 1.2 μs = 4.8 μs

∴ RippleCarry waiting time

$$= 4.8 \times 3 = 14.4 \mu\text{s}$$

Final Result time = 14.4 + 4.8 = 19.2 μsec

03. Ans: (a)

Sol: The given circuit is binary parallel adder/subtractor circuit. It performs A+B, A-B but not A + 1 operations.

K	C ₀	Operation
0	0	A+B (addition)
0	1	A+B+1 (addition with carry)



1	0	$A + \overline{B}$ (1's complement addition)
1	1	$A + \overline{B} + 1$ (2's complement subtraction)

04. Ans: (d)

Sol: It is expansion of 2:4 decoders to 1:8 demultiplexer A_1, A_0 must be connected to S_1, S_0 i.e., $R = S_0, S = S_1$
 Q must be connected to S_2 i.e., $Q = S_2$
 P is serial input must be connected to D_{in}

05. Ans: 6

Sol: $T = 0 \rightarrow \text{NOR} \rightarrow \text{MUX 1} \rightarrow \text{MUX 2}$
 $2\text{ns} \quad 1.5\text{ns} \quad 1.5\text{ns}$
 $\text{Delay} = 2\text{ns} + 1.5\text{ns} + 1.5\text{ns} = 5\text{ns}$
 $T = 1 \rightarrow \text{NOT} \rightarrow \text{MUX 1} \rightarrow \text{NOR} \rightarrow \text{MUX 2}$
 $1\text{ns} \quad 1.5\text{ns} \quad 2\text{ns} \quad 1.5\text{ns}$
 $\text{Delay} = 1\text{ns} + 1.5\text{ns} + 2\text{ns} + 1.5\text{ns} = 6\text{ns}$
Hence, the maximum delay of the circuit is 6ns

06. Ans: -1

Sol: When all bits in 'B' register is '1', then only it gives highest delay.
 \therefore '-1' in 8 bit notation of 2's complement is 1111 1111

07. Ans: (d)

Sol: The race hazard problem does not occur in combinational circuits.
The output of a combinational circuit depends upon present inputs only.
Statement-I is false but Statement-II is true.


08. Ans: (b)

Sol: A de-multiplexer can be used as a decoder. A decoder with enable input acts as a de-multiplexer, while using Enable input as a data input line. De-multiplexer is realized using AND gates.


A	B	F
0	0	C
0	1	C
1	0	\overline{C}
1	1	\overline{C}

09. Ans: (b)


Sol: Half Adder

 


D-Flipflop

 

T-Flipflop

 


Exclusive - OR

 



10. Ans: (b)

Sol: → A 64 input MUX using 8-input MUX

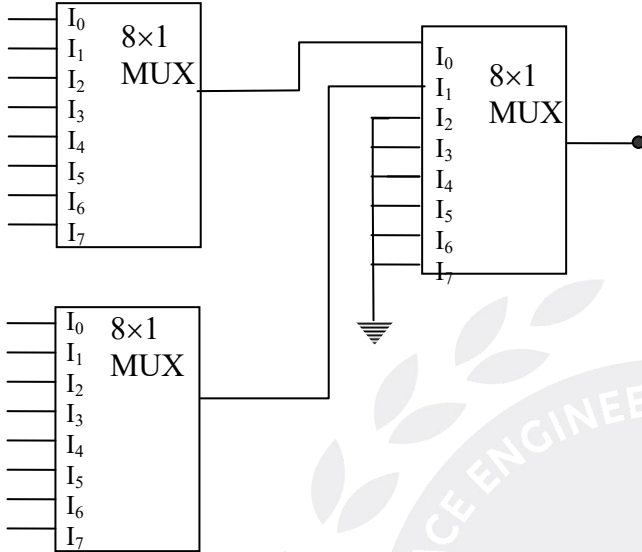

→ A 6-variable function can be implemented using 6-input MUX

11. Ans: 195

Sol: In a 16 bit parallel binary adder, the carry has to propagate 15 stages plus the maximum of time taken for producing sum and carry worst case Delay, $T = 15 \times 12 + 15$
 $T = 180 + 15$
 $T = 195 \text{ ns}$

12. Ans: (b)

Sol: Any Boolean function can be realized by using a suitable multiplexer.
 A multiplexer can be realized using NAND and NOR gates, which are universal gates.
 Both statements are correct but statement-II is not a correct explanation for statement-I.


5. Sequential Circuits

01. Ans: (c)

Sol: Given Clk, X_1 , X_2

Output of First D-FF is Q_1

Output of Second D-FF is Q_2

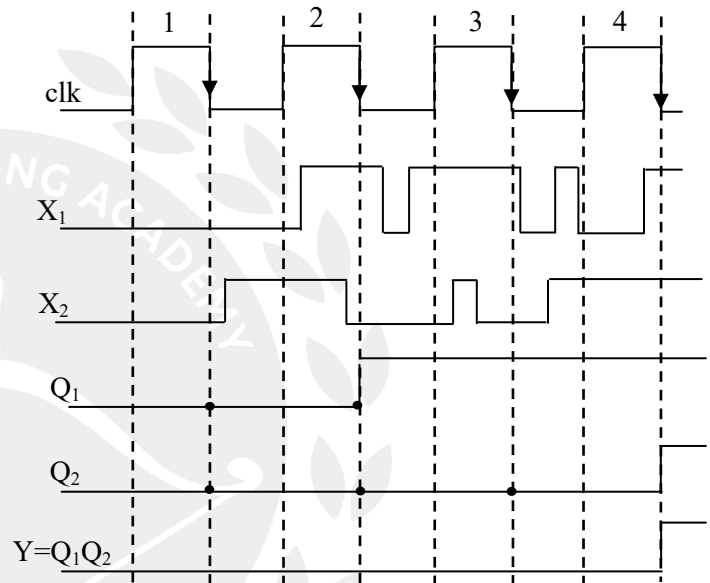

02. Ans: 4

Sol: In the given first loop of states, zero has repeated 3 times. So, minimum 4 number of Flip-flops are needed.

03. Ans: 7

Sol: The counter is cleared when

$$Q_D Q_C Q_B Q_A = 0110$$

Clk	Q_D	Q_C	Q_B	Q_A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0



3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	0	0	0

As the clear input is given to be synchronous so it waits upto the next clock pulse to clear the counter & hence the counter get's cleared during the 7th clock pulse.

∴ mod of counter = 7


04. Ans: (b)

Sol: The given circuit is a mod 4 ripple down counter. Q_1 is coming to 1 after the delay of $2\Delta t$.

CLK	Q_1	Q_0
	0	0
1	1	1
2	1	0
3	0	1
4	0	0

05. Ans: (c)

Sol: Assume $n = 2$

 

Outputs of counter is connected to inputs of decoder

Counter outputs		Decoder inputs		Decoder outputs			
Q_1	Q_0	a	b	d_3	d_2	d_1	d_0
0	0	0	0	0	0	0	1
0	1	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0

The overall circuit acts as 4-bit ring counter
 $n = 2$

∴ $k = 2^2 = 4$, k-bit ring counter

06. Ans: (b)

Sol:

CLK	Serial in= $B \oplus C \oplus D$	A B C D
0		1 0 1 0
1	1	1 1 0 1
2	0	0 1 1 0
3	0	0 0 1 1
4	0	0 0 0 1
5	1	1 0 0 0
6	0	0 1 0 0
7	1	1 0 1 0

∴ After 7 clock pulses content of shift register become 1010 again

07. Ans: (b)

Sol:

J	K	Q	\bar{Q}_n	$T = (J + Q_n) (K + \bar{Q}_n)$	Q_{n+1}
0	0	0	1	$0.1 = 0$	0 } Q_n
0	0	1	0	$1.0 = 0$	
0	1	0	1	$0.1 = 0$	0 } 0
0	1	1	0	$1.1 = 1$	
1	0	0	1	$1.1 = 1$	1 } 1
1	0	1	0	$1.0 = 0$	



1	1	0	1	1.1 = 1	1 } 0 } \bar{Q}_n
1	1	1	0	1.1 = 1	

J	KQ_n			
	00	01	11	10
0			1	
1	1		1	1


$$T = J \bar{Q}_n + KQ_n = (J+Q_n)(K + \bar{Q}_n)$$

08. Ans: 1.5

Sol:

C/k	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Y = Q ₃ + Q ₅
0	0	1	0	1	0	0
1	0	0	1	0	1	1
2	1	0	0	1	0	0
3	0	1	0	0	1	1
4	1	0	1	0	0	1
5	0	1	0	1	0	0

 The waveform at OR gate output, Y is [A = +5V]



Average power

$$\begin{aligned}
 P &= \frac{V_{Ao}^2}{R} = \frac{1}{R} \left[\int_{T_1 \rightarrow \infty}^{T_1} y^2(t) dt \right] \\
 &= \frac{1}{RT_1} \left[\int_T^{2T} A^2 dt + \int_{3T}^{5T} A^2 dt \right] \\
 &= \frac{A^2}{RT_1} [(2T - T) + (5T - 3T)]
 \end{aligned}$$

$$= \frac{A^2 \cdot 3T}{R(5T)} = \frac{5^2 \cdot 3}{10 \times 5} = 1.5 \text{ mw}$$

09. Ans: (b)

Sol:

Present State	Next State		Output (Y)	
	X = 0	X = 1	X = 0	X = 1
A	A	E	0	0
B	C	A	1	0
C	B	A	1	0
D	A	B	0	1
E	A	C	0	1

Step (1):

By replacing state B as state C then state B, C are equal.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	E
B	B	A
B	B	A
D	A	B
E	A	B

Step (2):

Reducing state table		
Present state	Next state	
	X = 0	X = 1



A	A	E
B	B	A
D	A	B
E	A	B

State D, E are equal, remove state E and replace E with D in next state.

Reducing state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B
D	A	B

Finally reduced state table is

Reduced state table		
Present state	Next state	
	X = 0	X = 1
A	A	D
B	B	A
D	A	B

∴ 3 states are present in the reduced state table

10. Ans: (c)

Sol: State table for the given state diagram

State	Input	Output
S ₀	0	1

S ₀	1	0
S ₁	0	1
S ₁	1	0

Output is 1's complement of input.

11. Ans: (c)

Sol: In state (C), when XYZ = 111, then Ambiguity occurs

Because, from state (C)

⇒ When X = 1, Z = 1

⇒ N.S is (A)

When Y = 1, Z = 1 ⇒ N.S is (B)

12. Ans: (c)

Sol: For Asynchronous sequential circuits clock is applied at one flip flop and the next stage receives clock from previous stage output.

13. Ans: (d)

Sol: Master slave JK flip flop is a edge triggered flip flop.

14. Ans: (b)

Sol: Divider : Bi stable multivibrator

Clips input voltage at Two predetermined levels: Schmitt trigger

Square wave generator: Astable multivibrator

Narrow current pulse generator: Blocking oscillator

15. Ans: (a)

Sol: A flip-flop is a bistable multivibrator.

A flip-flop remains in one stable state indefinitely until it is directed by an input



signal to switch over to the other stable state.

Both statements are correct and statement - II is correct explanation of statement-I

16. Ans: (a)

Sol: The collection of all state variables (memory element stored values) at any time, contain all the information about the past, necessary to account for the circuit's future behaviour. A change in the stored values in memory elements changes the sequential circuit from one state to another.
Both statements are correct and statement-II is correct explanation of statement-I.

6. AD and DA Converters


01. Ans: (b)

Sol:

CLK	Counter			Decoder				V ₀
	Q ₂	Q ₁	Q ₀	D ₃	D ₂	D ₁	D ₀	
1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	1
3	0	1	0	0	0	1	0	2
4	0	1	1	0	0	1	1	3
5	1	0	0	1	0	0	0	8
6	1	0	1	1	0	0	1	9
7	1	1	0	1	0	1	0	10
8	1	1	1	1	0	1	1	11

02. Ans: (b)

Sol:

 

$$R_{\text{equ}} = (((((2R \parallel 2R) + R) \parallel 2R) + R) \parallel 2R) + R \parallel 2R$$

$$R_{\text{equ}} = R = 10k\Omega$$

$$I = \frac{V_R}{R} = \frac{10V}{10k} = 1mA$$

$$\begin{aligned} \text{Current division at } \frac{I}{16} \\ = \frac{1 \times 10^{-3}}{16} = 62.5 \mu A \end{aligned}$$

03. Ans: (c)

Sol: Net current at inverting terminal,

$$I_i = \frac{I}{4} + \frac{I}{16} = \frac{5I}{16}$$

$$V_0 = -I_i R = -\frac{5I}{16} \times 10k\Omega$$

$$= \frac{-5 \times 1 \times 10^{-3} \times 10 \times 10^3}{16}$$

$$= -3.125V$$

04. Ans: (d)

Sol: Given that $V_{\text{DAC}} = \sum_{n=0}^3 2^{n-1} b_n$ Volts

$$V_{\text{DAC}} = 2^{-1} b_0 + 2^0 b_1 + 2^1 b_2 + 2^2 b_3$$

$$\Rightarrow V_{\text{DAC}} = 0.5b_0 + b_1 + 2b_2 + 4b_3$$

Initially counter is in 0000 state



Up counter o/p	$V_{DAC}(V)$	o/p of comparator
$b_3 b_2 b_1 b_0$		
0 0 0 0	0	1
0 0 0 1	0.5	1
0 0 1 0	1	1
0 0 1 1	1.5	1
0 1 0 0	2	1
0 1 0 1	2.5	1
0 1 1 0	3	1
0 1 1 1	3.5	1
1 0 0 0	4	1
1 0 0 1	4.5	1
1 0 1 0	5	1
1 0 1 1	5.5	1
1 1 0 0	6	1
1 1 0 1	6.5	0

When $V_{DAC} = 6.5 V$, the o/p of comparator is '0'. At this instant, the clock pulses to the counter are stopped and the counter remains in 1101 state.

\therefore The stable reading of the LED display is 13.

05. Ans: (b)

Sol: The magnitude of error between V_{DAC} & V_{in} at steady state is $|V_{DAC} - V_{in}| = |6.5 - 6.2| = 0.3 V$

06. Ans: (a)

Sol: In Dual slope


$$\begin{aligned}
 \text{ADC} \Rightarrow V_{in} T_1 &= V_R \cdot T_2 \\
 \Rightarrow V_{in} &= \frac{V_R T_2}{T_1} \\
 &= \frac{100 \text{ mV} \times 370.2 \text{ ms}}{300 \text{ ms}}
 \end{aligned}$$

DVM indicates = 123.4

07. Ans: (d)

Sol: No. of bits = 8,

Reference voltage = 8V

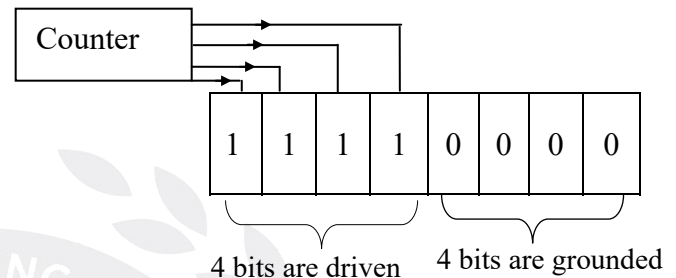

Maximum peak to peak amplitude of the waveform at the output of the digital to analog converter is

$$\begin{aligned}
 V_{\max} &= \frac{V_{\text{ref}}}{2^n} (d_n 2^n) \\
 &= \frac{8}{256} \times 240 = 7.5V
 \end{aligned}$$

08. Ans: (d)

Sol: Ex: $f_{in} = 1 \text{ kHz} \rightarrow f_s = 2 \text{ kHz}$

$f_{in} = 25 \text{ kHz} \leftarrow f_s = 50 \text{ kHz}$

1. Max conversion time = $2^{N+1} T = 2^{11} \cdot 1 \mu s = 2048 \mu s$

2. Sampling period = $T_s \geq$ maximum conversion time

$$T_s \geq 2048 \mu s$$


3. Sampling rate $f_s = \frac{1}{T_s} \leq \frac{1}{2048 \times 10^{-6}}$
 $f_s \leq 488 \quad f_s \leq 500 \text{ Hz}$

4. $f_{in} = \frac{f_s}{2} = 250 \text{ Hz}$



09. Ans: (b)

Sol:

 

$$V_{in}^1 = \frac{V_{in}}{RC_{eq}} T$$

V_{in}^1 has to settle down within $\frac{1}{2}$ LSB of full scale value.

$$\text{i.e } \frac{509}{510} V_{in} = \frac{V_{in} \cdot T}{75 \times (255 \times 8 \times 10^{-12})}$$

$$\Rightarrow T = (75 \times 255 \times 8 \times 10^{-12}) \times \frac{509}{510}$$

$$T \approx 0.15 \mu\text{sec}$$

Thus sample period $T_s \geq T$

$$T_s \geq 0.15 \text{ m sec}$$

$$f_s \text{ max} = \frac{1}{T_{s, \text{min}}}$$

$$= \frac{1}{0.15 \times 10^{-6}} \text{ Hz}$$

$$\approx 6 \text{ Megasamples}$$

10. Ans: (a)

Sol: Dual-slope A/D converter is the most preferred A/D conversion approach in digital multimeters.

Dual-slope A/D converter provides high accuracy in A/D conversion, while at the same time suppressing the hum effect on the input signal.

Both Statements are true and statement-II is the correct explanation of statement-I.

11. Ans: (d)

Sol: SAR type ADC : Settling time for n-bits is $(n+2) T$ clock pulses

Flash ADC : $(2^n - 1)$ comparators required for n-bit dual

Dual slope ADC : Works well even in noisy environment

Counter DAD : Settling time dependent on the input

12. Ans: (c)

Sol: Dual slope ADC : Hum rejection approximation

Counter-ramp ADC : Conversion time dependent on single amplitude

Successive ADC : Fixed conversion time, depends on the number of bits

Simultaneous ADC: High speed operation

13. Ans: (a)

Sol: The output of an 8-bit A to D converter is 40H for an input of 2.5V.

ADC has an output range of 00 to FFH for an input range of $-5V$ to $+5V$.

Both Statements are true and statement-II is the correct explanation of statement-I.

14. Ans: (c)

Sol: Digital ramp converter is the slowest ADC.

Conversion time for digital ramp ADC is not $N^2 T$.



15. Ans: (b)

Sol: Resolution for n-bit A/D converter in percentage.

$$= \frac{1}{2^n - 1} \times 100$$

$$= \frac{1}{2^{12} - 1} \times 100$$

$$= 2.443 \times 10^{-4} \times 100$$

$$= 0.02441$$

7. Architecture, Pin Details of 8085 & Interfacing with 8085

01. Ans: (a)


Sol: chip select is an active low signal for $\overline{\text{chipselect}} = 0$; the inputs for NAND gate must be let us see all possible cases for $\overline{\text{chipselect}} = 0$ condition

A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	
0	0	0	0	0	0	X	X	
0	0	1	1	0	0	X	X	
0	1	0	1	0	0	X	X	
0	1	1	0	0	0	X	X	→ 60H (A ₁ A ₀ =00)
1	0	0	1	0	0	X	X	
1	0	1	0	0	0	X	X	
0	0	0	0	1	1	X	X	
0	0	1	1	1	1	X	X	
0	1	0	1	0	0	X	X	→ 63H (A ₁ A ₀ =11)
0	1	1	0	0	0	X	X	
1	0	0	1	0	0	X	X	
1	0	0	0	0	0	X	X	

The only option that suits here is option(a)

A₀ & A₁ are used for line selection

A₂ to A₇ are used for chip selection

 

∴ Address space is 60H to 63H

A₀ to A₁₁ are used for line selection

A₁₂ to A₁₅ are used for chip selection

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	-----	A ₀	
1	1	1	0	0	-----	0	=E000H
1	1	1	0	1	-----	1	=EFFFH

02. Ans: (d)

Sol: • Both the chips have active high chip select inputs.

- Chip 1 is selected when A₈ = 1, A₉ = 0
- Chip 2 is selected when A₈ = 0, A₉ = 1
- Chips are not selected for combination of 00 & 11 of A₈ & A₉
- Upon observing A₈ & A₉ of given address Ranges, F800 to F9FF is not represented



03. Ans: (d)

Sol: The I/O device is interfaced using “Memory Mapped I/O” technique.

The address of the Input device is

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
1	1	1	1	1	0	0	0	1	1	1	1	1	0	0	0

=F8F8_H

The Instruction for correct data transfer is
= LDA F8F8H

04. Ans: (b)

Sol: • Out put 2 of 3×8 Decoder is used for selecting the output port. ∴ Select code is 010


A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	---	A ₀
0	1	0	1	0	0	---	0

⇒ 5000H

- This mapping is memory mapped I/O

06. Ans: (a)

Sol: Address Range given is

 

	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
1000H →	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
2FFFH →	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1

To provide \overline{CS} as low, The condition is

A₁₅ = A₁₄ = 0 and A₁₃ A₁₂ = 01 (or) (10)

i.e A₁₅ = A₁₄ = 0 and A₁₃ A₁₂ shouldn't be 00, 11.

Thus it is A₁₅ + A₁₄ + [A₁₃A₁₂ + $\overline{A_{13}}$ $\overline{A_{12}}$]

05. Ans: (d)


Sol:

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉ --- A ₀	
0	0	0	0	1	0	0 --- 0	=0800H
			⋮			⋮	⋮
0	0	0	0	1	0	1 --- 1	=0BFFH
0	0	0	1	1	0	0 --- 0	=1800H
			⋮			⋮	⋮
0	0	0	1	1	0	1 --- 1	=1BFFH
0	0	1	0	1	0	0 --- 0	=2800H
			⋮			⋮	⋮
0	0	1	0	1	0	1 --- 1	=2BFFH
0	0	1	1	1	0	0 --- 0	=3800H
			⋮			⋮	⋮
0	0	1	1	1	0	1 --- 1	=3BFFH



07. Ans: (a)

Sol:

 

A_{15}, A_{14} are used for chip selection

A_{13}, A_{12}, A_{11} are used for input of decoder

$A_{15} \ A_{14}$	$A_{13} \ A_{12} \ A_{11}$	$A_{10} \text{ ----- } A_0$
Enable of decoder	Input of decoder	Address of chip

Size of each memory block = $2^{11} = 2K$

08. Ans: (a)

Sol: The data path contains all the circuits to process data within the CPU with the help of which data is suitably transformed.

It is the responsibility of the control path to generate control and timing signals as required by the opcode.

Both Statements are true and statement-II is the correct explanation of statement-I.

09. Ans: (b)

Sol: Program counter is a register that contains the address of the next instruction to be executed.

IR (Instruction Register) is not accessible to programmer.

Both Statements are true but statement-II is not correct explanation of statement-I.

10. Ans: (a)

Sol: A processor can reference a memory stack without specifying an address.

The address is always available and automatically updated in the stack pointer.

Both Statements are true and statement-II is the correct explanation of statement-I.

11. Ans: (c)

Sol: The programmer has to initialize the stack pointer based on design requirements.

12. Ans: (b)

Sol: The DMA technique is more efficient than the Interrupt-driven technique for high volume I/O data transfer.

The DMA technique does not make use of the Interrupt mechanism.

Both Statements are true but statement-II is not correct explanation of statement-I.

13. Ans: (c)

Sol: A microcontroller has onchip (inbuilt) memory, whereas a microprocessor has no such internal memory.

The program to be run by microprocessor is to be stored in separate memory (E^2 PROM) chip and to be interfaced microprocessor.

14. Ans: (d)

Sol: INTR is a non vectored interrupt. As such external hardware is required to supply vector address. SIM is not used with respect to INTR. The SIM is used for selective local masking of three hardware maskable vectored interrupts (RST 7.5, RST 6.5, RST 5.5)

8. Instruction Set of 8085 & Programming with 8085

01. Ans: (c)

Sol: 6010H : LXI H,8A79H ; (HL) = 8A79H
6013H : MOV A, L ; (A) ← (L) = 79
6014H : ADD H ; (A) = 0111 1001
+
; (H) = 1000 1010
; (A) = 0000 0011
CY = 1, AC = 1
6015H : DAA ; 66 Added to (A)
since CY=1 &
AC=1
; (A) = 69H
6016H : MOV H,A ; (H) ← (A) = 69H
6017H : PCHL ; (PC) ← (HL) = 6979H

02. Ans: (c)

Sol: 0100H : LXI SP, 00FFH ; (SP) = 00FFH
0103H : LXI H, 0107 H ; (HL) = 0107H
0106H : MVI A, 20H ; (A) = 20H
0108H : SUB M ; (A) ← (A) - (0107)
; (0107) = 20H
; (A) = 00H

The contents of Accumulator is 00H

03. Ans: (c)

Sol: LXI SP, 00FFH ; (SP) = 00FFH
 LXI H, 0107H ; (HL) = 0107H
 MVI A, 20H ; (A) = 20H
 SUB M ; (A) ← (A) – (0107)
 ; (0107) = 20H = M
 ; (A) = 00H
 ORI 40H ; A ∨ 40H
 A = 40H
 ADD M ; 40H + 20H = 60H

04. Ans: (c)

Sol: SUB1 : MVI A, 00H A ← 00H
CALL SUB2 → program will shifted to
SUB 2 address location A
SUB 2 : INR A →

01H

RET → returned to the main program
 ∴ The contents of Accumulator after execution of the above SUB2 is 02H

05. Ans: (c)

Sol: The loop will be executed until the value in register equals to zero, then,
Execution time

$$= 9(7T + 4T + 4T + 10T) + (7T + 4T + 4T + 7T) + 7T$$

$$= 254T$$

06. Ans: (d)

Sol: H=255 : L = 255, 254, 253, ---0
H=254 : L = 0, 255, 254, -----0
|
H=1 : L = 0,255,254,253,---0
H=0 : ———



→ In first iteration (with $H = 255$), the value in L is decremented from 255 to 0 i.e., 255 times

→ In further remaining 254 iterations, the value in L is decremented from 0 to 0 i.e., 256 times

∴ 'DCRL' instruction gets executed for

$\Rightarrow [255 + (254 \times 256)]$

$\Rightarrow 65279$ times

07. Ans: (a)

Sol: "STA 1234H" is a 3-Byte Instruction and it requires 4 Machine cycles (Opcode fetch, Operand1 Read, Operand2 Read, Memory write). The Higher order Address ($A_{15} - A_8$) sent in 4 machine cycles is as follows

Given "STA 1234" is stored at 1FFE_H

i.e., Address Instruction

1FFE, 1FFF, 2000 : STA 1234H

Machine cycle	Address ($A_{15}-A_0$)	Higher order address ($A_{15}-A_8$)
1. Opcode fetch	1FFE _H	1F _H
2. Operand1 Read	1FFF _H	1F _H
3. Operand2 Read	2000 _H	20 _H
4. Memory Write	1234 _H	12 _H

i.e. Higher order Address sent on $A_{15}-A_8$ for 4 Machine Cycles are 1F_H, 1F_H, 20_H, 12_H.

08. Ans: (d)

Sol: The operation SBI BE_H indicates A-BE → A where A indicates accumulator. Thus the result of the subtraction operation is stored in the accumulator and the contents of accumulator are changed.

09. Ans: (c)

Sol: If the content in register B is to be multiplied with the content in register C, the contents of register B is added to the accumulator (initial value of accumulator is 0) for C times.

10. Ans: (c)

Sol: Push takes 12T states due to pre decrement and pop takes 10T states.

11. Ans: (d)

Sol:

CY

Given $A = A7_H = \boxed{10100111} \ 0$

After executing RLC $\Rightarrow A = \boxed{01001111} \ 1$

$A = 4F_H$ and $cy = 1$

12. Ans: (b)

Sol: OUT: output data from accumulator to a port with 8-bit addresses. The contents of the accumulator are copied into the I/O ports specified by the operand.

IN: Input data to accumulator from a port with 8-bit address. The contents of the input port designated in the operand are read and loaded into the accumulator.



13. Ans: (a)

Sol: When RET instruction is executed by any subroutine then the top of the stack will be popped out and assigned to the PC.

14. Ans: (b)

Sol: PUSH PSW \Rightarrow 1 Byte instruction
 \Rightarrow OPFC + 2T + MW1C + MW2C
 \Rightarrow Special OPFC + MW1C + MW2C
 \Rightarrow 3 Machine cycles

15. Ans: (c)

Sol: Flags are not affected for execution of data transfer instructions since there is no involvement of ALU

16. Ans: (a)

Sol: Immediate addressing : LXI H, 2050H
 Implied addressing : RRC
 Register addressing : MOV A,B
 Direct addressing : LDA 30FF

17. Ans: (c)

Sol: 'DAD' instruction adds contents of HL register pair with specified register pair contents and stored in HL register pair.

18. Ans: (a)

Sol: Format of instruction Template:-

Label	Mnemonics	operand	comments

19. Ans: (b)

Sol: Implicit addressing mode
 : RAL

Register-indirect addressing mode

: MOV A, M

Immediate addressing mode

: JMP 3FA0H

Direct addressing mode

LDA 03FCH

20. Ans: (a)

Sol: Total no. of machine cycles in CALL instruction is 18.

1. Opcode fetch=6T

2. Two memory READ machine cycles to read subroutine address = 3T + 3T = 6T

3. Two memory WRITE machine cycles on the stack = 3T + 3T = 6T

\therefore I/O was not used in CALL instruction

21. Ans: (d)

Sol: PCHL : Transfer the contents of HL to the program counter.

SPHL : Transfer the contents of HL to the stack pointer

XTHL : Exchange the top of the stack with the contents of HL pair

XCHG : Exchange the contents of HL with those of DE pair

9. 8086 Microprocessors

01. Ans: (c)

Sol: 16-bit microprocessor has more speed and more data handling capability compared to 8-bit microprocessor.



02. Ans: (c)

Sol: In case of a 16-bit processor, a single instruction is enough to process a function. For processing the same function a long

sequence of instructions will be required for a 8-bit processor.

03. Ans: (c)

Sol: • 8086 μ p has 20 Address output lines. As such, a total of about 2^{20} i.e., 1MB memory can be directly addressed by 8086 μ p

- The programming model of 8086 μ p has the following registers

AX, BX, CX, DX

CS, DS, SS, ES

Flag registers: SP, IP, BP, SI, DI i.e., a total no. of 14 registers

- There are total 9 flags in 8086 μ p and the flag register is divided into two types.

(a) Status flags: The six status flags are

1. Sign flag (S)
2. Zero flag (Z)
3. Auxiliary carry flag (AC)
4. Parity flag (P)
5. Carry flag (CY)
6. Overflow flag (O)

(b) Control flags: The three control flags are

1. Directional flag (D)
2. Interrupt flag (I)
3. Trap flag (T)

D ₁₅	D ₁₄	D ₁₃	D ₁₂	D ₁₁	D ₁₀	D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
				O	D	I	T	S	Z		AC		P		CY

Fig: Format of flag register



04. Ans: (c)

Sol: Setting Trap flag puts the processor into single mode for debugging. In single stepping microprocessor executes an instruction and enters into single step ISR. If $TF = 1$, the CPU automatically generates an internal interrupt after each instruction, allowing a program to be inspected as it executes instruction by instruction.

05. Ans: (b)

Sol: For 8086 μP , the jump distance in bytes for short jump range is forward 127 and backward 128.

06. Ans: (a)

Sol: Number of address lines in 8086 is 20. Address space is $2^{20} = 1\text{MB}$

07. Ans: (d)

Sol: The instruction queue length in 8086 is 6 bytes and in 8088 is 4 bytes.

08. Ans: (d)

Sol: 8086 microprocessor can be operated in multiprocessor configuration when $\overline{MN}/\overline{MX}$ input connected to ground.

09. Ans: (d)

Sol: A 16 bit μP completes access of a word starting from even address in one bus cycle.

10. Ans: (b)

Sol: In relative base indexed Addressing mode, the 20 bit physical address of Data segment location is calculated as followed.

$$\begin{aligned} P.A &= (D.S \text{ register}) \times 10H + (B \times \text{register}) \\ &\quad + (DI \text{ register}) + 16 \text{ bit displacement} \\ &= 2100H \times 10H + 0158H + 1045H \\ &\quad + 1B57H \\ &= 21000H + 2CF4H \\ &= 23CF4H \end{aligned}$$

11. Ans: (a)

$$\begin{aligned} \text{Sol: Effective Address} &= (C.S \text{ reg}) \times 10H \\ &\quad + (IP \text{ reg}) \\ &= 1FABH \times 10H + 10A1H \\ &= 20B51H \end{aligned}$$

12. Ans: (c)

Sol: SI is the source index, used as a pointer to the current character being read in a string instruction. It is also available as an offset to add to BX or BP when doing indirect addressing.

DI is the destination index, used as a pointer to the current character being written or compared in a string instruction. It is also available as an offset.

13. Ans: (b)

Sol: The intermediate wait states are always, inserted between the clock cycles T_2 and T_3 .



14. Ans: (a)

Sol: For a type 0 interrupt, the 8086 pushes the flag register on the stack, resets IF and TF and pushes the return addresses on the stack.

15. Ans: (c)

Sol: The interrupt vector table IVT of 8086 contains the starting CS and IP values of the interrupt service routine.

16. Ans: (d)

Sol: The 8086 arithmetic instructions work on Signed and unsigned numbers Unpacked BCD data

17. Ans: (c)

Sol: LOOP and ROTATE instructions of an 8086 μ p uses the contents of a CX register as a counter.

18. Ans: (c)

Sol: In a multi-processor configuration, the two co-processor instruction sets must be disjoint.

19. Ans: (b)

Sol: MOV [1234 H], AX
Move the contents of register AX to memory offset 1234 H and 1235 H.

