



ACE

Engineering Academy

TEST ID: 201

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

ESE- 2019 (Prelims) - Offline Test Series

Test-1

ELECTRICAL ENGINEERING

SUBJECT: ANALOG, DIGITAL ELECTRONICS AND BASIC ELECTRONICS ENGINEERING SOLUTIONS

01. Ans: (d)

Sol:

1. With increase in the temperature zener break down voltage reduces
2. The Avalanche breakdown voltage has positive temperature coefficient
3. Zener breakdown occurs due to large electric field across reverse biased junction
4. Avalanche break down occurs in lightly doped junctions

02. Ans: (b)

Sol:
$$C_D = \frac{\tau I}{\eta V_T} = \frac{1n \times 1m}{25m}$$
$$= \frac{1n}{25}$$
$$= \frac{1000PF}{25}$$
$$= 40PF$$

Derivation for diffusion capacitance:

$$C_D = \frac{dQ}{dV_D}$$

$$Q = \tau I_s \left(e^{\frac{V_D}{\eta V_T}} - 1 \right)$$

$$\frac{dQ}{dV_D} = \frac{\tau I_s e^{\frac{V_D}{\eta V_T}}}{\eta V_T}$$
$$= \frac{\tau I}{\eta V_T}$$

03. Ans: (b)

Sol:
$$I_D = I_s \left(e^{\frac{V_D}{\eta V_T}} - 1 \right)$$


$$\frac{dI_D}{dV_D} = \frac{I_s e^{\frac{V_D}{\eta V_T}}}{\eta V_T}$$
$$\cong \frac{I_D}{\eta V_T}$$

$$r_{dynamic} = \frac{\partial V_D}{\partial I_D} = \frac{\eta V_T}{I_D} = \frac{26mV}{20m} = 1.3\Omega$$



04. Ans: (b)

Sol:

 

$$P_D = V_D I_D + I_D^2 r_{DC}$$

$$r_{DC} = \frac{V_D}{I_D} = \frac{0.6}{3}$$

$$= 0.2$$

$$P_D = 0.5 \times 3 + (3)^2 \times 0.2$$

$$= 1.5 + 1.8$$

$$= 3.3 \text{ W}$$

05. Ans: (c)

Sol: $V_{3k} = 15 \cdot \frac{3}{2+3}$

$$= 9\text{V}$$

$V_{3k} < V_Z$ Hence zener diode is O.C

Hence

$$I_L = \frac{15}{2k+3k} = 3\text{mA}$$

06. Ans: (d)

Sol: As V_{CB} increases

1. Recombination of the charge carriers with in the base decreases.
2. The concentration gradient of minority carriers increases with in the base.

3. C.E. current gain β increases.

4. CB current gain α increases.

07. Ans: (d)

Sol:

1. In the input characteristics of C.E. Configuration for same V_{BE} as V_{CE} increases, input current I_B decreases.
2. The input resistance of C.B. configuration is less compared to C.E.
3. Only voltage gains is high in C.B. configuration and current gain is approximately equal to 1.

08. Ans: (a)

Sol:

1. The Leakage current I_{CB0} increases
2. Base emitter voltage V_{BE} decreases.
3. Power dissipation increases

09. Ans: (a)

Sol: $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{-2I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$= -2 \times \frac{2\text{mA}}{-4} \left(1 - \frac{-2}{-4} \right)$$

$$= 1\text{m} \left(1 - \frac{1}{2} \right)$$

$$= 0.5 \text{ m}\Omega$$



SHORT TERM BATCHES

SUMMER

» SHORT TERM BATCHES

GATE+PSUs - 2020

Admissions Open From 14th NOV 2018

— HYDERABAD —

29th April | 06th May | 11th May

18th May | 26th May | 02nd June 2019

— DELHI —

11th May | 23rd May 2019

Start Early.. Gain Surely...

EARLY BIRD OFFER :

Register on or Before 31st December 2018 : 5000/- Off | Register on or Before 31st March 2019 : 3000/- Off



TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2019

Date of Exam : 20th January 2019

Last Date to Apply : 31st December 2018

Highlights :

- Get real-time experience of **GATE-2019** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post GATE guidance sessions by experts.
- Encouraging awards for **GATE-2019** toppers.




10. Ans: (a)

Sol: $I_C = \beta I_B + I_{CE0}$
 $= \beta I_B + (\beta + 1) I_{CB0}$
 $= 100 (10\mu A) + 101 (100 \text{ nA})$
 $= 1\text{mA} + 0.0101\text{mA}$
 $= 1.0101 \text{ mA}$

11. Ans: (b)

Sol:

 

$$S = \frac{1 + \beta}{1 + \beta \frac{R_E}{R_E + R_B}}$$

$$= \frac{1 + 99}{1 + 99 \left(\frac{1}{10} \right)}$$

$$= \frac{100}{10.9} = 9.17$$


12. Ans: (a)

Sol: For thermal stability of the BJT amplifier, the rate at which heat released at the junction must be less than rated which heat is transfer to the atmosphere.

So, $\frac{\partial P_C}{\partial T_J} < \frac{1}{\theta_{JA}}$

13. Ans: (c)

Sol:

 

$$10.7 = 10kI_B + (\beta + 1) I_B (900) + 0.7$$

$$\beta = 99$$

$$10.7 = [10k + 100 (900)] I_B + 0.7$$

$$10 = (100k) I_B$$

$$I_B = \frac{1}{10} \text{ mA}$$

$$= 0.1 \text{ mA}$$

$$I_E = (\beta + 1) I_B$$

$$= (0.1) \text{ m} (100)$$

$$= 10 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25\text{m}}{10\text{m}}$$

$$= 2.5\Omega$$

$$h_{ie} = h_{fe} \times r_e$$

$$A_V = \text{gain} = \frac{-h_{fe}}{h_{ie}} (R_C // R_L)$$

$$= - \frac{(R_C // R_L)}{r_e} = - \frac{0.5k // 0.5k}{2.5}$$

$$= - \frac{0.25k}{2.5}$$

$$= -100$$



14. Ans: (a)

Sol: $V_0 = -g_m [R_D \parallel R_L \parallel r_d]$

$$r_d \approx \infty$$

$$= -2m [10k \parallel 10k]$$

$$= -2m [5k]$$

$$= -10$$

15. Ans: (a)

Sol: $f'_L = \frac{f_L}{\sqrt{2^{\frac{1}{n}} - 1}}$

$$f'_L = \frac{20}{\sqrt{2^{1/3} - 1}} = 39.229$$

16. Ans: (a)

Sol: From DC analysis

$$V_B = \frac{11.4}{2} = 5.7 \text{ V}$$

$$V_B = V_{BE} + I_E R_E$$

$$5.7 = 0.7 + I_E 1k$$

$$5 \text{ mA} = I_E$$

$$r_e = \frac{V_T}{I_E} = \frac{25mV}{5mA} = 5 \Omega$$

$$\text{Let } r_0 = \infty$$

$$\text{Voltage gain} = -\frac{r_0 \parallel R_c}{r_e} = \frac{1k}{5} = -200$$

$$C_i = C_{oi} + C_{be} + C_{bc} [1 - A_v]$$


$$= 1 \text{ pF} + 1 \text{ pF} + 0.1 [1 + 200] \text{ pF}$$

$$= 2 \text{ pF} + 201 \text{ pF}$$

$$= 22.1 \text{ pF}$$

17. Ans: (b)

Sol: Equivalent circuit

 

$$V_{GS} = -V_0$$

$$I_0 = \frac{V_0}{R_s} + \frac{V_0}{r_d} + g_m V_{GS}$$

$$= V_0 \left[\frac{1}{R_s} + \frac{1}{r_d} + g_m \right]$$

$$\frac{V_0}{I_0} = \frac{1}{\frac{1}{R_s} + \frac{1}{r_d} + \frac{1}{1/g_m}}$$

$$= R_s \parallel r_d \parallel 1/g_m$$

$$= 2k \parallel 1/1m$$


$$= \frac{2 \times 1}{2 + 1} = \frac{2}{3} k$$

$$= 666.66 \Omega$$

18. Ans: (a)

Sol: DC analysis:

$$V_B = \frac{11.4}{2} = 5.7$$

 



$$I_B = \frac{5.7 - 0.7}{25k} = \frac{5}{25k} = 0.2 \text{ mA}$$

$$I_E = (1 + \beta) I_B = 100(0.2 \text{ mA}) \\ = 20 \text{ mA}$$

$$r_e = \frac{V_E}{I_E} = \frac{25 \text{ mV}}{20 \text{ mA}} = 1.25 \Omega$$

$$h_{ie} = \beta \times r_e = 1.25 \times 99 = 123.75$$

$$\text{Let } \omega_{Li} = \frac{1}{R_{in} \cdot C_{in}}$$

$$R_{in} = R_1 \parallel R_2 \parallel h_{ie} \\ = 50 \text{ k} \parallel 50 \text{ k} \parallel 123.75 \\ = 123$$

$$\omega_{Li} = \frac{1}{123 \times 100 \mu} = 81 \text{ rad/sec}$$

19. Ans: (a)

$$\text{Sol: } f_T = \frac{1}{2\pi r_e (C_{bc} + C_{be})}$$

DC analysis:

$$I_B = \frac{10.7 - 0.7}{4k}$$

$$= \frac{10}{4k} = 2.5 \text{ mA}$$

$$r_e = \frac{V_I}{I_E} = \frac{25 \text{ mV}}{2.5 \text{ mA}} = 10 \Omega$$

$$f_T = \frac{1}{2\pi(10)(2) \times 10^{-12}}$$

$$= \frac{1}{40\pi \times 10^{-12}}$$

$$= \frac{10^{12}}{40\pi} = 7.957 \text{ GHz}$$

20. Ans: (b)

$$\text{Sol: } R_{if} = \frac{R_i}{1 + AB} = \frac{20}{1 + (10)(0.9)} = 2 \Omega$$

21. Ans: (a)

Sol: Here the feedback element is R_2 and the sampling signal is part of the output voltage V_o . Hence voltage sampling feedback element is connected in series with the input hence voltage mixing.

The given amplifier is voltage series amplifier.

22. Ans: (a)

$$\text{Sol: } \beta = \frac{V_f}{V_o}$$

$$= \frac{R_2}{R_1 + R_2} = \frac{10}{20} = \frac{1}{2} = 0.5$$

$$A_f = \frac{A}{1 + A\beta} = \frac{18}{1 + 18(0.5)} = 1.8$$

23. Ans: (b)

Sol: The given amplifier is current amplifier. By using feedback, input resistance decreases and output resistance increases.

24. Ans: (b)

$$\text{Sol: } \omega_0 = \frac{1}{\sqrt{LC_{eq}}}$$

$$C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{900 \text{ p}}{100} = 9 \text{ pF}$$



$$= \frac{1}{\sqrt{1\mu 9p}}$$

$$= \frac{1}{\sqrt{9 \times 10^{-18}}}$$

$$= \frac{10^9}{3} \text{ rad/sec}$$

$$= 3.33 \times 10^8 \text{ rad/sec}$$

$$\beta = \frac{C_2}{C_1} = \frac{10}{90} = \frac{1}{9}$$

25. Ans: (b)

Sol:

1. Crystal oscillators were used whenever the greater stability of oscillations are required
2. RC oscillators are low frequency oscillators
3. LC oscillators are high frequency oscillators
4. In Hartley oscillator mutual inductance between two feedback inductors will effects the frequency of oscillation

26. Ans: (d)

Sol: (1) $f = \frac{1}{2\pi\sqrt{R_3 R_4 C_1 C_2}}$

(2) $\frac{R_2}{R_1} = \frac{R_3}{R_4} + \frac{C_2}{C_1}$


27. Ans: (d)

Sol: The deviation in the frequency of oscillation of oscillator is due to variation in

- (1) Circuit component
- (2) Transistor parameters
- (3) temperature
- (4) Supply voltage
- (5) load
- (6) Stray capacitance

28. Ans: (d)

Sol:

 

Applying KVL at inverting node

$$\frac{V_1 - V_0}{R_1} + \frac{V_1 - V_i - V_1}{2R_1} = 0$$

$$\frac{V_1 - V_0}{R_1} = \frac{V_i}{2R_1}$$

$$V_1 - V_0 = \frac{V_i}{2}$$

Applying KVL at non inverting node

$$\frac{V_1 + V_i - V_1}{2R_1} + \frac{V_1}{R_1} = 0$$

$$\frac{V_i}{2} = -V_1$$



$$\frac{-V_i}{2} - V_0 = \frac{V_i}{2}$$

$$\frac{-V_i}{2} - \frac{V_i}{2} = V_0$$

$$\frac{V_0}{V_i} = -1$$

29. Ans: (a)

Sol: $T = 2RC \ln \left[\frac{1+\beta}{1-\beta} \right]$

$$\beta = \frac{R_2}{R_1 + R_2} = \frac{1}{2} = 0.5$$

$$T = 2 \times 50 \text{ k} (0.01 \text{ } \mu\text{F}) \ln \left(\frac{1+0.5}{1-0.5} \right)$$


$$= 100 \text{ k} (0.01 \mu) \ln 3$$

$$= 10^{-3} \ln 3$$

$$f = \frac{1}{T} = \frac{1 \text{ k}}{\ln 3}$$

30. Ans: (d)

Sol:

 

Applying KVL at non inverting node

$$\frac{V_1 - 10}{R_1} + \frac{V_1 - 10}{R_1} + \frac{V_1}{R_1} = 0$$

$$V_1(3) = 20$$

$$V_1 = \frac{20}{3}$$

Applying inverting node


$$\frac{V_1 - 20}{R_1} + \frac{V_1 - 20}{R_1} + \frac{V_1 - V_0}{R_1} = 0$$

$$3V_1 - 40 = V_0$$

$$20 - 40 = -20$$

31. Ans: (a)

Sol:

 

$$V_A = V_B = 0$$

$$\frac{0 - V_1}{R_1} + \frac{0 - V_2}{R_2} = 0 \quad \dots\dots\dots (1)$$

$$\frac{V_2 - 0}{R_2} + \frac{V_2 - V_0}{R_3} + \frac{V_2 - 0}{R_4} = 0 \quad \dots\dots\dots (2)$$

$$V_1 R_2 = -V_2 R_1 \quad \dots\dots (3)$$

$$V_2 [R_3 R_4 + R_2 R_4 + R_2 R_3] = V_0 R_2 R_4$$

$$V_0 = V_2 \left(\frac{R_3}{R_2} + 1 + \frac{R_3}{R_4} \right) \quad \dots\dots\dots (4)$$


$$V_2 = -V_1 \cdot \frac{R_2}{R_1} \text{ sub in (4)}$$

$$V_0 = -\frac{V_1}{R_1} \left(R_2 + R_3 + \frac{R_2 R_3}{R_4} \right)$$

$$= \frac{- \left(R_2 + R_3 + \frac{R_2 R_3}{R_4} \right)}{R_1}$$



SHORT CUT

 

$$\text{Gain} = \frac{-\left(R_A + R_B + \frac{R_A R_B}{R_C}\right)}{R_D}$$

32. Ans: (a)

Sol: 1. Input resistance is infinity

2. Output resistance is zero

3. Input offset current is zero

4. Band width of the amplifier is infinite

5. CMRR should be infinite.

33. Ans: (b)

Sol: It acts as Miller circuit

Input capacitance $C_{in} = C(1 - A)$

Output capacitance $C_o = \frac{C(A - 1)}{A}$

34. Ans: (b)

Sol: $S.R = 2\pi f_{\max} V_{0\max}$


$$= \frac{2\pi \times 10^3}{2} \cdot 3$$

$$= 3\pi \times 10^3 \text{ V/sec}$$

$$= 3\pi \times 10^{-3} \text{ V/}\mu\text{sec}$$

35. Ans: (d)

Sol:

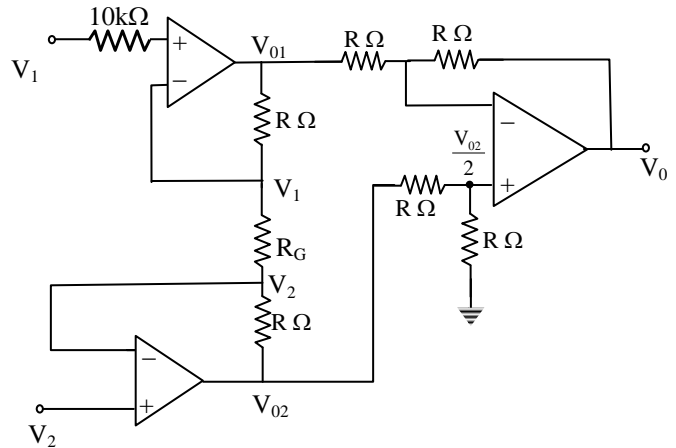

$$\frac{V_1 - V_{01}}{R} + \frac{V_1 - V_2}{R_G} = 0 \quad \dots\dots\dots (1)$$

$$\frac{V_2 - V_{02}}{R} + \frac{V_2 - V_1}{R_G} = 0 \quad \dots\dots\dots (2)$$

Eq. (1) – Eq. (2)

$$V_1 - V_2 - V_{01} + V_{02} + 2V_1 - 2V_2 = 0$$

$$3V_2 - 3V_1 = V_{02} - V_{01}$$

$$V_0 = -V_{01} + \frac{V_{02}}{2}(1+1)$$


$$= V_{02} - V_{01}$$

$$= 3(V_2 - V_1)$$

$$= 3(5 - 10) = -15$$

36. Ans: (b)

Sol:

 

$$V_1(s) = V_{in}(s) \frac{R}{R + 1/sc}$$



$$\frac{V_1(s) - V_0(s)}{R_x} + \frac{V_1(s) - V_{in}(s)}{R_x} = 0$$


$$2V_1(s) = V_0(s) + V_{in}(s)$$

$$V_{in}(s) \frac{2R}{R + \frac{1}{sc}} - V_{in}(s) = V_0(s)$$

$$H(s) = \frac{V_0(s)}{V_{in}(s)} = \frac{R - 1/sc}{R + \frac{1}{sc}}$$

 37. Ans: (c)


Sol: At $f = 0$ capacitors will be open circuited.



$$V_1 = \frac{R_3}{R_2 + R_3} \times V_{in}$$

$$V_0 = V_1 = \frac{R_3}{R_2 + R_3} \times V_{in}$$

 At $f = \infty$ capacitors will be acted like short circuited.



$$V_1 = \frac{R_3}{R_2 + R_3} \times V_{in}$$

$$V_0 = V_1 = \frac{R_3}{R_2 + R_3} \times V_{in}$$

So the given filter is the band stop filter.

38. Ans: (c)

Sol: Truth table of comparator:

A	B	A = B	A < B	A > B
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	1	0	0

$$X = A\bar{B} = A > B$$

$$Y = \bar{A}B = A < B$$

$$Z = A \odot B = A = B$$

\therefore It is a comparator

39. Ans: (d)

Sol: $f(A, B, C, D) = AB + \bar{B}\bar{C} + BD$

		$f(A, B, C, D)$				$\overline{f(A, B, C, D)}$			
AB	CD	00	01	11	10	00	01	11	10
00						1	1	1	1
01		1	1	1					1
11		1	1	1	1				
10						1	1	1	1

\therefore Number of minterms in $\overline{f(A, B, C, D)}$ is 9.



Launching
Spark Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ DELHI



Launching
Regular Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ BHOPAL & LUCKNOW



40 Ans: (c)

Sol: $f(A,B,C,D) = \Sigma m(1, 5, 7, 12, 13, 14) + d(3, 11, 15)$

CD \ AB	00	01	11	10
00		1	×	
01		1	1	
11	1	1	×	1
10			×	

$$f(A,B,C,D) = AB + \bar{A}\bar{D}$$

For the input 0011, $f = (0.0) + (1.1) = 1$

For the input 1011, $f = (1.0) + (0.1) = 0$

41. Ans: (c)

Sol: Minimization of Boolean expression is reducing complexity and cost of system. It reduces number of gates required for implementation and also number of inputs (fan-in) of gates.

42. Ans: (d)

Sol: A synchronous counter state changes in one Flipflop delay, if it is changing from one state to another state. The propagation delay is independent of number of bits.

\therefore The maximum time required is 10ns.

43. Ans: (c)

Sol: Synchronous counter will provide clock at a time to all flip flops. Hence it provides least delay.

44. Ans: (a)

Sol: It is mod 12 counter .

After 300 clock cycles

$$300 \% 12 = 0$$

So the state after 300 clock cycles is initial state only.

So $Q_3 Q_2 Q_1 Q_0$ state after 300 clock cycles is 0000.

45. Ans: (b)

Sol: It is a ring counter . So $D_3 = Q_0$, $D_2 = Q_3$, $D_1 = Q_2$, $D_0 = Q_1$

Q_3	Q_2	Q_1	Q_0
1	0	1	0
0	1	0	1
1	0	1	0

The modulus of counter is '2'


46. Ans: (d)

$$\begin{aligned} \text{Sol: } Z &= \bar{C}\bar{D}\bar{A}\bar{B} + \bar{C}D(\bar{A}B + AB) + CDAB \\ &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + AB\bar{C}D + ABCD \\ &= \Sigma m(0,5,13,15) \end{aligned}$$

 47. Ans: (c)

Sol: The circuit is SR flip flop with $S = \bar{Q}$ and $R = Q$.

So the output Q is complementing at every clock cycle





$$T_Q = 2T$$

$$f_Q = \frac{1}{2T} = \frac{f}{2}$$

$$= \frac{1\text{GHz}}{2} = 0.5\text{GHz}$$

48. Ans: (c)

$$\text{Sol: Resolution} = \frac{100 - 0}{2^6 - 1} = \frac{100}{63} \text{ rpm}$$

The number of steps required for 50 speed is

$$= \frac{50}{100/63} \approx 32_{10}$$

$$= 100000_2$$

49. Ans: (b)

Sol: A dual slope ADC integrates an unknown input voltage (V_{in}) for a fixed amount of time (T_{int}), then de-integrates (T_{De-int}) using a known reference voltage (V_{REF}) for a variable amount of time.

T_{INT} is fixed

$$T_{DE-int} \propto \frac{V_{IN}}{V_{REF}}$$

Any error introduced by a component value during the integrate cycle will be cancelled out during the de-integrate phase.

\therefore De-integration time period is variable and depends on number of pulses counted during 1st integration.

50. Ans: (B)


$$\text{Sol: Resolution} = 0.01\% = \frac{0.01}{100}$$

$$= \frac{1}{10,000} = \frac{1}{2^n}$$

Minimum number of bits = 14

51. Ans: (b)

Sol: Gray to Binary circuit

 

$$t_{tot} = (N - 1) t_{pd}$$

$$= 3 t_{pd}$$

$$= 3 \times 2 \text{ nsec}$$

$$= 6\text{nsec}$$

52. Ans: (a)

Sol: MVI B, 00H; [B] = 00H

MVI C, 00H; [C] = 00H

LOOP: DCR C ; [C] = FFH

JNZ LOOP ; Z-flag = 1 so again

loop executes till [C] = 00H, i.e 256 times

DCR B ; [B] = FFH

JNZ LOOP ; zero flag = 1 so

again loop executes

For [B] = FFH \rightarrow 256 times

For [B] = FEH \rightarrow 256 times



For [B] = FDH \rightarrow 256 times

⋮

For [B] = 00H \rightarrow 256 times

\therefore Loop executes for 256×256 times

53. Ans: (b)

Sol: XRA A ; [A] = 00H, CY = 0

ACI 05H ; [A] = [A] + CY + 05H
= 05H = 00000101

RLC ; [A] = 00001010 = 0AH, CY = 0

MOV B, A ; [B] = 0AH

RLC ; [A] = 00010100, CY = 0

RLC ; [A] = 00101000, CY = 0

ADD B ; [A] \leftarrow [A] + [B]

0 0 1 0 1 0 0 0

0 0 0 0 1 0 1 0

+

0 0 1 1 0 0 1 0 = 32H

MOV C, A ; [C] = 32H

54. Ans: (b)

Sol: The time delay for JNZ is 10T if it satisfies the condition otherwise it is 7T.

LOOP executes till the content of C register becomes 0, i.e., for 5 times.

For the first four times JNZ condition will not satisfy, so this instruction will take 10T states.

But during 5th time, JNZ satisfies, which takes 7T states.

Delay = $T_O + T_L - 3T$

= $14T + (5 \times 26T) - 3T = 141T$

55. Ans: (c)

Sol: 1. READY is active high signal. When it is high, it indicates that the device is ready to transfer data. When it is low, it indicates wait state.

2. ALE is high only during T1. when ALE goes low, the address is saved and AD7-AD0 lines can be used for their purpose as the bi-directional data lines.

\therefore Statements (1) and (2) are false.

56. Ans: (c)

Sol: DSBSC Signal

$S(t) = m(t) \cdot \cos \omega_c t$

if $m(t)$ signal crosses zero i.e. $m(t)$ voltage changes from +ve to -ve

for $m(t) > 0$

assume $S(t) = k \cos \omega_c t$ (here k is positive)

for $m(t) < 0$

$S(t) = -k \cos \omega_c t$

= $k \cos (\omega_c t + \pi)$

($\because \cos(\pi + \theta) = -\cos \theta$)

Therefore the modulated wave undergoes phase reversal (π -radians) whenever $m(t)$ (modulating signal) crosses zero.



57. Ans: (b)

Sol: TRAP is represented as RST 4.5

\therefore Vector location = $4.5 \times 8 = 36 D$

In Hexadecimal, $36 D = 24 H$

58. Ans (b)

Sol: Accumulator = 11010100 (-43_{10})

RLC ---- 10101001 cy = 1

RRC ---- 11010100 cy = 1

RAL----- 10101001(-86_{10}) cy = 1

59. Ans: (b)

Sol: Hardware interrupts in decreasing order of priority:

TRAP

RST 7.5

RST 6.5

RST 5.5

INTR

60. Ans: (d)

Sol: HL register is primary data pointer register used to hold address of a memory location in data RAM.

61. Ans: (b)

Sol: For Compare instruction execution, 8085's ALU performs subtraction operation but result is not saved into accumulator.

\therefore Accumulator is unaltered.

62. Ans: (b)

Sol: The DSB-SC signal is multiplied with carrier of phase angle θ .

$$\Rightarrow [m(t)\cos\omega_c t] \cos(\omega_c t + \theta)$$

$$= \frac{m(t)}{2} [\cos(2\omega_c t + \theta) + \cos\theta]$$

The output of the coherent detector is

$$\frac{m(t)}{2} \cos\theta$$

When $\theta = 60^\circ$, then output is $\frac{m(t)}{4}$

63. Ans: (c)

$$\text{Sol: } \beta_f = \frac{\Delta f}{f_m}$$

Carrier swing $2\Delta f = 100 \text{ kHz}$

$$\Rightarrow \Delta f = 50 \text{ kHz}$$

$$f_m = 8 \text{ kHz}$$

$$\beta_f = \frac{50k}{8k} = 6.25$$

64. Ans: (b)

Sol: Too high IF value would result in poor selectivity, which implies poor adjacent channel rejection. Assume that IF instead of standard 455 kHz if a very high value of 2MHz is considered with bandwidth either 10 kHz or less than 10 kHz than we require very sharp cut-off filters which also increases the cost of the receiver.

Design of such filters is very complex.



65. Ans: (a)

Sol: If the input to the quantizer 0^+ the output voltage $+5V$ and if the input is 0^- , the output is $-5V$. So, the quantization error varies from $-5V$ to $+5V$.

66. Ans: (b)

Sol: Bandwidth is decreases by $2/3$ in VSB, but bandwidth is decreases by $1/2$ in SSB. So option 1 is wrong. And in VSB it is a condition that it should avoids phase distortion at low frequencies.

67. Ans: (b)

Sol:

1. Slope overload distortion occurs in DM.
2. Sampling frequency in DM is far greater than sampling frequency in PCM. So DM has larger bandwidth.
3. DM has simple circuitry.
4. DM has poor performance compared to PCM.

68. Ans: (b)

Sol: Carrier Amplitude $A_c = 6$;

Average power:

$$P_{avg} = \frac{A_c^2}{2R}; R = 1\Omega$$

$$P_{avg} = \frac{A_c^2}{2R} = \frac{6^2}{2} = 18 W$$

69. Ans: (d)

Sol: DMA is a process where the data is transferred between two peripherals directly without the involvement of the microprocessor.

\therefore Statement (1) is false

70. Ans: (a)


Sol: Power of angle modulated signal depends only on the amplitude of the carrier. So, both statement I, statement II are true and statement II is correct explanation of statement I.

71. Ans: (d)

Sol: Both DSB & SSB have identical noise performance. Statement-I is false and statement-II is correct.

72. Ans: (b)

Sol: Demultiplexer using AND gates

 



Where A, B are control inputs

O_0, O_1, O_2, O_3 are outputs

A demultiplexer can be used as decoder and demultiplexer can be built by AND gates.

Statement (I) is true. Statement (II) is also true, but not giving correct explanation for I

73. Ans: (b)

Sol: Statement (I): At low frequency the gain of R-C coupled amplifier decreases due to the finite impedance of coupling, bypass capacitances.

Statement (II): Parasitic capacitance of active device, winding capacitances effect the gain of the system at high frequency.

74. Ans: (c)

Sol: As the temperature \uparrow

1. Depletion layers width \downarrow , channel width \uparrow , Hence current \uparrow .
2. Carrier mobility \downarrow , Resistance of channel \uparrow , current \downarrow both 1 & 2 are opposite effects to each other.

75. Ans: (a)

Sol: Statement (I): Compared to JET and BJT MOSFET has high input impedance.

Statement (II): Due to SiO_2 layer between gate and channel, it has high input impedance.

OUR **GATE** - 2018 TOP RANKERS

AIR 1		AIR 1		AIR 1		AIR 1		AIR 1	
									
AKASH CHOUDHARY CE		ADARSH ADHIKARY EC		NANITA KALRA CSIT		NAMAN JAGDISH IN			
AIR 2		AIR 2		AIR 2		AIR 3		AIR 3	
									
JIJO JOSE EC		ADARSH KUMAR IN		NAIRUL HAQUE IN		PANKAJ MONDAL EE		NAVEET NAIR EC	
AIR 3		AIR 3		AIR 3		AIR 3		AIR 4	
									
SOUVIK SAHA CE		SAHIL PANDEY CSIT		DIVYANSHU PI		ALOK SHAKTI CE			
AIR 4		AIR 4		AIR 4		AIR 5		AIR 5	
									
NIRAJ AHIRAD ME		ADITYA SHRIVASTAVA EE		RANESH KAMILLA IN		ANIT SHAKTI IN		ARJUN AGARWAL CE	
AIR 5		AIR 6		AIR 6		AIR 6		AIR 7	
									
ANMOL SALPASI PI		SIDDHI BHUSHAN EC		NITIN PRASAD CSIT		NISHA SHRIVASTAVA IN		NISHANT PURI IN	
AIR 7		AIR 7		AIR 7		AIR 8		AIR 8	
									
SHREYA ALVA CSIT		PAARTH GUPTA CSIT		GAUTHAM KUMAR PI		NISHANT SHRIVASTAVA PI		PRAKASH THAKUR EE	
AIR 8		AIR 8		AIR 8		AIR 9		AIR 9	
									
ZAHERE KAPIL ME		TARUN GUPTA IN		VIKRAM SINGH CE		NISHANT SHRIVASTAVA CE			
AIR 9		AIR 9		AIR 9		AIR 9		AIR 10	
									
SAIDEEP C EC		CHANDRASEKAR M CSIT		D. AJAY KUMAR EE		AMAN SINGH ME		SHREYA PANDEY IN	
AIR 10		AIR 10		AIR 10		AIR 10		AIR 10	
									
GHANSHYAM PI		DHEERAJ KUMAR EC		VIPIN CHANDRA IN		ANIKET MISHRA IN			
E TOP 10 TOP 100		E TOP 10 TOP 100		E TOP 10 TOP 100		C TOP 10 TOP 100		N TOP 10 TOP 100	
9 74		7 69		7 42		4 54		6 31	
I TOP 10 TOP 100		P TOP 10 TOP 100		P TOP 10 TOP 100		P TOP 10 TOP 100		P TOP 10 TOP 100	
11 78		5 50							

OUR **ESE** - 2017 TOP RANKERS

AIR 1  NANIT JAIN CE	AIR 2  SUDHANSHU E&T	AIR 2  PRAVIND SINGH CE	AIR 2  PREETI KUMAR EE	AIR 3  ANKIT CE	AIR 3  SAURABH ME	AIR 3  SUMAN CHAKRABORTY EE	AIR 3  A SRINIVASULU EE	AIR 4  AMIT KUMAR RAY ME
AIR 4  HARSHIT KUMAR EE	AIR 5  NIKHIL KUMAR EE	AIR 5  ANURAG GAUTAM E&T	AIR 6  RISHABH D CE	AIR 6  ANKUR GUPTA ME	AIR 6  DUSHYANT SINGH EE	AIR 6  SUDHANSHU E&T	AIR 7  DHURUV JHA ME	AIR 7  D PAVAN KUMAR E&T
AIR 8  ADITYA SINGH CE	AIR 8  APOORVA GUPTA EE	AIR 8  DEEPAALI BHATNAGAR E&T	AIR 9  NISHANT CE	AIR 9  ACHARAJ GUPTA ME	AIR 9  KIRAN BADU K EE	AIR 9  ANISH E&T	AIR 10  AJAY DUBEY CE	AIR 10  UNISH E&T
TOTAL SELECTIONS		196		C E 86	M E 44	E E 36	E & T 30	



ACE
Engineering Academy
Leading Institute for ESE/GATE/PSUs

43rd
ALL INDIA 1st RANKS IN GATE

7th
ALL INDIA 1st RANKS IN ESE