



ACE

Engineering Academy

TEST ID: 303

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

ESE- 2019 (Prelims) - Offline Test Series

Test-5


ELECTRICAL ENGINEERING

SUBJECT: Control Systems and Power Electronics

SOLUTIONS

01. Ans: (a)

Sol:

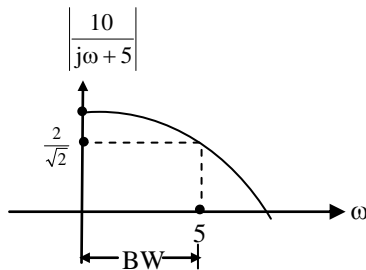

Bandwidth = 5 rad/sec

02. Ans: (d)

Sol: From option (d)

No poles and zeros lies in the right side of s-plane.

03. Ans: (c)

Sol:
$$TF = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$

$$A = \left| \frac{1}{j\omega + 1} \right| = \frac{1}{\sqrt{\omega^2 + 1}} \Big|_{\omega=1} = \frac{1}{\sqrt{2}}$$

$$\phi = \angle \frac{1}{j\omega + 1} = -\tan^{-1} \omega \Big|_{\omega=1} = -45^\circ$$


$$\therefore \text{Output } A \sin(t+\phi) = \frac{1}{\sqrt{2}} \sin(t - 45^\circ)$$

04. Ans: (c)

Sol:
$$CE = 1 + \frac{k(s+5)}{s(s+3)(s+7)} = 0$$

$$s(s^2 + 10s + 21) + k(s+5) = 0$$

$$s^3 + 10s^2 + (21+k)s + 5k = 0$$

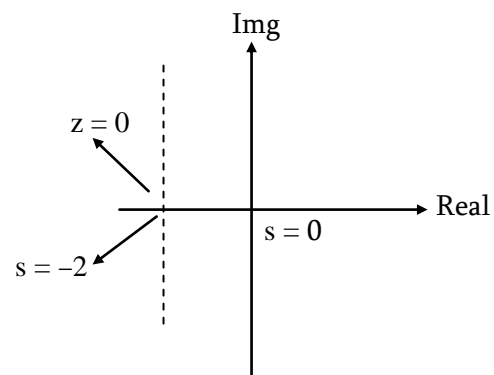



Substitute $s = (z-2)$

$$(z-2)^3 + 10(z-2)^2 + (21+k)(z-2) + 5k = 0$$

$$z^3 - 6z^2 + 12z - 8 + 10z^2 - 40z + 40 + 21z + kz - 42 - 2k + 5k = 0$$

$$z^3 + 4z^2 + (k-7)z + 3k - 10 = 0$$

z^3	1	$k-7$
z^2	4	$3k-10$
z^1	$\frac{4(K-7)-(3K-10)}{4}$	
z^0	$3k-10$	

$$\frac{4(K-7)-(3K-10)}{4} > 0 \Rightarrow k > 18$$

$$\text{And } (3K-10) > 0 \Rightarrow k > \frac{10}{3}$$

\therefore For $k > 18$ the closed loop poles lie left side of $s = -2$

05. Ans: (a)

$$\text{Sol: } M_r = \frac{2}{2\zeta\sqrt{1-\zeta^2}} = 5 \dots\dots 0 \leq \zeta \leq 0.707$$

Solve

$$\zeta = 0.2 \text{ and } \zeta = 0.97$$

$\therefore \zeta = 0.2$ is valid

06. Ans: (b)

Sol: Routh Hurwitz \rightarrow Stability

W.R.Evans \rightarrow Root locus

Bode \rightarrow Asymptotic

Nyquist \rightarrow Polar plot

07. Ans: (b)

Sol: No. of forward paths = 1

No. of loops = 2

Two non touching loops = 1

$$\begin{aligned} \text{TF} &= \frac{G \times 4 \left(\frac{1}{4}\right)}{1 - (-H_1 - H_2) + H_1 H_2} \\ &= \frac{G}{1 + H_1 + H_2 + H_1 H_2} \end{aligned}$$

08. Ans: (b)

Sol: As k increases, ζ decreases ($\because k \propto \frac{1}{\zeta^2}$)

If ζ decreases, rise time decreases. Hence bandwidth increases (\because Bandwidth $\propto \frac{1}{\text{rise time}}$)

If ζ decreases, ω_d increases ($\because \omega_d = \omega_n \sqrt{1-\zeta^2}$)

\therefore Oscillatory nature of response increases.

As k increases ζ decreases \Rightarrow stability decreases.

09. Ans: (c)

Sol:

$$\begin{aligned} \frac{C(s)}{R(s)} &= \frac{G_1 G_2}{1 - G_1 G_2} (G_3 - X) \\ &= \frac{G_1 G_2 G_3}{1 - G_1 G_2} - \frac{X G_1 G_2}{1 - G_1 G_2} \end{aligned}$$



$$\frac{C(s)}{R(s)} = \frac{G_1 G_2 G_3 - 1 + G_1 G_2}{1 - G_1 G_2}$$

10. Ans: (c)

Sol: CLTF is

$$\frac{C(s)}{R(s)} = \frac{\frac{20}{s^2}}{1 + \frac{20}{s^2}(s+5)} = \frac{20}{s^2 + 20s + 100}$$

$$C(s) = \frac{20R(s)}{s^2 + 20s + 100} = \frac{20}{s(s^2 + 20s + 100)}$$

Steady state

$$\text{output } c(\infty) = \lim_{s \rightarrow 0} s C(s)$$

$$= \lim_{s \rightarrow 0} s \frac{20}{s(s^2 + 20s + 100)} = \frac{20}{100} = 0.2$$

11. Ans: (c)

Sol: Output is more sensitive to feedback path parameter changes than the forward path parameter changes.

12. Ans: (a)

$$\text{Sol: OLTF} = \frac{\text{CLTF}}{1 - \text{CLTF}} = \frac{1}{10s}$$

$$k_v = \lim_{s \rightarrow 0} sG(s) = \frac{1}{10}$$

$$\text{Steady state error } e_{ss} = \frac{1}{k_v} = 10$$

13. Ans: (b)

$$\text{Sol: } M_p = \frac{11.63 - 10}{10} \times 100 = 16.3\%$$

$$\text{i.e } \zeta = 0.5$$

$$\text{settling time } t_s (\pm 2\% \text{ tolerance}) = \frac{4}{\zeta \omega_n} = 4$$

$$\zeta \omega_n = 1$$

$$\omega_n = 2$$

$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$

$$= 2\sqrt{1 - 0.5^2}$$

$$= 1.73 \text{ rad/sec}$$

14. Ans: (a)

Sol: G(s) is type-1 system

By introducing integral controller

It becomes type-2 system

And for the step input to type-2 system steady state error is zero.

15. Ans: (a)

$$\text{Sol: C.E} = s^3 + 11s^2 + 10s + 2k = 0$$

$$110 = 2k$$

$$k_{\text{marginal}} = 55$$

$$11s^2 + 110 = 0$$

$$s = \pm j10$$

$$\omega_n = \sqrt{10} = 3.16 \text{ rad/sec}$$



SHORT TERM BATCHES

SUMMER

SHORT TERM BATCHES

GATE+PSUs - 2020

Admissions Open From 14th NOV 2018

HYDERABAD

29th April | 06th May | 11th May

18th May | 26th May | 02nd June 2019

DELHI

11th May | 23rd May 2019

Start Early.. Gain Surely...

EARLY BIRD OFFER :

Register on or Before 31st December 2018 : 5000/- Off | Register on or Before 31st March 2019 : 3000/- Off



TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2019

Date of Exam : 20th January 2019

Last Date to Apply : 31st December 2018

Highlights :

- Get real-time experience of **GATE-2019** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post GATE guidance sessions by experts.
- Encouraging awards for **GATE-2019** toppers.



16. Ans: (c)

Sol: $G(s) = \frac{K(s+2)^3}{s^2}$

Two poles at the origin

∴ Type 2 system

CE = 1 + G(s) = 0

$s^2 + K(s+2)^3 = 0$, three roots

∴ order is '3'.

17. Ans: (d)

Sol: Ex: Consider 2nd order system $as^2 + bs + c = 0$

In R-H tabulation,

$$\begin{array}{c|cc} s^2 & a & c \\ s^1 & b & \\ s^0 & c & \end{array}$$

For all positive values of a, b, c system is stable

18. Ans: (b)

Sol: R-H tabulation

$$\begin{array}{c|ccc} s^4 & 1 & 11 & 18 \\ s^3 & 2 & 18 & \\ s^2 & 2 & 18 & \\ s^1 & 0(2) & & \\ s^0 & 18 & & \end{array}$$

No sign changes

2- Imaginary poles

2-left side poles

19. Ans: (c)

Sol: $(TF)_{PD} = k_p (1+T_D s)$

One zero at $-\frac{1}{T_D}$

20. Ans: (a)


Sol: $(TF)_{PI} = k_p \left(1 + \frac{1}{T_I s}\right)$
 $= \frac{k_p}{T_I} \left(\frac{1 + T_I s}{s}\right)$

Pole: $s = 0$

Zero: $s = -\frac{1}{T_I}$

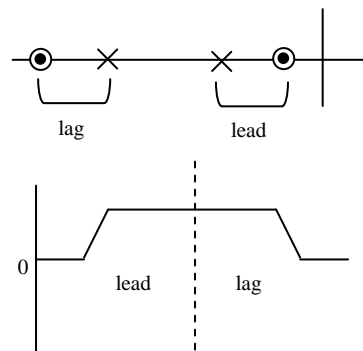21. Ans: (c)

Sol: Pole zero plot of lead-lag compensator



22. Ans: (c)

Sol: $K_p = \lim_{s \rightarrow 0} \frac{K}{s+A} = \frac{K}{A}$

$e_{ss} = \frac{1}{1+K_p} = \frac{1}{1+\frac{K}{A}} = \frac{A}{K+A}$

$S_K^{e_{ss}} = \frac{\partial e_{ss}}{\partial K} \frac{K}{e_{ss}} = \frac{\partial}{\partial K} \left[\frac{A}{K+A} \right] \frac{K}{e_{ss}}$



$$= \frac{A(-1)}{(K+A)^2} \frac{K}{\left(\frac{A}{K+A}\right)}$$

$$S_K^{e_{ss}} = \frac{-K}{(K+A)}$$

23. Ans: (a)

Sol: It is a lead compensator

Transfer function of lead compensator is

$$G_C(s) = \frac{(1+aTs)}{(1+Ts)} \quad \text{where } (a > 1)$$

Maximum phase angle lead provided by the compensator is

$$\phi_m = \sin^{-1} \left(\frac{a-1}{a+1} \right) \quad (a > 1)$$

From above transfer function, $T = 1$, $aT = 3$,

$$\therefore a = 3$$

$$\phi_m = \sin^{-1} \left(\frac{3-1}{3+1} \right) = \sin^{-1} \left(\frac{1}{2} \right) = 30^\circ$$

24. Ans: (b)

Sol: By using Laplace Transform on both the sides

$$(s^3 + 4s^2 + 5s + 2)Y(s) = (s+1)X(s)$$

$$\frac{Y(s)}{X(s)} = \frac{(s+1)}{s^3 + 4s^2 + 5s + 2}$$

$$\begin{array}{l|ll} s^3 & 1 & 5 \\ s^2 & 4 & 2 \end{array}$$

$$\begin{array}{l|ll} s^1 & 18/4 & 0 \\ s^0 & 2 & \end{array}$$

Number of sign changes = 0

\therefore All the three poles are in LHP.

25. Ans: (b)

Sol: System is critically damped at A and B

26. Ans: (a)

Sol: Number of forward paths = 2

Number of loops = 3

There is no two non touching loops

27. Ans: (b)

Sol: Two poles at origin and one pole at $s = -T$

$$\therefore \text{Loop transfer function} = \frac{k}{s^2(s+T)}$$

28. Ans: (b)

Sol: System will not oscillations when $\zeta \geq 1$.

29. Ans: (d)

$$\text{Sol: } \left| \frac{k}{s} \right|_{\omega=1} = 36\text{dB}$$

$$\frac{k}{\omega} = 2^6$$

$$k = 2^6 (\omega)$$

$$k = 2^6 = 64$$

$$\therefore K_v = k = 64$$



30. Ans: (c)

Sol: Given $A = 10^3$

$$dA = 200$$

$$\beta = 0.4\%$$

$$A_f = \frac{A}{1 + \beta A} = \frac{1000}{1 + \frac{4}{1000} \times 1000}$$

$$= \frac{1000}{5}$$

$$A_f = 200$$

% change in gain of feedback amplifier $A_f =$

$$\left(\frac{1}{1 + A\beta} \right) (\% \text{ change in } A)$$

$$= \frac{1}{5} \times \frac{200}{10^3} \times 100$$

$$= 4$$

31. Ans: (c)

Sol: $2k > -1 \Rightarrow k > \frac{-1}{2}$

$$\text{and } \frac{k}{5} < 1 \Rightarrow k < 5$$

$$\therefore \text{Range } -\frac{1}{2} < k < 5$$

32. Ans: (d)

Sol: CE = $s^2 + 0.5s + k = 0$

$$\text{Compare with } s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$2\zeta\omega_n = 0.5$$

$$\omega_n = \frac{1}{4}$$

$$k = \left(\frac{1}{4} \right)^2 = \frac{1}{16}$$

$$= 0.0625$$

33. Ans: (a)

Sol: $\frac{dk}{ds} = 0 \Rightarrow \frac{d}{ds} [s^2 + 2s] = 0$

$$\Rightarrow 2s + 2 = 0$$

$$\therefore s = -1$$

Breakaway point is $s = -1$.

34. Ans: (a)

Sol: CE = $|sI - A| = 0$

$$\begin{vmatrix} s-2 & -1 \\ -4 & s-5 \end{vmatrix} = 0$$

$$(s-2)(s-5) - 4 = 0$$

$$s^2 - 7s + 10 - 4 = 0$$

$$s^2 - 7s + 6 = 0$$

$$(s-6)(s-1) = 0$$

$$s = 1, 6$$

Poles of system are 1, 6.

35. Ans: (b)

Sol: By applying Gilbert's test, X_1 is not controllable

36. Ans: (b)

Sol: TF = $C[SI - A]^{-1}B$

$$sI - A = \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 0 & 1 \\ 4 & 3 \end{bmatrix}$$



$$= \begin{bmatrix} s & -1 \\ -4 & s-3 \end{bmatrix}$$

$$(sI-A)^{-1} = \frac{1}{s(s-3)-4} \begin{bmatrix} s-3 & 1 \\ 4 & s \end{bmatrix}$$

$$TF = [1 \quad 0] \frac{1}{s(s-3)-4} \begin{bmatrix} s-3 & 1 \\ 4 & s \end{bmatrix} \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$TF = \frac{2}{s^2 - 3s - 4}$$

37. Ans: (a)

Sol: As inductance is added to the load, the current waveform is improved; i.e., waveform becomes smooth. So, the form factor decreases and as a waveform higher average on state current I_{rms} can be handled by the device.

38. Ans: (b)

Sol: Without the application of gate currents the thyristor can be turned ON by applying peak working off state forward voltage (V_{DWM}).

39. Ans: (a)

Sol: In the figure, the voltage across device decreases and current increases from zero. So, it is turn ON of device.

$$E = \int V(t).i(t)dt$$

From ($0 < t < t_1$)

$$E_1 = \int_0^{t_1} (V)I \left(\frac{t}{t_1} \right) dt$$

$$= \left(\frac{VI}{t_1} \right) \int_0^{t_1} t dt$$

$$= \left(\frac{VI}{t_1} \right) \left(\frac{t_1^2}{2} \right) = \frac{VI t_1}{2}$$

From $t_1 < t < t_1 + t_2$ (or) $0 < t' < t_2$

$$I(t') = I; \quad v(t') = V(1 - t'/t_2)$$

$$E_2 = \int_0^{t_2} V(t).i(t)dt$$

$$= \int_0^{t_2} V \left(1 - \frac{t'}{t_2} \right) I dt'$$

$$= (VI) \left[t_2 - \left(\frac{1}{t_2} \right) \cdot \frac{t_2^2}{2} \right]$$

$$= \left(\frac{VI}{2} \right) \cdot t_2$$

$$\therefore E = E_1 + E_2 = \left(\frac{VI}{2} \right) (t_1 + t_2)$$


40. Ans: (c)

Sol: While turning off an SCR, as diode is connected in anti parallel, during reverse recovery the diode turn on and negative voltage of 0.7 V appears across SCR. So, because of negative voltage reverse recovery happens much faster and turn off time is decreased. So, turn off power loss is decreased. Similarly due to this negative voltage while turning on it takes more time.



41. Ans: (a)

Sol:

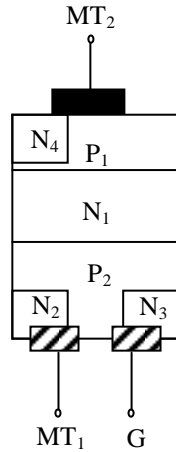

The above figure is the structure of TRIAC and it obeys all the above statements.

42. Ans: (a)

Sol: $t_{on} = 30 \mu s$;

$$T = \frac{1}{f} = \frac{1}{2.5} \times 10^{-3} = 400 \mu s$$

$$\frac{\text{mark}}{\text{spaceratio}} = \frac{T_{on}}{T_{off}} = 1$$

$$\Rightarrow D = \frac{T_{on}}{T_{on} + T_{off}} = \frac{1}{2}$$

$$\therefore \text{Pulse is given for } T_{on} = \left(\frac{1}{2}\right)(400) = 200$$

$$\mu s > t_{on}$$

\therefore Thyristor is ON.

43. Ans: (a)

Sol: $V_T = 500 \text{ V}$, $I_T = 75 \text{ A}$

$V = 7.5 \text{ kV}$, $I = 1 \text{ kA}$

$$\eta = 86\% = 0.86 = \frac{V}{(n) \times V_T}$$

$$\Rightarrow n = \frac{7.5 \times 1000}{0.86 \times 500} = 18$$

$$n = \frac{I}{\eta \times I_T} = \frac{1000}{0.86 \times 75} = 16$$

44. Ans: (d)

Sol: Base emitter junction is a normal p-n junction. When p-n junction is reverse biased, width of depletion region increases. Width of depletion region is directly proportional to reverse voltage. Capacitance of p-n junction depends on depletion region width. Therefore base emitter junction can be represented as voltage dependent capacitor.

45. Ans. (b)

Sol: $V_s = 500 \text{ V}$; $\frac{dV}{dt} = 200 \text{ V}/\mu s$;

$$\frac{di}{dt} = 60 \text{ A}/\mu s; \quad \zeta = 0.5$$

$$\left(\frac{dV}{dt}\right) = R \left(\frac{di}{dt}\right)$$

$$\Rightarrow R = \frac{200}{60} = \frac{10}{3} = 3.33 \Omega$$

$$V_s = L \left(\frac{di}{dt}\right)$$

$$\Rightarrow L = \frac{500}{60} \mu H = 8.33 \mu H$$





$$R_s = 2\zeta \sqrt{\frac{L}{C_s}}$$

$$\Rightarrow C_s = \left(\frac{2\zeta}{R_s}\right)^2 L = \left(\frac{2 \times 0.5}{\left(\frac{10}{3}\right)}\right)^2 \times \left(\frac{25}{3}\right) \mu\text{F}$$

$$= 0.75 \mu\text{F}$$

46. Ans: (a)

Sol:

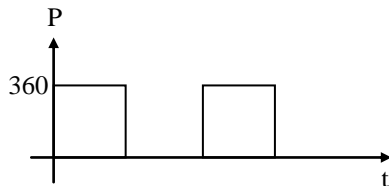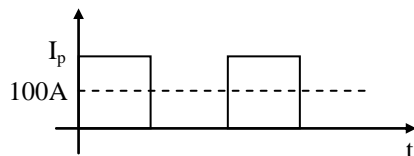

$$I_{\text{avg}} = 100 \text{ A};$$

$$I_{\text{avg}} = I_p (D) = I_p (1/2)$$

$$\Rightarrow I_p = 200 \text{ A}$$

From graph at $I_p = 200 \text{ A}$, $V_t = 1.8 \text{ V}$

$$\therefore P(t) = V(t) \cdot i(t)$$

$$= 200 \times (1.8) = 360 \text{ W}$$

$$P(t) = \begin{cases} 360 \text{ W}; & 0 < t < T/2 \\ 0; & T/2 < t < T \end{cases}$$

$$\therefore P_{\text{avg}} = (360) \cdot (1/2) = 180 \text{ W}$$

47. Ans: (d)

Sol: Load is combination of R and C in parallel

$$i(t) = \frac{V_m \sin \omega t}{R} + C \frac{dv}{dt}$$

$$i(t) = \frac{V_m \sin \omega t}{R} + C \cdot V_m \omega \cos \omega t$$

As 'C' is large, the above waveform is peaky in nature at positive half of input voltage.

48. Ans: (b)

Sol: If the inductance of the load is increased current waveform becomes smooth and ripple content decreases. If resistance of load is increased, the load current decreases, ripple content increases and if inductance is very small, there is a possibility of discontinuity.

49. Ans: (b)

Sol: For a 3 pulse rectifier $PIV = V_{m1} = 1000 \text{ V}$

For a full bridge rectifier $PIV = V_{m1} = 1000 \text{ V}$

For a midpoint 6 pulse rectifier $PIV = 2 V_{mp}$

$$= \frac{2 \times 1000}{\sqrt{3}} = 1155 \text{ V}$$

50. Ans: (d)

$$\text{Sol: } V_0 = \frac{3V_{m1}}{\pi} \cos \alpha = 200 \quad (\alpha = 0^\circ)$$

$$\Rightarrow \frac{3V_{m1}}{\pi} = 200$$



$$V_0 = \frac{1}{\left(\frac{\pi}{3}\right)^{\frac{\pi}{3} + \alpha}} \int_{\frac{\pi}{3} + \alpha}^{\pi} V_m \sin \omega t d\omega t$$

$$= \frac{3V_{m1}}{\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{3} \right) \right] \quad (\text{R-load})$$

$$V_0 = 200 [1 + \cos(150^\circ)]$$

$$= 200 [1 - \sqrt{3}/2]$$

$$= 200 - 100\sqrt{3}$$

$$= 26.8 \text{ V}$$

51. Ans: (b)

Sol: For $\alpha = 0^\circ$, the thyristor 'T₁' conducts from 30° to 150° , in a 3-phase converter, so, for firing angle ' α ', the thyristor conducts from $30 + \alpha$ to $150 + \alpha$.

So, ' α ' can be varied from 0 to 150° . But after 150° , as it is 'R'-load the thyristor will never conduct.

So, $0 < \alpha < 150^\circ$.

52. Ans: (c)

$$\text{Sol: } I_0 = \frac{1}{2\pi R} \int_0^{\pi - \theta} (V_m \sin \omega t - E) d\omega t$$

$$= \frac{1}{2\pi R} [2V_m \cos \theta - E(\pi - 2\theta)]$$

$$V_m \sin \theta = E$$

$$\Rightarrow \sin \theta = \frac{50}{100} = \frac{1}{2} \Rightarrow \theta = \frac{\pi}{6} = 30^\circ$$

$$\Rightarrow I_0 = \frac{1}{(2\pi)(10)} [2 \times (100) \left(\frac{\sqrt{3}}{2}\right) - E(2\pi/3)]$$

$$= \frac{100\sqrt{3}}{20\pi} - \frac{(50)(2\pi)}{(20)3}$$

$$= \frac{5\sqrt{3}}{\pi} - \frac{5}{3}$$

$$= 1.09 \text{ A}$$


53. Ans: (c)

Sol: By using a free wheeling diode, the output voltage of the circuit increases. So, power factor also increases.

$$\text{Input power factor} = \frac{V_0 \cdot I_0}{V_s \cdot I_s}$$

54. Ans: (b)

Sol:

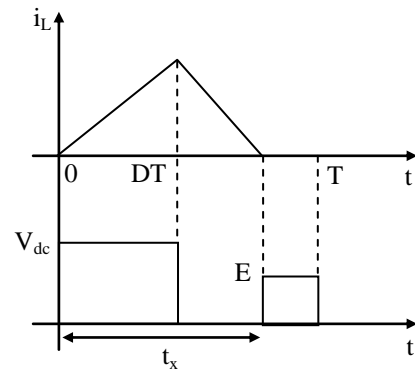

$$V_0 = \frac{DTV_{dc} + E(T - t_x)}{T}$$

$$V_0 = DV_{dc} + \left(1 - \frac{t_x}{T}\right)E$$



Launching
Spark Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ DELHI



Launching
Regular Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ BHOPAL & LUCKNOW



55 Ans: (d)

Sol: TRC means time ratio control.

$$f = 2 \text{ kHz}; T = 0.5 \text{ ms}$$

$$D = \frac{V_o}{V_{in}} = \frac{170}{220} = \frac{17}{22};$$

$$T_{on} = D.T$$

$$= \left(\frac{17}{22}\right) \times (0.5) = 0.386 \text{ ms.}$$

56. Ans: (c)

Sol: Conduction time = $\pi\sqrt{LC}$

$$= \pi\sqrt{16\mu \times 4\mu}$$

$$= 8\pi\mu$$

$$= 25.133 \mu\text{s}$$

$$\text{Capacitor voltage } V_c = V_s(1 - \cos\omega t)$$

$$= V_s(1 - \cos\pi)$$

$$= 2V_s$$

$$= 400 \text{ V}$$

$$\text{Thyristor voltage } V_T = V_s \cos\omega t$$

$$V_T = -200 \text{ V}$$

57. Ans: (c)

Sol: Turn off time of SCR = 50 μs

$$\text{Safety margin} = 4$$

Circuit turn off time > SCR turn off time for the circuit to work.

$$\Rightarrow t_c = (4) \cdot (50 \mu\text{s}) = 200 \mu\text{s}$$

$$R_1 = R_2 = 25 \Omega;$$

$$RC \ln 2 = t_c$$

$$\Rightarrow C = \frac{200\mu\text{F}}{25 \times (\ln 2)}$$

$$= \frac{8}{0.693} \mu\text{F}$$

$$= 11.54 \mu\text{F}$$

58. Ans: (c)

Sol: Diode rectifies the secondary voltage in ON state of forward converter and blocks the back propagation of secondary voltage during of state of forward converter.

59. Ans: (b)

Sol: $i_0 = 200 \sin(\omega t - 45^\circ) \text{ mA}$

$$V(t) = \frac{4V_{dc}}{\pi} \sin \omega t$$

$$P = \frac{2\sqrt{2}V_{dc}}{\pi} \times \frac{(200)}{\sqrt{2}} \times \cos 45^\circ \times 10^{-3}$$

$$= (0.9) \cdot (220) \cdot (100) \times 10^{-3}$$

$$= 19.8 \text{ W}$$

60. Ans: (b)

Sol: $V_c = 4$; $f_c = 6 \text{ kHz}$; $V_r = 1 \text{ V}$; $f = 1 \text{ kHz}$

$$N = \frac{f_c}{2f} = \frac{6}{2} = 3$$

$$m_a = \frac{V_r}{V_c} = \frac{1}{4}$$

$$\Rightarrow \frac{2d}{N} = (1 - m_a) \left(\frac{\pi}{N}\right)$$

$$\Rightarrow \text{Pulse width, } \frac{2d}{N} = \left(1 - \frac{1}{4}\right) \left(\frac{\pi}{3}\right) = \frac{\pi}{4} = 45^\circ$$



61. Ans: (d)

Sol: $V_c = 5V$; $V_r = 3V$, $f_c = 1kHz$,
 $f = 50Hz$

As peak of triangular carrier coincide with zero of the reference sinusoid

$$N = \frac{f_c}{2f} = \frac{1000}{2 \times 50} = 10$$

\therefore Dominate harmonics are $2N \pm 1 = 19, 21$

$$m_a = \frac{V_r}{V_c} = 0.6$$

62. Ans (b)

Sol: To obtain good quality voltage waveform in sinusoidal PWM $m_a \leq 1$. Maximum can be obtained for $m_a = 1$.

$$V_{dc} = 283 \text{ V}$$

$$\begin{aligned} \hat{V}_{AN} &= (m_a) \times \left(\frac{V_{dc}}{2} \right) \\ &= (m_a) \times \left(\frac{V_{dc}}{2\sqrt{2}} \right) \\ &= \left(\frac{283}{2\sqrt{2}} \right) \times (1) = 100V \end{aligned}$$

63. Ans: (c)

Sol: Mc Murray inverter works on current commutation when auxiliary thyristor is turned ON, the current through the main thyristor decreases to zero and there after the current flows through anti parallel diode. As the diode is conducting $V_T = -V_D = -0.7$ (-

ve). This makes sure that the thyristor is turned OFF. It also provides path to reactive component of load current.

64. Ans: (c)

Sol: A single phase ACVR produces fundamental and harmonics in its output. Heater works as a R load, so it uses both fundamental and harmonic components whereas induction motor works as RLE load, so only fundamental voltage is used for better performance. Because harmonics in induction motor create unnecessary losses and harmonic fluxes.

65. Ans: (d)

$$\begin{aligned} \text{Sol: } V_{rms} &= \frac{V_m}{\sqrt{2}} \times \sqrt{\frac{N}{N+M}} \\ &= \frac{230}{\sqrt{2}} \times \sqrt{\frac{2}{2+7}} \\ &= 76.66 \text{ V} \end{aligned}$$

66. Ans: (c)

Sol: $k = 0.5V / rpm$

$$I = 5A, R = 2\Omega, \alpha = 60^\circ$$

$$\begin{aligned} V_o &= \frac{V_m}{\pi} (1 + \cos 60) \\ &= \left(\frac{230\sqrt{2}}{\pi} \right) \times \left(\frac{3}{2} \right) = 155.25V \end{aligned}$$

$$V_o = RI_o + E$$



$$\begin{aligned} \Rightarrow E &= 155.25 - (2)(5) \\ &= 155.25 - 10 = 145.25 \\ E &= K \times N \\ \Rightarrow N &= 145.25 \times 2 = 290.5 \text{ rpm} \end{aligned}$$

67. Ans: (d)

Sol: For natural commutation to occur load must be RLC under damped load because for under damped load $X_C > X_L$. Therefore current waveform advances voltage waveform. For a normal full bridge inverter resonant frequency of RLC load must be greater than output frequency because current has to be zero before switch turns off. If sinusoidal PWM is used in inverter then resonant frequency of RLC load must be greater than switching frequency.

68. Ans: (d)

Sol: Triac is a semiconrolled switch. It can be turned on by gate current but can not be turned off by gate. So, statement (I) is false.

69. Ans: (a)

Sol: In series converter, thyristor turn off time t_q

$$\min = \frac{\pi}{\omega} - \frac{\pi}{\omega_r} > 0$$

$$\Rightarrow \frac{1}{\omega} > \frac{1}{\omega_r}$$

$$\Rightarrow \omega < \omega_r$$

70. Ans: (a)

Sol:

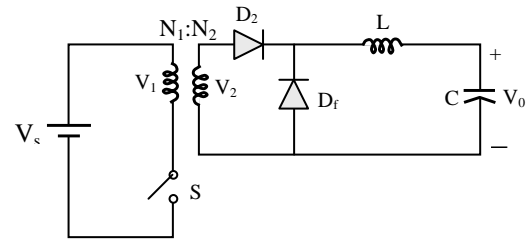


Fig: Under no load condition

Under no load condition, when switch is ON, on secondary side D_2 is ON and it forms a series LC circuit.

$$V_0(t) = V_2(1 - \cos \omega t); \quad I_s(t) = \frac{V_2}{\omega L} \sin \omega t$$

(where I_s is secondary current)

From above equations V_0 can obtain a maximum of $2V_2$. Thus excess voltage is produced.

71. Ans: (a)


Sol: Given $G(s)H(s) = \frac{10(s+4)}{s(s+2)}$

$$|G(j\omega)H(j\omega)| = \frac{10\sqrt{\omega^2 + 16}}{\omega\sqrt{\omega^2 + 4}}$$

$$\angle G(j\omega)H(j\omega) = -90^\circ - \tan^{-1}\left(\frac{\omega}{2}\right) + \tan^{-1}\left(\frac{\omega}{4}\right)$$

$$\omega = 0 \quad \infty \angle -90^\circ$$
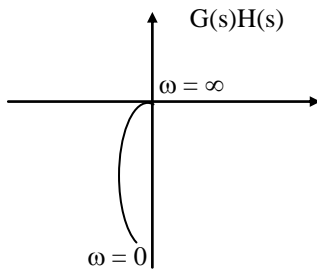
$$\omega = \infty \quad 0 \angle -90^\circ$$



Nyquist plot does not intersect the negative real axis hence $GM = \infty$.

72. Ans: (c)

Sol: Number of right half of s-plane poles can not be found from the Bode plot.

73. Ans: (c)

Sol: By adding pole to the open loop system order increases hence rise time increases.

Rise time is inversely proportional to bandwidth. Hence statement (II) wrong.

74. Ans: (a)

Sol: $CE = s^2 + 4s + 4 = 0$

$$2\zeta\omega_n = 4$$

$$\omega_n = 2 \text{ rad/sec,}$$

$$\zeta = 1$$

$$\therefore M_P = e^{\frac{-\zeta\pi}{\sqrt{1-\zeta^2}}} = 0$$

75. Ans: (d)

Sol: If open loop control system is stable we can not say exactly closed loop control system is stable. Closed loop system may or may not be stable.



CONGRATULATIONS TO OUR ESE - 2018 TOP RANKERS

AIR 1 SHASHANK E&T	AIR 1 CHIRAG JHA EE	AIR 1 VINAY PRAKASH CE	AIR 1 AMAN JAIN ME		
AIR 2 CHERUVURI SAIDEEP E&T	AIR 2 SHADAB AHAMAD EE	AIR 2 PUNIT SINGH CE	AIR 2 CHIRAG SINGLA ME	AIR 3 RAMESH KAMULLA E&T	AIR 3 SRIJAN VARMA EE
AIR 3 PRAVEEN KUMAR CE	AIR 3 MAYUR PATIL ME	AIR 4 JAPJIT SINGH E&T	AIR 4 ANKIT GARG EE	AIR 4 AMIT KUMAR ME	AIR 5 NARENDRA KUMAR E&T
AIR 5 KARTHIK KOTTURU EE	AIR 5 RISHABH DUTT CE	AIR 5 VITTHAL PANDEY ME	AIR 6 KUNUD JINDAL E&T	AIR 6 RATIPALLI NAGESWAR EE	AIR 7 KARTIKEYA DUTTA E&T
AIR 7 TEJCHAND DESHWAL EE	AIR 7 ROHIT KUMAR CE	AIR 8 SURYASH GAITAM E&T	AIR 8 RAVI TEJA MANNE EE	AIR 8 VIJAYA NANDAN CE	AIR 8 ROHIT BANSAL ME
AIR 9 SHANAVAS CP E&T	AIR 9 SOUVIK DEB ROY EE	AIR 9 ROODESH MITTAL CE	AIR 10 PRATHAMESH E&T	AIR 10 MILAN KRISHNA EE	AIR 10 SRI CHAND POONIYA CE

TOTAL SELECTIONS
in Top 10

34

E & T
TOP 10
10

E E
TOP 10
10

C E
TOP 10
8

M E
TOP 10
6

and many more...