

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennal | Vijayawada | Vizag | Tirupati | Kukatpaliy | Kolkata | Ahmedabad

ESE- 2019 (Prelims) - Offline Test Series

ELECTRONICS & TELECOMMUNICATION ENGINEERING

SUBJECT: MATERIALS SCIENCE AND NETWORK THEORY SOLUTIONS

01. Ans: (c)

Sol:
$$R_1 = \frac{\ell}{\sigma_1 \ell^2} = \frac{1}{\sigma_1 \ell}$$

 $R_2 = \frac{2\ell}{\sigma_2 4 \ell^2} = \frac{1}{2\ell \sigma_2}$
So, $R_1 = R_2 \Rightarrow \frac{1}{\sigma_1 \ell} = \frac{1}{2\ell \sigma_2}$
 $\Rightarrow \frac{\sigma_1}{\sigma_2} = \frac{2}{1}$

02. Ans: (b)

Sol: The charge deposited on the object, q = it $q = 8 k \times 15 \mu = 120 mC$


03. Ans: (a)

Sol: In a Pure capacitor

Let applied voltage $V=V_m sin\omega t$

Current drawn from the supply $I{=}I_{m}{cos}\omega t$ (as capacitor is pure)

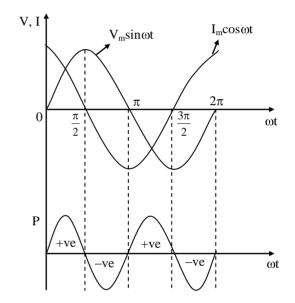Power drawn from the source will be positive when applied voltage increases but current decreases.



Test-9

04. Ans: (b)

Sol: The supply voltage =220 V

Initial current $I(0^+) = I(0^-) = 0A$

Steady state current,
$$I(\infty) = \frac{220}{100} = 2.2A$$

Time constant,
$$\tau = \frac{L}{R} = \frac{0.5}{100} = 5 \text{mSec}$$

The current flowing through Inductor,

$$I(t) = I(\infty) + [I(0^+) - I(\infty)]e^{-t/\tau}$$
$$1 = 2.2 [1 - e^{-200t}]$$



Sol:
$$\cos \phi = \frac{R}{|Z|} = \frac{10}{\sqrt{100 + 100}} = \frac{1}{\sqrt{2}}$$

= 0.707 (lead)
 $\therefore X_{\rm C} > X_{\rm L}$

06. Ans: (c)

Sol: Current
$$i = 2 \left[\frac{100 \angle 0^{\circ}}{\sqrt{64 + 36}} \right] = 20 \text{ A}$$

07. Ans: (d)

Sol: At parallel resonance the supply current, voltages are in phase.

 \Rightarrow Input power factor is unity. \Rightarrow Supply voltage (V) and current (I) are in phase

08. Ans: (a)

Sol:
$$S_1 = P_1 + jQ_1 \Longrightarrow S_1 = 20000 + j0$$

 $S_2 = P_2 + jQ_2$
 $\Longrightarrow S_2 = 30000 (0.8) + j30000 (0.6)$
 $S_3 = P_3 - jQ_3$
 $\Longrightarrow S_3 = 35000 (0.9) - j35000 (\sqrt{1 - 0.9^2})$
Total active power, $P_T = P_1 + P_2 + P_3$
 $= 20 \text{ k} + 24 \text{ k} + 31.5 \text{ k}$
 $= 75.5 \text{ kW}$

09. Ans: (d)

Sol: Given $V = 3 \cos 3t$,

$$I = -2 \sin(3t + 10^{\circ})$$

= 2 cos (3t + 10^{\circ} + 90^{\circ})

$$= 2\cos(3t + 100^\circ)$$

I leads V by an angle 100°

10. Ans: (a)
Sol:
$$Z_1 = 3+j4, Z_2 = 10 + j0$$

 $I_1Z_1 = I_2Z_2 [\because \text{parallel}]$
 $\frac{|I_1|}{|I_2|} = \frac{|Z_2|}{|Z_1|} = \frac{10}{\sqrt{3^2 + 4^2}} = 2$
 $\Rightarrow |I_1| = 2 |I_2|$
 $\frac{P_1}{P_2} = \frac{|I_1|^2 R_1}{|I_2|^2 R_2} = \frac{[|2I_2|^2]_3}{|I_2|^2 .10}$
 $\frac{P_1}{P_2} = \frac{12}{10} = \frac{6}{5}$ (1)
& P_1 + P_2 = 1100(2)
So, P_1 = 600 W, P_2 = 500 W

11. Ans: (b)

Sol:
$$P_{Lost} = (I_{Rms})^2 . R$$


 $I_{Rms} = \sqrt{\frac{1}{8} [100(2) + 16(2) + 4(2)]}$
 $= \sqrt{\frac{120 \times 2}{8}}$
 $= \sqrt{\frac{120}{4}}$
 $= \sqrt{30}$
 $P = (\sqrt{30})^2 (1) = 30 W$

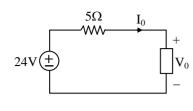12. Ans: (b)

Sol: Apply Thevenin's theorem

$$\rightarrow R_{TH} = 2 + [12//4] = 5 \Omega$$
$$\rightarrow V_{TH} = 32 \left[\frac{12}{16} \right] = 24 V$$





$$\begin{split} KVL & -24 + 5I_0 + V_0 = 0 \\ & V_0 = 24 - 5I_0 \end{split}$$

Sol: time constant, $\tau = \frac{L}{R} = \frac{20}{(10/10)} = 4 \text{ sec}$


14. Ans: (c)

Sol:
$$I_N = 10 \left[\frac{3}{9} \right] = \frac{10}{3} = 3.33 \text{ A}$$

 $R_N = 6 + 3 = 9 \Omega$

15. Ans: (d)

Sol:

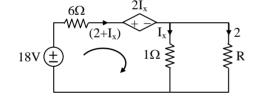

KVL $-18 + 6[2 + I_x] + 2[I_x] + I_x = 0$ $9I_x = 18 - 12$ $I_x = \frac{2}{3} A$ Voltage across R = $\frac{2}{3} V$ 2

Then R = $\frac{V}{i} = \frac{\frac{2}{3}}{\frac{2}{3}} = \frac{1}{3}\Omega$

16. Ans: (d)
Sol:
$$R_A = \frac{12 \times 12}{36} = 4 \Omega$$

 $R_B = \frac{12 \times 12}{24} = 6 \Omega$
 $R_C = \frac{12 \times 12}{48} = 3 \Omega$
 $12V - 4\Omega \approx 6\Omega \approx 4A$

 $I_T = 3 + 2 + 4 = 9 A$

If another 11 A flows fuse will blow but each bulb A carries 3A.

So, x[3]
$$\ge 11$$

x $\ge \frac{11}{3} \approx 3.66 = 4$ bulbs

17. Ans: (d)

:3:

Sol: Network nodes (n) =4

Branches (b) =6

Complete graph will have nc₂ branches

 \Rightarrow 4c₂ = 6, given network graph is complete.

Number of trees = n^{n-2}

(\because as graph is complete)

= 16

Number of cut set matrices = Number of tie set matrices =number of trees= 16



Sol:


$$\begin{aligned} & \begin{array}{c} -\frac{j}{2C} + j2\sqrt{2} \\ V_{1} & \begin{array}{c} & & \\ & & \\ \hline & & \\ \end{array} \\ & \begin{array}{c} V_{1} & \end{array} \\ & \begin{array}{c} & & \\ \hline & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & \end{array} \\ & \begin{array}{c} & & \\ & & \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & \\ & & \end{array} \\ & \begin{array}{c} & & \\ & & \\ \end{array} \\ & \begin{array}{c} & & & \\ & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ & \begin{array}{c} & & & \\ & & \end{array} \\ \\ & \end{array} \\ & \begin{array}{c} & & & \\ & \end{array} \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \end{array} \\ \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \end{array} \\ \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \end{array} \\ \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \begin{array}{c} & & & \\ & \end{array} \\ \\ & \end{array} \\ \\ \\ \end{array} \\$$

Under Resonance,

$$\begin{split} I_m(z_{in}) &= 0 \Longrightarrow -j + j8C - j2C = 0 \\ & 6C = 1 \\ & C = \frac{1}{6}F \end{split}$$

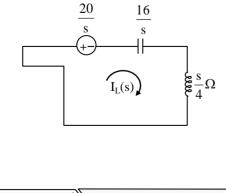19. Ans: (a)


Sol:
$$V_c(0^-) = 20 V$$
, $i_L(0^-) = 0$



$$I(s)\left[\frac{16}{s} + \frac{s}{4}\right] = -\frac{20}{s}$$
$$I(s)\left[\frac{64 + s^{2}}{4s}\right] = -\frac{20}{s}$$
$$I(s) = \frac{-80}{s^{2} + 8^{2}} = -10\left[\frac{8}{s^{2} + 8^{2}}\right]$$
$$i(t) = -10\sin 8t \text{ A}$$

20. Ans: (b)

Sol: Circuit at $t = 0^+$

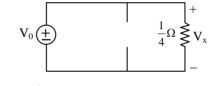

 $V_x(0^+) = V_0 = 2V \text{ only}$

- 21. Ans: (d)
- Sol: The h-parameters

$$V_{1} = h_{11}I_{1} + h_{12}V_{2}$$

$$I_{2} = h_{21}I_{1} + h_{22}V_{2}$$
When $I_{1} = 0$

$$V_{1} = 20 I_{2}$$

$$V_{2} = 20 I_{2}$$

$$h_{12} = \frac{V_{1}}{V_{2}} = 1$$

$$h_{22} = \frac{I_{2}}{V_{2}} = \frac{1}{20} = 0.05$$
When $V_{2} = 0$,

$$V_{1} = 10I_{1}$$

$$I_{1} = -I_{2}$$

$$h_{11} = \frac{V_{1}}{I_{1}} = \frac{10}{1} = 10$$

$$h_{21} = \frac{I_{2}}{I_{1}} = -1$$




22. Ans: (a) Sol: $\frac{F(s)}{s} = \frac{1}{s} - \frac{1}{(s+\alpha)}$ $F(s) = 1 - \frac{s}{s+\alpha}$ $= 1 - \left[\frac{s+\alpha-\alpha}{s+\alpha}\right]$ $= 1 - \left[1 - \frac{\alpha}{s+\alpha}\right]$ $= \frac{\alpha}{s+\alpha}$


Impulse response is, $\alpha e^{-\alpha t}$

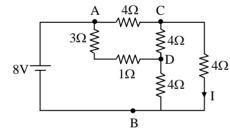23. Ans: (b)

Sol: What is the current I in the given below



Redrawn the circuit

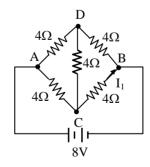

As the bridge is balanced the current flowing through in the branch CD is zero.

So
$$I_1 = \frac{8V}{8\Omega} = 1A$$

24. Ans: (c)

:5:

Sol: Tree is a connected sub graph, which connects all the nodes without any closed loop.

Tree branches are called twigs

The number of tree branches of any graph = (n-1)

The rank of tree is n-1

- 25. Ans: (c)
- **Sol:** damped frequency, $\omega_d = \omega_0 \sqrt{1-\delta^2}$

$$\begin{split} \sqrt{15} &= \omega_0 \sqrt{1-\delta^2} \\ Bandwidth, BW &= \frac{\omega_0}{Q} \ , \ Q = \frac{1}{2\delta} \\ BW &= 2\delta\omega_0 \ , \\ 2 &= 2\delta\omega_0 \ , \\ \delta\omega_0 &= 1 \\ \omega_0^2 \left(1-\delta^2\right) &= 15 \\ \omega_0^2 &- \omega_0^2 \, \delta^2 \, = 15 \\ \omega_0^2 &= 15 + 1 \, = \, 16 \ , \end{split}$$

Resonant frequency = 4 rad/sec

26. Ans: (c)

Sol: In $3-\phi$ star-connected system

$$V_{\rm L} = \sqrt{3} V_{\rm phase}$$

 $I_L = I_{ph}$

Line voltages are 30° ahead of the corresponding phase voltage

Output power = $3V_{ph}I_{ph}\cos\phi = \sqrt{3}V_LI_L\cos\phi$ Where ϕ angle between phase voltage and phase current





GATE+PSUs - 2020

Admissions Open From 14th NOV 2018

HYDERABAD -

29th April | 06th May | 11th May 18th May | 26th May | 02nd June 2019

DELHI

11th May 23rd May 2019

EARLY BIRD OFFER :

Register on or Before 31" December 2018 : 5000/- Off | Register on or Before 31" March 2019 : 3000/- Off



TEST YOUR PREP IN A REAL TEST ENVIRONMENT

Pre GATE - 2019

Date of Exam : 20th January 2019 Last Date to Apply : 31st December 2018


Highlights:


- Get real-time experience of GATE-2019 test pattern and environment.
- * Virtual calculator will be enabled.
- * Post exam learning analytics and All India Rank will be provided.
- * Post GATE guidance sessions by experts.
- * Encouraging awards for GATE-2019 toppers.




27. Ans: (c)

Sol:

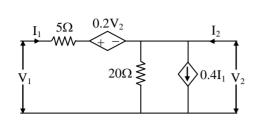

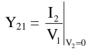

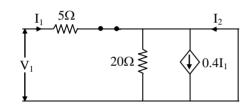

$$V_1 = 5I_1$$

$$I_1 + I_2 = 0.4 I_1$$

$$\Rightarrow I_2 = -0.6I_1$$

$$= -0.6 \times \frac{V_1}{5}$$

$$\frac{I_2}{V_1} = -0.12$$

28. Ans: (b)

Sol: Resistance of blub, R =
$$\frac{V^2}{P}$$

= $\frac{(120)(120)}{60}$
= 240 Ω

29. Ans: (b)

30. Ans: (c) Sol: $I_1 = 4 V_1 + V_2$

$$\begin{split} I_2 &= 2 \ V_1 + 3 \ V_2 \\ Z_{22} &= \left. \frac{V_2}{I_2} \right|_{I_1 = 0} \\ I_1 &= 0, \ V_2 = -4 \ V_1 \ , \ I_2 = -10 \ V_1 \ , \\ Z_{22} &= 0.4 \Omega \end{split}$$

31. Ans: (b)

- 32. Ans: (a)
- **Sol:** $L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = v_s(t)$

Characteristic equation:


$$\frac{\mathrm{d}^{2}\,\mathrm{i}}{\mathrm{d}\,\mathrm{t}^{2}} + \frac{\mathrm{R}}{\mathrm{L}}\frac{\mathrm{d}\,\mathrm{i}}{\mathrm{d}\,\mathrm{t}} + \frac{1}{\mathrm{LC}}\,\mathrm{i}(\mathrm{t}) = 0$$

For critical damping:

$$\left(\frac{R}{L}\right)^2 = \left(\frac{4}{LC}\right), R^2 = 4\frac{L}{C}, R = 2\sqrt{\frac{L}{C}}$$
$$R = 2\sqrt{\frac{1}{4}} = 1\Omega$$

33. Ans: (c)

Sol: R = resistance of each phase.

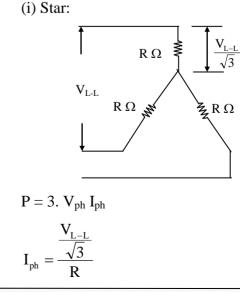




$$\Rightarrow p = (3)(V_{ph})(I_{ph}) = (3)\left(\frac{V_{L-L}}{\sqrt{3}}\right)\left(\frac{\frac{V_{L-L}}{\sqrt{3}}}{R}\right)$$

$$P_{\rm Y} = \frac{V_{\rm L-L}^2}{R}$$

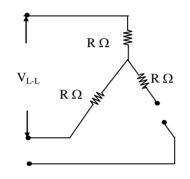If one of the resistance in star connection gets open




$$P = \frac{(V_{L-L})^2}{(R+R)} = \frac{V_{L-L}^2}{2R}$$


 P_{open-Y} = reduction power consume

Reduction in load =
$$\frac{P_{Y} - P_{open-Y}}{P_{Y}} = 50\%$$

(ii) Delta

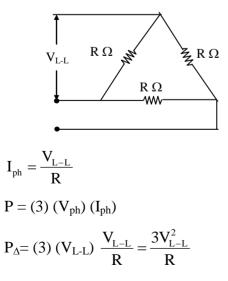

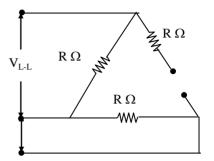If one of the resistance in delta connection gets open



$$P = \frac{(V_{L-L})^2}{R} + \frac{(V_{L-L})^2}{R}$$
$$P_{open-\Delta} = \frac{2V_{L-L}^2}{R}$$

Reduction in load =
$$\frac{P_{\Delta} - P_{open-\Delta}}{P_{\Delta}} = 33.33\%$$

34. Ans: (a)

Sol: Given $V_C(0) = 2V$, $V_C(\infty) = 1$, $\tau = R_{eq} \cdot C = 2 \times 1/4 = 0.5$ sec Voltage across capacitor $V_C(t) = 1 + (2 - 1) e^{-2t} V$ $= 1 + e^{-2t}$


Sol: Bandwidth
$$=\frac{1}{\tau} = \frac{1}{RC}$$

So, $R = \frac{1}{BW \times C}$
 $=\frac{1}{10 \times 10^3 \times 100 \times 10^{-12}}$
 $=\frac{10^6}{1} = 10^6 \Omega$
 $\Rightarrow R = 1M\Omega$



Sol: $L_{eff} = L_1 + L_2 + L_3 + 2(M_{12} + M_{13} + M_{23})$ $L_1 = 2H, M_{12} = 1H,$ $L_2 = 3H, M_{23} = 1H,$ $L_3 = 5H, M_{13} = 2H,$ $L_{eff} = 2 + 3 + 5 + 2(1 + 1 + 2)$ = 18 H

37. Ans:(a)

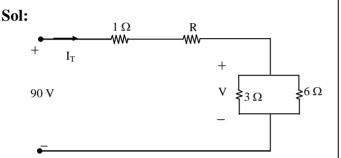

Given that

$$P_{3} = 300 \text{ W} \Rightarrow \frac{\text{V}^{2}}{3} = 300$$
$$\Rightarrow \text{V} = 30\text{V}$$
So, $I_{T} = \frac{30}{3} + \frac{30}{6} = 15 \text{ A}$ By KVL
$$-90 + 15(1) + 15 \text{ R} + 30 = 0$$
$$15 \text{ R} = 90 - 45 \Rightarrow \text{R} = \frac{45}{15} = 3\Omega$$

38. Ans: (c)

Sol: If the radius ratio x = 0.414, a more stable configuration is possible with six anions bonding with a cation. This configuration called the octahedral configuration is stable for 0.414 < x < 0.732. Here the cation

ESE - 2019 (Prelims) Offline Test Series

occupies the void created by six anions forming an octahedral structure.

39. Ans: (d)

Sol: A crystal structure characterized by a rectangular lattice and square base and height.

 $a = b = c, \alpha = \beta = \gamma \neq 90^{\circ}$

This is formed in As, Sb, Bi and Calcite

 Γ

40. Ans: (d)

Sol: Volume of unit cell = a^3

number of atoms per unit cell = 4

radius of Atoms =
$$\frac{a\sqrt{2}}{4}$$

packing fraction = $\frac{4 \times \frac{4}{3}\pi r^3}{a^3}$
= $4 \times \frac{4}{3}\pi \left(\frac{\sqrt{2}}{2}\right)^3$

$$= \frac{\pi\sqrt{8}}{12} \Rightarrow \frac{\pi\times 2\sqrt{2}}{12}$$
$$= \frac{\pi\sqrt{2}}{6}$$

41. Ans: (b)

Sol: The number of atoms per unit cell of HCP crystal = 6.

The number of atoms per unit cell of FCC crystal = 4.

So difference is = 6 - 4 = 2



42. Ans: (c)

Sol: Physical mixing of more than two materials is called as composite that may not be required in similar phases. Composite is a combination of matrix and reinforcement where thermostets are used preferably due to their high strength.

43. Ans: (b)

Sol: Charcoal – Amorphous Chromium – BCC Copper – FCC Graphite - . H.C.P

44. Ans: (a)

Sol: A special class of ferrites called 'ferrox cubes' are used as computer memory elements.

45. Ans: (c)

Sol: If the temperature of metal increases, the lattice vibration in the crystal structure increases. Hence collision frequency increases and relaxation time decreases. Due to the resistivity of metal increases.

46. Ans: (b)

Sol: Any impurities will act as scattering centers and resistivity increases (or) conductivity decreases

47. Ans: (a)

Sol: Ionic compounds are very strong in nature. They require a lot of energy to break them. Therefore they have high melting and boiling points.

48. Ans: (d)

Sol: In tungsten, atoms are arranged in all eight corners and has an additional atom in the centre satisfying the body centered cubic lattice condition.

49. Ans: (b)

Sol: When a large value of a.c. current is applied to a super conducting material it induces some magnetic field in the material and because of this magnetic field, the superconducting property of the material is destroyed.

50. Ans: (a)

Sol: Magnetic lines of force are defined as the continuous curve in a magnetic field. The tangent drawn at any point on the curve gives the direction of resultant magnetic field at that point.

ACE Engineering Academy

:11:

51. Ans: (a)

Sol: Nano particles are produced by generating plasma using Radio frequency heating coils in plasma arching method. It consists of an evacuated chamber, wounded by high voltage RF coils.

52. Ans: (b)

Sol: When alkali halides are heated in an atmosphere of the constituent metal, halide ions diffuse to the surface to react with the vapour particles. These results in excess of cations over anions.

53. Ans: (a)

Sol: The magnetic bubbles used in computer memories to store the data which made up of Yttrium-iron garnet.

54. Ans: (d)

- Sol: Maglev trains which can reach very high velocity
 - → MRI scan machine (medical science, brain imaging)
 - \rightarrow energy storage
 - \rightarrow The Large Hadron Collider (LHC) for generating high velocity particles travelling at speed of high.

55. Ans: (b)
Sol:
$$\sqrt{2} a = 4R$$

 $a = \frac{4R}{\sqrt{2}}$
 $= \frac{4(0.175)}{\sqrt{2}}$
 $= 0.494 \text{ nm}$

56. Ans: (a) Sol: Given data: V = 10 $d = 2 \times 10^{-3} \text{ m}$ $\varepsilon_r = 6$ $\varepsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

Dielectric displacement $D=\epsilon_0\epsilon_r\,E$

$$\therefore E = \frac{V}{d} = \frac{10}{2 \times 10^{-3} \,\text{V/m}}$$
$$D = 6 \times 8.85 \times 10^{-12} \times 5 \times 10^{3}$$
$$= 265.5 \times 10^{-9} \,\text{C/m}^{2}$$

57. Ans: (d)

Sol: In an intrinsic semiconductor the probability of finding an electron at the edge of the conduction band is equal to that of finding a hole at the edge of valence band at all temperatures.

Hence the Fermi level lies in the middle of the band gap always at all temperatures.



Launching Spark Batches for ESE / GATE - 2020 from Mid May 2019

Admissions from January 1st, 2019

o delhi



Launching Regular Batches for ESE / GATE - 2020

from Mid May 2019

Admissions from January 1st, 2019





58. Ans: (b)

Sol: Metallic materials have large number of valence electron and they are more compact than non-metallic elements.

59. Ans: (c)

Sol: Dielectric constant depends on a frequency and temperature.

60. Ans: (b)

- **Sol:** The residual polarization can be eliminated by
 - \rightarrow Applying field in opposite direction
 - \rightarrow Heating material above curie temperature

61. Ans: (b)


Sol: Statement 3 is incorrect, only some of piezo electric materials are ferro electric materials.

62. Ans: (c)

- **Sol:** The material for use as permanent magnets should have the following:
 - \rightarrow Low permeability
 - \rightarrow High coercive force
 - \rightarrow Appreciable remnant flue density
 - → High curie temperature, to minimize easy demagnetization.

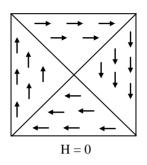63. Ans: (c)

Sol: As per wiess-Domain theory, atomic dipole moment is individual domain is parallel



64. Ans: (b)

Sol: Ferrites for permanent magnets → Hard ferrites
Ferrites for transformers and inductors→

Soft ferrites

Data storage \rightarrow rectangular loop ferrites Microwave isolators \rightarrow Ferrites and Garnets

65. Ans: (d)

Sol: The conductivity is in descending order as follows. Hard drawn copper, cadmium copper, Aluminium & galvanised steel.

66. Ans: (a)

- Sol: \rightarrow In rock salt structure, number of cations =4 and number of anions = 4
 - \rightarrow Coordination number is 6
 - →MgO, FeO are rock salt structure materials.
 - \rightarrow Automatic packing factor = 0.793

67. Ans: (c)

Sol: \rightarrow Magnetic susceptibility equal to -1

 \rightarrow Magnetic flux density of super conductor is not zero.

Engineering Academy

 \rightarrow Super conductors are used in maglev trains.

 \rightarrow With increasing temperature of a super conductor required magnetic field to destroy super conductor is decreases.

68. Ans: (b)

Sol: Physical mixing of more from two materials is known as composite. Based on the combination of materials, the final properties are dependent.


69. Ans: (a)

Sol: The Curie temperature is the critical point material's intrinsic where a magnetic change direction. Magnetic moments moments are permanent dipole moments within the atom which originate from electrons angular momentum and spin. Materials have different structures of intrinsic magnetic moments that depend on temperature. At а material's Curie those intrinsic magnetic temperature moments change direction.

70. Ans: (a)

- **Sol:** Ferrox cube in also known as rectangular ferrite with rectangle hysteresis loop.
 - Eg: Mn-Mg Fe₂O₄

Zn-MnFe₂O₄

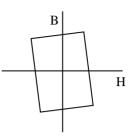

71. Ans: (c)

:14:

Sol: Fine grain materials are produced by fast cooling rate and possess more grain boundaries with small grain and these materials require more applied field to magnetize.

72. Ans: (c)

Sol: Statement (II) is incorrect, quantum dot is a zero dimensional material produced by reducing size of bulk material in all dimensions.

73. Ans: (c)

Sol: In frequency domain, the response obtained after solution contain both steady state response as well as transient response. So statement –II is wrong.

74. Ans: (c)

Sol: Cross section of A is less than $B \Rightarrow$ for same length the resistance experienced by A will be more than B.



: 15 : ESE - 2019 (Prelims) Offline Test Series

Section near to A will be more heated compared to section near $B \Rightarrow$ Statement I is correct Current per area section near A will be more than $B \Rightarrow$ Statement II is incorrect.

75. Ans: (a)

Sol: In resonance the current in series RLC circuit is maximum and the voltage across the capacitor is quality factor times the input voltage.



CONGRATULATIONS TO OUR ESE - 2018 TOP RANKERS

AIR









SHADAB ANAMAD

AIR



CHIRAG JHA









CE

AIR



AMAN JAIN ME

SRUAN VARMA EE



KARTHIK KOTTURU

SHANAVAS CP

TENCH



EE





ROHIT KUMAR CE

SOUVIK DEB ROY

EE.

AIR



EF.



BURYASH GAUTAM

ROOPESH MITTAL CE



RAVI TEJA MANNE

PRATHAMESH





VUAYA NANDAN CE

MILAN KRISHNA













www.aceenggacademy.com



AIF

п

AIR

AIF





CHIRAG





AIR





EAT



BARENDRA KUMAR