



ACE

Engineering Academy

TEST ID: 207

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

ESE- 2019 (Prelims) - Offline Test Series

Test-13

ELECTRONICS & TELECOMMUNICATION ENGINEERING

SUBJECT: CONTROL SYSTEMS, ANALOG ELECTRONICS AND DIGITAL ELECTRONICS & MICRO-PROCESSORS SOLUTIONS

01. Ans: (a)

Sol: Number of forward paths = 4

$$R_{X_1 X_2 X_3 X_4 C}$$

$$R_{X_1 X_3 X_4 C}$$

$$R_{X_1 X_2 X_4 C}$$

$$R_{X_1 X_3 X_2 X_4 C}$$

Number of loops = 5

$$X_1 X_2 X_4 X_1$$

$$X_2 X_3 X_2$$

$$X_1 X_3 X_4 X_1$$

$$X_1 X_2 X_3 X_4 X_1$$

$$X_1 X_3 X_2 X_4 X_1$$

02. Ans: (c)

Sol: $S_k^T = \frac{\partial T}{\partial K} \frac{K}{T}$

$$= \frac{\partial}{\partial K} \left(\frac{1+3K}{1+2K} \right) \frac{K}{\left(\frac{1+3K}{1+2K} \right)}$$

$$= \left[\frac{(1+2K)3 - (1+3K)2}{(1+2K)^2} \right] \frac{K(1+2K)}{1+3K}$$

$$= \frac{K}{(1+3K)(1+2K)}$$

$$= \frac{K}{1+5K+6K^2}$$

Substitute $K = 1$

$$S_k^T = \frac{1}{12}$$



03. Ans: (d)

Sol: $c(t) = L^{-1}[R(s)G_2(s)]$
 $= L^{-1}\left[\frac{1}{s} \cdot \frac{1}{s+2}\right]$
 $= 0.5 (1 - e^{-2t}) u(t)$

04. Ans: (c)

Sol: $CE = s^4 + 2s^2 + 3 = 0$

s^4	1	2	3
s^3	0(4)	0(4)	0
s^2	1	3	
s^1	-8	0	
s^0	3		


Given equation is AE, $\frac{dAE}{ds} = 4s^3 + 4s = 0$

Number of sign changes below the AE = 2

Number of RHP = Number of LHP = 2

Number of $j\omega P = 0$




 
The four poles are located in quadrate as shown below







05. Ans: (a)

Sol: Location of poles

Unit step response

    

    

06. Ans: (c)

Sol:
$$\frac{V_o(s)}{V_i(s)} = \frac{\left[\frac{1}{Cs}\right]\left[\frac{1}{Cs}\right]}{R\left[R + \frac{1}{Cs} + \frac{1}{Cs}\right] + \frac{1}{Cs}\left[R + \frac{1}{Cs}\right]}$$

Substitute $R = 1\Omega$, $C = 1F$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 + 3s + 1}$$

07. Ans: (c)

Sol: $C(s) = TF \times R(s)$

$$R(s) = L[\cos t] = \frac{s}{s^2 + 1}$$

$$C(s) = \frac{1}{s^2} \cdot \frac{s}{s^2 + 1} = \frac{1}{s(s^2 + 1)} = \frac{1}{s} + \frac{-s}{s^2 + 1}$$

$$c(t) = L^{-1}[C(s)] = 1 - \cos t$$

08. Ans: (d)

Sol: Noise transfer function
$$\frac{C(s)}{N(s)} = \frac{G_1}{1 - (-2G_1G_2H)}$$

$$= \frac{G_1}{2G_2G_1H + 1}$$

09. Ans: (b)

Sol: From option (b)

$$\omega = 0 \dots \angle\phi = -270^\circ$$

$$\omega = \infty \dots \angle\phi = -180^\circ$$



SUMMER

SHORT TERM BATCHES

GATE+PSUs - 2020

Admissions Open From 14th NOV 2018

HYDERABAD

29th April | 06th May | 11th May

18th May | 26th May | 02nd June 2019

DELHI

11th May | 23rd May 2019

EARLY BIRD OFFER :

Register on or Before 31st December 2018 : 5000/- Off | Register on or Before 31st March 2019 : 3000/- Off

Start Early.. Gain Surely...

SHORT TERM BATCHES



TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2019

Date of Exam : 20th January 2019

Last Date to Apply : 31st December 2018

Highlights :

- Get real-time experience of **GATE-2019** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post GATE guidance sessions by experts.
- Encouraging awards for **GATE-2019** toppers.



10. Ans: (b)

Sol: $\left. \frac{k}{s^2} \right|_{\omega=10} = 1$
 $\frac{k}{\omega^2} = 1$

$k = \omega^2 = 10^2$
 $\therefore K_a = k = 100$

11. Ans: (a)

Sol: The number of loops = 4
 Loop gains = 1, 1, 1, -1
 \therefore Sum of individual loop gains = 1 + 1 + 1 - 1 = 2

12. Ans: (b)

Sol: $PM = 180^\circ + \angle \left. \frac{j\omega + 1}{(j\omega)^2 \sqrt{2}} \right|_{\omega=\omega_{gc}}$

$\left| \frac{j\omega_{gc} + 1}{(j\omega_{gc})^2 \sqrt{2}} \right| = \frac{\sqrt{\omega_{gc}^2 + 1}}{\omega_{gc}^2 \sqrt{2}} = 1$

$\omega_{gc} = 1 \text{ rad/sec}$
 $\therefore PM = 180^\circ + \tan^{-1} \omega_{gc} - 180^\circ$
 $PM = 45^\circ$

13. Ans: (c)

Sol: For region 1 $N = -1$
 For region 2 $N = -2$
 For region 3 $N = 0$
 Given,
 $P = 0, Z = 0$
 $\therefore N = P - Z = 0$
 Only if $(-1, j0)$ lies in region (3) N is zero

14. Ans: (a)


Sol: A derivative controller
 \rightarrow improves the stability of the system
 \rightarrow improves phase margin
 \rightarrow decreases overshoot
 \rightarrow decreases settling time

15. Ans: (b)

Sol: Transfer function of lag-lead compensator is
 $G_c(s) = \frac{(s + Z_1)(s + Z_2)}{(s + P_1)(s + P_2)}$ where $P_1 < Z_1 < Z_2 < P_2$



Pole zero plot of lag-lead compensator

 

16. Ans: (b)

Sol: $k_p = \lim_{s \rightarrow 0} G(s) = \infty$

$$k_v = \lim_{s \rightarrow 0} sG(s) = \infty$$


$$k_a = \lim_{s \rightarrow 0} s^2G(s) = 10$$

$$\text{Error due to } 1 + t + \frac{t^2}{2} = \frac{1}{1+k_p} + \frac{1}{k_v} + \frac{1}{k_a} = 0.1$$

17. Ans: (b)

Sol: Let $G_c(s) = \frac{1 + s/10}{1 + s/1}$

Pole zero plot of lag compensator

 

18. Ans: (c)

Sol: Given positive feedback system

$$\therefore \text{Characteristic equation } 1 - G(s)H(s) = 0$$

$$1 - \frac{k}{s-6} = 0$$

$$s - 6 - k = 0$$

$$s - (k + 6) = 0$$

$$k + 6 < 0$$

$$k < -6$$

19. Ans: (c)

Sol: $G(s)H(s) = \frac{k}{s(s+1)(s+2)}$

$$\text{CE} = 1 + G(s)H(s) = 0$$

$$s(s+1)(s+2) + k = 0$$

$$s^3 + 3s^2 + 2s + k = 0$$



$$\begin{array}{l|ll} s^3 & 1 & 2 \\ s^2 & 3 & k \\ s^1 & \frac{6-k}{3} & 0 \\ s^0 & k & \end{array}$$

$k_{\text{marginal}} = 6$

∴ The value of k at point A = 6

20. Ans: (b)

Sol: Every branch of the RLD starts at a pole ($k = 0$), and terminates at a zero ($k = \infty$) of the OLTF $G(s)H(s)$.

On the real axis to the right side of any section, if the sum of total no. of open loop poles and zeros are odd, RLD exists in that section.

21. Ans: (d)

Sol: $\frac{C(s)}{R(s)} = T(s) = \frac{(s + 2)e^{-s}}{(s^2 + 4)}$

Impulse response = $L^{-1}(T(s))$

$$T(s) = \frac{se^{-s}}{s^2 + 4} + \frac{2e^{-s}}{s^2 + 4}$$


IR = $L^{-1}(T(s))$

$$IR = L^{-1}\left[\frac{se^{-s}}{s^2 + 4}\right] + L^{-1}\left[\frac{2e^{-s}}{s^2 + 4}\right]$$

IR = $\cos 2(t-1) + \sin 2(t-1)$


22. Ans: (b)

Sol:

 

23. Ans: (c)

Sol: When the switch (S/W) is on:

 




$$V_0 = -\frac{R_f}{R} = -\frac{100k}{100k//100k} \times V_{in}$$

$$\frac{V_0}{V_{in}} = -2 \Rightarrow X = -2$$

When the switch is OFF:

 

$$\frac{V_0}{V_{in}} = \frac{-100k}{100k} = -1 \Rightarrow Y = -1$$

$$X = -2, Y = -1$$

$$X = -1 - 1$$

$$X = Y - 1$$

24. Ans: (c)

Sol: If the emitter bypass capacitor in a common emitter amplifier is removed,

- i) The input resistance of the amplifier will be increased
- ii) The voltage gain of the amplifier will be decreased.

25. Ans: (c)

Sol: During positive half-cycle of input voltage,


$D_1 \rightarrow \text{ON}$

$D_2 \rightarrow \text{OFF} \Rightarrow I_{D_2} = 0$

During negative half-cycle of input voltage,

$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

 




$$V_0 = -30V_{in} \text{ and } V_{in} = -2 \sin \omega t$$

$$\therefore V_0 = 60 \sin \omega t$$

 The output voltage waveforms are shown below




$$I_{D2} = \frac{V_0}{720k} + \frac{V_0}{360k} = \frac{V_0}{240k} = 0.25 \sin \omega t \text{ mA when } V_{in} < 0$$

$$\text{RMS value of } I_{D2} = \frac{0.25}{2} = 0.125 \text{ mA}$$


26. **Ans: (c)**

Sol: Open loop configuration:

 

$$V_0 = (-5 - 2) A_0 \Rightarrow -Ve$$

 $\therefore D_1 \rightarrow \text{OFF}; D_2 \text{ is ON}$



$$V_0 = -215 \text{ V}$$

$$|V_0| \geq |-12| \Rightarrow V_0 = -12 \text{ V}$$

27. **Ans: (c)**

Sol:

(i) For cut-off region:

$$V_{SG} < |V_{tp}|$$

$$V_S - V_G < 0.5$$



$$-V_G < 0.5 - 3$$

$$V_G > 2.5V$$

(ii) For triode region:

$$V_{SD} < V_{SG} - |V_{tp}|$$

$$V_S - V_D < V_S - V_G - 0.5$$

$$3 - 1 < 3 - V_G - 0.5$$

$$V_G < 0.5V$$

(iii) For saturation region:

$$V_{SD} \geq V_{SG} - |V_{tp}|$$

$$3 - 1 \geq 3 - V_G - 0.5$$

$$V_G \geq 0.5V$$

28. Ans: (b)

Sol: $-V_{D2} + V_{D1} + V = 0$

$$V = V_{D2} - V_{D1} = 50mV$$


$$10mV = I_1 + I_2$$

$$\frac{I_2}{I_1} = \frac{I_s e^{\frac{V_{D2}}{V_T}}}{I_s e^{\frac{V_{D1}}{V_T}}} = e^{\frac{V_{D2} - V_{D1}}{V_T}}$$

$$\frac{I_2}{I_1} = e^{\frac{50mV}{25mV}} = e^2$$

29. Ans: (c)

Sol:

 

$$I_1 = \frac{1}{10k} = 0.1mA$$

$$I_2 = I_1 = 0.1mA$$

$$(10k I_2) + (100 I_3) = 0$$

$$I_3 = \frac{-10k \times 0.1m}{100} = -10mA$$

$$V_x = -100 \times 10m$$

$$V_x = -1V;$$



$$I_L = I_2 - I_3$$

$$= 10.1 \text{ mA}$$

$$V_0 = V_x - I_L R_L$$

$$V_0 = -1 - 10.1 \text{ m} R_L$$

When $R_L = 100\Omega$

$$\rightarrow V_{0\text{max}} = -1 - (10.1 \times 10^{-3} \times 100)$$

$$= -2.01 \text{ V}$$

When $R_L = 1\text{k}\Omega$


$$\rightarrow V_{0\text{min}} = -1 - (10.1 \times 10^{-3} \times 10^3)$$

$$= -11.1 \text{ V}$$

$$-11.1 \text{ V} < V_0 < -2.01 \text{ V}$$

30. Ans: (c)

Sol: Output Characteristics: I_C vs $V_{CB}|I_E$

 

Saturation Region:

- Saturation region is the region left side to $V_{CB} = 0$ line.
- In saturation region, emitter and collector junction are in forward bias.
- In saturation region, collector current increases exponentially.
- It can be used as ON switch in saturation region.

31. Ans: (c)

Sol: The emitter capacitance (C_E) increases the gain $\left(\frac{V_0}{V_s}\right)$ and input resistance (R_{in}) decreases for AC signals.

32. Ans: (c)

Sol: A 555 timer change the state when threshold voltage, V_{th} is just greater than $\frac{2V_{CC}}{3}$ volts and trigger voltage, V_{tg} is just below the $\frac{V_{CC}}{3}$ volts.

$$V_{th} = \frac{2}{3} \times 9 = 6 \text{ V}$$

$$I = \frac{9 - 6}{3\text{k}} = 1 \text{ mA}$$




Apply KVL:

$$-6 + 2 + 1 + V_C = 0 \Rightarrow V_C = 3V$$

$$V_{tg} = \frac{1}{3} \times 9 = 3V$$

$$I = \frac{9-3}{5k} = \frac{6}{5} \text{mA}$$

$$V_C = 1.8V$$

 


Therefore, the range of the voltage across the capacitor, V_C is 1.8V to 3V

33. Ans: (c)

Sol: When $V_i = +10V$, diode is forward biased

$$\therefore V_0 = 2V$$

 


$$-10 - V_C - V_0 = 0$$

$$10 - V_C - 2 = 0$$


$$V_C = +8V$$

 When $V_{in} = -10V$, diode is reverse biased.



$$-10 - 8 = V_0 \Rightarrow V_0 = -18V$$

The output wave form:

 

Average output voltage,

$$V_0 = \frac{2 \times 10m - 18 \times 10m}{20m} = -8V$$



34. **Ans: (c)**

Sol: In E-MOSFET

$$V_{GS} = 0 \text{ then } I_D = 0$$


If $+V_{GS}$ increases then ' I_D ' also Increases

35. **Ans: (c)**

Sol: The phase of loop gain should be zero. So statement(ii) is wrong.

36. **Ans: (c)**

Sol:

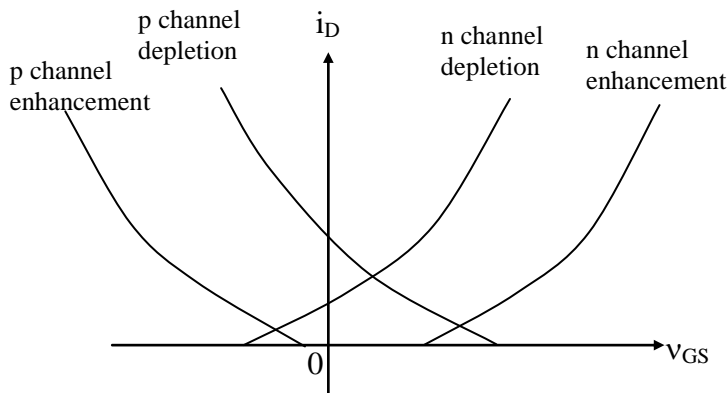

\therefore P- III, Q-II, R-IV, S-I

37. **Ans: (c)**

Sol: Overall voltage gain = product of individual voltage gains = $25 \times 10 \times 4 = 1000$

$$\text{Overall gain in dB} = 20 \log_{10} 1000 = 60\text{dB}$$

38. **Ans: (d)**


$$\text{Sol: } I_D = \frac{2.5 - 1.8}{R}$$

$$0.5\text{mA} = \frac{0.7\text{V}}{R}$$

$$R = \frac{0.7}{0.5\text{m}} = 1.4\text{k}\Omega$$

 39. **Ans: (b)**

Sol: For $V_i = 3\text{V}$, D_1 is in forward bias, D_2 is in reverse bias




\therefore RED lamp gets ON

GREEN lamp gets OFF



 40. Ans: (c)

Sol: By open-loop comparator, D_1 is ON and D_2 is OFF



$$\frac{0 + 2}{2k} + \frac{0 - V_0}{2k} = 0$$

$$V_0 = 2V$$

The current through resistor, $I = \frac{-2}{2k} = -1mA$

41. Ans: (a)

Sol:
$$f'_L = \frac{f_L}{\sqrt{2^{1/n} - 1}}$$

$$f'_L = \frac{20}{\sqrt{2^{1/3} - 1}} = 39.229 \text{ Hz}$$

42. Ans: (a)

- Sol:**
1. The Leakage current I_{CB0} doubles for every $10^{\circ}C$ rise in temperature.
 2. Base emitter voltage V_{BE} decreases by 2.5 mV for every $1^{\circ}C$ rise in temperature.
 3. As temperature increases I_c increases so power dissipation at the junction increases.

43. Ans: (a)

Sol:

$$\begin{aligned} I_c &= \beta I_B + I_{CE0} \\ &= \beta I_B + (\beta + 1) I_{CB0} \\ &= 100 (10\mu A) + 101 (100 \text{ nA}) \\ &= 1 \text{ mA} + 0.0101 \text{ mA} \\ &= 1.0101 \text{ mA} \end{aligned}$$

44. Ans: (c)

Sol:

$$\begin{aligned} V_{3k} &= 15 \cdot \frac{3}{2 + 3} \\ &= 9V \end{aligned}$$

$V_{3k} < V_z$ Hence zener diode is O.C

Hence

$$I_L = \frac{15}{2K + 3K} = 3mA$$



45. Ans: (b)

- Sol:**
1. Crystal oscillators were used whenever the greater stability of oscillations are required
 2. RC oscillators are low frequency oscillators
 3. LC oscillators are high frequency oscillators
 4. In Hartley oscillator mutual inductance between two feedback inductors will effects the frequency of oscillation

46. Ans: (b)

- Sol:** If $V_{in} > V_{out}$ set next bit
 If $V_{in} < V_{out}$ set bit is going to reset and will set next bit
 Here given that,
 Analog input (V_{in}) = 6.2V
 Digital output is greater than 6.2V so reset the last set bit and set the next bit.
 Given digital input is equal to 11010000
 \therefore next value of SAR is 11001000

47. Ans: (c)

- Sol:** The maximum number of Boolean functions with 'n' variables = 2^{2^n}
 For '5' variables = 2^{2^5}
 $= 2^{32}$
 $= 4294967296$

48. Ans: (b)

- Sol:**
- 1) Without using any additional logic gates , we cannot implement all Boolean functions using decoder.
 - 2) Any function can be implemented using suitable MUX.
 - 3) MUX is producing only one output, it cannot be used for multiple output function.

49. Ans: (b)

- Sol:** $f(A,B,C,D) = \prod M(0,4,5,7,12,15)$
 $= \sum m(1,2,3,6,8,9,10,11,13,14)$

A	B	I_0	I_1	I_2	I_3
S_1	S_0	0 0	0 1	1 0	1 1
$\overline{C}\overline{D}$ (00)		0	4	⑧	12
$\overline{C}D$ (01)		①	5	⑨	⑬
$C\overline{D}$ (10)		②	⑥	⑩	⑭
CD (11)		③	7	⑪	15
		$C+D$	$C\overline{D}$	1	$C\oplus D$

$I_0 = C + D$
 $I_1 = C\overline{D}$
 $I_2 = 1$
 $I_3 = C \oplus D$



Launching
Spark Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ DELHI



Launching
Regular Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ BHOPAL & LUCKNOW



50. Ans: (d)

Sol: $f(A, B, C, D) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}BCD + A\bar{B}CD + ABCD$
 $= \Sigma m(0, 1, 2, 3, 7, 11, 15)$

		CD			
	AB	00	01	11	10
00		1	1	1	1
01				1	
11				1	
10				1	

The simplified form of $f(A, B, C, D) = \bar{A}\bar{B} + CD$

51. Ans: (c)

Sol: $(63)_{16} + (37)_{16} = (9A)_{16}$
 $\therefore Y = 9A H$

52. Ans: (b)

Sol: It is up counter

All the flip flops are clearing when $Q_2 Q_1 = 11$

0 0 0
 0 0 1
 0 1 0
 0 1 1
 1 0 0 \Rightarrow 0 0 0

As it is asynchronous counter 100 state is overwriting with 000.

So it is counting only 4 states

53. Ans: (a)

Sol:

A	B	$Q(n+1)$
0	0	0
0	1	$\overline{Q(n)}$
1	0	$\overline{Q(n)}$
1	1	1



	A	B	Q(n)	Q(n+1)
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

	B Q(n)			
A	00	01	11	10
0				1
1	1		1	1

$$Q(n+1) = A\overline{Q(n)} + B\overline{Q(n)} + AB$$

54. Ans: (d)

Sol: The 10's complement of decimal number = 9's complement + 1

$$\begin{array}{r}
 9999 . 99999 \\
 (-) 6091 . 20100 \\
 \hline
 9's \text{ complement} \Rightarrow 3908 . 79899 \\
 (+) \quad \quad \quad \quad 1 \\
 \hline
 10's \text{ complement} \Rightarrow 3908 . 79900
 \end{array}$$

55. Ans: (c)

Sol:

	\overline{A}			
DE	00	01	11	10
BC				
00		1		
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1


	A			
DE	00	01	11	10
BC				
00		1		
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

Total number of minterms = 26

 56. Ans: (c)

Sol: $f = AB + BC + AC$

$$\begin{aligned}
 &= \overline{\overline{AB + BC + AC}} \\
 &= \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{AC}} \\
 &= \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{AC}}
 \end{aligned}$$



The function requires minimum 6 number of NAND gates to be realized.

57. **Ans: (c)**

Sol: ECL logic family has

- (1) Very high switching speed
- (2) High power dissipation
- (3)

Voltage Level	State	Boolean Logic
-0.8V	HIGH	Logic '1'
-1.8V	LOW	Logic '0'

ECL logic family uses negative voltage levels for both logic 1 and 0.

- (4) Fan-out capability is high

58. **Ans: (d)**

Sol: In fourth generation embedded system, the system on chip(SOC) is used.

59. **Ans: (a)**

Sol: Given that rotor is at "C" initially

Input (xy)	Rotor Position
	C
00	C
01	D
10	C
10	B
11	B
00	B
10	A
11	A

Therefore position of rotor after the inputs in given sequence is 'A' .

60. **Ans: (c)**

- Sol:**
- 1) Registers are made of edge triggered flops where as latches are made from level triggered flip flops.
 - 2) Latch employs cross coupled feed back connections.
 - 3) Noise immunity is the amount of noise which can be applied at the input of the gate without causing the gate to change state.
 - 4) Propagation delay is the time required for a gate to change its state.



61. Ans: (c)

Sol: S₁: Flash ADC is fastest ADC.

S₂: The most widely used ADC in multimeter is Successive approximation ADC.

S₃: The conversion time for Successive approximation ADC depends only on number of output bits. It doesn't depend on applied input voltage.

S₄: In dual slope ADC integrator is used.

62. Ans: (d)

Sol: CMOS logic family is having the given two merits, Hence it became familiar in most of the real time applications today.

63. Ans: (d)

Sol: MVI A, 06_H; [A] = 06H = 00000110₂

RLC ; [A] = 00001100₂ = 0CH

MOV B, A ; [B] = 0CH = 00001100₂

RLC ; [A] = 00011000₂

RLC ; [A] = 00110000₂ = 30H

ADD B [A] = [A]+[B] = 30H + 0CH = 3C_H

HLT

64. Ans: (c)

Sol: The 8051 requires an external oscillator circuit. The oscillator circuit usually runs around 12MHz. Each machine cycle in the 8051 is 12 clock cycles, giving an effective cycle rate at 1MHz to 3.33 MHz.

One Machine cycle has 6 states. One state is 2T-states.

∴ One machine cycle is 12T-states.

65. Ans: (c)

Sol: Interrupt vector table on 8086 is a vector that consists of 256 total interrupts placed at first 1kB of memory from 0000H to 03FFH.

66. Ans: (b)

Sol: Segmentation is a technique for allocating memory in chunks of varying and meaningful sizes instead of one arbitrary page size i.e., segmentation splits the memory into unequal units.

Therefore statement (3) is wrong

67. Ans: (b)

Sol:

(A) XTHL: Exchanges the contents of H and L registers with top of stack.

It takes 5 machine cycles = 16T states

(B) PUSH B: The contents of the register pair designated in the operand are copied onto the stack in the following sequence. The stack pointer register is decremented and the contents of the high order register (B) are copied into the location.

The stack pointer register is decremented again and the contents of the low-order register (C) are copied to that location.

3 Machine cycles = 12 T-states



- (C) HLT: Halt and enter into wait state
It takes 5 T-states.
- (D) XCHG: The contents of the register H are exchanged with the contents of register D, and the contents of register L are exchanged with the contents of register E.
1-Fetch machine cycle = 4T states

68. Ans: (d)

Sol: AAD stands for “ASCII Adjust before Division”.


This instruction adjusts two unpacked BCD digits (Least significant digit in AL register and the most significant digit in AH register) so that a division operation performed on the result will yield a correct unpacked BCD value.

AAAD instruction useful only when it precedes a DIV instruction.

 69. Ans: (d)

Sol: Statement (I): If impulse is applied to second order system, it oscillates with its natural frequency, only if the poles lie on the imaginary axis.

Statement (II): Impulse consists of infinite frequency components, whose spectrum is shown in figure below.



70. Ans: (d)

Sol: Given C.E is

$$4s^2 + 6s + 1 = 0 \rightarrow (1)$$

Standard form of characteristic equation is,

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0 \rightarrow (2)$$

Compare eq(1) and (2), then we get

$$\omega_n = 0.5 \text{ rad/sec and } \zeta = 1.5$$

System is over damped ($\zeta > 1$)

71. Ans: (a)

Sol:
$$\text{CLTF} = \frac{G(s)}{1 + G(s)H(s)}$$

$$\text{CE} = 1 + G(s)H(s) = 0$$

For system to be stable roots (zeros) of characteristic equation must lie on left half of s-plane.

Poles of CLTF is nothing but zeros of characteristic equation.

72. Ans: (b)

Sol: Both the statements are correct but statement (II) is not the correct explanation for Statement (I).



73. Ans: (a)

Sol: In a BJT, the majority of the stored charge is in the form of minority carriers which are diffusing across the device in forward operation. Whereas in FET current is only due to majority carriers. So there is no minority stored charge in FET.

Both the statements are true and statement (II) is correct explanation for statement (I).

74. Ans: (d)

Sol: DRAM stores charge in the form of charge. Each memory cell in DRAM is made of transistor and capacitor. The data will be stored in capacitor. So, DRAM must be refreshed regularly since capacitor loose charge due to leakage.

SRAM is faster than DRAM since it doesn't have refreshing circuit.

75. Ans: (c)

Sol: **Statement (I)** is true because $(0100\ 0111\ 1000\ 1001)_2$, 16 bit can be stored as $(4789)_{16}$ in hexadecimal.

Statement (II) is False, since four times of binary number is 8 not 16.



ACE

Engineering Academy
Leading Institute for ESE/GATE/PSUs



CONGRATULATIONS TO OUR ESE - 2018 TOP RANKERS

AIR 1  SHASHANK E&T	AIR 1  CHIRAG JHA EE	AIR 1  VINAY PRAKASH CE	AIR 1  AMAN JAIN ME		
AIR 2  CHERKURI SAIDEEP E&T	AIR 2  SHADAB AHAMAD EE	AIR 2  PUNIT SINGH CE	AIR 2  CHIRAG SINGLA ME	AIR 3  RAMESH KAMULLA E&T	AIR 3  SRIJAN VARMA EE
AIR 3  PRAVEEN KUMAR CE	AIR 3  MAYUR PATIL ME	AIR 4  JAPJIT SINGH E&T	AIR 4  ANKIT GARG EE	AIR 4  AMIT KUMAR ME	AIR 5  NARENDRA KUMAR E&T
AIR 5  KARTHIK KOTTURU EE	AIR 5  RISHABH DUTT CE	AIR 5  VITHAL PANDEY ME	AIR 6  KUMUD JINDAL E&T	AIR 6  NATPALLI NAGESHWAR EE	AIR 7  KARTIKEYA DUTTA E&T
AIR 7  TENCHAND DESHWAL EE	AIR 7  ROHIT KUMAR CE	AIR 8  SURYASH GAUTAM E&T	AIR 8  RAVI TEJA MANNE EE	AIR 8  VIJAYA NANDAN CE	AIR 8  ROHIT BANSAL ME
AIR 9  SHANAVAS CP E&T	AIR 9  SOUVIK DEB ROY EE	AIR 9  ROOPESH MITTAL CE	AIR 10  PRATHAMESH E&T	AIR 10  MILAN KRISHNA EE	AIR 10  BRICHAND POONIYA CE

TOTAL SELECTIONS
in Top 10

34

E & T
TOP 10
10

E
TOP 10
10

CE
TOP 10
8

ME
TOP 10
6

and many more...