



ACE

Engineering Academy

TEST ID: 307

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

ESE- 2019 (Prelims) - Offline Test Series

Test-13

ELECTRICAL ENGINEERING

SUBJECT: CONTROL SYSTEMS, ANALOG ELECTRONICS AND DIGITAL ELECTRONICS & BASIC ELECTRONICS ENGINEERING

SOLUTIONS

01. Ans: (a)

Sol: Number of forward paths = 4

$$R X_1 X_2 X_3 X_4 C$$

$$R X_1 X_3 X_4 C$$

$$R X_1 X_2 X_4 C$$

$$R X_1 X_3 X_2 X_4 C$$

Number of loops = 5

$$X_1 X_2 X_4 X_1$$

$$X_2 X_3 X_2$$

$$X_1 X_3 X_4 X_1$$

$$X_1 X_2 X_3 X_4 X_1$$

$$X_1 X_3 X_2 X_4 X_1$$

02. Ans: (c)

$$\text{Sol: } S_K^T = \frac{\partial T}{\partial K} \frac{K}{T}$$

$$= \frac{\partial}{\partial K} \left(\frac{1+3K}{1+2K} \right) \frac{K}{\left(\frac{1+3K}{1+2K} \right)}$$

$$= \left[\frac{(1+2K)3 - (1+3K)2}{(1+2K)^2} \right] \frac{K(1+2K)}{1+3K}$$

$$= \frac{K}{(1+3K)(1+2K)}$$

$$= \frac{K}{1+5K+6K^2}$$

Substitute $K = 1$

$$S_K^T = \frac{1}{12}$$

03. Ans: (d)

$$\text{Sol: } c(t) = L^{-1}[R(s)G_2(s)]$$

$$= L^{-1} \left[\frac{1}{s} \cdot \frac{1}{s+2} \right]$$

$$= 0.5 (1 - e^{-2t}) u(t)$$

04. Ans: (c)

$$\text{Sol: } CE = s^4 + 2s^2 + 3 = 0$$

s^4	1	2	3
s^3	0(4)	0(4)	0
s^2	1	3	
s^1	-8	0	
s^0	3		




Given equation is $AE, \frac{dAE}{ds} = 4s^3 + 4s = 0$

Number of sign changes below the AE = 2

Number of RHP = Number of LHP = 2

Number of $j\omega P = 0$








 
The four poles are located in quadrate as shown below



05. Ans: (a)

Sol: Location of poles

Unit step response

        



06. Ans: (c)

$$\text{Sol: } \frac{V_o(s)}{V_i(s)} = \frac{\left[\frac{1}{Cs} \right] \left[\frac{1}{Cs} \right]}{R \left[R + \frac{1}{Cs} + \frac{1}{Cs} \right] + \frac{1}{Cs} \left[R + \frac{1}{Cs} \right]}$$

Substitute $R = 1\Omega$, $C = 1F$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 + 3s + 1}$$

07. Ans: (c)

Sol: $C(s) = TF \times R(s)$

$$R(s) = L[\cos t] = \frac{s}{s^2 + 1}$$

$$C(s) = \frac{1}{s^2} \cdot \frac{s}{s^2 + 1}$$

$$= \frac{1}{s(s^2 + 1)} = \frac{1}{s} + \frac{-s}{s^2 + 1}$$

$$c(t) = L^{-1}[C(s)] = 1 - \cos t$$

08. Ans: (d)

Sol: Noise transfer function

$$\frac{C(s)}{N(s)} = \frac{G_1}{1 - (-2G_1G_2H)} = \frac{G_1}{2G_2G_1H + 1}$$

09. Ans: (b)

Sol: From option (b)

$$\omega = 0 \dots \angle \phi = -270^\circ$$

$$\omega = \infty \dots \angle \phi = -180^\circ$$

$$\text{At } \omega = 0; \angle \phi = -270^\circ$$

i.e., 3-poles at origin

10. Ans: (b)

$$\text{Sol: } \left| \frac{k}{s^2} \right|_{\omega=10} = 1$$

$$\frac{k}{\omega^2} = 1$$

$$k = \omega^2 = 10^2$$

$$\therefore K_a = k = 100$$

11. Ans: (a)

Sol: The number of loops = 4

Loop gains = 1, 1, 1, -1

$$\therefore \text{Sum of individual loop gains} = 1 + 1 + 1 - 1 = 2$$

12. Ans: (b)

$$\text{Sol: } PM = 180^\circ + \angle \frac{j\omega + 1}{(j\omega)^2 \sqrt{2}} \bigg|_{\omega=\omega_{gc}}$$

$$\left| \frac{j\omega_{gc} + 1}{(j\omega_{gc})^2 \sqrt{2}} \right| = \frac{\sqrt{\omega_{gc}^2 + 1}}{\omega_{gc}^2 \sqrt{2}} = 1$$

$$\omega_{gc} = 1 \text{ rad/sec}$$

$$\therefore PM = 180^\circ + \tan^{-1} \omega_{gc} - 180^\circ$$

$$PM = 45^\circ$$

13. Ans: (c)

Sol: For region 1 $N = -1$

For region 2 $N = -2$

For region 3 $N = 0$

Given,



$$P = 0, Z = 0$$

$$\therefore N = P - Z = 0$$

Only if $(-1, j0)$ lies in region (3) N is zero

14. Ans: (a)

Sol: A derivative controller

→ improves the stability of the system

→ improves phase margin

→ decreases overshoot

→ decreases settling time


15. Ans: (b)

Sol: Transfer function of lag-lead compensator is

$$G_c(s) = \frac{(s + Z_1)(s + Z_2)}{(s + P_1)(s + P_2)}$$

Where $P_1 < Z_1 < Z_2 < P_2$

Pole zero plot of lag-lead compensator

 

16. Ans: (b)

Sol: $k_p = \lim_{s \rightarrow 0} G(s) = \infty$

$$k_v = \lim_{s \rightarrow 0} s G(s) = \infty$$


$$k_a = \lim_{s \rightarrow 0} s^2 G(s) = 10$$

$$\begin{aligned} \text{Error due to } 1 + t + \frac{t^2}{2} &= \frac{1}{1 + k_p} + \frac{1}{k_v} + \frac{1}{k_a} \\ &= 0.1 \end{aligned}$$

17. Ans: (b)

Sol: Let $G_c(s) = \frac{1 + s/10}{1 + s/1}$

Pole zero plot of lag compensator

 

18. Ans: (c)

Sol: Given positive feedback system

∴ Characteristic equation $1 - G(s)H(s) = 0$

$$1 - \frac{k}{s - 6} = 0$$

$$s - 6 - k = 0$$

$$s - (k + 6) = 0$$

$$k + 6 < 0$$

$$k < -6$$

19. Ans: (c)

Sol: $G(s)H(s) = \frac{k}{s(s+1)(s+2)}$

$$CE = 1 + G(s)H(s) = 0$$

$$s(s+1)(s+2) + k = 0$$

$$s^3 + 3s^2 + 2s + k = 0$$

s^3	1	2
s^2	3	k
s^1	$\frac{6-k}{3}$	0
s^0	k	



$$k_{\text{marginal}} = 6$$

∴ The value of k at point A = 6

20. Ans: (b)

Sol: Every branch of the RLD starts at a pole ($k = 0$), and terminates at a zero ($k = \infty$) of the OLTF $G(s)H(s)$.

On the real axis to the right side of any section, if the sum of total no. of open loop poles and zeros are odd, RLD exists in that section.

21. Ans: (d)

Sol: $\frac{C(s)}{R(s)} = T(s) = \frac{(s+2)e^{-s}}{(s^2+4)}$

Impulse response = $L^{-1}(T(s))$

$$T(s) = \frac{se^{-s}}{s^2+4} + \frac{2e^{-s}}{s^2+4}$$


$$\text{IR} = L^{-1}(T(s))$$

$$\text{IR} = L^{-1}\left[\frac{se^{-s}}{s^2+4}\right] + L^{-1}\left[\frac{2e^{-s}}{s^2+4}\right]$$

$$\text{IR} = \cos 2(t-1) + \sin 2(t-1)$$


22. Ans: (b)

Sol:

 

23. Ans: (c)


Sol: When the switch (S/W) is on:

 

$$V_0 = -\frac{R_f}{R} = -\frac{100k}{100k // 100k} \times V_{in}$$

$$\frac{V_0}{V_{in}} = -2 \Rightarrow X = -2$$

When the switch is OFF:

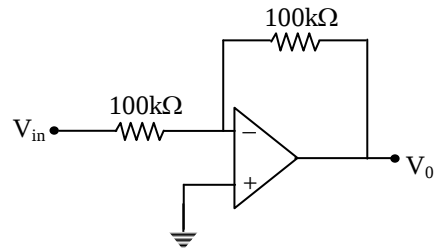

$$\frac{V_0}{V_{in}} = \frac{-100k}{100k} = -1$$

$$\Rightarrow Y = -1$$

$$X = -2, Y = -1$$

$$X = -1 - 1$$

$$X = Y - 1$$

24. Ans: (c)

Sol: If the emitter bypass capacitor in a common emitter amplifier is removed,



- i) The input resistance of the amplifier will be increased
- ii) The voltage gain of the amplifier will be decreased.

25. Ans: (c)

Sol: During positive half-cycle of input voltage,


$D_1 \rightarrow \text{ON}$

$D_2 \rightarrow \text{OFF} \Rightarrow I_{D_2} = 0$

During negative half-cycle of input voltage,

$D_1 \rightarrow \text{OFF}$


$D_2 \rightarrow \text{ON}$

 

$$V_0 = -30V_{in} \text{ and } V_{in} = -2\sin\omega t$$

$$\therefore V_0 = 60\sin\omega t$$

 The output voltage waveforms are shown below




$$I_{D_2} = \frac{V_0}{720k} + \frac{V_0}{360k}$$

$$= \frac{V_0}{240k} = 0.25\sin\omega t \text{ mA when } V_{in} < 0$$

$$\text{RMS value of } I_{D_2} = \frac{0.25}{2} = 0.125\text{mA}$$


26. Ans: (c)

Sol: Open loop configuration:

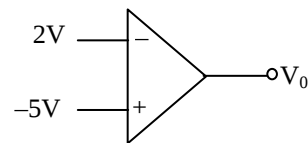

$$V_0 = (-5 - 2) A_0 \Rightarrow -V_e$$
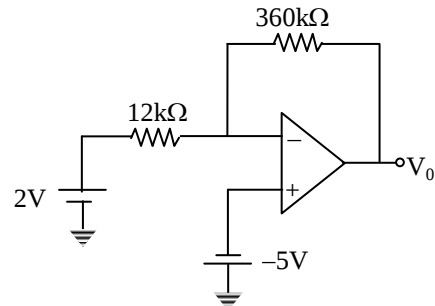
$$\therefore D_1 \rightarrow \text{OFF}; D_2 \text{ is ON}$$



$$V_0 = -215 \text{ V}$$

$$|V_0| \geq |-12|$$

$$\Rightarrow V_0 = -12 \text{ V}$$



SHORT TERM BATCHES

SUMMER

» SHORT TERM BATCHES

GATE+PSUs - 2020

Admissions Open From 14th NOV 2018

— HYDERABAD —

29th April | 06th May | 11th May

18th May | 26th May | 02nd June 2019

— DELHI —

11th May | 23rd May 2019

Start Early.. Gain Surely...

EARLY BIRD OFFER :

Register on or Before 31st December 2018 : 5000/- Off | Register on or Before 31st March 2019 : 3000/- Off



TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2019

Date of Exam : 20th January 2019

Last Date to Apply : 31st December 2018

Highlights :

- Get real-time experience of **GATE-2019** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post GATE guidance sessions by experts.
- Encouraging awards for **GATE-2019** toppers.



27. Ans: (c)

Sol: 1. p-n junction diode is a passive component

2. $W \propto V_j^{1/n}$ ($n = 2$ for non-linear junction
 $n = 3$ for linear junction) and

$V_j = V_0 - V_B \rightarrow$ For forward biasing

3. $I_{02} = I_{01} \times 2^{\frac{T_2 - T_1}{10}}$ (reverse saturation current
increases with increasing in
temperature)

So statement (2) and (3) are correct and (1)
is false.

28. Ans: (b)

Sol: $-V_{D2} + V_{D1} + V = 0$

$V = V_{D2} - V_{D1} = 50\text{mV}$


$10\text{mV} = I_1 + I_2$

$$\frac{I_2}{I_1} = \frac{I_s e^{\frac{V_{D2}}{V_T}}}{I_s e^{\frac{V_{D1}}{V_T}}} = e^{\frac{V_{D2} - V_{D1}}{V_T}}$$

$$\frac{I_2}{I_1} = e^{\frac{50\text{mV}}{25\text{mV}}} = e^2$$

29. Ans: (c)

Sol:

 

$$I_1 = \frac{1}{10\text{k}} = 0.1\text{mA}$$

$$I_2 = I_1 = 0.1\text{mA}$$

$$(10\text{k} I_2) + (100 I_3) = 0$$

$$I_3 = \frac{-10\text{k} \times 0.1\text{mA}}{100} = -10\text{mA}$$

$$V_x = -100 \times 10\text{m}$$

$$V_x = -1\text{V};$$

$$I_L = I_2 - I_3$$

$$= 10.1\text{mA}$$

$$V_0 = V_x - I_L R_L$$

$$V_0 = -1 - 10.1\text{mA} R_L$$

When $R_L = 100\Omega$

$$\rightarrow V_{0\text{max}} = -1 - (10.1 \times 10^{-3} \times 100) \\ = -2.01\text{V}$$


When $R_L = 1\text{k}\Omega$

$$\rightarrow V_{0\text{min}} = -1 - (10.1 \times 10^{-3} \times 10^3) \\ = -11.1\text{V}$$

$$-11.1\text{V} < V_0 < -2.01\text{V}$$

30. Ans: (c)

Sol: Output Characteristics: I_C vs $V_{CB}|I_E$

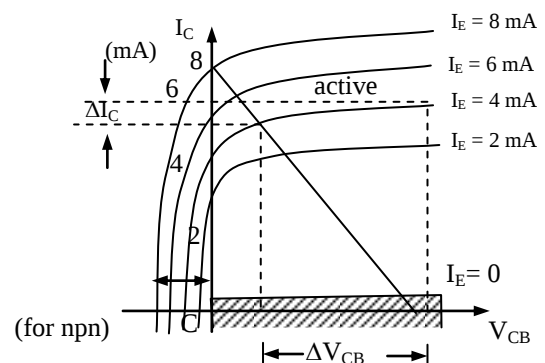



Saturation Region:

- Saturation region is the region left side to $V_{CB} = 0$ line.
- In saturation region, emitter and collector junction are in forward bias.
- In saturation region, collector current increases exponentially.
- It can be used as ON switch in saturation region.


31. Ans: (c)

Sol: The emitter capacitance (C_E) increases the gain $\left(\frac{V_o}{V_s}\right)$ and input resistance (R_{in}) decreases for AC signals.

32. Ans: (b)

Sol: For $V_i = -5V$

(Q_2) gets ON, (Q_1) gets OFF

 

Q_2 is in active region

$$V_B = V_o - 0.7$$

Apply KVL

$$I_E + 0.7 + 10I_B - 5 = 0$$

$$I_E + 10\left(\frac{I_E}{100}\right) = 5 - 0.7$$


$$I_E = \frac{4.3}{1.1} = 3.9mA$$

$$V_o = -I_E(1k) = -3.9V$$

33. Ans: (c)

Sol: When $V_i = +10V$, diode is forward biased

$$\therefore V_o = 2V$$

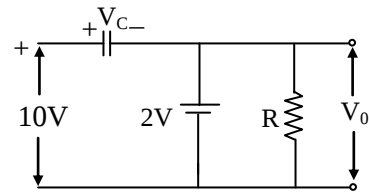


$$-10 - V_C - V_o = 0$$

$$10 - V_C - 2 = 0$$


$$V_C = +8V$$

 When $V_{in} = -10V$, diode is reverse biased.



$$-10 - 8 = V_o \Rightarrow V_o = -18V$$

The output wave form:

 



Average output voltage,

$$V_o = \frac{2 \times 10\text{m} - 18 \times 10\text{m}}{20\text{m}} = -8\text{V}$$

34. Ans: (c)

Sol: In E-MOSFET

$$V_{GS} = 0 \text{ then } I_D = 0$$


If $+V_{GS}$ increases then ' I_D ' also Increases

35. Ans: (c)

Sol: The phase of loop gain should be zero. So statement (ii) is wrong.

36. Ans: (c)

Sol:

 

$\therefore$ P- III, Q-II, R-IV, S-I

37. Ans: (c)

Sol: Overall voltage gain = product of individual voltage gains = $25 \times 10 \times 4 = 1000$

$$\text{Overall gain in dB} = 20 \log_{10} 1000 = 60\text{dB}$$

38. Ans: (a)

Sol: Given that, $\frac{dA}{A} = \frac{10}{100} = 0.1$

Variation in closed loop gain


$$\frac{dA_f}{A_f} = \frac{0.1}{100} = 0.001$$

$$\text{Sensitivity factor} = \frac{1}{1 + A\beta}$$

$$\text{Desensitivity factor} = \frac{1}{\text{Sensitivity}} = 1 + A\beta$$

 39. Ans: (b)

Sol: For $V_i = 3\text{V}$, D_1 is in forward bias, D_2 is in reverse bias




$\therefore$ RED lamp gets ON

GREEN lamp gets OFF

 40. Ans: (c)

Sol: By open-loop comparator, D_1 is ON and D_2 is OFF





$$\frac{0+2}{2k} + \frac{0-V_0}{2k} = 0$$

$$V_0 = 2V$$

The current through resistor,

$$I = \frac{-2}{2k} = -1\text{mA}$$

41. Ans: (d)

Sol: Let I_1 be current flowing through the resistor

R_C

$$I_1 = I_E = I_C + I_B = (\beta + 1)I_B = 50I_B$$

$$I_B = \frac{V_{CE} - V_{BE}}{R} = \frac{5 - 0.7}{R} = \frac{4.3V}{R}$$

Now, taking KVL in the collector-emitter circuit and using the above result.

$$I_1 R_C + I_E R_E = V_{CC} - V_{CE}$$

$$\Rightarrow 50 \times \left(\frac{4.3V}{R} \right) (7K + 250\Omega) = 20 - 5 = 15V$$

$$\Rightarrow R = \frac{50 \times 4.3 \times 7.25K}{15} = 104k\Omega$$

42. Ans: (a)

$$\text{Sol: } \sigma_p = (n\mu_n + p\mu_p)q$$

$$= \left(\frac{n_i^2}{n_i \left(\frac{\mu_n}{\mu_p} \right)} \mu_n + n_i \left(\frac{\mu_n}{\mu_p} \right) \cdot \mu_p \right) q$$

$$= (n_i \mu_p + n_i \mu_n) \cdot q = \sigma_i$$

43. Ans: (d)

$$\text{Sol: } \sigma = q(n\mu_n + p\mu_p) = q \left(n\mu_n + \mu_p \frac{n_i^2}{n} \right)$$

$$\frac{d\sigma}{dn} = q \left(\mu_n - \mu_p \frac{n_i^2}{n^2} \right)$$



Equate $\frac{d\sigma}{dn}$ to zero for minimum conductivity

$$n^2 = n_i^2 \frac{\mu_p}{\mu_n} \Rightarrow n = n_i \sqrt{\frac{\mu_p}{\mu_n}}$$

44. Ans: (b)



Sol: n-type semiconductor

p-type semiconductor

 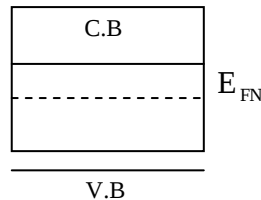

Intrinsic semiconductor

Degenerative n-type semiconductor

  

45. Ans: (a)

Sol:

$$\begin{array}{r} 2 \overline{) 47} \\ 2 \overline{) 23-1} \\ 2 \overline{) 11-1} \\ 2 \overline{) 5-1} \\ 2 \overline{) 2-1} \\ 1-0 \end{array}$$



$$+47 = 00101111$$

$\swarrow$ magnitude
 $\searrow$ sign

46. Ans: (b)

Sol: If $V_{in} > V_{out}$ set next bit

If $V_{in} < V_{out}$ set bit is going to reset and will set next bit

Here given that,

Analog input (V_{in}) = 6.2V

Digital output is greater than 6.2V so reset the last set bit and set the next bit.

Given digital input is equal to 11010000

$\therefore$ next value of SAR is 11001000

47. Ans: (c)

Sol: The maximum number of Boolean functions with

'n' variables = 2^{2^n}

For '5' variables = $2^{2^5} = 2^{32} = 4294967296$

48. Ans: (b)

Sol: 1) Without using any additional logic gates, we cannot implement any function (boolean function of more than one variable) using decoder.

2) Any function can be implemented using suitable MUX.

3) MUX is producing only one output, it cannot be used for multiple output function.

49. Ans: (b)

Sol: $f(A,B,C,D) = \prod M(0,4,5,7,12,15)$

$$= \sum m(1,2,3,6,8,9,10,11,13,14)$$

A	B	I_0	I_1	I_2	I_3
S_1	S_0	0 0	0 1	1 0	1 1
$\overline{C}\overline{D}$ (00)		0	4	⑧	12
$\overline{C}D$ (01)		①	5	⑨	⑬
$C\overline{D}$ (10)		②	⑥	⑩	⑭
CD (11)		③	7	⑪	15
		$C+D$	$C\overline{D}$	1	$C\oplus D$

$$I_0 = C + D$$

$$I_1 = C\overline{D}$$

$$I_2 = 1$$

$$I_3 = C \oplus D$$

50. Ans: (d)

Sol

$$\begin{aligned}
 f(A,B,C,D) &= \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} \\
 &\quad + \overline{A}\overline{B}CD + \overline{A}BC\overline{D} + \overline{A}BCD + ABC\overline{D} + ABCD \\
 &= \sum m(0, 1, 2, 3, 7, 11, 15)
 \end{aligned}$$

AB \ CD				
	00	01	11	10
00	1	1	1	1
01			1	
11			1	
10			1	

The simplified form of $f(A, B, C, D)$

$$= \overline{A}\overline{B} + CD$$



51. Ans: (c)

Sol: $(63)_{16} + (37)_{16} = (9A)_{16}$

$\therefore Y = 9A H$

52. Ans: (b)

Sol: It is up counter

All the flip flops are clearing when $Q_2 Q_1$

= 11

$$\begin{array}{r} 000 \\ 001 \\ 010 \\ 011 \\ 100 \Rightarrow 000 \end{array}$$

As it is asynchronous counter 100 state is overwriting with 000.

So it is counting only 4 states

53. Ans: (a)

Sol:

A	B	$Q(n+1)$
0	0	0
0	1	$\overline{Q(n)}$
1	0	$\overline{Q(n)}$
1	1	1

	A	B	$Q(n)$	$Q(n+1)$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0

4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

		B $Q(n)$			
A		00	01	11	10
	0				1
1		1		1	1

54. Ans: $Q(n+1) = A\overline{Q(n)} + B\overline{Q(n)} + AB$

Sol. The 10's complement of decimal number
= 9's complement + 1

$$\begin{array}{r} 9999.99999 \\ (-) 6091.20100 \\ \hline 9's \text{ complement} \Rightarrow 3908.79899 \\ (+) \quad \quad \quad 1 \\ \hline 10's \text{ complement} \Rightarrow 3908.79900 \end{array}$$

55. Ans: (c)

Sol:

		$\overline{A}$			
BC	DE	00	01	11	10
	00		1		
01		1	1	1	1
11		1	1	1	1
10		1	1	1	1

		A			
BC	DE	00	01	11	10
	00		1		
01		1	1	1	1
11		1	1	1	1
10		1	1	1	1

Total number of minterms = 26



Launching
Spark Batches for
ESE / GATE - 2020
from Mid May 2019

Admissions from January 1st, 2019

@ DELHI



Launching
Regular Batches for
ESE / GATE - 2020
from Mid May 2019


Admissions from January 1st, 2019

@ BHOPAL & LUCKNOW



56. Ans: (c)

Sol:

 

$$f = AB + BC + AC$$

$$= \overline{\overline{AB + BC + AC}}$$

$$= \overline{AB \cdot BC \cdot AC}$$

$$= \overline{AB \cdot BC \cdot AC}$$

The function requires minimum 6 number of NAND gates to be realized.

57. Ans: (c)

Sol: BCD to 7 segment ---combinational circuit

4 to 1 multiplexer ---- combinational circuit

4 bit shift register --- sequential circuit

BCD counter ---- sequential circuit

58. Ans:(c)

Sol: $f(A,B,C,D) = \sum m(1, 5, 7, 12, 13, 14) + d(3, 11, 15)$

		CD			
AB	00	01	11	10	
00		1	×		$\bar{A}\bar{D}$
01		1	1		
11	1	1	×	1	AB
10			×		

$$f(A, B, C, D) = AB + \bar{A}\bar{D}$$

For the input 0011, $f = (0.0) + (1.1) = 1$

For the input 1011, $f = (1.0) + (0.1) = 0$

59. Ans: (b)

Sol: (A) XTHL: Exchanges the contents of H and L registers with top of stack.

It takes 5 machine cycles = 16T states

(B) PUSH B: The contents of the register pair designated in the operand are copied onto the stack in the following sequence. The stack pointer register is decremented and the contents of the high order register (B) are copied into the location. The stack pointer register is decremented again and the contents of the low-order register (C) are copied to that location.

3 Machine cycles = 12 T-states

(C) HLT: Halt and enter into wait state

It takes 5 T-states.

(D) XCHG: The contents of the register H are exchanged with the contents of register D, and the contents of register L are exchanged with the contents of register E.

1-Fetch machine cycle = 4T states

60. Ans: (c)

Sol: 1) Registers are made of edge triggered flops where as latches are made from level triggered flip flops.

- 2) Latch employs cross coupled feed back connections.
- 3) Noise immunity is the amount of noise which can be applied at the input of the gate without causing the gate to change state.
- 4) Propagation delay is the time required for a gate to change its state.

61. Ans: (c)

Sol: S_1 : Flash ADC is fastest ADC.

S₂: The most widely used ADC in multimeter is Successive approximation ADC.

S₃: The conversion time for Successive approximation ADC depends only on number of output bits. It doesn't depends on applied input voltage.

S₄: In dual slope ADC integrator is used.

62. Ans: (d)

```

Sol: MVI      A, 06H ; [A] = 06H = 000001102
      RLC          ; [A] = 000011002 = 0CH
      MOV     B, A  ; [B] = 0CH = 000011002
      RLC          ; [A] = 000110002
      RLC          ; [A] = 001100002 = 30H
      ADD     B     [A] = [A]+[B] = 30H + 0CH
                        = 3CH
      HLT

```

63. Ans: (c)

Sol: $T_0 = 2 \times 10^{-4}$ sec

$$f_0 = \frac{1}{T_0} = 5\text{kHz}$$

$$f_m = 3f_0 = 15\text{kHz}$$

$$\therefore \beta_{\text{FM}} = \frac{\Delta f_{\text{MAX}}}{f_{\text{MAX}}} = \frac{k_f A_m}{f_m}$$

$$= \frac{10^5 \times 1}{15 \times 10^3} = \frac{100}{15} > 1$$

$\therefore$ WBFM signal

$$\begin{aligned} BW_{FM} &= 2(\beta + 1)f_m \\ &= 2 \left[\frac{115}{15} \right] \times 15 \times 10^3 \end{aligned}$$

$$\text{BW}_{\text{FM}} = 230 \text{ kHz}$$

64. Ans: (a)

Sol: $\beta = \frac{\Delta f_{\max}}{f_{\max}}$

$$f_{\max} = 1000 \text{ Hz}$$

$$\Delta f_i(t) = \frac{1}{2\pi} \frac{d}{dt} [\Delta \theta_i(t)]$$

$$= \frac{1}{2\pi} \frac{d}{dt} [5 \sin 3000t + 10 \sin 2000\pi t]$$

$$\Delta f_i(t) = \frac{1}{2\pi} [15000 \cos 3000t + 20000\pi \cos 2000\pi t]$$

$$\Delta f_i(t)_{\max} = \frac{1}{2\pi} [15000 + 20000\pi]$$

$$\Delta f_i(t)_{\max} = 12387.32 \text{ Hz}$$

Hence, $\beta = \frac{12387.32}{1000}$

$$\therefore \beta = 12.387 \approx 12$$



65. Ans: (d)

Sol: $N = 5$

$$f_m = 100\text{Hz}$$

$$f_q = 200\text{Hz}$$

$$f_s = 50\% \text{ higher than } f_q = 1.5 f_q$$

$$\therefore f_s = 200 \times 1.5 = 300 \text{ samples/sec}$$

$$r_b = [Nm + a]f_s$$

$$Nm = 5 \times 8 = 40 \text{ bits}$$

$$a = \frac{1.25}{100} \times 40 = \frac{5}{400} \times 40 = 0.5$$

$$\therefore r_b = (40 + 0.5)300$$

$$r_b = 12150 \text{ bps}$$

66. Ans: (d)

$$\begin{aligned} \text{Sol: } \mu &= \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}} \\ &= \frac{5-1}{5+1} = \frac{4}{6} = \frac{2}{3} \end{aligned}$$

67. Ans:(b)

$$\text{Sol: Transmission Bandwidth} = \frac{r_b}{2}(1 + \alpha)$$

[When Nyquist criterion pulses are used]

$$4 \times 10^3 = \frac{6 \times 10^3}{2} [1 + \alpha] \Rightarrow 1 + \alpha = \frac{4}{3}$$

$$\therefore \alpha = \frac{4}{3} - 1 = \frac{1}{3} = 0.33$$

68. Ans: (b)

Sol: RST instruction is equivalent to 1-byte call instruction, however these software

instructions used in a program to transfer program execution to one of the eight locations.

RST0 0000 H

RST1 0008 H

RST2 0010 H

• •

• •


RST6 0030 H

RST7 0038 H

 69. Ans: (d)

Sol: Statement (I): If impulse is applied to second order system, it oscillates with its natural frequency, only if the poles lie on the imaginary axis.

Statement (II): Impulse consists of infinite frequency components, whose spectrum is shown in figure below.



70. Ans: (d)

Sol: Given C.E is

$$4s^2 + 6s + 1 = 0 \quad \dots\dots\dots (1)$$

Standard form of characteristic equation is,

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0 \quad \dots\dots\dots (2)$$

Compare eq. (1) and (2), then we get

$$\omega_n = 0.5 \text{ rad/sec and } \zeta = 1.5$$

System is over damped ($\zeta > 1$)



71. Ans: (a)

Sol: $CLTF = \frac{G(s)}{1 + G(s)H(s)}$

$$CE = 1 + G(s)H(s) = 0$$

For system to be stable roots (zeros) of characteristic equation must lie on left half of s-plane.

Poles of CLTF is nothing but zeros of characteristic equation.

72. Ans: (b)

Sol: Both the statements are correct but statement (II) is not the reason for Statement (I).

73. Ans: (a)

Sol: In a BJT, the majority of the stored charge is in the form of minority carriers which are diffusing across the device in forward operation. Whereas in FET current is only

due to majority carriers. So there is no minority stored charge in FET.

Both the statements are true and statement (II) is correct reason for statement (I).

74. Ans: (c)

Sol: As reverse voltage changes minority carriers will not change, they change only due to temperature. So, statement (II) is false.

I_0 is not depends on reverse biased voltage.

So $\frac{dI_0}{dV} = 0$. statement(I) is true.

75. Ans: (c)

Sol: Statement (I): is true because $(0100\ 0111\ 1000\ 1001)_2$, 16 bit can be stored as $(4789)_{16}$ in hexadecimal.

Statement (II): is False, since four times of binary number is 8 not 16.



ACE

Engineering Academy
Leading Institute for ESE/GATE/PSUs



CONGRATULATIONS TO OUR ESE - 2018 TOP RANKERS

AIR 1  SHASHANK E&T	AIR 1  CHIRAG JHA EE	AIR 1  VINAY PRAKASH CE	AIR 1  AMAN JAIN ME		
AIR 2  CHERUKURI SAIDEEP E&T	AIR 2  SHADAB AHAMAD EE	AIR 2  PUNIT SINGH CE	AIR 2  CHIRAG SINGLA ME	AIR 3  RAMESH KAMULLA E&T	AIR 3  SRIJAN VARMA EE
AIR 3  PRAVEEN KUMAR CE	AIR 3  MAYUR PATIL ME	AIR 4  JAPJIT SINGH E&T	AIR 4  ANKIT GARG EE	AIR 4  AMIT KUMAR ME	AIR 5  NARENDRA KUMAR E&T
AIR 5  KARTHIK KOTTURU EE	AIR 5  RISHABH DUTT CE	AIR 5  VITHAL PANDEY ME	AIR 6  KUMUD JINDAL E&T	AIR 6  RATIPALLI NAGABHAR EE	AIR 7  KARTIKEYA DUTTA E&T
AIR 7  TARCHAND DESHWAL EE	AIR 7  ROHIT KUMAR CE	AIR 8  SURYASH GAUTAM E&T	AIR 8  RAVI TEJA MANNE EE	AIR 8  VIJAYA NANDAN CE	AIR 8  ROHIT BANSAL ME
AIR 9  SHANAVAS CP E&T	AIR 9  SOUVIK DEB ROY EE	AIR 9  ROOPESTH MITTAL CE	AIR 10  PRATHAMESH E&T	AIR 10  MILAN KRISHNA EE	AIR 10  SRICHAND POONIYA CE

TOTAL SELECTIONS
in Top 10

34

E & T
TOP 10
10

E E
TOP 10
10

C E
TOP 10
8

M E
TOP 10
6

and many more...