



# ACE

## Engineering Academy

TEST ID: 312

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

ESE- 2019 (Prelims) - Offline Test Series


Test - 24

ELECTRICAL ENGINEERING

Mock-2 (Paper - II) - SOLUTIONS


01. Ans: (a)

Sol:

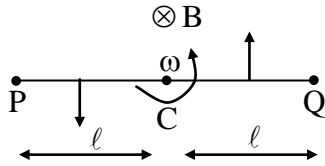

$$V_{CP} = \frac{B\omega\ell^2}{2}$$

$$V_{CQ} = \frac{B\omega\ell^2}{2}$$

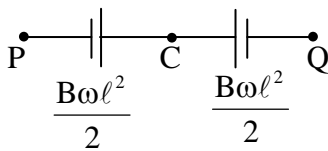

$$V_{PC} = \frac{-B\omega\ell^2}{2}$$

$$V_{PQ} = 0$$

02. Ans: (c)

Sol: A, B, C, D, E are the points on the equipotential surface.

So, the work done is zero.

03. Ans: (a)

Sol:  $\vec{\tau} = \vec{M} \times \vec{B}$

$$\vec{M} = NIA\hat{n}$$

$$\vec{M} = 100 \times 5 \times 10^{-1} \times 4 \times 8 \times 10^{-4} \hat{a}_x$$

$$\vec{M} = 0.16 \hat{a}_x \text{ A.m}^2$$

$$\vec{\tau} = \vec{M} \times \vec{B}$$

$$\vec{\tau} = 5.66 \times 10^{-3} \hat{a}_z$$

04. Ans : (b)


Sol: Capacitance of an isolated sphere =  $4\pi\epsilon a$

Where 'a' is the radius of the sphere

$$C = 4\pi\epsilon_0 \frac{1}{2\pi\epsilon_0} = 2 \text{ F}$$

05. Ans: (d)

Sol: To get  $V_{Th}$ :

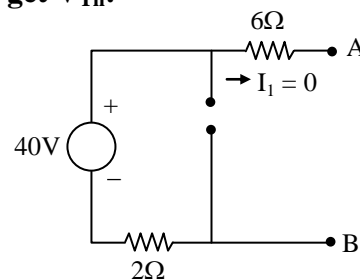




$$V_{th} = 40V \text{ As } I_1=0$$

To get  $R_{th}$  :

$$R_{th} = \frac{V_{th}}{I_{st}}$$

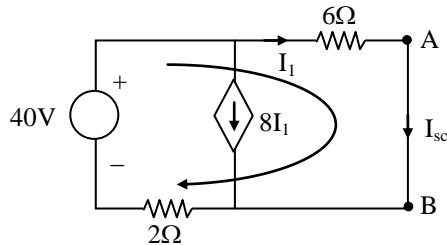

$$I_1 = I_{sc}$$

Apply KVL to the loop

$$-40 + 6I_{sc} + 2(I_{sc} + 8I_{sc}) = 0$$


$$24I_{sc} = 40$$

$$I_{sc} = \frac{5}{3}$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{40}{\frac{5}{3}} = 24\Omega$$

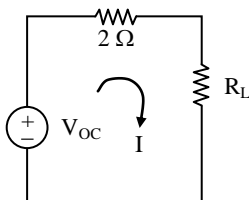**06. Ans: (c)**

**Sol:** Given data,  $V_{OC} = 20 \text{ V}$ ,  $I_{SC} = 10 \text{ A}$  and  $R_L = 3 \Omega$ .



$$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{20}{10} = 2 \Omega$$

$$I = \frac{20}{2+3} = 4 \text{ A}$$


**07. Ans: (d)**

$$\text{Sol: } R_{Total} = \frac{\Delta V}{\Delta I} = 24 \Omega$$

$$R_{int} = 24 - 10 = 14 \Omega$$

**08. Ans: (c)**


**Sol:**  $t < 0$

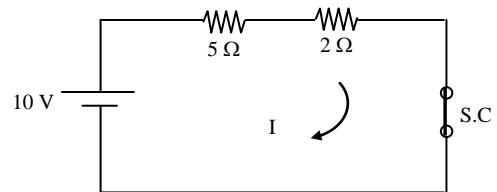

$$I = \frac{10}{7} \text{ A}$$

$$I_L = (0^-) = I_L(0^+)$$

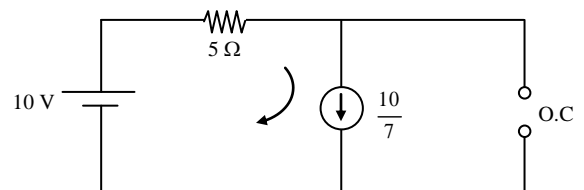at  $t = 0$ , Inductor acts as open circuit



Now, current in the circuit is

$$I = \frac{10}{7} \text{ A}$$

**09. Ans: (a)**

**Sol:** For an RL- circuit

$$\tau = \frac{L}{R} = \frac{1}{1} = 1 \text{ sec}$$

The condition for the transient free response

$$\omega t_0 + \phi = \tan^{-1} \omega \tau + \frac{\pi}{2}$$

$$\Rightarrow 1.t_0 + \frac{\pi}{3} = \tan^{-1}(1.1) + \frac{\pi}{2}$$



$$\Rightarrow t_0 + \frac{\pi}{3} = \frac{\pi}{4} + \frac{\pi}{2}$$

$$\Rightarrow t_0 = \frac{5\pi}{12}$$

**10. Ans: (a)**

**Sol:**  $X_C = \frac{1}{\omega C} = 8$

$X_{Leq} = 8$  for series resonance

$X_{L_1} = \omega L_1 = 2$

$X_{L_2} = \omega L_2 = 4$

$\rightarrow X_{L_1} + X_{L_2} = 6 < X_{Leq} = 8$

So coils must be connected in the aiding manner

$\Rightarrow L_{eq} = L_1 + L_2 + 2M$

$\omega L_{eq} = \omega L_1 + \omega L_2 + 2K \sqrt{\omega L_1 \cdot \omega L_2}$

$X_{Leq} = X_{L_1} + X_{L_2} + 2K \sqrt{X_{L_1} \cdot X_{L_2}}$

$\Rightarrow 8 = 2 + 4 + 2K \sqrt{2 \cdot 4}$


$\Rightarrow 8 = 6 + 4K \sqrt{2}$

$\Rightarrow 4K \sqrt{2} = 2$

$\Rightarrow K = \frac{1}{2\sqrt{2}}$

**11. Ans: (b)**

**Sol:**

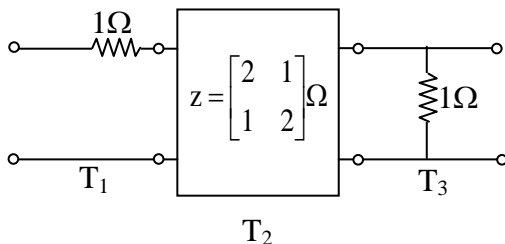

$T_1: Z_1 = 1\Omega$

$Z_2 = \infty\Omega$

$$T_1 = \begin{pmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 \\ \frac{1}{Z_2} & 1 \end{pmatrix} = \begin{pmatrix} 1 & 1 \\ 0 & 1 \end{pmatrix}$$

$T_2:$

$V_1 = 2I_1 + I_2$  -----(1)

$V_2 = I_1 + 2I_2$  -----(2)

(2)  $\Rightarrow I_1 = V_2 - 2I_2$  -----(3)

(3) in (1)

$V_1 = 2V_2 - 3I_2$  -----(4)

$$T_2 = \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$$

$T_3: Z_1 = 0\Omega$

$Z_2 = 1\Omega$

$$T_3 = \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix}$$

In cascade connection

$T = (T_1) \cdot (T_2) \cdot (T_3)$

$$= \begin{pmatrix} 1 & 1 \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 2 & 3 \\ 1 & 2 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix}$$

$$= \begin{pmatrix} 1 & 1 \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 5 & 3 \\ 3 & 2 \end{pmatrix} = \begin{pmatrix} 8 & 5 \\ 3 & 2 \end{pmatrix}$$

Check: Here  $AD - BC = 1$

Since passive and hence must be reciprocal.

**12. Ans: (a)**

**Sol:** Here,  $V = 10\sqrt{2} \sin(314t) = 10\sqrt{2} \angle 0^\circ$

$R = 1\Omega$



$$X_L = 314 \times 3.18 \times 10^{-3} \approx 1\Omega$$

$$\therefore Z = (1+j1)\Omega$$

$$\therefore I = \frac{V}{Z} = \frac{10\sqrt{2}\angle 0}{\sqrt{2}\angle 45} = 10\angle -45^\circ$$

$$\therefore I = 10\sin(314t - 45^\circ)$$

$$P_{\text{avg}} = \frac{V_m I_m}{2} \cos \phi$$

$$= \frac{10\sqrt{2} \times 10}{2} \cos(45^\circ) = \frac{100\sqrt{2}}{2} \times \frac{1}{\sqrt{2}}$$

$$= 50 \text{ Watts}$$

13. Ans: (d)

14. Ans: (d)

Sol: Here,  $V_c(0) = 4$  volts

$$V_c(\infty) = 1 \text{ Volts}$$

$$\tau = R_{\text{eq}}C = 2 \times \frac{1}{4} = \frac{1}{2} = 0.5 \text{ sec}$$

$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau}$$

$$= 1 + (4 - 1)e^{-2t} = 1 + 3e^{-2t} \text{ Volts}$$

15. Ans: (c)

Sol: The Voltage across resistor 'R' is

$$V_R(s) = I(s) \times 2$$


$$\Rightarrow V_R(s) = \frac{2}{s^2 + 2s + 2}$$

$$= \frac{2}{(s+1)^2 + 1}$$

$$\Rightarrow V_R(t) = 2e^{-t} \sin t u(t) \text{ Volts}$$

16. Ans: (a)

Sol:

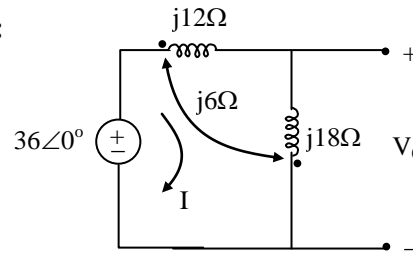

By KVL,  $-36\angle 0^\circ + j12I - j12I + j18I = 0$

$$\Rightarrow -36\angle 0^\circ + j18I = 0$$

$$\Rightarrow I = \frac{36\angle 0^\circ}{18\angle 90^\circ} = 2\angle -90^\circ = -j2 \text{ Ampere}$$

Again by KVL,  $-V_0 + j18I - j6I = 0$

$$\Rightarrow V_0 = j12I$$



$$\Rightarrow V_0 = j12 \times (-j2)$$


$$\Rightarrow V_0 = 24\angle 0^\circ$$

$$\Rightarrow V_0(t) = 24 \sin 2t \text{ Volts}$$

17. Ans: (a)

Sol:

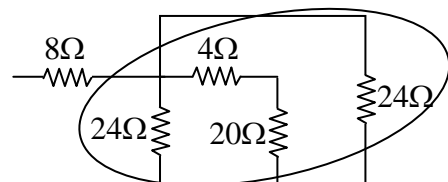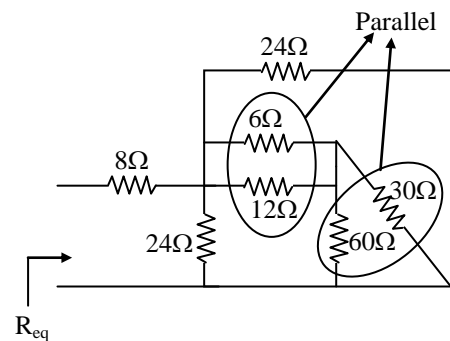

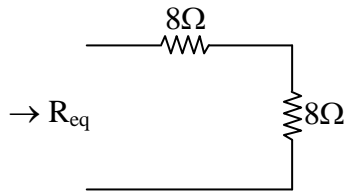

$$R_{eq} = 16\Omega$$

18. Ans: (b)

Sol: Rotor speed =  $\frac{120 \times \text{supply frequency}}{\text{Rotor poles}}$

$$= \frac{120 \times 50}{10}$$

$$= 600 \text{ rpm}$$

19. Ans: (b)

Sol: **Shaded pole motor:** These motors employ salient pole stator construction and cage type rotor with skewed slots.

**Hysteresis motor:** The stator winding is of the permanent split capacitor type or of the shaded pole type for very small sizes.

The periphery of the rotor is without any slots and therefore without any winding.

**Reluctance motor:** Stator is similar to the stator of any of the single phase induction motors. The rotor construction is completed just like squirrel cage rotor.

**Repulsion motor:** Stator of this motor carries a single phase exciting winding, similar to the main winding of a single phase induction motor. The rotor carries an

ordinary distributed dc type winding connected to the commutation at one end.

20. Ans: (b)

Sol: Given data:

$$B_{mA} = 1.2 \text{ wb/m}^2$$

$$B_{mB} = 1.4 \text{ wb/m}^2$$

So transformer with more flux densities will require less core area for given kVA.

$$A = \frac{\phi}{B_m}$$

So weight of transformer 'A' per kVA is more than that B.

21. Ans: (b)

Sol: With an air-gap introduced in the core, the reluctance of the core flux path increases appreciably. Hence magnetizing inductance decreases by a large amount, and the corresponding magnetizing reactance also becomes small. At rated voltage operation, the no-load current will become much larger. Option (b) is correct. Other options are obviously wrong.

22. Ans: (a)

Sol: With V and f variable but V/f constant, maximum core flux density  $B_{max}$  remains unchanged irrespective of values of V and f.

Hysteresis loss =  $K_h f B_{max}^x$ , thus changes as f changes.



Eddy current loss =  $K_e f^2 B_{max}^2$ , also changes as  $f$  changes.

**23. Ans: (b)**

**Sol:**  $S_{new} = S_{old} - \frac{E_j}{E_{20}}$

If  $E_j$  and  $E_{20}$  are in the same phase, then  $E_j$  and  $E_{20}$  have the same sign, there  $S_{new}$  decrease and the speed increase. If  $S_{old}$  is less than  $\frac{E_j}{E_{20}}$ ,  $S_{new}$  became negative, the rotor speed will be more than synchronous, super synchronous speed.

**24. Ans: (a)**

**25. Ans: (b)**

**Sol:** With constant excitation, the maximum flux density  $B_m$  in the armature core is constant. (It is only here that core losses occur).

Hysteresis loss =  $W_h = K_h f B_m^n$  where  $k_h$  &  $n$  are constants.

Eddy current loss =  $W_e = K_e f^2 B_m^2$  where  $k_e$  is constant.

As speed is doubled, frequency of flux reversals in armature core is doubled. Hence  $W_h$  is doubled while  $W_e$  increase by 4 times.


**26. Ans: (a)**

**Sol:** Based on the “Degree of compounding” the “cumulative compound machine” are classified has

(i) Over compound machine  $\Rightarrow V > E$

(ii) Under compound machine  $\Rightarrow V < E$

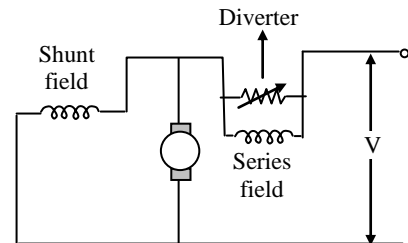(i) Flat compound machine  $\Rightarrow V = E$



The degree of compounding can be controlled (obtained) by connecting a suitable low resistance across series field winding called “diverter”.

**27. Ans: (b)**

**Sol: (i) O.C voltage:**

If the excitation is kept constant, induced emf which is equal to the O.C voltage is directly proportional to speed.

At rated speed, for an excitation  $I_f$  let the induced voltage =  $E$  volts. Then at 110% rated speed, for the same excitation, induced voltage =  $(110/100)E = 1.1 E$  volts.

**Induced voltage increases by 10%.**

**(ii) S.C current:**

Let synchronous inductance per phase be  $L_s$   
H. Let resistance (which will anyway be



small) be neglected. Consider an excitation

$I_f$

**At rated speed:** open-circuit voltage =  $E$ .

Let the frequency be  $f$  Hz. Synchronous reactance =  $2\pi fL_s$ . Short-circuit current ( $E/2\pi fL_s$ ).

**At 110% rated speed:** open-circuit voltage =  $1.1 E$  and synchronous reactance =  $2\pi(1.1f)L_s$ .

Short-circuit current =  $(1.1E)/2\pi(1.1f)L_s$   
=  $E/2\pi fL_s$ .

The short-circuit current is unaltered.

**28. Ans: (a)**

**Sol:** When only the winding on the salient pole rotor is excited:

Whatever be the position of the salient pole rotor, the path for the field flux is always one of least reluctance. Since reluctance torque tends to bring the rotor into a position where the reluctance of the flux path is minimum. Since the rotor is always in that position, no reluctance torque will be produced. **Statement 1 is wrong.**

When only the winding on the stator is excited:

Reluctance torque will be produced tending to align the rotor along the minimum reluctance position, that is, the stator axis.

**Statement 2 is correct.**

When windings on the rotor as well as the stator are excited:

There will be reluctance torque as well as electromagnetic torque. **Statement 4 is correct. Statement 3**, which implies that only electromagnetic torque is produced when both stator windings are excited but no reluctance torque, **is wrong.**

**29. Ans: (d)**

**Sol:** Power in watts  $P = \sqrt{3}V_L I_L \cos\phi$

Given  $P = 500$  MW,

$V_L = 12.5$  kV,  $\cos\phi = 0.8$  Pf

$\therefore$  Full load current

$$(I_L) = \frac{P}{\sqrt{3} V_L \cos\phi} = \frac{500 \times 10^6}{\sqrt{3} \times 12.5 \times 10^3 \times 0.8}$$

$$= 28.86 \text{ kA}$$

**30. Ans: (d)**

**Sol:** In the system  $AX = 0$ , if  $|A| \neq 0$  then the system has only zero solution.

**31. Ans: (b)**

**Sol:**  $f(x) = \frac{xe^{\frac{1}{x}}}{1 + e^{\frac{1}{x}}}$ ,  $x \neq 0$

$$= 0, \quad x = 0$$



$$\lim_{x \rightarrow 0^-} f(x) = \lim_{x \rightarrow 0^-} \left( \frac{x e^{\frac{1}{x}}}{1 + e^x} \right) = \frac{0}{1} = 0$$

$$\lim_{x \rightarrow 0^+} f(x) = \lim_{x \rightarrow 0^+} \left( \frac{x e^{\frac{1}{x}}}{1 + e^x} \right) = \lim_{x \rightarrow 0^+} \left[ \frac{x}{e^{\frac{1}{x}} + 1} \right] = 0$$

$$f(0) = 0$$

∴ f(x) is continuous at x = 0

**32. Ans: (a)**

**Sol:** If  $(-1 + \sqrt{3})$  is an eigen value of a matrix, then  $(-1 - \sqrt{3})$  is also an eigen value of A.

Let  $\lambda$  be the third eigen value of A. Sum of the eigen values = Trace of A.

$$\Rightarrow (-1 + \sqrt{3}) + (-1 - \sqrt{3}) + \lambda = 0$$

$$\Rightarrow \lambda = 2$$

**33. Ans: (c)**

**Sol:** Let  $I = \int_{-\pi}^{\pi} \sin^4 x \, dx$ ,

$$\text{Let } f(x) = \sin^4 x$$

$$f(-x) = \sin^4(\pi - x) = \sin^4 x = f(x)$$

∴ f(x) is even function

$$I = 2 \int_0^{\pi} \sin^4 x \, dx$$

$$= 2 \times 2 \int_0^{\pi/2} \sin^4 x \, dx = 4 \cdot \frac{3}{4} \cdot \frac{1}{2} \cdot \frac{\pi}{2} = \frac{3\pi}{4}$$

**34. Ans: (a)**

**Sol:** Let  $u = x^2 y$

$$\begin{aligned} \frac{du}{dx} &= \frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} \left( \frac{dy}{dx} \right) \\ &= 2xy + x^2 \left( \frac{dy}{dx} \right) \dots\dots (1) \end{aligned}$$

$$\text{Given, } x^2 + xy + y^2 = 1$$

Differentiating with respect to x, we have

$$2x + x \frac{dy}{dx} + y + 2y \frac{dy}{dx} = 0$$


$$\frac{dy}{dx} = - \left( \frac{2x + y}{x + 2y} \right)$$

Substituting in (1), we have

$$\frac{du}{dx} = 2xy - x^2 \left( \frac{2x + y}{x + 2y} \right)$$

**35. Ans: (a)**

**Sol:**

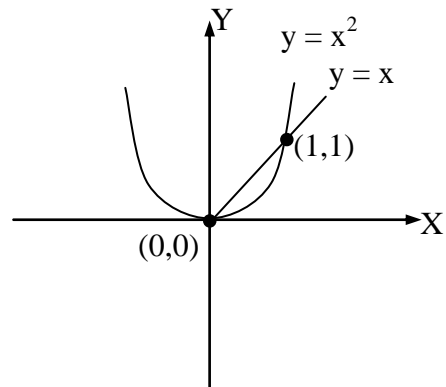

Green's theorem is

$$\begin{aligned} \oint_C (M \, dx + N \, dy) &= \iint_R \left( \frac{\partial N}{\partial x} - \frac{\partial M}{\partial y} \right) dx \, dy \\ \Rightarrow \oint_C [(xy + y^2) \, dx + x^2 \, dy] &= \iint_R [2x - (x + 2y)] \, dx \, dy \\ \Rightarrow \int_{x=0}^1 \int_{y=x^2}^x (x - 2y) \, dx \, dy \end{aligned}$$





$$\begin{aligned} &= \int_{x=0}^1 \{xy - y^2\}_{y=x^2}^x dx \\ &= \int_{x=0}^1 \{(x^2 - x^2) - (x^3 - x^4)\} dx \\ &= \int_0^1 (x^4 - x^3) dx = \left( \frac{x^5}{5} - \frac{x^4}{4} \right)_0^1 \\ &= \frac{1}{5} - \frac{1}{4} = \frac{-1}{20} \end{aligned}$$

**36. Ans: (d)**

**Sol:** A pair of fair dice is tossed 2 times.

Probability of not getting 7 or 11

$$= 1 - \left( \frac{6+2}{36} \right) = \frac{28}{36} = \frac{7}{9}$$

$$\text{Required probability} = \frac{7}{9} \times \frac{7}{9} = \frac{49}{81}$$

**37. Ans: (b)**

**Sol:** Given  $\frac{dy}{dx} = e^{x+y}$ ,  $y(1) = 1$

$$\frac{dy}{dx} = e^x e^y$$

$$\Rightarrow \int e^{-y} dy = \int e^x dx$$

$$\Rightarrow -e^{-y} dy = e^x + C$$

$$\Rightarrow e^x + e^{-y} = k$$

$$\dots\dots\dots (1)$$

$$y(1) = 1, (1) \Rightarrow e + e^{-1} = k$$

$$\Rightarrow \frac{e^2 + 1}{e} = k$$

$$(1) \Rightarrow e^x + e^{-y} = \frac{e^2 + 1}{e}$$

when  $x = -1$

$$e^{-1} + e^{-y} = \frac{e^2 + 1}{e}$$

$$\Rightarrow e^{-y} = \frac{e^2 + 1}{e} - \frac{1}{e} = \frac{e^2 + 1 - 1}{e} = e$$

$$\Rightarrow -y = 1$$

$$\therefore y = -1$$

**38. Ans: (b)**

**Sol:**  $f(z) = \frac{9z+i}{1-\cos z}$

$$= \frac{9z+i}{1 - \left[ 1 - \frac{z^2}{2!} + \frac{z^4}{4!} - \frac{z^6}{6!} + \dots \right]}$$

$$= \frac{9z+i}{\left( \frac{z^2}{2!} - \frac{z^4}{4!} + \frac{z^6}{6!} - \dots \right)}$$

$$= \frac{(9z+i)}{z^2 \left[ \frac{1}{2!} - \frac{z^2}{4!} + \frac{z^4}{6!} - \dots \right]}$$

Let  $\phi(z) = 9z + i$

$$\phi(0) = i = \sqrt{-1} \neq 0$$

$\therefore z = 0$  is a double pole (or) pole of order 2

**39. Ans: (c)**

**Sol:** Given  $f(z) = \frac{2z}{(z-1)^2(z-2)}$

$F(z)$  has singular points at  $z = 1$  and  $z = 2$



$\Rightarrow z = 1$  is a pole of order two and  $z = 2$  is a pole of order one.

$$r_1 = \text{res}(f(z) : z = 2)$$

$$= \text{Lt}_{z \rightarrow 2} \left[ (z-2) \cdot \frac{2z}{(z-1)^2(z-2)} \right] = 4$$

$$R_2 = \text{Res}(f(z) : z = 1)$$

$$= \frac{1}{(m-1)!} \text{Lt}_{z \rightarrow z_0} \left[ \frac{d^{m-1}}{dz^{m-1}} \left\{ (z-z_0)^m f(z) \right\} \right]$$

$$= \frac{1}{(2-1)!} \text{Lt}_{z \rightarrow 1} \left[ \frac{d}{dz} \left\{ (z-1)^2 \cdot \frac{2z}{(z-1)^2(z-2)} \right\} \right]$$

$$= \text{Lt}_{z \rightarrow 1} \left[ \frac{(z-2)(2) - (2z)(1)}{(z-2)^2} \right] = -4$$

$$\therefore \text{Sum of residues of } f(z) = R_1 + R_2 \\ = 4 - 4 = 0$$

**40. Ans: (c)**

$$\text{Sol: } \frac{dy}{dx} = \frac{1 + 2 \cos^2 y - 1}{1 - (1 - 2 \sin^2 x)} = \frac{\cos^2 y}{\sin^2 x}$$

$$\Rightarrow \int \sec^2 y \, dy = \int \text{cosec}^2 x \, dx$$

$$\Rightarrow \tan y = -\cot x + C$$

$\therefore$  The solution is  $\tan y + \cot x = C$

**41. Ans: (a)**

$$\text{Sol: } V(x, y, z) = -(x \cos xy + y) \bar{i} + (y \cos xy)$$

$$\bar{j} + [\sin z^2 + x^2 + y^2] \bar{k}$$

$$\text{div } \bar{V} =$$

$$\frac{\partial}{\partial x} [-(x \cos xy + y)] + \frac{\partial}{\partial y} [y \cos xy]$$

$$+ \frac{\partial}{\partial z} [\sin z^2 + x^2 + y^2] = 2z \cos z^2$$

**42. Ans: (B)**

**Sol:** The brake magnet of an error free electro mechanical induction type energy meter is shifted from its position and moved a small distances towards the edge of the disc then the meter will continue to work, but register a lower kwh

**43. Ans: (C)**

$$\text{Sol: } \% \text{ error} = \left[ \frac{1.11}{1.57} - 1 \right] \times 100\% \\ = -29.29\%$$

**44. Ans: (c)**

**Sol:** Power factor of the load,

$$p.f = \cos \left[ \frac{2.5}{\sqrt{(2.5)^2 + 10^2}} \right] = 0.24 \text{ lag}$$

**Two wattmeter method of 3- $\phi$  power measurement:**

$$W_1 = V_L I_L \cos [30 - \phi]$$

$$W_2 = V_L I_L \cos [30 + \phi]$$

The relation between two meter readings for different power factors is shown in below table.

$\phi$	Power factor	$W_1$ & $W_2$
0	1	$W_1 = W_2$
30	0.866	$W_1 = 2W_2$
60	0.5	$W_1 \times W_2 = 0$
90	0	$W_1 = -W_2$



Power factor,  $p.f < 0.5$

∴ One of the wattmeter will indicate negative value.

**45. Ans: (b)**

**Sol:** →Parallel- comparator type ADC is fastest among the above given.

→Dual slope integrating type ADC's more accurate but slower

**46. Ans: (c)**

**Sol:**  $Q = \omega C_4 R_4$   
 $= 2\pi \times 1000 \times 0.5 \times 10^{-6} \times 1000$   
 $= 3.14$

**47. Ans: (c)**

**Sol:** The main sources of error that introduce error into Q-indication in direct connection of Q-meter are insertion resistance in Q-meter & self capacitance of test coil

**48. Ans: (a)**

**Sol:** We know that,  $T_1 = nT_s$

Where,  $T_1 =$  horizontal sweep speed

$T_s =$  Vertical input time period

∴ Here  $T_1 = 0.4$  millisecond

$$T_s = \frac{1}{5 \times 10^3} = 0.2 \text{ milliseconds}$$

$$\therefore n = \frac{T_1}{T_s} = \frac{0.4}{0.2} = 2$$

**49. Ans: (c)**

**Sol:** The average value for the set of measurements is given by

$$\bar{X}_n = \frac{\sum X_n}{10} = \frac{1005}{10} = 100.5$$

$$\text{Precision} = 1 - \left| \frac{X_n - \bar{X}_n}{\bar{X}_n} \right|$$

For the 6<sup>th</sup> reading, Precision

$$= 1 - \left| \frac{100 - 100.5}{100.5} \right| = 1 - \frac{0.5}{100.5} = \frac{100}{100.5} = 0.995$$

**50. Ans: (a)**

**Sol:** A piezoelectric transducer cannot be used to measure static variable

**51. Ans: (d)**

**Sol:**

1. Venture tube ..... Flow
2. Optical tachometer... Velocity
3. LVDT..... Displacement
4. Pirani gauge..... Pressure

**52. Ans: (c)**

**Sol:**  $G = 1+2v$

$$G = \frac{\left( \frac{\Delta R}{R} \right)}{\epsilon}$$

$$= \frac{(1009 - 1000)/1000}{0.0015} = 6$$

$$6 = 1+2v$$

$$\Rightarrow v = 2.5$$



SHORT TERM BATCHES

# SUMMER

## SHORT TERM BATCHES

### GATE+PSUs - 2020

Admissions Open From 14<sup>th</sup> NOV 2018

#### HYDERABAD

29<sup>th</sup> April | 06<sup>th</sup> May | 11<sup>th</sup> May

18<sup>th</sup> May | 26<sup>th</sup> May | 02<sup>nd</sup> June 2019

#### DELHI

11<sup>th</sup> May | 23<sup>rd</sup> May 2019

Start Early.. Gain Surely...

### EARLY BIRD OFFER :

Register on or Before 31<sup>st</sup> December 2018 : 5000/- Off | Register on or Before 31<sup>st</sup> March 2019 : 3000/- Off



## TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

### Pre GATE - 2019

Date of Exam : 20<sup>th</sup> January 2019

Last Date to Apply : 31<sup>st</sup> December 2018

#### Highlights :

- Get real-time experience of **GATE-2019** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post GATE guidance sessions by experts.
- Encouraging awards for **GATE-2019** toppers.



53. Ans: (d)

Sol: Error at CF =  $|-20 \log 2 \zeta| = |-20 \log 2 (0.4)| = 2\text{dB}$

54. Ans: (c)

Sol: Transfer function of given plot is

$$T.F = \frac{K(s+a)}{s(s-b)}$$

$$M = \frac{K \sqrt{\frac{\omega^2}{a^2} + 1}}{\omega \sqrt{\frac{\omega^2}{b^2} + 1}}$$

$$\phi = -90^\circ + \tan^{-1}\left(\frac{\omega}{a}\right) - \left[180^\circ - \tan^{-1}\left(\frac{\omega}{b}\right)\right]$$

	M	$\phi$
$\omega = 0$	$\infty$	$-270^\circ$
$\omega = \infty$	0	$-90^\circ$

It is type-1 system

$K_v = \text{finite}$

For type-1 system steady state error due to ramp input is finite.

For type-1 system steady state error due to parabolic input is infinite.

55. Ans: (a)

$$\text{Sol: } T(s) = \frac{R_2 + \frac{1}{Cs}}{R_1 + R_2 + \frac{1}{Cs}} = \frac{R_2Cs + 1}{(R_1 + R_2)Cs + 1}$$

$$T(s) = \frac{0.001s + 1}{0.003s + 1}$$

$$\tau = 0.001$$


$$\alpha\tau = 0.003$$

$$\alpha = 3$$

$$\phi_m = \sin^{-1}\left[\frac{1-\alpha}{1+\alpha}\right]$$

$$= \sin^{-1}\left[\frac{-2}{4}\right] = \sin^{-1}\left(\frac{-1}{2}\right)$$

$$\phi_m = -30^\circ$$

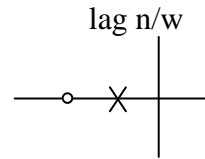

56. Ans: (a)

Sol: Angle of asymptotes  $\phi = \frac{(2\ell+1)\pi}{P-Z}$   $\ell = 0, 1, 2, \dots, |P-Z| - 1$

$$2 \dots \dots \dots |P-Z| - 1$$

Number of poles  $P = 3$


Number of zeros  $Z = 0$

$$\phi_0 = \frac{\pi}{4}, \phi_1 = \frac{3\pi}{4}, \phi_2 = \frac{5\pi}{4}, \phi_3 = \frac{7\pi}{4}$$

57. Ans: (c)

$$\text{Sol: } G(s) = \frac{10(1+s/5)}{s\left(1+\frac{s}{2}\right)\left(1+\frac{s}{20}+\frac{s^2}{100}\right)}$$

Magnitude plot

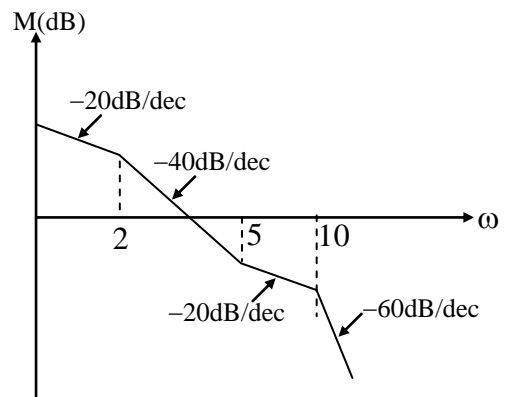



At  $\omega=0$  rad/sec change in slope

$\Rightarrow -20$  dB/dec to  $-60$  dB/dec

**58. Ans: (d)**

**Sol:** Number of poles  $P = 2$

Number of zero  $Z = 2$

Number of asymptotes  $= |P - Z| = 0$

$\therefore$  asymptotes does not exist.

**59. Ans: (c)**

**Sol:**  $G(s)H(s) = \frac{K}{s-2}$

$K|_{s=0} = |s-2|_{s=0} = 2$

**60. Ans: (b)**

**Sol:** Closed loop gain  $= \frac{8}{1 - \frac{8}{4}} = -8$

**61. Ans: (b)**

**Sol:** Using dominant pole approximation

T.F  $= \frac{150}{(s+2) \times 150} \Rightarrow \frac{1}{s+2}$

Time constant  $\tau = \frac{1}{2}$  sec

For 5% criterion,  $3\tau \Rightarrow 3/2$  sec

**62. Ans: (a)**

**Sol:** Given system is unstable if  $\frac{32-K}{8} < 0$

$32 < K$

$K > 32$

**63. Ans: (a)**

**Sol:** Number of loops  $= 0$

Number of forward paths  $= 9$

Number of two non touching loops  $= 0$

**64. Ans: (b)**

**Sol:**  $G(s) = \frac{K \times 100}{s^2 + 10s + 100}$

$s^2 + 10s + 100 \Rightarrow s^2 + 2s\xi\omega_n + \omega_n^2$

$\omega_n = 10$

$\xi = \frac{1}{2}$

$M = \frac{K}{2\xi\sqrt{1-\xi^2}} = \frac{10}{\sqrt{3}}$

$= \frac{K}{2(0.5)\sqrt{1-(0.5)^2}} = \frac{10}{\sqrt{3}}$

$K = 5$

**65. Ans: (a)**

**Sol:** C.E  $= \det [sI - A] = 0$

$\begin{vmatrix} s & 0 & 0 \\ 0 & s & 0 \\ 0 & 0 & s \end{vmatrix} - \begin{vmatrix} 0 & 0 & -20 \\ 1 & 0 & -24 \\ 0 & 1 & -9 \end{vmatrix} = 0$

$\begin{vmatrix} s & 0 & +20 \\ -1 & s & +24 \\ 0 & -1 & s+9 \end{vmatrix} = 0$

$s[s(s+9)+24] - 0 + 20(1) = 0$

$s^3 + 9s^2 + 24s + 20 = 0$



$s^3$	1	24
$s^2$	9	20
$s^1$	$\frac{9(24)-20}{9}$	0
$s^0$	20	

All coefficient of 1<sup>st</sup> row are positive. So, system is stable

**66. Ans: (c)**

**Sol:** The common alloying elements added to steel for improving its oxidation resistance are chromium, aluminum and nickel.

**67. Ans: (d)**

**Sol:**

- The most common copper alloys are the brasses, for which zinc, as a substitutional impurity, is the predominant alloying element.
- Some of the common uses for brass alloys include costume jewelry, cartridge casings, automotive radiators, musical instruments, electronic packaging and coins. Hence, given statement is incorrect.
- The bronzes are alloys of copper and several other elements, including tin, aluminum, silicon and nickel. These alloys are somewhat stronger than the

brasses, yet they still have a high degree of corrosion resistance.

- Applications include jet aircraft landing gear bearings and bushings, springs and surgical and dental instruments.

**68. And: (a)**

**Sol:**

Dominant Characteristics	Crystal structure
High strength	BCC
High ductility	FCC
Tend to be brittle	HCP

**69. Ans: (c)**

**Sol:** Poles of the system are at  $z = \pm j$

Since ROC is exterior of a circle hence system is causal.

But ROC is not including unit circle. So, system is unstable

$$\text{Now } H(z) = \frac{z}{z^2 + 1}, |z| > 1$$

$$\sin(\omega_0 n) u(n) \leftrightarrow \frac{z \sin \omega_0}{z^2 - 2z \cos \omega_0 + 1}, |z| > 1$$

$$z^2 + 1 = z^2 - 2z \cos \omega_0 + 1$$

$$\therefore 2z \cos \omega_0 = 0$$

$$\therefore \omega_0 = \frac{\pi}{2}$$

$$\therefore \sin\left(\frac{\pi}{2} n\right) u(n) = \frac{z \sin\left(\frac{\pi}{2}\right)}{z^2 - 2z \cos\left(\frac{\pi}{2}\right) + 1} = \frac{z}{z^2 + 1}$$

$$h(n) = \sin\left(\frac{\pi}{2} n\right) u(n)$$



70. Ans: (a)

Sol: In super conducting state, resistivity and the magnetic flux density is zero and since the super conductor is almost a perfect diamagnet, its susceptibility is negative and equal to units, shows  $\mu_x = 1 + \chi$  is almost zero. However, the transition between superconducting and normal states is reversible.

71. Ans: (b)

Sol: The soft magnetic materials have low hysteresis.

72. Ans: (d)

Sol: The values of dielectric strength are given as

Materials	Dielectric strength (kV/inch)
Rubber	450 to 550
Teflon	1500
Bakelite	300 to 550
Glass	2000 to 3000

73. Ans: (c)

Sol: Aluminum is a metal its resistivity is the lowest, where as mica is an insulator with highest resistivity. As pure silicon is an intrinsic semiconductor whose resistivity is slightly higher than the doped extrinsic silicon which has more charge carrier in it.

74. Ans: (c)

Sol: All the statements are correct. In fact soft superconductors also follow Meissner effect.

75. Ans: (b)

Sol: In Anti-ferromagnetic materials, above a specific Neel temperature the anti parallel arrangement breakdown and the material becomes paramagnetic, temperature dependence of susceptibility, i.e. When  $T >$

$$T_N \text{ (Neel Temperature)} \chi = \frac{C}{T+\theta}$$

76. Ans: (a)

Sol: Lead zirconate,  $\{Pb[zrxTil-x]O_3\}$ ,  $(0 \leq x \leq 1)$ , an inter metallic, inorganic compound is the most common piezo electric ceramic use

77. Ans: (c)

Sol: Turn ON delay time can be reduced by increasing gate current magnitude. Current rise time can be decreased by increasing rate of rise of gate current that is  $\frac{di_g}{dt}$ .

78. Ans: (a)

Sol: For turning ON of a N-MOS  $V_{GS} > V_{th}$  .So, during turn ON delay time gate to source voltage rises from zero to threshold value.





**79. Ans: (d)**

**Sol:**  $V_{th} \propto \phi_{ms}$ ;

$$\phi_{ms} = \phi_m - \phi_s$$

$\phi_m$  = work function of metal

$\phi_s$  = work function of semiconductor

$\phi_s \propto V_T \propto T$  (temperature)

So,  $V_{TH}$  decreases with increase in junction temperature.

As MOSFET is majority carrier device  $R_{DS}$  (resistance) increases with increase in temperature.

**80. Ans: (c)**

**Sol:** Blocking voltage of a layer is always determined by both thickness and doping level of the layer.

**81. Ans: (b)**

**Sol:** As IGBT acts as positive temperature coefficient device in conduction mode it can be inferred that most of the current flows through MOSFET.

**82. Ans: (b)**

**Sol:** In a three phase full converter each thyristor conducts for  $120^\circ$ .

$$\text{So, } I_{T, \text{rms}} = \frac{I}{\sqrt{3}},$$

$$I_{T, \text{avg}} = \frac{I}{3}$$

**83. Ans: (c)**

**Sol:** In a 3 pulse converter for  $\alpha = 60^\circ$ , both SCR and FD conduct for  $60^\circ$  each.

$$I_{T, \text{rms}} = I_0 \sqrt{\frac{60}{360}} = \frac{I_0}{\sqrt{6}}$$

As there are three SCR's, FD conducts for  $3 \times 60 = 180^\circ$ .

$$I_{FD, \text{rms}} = I_0 \sqrt{\frac{180}{360}} = \frac{I_0}{\sqrt{2}}$$

$$\therefore \text{Ratio} = 1 : \frac{1}{\sqrt{6}} : \frac{1}{\sqrt{2}}$$


**84. Ans: (d)**

**85. Ans: (a)**

**Sol:** For low variations of voltage, control circuit required is minimum. So cost is less.

**86. Ans: (c)**

**Sol:**

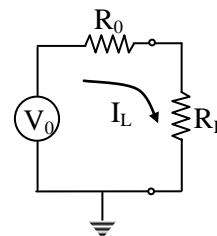

**Step (1):** For maximum power transfer into the load

$$R_L = R_0 = 4\Omega \text{ ----- (1)}$$

$$\Rightarrow I_L = \frac{V_0}{R_0 + R_L} = \frac{6V}{8\Omega} = \frac{3}{4} \text{ A ----- (2)}$$

$$\text{Step (2): } P_{L\text{max}} = I_L^2 R_L \text{ ----- (3)}$$




$$= \left(\frac{3}{4}\right)^2 \times 4W \text{ ----- (4)}$$

$$= \frac{3 \times 3}{4 \times 4} \times 4W \text{ ----- (5)}$$

$$P_{Lmax} = 2.25 W \text{ ----- (6)}$$

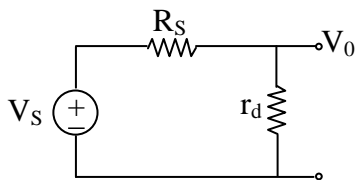**87. Ans: (a)**

**Sol:** The small signal equivalent circuit is as follows



For small signal response, open DC current source, short capacitors  $C_1$  and  $C_2$ . Replace diode with its small signal resistance ( $r_d$ ).

$$r_d = \frac{\eta V_T}{I}$$

$$V_0 = V_s \left[ \frac{r_d}{r_d + R_s} \right] = V_s \frac{\frac{\eta V_T}{I}}{\frac{\eta V_T}{I} + R_s}$$

$$V_0 = V_s \frac{\eta V_T}{\eta V_T + IR_s}$$

**88. Ans: (b)**

**Sol:**

- For CMRR to be high, common mode gain,  $|A_C| = \frac{R_C}{2R_E}$  should be low. In a differential amplifier, when  $R_E$  is

replaced with current mirror, as the current mirror is a constant current source, the common mode gain,  $A_C$  will be almost zero and hence CMRR becomes very high.

- Level shifter in op-amps reduce/shifts the unwanted DC level to almost zero, during AC amplification.
- Virtual ground in op-amps exist in case of open-loop gain of op-amp is very high (ideally infinite)
- Mismatching of internal transistors & false grounding are the two main reasons beyond error/off set voltage in op-amps.

**89. Ans: (d)**

**Sol:** In CS amplifier,  $A_V = \frac{V_0}{V_i} = -g_m (R_D // r_d) \Rightarrow$

$V_0$  is  $180^\circ$  out of phase with  $V_i$

In source follower (CD amplifier),  $R_0 =$

$$R_s // \frac{1}{g_m} \Rightarrow \text{If } R_s \text{ is large, } R_0 \approx \frac{1}{g_m}$$

In common gate amplifier,  $R_i = R_s // \frac{1}{g_m}$

and is low

**90. Ans: (a)**

**Sol:**  $s(t) = 10 \cos\{2\pi \times 10^6 t + 5 \cos(2\pi \times 10^3 t) + 10 \cos(4\pi \times 10^3 t)\}$



$$\begin{aligned} \Delta\phi &= \theta_{i,\max} \\ &= |5 \cos(2\pi \times 10^3 t) + 10 \cos(4\pi \times 10^3 t)|_{\max} \\ &= 15 \end{aligned}$$

**91. Ans: (a)**

**Sol:** For proper demodulation of  $m(t)$  [where  $\mu < 1$ ] using envelope detection, the time

constant 'RC' is  $RC \leq \frac{1}{\omega_m} \left[ \frac{\sqrt{1-\mu^2}}{\mu} \right]$

$$\therefore RC_{\max} = \frac{1}{\omega_m} \left[ \frac{\sqrt{1-\mu^2}}{\mu} \right]$$

**92. Ans: (b)**

**Sol:** The bandwidth of IF amplifier in FM is 200kHz


**93. Ans: (c)**

**Sol:** Bandwidth =  $2(\beta+1)f_m$

The ratio of frequency deviation and message signal frequency is called modulation index.

Since both becoming doubled modulation index will not change but bandwidth is directly proportional to message signal frequency. Hence bandwidth becomes doubled.

**94. Ans: (a)**

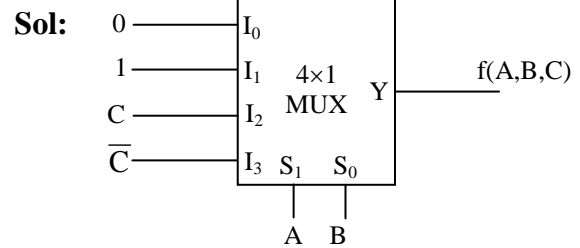

A B	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>
S <sub>1</sub> S <sub>0</sub>	0 0	0 1	1 0	1 1
$\bar{C}$ (0)	0	②	4	⑥
C (1)	1	③	⑤	7
	0	1	C	$\bar{C}$

$$f(A,B,C) = \sum m(2, 3, 5, 6)$$

	BC			
A	00	01	11	10
0			1	1
1		①		1

Minimized expression

$$f(A,B,C,D) = \bar{A}B + B\bar{C} + A\bar{B}C$$

**95. Ans: (a)**

**Sol:** A = 11110111  $\Rightarrow -9$

B = 00110111  $\Rightarrow +55$

A - B  $\Rightarrow -64$

$$\begin{array}{r} 11110111 \\ + 11001001 \\ \hline 11000000 \Rightarrow -64 \end{array}$$

**96. Ans: (a)**

**Sol:** For  $Q_3Q_2Q_1Q_0 = 1001$

$\Rightarrow$  Flip-Flops are cleared.

It counts from 0000, ..... 1000, 0000,.....

Its modulus = 9.



Launching  
**Spark Batches** for  
**ESE / GATE - 2020**  
from Mid May 2019

Admissions from January 1<sup>st</sup>, 2019

**@ DELHI**



Launching  
**Regular Batches** for  
**ESE / GATE - 2020**  
from Mid May 2019

Admissions from January 1<sup>st</sup>, 2019

**@ BHOPAL & LUCKNOW**



**97. Ans: (c)**

**Sol:** Analog output

$$= V_0 = K[2^3 b_3 + 2^2 b_2 + 2^1 b_1 + 2^0 b_0]$$

Given  $V_0 = 4.5V$  for Digital Input 1001 = 9  
input

$$\therefore K = \frac{V_0}{V_{in}} = \frac{4.5}{9} = 0.5$$

For digital Input = 0110 = 6

$$\text{Output} = K [6] = 0.5 \times 6 = 3V$$

**98. Ans: (c)**

**Sol:** A. Involution theorem :  $(x^1)^1 = x$

B. Absorption theorem :  $x + xy = x$

Proof:  $x + xy$

$$= x.1 + xy$$

$$= x(1+y)$$

$$= x.1$$

$$= x$$

C. Demorgan theorem :  $(x+y)^1 = x^1 y^1$

$$\text{Dual : } (xy)^1 = x^1 + y^1$$

D. Associative theorem :  $x+(y+z) = (x+y)+z$

$$\text{Dual : } x(yz) = (xy)z$$

**99. Ans: (c)**

**Sol:** After push, pop instruction  $DE = HL = 8500_H$

After DAD instruction,  $HL + DE \rightarrow HL$

$$\text{i.e., } 8500_H + 8500_H \rightarrow HL = 0A00_H$$

**100. Ans: (c)**

**Sol:**  $V_{BE} = 6V$ ,  $V_{BC} = 3V$ . Both junctions are Forward-bias.

Hence saturation region.

**101. Ans: (b)**

**Sol:** We have collector current

$$i_c = i_s \exp\left(\frac{V_{BE}}{\eta V_T}\right), \quad i_c = \beta I_B$$

$$\text{Trans conductance } (g_m) = \frac{\partial i_c}{\partial V_{BE}}$$

$$= \frac{i_s}{\eta V_T} \exp\left(\frac{V_{BE}}{\eta V_T}\right) = \frac{i_c}{\eta V_T}$$

$$r_\pi = \frac{\partial V_{BE}}{\partial i_B} = \frac{\partial V_{BE}}{\frac{1}{\beta} \partial i_c} = \frac{\beta}{g_m} = \frac{\eta \beta V_T}{i_c}$$

$$\therefore r_\pi = \frac{\eta \beta V_T}{i_c}$$

**102. Ans: (b)**

$$\text{Sol: } C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-14}}{50 \times 10^{-7}} = 69 \text{ nF/cm}^2$$

**103. Ans: (c)**

**Sol:** From graph, it can be easily seen that

$$V_{th} = 1V.$$

$$\text{Now, } V_{GS} = 3 - 1 = 2V.$$

$$\text{and } V_{DS} = 5 - 1 = 4V.$$

$$\text{Since } V_{DS} > V_{GS} \rightarrow V_{DS} > V_{GS} - V_T$$

Thus MOSFET is in saturation region.



**104. Ans: (b)**

**Sol:** Given  $x(n) = \cos\left(\frac{n\pi}{4}\right)$

$N = 4$

So,  $x(n) = \left\{1, \frac{1}{\sqrt{2}}, 0, -\frac{1}{\sqrt{2}}\right\}$

$$X(k) = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & -j & -1 & j \\ 1 & -1 & 1 & -1 \\ 1 & j & -1 & -j \end{bmatrix} \begin{bmatrix} 1 \\ 1/\sqrt{2} \\ 0 \\ -1/\sqrt{2} \end{bmatrix}$$

$X(k) = \{1, 1 - j1.414, 1, 1 + j1.414\}$

**105. Ans: (a)**

**Sol:**  $y(n) = 0.2x(n) - 0.5x(n-2) + 0.4x(n-3)$

Apply z-transform

$Y(z) = 0.2X(z) - 0.5z^{-2}X(z) + 0.4z^{-3}X(z)$

$H(z) = \frac{Y(z)}{X(z)} = 0.2 - 0.5z^{-2} + 0.4z^{-3}$

Apply Inverse z-transform, then

$h(n) = \{0.2, 0, -0.5, 0.4\}$

Given input  $x(n) = \{-1, 1, 0, 1\}$

$y(n) = x(n)*h(n)$

$$\begin{matrix} & 0.2 & 0 & -0.5 & 0.4 \\ -1 & \begin{bmatrix} -0.2 & 0 & 0.5 & -0.4 \\ 0.2 & 0 & -0.5 & 0.4 \\ 0 & 0 & 0 & 0 \\ 0.2 & 0 & -0.5 & 0.4 \end{bmatrix} \end{matrix}$$

$y(n) = \{-0.2, 0.2, 0.5, -0.7, 0.4, -0.5, 0.4\}$

$y(2) = 0.5$

**106. Ans: (c)**

**Sol:** To reduce the side lobes, it is desirable to optimize the frequency specification in the transition band of the filter. This optimization can be accomplished numerically on a digital computer by means of linear programming techniques.

**107. Ans: (b)**

**Sol:** Given  $H(\omega) = -3e^{-j2\omega}$

So,  $h(t) = -3\delta(t-2)$

Given  $x(t) = u(t) + \delta(t-3)$

$y(t) = x(t) * h(t)$

$= [u(t) + \delta(t-3)] * [-3\delta(t-2)]$

$= -3[u(t)*\delta(t-2) + \delta(t-3)*\delta(t-2)]$

$= -3[u(t-2) + \delta(t-5)] = -3u(t-2) - 3\delta(t-5)$

**108. Ans: (a)**

**Sol:**  $x(3t)$  is compressed by 3, So  $T = 2$ secs.

$P_{x(t)} = \frac{1}{T} \int_0^T |x(t)|^2 dt$

$P_{x(3t)} = \frac{1}{\left(\frac{T}{3}\right)} \int_0^{\frac{T}{3}} |x(3t)|^2 dt$

$P_{x(3t)} = P_{x(t)}$

$\therefore$  Power does not change.

**109. Ans: (c)**

**Sol:**  $\alpha^n x(n) \leftrightarrow X\left(\frac{Z}{\alpha}\right)$  with  $ROC = |\alpha|R$

$ROC = \left(\frac{5}{4}\right)(0.8) = 1$



**110. Ans: (c)**

$$\text{Sol: } \left(\frac{1}{2}\right)^n u(n) \xrightarrow{\text{DTFT}} \frac{1}{1 - \frac{1}{2}e^{-j\omega}}$$

$$Y(k) = X(e^{j\omega}) \Big|_{\omega = \frac{2\pi k}{10}} ; 0 \leq k \leq 9$$

$$Y(k) = \frac{1}{1 - \frac{1}{2}e^{-\frac{j2\pi k}{10}}} ; 0 \leq k \leq 9$$

$$a^n ; 0 \leq n \leq N-1 \longleftrightarrow \frac{1 - a^N}{1 - ae^{-\frac{j2\pi k}{N}}}$$

$$\left(\frac{1}{2}\right)^n \quad 0 \leq n \leq 9 \longleftrightarrow \frac{1 - \left(\frac{1}{2}\right)^{10}}{1 - \left(\frac{1}{2}\right)e^{-\frac{j2\pi k}{N}}}$$

$$y(n) = \frac{\left(\frac{1}{2}\right)^n}{1 - \left(\frac{1}{2}\right)^{10}} ; 0 \leq n \leq 9$$

**111. Ans: (c)**

**Sol:** Change in generation contributed by load is

$$\Delta P_g = \frac{-\Delta f}{R}$$

Drop on frequency,  $\Delta f = -0.0015$

$$\Delta P_g = \frac{-(-0.0015 \text{ pu})}{0.01 \text{ pu}} = 0.15 \text{ pu}$$

**112. Ans: (a)**

**Sol:** Always steady state stability limit is greater than transient stability limit. Steady state stability is due to the small and gradual variation of load where as Transient stability

limit is due to the sudden and large variation of load

**113. Ans: (b)**

$$\text{Sol: } SC \text{ MVA} = \frac{100}{0.2} = 500$$

**114. Ans: (a)**

**Sol:** Given Data

$$V_1 = 110 \text{ kV}, V_2 = 110 \text{ kV}, X = 100 \Omega$$

$$P = \frac{V_1 V_2}{X} \sin \delta$$

$$\text{(or) } P_{\max} = \frac{V_1 V_2}{X} \{ \sin \delta = 1 \}$$

$$\Rightarrow P_{\max} = \frac{110 \times 110}{100} = 121 \text{ MW}$$

**115. Ans: (b)**

**Sol:** Let radius of each sub conductor be 'r' and radius of single solid conductor be R then

$$\pi R^2 = 4 \times \pi r^2$$

$$R^2 = 4 r^2 \Rightarrow R = 2r$$

$$r = \frac{R}{2} = \frac{40 \text{ mm}}{2} = 20 \text{ mm}$$

**116. Ans: (c)**

**Sol:** Generally lighting strikes on topmost conducting body on the earth surface, to protect power lines from lightning strokes a wire kept on top of tower through the length by directly connecting that to the tower which is known as ground wire (or) earth



wire (or) lighting shield wire. This wire protects power lines only from direct lighting strokes, it won't carry neutral current and it won't protect system from indirect lighting strokes.

**117. Ans: (a)**

**Sol:** Output impedance of the transmission is given by

$$\text{Output impedance of the line} = \frac{V_r}{I_r}$$

$$\text{as } \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_r \\ I_r \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$= \frac{1}{AD-BC} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$\text{AS } AD-BC = 1$$

$$\begin{bmatrix} V_r \\ I_r \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$\text{Now } \frac{V_r}{I_r} = \frac{DV_s - BI_s}{-CV_s + AI_s}$$

$$\therefore z_0 = \frac{V_r}{I_r} = \frac{DV_s - BI_s}{-CV_s + AI_s}$$

**118. Ans: (a)**

**Sol:** In L-G fault, whenever the neutral of alternator is not connected to ground, the voltage in the healthy line will be  $\sqrt{3} V$ . It is called arc ground phenomena so damage of insulation may occur by flash over in healthy phase.

**119. Ans: (c)**

**Sol:** Given data,

$$Y_{12} = \frac{1}{j0.5}$$

$$\Rightarrow Y_{12} = -j2$$

$$Y_{13} = -5j$$

$$\Rightarrow Y_{23} = -4j$$

$$Y_{11} = Y_{12} + Y_{13} = -7j$$

$$Y_{22} = Y_{23} + Y_{12} = -6j$$

$$Y_{33} = Y_{13} + Y_{23} = -9j$$

**120. Ans (a)**

**Sol:** Due to the phenomena of correct chopping arc may restrike between the contacts of C.B, to reduce the rate of rise of restriking voltage a resistor is connected across the contacts of C.B

**121. Ans (d)**

**Sol:** Inrush current has a large third harmonic component which is prevented by harmonic restraint.

**122. Ans: (c)**

**123. Ans: (b)**

**124. Ans: (d)**

**125. Ans: (b)**





**126. Ans: (a)**

**Sol:** \* If exponent is e bits long then exponent is excess  $(2^{e-1}-1)$  code

\* For IEEE 754 Double precision (64 bits), exponent is 11 bits long.

**127. Ans: (b)**

**Sol:** Cache line size = 64KB =  $2^{16}$  Bytes

Offset width  $\Rightarrow$  16 bits

No. of cache lines

$$= \frac{4\text{MB}}{64\text{KB}} = \frac{2^{22}\text{Bytes}}{2^{16}\text{Bytes}} = 2^6 \text{ lines}$$

$$\text{No. of cache sets} = \frac{2^6}{2} = 2^5 \text{ sets}$$

Index width  $\Rightarrow$  5 bits

Main memory size = 1 GB =  $2^{30}$  Bytes

Physical address width  $\Rightarrow$  30 bits

Tag entry width =  $30-16-5 = 9$  bits

Size of Tag memory =  $9 \text{ bits} * 2^6 = 72 \text{ Bytes}$

**128. Ans: (d)**

**Sol:** Use to high overheads of other strategies.

**129. Ans: (a)**

**Sol:** Since the program contain head recursion, so the output of the given program is reverse of the given input string so it is SAVINIRS.

**130. Ans: (b)**

**Sol:** In fully associative cache memory any MM block can be mapped to anywhere in the one of the cache blocks i.e. conflict miss doesn't occur.

**131. Ans: (d)**

**Sol:** Defragmentation is applied in disk and it done by either device manager part of Operating System or by any application software.

**132. Ans: (b)**

**133. Ans: (a)**

**134. Ans: (c)**

**Sol:** Over the length of transposition cycle, the total flux linkages and hence net voltage induced in a near by telephone line is zero

**135. Ans: (a)**

**Sol:** Both correct and statement - II is correct explanation of statement I

$$\therefore Z(x) = Z_o \left[ \frac{Z_L \cos \beta x + jZ_o \sin \beta x}{Z_o \cos \beta x + jZ_L \sin \beta x} \right]$$

$$Z(x) = Z_{in} ; x=L$$

$$Z_{in} = Z(L) = Z_o \left[ \frac{Z_L \cos \beta L + jZ_o \sin \beta L}{Z_o \cos \beta L + jZ_L \sin \beta L} \right]$$

$$\text{But, } \beta L = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} = \frac{\pi}{2}$$

$$\Rightarrow Z_{in} = \frac{Z_o^2}{Z_L}$$

Now, Open circuit line,  $Z_L \rightarrow \infty$

$$\therefore Z_{in} = 0$$

Short circuit line,  $Z_L = 0$

$$\therefore Z_{in} = \infty$$



**136. Ans: (c)**

**Sol:** In electrostatics,  $\vec{E} = -\nabla V$

Similarly,  $\vec{H} = -\nabla V_m$

Where  $V_m$ : magnetic scalar potential, is generally known as magneto motive force, expressed in (amp or AT).

From ampere's law:  $\vec{J} = \nabla \times \vec{H}$

$$\vec{J} = \nabla \times (-\nabla V_m)$$

Curl of gradient of any scalar is always zero and hence  $\vec{J} = 0$ .

Therefore  $\vec{H} = -\nabla V_m$  is defined if and only if  $\vec{J} = 0$ .

This indicates magnetic scalar potential is defined only in the current free ( $\vec{J} = 0$ ) (or) non-conducting region.

$$\nabla \cdot \vec{B} = 0$$

Magnetic flux density is always solenoidal.

$$\nabla \cdot \mu \vec{H} = 0$$

If the medium is homogeneous, then

$$\mu \nabla \cdot \vec{H} = 0 \Rightarrow \nabla \cdot \vec{H} = 0$$

If the medium is non-homogeneous, then

$$\nabla \cdot \mu \vec{H} = 0 \text{ but } \nabla \cdot \vec{H} \neq 0.$$

Hence magnetic field intensity is not solenoidal always.

Therefore statement-I is true, but statement-II is false.

**137. Ans: (b)**

**Sol:** High frequency transformers are designed with thin laminations, therefore Stacking factor is low.


Eddy current loss is directly proportional to conductivity.

**138. Ans: (d)**

**Sol:** In figure, because of the short-circuit,  $V = 0$ . Since  $V = 0$ ,  $I_f R_f = 0$  and  $I_f$  is zero.

But residual magnetism will induce a voltage  $E_r$  in the armature, which circulates a current  $I_L$  in the armature and the short-

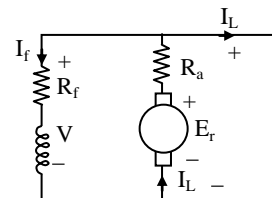circuit  $\left( I_L = \frac{E_r}{R_a} \right)$



‘Statement I’ is false, but ‘Statement II’ is true.

**139. Ans: (c)**

**Sol:** The speed of dc series motor sharply falls as torque increases. Hence, the mechanical (and electrical) power developed remains nearly constant at various loads, and prevents overloading.

‘Statement I’ is correct, ‘Statement II’ is false.



140. Ans: (a)

**Sol:** An overexcited synchronous motor operated under no-load condition called Synchronous condenser which is used to deliver the reactive power only such that power factor can be corrected, for this purpose diameter of shaft need not be large.

141. Ans: (b)

**Sol:** Both statements - I and Statement-II are true but Statement - II is not correct explanation for Statement-I.

142. Ans: (b)

**Sol:** Both Statement-I and Statement-II are true but Statement-II is not correct explanation for Statement-I.

143. Ans: (a)

**Sol:** At full load, exact braking torque will not produce proportional driving torque.

144. Ans: (c)

**Sol:** Due to hysteresis loss, inductor cannot be used as a lag network. Capacitor network is used as a lag network

145. Ans: (b)

**Sol:**

- Carbon Nanotubes structure consists of a single sheet of graphite, rolled into a tube, both ends of which are

capped with C60 fullerene hemispheres. The nano prefix denotes that tube diameters are of the order of a nanometer (i.e., 100 nm or less).

- These nanotubes are extremely strong and stiff and relatively ductile. For single-walled nanotubes, tensile strengths range between 50 and 200 GPa (approximately an order of magnitude greater than for carbon fibers); this is the strongest known material.

146. Ans: (b)

**Sol:** White iron has a characteristic white, crystalline fracture surface. Large amounts of Fe<sub>3</sub>C are formed during casting, giving a hard, brittle material.

- Gray iron has a gray fracture surface with a finely faceted structure. A significant silicon content (2 to 3 wt%) promotes graphite (C) precipitation rather than cementite (Fe<sub>3</sub>C). The sharp, pointed graphite flakes contribute to characteristic brittleness in gray iron.

147. Ans: (b)

**Sol:** In a collector to base bias amplifier circuit,

the stability factor,  $S = \frac{1 + \beta}{1 + \beta \left[ \frac{R_C}{R_C + R_B} \right]}$



i.e., by increasing  $R_C$  and decreasing  $R_B$ , the stability of Q-point can be improved.

The resistor  $R_B$  causes AC negative feedback in the amplifier and reduce the overall AC gain of the amplifier.

**148. Ans: (c)**

**Sol:** Statement-I is true & statement-II is false.

**149. Ans: (c)**

**Sol:** RIM instruction is used to read the status of hardware interrupts (RST 7.5, RST 6.5, RST 5.5). So statement (II) is incorrect.

**150. Ans: (A)**

$$\text{Sol: } \left(\frac{2}{3}\right)^n u(n) \leftrightarrow \frac{1}{1 - \frac{2}{3}z^{-1}}$$

From time shifting property

$$x(n - n_0) \leftrightarrow z^{-n_0} X(z)$$

$$\left(\frac{2}{3}\right)^{n+2} u(n+2) \leftrightarrow \frac{z^2}{1 - \frac{2}{3}z^{-1}}$$

$$\left(\frac{2}{3}\right)^n u(n+2) \leftrightarrow \frac{\frac{9}{4}z^2}{1 - \frac{2}{3}z^{-1}}$$



## CONGRATULATIONS TO OUR ESE - 2018 TOP RANKERS

AIR 1  SHASHANK E&T	AIR 1  CHIRAG JHA EE	AIR 1  VINAY PRAKASH CE	AIR 1  AMAN JAIN ME		
AIR 2  CHERUKURI SAIDEEP E&T	AIR 2  SHADAB AHMAD EE	AIR 2  PUNIT SINGH CE	AIR 2  CHIRAG SINGLA ME	AIR 3  RAMESH KAMULLA E&T	AIR 3  SRIJAN VARMA EE
AIR 3  PRAVEEN KUMAR CE	AIR 3  MAYUR PATIL ME	AIR 4  JAPJIT SINGH E&T	AIR 4  ANKIT GARG EE	AIR 4  AMIT KUMAR ME	AIR 5  NARENDRA KUMAR E&T
AIR 5  KARTHIK KOTTURU EE	AIR 5  RISHABH DUTT CE	AIR 5  VITTHAL PANDEY ME	AIR 6  KUMUD JINDAL E&T	AIR 6  RATIPALLI NAGESWAR EE	AIR 7  KARTIKEYA DUTTA E&T
AIR 7  TEJCHAND DESHWAL EE	AIR 7  ROHIT KUMAR CE	AIR 8  SURYASH GAUTAM E&T	AIR 8  RAVI TEJA MANNE EE	AIR 8  VIJAYA NANDAN CE	AIR 8  ROHIT BANSAL ME
AIR 9  SHANAVAS CP E&T	AIR 9  SOUVIK DEB ROY EE	AIR 9  ROOPESH MITTAL CE	AIR 10  PRATHAMESH E&T	AIR 10  MILAN KRISHNA EE	AIR 10  SRICHAND POONIYA CE

TOTAL SELECTIONS  
in Top 10

34

E&T TOP 10  
10

EE TOP 10  
10

CE TOP 10  
8

ME TOP 10  
6

and many more...