



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad – 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

GATE- 2019 – Offline GATE Mock -3

Electrical Engineering

Solutions

General Aptitude (GA)

Q. 01 to 05 Carry one mark each

01. Ans: (d)

Sol: Let the ages of A and B 10 years ago be x and $2x$ years respectively.

$$\text{Then, } \frac{x+10}{2x+10} = \frac{3}{4}$$

$$\Leftrightarrow 4(x+10) = 3(2x+10)$$

$$\Leftrightarrow 2x = 10 \Leftrightarrow x = 5$$

\therefore Sum of their present ages

$$= ((x+10) + 2x+10)$$

$$= (3x+20) = 35 \text{ years}$$

02. Ans: (c)

Sol: Rule $m+n$ is divisible by 10 does not hold true in the given case. Eg. 35, 10 are integers divisible by 5 but $35+10 = 45$, which is not divisible by 10.

03. Ans: (b)

04. Ans: (b)

05. Ans: (d)

Q. 06 to 10 carry two marks each

06. Ans: (c)

Sol: The interval of leaving two buses = 30 minutes
The time for the next bus = 15 minutes

$$\therefore \text{The passed} = 30 - 15 = 15 \text{ minutes}$$

The required time for the information given by enquiry clerk = $9:10 + 0.15 = 9:25$

07. Ans: (c)

Sol: Let one gets = Rs. x

Then, second gets = Rs. $(68000-x)$

Given, $A_1 = A_2$

$$x + \frac{x \times 10 \times 8}{100} = (68000 - x) + \frac{(68000 - x) \times 10 \times 6}{100}$$

$$x(100 + 80) = (68000 - x)[100 + 60]$$

$$\frac{180x}{160} = 68000 - x$$

$$34x = 68000 \times 16 \Rightarrow x = 32000/-$$

\therefore Second gets = Rs. 36000



08. Ans: (d)

Sol: The statement mentions the cause of family problems and does not deal with all the problems. So, statement 1 is not implicit. Also, it is mentioned that money is the cause of family problems. But this does not mean that problems always exist in a family. So, statement 2 is also not implicit.

09. Ans: (d)

Sol: → Single Unit Rectangles = 5 + 5 = 10
 → Double Unit Rectangles = 5 + 8 = 13
 → Three Unit Rectangles = 6
 → Four Unit Rectangles = 4 + 4 = 8
 → Six Unit Rectangles = 3
 → Five Unit Rectangles = 2
 → Eight Unit Rectangles = 2
 → Ten Unit Rectangles = 1

 45

Hence, option (d) is correct.

10. Ans: (d)

Electrical Engineering (EE)

Q. 01 to 25 carry one mark each

01. Ans: 5Ω (No Range)

Sol: $Z_{11} = 6\Omega, Z_{12} = Z_{21} = 4\Omega$

For symmetrical network, $Z_{11} = Z_{22} = 6\Omega$

ABCD parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

Now from Z – parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 = 6I_1 + 4I_2 \quad \dots\dots\dots (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 = 4I_1 + 6I_2 \quad \dots\dots\dots (2)$$

By putting $V_2 = 0$ in equation (2)

$$4I_1 = -6I_2$$

Put value of I_1 in equation (1) than

$$V_1 = 6\left(-\frac{6}{4}\right)I_2 + 4I_2$$


$$= I_2 \left[\frac{-36}{4} + 4 \right] = -5I_2$$

So $\frac{V_1}{I_2} = -5$

$$B = -(-5) = 5\Omega$$

02. Ans:(b)

Sol:

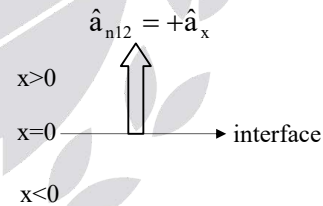

Given $\vec{K} = 10\hat{a}_z \text{ A/m}$

$$\vec{H}_1 = 12\hat{a}_y \text{ A/m}$$

As the interface is $x = 0$ (or) yz -plane, hence y, z are tangential components and x is normal component

$$\vec{H}_{t1} = 12\hat{a}_y, \vec{H}_{n1} = 0$$

$$\vec{H}_{t1} - \vec{H}_{t2} = \hat{a}_{n12} \times \vec{K}$$

$$12\hat{a}_y - \vec{H}_{t2} = \hat{a}_x \times 10\hat{a}_z$$

$$\vec{H}_{t2} = 22\hat{a}_y$$

$$\vec{H}_2 = 22\hat{a}_y \text{ A/m}$$



03. Ans: (a)

Sol: $Z_{2RB} = 100\% Z_{BC} + 50\% Z_{CD}$
 $= 8+2$
 $= 10\Omega$

04. Ans: 3

Sol: The eigen values of A are $\lambda = 2, 2, 2$,

The eigen vectors are given by the system

$$[A - 2I]X = 0$$

$\Rightarrow (A - 2I)$ is a zero matrix

\Rightarrow Rank of $(A - 2I) = 0$

\therefore The number of linearly independent eigen vectors of $A = n - r = 3 - 0 = 3$

Where $n =$ order of A and $r =$ rank of $[A-2I]$.

05. Ans: (d)

Sol: (i) Total core loss $\Rightarrow W_i = W_h + w_c$

$$V \uparrow, f \uparrow \Rightarrow \frac{V}{f} = \text{constant}$$

\therefore as $f \uparrow \Rightarrow W_h \uparrow, W_c \uparrow \Rightarrow W_i \uparrow$

(ii) Magnetizing flux $\phi \propto \frac{V}{f}$


$$\text{As } \frac{V}{f} = \text{fixed}$$

$\Rightarrow \phi$ fixed $\Rightarrow I_\mu$ fixed.


06. Ans: (c)

Sol: By super position principle $I = i_{x1}$ due to $1A + i_{x2}$ due to $2V + i_{x3}$ due to $1A$


1A source alone:

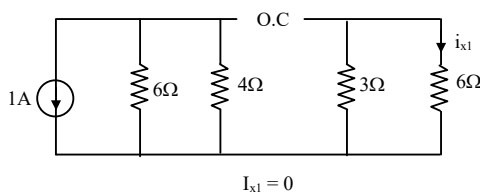

2V source alone:

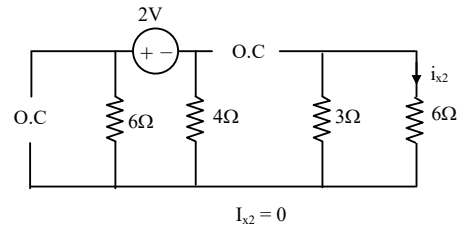

1A source alone:

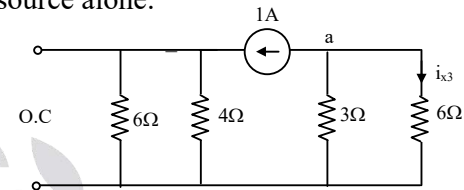

By KCL at a branch current leaving = current entering

$$i_{x3} = 1 \times \left(\frac{3}{3+6} \right)$$

$$= \frac{3}{9} = \frac{1}{3} \text{ A}$$

$$\therefore i_x = i_{x1} + i_{x2} + i_{x3}$$

$$= -\frac{1}{3}$$

07. Ans: 900.90 (Range: 899 to 902)

Sol: Given data:

$$B_{\text{max}} = 1.5 \text{ wb/m}^2$$

$$E/\text{turn} = 30V$$

$$E/\text{turn} = 4.44 \times \phi \times f$$

$$E/\text{turn} = 4.44 \times B_m \times A \times f$$


$$30 = 4.44 \times 1.5 \times A \times 50$$

$$A = 0.09009 \text{ m}^2$$

$$A = 900.90 \text{ cm}^2$$

08. Ans: (a)

Sol:

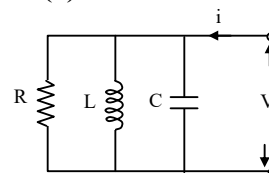



$$i = V \left(\frac{1}{R} + \frac{1}{SL} + SC \right)$$

$$= V \left(\frac{S^2 LCR + R + SL}{RSL} \right)$$

$$i = V.C \frac{\left(S^2 + \frac{R}{LCR} + \frac{SL}{RCL} \right)}{RSL}$$

$$V = \frac{i \frac{1}{C}}{S^2 + \frac{1}{RC}S + \frac{1}{LC}}$$

Equation is $S^2 + \frac{1}{RC}S + \frac{1}{LC} = 0$

$$\text{Roots } S_1, S_2 = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - 4\left(\frac{1}{LC}\right)^2}}{2}$$

$$= \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{LC}\right)^2}$$

By comparing

$$= \frac{1}{2RC} < \frac{1}{LC}$$

$$= \frac{1}{2 \times 4 \times 16} < \frac{1}{16 \times 4}$$

Roots are complex so circuit exhibits under damping

09. Ans: (d)

10. Ans: (c)

Sol: Rate of flickering = beat frequency

$$= f - f^1$$

$$= 50.3 - 50 = 0.3\text{Hz}$$

$$\Rightarrow 0.3 \text{ Flickers/sec} = 0.3 \times 60$$

$$= 18 \text{ filckers/min}$$

11. Ans: (c)

Sol: Let $I = \int_0^{\frac{\pi}{2}} \frac{1}{1 + \sqrt{\tan x}} dx$

$$= \int_0^{\frac{\pi}{2}} \frac{1}{1 + \sqrt{\frac{\sin x}{\cos x}}} dx$$

$$= \int_0^{\frac{\pi}{2}} \frac{1}{\frac{\sqrt{\cos x} + \sqrt{\sin x}}{\sqrt{\cos x}}} dx$$

$$I = \int_0^{\frac{\pi}{2}} \frac{\sqrt{\cos x}}{\sqrt{\cos x} + \sqrt{\sin x}} dx$$

$$I = \int_0^{\frac{\pi}{2}} \frac{\sqrt{\sin x}}{\sqrt{\sin x} + \sqrt{\cos x}} dx$$

$$[\because \int_0^a f(x) dx = \int_0^a f(a-x) dx]$$

Adding,


$$2I = \int_0^{\frac{\pi}{2}} dx = \frac{\pi}{2}$$

$$I = \frac{\pi}{4}$$

12. Ans: (a)

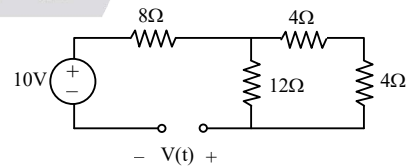
13. Ans: (d)

Sol: At $t = 0^-$ switch was closed position



$$V_c(0^+) = V(0^-) = 10V$$

At $t = 0^+$ switch is opened than

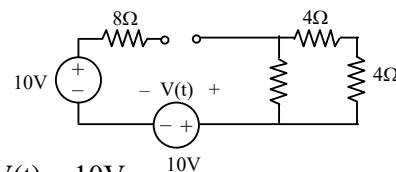

$$V(t) = 10V$$



14. Ans: (a)

$$\text{Sol: } \eta = \frac{P_0}{P_0 + P_{\text{loss}}} \Rightarrow P_0 = \frac{\eta}{1 - \eta} \times P_{\text{loss}}$$

If $\eta = 89\%$,

$$P_0 = \frac{0.89}{1 - 0.89} \times 200 \approx 1.6 \text{ kW}$$

If $\eta = 94\%$,

$$P_0 = \frac{0.94}{1 - 0.94} \times 200 \approx 3.13 \text{ kW}$$

Hence option 'a' is correct.

15. Ans: (b)

Sol: If rank of A is 2, then $|A| = 0$

$$\Rightarrow (x - 1)(x^2 + x + 1) = 0$$

$$\Rightarrow x = 1, \frac{-1 \pm \sqrt{3}i}{2}$$

$$\therefore x = 1$$

16. Ans: (a)

$$\text{Sol: The given limit} = \lim_{x \rightarrow \infty} \left[\left(\frac{x+4}{x+2} \right)^x \cdot \left(\frac{x+4}{x+2} \right)^3 \right]$$

$$= \lim_{x \rightarrow \infty} \left[\left(\frac{1 + \frac{4}{x}}{1 + \frac{2}{x}} \right)^x \cdot \left[\frac{1 + \frac{4}{x}}{1 + \frac{2}{x}} \right]^3 \right]$$


$$= \frac{e^4}{e^2} = e^2$$

17. Ans: (d)

Sol: The error in Simpson's $1/3^{\text{rd}}$ rule is of order h^4

18. Ans: (d)

Sol:

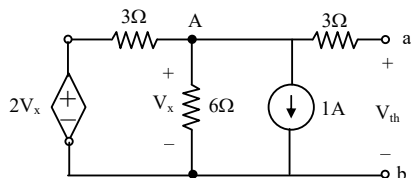

Current flowing through 3Ω is zero so

$$V_{\text{th}} = V_x$$


Apply KCL at node A, then

$$\frac{V_x - 2V_x}{3} + \frac{V_x}{6} + 1 = 0$$

$$-2V_x + V_x + 6 = 0$$

$$V_x = 6V$$

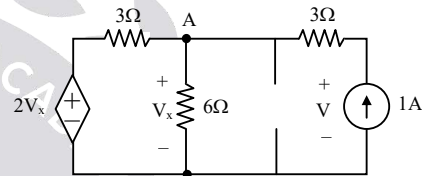R_{th} can be find out by exciting the circuit with 1A, replace all independent sources by their internal resistances



By KCL at node A

$$\frac{V_x}{6} + \frac{(V_x - 2V_x)}{3} - 1 = 0$$

$$V_x - 2V_x - 6 = 0$$

$$V_x = -6V$$

$$V = 3 + V_x = 3 - 6 = -3V$$

$$R_{\text{th}} = \frac{V}{I} = \frac{-3}{1} = -3\Omega$$

19. Ans: (d)

$$\text{Sol: } (1+t) \frac{dy}{dt} = 4y$$

$$\int \frac{1}{y} dy = \int \frac{4}{1+t} dt$$

$$\log y = 4 \log(1+t) + \log c$$

$$y = c(1+t)^4$$

$$y(0) = 1$$

$$\Rightarrow 1 = c(1+0)^4 \Rightarrow c = 1$$

$$\Rightarrow y = (1+t)^4$$



20. Ans: (c)

Sol: Generator buses = 10

Load buses = 90

5 load buses are converted into generator

buses total generator buses = 15

Load buses = 85

Generator equations = $(15 - 1) \times 1 = 14$

Load bus equations = $85 \times 2 = 170$

Total number of equations = 184.

21. Ans: (c)

22. Ans: (b)

Sol: Line address for $4K \times 8$ memory is 0FFFH.

End address = Starting address + Line address

\therefore End Address = AA00H + 0FFFH
= B9FFH

23. Ans: 4.88 (4.8 to 5)

Sol: Smallest increment change in output

$$\Delta V = \frac{1}{2^{10}} = \frac{1}{1024} \text{ V}$$

$$\text{For } 5V, \Delta V = 5 \times \frac{1}{1024} \approx 5 \text{ mV}$$

24. Ans: (d)

Sol: The switching order of inverter is

$D_1 D_4 - S_1 S_4 - D_2 D_3 - S_2 S_3$.

25. Ans: (c)

Sol: Given data,

$R_a = 0.2\Omega$, $N_1 = 1245 \text{ rpm}$, $I_{a1} = 125A$,

$V_t = 440V$, $\phi_2 = 0.75\phi_1$, $\tau_L = \text{constant}$

$\tau \propto \phi I_a$

$$I_{a2} \phi_2 = I_{a1} \phi_1$$

$$\Rightarrow I_{a2} = 125 \times \frac{\phi_1}{0.75\phi_1} = 166.67A$$

$$E_{b1} = V - I_{a1} R_a = 440 - 125(0.2) = 415V$$

$$E_{b2} = V - I_{a2} R_a = 440 - 166.67(0.2) = 406.6V$$

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1 \phi_1}{N_2 \phi_2}$$

$$\Rightarrow N_2 = \frac{1245 \times 406.6 \times \phi_1}{415 \times 0.75 \times \phi_1} = 1626.7 \text{ rpm}$$

Q. 26 to 55 carry two marks each

26. Ans: 0.376 (Range: 0.2 to 0.4)

$$\text{Sol: } \frac{C}{R} = \left(\frac{8}{1+8(2)} \right) \left(\frac{4}{1+4} \right) = \frac{32}{85} = 0.376$$

27. Ans: (a)

$$\text{Sol: } Q = \int dQ = \int \rho_v dv$$

$$= \int_0^{0.1} \int_0^\pi \int_0^{2\pi} 4r^2 \sin \theta dr d\theta d\phi = 4 \left[\frac{r^3}{3} \right]_0^{0.1} [-\cos \theta]_0^\pi [\phi]_0^{2\pi}$$

$$= 0.016755 \mu C$$

charge present between $10\text{cm} < r < r_0$ is

$$Q = \int_{0.10}^{r_0} \int_0^\pi \int_0^{2\pi} \frac{-3r^2}{r^3 + 0.001} \sin \theta dr d\theta d\phi$$

$$= -\ln \left[\frac{r_0^3 + 0.001}{0.002} \right] [2][2\pi] nC$$

Hence total charge present between $0 < r < r_0$ is

$$Q_{\text{tot}} = 16.755 nC - 4\pi \ln \left[\frac{r_0^3 + 0.001}{0.002} \right] nC = 0$$

$$\Rightarrow \ln \left[\frac{r_0^3 + 0.001}{0.002} \right] = 1.33332$$



$$\Rightarrow \left[\frac{r_0^3 + 0.001}{0.002} \right] = e^{1.33332} = 3.79362$$

$$\Rightarrow r_0 = 0.187456 = 18.746 \text{ cm}$$

28. Ans: (b)


$$\text{Sol: } G_1: X_{\text{pu}(\text{new})} = 0.2 \times \frac{150}{75} \left(\frac{11}{11} \right)^2 = 0.4$$

$$G_2: X_{\text{pu}(\text{new})} = 0.1 \times \frac{150}{50} \left(\frac{33}{33} \right)^2 = 0.3$$

$$G_3: X_{\text{pu}(\text{new})} = 0.35 \times \frac{150}{100} \left(\frac{33}{33} \right)^2 = 0.525$$


$$\text{T/F: } X_{(\text{pu})} = X_{s(\text{pu})} = 0.1$$
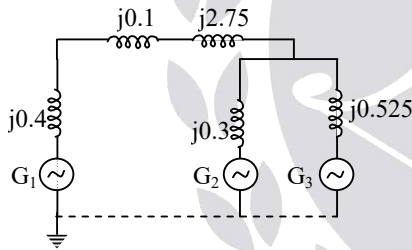
$$\text{OHTL: } X_{\text{pu}} = 20 \times \frac{150}{(33)^2} = 2.75$$



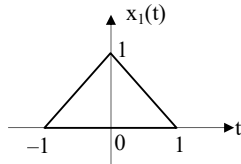
29. Ans: 0.75

$$\text{Sol: } x_1(t) = \text{Tri}(t) \xrightarrow{\text{FT}} \sin^2(f) = X_1(f)$$



$$X(f) = X_1(f) e^{-\frac{j\pi f}{2}}$$
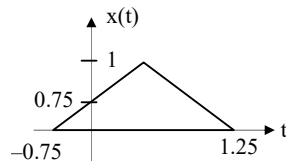
$$x(t) = x_1\left(t - \frac{1}{4}\right)$$



Area under spectrum = signal value at $t=0$

$$\int_{-\infty}^{\infty} X(f) df = x(0) = 0.75$$

30. Ans: 4.5 to 4.8

$$\text{Sol: } V_{LL} = 460 \text{ V} \Rightarrow V_{\text{ml}} = 460\sqrt{2}$$

$$L_s = 5 \text{ mH}; \omega = 100\pi \text{ rad/s}$$

$$P_0 = V_0 I_0 = 5000 \text{ W}$$

$$\Rightarrow I_0 = \frac{5000}{500} = 10 \text{ A}$$

$$V_0 = \frac{3V_{\text{ml}}}{\pi} \cos \alpha - \frac{3\omega L_s}{\pi} I_0 = 500 \text{ V}$$

$$\Rightarrow \frac{3 \times 460\sqrt{2}}{\pi} \cos \alpha - \frac{3 \times 100\pi \times 5 \times 10^{-3}}{\pi} \times 10 = 500$$

$$\Rightarrow \cos \alpha = 0.829 \Rightarrow \alpha = 34^\circ$$

$$\text{Now, } \cos(\alpha + \mu) = \cos \alpha - \frac{2\omega L_s I_0}{V_{\text{ml}}}$$

$$= 0.829 - \frac{2 \times 100\pi \times 5 \times 10^{-3}}{460\sqrt{2}} \times 10$$

$$= 0.7807$$

$$\Rightarrow \alpha + \mu = 38.67^\circ$$

$$\mu = 38.67 - 34 = 4.67^\circ$$

31. Ans: (a)

$$\text{Sol: } CE = 1 + \frac{4}{s(s+2)}$$

$$s^2 + 2s + 4 = 0$$

$$\omega_n = 2$$

$$2\zeta\omega_n = 2$$

$$\Rightarrow \zeta = \frac{1}{2}$$

$$t_p = \frac{\pi}{\omega_d} = \frac{\pi}{\omega_n \sqrt{1-\zeta^2}} = \frac{\pi}{2\sqrt{1-\frac{1}{4}}} = \frac{\pi}{\sqrt{3}} \text{ sec}$$



32. Ans: (a)

Sol: Given data: 440V, 50Hz and $W_i = 2500$

$$\frac{V}{f} = \text{constant}$$

$$W_i = Af + Bf^2$$

$$\text{For 50Hz: } 2500 = A \times 50 + B \times 2500 \dots\dots\dots (1)$$

$$\text{For 25Hz: } 850 = A \times 25 + B \times 625 \dots\dots\dots (2)$$

By solving (1) and (2),

$$A = 18, B = 0.64$$


At 50Hz:

$$\begin{aligned} \text{Eddy current loss} &= B \times f^2 \\ &= 0.64 \times 2500 \\ &= 1600 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Hysterisis loss} &= Af \\ &= 18 \times 50 \\ &= 900 \text{ W.} \end{aligned}$$

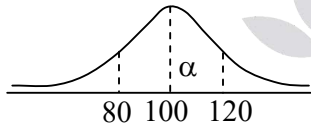33. Ans: (c)

Sol: The area under normal curve is 1 and the curve is symmetric about mean.



$$\therefore P(100 < X < 120) = P(80 < X < 120) = \alpha$$

$$\text{Now, } P(X < 80) = 0.5 - P(80 < X < 100)$$

$$= 0.5 - \alpha = \frac{1}{2} - \alpha$$

$$= \frac{1 - 2\alpha}{2}$$

34. Ans: 60 (Range 60 to 60)

$$\text{Sol: } \frac{y_1 - 30}{\log 2 - \log 0.1} = -40$$

$$\Rightarrow y_1 = 30 - 52 = -22 \text{ dB}$$

$$\frac{y_2 - (-22)}{\log 20 - \log 2} = -60$$

$$\Rightarrow y_2 = -82 \text{ dB}$$

$$\begin{aligned} \text{Therefore } y_1 - y_2 &= -22 - (-82) \\ &= 60 \text{ dB} \end{aligned}$$

35. Ans: 17.65 (Range 16 to 18)

Sol: A 3- ϕ , 11 kV, 10 MW, Y-connected, Alternator

$$V_L = 11 \text{ kV} \Rightarrow V_{ph} = \frac{11 \times 10^3}{\sqrt{3}} = 6351 \text{ V}$$

$$Z_s = 0.8 + j8 = 8.04 \angle (84.29^\circ = \theta)$$


$$E_L = 14 \text{ kV} \Rightarrow E_{ph} = \frac{14 \times 10^3}{\sqrt{3}} = 8082.9 \text{ V}$$

$$\begin{aligned} \Rightarrow P_{\max} &= \frac{EV}{Z_s} - \frac{V^2}{Z_s} \cos \theta \\ &= \frac{8082.9 \times 6351}{8.04} - \frac{6351^2}{8.04} \cos 84.29 \\ &= 5.885 \text{ MW} \end{aligned}$$

$$P_{\max(\text{Total})} = 3 \times 5.885 = 17.6551 \text{ MW}$$

36. Ans: (a)

Sol:

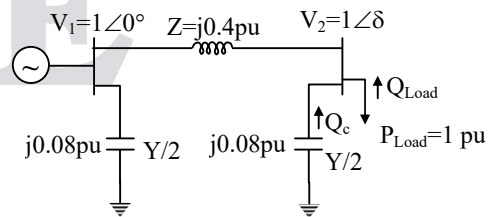

$$P_2 = P_{\text{load}} = 1 \text{ pu, as } P_2 = \frac{|V_1||V_2|}{X} \sin(0 - \delta)$$

$$\text{So, } 1 = \frac{1}{0.4} \sin(-\delta) \rightarrow \delta = -\sin^{-1}(0.4)$$

$$\delta = -23.6^\circ$$



$$\begin{aligned} \text{Now, } Q_2 &= \frac{|V_2|}{X} [|V_1| \cos \delta - |V_2|] \\ &= \frac{1}{0.4} [1 \times \cos(-23.6^\circ) - 1] \\ &= -0.209 \text{ pu} \end{aligned}$$

Reactive power balance

$$Q_2 + Q_c + Q_{\text{load}} = 0$$

Where Q_{load} is reactive power injected by load

$$\text{into bus bar and } Q_c = |V_2|^2 \left| \frac{Y}{2} \right|$$

$$\begin{aligned} Q_c &= 1 \times 0.08 \\ &= 0.08 \text{ pu} \end{aligned}$$

$$-0.209 + 0.08 + Q_{\text{load}} = 0$$

$$Q_{\text{load}} = 0.129 \text{ pu}$$

37. Ans: (a)

Sol: The given circuit is Wein-bridge oscillator.

$$\text{The gain of the amplifier, } \frac{V_2}{V_1} = \left(1 + \frac{2k\Omega}{1k\Omega} \right) = 3$$

\Rightarrow Oscillations will be sustained Frequency of

$$\text{oscillation, } f = \frac{1}{2\pi RC}$$


$$\text{Given : } f = 1\text{kHz, } R = 1k\Omega$$

$$C = \frac{1}{2\pi Rf} = \frac{1}{2\pi \times 10^3 \times 10^3}$$

$$\therefore C = \frac{1}{2\pi} \mu\text{F}$$

38. Ans: (c)

Sol:

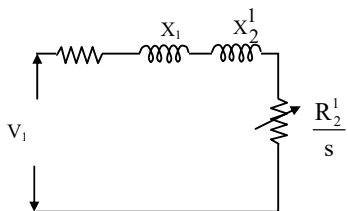

$$\text{For maximum slip, } \frac{R_2^1}{s} = \sqrt{R_1^2 + (X_{01})^2}$$

$$\frac{0.08}{s} = \sqrt{(0.07)^2 + (0.67)^2}$$

$$s = 0.1187$$

39. Ans: 7.29 (Range: 7.28 to 7.30)

Sol: $f_s = 200 \text{ kHz} \Rightarrow T = 5 \mu\text{s}$

$$V_0 = \frac{V_{\text{in}}}{1-D} \Rightarrow 12 = \frac{5}{1-D} \Rightarrow D = 0.5833$$

$$\Delta I_L = \frac{V_{\text{dc}}}{L} DT = 2A$$

$$\Rightarrow \frac{5}{L} \times 0.5833 \times 5\mu = 2$$

$$\Rightarrow L = 7.29 \mu\text{H}$$

40. Ans: (b)

Sol: Let X = number of accidents between 5 P.M and 6 P.M.

For Poisson distribution,

$$\lambda = np = (1000)(0.0001) = 0.1$$

$$P(X=x) = \frac{e^{-\lambda} \cdot \lambda^x}{x!} \quad (x = 0, 1, 2, \dots)$$

Required Probability = $P(X \geq 2)$

$$= 1 - P(X < 2)$$

$$= 1 - \{P(X=0) + P(X=1)\}$$

$$= 1 - e^{-0.1} (1 + 0.1)$$

$$= 0.0045$$

41. Ans: (c)

Sol: $P_0 = 20\text{kW, } V_t = 250\text{V, } N_1 = 1000 \text{ r.p.m}$

$$\phi\alpha = \frac{I}{50+I}, r_s = 0.01\Omega, r_a = 0.015\Omega$$

$$I_{a2} = 100\text{A, } N_2 = 1050 \text{ r.p.m and } V_b = 2\text{V}$$

$$I_{a1} = \frac{20 \times 10^3}{250} = 80\text{A}$$



Now field flux $\phi_1 = \frac{80}{50+80} \times 0.94$

(since in total ampere turns, the demagnetizing ampere turns are 6%)

$E_{a1} = 80(r_s + r_a) + V_b + V_t$
 $= 80(0.025) + 2 + 250$
 $= 254V$

Now $I_{a2} = 100A$

Net field flux $\phi_2 = \frac{100}{150} \times 0.94$

We know that, $\frac{E_{a1}}{E_{a2}} = \frac{N_1 \phi_1}{N_2 \phi_2}$

$E_{a2} = \frac{1050 \times 100 \times 0.94 \times 130}{150 \times 1000 \times 80 \times 0.94} \times 254$
 $= 288.925$

$E_{a2} = 100(0.025) + V_b + V_t$

$V_t = E_{a2} - (100 \times 0.025) - 2$
 $= 284.43V$

42. Ans: (c)

Sol: $2k > 1$ & $0.01k < 1$

$k > \frac{1}{2}$ & $k < 100$

$\therefore \frac{1}{2} < k < 100$

43. Ans: (c)

Sol: Given data

$H = \frac{K.E \text{ stored}}{\text{rating of the generator}}$

$5 = \frac{K.E \text{ stored}}{100}$

K.E = 500 MJ

K.E stored in 0.4 sec

$50 \times 0.4 = 20 \text{ MJ}$

$K.E \propto f^2$

$\frac{500}{520} = \left(\frac{50}{f_{\text{new}}} \right)^2$


$\frac{50}{f_{\text{new}}} = \sqrt{\frac{50}{52}}$

$f_{\text{new}} = 50 \sqrt{\frac{52}{50}}$

$= 50.99 \approx 51 \text{ Hz}$

44. Ans: (b)

Sol: Let $R = 4k\Omega$

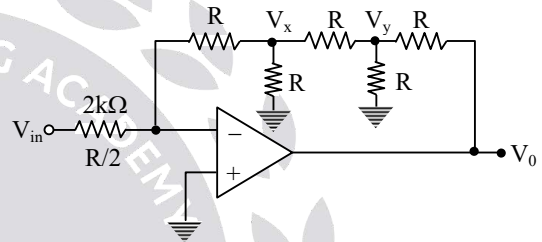

Applying KCL at inverting terminal,

$\frac{V_{in} - 0}{R/2} = \frac{0 - V_x}{R} \Rightarrow V_x = -2V_{in} \dots\dots\dots (1)$

Applying KCL at V_x ,

$\frac{V_x}{R} + \frac{V_x}{R} + \frac{V_x - V_y}{R} = 0$
 $\Rightarrow 3V_x - V_y = 0$

i.e. $3V_x = V_y \dots\dots\dots (2)$

Applying KCL at V_y ,

$\frac{V_y}{R} + \frac{V_y - V_x}{R} + \frac{V_y - V_0}{R} = 0$

$\Rightarrow 3V_y - V_x = V_0 \dots\dots\dots (3)$

Substituting (2) in (3),

$3(3V_x) - V_x = V_0$

$8V_x = V_0 \dots\dots\dots (4)$


Substituting (1) in (4)

$8(-2V_{in}) = V_0$

$\Rightarrow \frac{V_0}{V_{in}} = A_v = -16$

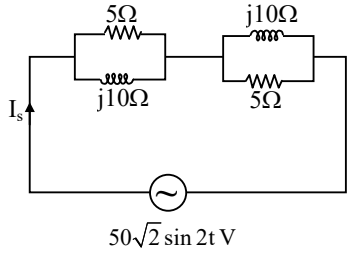45. Ans: (c)

Sol: If the galvanometer is short circuited then modified bridge circuit is shown below.




$$Z_{eq} = 2 \times \left(\frac{5 \times j10}{5 + j10} \right) = 4\sqrt{5} \angle 26.56$$

$$I_s = \frac{50 \angle 0^\circ}{4\sqrt{5} \angle 26.56} = 5.59 \angle -26.56^\circ$$

46. Ans: $V_1 = 68.6$ volts (Range: (67.5 to 69.5V))

Sol:

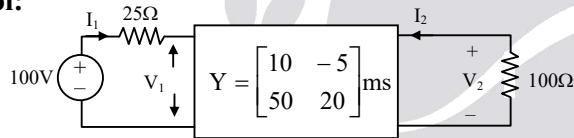

By applying at KVL input side

$$V_1 = 100 - 25I_1 \quad \dots\dots\dots (1)$$

$$V_2 = -100 I_2 \quad \dots\dots\dots (2)$$

From Y-parameters

$$I_1 = (10 \times 10^{-3}) V_1 - (5 \times 10^{-3}) V_2 \quad \dots\dots\dots (3)$$

$$I_2 = (50 \times 10^{-3}) V_1 + (20 \times 10^{-3}) V_2 \quad \dots\dots\dots (4)$$

By putting value of V_2 in equation (4)

$$I_2 = (50 \times 10^{-3}) V_1 + (20 \times 10^{-3}) (-100 I_2)$$

$$= (50 \times 10^{-3}) V_1 - 2I_2$$

$$3I_2 = (50 \times 10^{-3}) V_1$$

And from equation (3)

$$I_1 = (10 \times 10^{-3}) V_1 - (5 \times 10^{-3}) (-100 I_2)$$

$$= (10 \times 10^{-3}) V_1 + (5 \times 10^{-3} \times 100) \left(\frac{50 \times 10^{-3}}{3} \right) V_1$$

$$= (10 \times 10^{-3}) V_1 + \frac{25}{3} \times 10^{-3} V_1$$

$$= \frac{55}{3} \times 10^{-3} V_1$$

$$\therefore V_1 = 100 - [25 \times I_1]$$

$$V_1 = 100 - \left[25 \times \frac{55}{3} \times 10^{-3} V_1 \right]$$

$$V_1 \left[1 + 25 \times \frac{55}{3} \times 10^{-3} \right] = 100$$

$$V_1 = \frac{100}{1.458} = 68.57V$$

47. Ans: (a)

Sol: $P = V_{s1} I_{s1} \cos \phi_1 = 950$

$$\Rightarrow \text{DPF} = \cos \phi_1 = \frac{950}{120 \times 10} = 0.792$$

$$\text{IPF} = \text{DF} \times \text{DPF}$$

$$= \frac{\text{DPF}}{\sqrt{1 + (\text{THD})^2}} = \frac{0.792}{\sqrt{1 + (0.75)^2}} = 0.6336 \text{ lag}$$

48. Ans: (b)

Sol: According to the given data, state table can be prepared as follows.

Control Input	Present State		Next state		Flip-flop Input	
	Q_1	Q_0	Q_1	Q_0	T_1	T_0
y	Q_1	Q_0	Q_1	Q_0	T_1	T_0
0	0	0	1	1	1	1
0	0	1	0	0	0	1
0	1	0	0	1	1	1
0	1	1	1	0	0	1
1	0	0	0	1	0	1
1	0	1	1	0	1	1
1	1	0	1	1	0	1
1	1	1	0	0	1	1



K-map for T_1 : (in terms of present state & control inputs)

	Q_1Q_0			
y	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$\Rightarrow T_1 = \bar{y}\bar{Q}_0 + yQ_0 = \bar{y} \oplus Q_0$$

49. Ans: (c)

$$\text{Sol: } V_{PO} = \frac{16 \times 10^{-9}}{4\pi\epsilon_0} \left[\frac{1}{d(PQ)} - \frac{1}{d(OQ)} \right]$$

$$= \frac{16 \times 10^{-9}}{4\pi\epsilon_0} \left[\frac{1}{\sqrt{12}} - \frac{1}{\sqrt{38}} \right] = 18.21V$$

$$V_{PO} = \frac{-\rho_L}{2\pi\epsilon_0} [\ln(d_p) - \ln(d_o)]$$

Co-ordinate of point P are (4, 1, 3). Coordinate of the foot of the perpendicular dropped from P on the line charge (2, 4, 3)

$$\therefore d_p = \sqrt{(4-2)^2 + (1-4)^2} = \sqrt{13}$$

Co-ordinate of point O are (0,0,0). Coordinate of the foot of the perpendicular dropped from O on the line charge (2,4,0)

$$\therefore d_o = \sqrt{(0-2)^2 + (0-4)^2} = \sqrt{20}$$

$$V_{PO} = -\frac{5 \times 10^{-9}}{2\pi\epsilon_0} [\ln(\sqrt{13}) - \ln(\sqrt{20})]$$

$$= 19.3852V$$

$$V_{PO} (\text{total}) = 18.21 + 19.3852 = 37.5952V$$

$$\text{Now } V_{PQ} = V_P - V_O$$

$$\Rightarrow V_p = V_{PO} + V_O = 37.5952 + 100$$

$$= 137.5952V$$

50. Ans: 23040 (23000 to 24000)

Sol: Initial load = $(P_1) = 50 \times 0.8 = 4kW$

$$P_1 = 4kW$$

$$\text{Final load } (P_2) = 3 \times 0.8 = 2.4kW$$

$$(P_2 = 2.4kW)$$

Given meter rotates 400 times in 150 seconds

\therefore Revolutions made in 1hr = r_1

$$r_1 = 400 \times \frac{60 \times 60}{150} = 9600$$

\therefore meter constant of the meter is

$$(K_1) = \frac{r_1}{P_1} = \frac{9600}{4} = 2400 \text{ rev/kWh}$$

$$\text{But meter constant } (K) \propto \frac{r}{\phi^2 R}$$

r = resistance to eddy currents

R = radius of disc

ϕ = flux of brake magnet

Given flux of brake magnet is halved

$$\therefore \phi_2 = \frac{\phi_1}{2}$$

$$\Rightarrow K_2 (\text{new meter constant}) = 4K_1$$

$$\therefore K_2 = 9600 \text{ rev/kWh}$$

\therefore revolutions the new meter will do in

$$1 \text{ hour} = 9600 \times P_2 \times 1 = 9600 \times 2.4$$

$$= 23040 \text{ rev}$$

51. Ans: 4

Sol: Using conjugate symmetry property

$$X[k] = X^* [N - k]. \text{ Here, } N = 5$$

$$X[1] = X^* [4] = 8.78 + j1.4$$

$$X[3] = X^* [2] = -1.28 + j4.39$$

$$x_0 = \frac{1}{N} \sum_{k=0}^{4} X[k]$$


$$= \frac{1}{5} [X(0) + X(1) + X(2) + X(3) + X(4)]$$

$$= 4$$




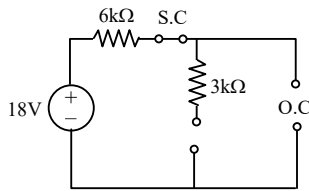52. Ans: – 60 V/sec (No Range)

Sol: At time $t = 0^-$ switch is in open condition



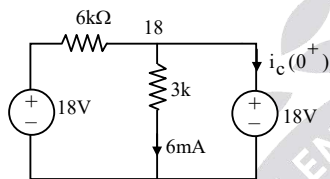So, L is short circuit, C is open circuit $i_L(0^-) = 0$



$$V_c(0^+) = V_c(0^-) = 18V$$

At $t = 0^+$ switch is closed

$$I_c(0^+) = C \frac{dv(0^+)}{dt}$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

$$i_c(0^+) = -6 \times 10^{-3} \text{ A}$$

$$\frac{dv(0^+)}{dt} = \frac{-6 \times 10^{-3}}{100 \times 10^{-6}}$$

$$\frac{dv(0^+)}{dt} = -60 \text{ V/sec}$$

53. Ans: 64 (No Range)

Sol: Since $F_3 = F_1$. $F_2 = \Sigma m(4, 6, 12)$, the function F_2 must have the minterms m_4, m_6 & m_{12} . Since $F_1 = \Sigma m(0, 1, 2, 3, 4, 6, 10, 11, 12, 13)$, the function F_2 may or may not have the remaining minterms viz. $m_5, m_7, m_8, m_9, m_{14}$ and m_{15} .

m_5	m_7	m_8	m_9	m_{14}	m_{15}	F_2
0	0	0	0	0	0	Σm (4,6,12)
0	0	0	0	0	1	Σm (4,6,12,15)
0	0	0	0	1	0	Σm (4,6,12,14)
⋮	⋮	⋮	⋮	⋮	⋮	⋮
1	1	1	1	1	1	Σm (4,5,6,7,8,9,12,14,15)

\Rightarrow Number of possible functions for F_2 is $2^6 = 64$

54. Ans: (a)

Sol: $\frac{d^2y}{dx^2} - y = 0$

$$m^2 - 1 = 0$$

$$\Rightarrow m = \pm 1$$

$$y = c_1 e^x + c_2 e^{-x}$$

$$y(0) = 2 \Rightarrow 2 = c_1 + c_2 \dots\dots\dots (1)$$

$$y' = c_1 e^x - c_2 e^{-x}$$

$$y'(0) = 0 \Rightarrow 0 = c_1 - c_2 \dots\dots\dots (2)$$

Solving (1) and (2), we get $c_1 = 1$ and $c_2 = 1$

$$y = e^x + e^{-x}$$

$$y = 2 \cosh x$$

55. Ans: (b)

Sol: $D = 0$, Load not change

$\Delta P_D = +ve$, so frequency decreases

$\Delta f = -ve$, so generation increases.