



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Offline GATE Mock – 4 _ Solutions

General Aptitude (GA)

One Mark Solutions:

01. Ans: (A)

(ACTION AND PURPOSE) One slices a cake before eating; one carves a turkey before cooking.





02. Ans: (C)

03. Ans: (A)

Apparent mean visible, easy to see or understand while Ambiguous mean no clear stated or defined.

04. Ans: (C)

Sol:

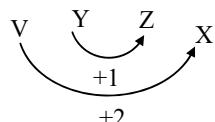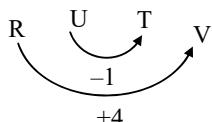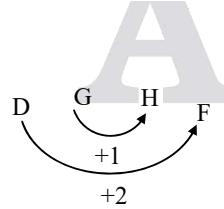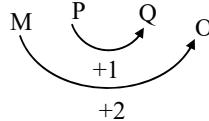

∴ RUTV is different Ans is (C)

05. Ans: (B)

Sol: Clearly, thirteenth result

$$= (\text{sum of 25 results}) - (\text{sum of 24 results})$$

$$= (18 \times 25) - [(14 \times 12) + (17 \times 12)]$$


$$= 450 - (168 + 204) = 450 - 372 = 78$$

Two Mark Solutions:

06. Ans: (C)

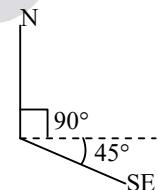
07. Ans: (C)

Sol: If south-East becomes north, it suggests that there is a movement of 135° in anti-clockwise direction.



Similarly, when North-East becomes west

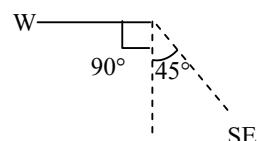∴ When west moves 135° in anti-clock wise direction, it becomes south-East





08. Ans: (B)

Sol: Dist covered by a wheel in 1 rev

= Circumference of the wheel

$$= 2\pi r$$

$$= 2 \times \frac{22}{7} \times 1.5$$

$$\text{No. of rev made} = \frac{\text{total distance covered}}{\text{distance in 1 Revolution}}$$

$$= \frac{5280}{2 \times \frac{22}{7} \times 1.5} \Rightarrow \frac{5280 \times 7}{66} \Rightarrow 560$$

$$\therefore \text{Time taken to cover the distance} = \frac{560}{28}$$

$$= 20 \text{ min}$$

09. Ans: (C)

Sol: Among all given alternatives, divisible by 3 is 48 only

$$\text{for } R \Rightarrow \frac{48}{3} = 16 \Rightarrow 48 - 16 = 32 + 4 = 36$$

$$\text{for } r S \Rightarrow \frac{36}{4} = 9 \Rightarrow 36 - 9 = 27 + 3 = 30$$

$$\text{for } T \Rightarrow \frac{30}{2} = 15 \Rightarrow 30 - 15 = 15 + 2 = 17$$

\therefore Ans 48

10. Ans: (B)

Specific section (EE)

One mark Solutions:

01. Ans: (C)

Sol: The given signal is finite duration both sided signal, so ROC is $0 < |z| < \infty$

02. Ans: (c)

Sol: Given $\frac{dy}{dx} = \left[\frac{y}{x} \right] + \tan\left(\frac{y}{x}\right)$

It is Homogeneous DE

$$\text{Put } \frac{y}{x} = v \Rightarrow y = vx$$

$$\Rightarrow \frac{dy}{dx} = v + x \frac{dy}{dx}$$

$$\frac{dy}{dx} = \left(\frac{y}{x} \right) + \tan\left(\frac{y}{x}\right)$$

$$\Rightarrow v + x \frac{dv}{dx} = v + \tan(v)$$

$$\Rightarrow x \frac{dv}{dx} = \tan v$$

$$\Rightarrow \int \cot v dv = \int \frac{dx}{x}$$


$$\Rightarrow \log(\sin v) = \log x + \log c$$

$$\Rightarrow \log(\sin v) = \log(cx)$$

$$\therefore \sin\left(\frac{y}{x}\right) = cx \text{ is required solution}$$

03. Ans: (A)

Sol: Capacitance Distribution Network

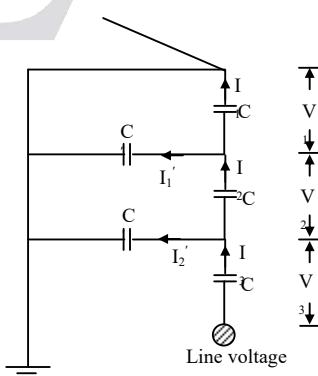

Top unit, $V_1 = 7\text{kV}$

Middle unit, $V_2 = 10\text{kV}$



$$\frac{\text{Pin to earth capacitance}}{\text{Self capacitance}} = K$$

$$V_2 = (1+K)V_1$$


$$10 = (1+K) \times 7$$

$$1 + K = \frac{10}{7}$$

$$K = \frac{10}{7} - 1 = 0.42$$

04. Ans: (D)

Sol: Calculate the terminal voltage

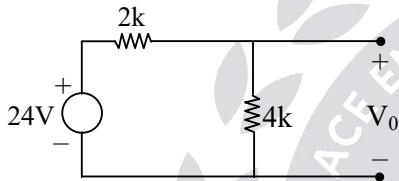

$$= \frac{24(4)}{2+4} = 16V$$

$V_0 < (V_z + V_{DON})$, therefore no current flows

$$\text{through zener, } I_L = \frac{V_0}{4k} = \frac{16}{4k} = 4\text{mA}$$

05. Ans: (D)

$$\text{Sol: Ripple factor, R.F} = \frac{\sqrt{V_{or}^2 - V_0^2}}{V_0}$$

$$R.F = \frac{\sqrt{\alpha V_s^2 - \alpha^2 V_s^2}}{\alpha V_s}$$

$$R.F = \sqrt{\frac{1}{\alpha} - 1} = \sqrt{(1-\alpha)/\alpha}$$

06. Ans: 8.66

$$\text{Sol: \% Reg} = \frac{V_{sc}}{E_2} \times \cos(\phi_{sc} - \phi) \times 100$$

$$= \frac{220}{2200} \times \cos(75 - 45^\circ) \times 100 = 8.66\%$$

07. Ans: (D)


Sol: Unstable system, hence error is unbounded

$$CE = 1 + \frac{9}{s^2(s+3)} = 0$$

$s^3 + 3s^2 + 9 = 0$ system is unstable and hence steady state error = ∞ .

08. Ans: (B)

Sol:

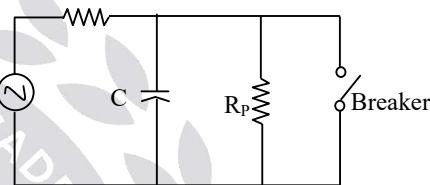

The value of resistance R_p needed for critical damping of restriking voltage is

$$R_p = \frac{1}{2} \sqrt{\frac{L}{C}} \Rightarrow R_p = \frac{1}{2} \sqrt{\frac{1}{0.01 \times 10^{-6}}} = 5000 \Omega = 5 \text{ k}\Omega$$

$$R_p = \frac{1}{2} \times 10^4 \Rightarrow R_p = 5000 \Omega = 5 \text{ k}\Omega$$

09. Ans: (D)

Sol: Let Q_n be the present state and Q_{n+1} be next state of given X – Y flip-flop.

X	Y	Q_n	Q_{n+1}
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0



Solving from K-map

	00	01	11	10
0	1	1	1	1
1	1	5	7	6

Characteristic equation of X – Y flip-flop is

$$Q_{n+1} = \overline{Y} \overline{Q}_n + \overline{X} Q_n$$

Characteristic equation of a J – K flip-flop is given by

$$Q_{n+1} = J\overline{Q}_n + \overline{K}Q_n$$

By comparing

$$J = \overline{Y}, K = X$$

10. Ans: (B)

Sol: efficiency $\eta = \frac{P_{out}}{P_{in}}$

$$P_{in} = \frac{P_{out}}{\eta} = \frac{7.46 \times 10^3}{0.85} = 8.77 \text{ kW}$$

Motor line current, $I_L = \frac{P_{in}}{V} = \frac{8.77 \times 10^3}{440}$
 $= 19.93 \text{ A}$

$$I_{sh} = \frac{V}{R_{sh}} = \frac{440}{200} = 2.2 \text{ A}$$

Armature current, $I_a = I_L - I_{sh} = 19.93 - 2.2$
 $= 17.73 \text{ A}$

$$E_a = V - I_a R_a = 440 - 17.73 \times 0.6 = 429.36 \text{ V}$$

11. Ans: (A)

In graph theory,

- Every f-loop consists of only one link in its representation
- Every f-cutset consists of only one twig in its representation

- Tree connects all the nodes without any closed loop
- In a complete graph, between any pair of nodes only one branch is connected for all the combinations.

12. Ans: 1

13. Ans: (B)

Sol: The probability density function of X is

$$f(x) = \begin{cases} \frac{1}{30}, & 0 < x < 30 \\ 0, & \text{otherwise} \end{cases}$$

$$P(5 < X < 10) = \int_5^{10} f(x) dx = \int_5^{10} \frac{1}{30} dx = \frac{1}{6}$$

14. Ans: 0.93 (Range: 0.9 – 0.95)

Sol: Required probability = $P(A \cup B \cup C)$

$$\begin{aligned} &= P(A) + P(B) + P(C) - P(A \cap B) - P(B \cap C) - \\ &P(A \cap C) + P(A \cap B \cap C) \\ &= 0.8 + 0.5 + 0.3 - (0.8)(0.5) - (0.5)(0.3) - \\ &(0.8)(0.3) + (0.8)(0.5)(0.3) \\ &= 0.93. \end{aligned}$$

15. Ans: (A)

Sol: $S = 2000 \text{ MW}; P = 1000 \text{ MW}$

$H = 5 \text{ MW/MVA}; R = 2.4 \text{ Hz/pu MW}$

$$B = \frac{\frac{1}{100} \times 1000}{\frac{1}{100} \times 50} = \frac{10}{0.5} = 20$$

Damping coefficient ‘B’ in pu MW/Hz

$$= \left(\frac{\partial P_D}{\partial f} \right) / P_r = \frac{20}{2000}$$

$$= 0.01 \text{ pu MW/Hz}$$



16. Ans: (A)

Sol: If A and B are independent, then

$$P(A \cap B) = P(A) \cdot P(B)$$

$$\Rightarrow P(A \cap B) = (0.4) \cdot P(B) \dots\dots\dots (1)$$

By addition theorem,

$$P(A \cup B) = P(A) + P(B) - P(A \cap B)$$

$$\Rightarrow 0.6 = (0.4) + P(B) - P(A \cap B) \dots\dots\dots (2)$$

From (1), and (2),

$$0.6 = 0.4 + P(B) - (0.4) P(B)$$

$$\Rightarrow P(B) = \frac{1}{3}$$


17. Ans: (C)

Sol: Both diodes are RB

$$I_D = \frac{15}{8k + 3k} = \frac{15}{11} \text{ mA}$$

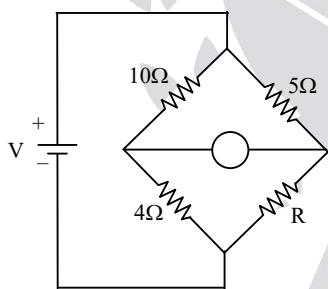18. Ans: (A)

Sol: By using wheatstone bridge principle



$$10 \times R = 20 \Rightarrow R = 2 \Omega$$

19. Ans: (B)

20. Ans: 1.14 Ω [Range 1.1 to 1.2]

Sol: $E_{b1} = V - I_a R_a = 240 - 40 (0.3) = 228 \text{ V}$

$$\frac{E_{b2}}{E_{b1}} = \frac{N_2}{N_1}$$

$$\Rightarrow E_{b2} = \frac{1200}{1500} \times 228$$

$$= 182.4 \text{ V}$$

$$\text{Now } E_{b2} = V - I_a (R_a + R_{se}) = 182.4 \text{ V}$$

$$\Rightarrow 240 - 40 (0.3 + R_{se}) = 182.4$$

$$\Rightarrow R_{se} = 1.14 \Omega$$

21. Ans: (C)

Sol: Stoke's theorem is

$$\oint \overline{H} \cdot d\overline{l} = \int J \cdot ds$$

Converts form closed line to open surface.

22. Ans: (A)

Sol: Root locus diagram starts at poles are at $s = 0$, $s = -20$ and $s = \infty$ and ends/terminates at $s = -10$, $s = -10$ and $s = -100$.

23. Ans: (D)

Sol: The given D.E

$$4y''' + 4y'' + y' = 0$$

$$\Rightarrow 4D^3 + 4D^2 + D = 0$$

$$\Rightarrow D(2D + 1)^2 = 0$$

$$\therefore D = 0, \frac{-1}{2}, \frac{-1}{2}$$

$$\therefore y_c = C_1 + (C_2 + C_3x)e^{-1/2}x$$

24. Ans: (D)

Sol: $I_{LV} = 10 \times 2 = 20 \text{ A}$

(transformation ratio = 2)

$$Z = 0.15 + j0.37 = 0.399 \angle 67^\circ$$

$$I_0 = \frac{200}{600} - \frac{j200}{300} = 0.33 - j0.67$$

$$I = I'_1 + I_0 = 20 \angle -36.86 + 0.33 - j0.67$$

$$= 20.65 \angle -37.8$$



25. Ans: 1

Sol: Here, $i_L(0^-) = 0A = i_L(0^+)$

$$V_C(0^-) = 0V = V_C(0^+)$$

By KVL in s-Domain \Rightarrow

$$\frac{10}{s} = 2I(s) + 1s I(s) + \frac{2}{s} I(s)$$

$$= I(s) \left(2 + s + \frac{2}{s} \right)$$

$$\Rightarrow \frac{10}{s} = I(s) \frac{(2s + s^2 + 2)}{s}$$

$$\Rightarrow I(s) = \frac{10}{s^2 + 2s + 2}$$

So, the characteristic equation is

$$s^2 + 2s + 2 = 0$$

by comparing with $s^2 + 2\xi\omega_n s + \omega_n^2 = 0$

$$\Rightarrow 2\xi\omega_n = 2 \Rightarrow \xi\omega_n = 1$$

$$\Rightarrow \tau = \frac{1}{\xi\omega_n} \text{ sec} = \frac{1}{1} = 1 \text{ sec}$$

Two Marks Solutions:

26. Ans: (A)

Sol: Let the output from the upper first level multiplexer is f_a and form the lower first level multiplexer is f_b

$$f_a = \bar{w}\bar{x} + w\bar{x},$$

$$f_b = \bar{w}\bar{x} + wx = x$$

$$f = f_a \bar{y}\bar{z} + f_b y\bar{z} + yz = (\bar{w}\bar{x} + w\bar{x})\bar{y}\bar{z} + xy\bar{z} + yz$$

$$= \bar{w}x\bar{y}\bar{z} + w\bar{x}\bar{y}\bar{z} + xy + yz$$

27. Ans: (C)

Sol: Given data:

$$R_1 = 1500\Omega, C_1 = 0.03$$


$$R_2 = 1876 \Omega \text{ in series with } C_2 = 0.03 \mu F$$

CD = unknown

$$DA = C_3 = 0.5 \mu F$$

We don't know the value of 'Z', but it is a combination of R, L (or) R, C.

$$Z_1 Z_4 = Z_2 Z_3$$

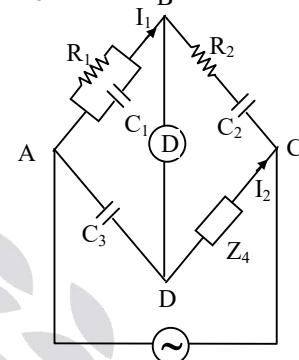

$$\left(\frac{R_1}{1 + j\omega C_1 R_1} \right) Z_4 = \left(R_2 + \frac{1}{j\omega C_2} \right) \frac{1}{j\omega C_3}$$

$$Z_4 = \left(\frac{R_2}{j\omega C_3} - \frac{1}{\omega^2 C_2 C_3} \right) \left(\frac{1 + j\omega C_1 R_1}{R_1} \right)$$

$$= \frac{R_2}{jR_1\omega C_3} + \frac{C_1}{j\omega C_2 C_3} + \frac{R_2 C_1}{C_3} - \frac{1}{\omega^2 C_2 C_3 R_1}$$

Substitute all values.

$$Z_4 = 112.559 - j716.3$$

Z_4 is a combination of R and C

$$\frac{1}{\omega C_4} = 716.3$$

$$C_4 = \frac{1}{716.3 \times 2\pi \times 10^3} = 0.222 \mu F$$

28. Ans: (C)

Sol: 2000H : LXI SP, 2724H ; (SP) = 2724H

2003H : CALL 2006H ;

(TOS) \leftarrow (PC), (SP) $\downarrow\downarrow$

(TOS) = 2006H

(SP) = 2722H

2006H : POP H ; (HL) \leftarrow (TOS), (SP) $\uparrow\uparrow$

(HL) = 2006H



$$(SP) = 2724 \text{ H}$$

$$2007\text{H} : \text{INR H} ; (H) \leftarrow (H) + 1$$


$$(H) = 21$$

Thus $(HL) = 2106\text{H}$ & $(SP) = 2724\text{H}$

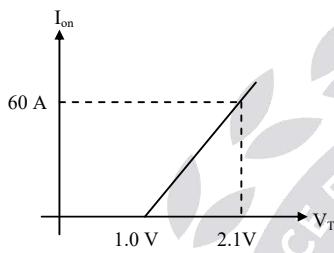29. Ans:(C)


Sol: Given that

$$v_T = 1 + \frac{2.1 - 1}{60} i_a = 1 + 0.0183 i_a$$




$$R_d = \frac{2.1 - 1.0}{60} = 18.33 \text{ m}\Omega$$

The diode is represented as follows

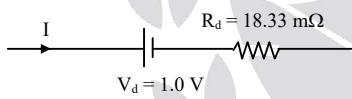

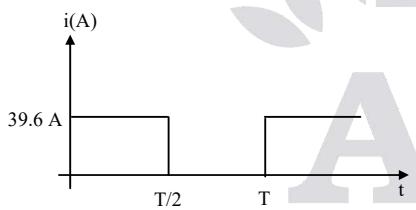A level current of 39.6 A for one half cycle.



$$I_{avg} = 39.6 \times \frac{T/2}{T} = \frac{39.6}{2} = 19.8 \text{ A}$$

$$I_{rms} = 39.6 \sqrt{\frac{\frac{T}{2}}{T}} = \frac{39.6}{\sqrt{2}}$$

$$I_{rms} = 28 \text{ A}$$

Mean power loss

$$= 19.8 \times 1 + 28^2 \times 18.33 \times 10^{-3}$$

$$= 34.17 \text{ W}$$

30. Ans: (D)

31. Ans: (421.39) Range: (417 to 424)

Sol: $|\bar{E}| = \frac{k}{\rho}$

$$W_E = \frac{\epsilon_0}{2} \int |\bar{E}|^2 dv$$

$$= \frac{\epsilon_0}{2} \int_2^3 \int_0^{\pi/2} \int_0^7 \frac{k^2}{\rho^2} \times \rho d\rho d\phi dz$$

$$= \frac{\epsilon_0}{2} \times k^2 \times [\ln \rho]_2^3 [\phi]_0^{\pi/2} [z]_5^7$$

$$= k^2 \times \frac{10^{-9}}{36\pi \times 2} \times \ln\left(\frac{3}{2}\right) \times \frac{\pi}{2} \times 2$$

$$= k^2 \times \frac{10^{-9}}{72} \times \ln\left(\frac{3}{2}\right)$$

$$W_E = 1 \mu J = 10^{-6}$$

$$\Rightarrow k^2 \times \frac{10^{-9}}{72} \times \ln\left(\frac{3}{2}\right) = 10^{-6}$$

$$\Rightarrow k^2 = \frac{72}{10^{-3} \times \ln\left(\frac{3}{2}\right)} = 177573.84$$

$$\Rightarrow k = 421.39$$

32. Ans : (A)

Sol: $A = 0.96 \angle 1^\circ$ $B = 100 \angle 80^\circ \Omega$; $\delta = 30^\circ$

$$|V_{SL}| = |V_{RL}| = 110 \text{ kV}$$

$$V_s = AV_r + BI_r$$

Receiving end voltage,

$$V_{rph} = \frac{110 \text{ kV}}{\sqrt{3}} \angle 0^\circ \text{ (reference)}$$

Sending end voltage,

$$V_{sph} = \frac{110 \text{ kV}}{\sqrt{3}} \angle 30^\circ$$

From ABCD equations,

$$V_{sph} = AV_{rph} + BI_{rph}$$



$$I_{\text{rph}} = \frac{V_{\text{sph}} - AV_{\text{rph}}}{B}$$

$$I_{\text{rph}} = \frac{\frac{110k}{\sqrt{3}} \angle 30^\circ - (0.96 \angle 1^\circ) \left(\frac{110k}{\sqrt{3}} \angle 0^\circ \right)}{100 \angle 80^\circ}$$

$$I_{\text{rph}} = 312.63 \angle 20.98^\circ \text{ A}$$


$$\begin{aligned} \text{Receiving end current magnitude } |I_{\text{rph}}| \\ = 312.63 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Receiving end power factor } \cos\phi_r \\ = \cos(\text{angle between } V_{\text{rph}} \text{ & } I_{\text{rph}}) \\ = \cos(0 - 20.98) = 0.933 \text{ leading} \end{aligned}$$

33. Ans: -38.5 (Range -37 to -39)

Sol: By superposition theorem


Take 50V (100V – short circuit)

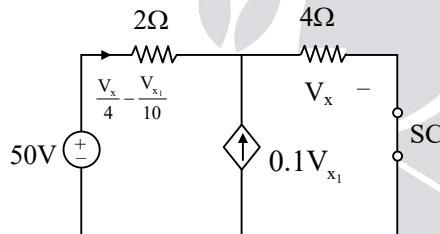

$$50 = \frac{V_{x_1}}{2} - \frac{V_{x_1}}{5} + V_{x_1}$$

$$V_{x_1} = 38.5 \text{ Volts}$$

Take 100V (50V – short circuit)

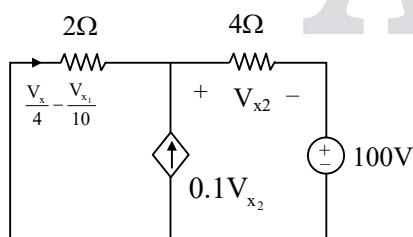

$$\frac{V_{x_2}}{2} - \frac{V_{x_2}}{5} + V_{x_2} + 100 = 0$$

$$5V_{x_2} - 2V_{x_2} + 10V_{x_2} + 1000 = 0$$

$$13V_{x_2} = -1000$$

$$V_{x_2} = -77$$

$$\begin{aligned} \text{By superposition theorem } V_x &= V_{x_1} + V_{x_2} \\ &= 38.5 - 77 \\ &= -38.5 \text{ V} \end{aligned}$$

34. Ans: δ_{cr} = 70.336 (68 to 72)

Sol: δ = 30°, P_{m2} = 0.5, P_{m3} = 1.5, P_s = 1.0

$$\delta_{0(\text{rad})} = 0.52$$

$$\delta_{\max} = 180 - \sin^{-1} \left(\frac{P_s}{P_{m3}} \right)$$

$$= 180 - \sin^{-1} \left(\frac{1.0}{1.5} \right)$$

$$\delta_{\max} = 180 - 41.80 = 138.18$$

$$\delta_{\max} = 138.18 \times \frac{\pi}{180} = 2.41$$

$$\delta_c = \cos^{-1} \left[\frac{1.0(2.41 - 0.523) + 1.5 \cos 138.18 - 0.5 \cos 30^\circ}{1.5 - 0.5} \right]$$

$$= \cos^{-1} \left[\frac{1.00 \times 1.887 + 1.5 \times -0.7452 - 0.5 \times \frac{\sqrt{3}}{2}}{1} \right]$$

$$= \cos^{-1} [1.887 + (-1.1175) - 0.433]$$

$$= \cos^{-1} [1.887 - 1.5505]$$

$$= \cos^{-1} [0.3365] = 70.336^\circ.$$

35. Ans: 6

Sol: Loops are L₁ = gh, L₂ = ab, L₃ = dc, L₄ = ef, L₅ = ebch and L₆ = gdaf.

36. Ans: (B)

$$\text{Sol: } e^{-|t|} \leftrightarrow \frac{2}{1 + \omega^2}$$

$$\frac{2}{1 + t^2} \leftrightarrow 2\pi e^{-|\omega|}$$

$$\frac{1}{1 + t^2} \leftrightarrow \pi e^{-|\omega|}$$



37. Ans: (C)

Sol: Force acting on electron

$$\bar{F} = -e\bar{E} = -1.6 \times 10^{-19} (-2.5 \times 10^6 \hat{a}_z)$$

$$= 4 \times 10^{-13} \hat{a}_z \text{ N}$$

$$F = ma = m \frac{dv}{dt}$$

$$\Rightarrow dv = \frac{F dt}{m}$$

$$v = \int \frac{F}{m} dt + C$$

$$= \int \frac{4 \times 10^{-13}}{9.11 \times 10^{-31}} dt + C$$

$$= 4.39 \times 10^{17} t + C$$

We have at $t = 0, v = 0$, so that $C = 0$

$$\therefore v(t) = 4.39 \times 10^{17} t \text{ m/sec}$$

38. Ans: (C)

Sol: Given that

$$3\text{-}\phi V_s = 230 \text{ V}, L_s = 4 \text{ mH}; 3$$

$$I_0 = 10 \text{ A}$$

$$\text{Given } V_0 = -210 \text{ V}$$


$$\cos \alpha = \frac{\pi \left(V_0 + \frac{3\omega L_s}{\pi} I_0 \right)}{3V_m \ell}$$

$$\cos \alpha = \frac{\pi(-210+12)}{3 \times \sqrt{2} \times 230} = -0.6375$$

$$\alpha = 129.60^\circ$$

39. Ans: - 2.886 (Range: - 2.6 to - 3.0)

Sol:

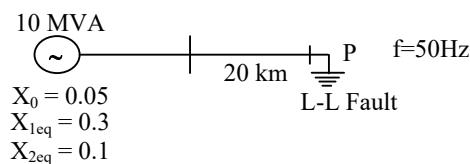

$$\text{GMD} = \sqrt[3]{5 \times 5 \times 5} = 5$$

$$\text{Self GMD} = 0.7788 \times 0.5 \times 10^{-2}$$

$$= 3.894 \times 10^{-3} \text{ m}$$

$$L = 2 \times 10^{-4} \ln \left(\frac{5}{3.894 \times 10^{-3}} \right)$$

$$= 14.315 \times 10^{-4} \text{ H/km}$$

For 20 km length total inductance

$$L_{\text{eq}} = 14.315 \times 10^{-4} \times 20$$

$$= 0.0286 \text{ H}$$

$$X_{\text{eq}} = 2\pi f L_{\text{eq}}$$

$$= 2\pi \times 50 \times 0.0286 = 8.994 \Omega$$


p.u. reactance of the line

$$= 8.994 \times \frac{10 \times 10^6}{(30 \text{ kV})^2} = j 0.1 \text{ p.u.}$$

Transmission line $X_{1\text{eq}} = X_{2\text{eq}} = j 0.1 \text{ p.u.}$

LL-fault occurs at point P.
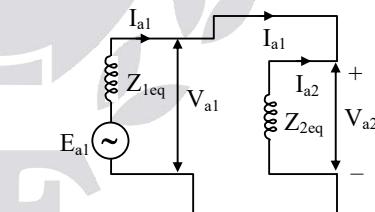
$$I_f = \frac{-j\sqrt{3} E_{a1}}{X_{1\text{eq}} + X_{2\text{eq}}} \quad [E_{a1} = \text{prefault voltage}]$$



$$I_f = \frac{-j\sqrt{3} \times 1.0}{(j0.3 + j0.1) + (j0.1 + j0.1)}$$

$$I_f = -2.886 \text{ p.u.}$$

40. Ans: 4

Sol: For the source free RC – circuit and with the given connection,

$$V_{C_1}(\infty) = V_{C_2}(\infty) = \frac{V_1 C_1 + V_2 C_2}{C_1 + C_2} \text{ Volts}$$

Where $V_1 = V_{C_1}(0)$ and $V_2 = V_{C_2}(0)$



$$\Rightarrow V_{C_1}(\infty) = V_{C_2}(\infty) = \frac{10.2 + 0.3}{2+3} \text{ Volts} \\ = 4V$$

41. Ans: (D)


Sol: $V_{E1} = 0.7V$

$$V_{E2} = V_{E1} - 0.7 = 0.7 - 0.7 = 0V$$

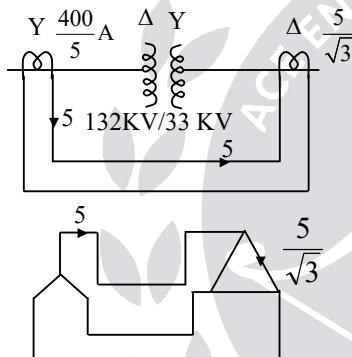42. Ans : 554.25 (Range :553 to 556)

Sol: The current transformer is connected opposite connection

i.e., Δ -side winding Y connection current transformer is taken to avoid phase angle.



The primary rating of current transformer is obtained by

$$400 \times 132 = 33 \times x$$

$$\Rightarrow x = 1600 \text{ A}$$

The phase current of secondary side of HV CT
= 5A

\therefore The pilot current = 5A = Line current

\therefore The phase current of Δ connected current

$$\text{transformer} = \frac{5}{\sqrt{3}} \text{ A.}$$

\therefore The current transformer ratio on LT side

$$= \frac{1600}{5/\sqrt{3}} = \frac{1600\sqrt{3}}{5} = 320\sqrt{3} = 554.25$$

Shortcut: The current in pilot wire and always taken as line current and current transformer rating is taken as phase currents.

43. Ans: (C)

Sol: $y(n) = x(n)*h_1(n)*h_2(n)$

$$Y(z) = X(z) H_1(z) H_2(z)$$

$$H_1(z) = \frac{1}{1 - 0.5z^{-1}}$$

$$H_2(z) = 1 - 0.5z^{-1}$$

$$Y(z) = X(z)$$

↓ IZT

$$y(n) = x(n)$$

44. Ans: (B)

Sol: The PM of a system is approximately equals to 100ξ

$$40^\circ = 100\xi$$

$$\therefore \xi = 0.4$$

45. Ans: (A)

Sol: $e = -N \frac{d\phi}{dt}$;

$$\phi = \frac{-1}{N} \int \text{edt}$$

$$= \frac{-1}{200} \int (200 \sin \omega t - 50 \sin 3\omega t) dt$$

$$\phi = \frac{1}{200} \left[\frac{200}{\omega} \cos \omega t - \frac{50}{3\omega} \cos 3\omega t \right] \text{Wb}$$

$$\omega = 100 \pi,$$

$$\phi = \frac{1000}{200} \left[\frac{200}{100\pi} \cos \omega t - \frac{50}{300\pi} \cos 3\omega t \right] \text{mWb}$$

$$\phi = 5 \left[\frac{2}{\pi} \cos \omega t - \frac{1}{6\pi} \cos 3\omega t \right] \text{mWb}$$



$$= \frac{5}{\pi} \left[2 \cos \omega t - \frac{1}{6} \cos 3\omega t \right]$$

$$W_e \propto \phi^2 f^2$$

$$W_1 = K[(2)^2 \times \omega^2 + (1/6)^2 \times 9\omega^2]$$

$$= K[4.25 \omega^2]$$

$$W_2 = K(2^2 \omega^2) = K \times 4\omega^2$$

$$\% \text{ Reduction} = \frac{4.25 - 4}{4.25} = 5.88\%$$

46. Ans: (D)

Sol: Let $f = 4x - 2y + 3z - 4$;

Then $\hat{a}_x = \pm \frac{\bar{\nabla}f}{|\bar{\nabla}f|}$ gives possible unit vector

which are perpendicular to f .

The unit vector with negative sign gives the unit vector which is directed from higher value of f toward the lower value of f . the unit vector with positive sign gives the unit vector which is directed from lower value of f towards the higher value of f .

We have to determine \bar{a}_{21}

In region 1, at $P_1(0, 0, 100)$;

$$f_1 = 4 \times 0 - 2 \times 0 + 3 \times 100 - 4 \\ = 296$$

In region 2, at $P_2(0, 0, -100)$;

$$f_2 = 4 \times 0 - 2 \times 0 + 3 \times -100 - 4 \\ = -304$$


Hence we have to determine the unit vector from lower value of f ($f_2 = -304$) towards higher value of f ($f_1 = 296$). That is with positive sign

$$\hat{a}_n = \frac{\bar{\nabla}f}{|\bar{\nabla}f|} = \frac{4\hat{a}_x - 2\hat{a}_y + 3\hat{a}_z}{\sqrt{(4)^2 + (-2)^2 + (3)^2}}$$

$$= 0.74\hat{a}_x - 0.37\hat{a}_y + 0.55\hat{a}_z$$

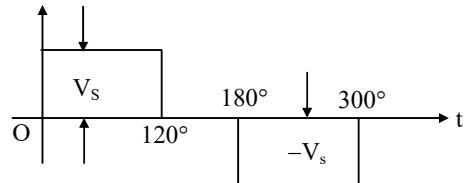47. Ans: 200 (200 to 200)

Sol: In 180° conduction mode the voltage wave form



$$\text{So, peak to peak voltage} = V_s - (-V_s)$$

$$= 2V_s$$

$$= 2 \times 100$$

48. Ans: (B)

$$\text{Sol: } \frac{V_o}{V_{in}} = \frac{+g_m R_c}{2} = \left(\frac{I_{CDC}}{v_t} \right) \cdot \frac{R_c}{2} = \frac{1mA}{Q5m} \left(\frac{2K}{2} \right) \\ = \frac{1000}{25} = 40$$

49. Ans: (C)

Sol: electrical input = $P_{\text{mech.output}} + \text{friction Loss} + \text{core Loss}$

$$= 9kW + 2kW + 0.8kW$$

$$P_{in} = 11.8kW.$$

$$\sqrt{3}V_L I_L \cos \phi = 11800$$

$$\Rightarrow \sqrt{3} \times 400 \times I_L \times 0.8 = 11800 \Rightarrow I_L = 21.29A$$

50. Ans: (B)

Sol: $-X = \bar{X} + 1$ in 2's complement form

$$\text{MVI A,X} ; \quad (\text{A}) = X$$

$$\text{CMA} ; \quad (\text{A}) = \bar{X}$$


$$\text{ADI 01H} ; \quad (\text{A}) = \bar{X} + 1$$



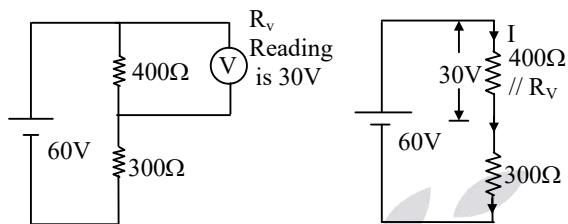51. Ans: 22.5 (Range: 22 to 23)

Sol: Say, the voltmeter resistance is R_v .

When the voltmeter is connected across 400Ω , the reading of the voltmeter is the voltage across parallel combination of 400Ω & R_v .



The voltage across 300Ω is 30V.

$$V_{300\Omega} = 60V - 30V = 30V$$

$$I = \frac{30V}{300\Omega} = 0.1A$$

Reading of voltmeter = 'V' across $400\Omega//R_v$

$$30V = 0.1A \times 400\Omega//R_v$$

$$\Rightarrow 400\Omega//R_v = \frac{30V}{0.1A}$$



$$\Rightarrow \frac{400\Omega \times R_v}{400\Omega + R_v} = 300\Omega$$

$$400\Omega \times R_v = 400\Omega \times 300\Omega + 300\Omega \times R_v$$

$$100\Omega \times R_v = 400\Omega \times 300\Omega$$

$$\Rightarrow R_v = 1200\Omega.$$

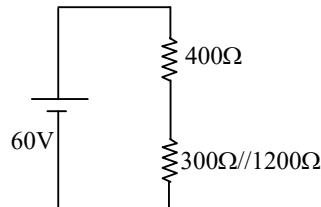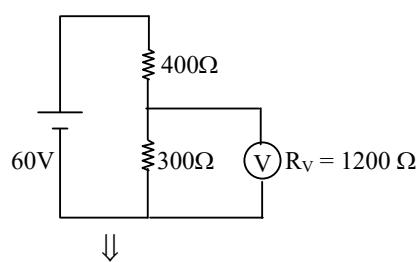Now, the same voltmeter (with R_v of 1200Ω) is connected across 300Ω . As such, the reading of voltmeter is the voltage across parallel combination of 300Ω & 1200Ω .



$$R_{eff} = \frac{300\Omega \times 1200\Omega}{1500\Omega} = 240\Omega$$

∴ Reading of voltmeter

$$= 60V \times \frac{240\Omega}{400\Omega + 240\Omega}$$

$$= 60V \times \frac{240\Omega}{640\Omega} = 22.5V$$

Voltmeter indicates 22.5V.

52. Ans: (B)

Sol: The given matrix is upper triangular. The eigen values of A are same as the diagonal elements of A.

∴ Eigen values are $\lambda = 2, 2, 2$

The eigen vectors for $\lambda = 2$ are given by

$$[A - 2I]X = 0 \text{ where } X = \begin{bmatrix} x \\ y \\ z \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow y = 0, \text{ and } z = 0$$

∴ Any non zero vector with y and z components as 0, is an eigen vector of A.

53. Ans: (A)

$$\text{Sol: } S_m = \frac{R_2}{X_2} = \frac{0.3}{2.5} = 0.12$$



$$\frac{T_{st}}{T_{max}} = \frac{2S_m}{S_m^2 + 1} = \frac{2 \times 0.12}{(0.12)^2 + 1} = 0.2366 \dots\dots(1)$$

Given $T_{max} = 3T_{full}$

from (1), $T_{st} = 0.2366[3 \times T_{full}]$

$$T_{st} = 3 \times 0.2366 T_{full}$$


In star-delta staring

$$T_{st} = \frac{1}{3} T_{full} = \frac{1}{3} \times 3 \times 0.2366$$

$$\frac{T_{st}}{T_{full}} = 0.2366$$

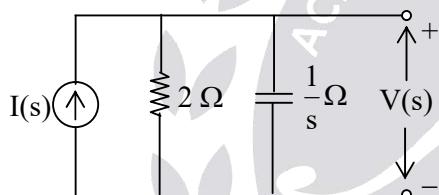54. Ans: (A)

Sol: The transform circuit is shown in below



$$V(s) = \frac{I(s)}{Y(s)}$$

$$Y(s) = s + 0.5$$

$$\text{For step response, } i(t) = 1 u(t), I(s) = \frac{1}{s}$$

$$V(s) = \frac{1}{s(s+0.5)} = \frac{A}{s} + \frac{B}{s+0.5} = \frac{2}{s} - \frac{2}{s+0.5}$$

$$v(t) = 2 [1 - e^{-0.5 t}] u(t)$$

55. Ans: (D)

$$\text{Sol: } \begin{bmatrix} \dot{x}_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u(t)$$

$$y(t) = [1 \ 3] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

$$A = \begin{bmatrix} 0 & 1 \\ 1 & 1 \end{bmatrix} B = \begin{bmatrix} 0 \\ 1 \end{bmatrix} C = [1 \ 3]$$

$$T.F = C [SI - A]^{-1} B$$

$$[SI - A] = \begin{bmatrix} s & -1 \\ -1 & s-1 \end{bmatrix}$$

$$[SI - A]^{-1} = \frac{\begin{bmatrix} s-1 & 1 \\ 1 & s \end{bmatrix}}{s^2 - s - 1}$$

$$C[SI - A]^{-1} B = \frac{\begin{bmatrix} 1 & 3 \end{bmatrix} \begin{bmatrix} s-1 & 1 \\ 1 & s \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix}}{s^2 - s - 1}$$

$$= \frac{\begin{bmatrix} 1 & 3 \end{bmatrix} \begin{bmatrix} 1 \\ s \end{bmatrix}}{s^2 - s - 1} = \frac{1 + 3s}{s^2 - s - 1}$$