

$$X_T = j0.96 + j0.286 + j(0.38 \parallel 0.38) + j0.286$$

$$= 1.722 \text{ pu}$$

$$P_0 = \frac{EV}{X} \sin \delta$$

$$P_0 = 1 \text{ pu}$$

$$\text{Minimum value } \sin \delta = 1$$

$$E_{\min} = \frac{PX}{V}$$


$$E_{\min} = \frac{1 \times 1.722}{1} = 1.722 \text{ pu}$$

44. Ans: (B)

Sol: Given that $\beta = 100$

To calculate 'r_e' value, apply DC Analysis

Apply KVL to input loop

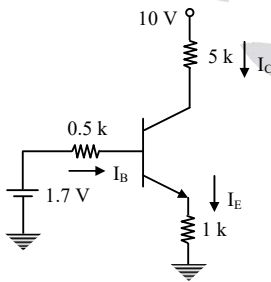

$$1.7 - 0.5 \times 10^3 I_B - 0.7 - 10^3(1+\beta)I_B = 0$$


$$I_B = \frac{1}{10^3(0.5+101)} = 9.852 \mu\text{A}$$

$$I_E = (1+\beta) I_B = 0.995 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = 25.12 \Omega$$

To calculate voltage gain apply AC Analysis

Voltage gain

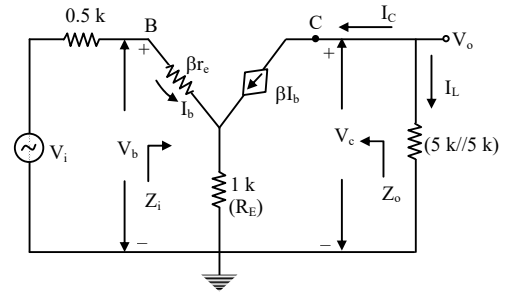

$$A_v = \left(\frac{V_o}{V_b} \right) = \frac{-I_C(2.5k)}{I_b [\beta r_e + (1+\beta)R_E]}$$

$$A_v = \frac{-\beta \times 2.5 \times 10^3}{\beta r_e + (1+\beta)R_E} = \frac{-100 \times 2.5 \times 10^3}{(2.512 + 101) \times 10^3}$$

$$= \frac{-250}{103.512}$$

$$= -2.415$$

$$\text{Voltage amplification } A = A_v \left(\frac{z_i^1}{z_i^1 + R_s} \right)$$

$$\text{Where } z_i^1 = Z_i = \beta r_e + (1+\beta) R_E$$

$$= 103.512 \text{ k}\Omega$$

$$A = -2.415 \left(\frac{103.512}{104.012} \right)$$

$$= -2.4034$$

$$\therefore A = -2.4$$

45. Ans: (B)

Sol: Given $\cos \theta = 0.8$

$$\theta = \cos^{-1} 0.8 = 36.86^\circ$$

$$P_1 = V_L I_L \cos (30 - 36.86)$$

$$P_2 = V_L I_L \cos (30 + 36.86)$$




$$P_1 = 208 \times 12 \cos (30 - 36.86)$$

$$P_1 = 2478 \text{ W}$$

$$P_2 = 208 \times 12 \cos (30 + 36.86) \Rightarrow P_2 = 980 \text{ W}$$

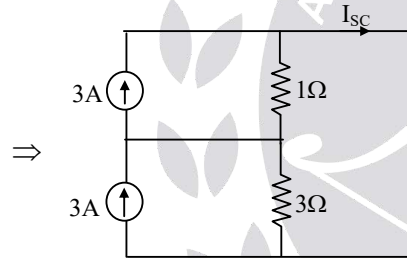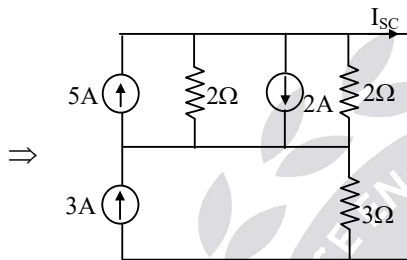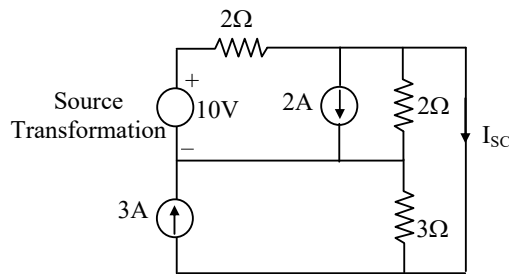46. Ans: 3 [Range 3]



Sol: Find out short circuit current (I_{sc})



$\therefore I_{sc} = 3A$

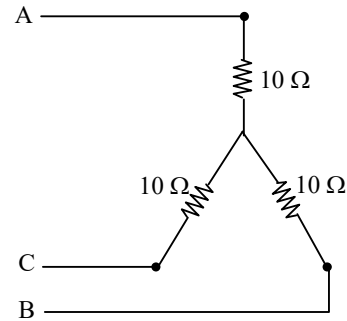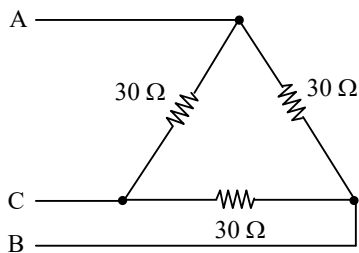47. Ans: (B)

Sol: Convert delta connected load into star connected load.



\therefore In 120° conduction scheme,

$$V_{ph} = \frac{V_{dc}}{\sqrt{6}} = 163.3V$$

3- ϕ load power

$$P_0 = 3 \left[\frac{V_{ph}^2}{R} \right] = 3 \times \frac{163.3^2}{10} = 8kW$$

48. Ans: (C)

Sol: $f(A, B, C, D) = \sum m(1, 3, 4, 7, 9, 12, 14, 15)$

$$= \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + ABC\bar{D} + ABCD$$

$$= \bar{B}CD(A + \bar{A}) + \bar{B}CD\bar{A} + B\bar{C}\bar{D}(A + \bar{A}) + BCD(A + \bar{A}) + BC\bar{D}A \dots(1)$$

$$\begin{aligned} \text{The output of the multiplexer} &= m_0I_0 + m_1I_1 + m_2I_2 + m_3I_3 + m_4I_4 + m_5I_5 + m_6I_6 + m_7I_7 \\ &= \bar{B}\bar{C}\bar{D}I_0 + \bar{B}\bar{C}DI_1 + \bar{B}C\bar{D}I_2 + \bar{B}CDI_3 + B\bar{C}\bar{D}I_4 \\ &\quad + B\bar{C}DI_5 + BC\bar{D}I_6 + BCDI_7 \end{aligned} \dots\dots\dots(2)$$

$$(1) = (2)$$

$$\Rightarrow I_0 = 0, I_1 = 1, I_2 = 0, I_3 = \bar{A}, I_4 = 1, I_5 = 0, I_6 = A, I_7 = 1$$



49. Ans: (B)

Sol: All sheets will produce electric field at point P is $-Ve$ Z direction.

$$E_T = \left[\frac{\sigma}{2\epsilon_0} + \frac{2\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} \right] (-\hat{Z})$$

$$= \frac{4\sigma}{2\epsilon_0} (-\hat{Z}) = \frac{2\sigma}{\epsilon_0} (-\hat{Z})$$

50. Ans: 50 [Range 50]

Sol: Peak to peak value of unknown ac voltage.

V_{P-P} = length of trace \times deflection sensitivity

$$V_{P-P} = 10 \times 10 = 100V$$

$$\text{Peak value of the voltage} = \frac{V_{P-P}}{2} = 50\text{Volt}$$

51. Ans: (A)

Sol: $\frac{x(t)}{t} \leftrightarrow \int_s^\infty X(s) ds$

$$x(t) = \sin at \cdot u(t), X(s) = \frac{a}{s^2 + a^2}$$

$$\int_s^\infty X(s) ds = \int_s^\infty \frac{a}{s^2 + a^2} ds$$

$$= a \cdot \frac{1}{a} \tan^{-1}(s/a) \Big|_s^\infty$$

$$= \tan^{-1}(\infty) - \tan^{-1}(s/a)$$

$$= \frac{\pi}{2} - \tan^{-1}(s/a)$$

$$= \cot^{-1}(s/a)$$

$$= \tan^{-1}(a/s)$$


52. Ans: 90 [Range 90]

Sol: By using impedance transformation from output to input. The transformer are ideal (no power loss)

$$Z_{in} = \frac{Z_L}{k_1^2 k_2^2}$$

$$k_1 = \frac{20}{1} = 20, k_2 = \frac{1}{30}$$

$$Z_L = 10\Omega$$

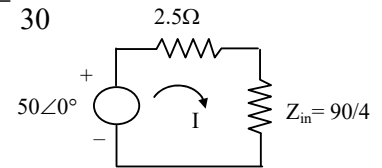

$$Z_{in} = \frac{10 \times 30 \times 30}{20 \times 20} = \frac{90}{4}$$

$$I = 2A$$

This current is transformed input to output

$$\text{then } I_L = \frac{I_{in}}{k_1^2 k_2^2} = \frac{2 \times 30}{20} = 3A$$

$$P_{\text{dissipated } '10\Omega'} = I^2 R = (3)^2 \times 10 = 90 \text{ W}$$

53. Ans: (3) [Range]

Sol: $(143)_5 = (x3)_y$

$$\Rightarrow 1 \times 5^2 + 4 \times 5 + 3 = xy + 3$$

$$\Rightarrow xy = 45$$

$$y > 3 \text{ and } y > x$$

Possible solutions are

$$x = 1, y = 45$$

$$x = 3, y = 15$$

$$x = 5, y = 9$$

54. Ans: (B)

Sol: For uniform distribution, $f(x) = \frac{1}{b-a}$

for $a < x < b$

$$\text{Here } f(x) = \frac{1}{0.5-0} = 2$$

$$E(x^4) = \int_0^{0.5} x^4 f(x) dx = 1/80$$



55. Ans: 980 (Range: 978 to 982)

Sol: Developed power,

$$P = \frac{735.5}{75} \times Q \times W \times H \times \eta \text{ Watts}$$

Here,

Discharge of water (Q) = $1\text{m}^3/\text{s}$,

Efficiency (η) = 100% and

Water head (H) = 1m

$$\therefore P = \frac{735.5}{75} \times 1000 \times 10 \times 10 = 980\text{kW}$$

