



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Offline GATE Mock -5 _ Solutions

General Aptitude (GA)

One Mark Solutions:

01. Ans: (B)

$$\text{Sol: } \sec \theta - \tan \theta = \frac{1}{\sqrt{3}}$$

$$\Rightarrow \frac{1-\sin \theta}{\cos \theta} = \frac{1}{\sqrt{3}}$$

$$\Rightarrow \sqrt{3} - \sqrt{3} \sin \theta = \cos \theta$$

$$\Rightarrow \theta = 30^\circ$$

$$\therefore \sec \theta \cdot \tan \theta = \frac{2}{\sqrt{3}} \times \frac{1}{\sqrt{3}} \\ = \frac{2}{3}$$

02. Ans: (B)

03. Ans: (B)

04. Ans: (C)

05. Ans: (D)

Sol: irretrievably means impossible to recover or get back, so irrevocably is the correct synonym, which means not capable of being changed : impossible to revoke.

Two Mark Solutions:

06. Ans: (C)

$$\text{Sol: P & Q one day work} = \frac{1}{6}$$

$$\text{Q & R one day work} = \frac{7}{60}$$

$$\text{Q & R work on 6 days} = \frac{7}{60} \times 6 = \frac{7}{10}$$

$$\therefore \text{P's work in 3 days} = \frac{3}{10}$$

$$\text{P's one day work} = \frac{1}{10}$$

$$\text{Q's one day work} = \frac{1}{6} - \frac{1}{10} = \frac{1}{15}$$

$$\text{R's one day work} = \frac{7}{60} - \frac{1}{15} = \frac{1}{20}$$

$$\therefore \text{R-P} = 20-10=10 \text{ days}$$

07. Ans: (B)

$$\text{Sol: Spent on library} = \frac{60}{360} \times 100 = 16.6\%$$

08. Ans: (B)

Sol: The pattern followed is

$$\begin{aligned} I &= (2 + 6 + 3 + 2)^2 - 1 = (13)^2 - 1 = 169 - 1 \\ &= 168 \end{aligned}$$

$$\begin{aligned} II &= (5 + 1 + 2 + 3)^2 - 1 = (11)^2 - 1 = 121 - 1 \\ &= 120 \end{aligned}$$



$$\text{III} = (5 + 4 + 2 + 3)^2 - 1 = (14)^2 - 1 = 196 - 1 = 195$$

09. Ans: (D)

Sol: 15 men can complete total work $= 7 \times 3 = 21$ days

$$M_1 D_1 = M_2 D_2$$

$$\Rightarrow 15 \times 21 = 5 \times M_2$$

$$\Rightarrow M_2 = 63$$

10. Ans: (B)

Sol: Total students $= 20 + 30 = 50$

$$\begin{aligned}\text{Total pass students} &= (20 \times 0.8) + (30 \times 0.6) \\ &= 16 + 18 \\ &= 34\end{aligned}$$

$$\therefore \text{Pass percentage} = \frac{34}{50} = 68\%$$

10. Ans: (B)

Specific Section (EE)


One mark Solutions:

01. Ans: (A)

Sol: Consider the equivalent two port network

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

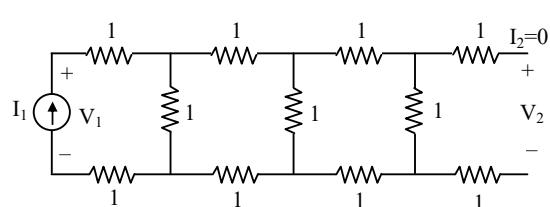

$$Z_{11} = \frac{V_1}{I_1} = [(3 \parallel 1) + 2] \parallel 1 + 2 = 2.73 \Omega$$

02. Ans: (B)

03. Ans: (A)

Sol: Maximum value of restriking voltage
 $= 2 \times \text{peak value of the system voltage}$
 $= 2 \times \frac{17.32}{\sqrt{3}} \times \sqrt{2} = 28.28 \text{ kV}$

04. Ans : (A)

$$\text{Sol: } f(z) = \frac{1}{(z+2)^2 (z-2)^2}$$

$z = 2$ is a pole of $f(z)$ of order 2

Res $(f(z) : z = z_0)$

$$= \frac{1}{(m-1)!} \left[\underset{z \rightarrow z_0}{\text{Lt}} \frac{d^{m-1}}{dz^{m-1}} ((z-z_0)^m f(z)) \right]$$

Res $(f(z) : z = 2)$

$$= \frac{1}{(2-1)!} \left[\underset{z \rightarrow 2}{\text{Lt}} \frac{d^{2-1}}{dz^{2-1}} \left((z-2)^2 \frac{1}{(z+2)^2 (z-2)^2} \right) \right]$$

$$= \underset{z \rightarrow 2}{\text{Lt}} \left[\frac{(-2)}{(z+2)^3} \right] = -\frac{1}{32}$$

05. Ans: (A)

06. Ans: 1 [Range : 1]

Sol: $\vec{E} = -\nabla \cdot V$,

$$\vec{E} = -[y(2x+z)\hat{x} + x(x+z)\hat{y} + xy\hat{z}] \text{ V/m}$$

$$\vec{E}_{(0,1,1)} = -\hat{x}$$

$$|\vec{E}| = 1$$



07. Ans: 1.14 Ω [Range 1.1 to 1.2]

Sol: $E_{b1} = V - I_a R_a = 240 - 40 (0.3) = 228 \text{ V}$

$$\frac{E_{b2}}{E_{b1}} = \frac{N_2}{N_1}$$

$$\Rightarrow E_{b2} = \frac{1200}{1500} \times 228 \\ = 182.4 \text{ V}$$


Now $E_{b2} = V - I_a (R_a + R_{se}) = 182.4 \text{ V}$

$$\Rightarrow 240 - 40 (0.3 + R_{se}) = 182.4$$

$$\Rightarrow R_{se} = 1.14 \Omega$$

08. Ans: (C)

Sol: Let name the nodes of the figure

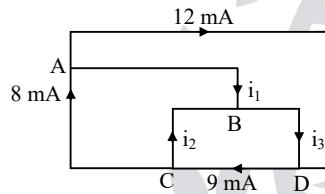

KCL at node A

$$8 = 12 + i_1 \Rightarrow i_1 = -4 \text{ mA}$$

KCL at Node D

$$12 \text{ mA} + i_3 = 9 \text{ mA}$$

$$i_3 = -3 \text{ mA}$$

KCL at Node B

$$i_1 + i_2 = i_3$$

$$i_2 = i_3 - i_1 = -3 \text{ mA} + 4 \text{ mA}$$

$$= 1 \text{ mA}$$

$$i_1 + i_2 + i_3 = -4 + 1 - 3$$

$$= -7 + 1 = -6 \text{ mA}$$

09. Ans: (D)

$$\text{Sol: } \frac{C(s)}{R(s)} = \frac{10}{(s-1)(s+2)}$$

For unit step input

$$R(s) = \frac{1}{s}$$

$$\Rightarrow C(s) = \frac{10}{s(s-1)(s+2)}$$

By applying initial value theorem

$$c(0) = \lim_{s \rightarrow \infty} s C(s)$$

$$= \lim_{s \rightarrow \infty} \frac{10}{(s-1)(s+2)} = 0$$

$$c(0) = 0$$

Final value theorem cannot be applied since poles are in the right half of s-plane. Output is unbounded

$$\therefore c(\infty) = \infty$$

10. Ans: 132 (Range: 130 to 134)

Sol: Full load Cu loss = $I_{fl}^2 R_{eq} = 80 \text{ W}$

We want to know rated load (nothing but rated current I) at which a short circuit test can be regarded as an economic heat run test.

$$\begin{aligned} \text{In heat run test, losses} &= \text{Iron loss} + F_1 \text{ cu loss} \\ &= 80 + 60 = 140 \text{ W} \end{aligned}$$

Let us calculate rated current (load) at which these losses will take place.

$$\text{Copper losses} \propto I^2$$

$$\frac{I}{I_{fl}} = \sqrt{\frac{140}{80}} = 1.32 \times 100 = 132 \%$$

11. Ans: (C)

Sol: The given Newton's iterative formula is

$$x_{n+1} = \frac{1}{2} \left(x_n + \frac{R}{x_n} \right)$$



Let us suppose the formula converges to the root after n iterations

Then $x_n = x_{n+1} = x$ (root)

$$\text{The formula becomes } x = \frac{1}{2} \left(x + \frac{R}{x} \right)$$

$$\therefore x = \sqrt{R}$$

12. Ans: 5.49 (Range: 5.3 to 5.6)

Sol: Given that

$$I_E = 1 \text{ mA}$$

$$\text{Then } I_B = \frac{I_E}{1 + \beta} = 10 \mu\text{A}$$

$$I_C = \beta I_B = 0.99 \text{ mA}$$

$$V_B = -50 \times 10^3 I_B = -0.5 \text{ V}$$

$$V_B - V_E = 0.7$$

$$\Rightarrow V_E = V_B - 0.7$$

$$= -1.2 \text{ V}$$

$$V_C = 9 - 4.7 \times 10^3 I_C \\ = 9 - 4.7(0.99)$$

$$V_C = 4.347 \text{ V}$$

$$\text{Then } V_{CE} = V_C - V_E = 5.547 \text{ V}$$

The power dissipation in transistor is

$$P_D = V_{CE} \times I_C \\ = 5.547 \times 0.99 \times 10^{-3} \\ = 5.49 \text{ mW}$$

13. Ans: (A)

$$\text{Sol: Nodal } \Rightarrow -5 + \frac{V_1}{4} + \frac{V_1}{4} + 2I = 0$$

$$\Rightarrow -5 + \frac{2V_1}{4} + 2 \times \frac{V_1}{4} + = 0$$

$$\Rightarrow V_1 = 5 \text{ V}$$

$$\text{BY KVL } \Rightarrow V_2 - 20 - 5 = 0 \Rightarrow V_2 = 25 \text{ V}$$

14 Ans: (A)

Sol: To eliminate any harmonic from the output waveform, the amplitude of the waveform should be equal to zero. For that value of n . By referring Fourier analysis expression,

$$\sin nd = 0$$

$$\therefore nd = \pi \Rightarrow d = \frac{\pi}{n}$$

$$\text{Width of pulse } (\alpha) = 2d = \frac{2\pi}{n} = \frac{2\pi}{5} = 72^\circ$$

15. Ans: (A)

$$\text{Sol: } \phi(x) = \int_0^{x^2} \sqrt{t} dt = \frac{2}{3} x^3 \\ \Rightarrow \frac{d\phi}{dx} = 2x^2$$

16. Ans: (C)

$$\text{Sol: } \int_0^1 x \log x \, dx = \log x \cdot \frac{x^2}{2} - \int \frac{x^2}{2} \cdot \frac{1}{x} dx \\ = \left[\frac{x^2}{2} \log x - \frac{x^2}{4} \right]_0^1 \\ = \left(0 - \frac{1}{4} \right) - \lim_{x \rightarrow 0} \left[\frac{x^2 \log x}{2} \right] - 0 \\ = \frac{-1}{4}$$

17. Ans : (D)

$$\text{Sol: Given } \frac{dy}{dx} + \frac{y}{x} = x \quad \dots \dots \quad (1) \quad \text{and}$$

$$y = 1 \text{ at } x = 1 \quad \dots \dots \quad (2)$$

$$\text{I.F} = e^{\int \frac{1}{x} dx} = e^{\log x} = x$$

The general solution of (1) is



$$xy = \frac{x^3}{3} + C \quad \dots \dots (3)$$


Using (2), (3) becomes

$$1 = \frac{1}{3} + C \Rightarrow C = 2/3$$

$$\therefore y = \frac{x^2}{3} + \frac{2}{3x}$$

18. Ans: 1 (No Range)

Sol:

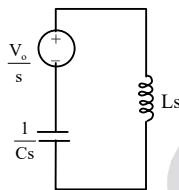

Applying KVL in s-domain,

$$I(s) = \frac{V_o/s}{\frac{1}{C_s} + Ls}$$

$$= \frac{V_o C}{L C s^2 + 1}$$

$$\Rightarrow i(t) = V_o \sqrt{\frac{C}{L}} \sin \frac{1}{\sqrt{LC}} t$$

$$\Rightarrow i(\max) = V_o \sqrt{\frac{C}{L}}$$

$$= 10 \sqrt{\frac{10^{-6}}{0.1 \times 10^{-3}}} = 1A$$

19. Ans: (C)

Sol $E = \{(1,2), (1,3), (1,4), (1,5), (1,6), (2,3), (2,4), (2,5), (2,6), (3,4), (3,5), (3,6), (4,5), (4,6), (5,6)\}$

$$n(E) = 15, \quad n(S) = 36$$

$$\text{Required probability} = \frac{n(E)}{n(S)} = \frac{15}{36} = \frac{5}{12}$$

20. Ans: 0.396 (Range: 0.35 to 0.45)

$$\text{Sol: } X = X_{(\text{pu})(\text{old})} \times \frac{\text{MVA}_{\text{new}}}{\text{MVA}_{\text{old}}} \left(\frac{kV_{\text{old}}}{kV_{\text{new}}} \right)^2$$

$$= 0.6 \times \frac{80}{100} \left(\frac{10}{11} \right)^2$$


$$= 0.6 \times \frac{4}{5} \left(\frac{10}{11} \right)^2$$

$$= 0.396$$

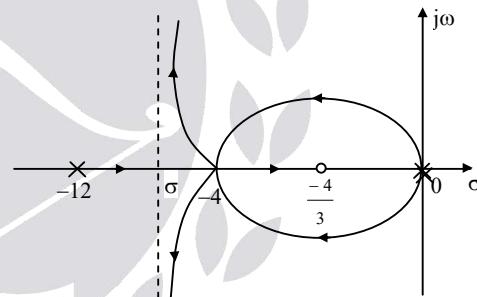21. Ans: 48 [Range 48]

Sol: Since the roots are equal at the point. Therefore the point must be a break point.

\therefore At the break point $\frac{dk}{ds} = 0$



$$\Rightarrow \frac{d}{ds} \left[\frac{s^3 + 12s^2}{s + 4/3} \right] = 0$$

$$\Rightarrow s = 0, -4$$

The root locus for the given transfer function is

At $s = -4$, the three root locus branches meet and the three roots are equal

At $s = -4$,

$$k = \frac{4 \times 4 \times 8}{8/3} = 48$$

$$\therefore k = 48$$



22. Ans: (B)

Sol: $-X = \bar{X} + 1$ in 2's complement form

$$\text{MVI A}, X ; \quad (A) = X$$

$$\text{CMA} ; \quad (A) = \bar{X}$$

$$\text{ADI 01H} ; \quad (A) = \bar{X} + 1$$

23. Ans: (A)

Sol: given $I = 100 \pm 2 \text{ A} = 100 \pm 2\%$

$$R = 100 \pm 1 \Omega = 100 \pm 1\%$$

we know that

$$P = I^2 R$$

Limiting error will be $\Rightarrow 2 \times 2 + 1 = 5\%$

24. Ans: (C)

Sol: Pick up value = Operating current \times current setting

$$= 8 \times 0.15 = 1.2 \text{ A}$$


25. Ans: (D)

Two Marks Solutions:

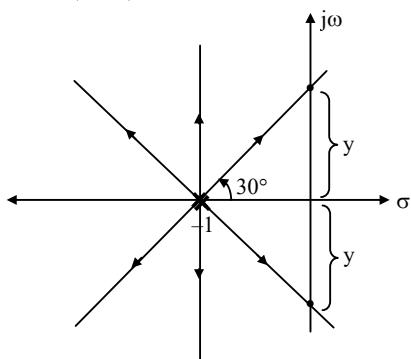26. Ans: (A)

Sol: Method-I: The root locus for the given open loop transfer function

$$G(s) = \frac{k}{(s+1)^6} \text{ is as shown below}$$



In this case asymptotes become the root locus branches. When 'k' is increased two of the root locus branches move towards $j\omega$ axis And these two root locus branches cut the $j\omega$ axis at the point which is obtained as follows

$$\tan 30^\circ = \frac{y}{1} \Rightarrow y = \frac{1}{\sqrt{3}}$$

$$\therefore \text{Root locus cuts the } j\omega \text{ axis at } s = \pm \frac{j}{\sqrt{3}}$$

$$\text{At } s = \frac{j}{\sqrt{3}}, k = \left(\sqrt{1 + \frac{1}{3}} \right)^6$$

$$= \left(\frac{2}{\sqrt{3}} \right)^6 = \frac{64}{27}$$

$$\therefore \text{For stability } 0 < k < \frac{64}{27}$$

Method-II

For marginal stability gain margin = 1

Phase margin = 0

$$\text{Gain margin} = \frac{1}{|G(s)H(s)|_{\omega=\omega_{pc}}}$$

$$\text{At } \omega = \omega_{pc} \angle G(s)H(s) = -180^\circ$$

$$\Rightarrow -6 \tan^{-1}(\omega_{pc}) = -180^\circ \Rightarrow \omega_{pc} = \frac{1}{\sqrt{3}}$$

And gain margin = 1

$$\Rightarrow \frac{k}{\left(\sqrt{1 + \left(\frac{1}{\sqrt{3}} \right)^2} \right)^6} = 1$$

$$\Rightarrow k = \left(\frac{2}{\sqrt{3}} \right)^6 = \frac{64}{27}$$

$$\therefore 0 < k < \frac{64}{27}$$



27. Ans: (A)

Sol: $\bar{F} = q\bar{V} \times \bar{B} = qV_0 \hat{x} \times B_0 \hat{z} = ma$

$$s = ut + \frac{1}{2}at^2$$


$$s = V_0 \hat{x}t + \frac{1}{2} \left(\frac{qv_0 \hat{x}}{m} \right) (-\hat{y})$$

28. Ans: (D)

Sol: Transmission line base voltages = $11 \times \frac{121}{10.8} = 123.2 \text{ kV}$

Motor voltage in base $123.2 \times \frac{10.8}{121} = 11 \text{ kV}$

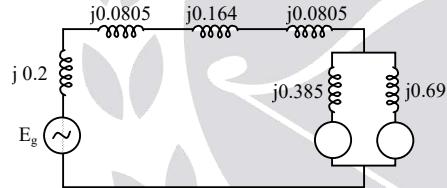Transformer = $0.1 \times \frac{25}{30} \times \left(\frac{10.8}{11} \right)^2 = 0.0805$



Line reactance = $\frac{100 \times 25}{(123.2)^2} = 0.164 \text{ pu}$

Motor 1 = $0.28 \times \frac{25}{15} \left(\frac{10}{11} \right)^2 = 0.385 \text{ pu}$

Motor 2 = $0.25 \times \frac{25}{75} \times \left(\frac{10}{11} \right)^2 = 0.069 \text{ pu}$

29. Ans: 0.5 [Range 0.5]

Sol: $H_1(Z) = \frac{Z}{Z-\alpha}, \quad H_2(Z) = \frac{Z}{Z+\alpha}$

$$H_C(Z) = H_1(Z) H_2(Z) = \frac{Z}{Z^2 - \alpha^2}$$

$$H_P(Z) = H_1(Z) + H_2(Z) = \frac{Z}{Z-\alpha} + \frac{Z}{Z+\alpha} =$$

$$\frac{2Z^2}{Z^2 - \alpha^2}$$

$$H_P(Z) = 2H_C(Z)$$

$$H_C(z) = 0.5H_P(z).$$

30. Ans: 14.414 [Range 13.5 to 15]

Sol: Let V_s is rms value of input voltage, I is current in the load under fully discharged condition

for diode bridge rectifier,

$$\text{The average output } V_0 = \frac{2V_m}{\pi} = \frac{2\sqrt{2}V_s}{\pi}$$

$$I_0 = \frac{V_0 - E}{R}$$

$$E = V_0 - I_0 R \dots\dots\dots(1)$$

Substitute the given values in the equation (1)

Under fully discharge condition

$$10.2 = \frac{2\sqrt{2}V_s}{\pi} - I_0 R \dots\dots\dots(2)$$

Under fully charge condition

$$12.7 = \frac{2\sqrt{2}V_s}{\pi} - (I \times 0.1) \times 0.1 \dots\dots\dots(3)$$

Solve (2) & (3)

$$2.5 = 0.09I$$

$$I = \frac{2.5}{0.09} = 27.78 \text{ A}$$

$$V_0 = E + IR$$

$$= 10.2 + 27.78 \times 0.1$$

$$= 12.98 \text{ V}$$

$$\text{For full bridge rectifier } V_0 = \frac{2V_m}{\pi}$$

$$V_s = \frac{12.98 \times \pi}{2\sqrt{2}} = 14.414 \text{ V}$$



31. Ans: (A)

$$\text{Sol: From the Bode plot, } G(s) = \frac{K \left(1 + \frac{s}{1}\right)}{s \left(1 + \frac{s}{100}\right)}$$

$$\theta(\omega) = \angle G(j\omega)$$

$$= -90^\circ + \tan^{-1}(\omega) - \tan^{-1}\left(\frac{\omega}{100}\right)$$

$\theta(\omega)$ is absolute minimum at

$$\omega = \sqrt{(1)(100)} = 10 \text{ rad/sec}$$

\therefore Minimum phase angle

$$= -90^\circ + 84.3^\circ - 5.7^\circ$$

$$= -11.4^\circ$$

32. Ans: 27% [Range 27]

Sol: $I_{st} = 3 I_{full}$ and $S_f = 0.03$

$$\frac{\tau_{st}}{\tau_{full}} = \left(\frac{I_{st}}{I_{full}} \right)^2 S_f$$

$$= \left(\frac{3I_{full}}{I_{full}} \right)^2 \times 0.03$$

$$= 0.27$$

In percentage is 27%

33. Ans: (A)

Sol: Let X = Number of tosses required for head
(or) four tails


| X | H | TH | TTH | (TTTH) or (TTTT) |
|------|---------------|---------------|---------------|------------------|
| P(x) | $\frac{1}{2}$ | $\frac{1}{4}$ | $\frac{1}{8}$ | $\frac{1}{8}$ |

$$E(X) = 1 \times \frac{1}{2} + 2 \times \frac{1}{4} + 3 \times \frac{1}{8} + 4 \times \frac{1}{8} = \frac{15}{8}$$

34. Ans: (C)

Sol: The nyquist plot of $G(s)H(s) = \frac{(s-2)}{(s+1)^2}$ is as

shown below

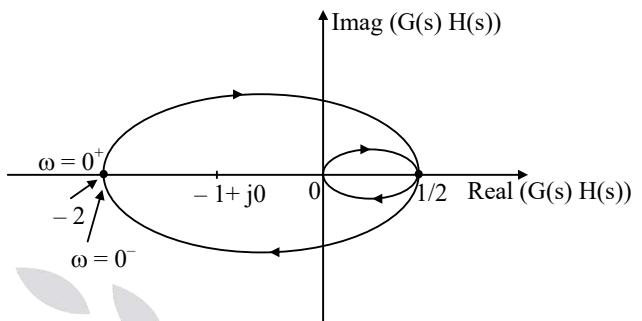

Number of anticlockwise encirclements about origin = $(P - Z)_{OLTF}$

Where 'P' and 'Z' are the number of right side poles and number of right side zeros of openloop transfer function.

$$\therefore N_{(0,0)} = 0 - 1 = -1$$

\therefore It will encircle the origin once in clockwise direction

To find anticlockwise encirclements about $(-1+j0)$, $N = P - Z$

Where, P = number of right side poles of OLTF

Z = number of right side poles of CLTF

The characteristic equation is

$$1 + G(s) H(s) = 0$$

$$\Rightarrow 1 + \frac{(s-2)}{(s+1)^2} = 0$$

$$\Rightarrow s^2 + 2s + 1 + s - 2 = 0$$

$$\Rightarrow s^2 + 3s - 1 = 0$$

$$\Rightarrow s = 0.302, -3.302$$

$$\therefore Z = 1$$

$$\therefore N_{(-1,0)} = 0 - 1 = -1$$



∴ It will encircle $(-1, 0)$ once in clockwise direction

(or)

From the figure we can directly say that number of encirclements.

35. Ans: 13.982 [Range: 13 to 14]

Sol: Given data, $V_t = 300 - 0.5 I_L$, $P_0 = 6 \text{ kW}$

$$P_0 = V_t I_L$$

$$6 \times 10^3 = (300 - 0.5 I_L) I_L$$

$$0.5 I_L^2 - 300 I_L + 6 \times 10^3 = 0$$

$$I_L = \frac{300 \pm \sqrt{9 \times 10^4 - 12 \times 10^3}}{1}$$

$$= 300 \pm 279.28$$

= 579.28 and 20715 A for a load

6 kW, 20.7156 A is suitable load current

$$I_L^2 R_L = 6000$$

$$\Rightarrow R_L = 13.982 \Omega$$

36. Ans: (D)


37. Ans: 1.86 (Range: 1.8 to 1.9)

Sol: The given circuit can be redrawn as

$$V_B = 0$$

$$V_E = -0.7 \text{ V}$$
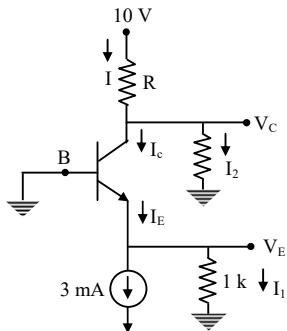
$$I_1 = \frac{V_E}{1k} = -0.7 \text{ mA}$$



$$I_E = I_1 + 3 \text{ mA}$$

$$I_E = 2.3 \text{ mA}$$

$$I_E \approx I_C = 2.3 \text{ mA}$$

$$\text{Given } V_{CE} = 2.7 \text{ V}$$

$$V_C - V_E = 2.7$$

$$V_C = V_E + 2.7$$

$$V_C = 2 \text{ V} \text{ then } I_2 = \frac{V_C}{1k} = 2 \text{ mA}$$

$$\Rightarrow I = I_C + I_2$$

$$I = 4.3 \text{ mA} = \left(\frac{10 - V_C}{R} \right)$$

$$R = \frac{10 - 2}{4.3 \times 10^{-3}} = 1.86 \text{ k}\Omega$$

38. Ans: (C)

Sol: electrical input = $P_{\text{mech.output}} + \text{friction Loss} + \text{core Loss}$

$$= 9 \text{ kW} + 2 \text{ kW} + 0.8 \text{ kW}$$

$$P_{\text{in}} = 11.8 \text{ kW}$$

$$\sqrt{3} V_L I_L \cos \phi = 11800$$

$$\Rightarrow \sqrt{3} \times 400 \times I_L \times 0.8 = 11800 \Rightarrow I_L = 21.29 \text{ A}$$

39. Ans: (B)

Sol: $V_{dc} = 6 \text{ V}$, $V_0 = 15 \text{ V}$

$$V_0 = \frac{V_{dc}}{1-D}$$

$$1-D = \frac{V_{dc}}{V_0}$$

$$D = 1 - \frac{V_{dc}}{V_0}$$

$$= 1 - \frac{6}{15}$$

$$= 0.6$$



$$R_{cr} = \frac{2L}{D(1-D)^2 T}$$

$$= \frac{2 \times 250 \times 10^{-6}}{0.6(1-0.6)^2 \times (1/20 \times 10^3)}$$

$$= 104.17 \Omega$$

40. Ans : (A)

Sol: Given $A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$

$\Rightarrow |A| = 1 \neq 0$ and

$$\text{adj}(A) = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$


$$\therefore A^{-1} = \frac{\text{adj}(A)}{|A|} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

41. Ans: (C)

Sol:




It can be redrawn as follows

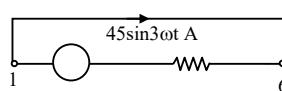

$$300[\sin\omega t + \sin(\omega t - 120^\circ) + \sin(\omega t + 120^\circ)] + 135\sin 3\omega t = 135\sin 3\omega t + V$$

It is seen that the current in the delta loop is $45\sin 3\omega t$ A, flowing from terminal 1 to 6 through resistance.

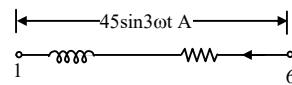Now consider only the winding between terminals 1 and 2



The voltage across terminals 1 and 2 is $300 \sin\omega t$

42. Ans: (C)

Sol: $SI - A = \begin{bmatrix} s & -1 \\ 0 & s+3 \end{bmatrix}$

$$(SI - A)^{-1} = \begin{bmatrix} \frac{1}{s} & \frac{1}{s(s+3)} \\ 0 & \frac{s+3}{s} \end{bmatrix}$$

$$e^{At} = L^{-1}[(SI - A)^{-1}] = \begin{bmatrix} 1 & \frac{1}{3}(1 - e^{-3t}) \\ 0 & e^{-3t} \end{bmatrix}$$

$$x(t) = e^{At}x(0) + \int_0^t e^{A(t-\tau)}BU(\tau)d\tau$$

$U(\tau)$ = unit step input

$$x(t) = \begin{bmatrix} 1 & \frac{1}{3}(1 - e^{-3t}) \\ 0 & e^{-3t} \end{bmatrix} \begin{bmatrix} -1 \\ 3 \end{bmatrix} + \int_0^t \begin{bmatrix} 1 & \frac{1}{3}(1 - e^{-3(t-\tau)}) \\ 0 & e^{-3(t-\tau)} \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} (1)d\tau$$

$$= \begin{bmatrix} -e^{-3t} \\ 3e^{-3t} \end{bmatrix} + \int_0^t \begin{bmatrix} 1 \\ 0 \end{bmatrix} d\tau$$

$$= \begin{bmatrix} -e^{-3t} \\ 3e^{-3t} \end{bmatrix} + \begin{bmatrix} t \\ 0 \end{bmatrix}$$

$$x(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} t - e^{-3t} \\ 3e^{-3t} \end{bmatrix}$$


43. Ans: 1.722 [Range: 1.6 to 1.8]

Sol: $X_S = 0.96 \text{ pu}$

$$X_{T1} = X_{T2} = 0.286 \text{ pu},$$

$$X_{L1} = X_{L2} = 0.38 \text{ pu}$$
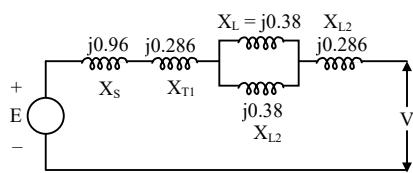
$$E = 1.2 \text{ pu} \quad V = 1.0 \text{ pu}$$



$$X_T = j0.96 + j0.286 + j(0.38 \parallel 0.38) + j0.286 \\ = 1.722 \text{ pu}$$

$$P_0 = \frac{EV}{X} \sin \delta$$

$$P_0 = 1 \text{ pu}$$

Minimum value $\sin \delta = 1$

$$E_{\min} = \frac{PX}{V}$$


$$E_{\min} = \frac{1 \times 1.722}{1} = 1.722 \text{ pu}$$

44. Ans: (B)

Sol: Given that $\beta = 100$

To calculate ' r_e ' value, apply DC Analysis

Apply KVL to input loop

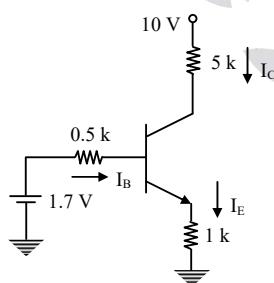


$$1.7 - 0.5 \times 10^3 I_B - 0.7 - 10^3(1+\beta)I_B = 0$$

$$I_B = \frac{1}{10^3(0.5+101)} = 9.852 \mu\text{A}$$

$$I_E = (1+\beta) I_B = 0.995 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = 25.12 \Omega$$

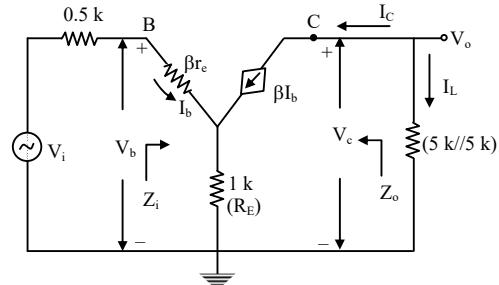To calculate voltage gain apply AC Analysis
Voltage gain



$$A_v = \left(\frac{V_o}{V_b} \right) = \frac{-I_c(2.5k)}{I_b[\beta r_e + (1+\beta)R_E]}$$

$$A_v = \frac{-\beta \times 2.5 \times 10^3}{\beta r_e + (1+\beta)R_E} = \frac{-100 \times 2.5 \times 10^3}{(2.512 + 101) \times 10^3} \\ = \frac{-250}{103.512} \\ = -2.415$$

$$\text{Voltage amplification } A = A_v \left(\frac{Z_i^1}{Z_i^1 + R_s} \right)$$

$$\text{Where } Z_i^1 = Z_i = \beta r_e + (1+\beta) R_E \\ = 103.512 \text{ k}\Omega$$

$$A = -2.415 \left(\frac{103.512}{104.012} \right) \\ = -2.4034$$

$$\therefore A = -2.4$$

45. Ans: (B)

Sol: Given $\cos \theta = 0.8$

$$\theta = \cos^{-1} 0.8 = 36.86^\circ$$

$$P_1 = V_L I_L \cos (30 - 36.86)$$

$$P_2 = V_L I_L \cos (30 + 36.86)$$

$$P_1 = 208 \times 12 \cos (30 - 36.86)$$




$$P_1 = 2478 \text{ W}$$

$$P_2 = 208 \times 12 \cos (30 + 36.86) \Rightarrow P_2 = 980 \text{ W}$$



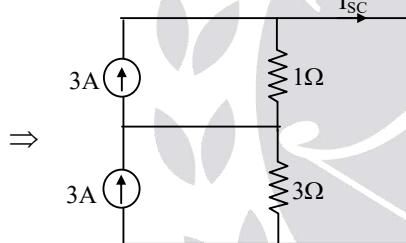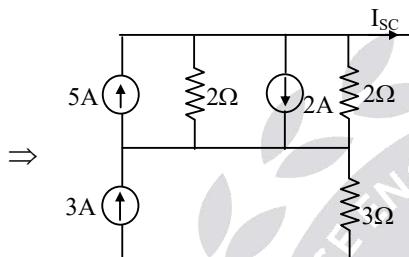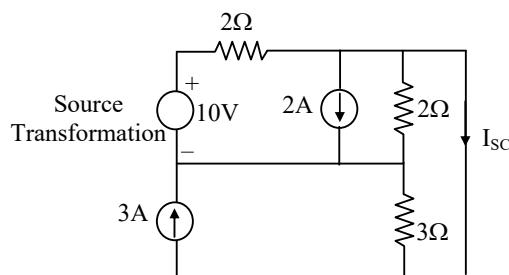46. Ans: 3 [Range 3]



Sol: Find out short circuit current (I_{SC})



$$\therefore I_{SC} = 3A$$

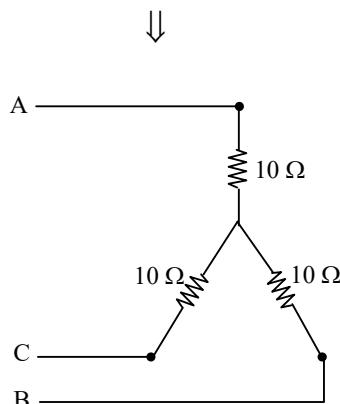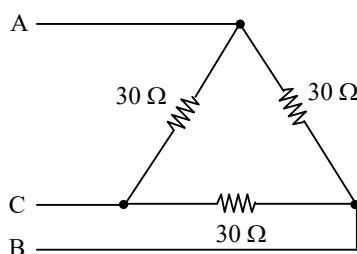47. Ans: (B)

Sol: Convert delta connected load into star connected load.



\therefore In 120° conduction scheme,

$$V_{ph} = \frac{V_{dc}}{\sqrt{6}} = 163.3 \text{ V}$$

3-φ load power

$$P_0 = 3 \left[\frac{V^2}{R} \right] = 3 \times \frac{163.3^2}{10} = 8 \text{ kW}$$

48. Ans: (C)

Sol: $f(A, B, C, D) = \Sigma m(1, 3, 4, 7, 9, 12, 14, 15)$

$$= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + AB\bar{C}\bar{D} + ABC\bar{D} + ABCD$$

$$= \bar{B}\bar{C}\bar{D}(A + \bar{A}) + \bar{B}CD\bar{A} + B\bar{C}\bar{D}(A + \bar{A}) + BCD(A + \bar{A}) + BC\bar{D}A$$

$$= \bar{B}\bar{C}\bar{D} + \bar{B}CD\bar{A} + B\bar{C}\bar{D} + BCD + BC\bar{D}A \dots\dots\dots(1)$$

$$\begin{aligned} \text{The output of the multiplexer} &= m_0I_0 + m_1I_1 \\ &+ m_2I_2 + m_3I_3 + m_4I_4 + m_5I_5 + m_6I_6 + m_7I_7 \\ &= \bar{B}\bar{C}\bar{D}I_0 + \bar{B}\bar{C}DI_1 + \bar{B}C\bar{D}I_2 + \bar{B}CDI_3 + B\bar{C}\bar{D}I_4 \\ &\quad + B\bar{C}DI_5 + BC\bar{D}I_6 + BCDI_7 \\ &\dots\dots\dots(2) \end{aligned}$$

$$(1) = (2)$$

$$\Rightarrow I_0 = 0, I_1 = 1, I_2 = 0, I_3 = \bar{A}, I_4 = 1, I_5 = 0, I_6 = A, I_7 = 1$$



49. Ans: (B)

Sol: All sheets will produce electric field at point P is -Ve Z direction.

$$\begin{aligned} E_T &= \left[\frac{\sigma}{2\epsilon_0} + \frac{2\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} \right] (-\hat{Z}) \\ &= \frac{4\sigma}{2\epsilon_0} (-\hat{Z}) = \frac{2\sigma}{\epsilon_0} (-\hat{Z}) \end{aligned}$$

50. Ans: 50 [Range 50]

Sol: Peak to peak value of unknown ac voltage.

$V_{P-P} = \text{length of trace} \times \text{deflection sensitivity}$

$$V_{P-P} = 10 \times 10 = 100V$$

$$\text{Peak value of the voltage} = \frac{V_{P-P}}{2} = 50 \text{ Volt}$$

51. Ans: (A)

$$\text{Sol: } \frac{x(t)}{t} \leftrightarrow \int_s^{\infty} X(s) ds$$

$$x(t) = \sin at, u(t), X(s) = \frac{a}{s^2 + a^2}$$

$$\int_s^{\infty} X(s) ds = \int_s^{\infty} \frac{a}{s^2 + a^2} ds$$

$$= a \cdot \frac{1}{a} \tan^{-1}(s/a) \Big|_s^{\infty}$$

$$= \tan^{-1}(\infty) - \tan^{-1}(s/a)$$

$$= \frac{\pi}{2} - \tan^{-1}(s/a)$$

$$= \cot^{-1}(s/a)$$

$$= \tan^{-1}(a/s)$$


52. Ans: 90 [Range 90]

Sol: By using impedance transformation from output to input. The transformer are ideal (no power loss)

$$Z_{in} = \frac{Z_L}{k_1^2 k_2^2}$$

$$k_1 = \frac{20}{1} = 20, k_2 = \frac{1}{30}$$

$$Z_L = 10\Omega$$

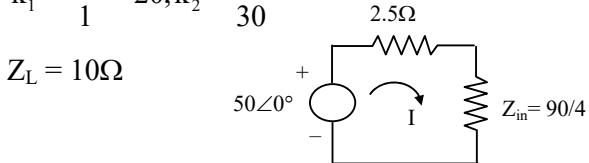

$$Z_{in} = \frac{10 \times 30 \times 30}{20 \times 20} = \frac{90}{4}$$

$$I = 2A$$

This current is transformed input to output

$$\text{then } I_L = \frac{I_{in}}{k_1^2 k_2^2} = \frac{2 \times 30}{20} = 3A$$

$$P_{dissipated \ 10\Omega} = I^2 R = (3)^2 \times 10 = 90 \text{ W}$$

53. Ans: (3) [Range]

$$\text{Sol: } (143)_5 = (x3)_y$$

$$\Rightarrow 1 \times 5^2 + 4 \times 5 + 3 = xy + 3$$

$$\Rightarrow xy = 45$$

$$y > 3 \text{ and } y > x$$

Possible solutions are

$$x = 1, y = 45$$

$$x = 3, y = 15$$

$$x = 5, y = 9$$

54. Ans: (B)

Sol: For uniform distribution, $f(x) = \frac{1}{b-a}$

for $a < x < b$

$$\text{Here } f(x) = \frac{1}{0.5 - 0} = 2$$

$$E(x^4) = \int_0^{0.5} x^4 f(x) dx = 1/80$$



55. Ans: 980 (Range: 978 to 982)

Sol: Developed power,

$$P = \frac{735.5}{75} \times Q \times W \times H \times \eta \text{ Watts}$$

Here,

Discharge of water (Q) = $1\text{m}^3/\text{s}$,

Efficiency (η) = 100% and

Water head (H) = 1m

$$\therefore P = \frac{735.5}{75} \times 1000 \times 10 \times 10 = 980\text{kW}$$

