



# ACE

## Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

### Offline GATE Mock -6 \_ Solutions

#### General Aptitude (GA)

##### One Mark Solutions:

01. Ans: (A)

02. Ans: (C)

03. Ans: (D)

**Sol:** Though most people disregarded or made fun of her book, some appreciated it.

04. Ans: (B)

05. Ans: (D)

**Sol:** The sequence is a combination of two series;

(I): 19, 38, 114, (----) and (II): 2, 3, 4

The pattern followed in (I) is  $\times 2, \times 3, \dots$

$\therefore$  Missing number =  $114 \times 4 = 456$

06. Ans: (B)

**Sol:**  $\log_{10} 5 + \log_{10}(5x+1) = \log_{10}(x+5) + 1$

$$\log_{10} 5 + \log_{10}(5x+1) = \log_{10}(x+5) + \log_{10} 10$$

$$\log_{10}(5(5x+1)) = \log_{10}(10(x+5))$$

$$5(5x+1) = 10(x+5)$$

$$25x+5 = 10x+50$$

$$15x = 45$$

$$x = 3$$

07. Ans: (A)

**Sol:**  $LCM = 44 HCF \Rightarrow 1 = 44H$

$$LCM + HCF = 1125 \Rightarrow 44H + H = 1125$$

$$45H = 1125$$

$$\therefore L = 44 \times 25$$

$$= 1100$$

$$a \times b = L \times H$$

$$25 \times b = 1100 \times 25$$

$$b = 1100$$

08. Ans: (C)

**Sol:** Both friends are coming to meet each other

Distance travelled by them on first day

$$= 20 + 10 = 30\text{km}$$

Distance travelled by them on 2<sup>nd</sup> day

$$= 19 + 12 = 31\text{km}$$

Distance travelled by them on third day

$$= 18 + 14 = 32\text{km}$$

So, he distances travelled by them for ms an A.P, with first term (A) = 30 and common difference (D) = 1

Let they meet after n days, then

$$S_n = \frac{n}{2} [2a + (n-1)d]$$



$$385 = \frac{n}{2} [2 \times 30 + (n-1) \times 1]$$

$$385 = \frac{n}{2} [60 + (n-1)]$$

$$770 = n(59+n)$$

$$n^2 + 59n - 770 = 0$$

$$n^2 + 70n - 11n - 770 = 0$$

$$n(n+70) - 11(n+70) = 0$$

$$(n-11)(n+70) = 0$$

But  $n \neq -70$

Hence, they will meet after 11 days.

#### 09. Ans: (D)

**Sol:** The total monthly budget of an average household

$$= 4000 + 1200 + 2000 + 1500 + 1800$$

$$= \text{Rs. } 10500$$

Percentage of the monthly budget spent on savings

$$= \frac{\text{savings amount}}{\text{Total expenses}}$$

$$= \frac{1500}{10500} \times 100 = 14.285\%$$

∴ The approximate percentage of the

$$= 100 - 14.285 = 85.714 \approx 86\%$$

monthly budget NOT spent on savings

#### 10. Ans: (B)

**Sol:** To perform the given operation, both operands must have same number of bits.

#### Specific Section (EE)

##### One mark Solutions:

###### 01. Ans: (A)

**Sol:**  $\frac{dy}{dx} = y + x$

$$x_0 = 0, y_0 = 1$$

$$x_1 = x_0 + h = 0.1$$

$$x_2 = x_0 + 2h = 0.2$$

$$y_1 = y_0 + h f(x_0, y_0)$$

$$= 1 + (0.1)(1)$$

$$= 1.1$$

$$y_2 = y_1 + h f(x_1, y_1)$$

$$= 1.1 + 0.1 [0.1 + 1.1]$$

$$= 1.1 + 0.12$$

$$= 1.22$$

###### 02. Ans: (D)

**Sol:** To perform the given operation, both operands must have same number of bits.

Hence by extending the sign bit, A = 111011

$$\text{Now, } A - B = 111011 - 100101$$

$$= 111011 + 2\text{'s complement of}$$

$$100101$$

$$= 111011 + 011011$$

$$\begin{array}{r}
 111011 \\
 + 011011 \\
 \hline
 \overbrace{1}^{1} 010110
 \end{array}$$

EAC is neglected in 2's complement operation

(EAC – End Around Carry )

$$\text{Hence } A - B = 010110$$



03. Ans: 2.121 (Range: 2 to 2.4)

Sol:  $f(x, y, z) = 2y + z$

$$\text{Directional derivate} = (\nabla f) \cdot \frac{\bar{a}}{|\bar{a}|}$$

$$\begin{aligned}\nabla f &= \bar{j} \frac{\partial f}{\partial y} + \bar{k} \frac{\partial f}{\partial z} \\ &= \bar{j}.2 + \bar{k}.1 \\ &= 2\bar{j} + \bar{k}\end{aligned}$$

$$\begin{aligned}\therefore \text{Directional derivate} &= (2\bar{j} + \bar{k}) \frac{(\bar{j} + \bar{k})}{\sqrt{2}} \\ &= \frac{2+1}{\sqrt{2}} \\ &= \frac{3}{\sqrt{2}} \\ &= 2.121\end{aligned}$$

04. Ans: (A)

05. Ans: (B)

Sol: We have  $\lim_{x \rightarrow 0} f(x) = f(0) = 0$

$\therefore f(x)$  is continuous at  $x = 0$

$$f'(0) = \lim_{h \rightarrow 0} \frac{f(0+h) - f(0)}{h}$$

$$= \lim_{h \rightarrow 0} \frac{h^2 \sin\left(\frac{1}{h}\right) - 0}{h} = 0$$

$\therefore f(x)$  is differentiable at  $x = 0$

06. Ans: (B)

Sol: A ideal PMMC voltmeter will read average voltage.

for 1- $\phi$ , half wave voltage controller, output

$$\text{voltage, } V_0 = \frac{V_m}{2\pi} [\cos \alpha - 1]$$

$$\begin{aligned}&= \frac{V_m}{2\pi} [-1 - 1] \\ &= \frac{-V_m}{\pi}\end{aligned}$$

07. Ans: (B)


Sol: In figure 'b' all the three systems have the identical damped frequency  $\omega_d$

$$\therefore \text{Peak time is same, } t_p = \frac{\pi}{\omega_d}$$

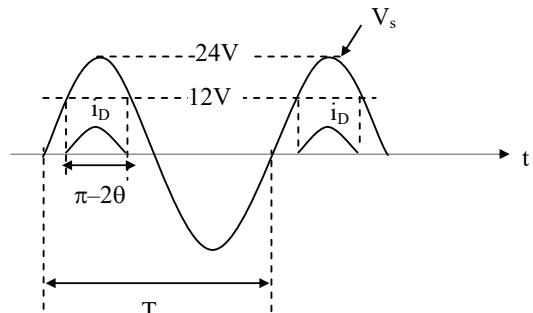08. Ans: (B)

Sol: The maximum reverse voltage across the diode occurs when  $V_s$  is at its negative peak and is equal to  $24 + 12 = 36$  V

The diode conducts only when  $V_s$  exceeds 12 V as shown below



The conduction angle is  $2\theta$ , where  $\theta$  is given by  $24\sin\theta = 12$

$$\Rightarrow \theta = \sin^{-1}(1/2) = 30^\circ$$

Thus the conduction angle is  $120^\circ$  which corresponds to one-third of a cycle

Hence the diode conducts for a duration of  $T/3$  s during each cycle.



**09. Ans: (C)**

**Sol:** The load current referred to primary is 2A, and the magnetizing current is 1A. These two have a phase difference of  $90^\circ$  w.r.t each other. Hence the primary current is  $\sqrt{(2^2 + 1^2)} = 2.24$  A.

**10. Ans: 50.24 (range 48 to 52)**

**Sol:**  $Z = R + j\omega L = 362 + j(100\pi) 2$

$$i = \frac{V}{Z}$$

$$= \frac{230}{362 + j200\pi} = \frac{230}{725.14 \angle 60^\circ}$$

$$= 0.317 \angle -60^\circ$$

∴ The current  $I = 0.317 \times \sqrt{2} \sin(\omega t - 60^\circ)$

Instantaneous voltage is maximum at  $\omega t = \frac{\pi}{2}$

$$i = 0.317 \times \sqrt{2} \sin(90^\circ - 60^\circ)$$

$$i = 0.317 \times \sqrt{2} \cos 60^\circ$$

$$= 0.224A$$

$$\therefore \text{The energy stored} = \frac{1}{2} LI^2$$

$$= \frac{1}{2} \times 2 \times (0.224)^2 = 50.2mJ$$

**11. Ans: (B)**

**Sol:** Let P be the input,  $Q_n$  be present state and  $Q_{n+1}$  be next state.

$$R = \overline{P \oplus Q_n} \quad S = P \oplus Q_n$$

Characteristic equation of SR flip-flop is

$$Q_{n+1} = S + \overline{R} Q_n$$

$$= (P \oplus Q_n) + (\overline{P \oplus Q_n}) Q_n$$

$$= (P \oplus Q_n) + (P \oplus Q_n) Q_n$$

$$= (P \oplus Q_n) (1 + Q_n)$$

$$Q_{n+1} = P \oplus Q_n$$

$$\text{For } P = 0, Q_{n+1} = Q_n$$

$$\text{For } P = 1 \quad Q_{n+1} = \overline{Q}_n$$

Hence the circuit functions as T flip-flop.

**12. Ans: (B)**

**Sol:** Inertia constant (H) =

$$\frac{\text{kinetic energy stored in rotor(MJ)}}{\text{MVA rating of alternator(s)}}$$

$$H_1 = \frac{400}{100} = 4 ; H_2 = \frac{900}{150} = 6$$

$$H_{eq} = \frac{H_1 H_2}{H_1 + H_2} = \frac{4 \times 6}{4 + 6} = 2.4$$

**13. Ans: (A)**

**Sol:** Probability that there are exactly 2 defectives

$$\text{in the first 5 selected articles} = \frac{3C_2 \cdot 7C_3}{10C_5} = \frac{5}{12}$$

Probability that 6<sup>th</sup> article is defective =

$$\frac{1}{5} \text{ Required probability} = \frac{5}{12} \cdot \frac{1}{5} = \frac{1}{12}$$

**14. Ans: 11 (11 to 11)**

**Sol:** The rms value of the square-wave voltage is

$$E_{rms} = \sqrt{\frac{1}{T} \int_0^T e^2 dt} = E_m$$

And the average value is

$$E_{av} = \frac{2}{T} \int_0^{T/2} e \cdot dt = E_m$$

So that the form factor equals, by definition,



$$k = \frac{E_{rms}}{E_{av}} = 1$$

The meter scale is calibrated in terms of the rms value of a sine-wave voltage, where  $E_{rms} = k \times E_{av} = 1.11E_{av}$ . For the square-wave voltage,  $E_{rms} = E_{av}$ , since  $k = 1$ . Therefore the meter indication for the square-wave voltage is high by a factor  $k_{\text{sine wave}}/k_{\text{square wave}} = 1.11$ . The percentage error equals

$$\frac{1.11-1}{1} \times 100\% = 11\%$$

### 15. Ans: 6

**Sol:** If the system has a non-zero solution then determinant of coefficient matrix is zero.

$$\Rightarrow \begin{vmatrix} 1-\lambda & 2 & 3 \\ 3 & 1-\lambda & 2 \\ 2 & 3 & 1-\lambda \end{vmatrix} = 0$$

$$\Rightarrow (6 - \lambda)(\lambda^2 + 3\lambda + 3) = 0$$

$$\Rightarrow \lambda = 6$$

### 16. Ans: -10

$$\text{Sol: } \frac{V_0}{V_{in}} \cong \frac{-R_C}{R_E} \cong \frac{-1k}{100} \cong -10$$

### 17. Ans: 0.02 (No range)

$$\text{Sol: } D = \frac{1.25 \times 80}{1 \times 50} \text{ MW / Hz}$$


$$= 2 \text{ MW/Hz}$$

$$= \frac{2}{100} \text{ pu MW / Hz}$$

$$= 0.02 \text{ pu MW/Hz}$$

### 18. Ans: 58 (Range: 58 to 58)

**Sol:**

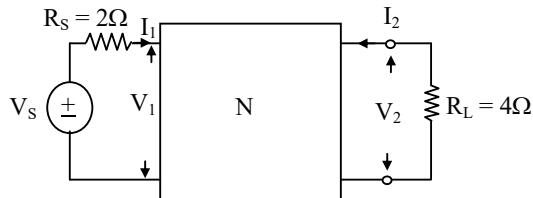

From h-parameter equations are

$$V_1 = h_{11}I_1 + h_{12}V_2 = 2I_1 + 4V_2 \dots\dots (1)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 = -5I_1 + 2V_2 \dots\dots (2)$$

$$\text{But } V_2 = -4I_2$$

$$I_2 = -5I_1 + 2(-4I_2)$$

$$9I_2 = -5I_1$$

Power dissipated is  $4\Omega$  resistor = 25W

$$\frac{V_2^2}{R_L} = 25 \text{ W}$$

$$V_2 = \sqrt{25 \times 4} = 10 \text{ V}$$

$$I_2 = \frac{-V_2}{4} = -\frac{10}{4} = -2.5$$

$$\therefore I_1 = -\frac{9}{5}(I_2)$$

$$= -\frac{9}{5}(-2.5)$$

$$= 4.5 \text{ A}$$

$$\therefore V_1 = 2(4.5) + 4(10) = 49 \text{ V}$$

$$V_s = V_1 + I_1 R_s$$

$$= 49 + (4.5 \times 2)$$

$$V_s = 58 \text{ V}$$

### 19. Ans: (A)

$$\text{Sol: } \int_2^{2i} \frac{dz}{z}$$

$$= [\log z]_2^{2i}$$

$$= \log 2i - \log 2$$



$$= \log 2 + \log i - \log 2$$

$$= \log i$$

$$= \log e^{\frac{i\pi}{2}}$$

$$= \frac{i\pi}{2}$$

**20. Ans: (B)**

**Sol:** Sending end voltage is given as

$$V_s = AV_r + BI_r$$

Receiving end current under open condition is zero

$$I_R = 0$$

$$V_s = AV_R$$

$$V_R = \frac{V_s}{A} \Rightarrow \frac{400}{0.8} = 500 \text{ kV}$$

**21 Ans: (A)**

**22. Ans: (D)**

**23. Ans: (C)**

**Sol:** For ripple counter,

$$\text{Maximum frequency of operation, } f \leq \frac{1}{n \cdot t_{pd}}$$

$n \rightarrow$  number of flip-flops

$t_{pd} \rightarrow$  propagation delay of flip-flop

$$(12 \times 10^6) \leq \frac{1}{n(12 \times 10^{-9})}$$

$$n \leq \frac{1}{(12 \times 12 \times 10^{-3})}$$

$$n \leq 6.94$$

Always n is an integer  $\therefore n = 6$

With n = 6, the modulus of counter =  $2^n$

$$= 2^6$$

$$= 64$$

**24. Ans: (d)**

**Sol:** System is unstable, therefore error is unbounded.

**25. Ans: (B)**

**Sol:** Deflection of electron beam on the screen in

$$y\text{-direction, } D = \frac{Ll_d E_d}{2dE_a} \text{ m}$$

Where L  $\rightarrow$  distance between the screen and centre of the deflecting plates.

$l_d \rightarrow$  length of deflecting plates

$E_d \rightarrow$  Potential between deflecting plates

d  $\rightarrow$  distance between deflecting plates.

$E_a \rightarrow$  Pre-accelerating anode voltage

$$D \propto \frac{E_d}{E_a}$$

$$D_1 = \frac{E_{d1}}{E_{a1}}$$

$$D_2 = \frac{2E_{d1}}{\frac{1}{2}E_{a1}}$$

$$D_2 = 4D_1$$

$$D_2 = 40 \text{ mm}$$

**Two marks Solutions:**

**26. Ans: 2**

**Sol:** Since A is upper triangular matrix the eigen values are same as the diagonal elements of A.

$\therefore$  Eigen values are  $\lambda = 1, 1, 1$

The eigen vectors for  $\lambda = 1$  are given by



$$[A - \lambda I] X = 0$$

$$\Rightarrow \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$


Here rank of  $(A - \lambda I) = k = 1$

Number of variables =  $n = 3$

Number of linearly independent eigen vectors  
 $= n - k = 2$
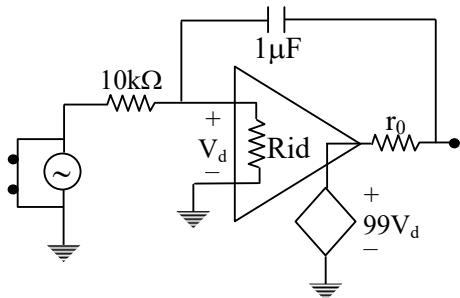
### 27. Ans: (D)

**Sol:** For the overall time constant of this circuit input voltage source is short circuited



$$\frac{1}{R_{\text{eq}}} = \frac{1}{10k} + \frac{1}{10k} = \frac{1}{5k} \quad R_{\text{eq}} = 5k$$

$$\tau = R_{\text{th}} C_{\text{eq}}$$

$$= [10k||10k] 1\mu [1 + 99] \\ = [5k] 10^{-6} [10^2] = 0.5\text{sec}$$

### 28. Ans: (C)

$$\text{Sol: } G(s) = \frac{k(s+2)(s+3)}{(s+1)(s+4)}$$

$$\text{CLTF} = \left. \frac{G(s)}{1+G(s)} \right|_{k=1} = \frac{(s+2)(s+3)}{(s+1)(s+4) + (s+2)(s+3)}$$

### 29. Ans: (B)

**Sol:** Turn on cycle  $T = \frac{1}{f} = \frac{1}{60} \text{ sec}$

Rate of change of current

$$\frac{di}{dt} = 0.4$$

$$= 0.4 \times 60 = 24 \text{ A/sec}$$

$$V_s = L \frac{di}{dt}$$

$$\text{Source inductance } L = \frac{V_s}{\left(\frac{di}{dt}\right)} = \frac{240}{24} \\ = 10 \text{ H}$$

Circuit turn off time is given by


$$t_c = R \times C \times \ln 2$$

$$2 \times 15 \times 10^{-6} = 12 \times C \times \ln 2$$

$$C = 3.6067 \mu\text{F}$$

### 30. Ans: (B)

**Sol:**

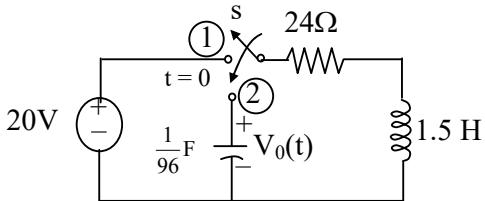

For  $t < 0$  switch is at position (1)



$L \rightarrow 20 \text{ V only}$

$C \rightarrow V_c(0) = 0$

$$20V \xrightarrow{\text{24Ω}} i_L(0^+) = \frac{20}{24} = \frac{5}{6} \text{ A}$$



For  $t > 0$  s is in position (2)

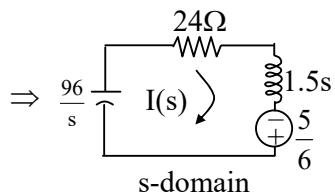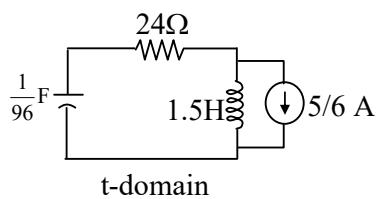

$$\frac{5}{6} = I(s) \left( \frac{96}{s} + 24 + \frac{3}{2}s \right)$$

$$\frac{5}{6} = I(s) \left( \frac{96 + 24s + 1.5s^2}{s} \right)$$

$$I(s) = \frac{5s}{6(1.5s^2 + 24s + 96)}$$

$$s = \frac{-24 \pm \sqrt{(24)^2 - 4(1.5)(96)}}{2(1.5)}$$

$$s = \frac{-24 \pm \sqrt{576 - 576}}{3} = -8$$

$$s = -8$$

Roots are real & equal  $i(t)$  is critically damped.

$$V_0(t) = \frac{96}{s} I(s) = \frac{96}{s} \frac{5s}{6(s+8)^2} = \frac{80}{(s+8)^2}$$


$$V_0(t) = (A + Bt)e^{-8t}$$

### 31. Ans: (C)
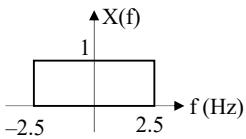
### 32. Ans: (A)

Sol:  $x(t) = 5 \operatorname{sinc}(5t)$

$$= \frac{5 \sin 5\pi t}{5\pi t} \xrightarrow{\text{FT}}$$




$$\text{Sampled spectrum } X_\delta(f) = \frac{1}{T_s} \sum_{n=-\infty}^{+\infty} X(f - nf_s)$$

Given  $f_s = 10 \text{ Hz}$


$$T_s = \frac{1}{10}$$
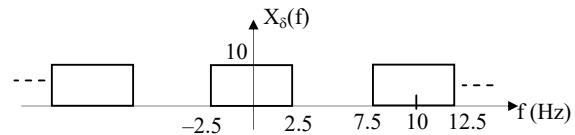
$$= 10 \sum_{n=-\infty}^{+\infty} X(f - 10n)$$



The above signal passed through ideal LPF with cut-off frequency 5 Hz

So, the output of the filter is

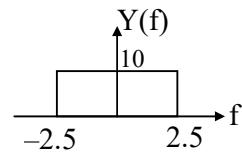

$$Y(f) = 10 \operatorname{rect}(f/5)$$

### 33. Ans: 26.18 (Range: 25 to 27)

Sol: Given specifications of synchronous generator are MVA rating = 500 MVA

kV rating = 20 kV

poles (P) = 4

Inertia constant H = 6.0 MJ/MVA

Also given that

Power being delivered to infinite bus

$$(P_0) = 1 \text{ pu}$$

Maximum power that can be delivered

$$(P_m) = 2.5 \text{ pu}$$

A fault occurs on the generator such that

Output of generator becomes zero.

$\therefore P_e = \text{Electrical output of the generator} = 0$



$$\therefore P_e = 0$$

$P_m$  = Mechanical input to the generator = 1 pu

$$P_a = P_m - P_e = 1 - 0 = 1 \text{ pu}$$

$$P_a = 1 \text{ pu}$$

$P_a$  = Accelerating power

Angular acceleration is given by

$$\frac{d^2\delta}{dt^2} = \frac{P_a}{M}$$

$M$  = angular momentum

$$\therefore M = \frac{GH}{\pi f} \text{ MJ-sec/rad}$$

In pu terms

$$M = \frac{H}{\pi f} \text{ MJ-sec/rad}$$

$$\therefore \frac{d^2\delta}{dt^2} = \frac{\pi f}{H} \quad [\because P_a = 1 \text{ pu}]$$

$$\frac{d^2\delta}{dt^2} = \frac{(3.14)(50)}{6}$$

$$\frac{d^2\delta}{dt^2} = 26.18 \text{ rad/sec}^2$$

#### 34. Ans: -0.535 (Range: -0.5 to -0.6)

$$\text{Sol: } G(s)H(s) = \frac{K(s+4)}{s(s+1)}$$

$$\text{For break in/away points } \frac{dK}{ds} = 0$$

$$s(s+1) - (s+4)(2s+1) = 0$$

$$s^2 + s = 2s^2 + 9s + 4$$



$$s = \frac{-8 \pm \sqrt{64 - 16}}{2}$$

$$s_1 = -4 + 3.464, s_2 = -4 - 3.464$$

$$s_1 = -0.535, s_2 = -7.464$$

#### 35. Ans: (C)

Sol:

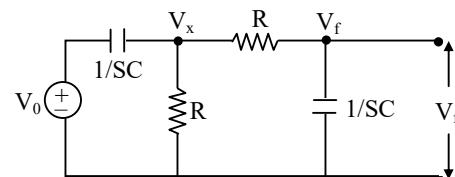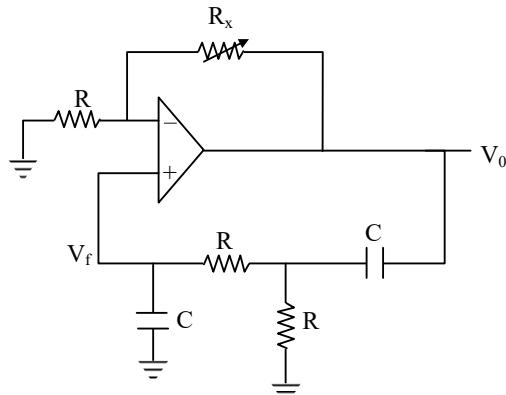

$$\frac{V_0 - V_x}{\frac{1}{SC}} = \frac{V_x}{R} + \frac{V_x - V_f}{R} \quad \dots\dots (1)$$


$$\text{and } \frac{V_x - V_f}{R} = \frac{V_f}{\frac{1}{SC}} \quad \dots\dots (2)$$

$$\therefore V_x = (1 + SRC) V_f \quad \dots\dots (3)$$

$$\Rightarrow \beta = \frac{V_f}{V_0} = \frac{SRC}{S^2 C^2 R^2 + 3SCR + 1}$$

[\because \text{from equation (1), (2) \& (3)}]
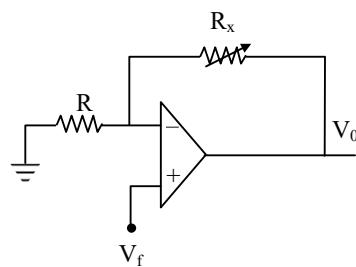
$$\therefore \beta = \frac{1}{3 + j \left[ \omega CR - \frac{1}{\omega CR} \right]}$$





$$\frac{V_0}{V_f} = 1 + \frac{R_x}{R}$$

Since for sustained oscillations  $\beta A = 1$

$$\Rightarrow A = \frac{1}{\beta}$$

$$\therefore 1 + \frac{R_x}{R} = 3 + j \left[ \omega CR - \frac{1}{\omega CR} \right]$$

Equating img., parts

$$\Rightarrow \omega CR - \frac{1}{\omega CR} = 0$$


$$\Rightarrow f = \frac{1}{2\pi RC} \text{ Hz}$$

$$\& 1 + \frac{R_x}{R} = 3$$

$$\therefore R_x = 2R$$
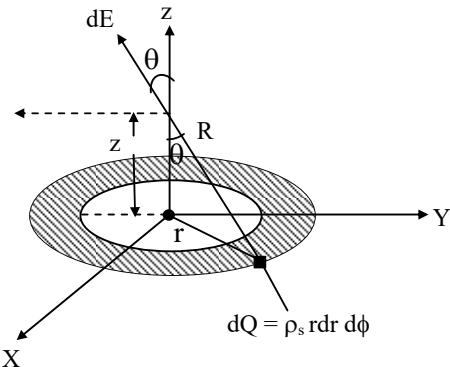
### 36. Ans: (B)

**Sol:** From fig. by symmetry only the z-components of the field exists along the z-axis.



$$dQ = \rho_s r dr d\phi$$

$$\cos \theta = \frac{z}{R}, \quad R = \sqrt{r^2 + z^2}$$

Hence

$$dE_z = \frac{dQ}{4\pi \epsilon_0 R^2} \cos \theta$$

$$= \frac{\rho_s r dr d\phi}{4\pi \epsilon_0 (r^2 + z^2)} \cdot \frac{z}{\sqrt{r^2 + z^2}}$$

$$= \frac{100 \times 10^{-6}}{4\pi \times \frac{1}{36\pi} \times 10^{-9} (r^2 + z^2)^{3/2}} \times r dr d\phi \times z$$

At  $z = 10$  m

$$E_z = 9 \times 10^6 \int_{r=1}^2 \int_{\phi=0}^{2\pi} \frac{dr d\phi}{(r^2 + 100)^{3/2}}$$

$$= 18\pi \times 10^6 \int_{r=1}^2 \frac{dr}{(r^2 + 100)^{3/2}}$$

$$= 18\pi \times 10^6 \left[ \frac{r}{100\sqrt{r^2 + 100}} \right]_{r=1}^2$$

$$= 54.63 \text{ kV/m}$$

### 37. Ans: (B)

**Sol:** In case of motor

$$V = E_b + I_a R_a$$

$$E_b = V - I_a R_a$$

At 900 rpm

$$E_b = 60 - (30 \times 0.35)$$

$$= 60 - 10.5 = 49.5$$

The back emf corresponding to speed of 300 rpm is

$$E_b \propto N\phi$$

$$E_{b2} = E_{b1} \times \frac{N_2}{N_1}$$

$$E_{b2} = 49.5 \times \frac{300}{900}$$

$$= 16.5 \text{ V}$$

$$\therefore V = E_{b2} + I_a R_a$$

$$= 16.5 + (30 \times 0.35) = 27$$

For a chopper  $V_0 = D \times V$



$$27 = D \times 60$$

$$D = 0.45$$

**38. Ans: (B)**

$$\begin{aligned} h_c(n) &= h_1(n) * h_2(n) = [\delta(n+1) - \delta(n)] * [\delta(n) - \delta(n-1)] \\ &= \delta(n+1) - 2\delta(n) + \delta(n-1) \\ &= \{1, -2, 1\} \end{aligned}$$

$$h_c(n) \neq 0, n < 0$$

so, non causal

$$\sum_{n=-\infty}^{\infty} |h_c(n)| \neq \infty, \text{ stable}$$

**39. Ans: 2.28 (Range 2 to 2.5)**

$$\text{Sol: The phase voltage } = \frac{V_{L-L}}{\sqrt{3}} = \frac{398}{\sqrt{3}} = 230V$$

$$Z_1 = 20 + j37.7$$

$$I_1 = \frac{V_1}{Z_1} = \frac{230}{20 + j37.7}$$

$$= 5.39 \angle -62.05$$

$$= 2.52 - j4.76$$

The equivalent star impedance

$$(Z_2)_{eg} = \frac{Z_2}{3} = 10 - j53.1$$

$$I_2 = \frac{V_1}{(Z_2)_{eg}} = \frac{230}{10 - j53.1}$$

$$= 0.79 + j4.19$$

$$\text{So total current } I = I_1 + I_2$$

$$= 2.52 - j4.76 + 0.79 + j4.19$$

$$= 3.31 - j0.57$$

$$= 3.36 \angle -9.8^\circ$$


∴ The power  $P = 3 \times \text{power per phase}$

$$= 3 \times 230 \times 3.36 \times \cos(9.8)$$

$$= 2284.6W$$

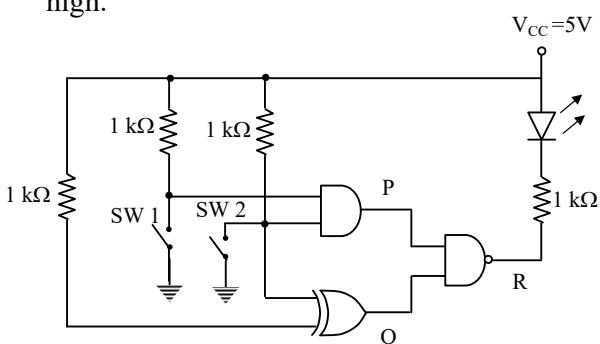**40. Ans: (D)**

**Sol:** Output of NAND gate must be low for LED to emit light.  
 $\Rightarrow$  Output of AND and Ex-OR gate should be high.



SW1	SW2	P	Q	R
Open	Open	1	0	1
Open	Close	0	1	1
Close	Open	0	0	1
Close	Close	0	1	1

Hence, there can't be both high inputs to NAND gate and hence LED doesn't emit light for any combination.

**41. Ans: 260.2 (Range: 258 to 262)**

**Sol:** Loop inductance of the line  $d = 7.5 \times 10^{-2}$

$$r = \frac{7.5}{2} \times 10^{-2}$$

$$= 3.75 \times 10^{-2}$$

$$L = \frac{N\phi}{I} \quad \because N = 1$$

$$\phi = LI$$

$$L = 4 \times 10^{-7} \left( \frac{GMD}{GMR} \right)$$



$$\phi = 4 \times 10^{-7} \times 800 \times \ln\left(\frac{0.6}{3.75 \times 10^{-2}}\right)$$

$$\phi = 8.87 \times 10^{-4}$$

Voltage induced in sheath

$$v = \omega \phi$$

$$v = 2\pi f \phi$$

$$v = 314 \times 8.87 \times 10^{-4}$$

$$v = 0.2602 \text{ V}$$

$$v = 260.2 \text{ Volt/km}$$

#### 42. Ans: (D)

**Sol:** total losses =  $3[0.01+0.02] = 0.09 \text{ pu}$

The current carried by each transformer in open delta is  $\sqrt{3}$  pu and core losses in each transformer remain unchanged

$$\text{Now Cu losses} = 2(\sqrt{3})^2 (0.02) = 0.12$$

$$\text{Core losses} = 2(0.01) = 0.02$$

$$\text{Total losses} = 0.02 + 0.12 = 0.14$$

$$\% \text{ increase} = \frac{0.14 - 0.09}{0.09} \times 100 = 55.56\%$$

#### 43. Ans: (C)

$$\text{Sol: } f(x) = \int_0^{\frac{\pi}{2}} \frac{\cos x + i \sin x}{\cos x - i \sin x} dx$$

$$= \int_0^{\frac{\pi}{2}} \left[ \frac{\cos x + i \sin x}{\cos x - i \sin x} \times \frac{\cos x + i \sin x}{\cos x + i \sin x} \right] dx$$

$$= \int_0^{\frac{\pi}{2}} \frac{\cos^2 x - \sin^2 x + i \sin 2x}{\cos^2 x + \sin^2 x} dx$$

$$= \int_0^{\frac{\pi}{2}} (\cos 2x + i \sin 2x) dx$$

$$= \left[ \frac{\sin 2x}{2} - \frac{i \cos 2x}{2} \right]_0^{\frac{\pi}{2}}$$

$$= \frac{-i}{2} [-1 - 1]$$

$$= i$$

#### 44. Ans: (C)

**Sol:** when converter circuit is working in an inverter mode,

$$V_0 = -E_0 + I_0 R$$

$$= -230 + (25 \times 2)$$

$$= -180$$

$$= \frac{3V_m}{2\pi} \cos \alpha - \frac{3\omega L_s}{2\pi} I_0 = V_0$$

$$\frac{3 \times \sqrt{2} \times 400}{2\pi} \cos \alpha - \frac{3 \times 100\pi \times 2 \times 10^{-3} \times 25}{2\pi} = -180$$

$$\cos \alpha = -0.63$$

$$\alpha = 129.7^\circ$$

$$I_0 = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$25 = \frac{\sqrt{2} \times 400}{2 \times 100\pi \times 2 \times 10^{-3}} [\cos 129.7 - \cos(129.7 + \mu)]$$

$$0.055 = \cos(129.7) - \cos(129.7 + \mu)$$

$$\cos(129.7 + \mu) = -0.069$$

$$\mu = 4.27^\circ$$

#### 45. Ans: (B)

**Sol:**  $E_b = V - I_a R_a = 500 - 60(0.5) = 470 \text{ V}$

$$\omega \times \tau_e = E_b I_a$$

$$\frac{2\pi \times 800}{60} \times \tau_e = 470 \times 60$$

$$\tau_e = 336.61 \text{ Nm}$$

$$\text{New load torque} = 2.5 \times 336.61 = 841.52 \text{ Nm}$$



Torque developed by the set

$$\Rightarrow 841.52 = \frac{2(250 - I_a \times 0.5) \times I_a}{(2\pi \times 400)} \times 60$$

$$\Rightarrow I_a^2 - 500I_a + 35250 = 0$$


$$I_a = \frac{500 \pm \sqrt{(500)^2 - 4 \times 35250}}{2}$$

$$= \frac{500 \pm 330.15}{2}$$

$$I_a = 415 (\text{or}) 84.92 \text{ A}$$

#### 46. Ans: (D)

Sol:

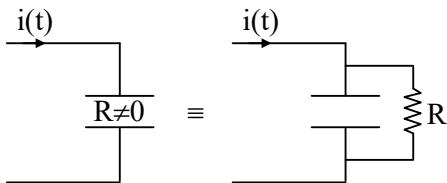

$$i(t) = C \frac{dv}{dt} + \frac{v}{R}$$

$$R = \frac{\rho d}{A} = \frac{d}{\sigma A} = \frac{5 \times 10^{-3}}{10^{-3} \times 1 \text{ m}^2} = 5 \Omega$$

$$i(t) = C \frac{dv(t)}{dt} + \frac{v(t)}{R}$$

$$\therefore i(t) = 8 \times 10^{-6} \times 10 \cos(2\pi \times 50t) \times 2\pi \times 50$$

$$+ \frac{10 \sin(2\pi \times 50t)}{5}$$

$$\therefore i(t) = 8\pi \times 10^{-3} \cos(2\pi \times 50t) + 2\sin(2\pi \times 50t)$$

$$\text{If } i(t) = A \cos \omega t + B \sin \omega t$$

$$i_{\text{rms}}(t) = \sqrt{\frac{A^2}{2} + \frac{B^2}{2}}$$

$$i_{\text{rms}}(t) = \sqrt{\frac{(8\pi \times 10^{-3})^2}{2} + \frac{2^2}{2}}$$

$$\therefore i(t)_{\text{rms}} = 1.414 \text{ Amp}$$

#### 47. Ans: 0.568 (Range: 0.45 to 0.7)

Sol: Per phase rotor resistance,

$$r_2 = \frac{0.04}{2} = 0.02 \Omega$$

Full-load slip,  $s_1 = 0.02$

$$\text{New slip, } s_2 = \frac{500 - 350}{500} = 0.30$$

Now load torque,  $T_L \propto n^2$

$$T_{L1} \propto [(1 - 0.02) 500]^2$$

$$T_{L1} \propto (490)^2$$

$$\text{And } T_{L2} \propto (350)^2$$

Therefore,

$$R_2 = r_2 \left( \frac{s_2}{s_1} \right) \left( \frac{T_{L1}}{T_{L2}} \right) = 0.02 \left( \frac{0.30}{0.02} \right) \left( \frac{490}{350} \right)^2 = 0.588 \Omega$$

$\therefore$  External resistance that must be inserted in each rotor phase =  $0.588 - 0.02 \Rightarrow 0.568 \Omega$

#### 48. Ans: (A)

$$\text{Sol: } P = \frac{EV}{X_s} \sin \delta = \text{constant}$$

$\Rightarrow E = \text{constant} \because \text{Excitation is constant}$

$V$  &  $f$  are reduced by 10% i.e  $V^l = 0.9V$ ,  $f^l = 0.9f$

$$\frac{P^l}{P} = \frac{\frac{E^l V^l}{X_s^l} \sin \delta^l}{\frac{EV}{X_s} \sin \delta} = \frac{\frac{E \times 0.9V}{0.9X_s} \sin \delta^l}{\frac{EV}{X_s} \sin 30^\circ} = 1$$

$$\Rightarrow \frac{\sin \delta^l}{\sin 30^\circ} = 1$$


$$\Rightarrow \sin \delta^l = \sin 30^\circ$$

$$\therefore \delta^l = 30^\circ$$



49. Ans: (C)

Sol:

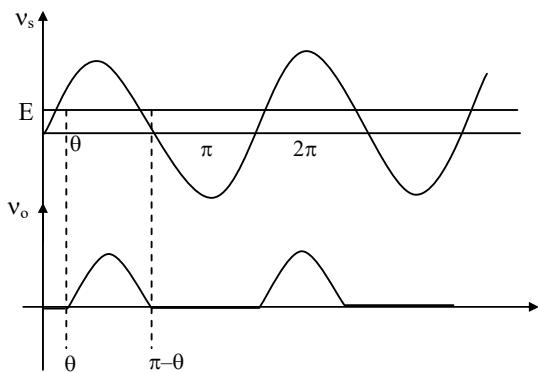

$$\theta = \sin^{-1} \left( \frac{E+1}{V_m} \right)$$

$$= \sin^{-1} \left( \frac{7}{\sqrt{2} \times 30} \right) = 9.49^\circ$$

For a diode rectifier

$$I_0 = \frac{1}{2\pi R} [2V_m \cos \theta - (E+1)(\pi - 2\theta)]$$

$$4 = \frac{1}{2\pi R} \left[ \frac{2 \times \sqrt{2} \times 30 \cos(9.49^\circ) - (6+1)}{(\pi - 2 \times 9.49^\circ) \times \frac{\pi}{180}} \right]$$

$$4 = \frac{1}{2\pi R} (83.69 - 19.67)$$

$$R = 2.54\Omega$$

50. Ans: (B)


Sol: The potential at 'p' is  $V_p = \frac{2q}{4\pi\epsilon_0(\sqrt{2}d)}$

The work done to bring

(-5Q) from  $\infty$  to 'p' is  $= (-5Q)V_p$

$$= (-5Q) \left( \frac{2q}{4\pi\epsilon_0\sqrt{2}d} \right)$$
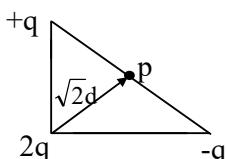
$$W = \frac{-10Qq}{4\pi\epsilon_0\sqrt{2}d}$$




$$= \frac{-10 \times 1 \times 10^{-3} \times 10^{-6}}{4\pi \times \frac{1}{36\pi} \times 10^{-9} \times \sqrt{2} \times \sqrt{2}}$$

$$= -\frac{90}{2} = -45(J)$$

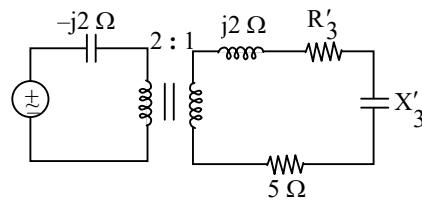51. Ans: (C)



Sol: Reflecting the secondary impedances to the primary side




$$R'_3 = \frac{R_3}{n^2} = \frac{80}{(4)^2} = 5\Omega \text{ (n = 4)}$$

$$X'_3 = \frac{X_3}{n^2} = \frac{-j16}{(4)^2} = -j1\Omega$$

Now circuit becomes as

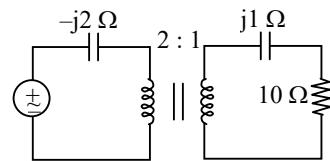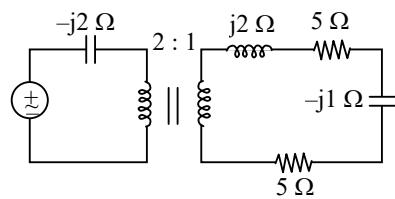

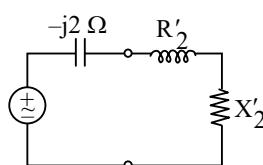Again reflecting the secondary impedance to the primary side





$$X'_2 = \frac{j1}{(n)^2} = \frac{j1}{(1/2)^2} = j4\Omega \quad (n=1/2)$$

$$R'_2 = \frac{10}{(n)^2} = \frac{10}{(1/2)^2} = 40\Omega$$

Total impedance seen by source

$$\begin{aligned} Z_{in} &= -j2 + R'_2 + X'_2 = -j2 + j4 + 40 \\ &= j2 + 40 \end{aligned}$$

**52. Ans: 93.07 (92.5 to 94)**

$$\text{Sol: } \eta_{15 \text{ KVA}} = \frac{15 \times 1}{15 \times 1 + 2W_i} = 0.95$$

$W_i = W_{cu} = 0.394 \text{ Kw}$  at  $\frac{3}{4}$  load.

Copper loss at full


$$\text{load} = \left(\frac{4}{3}\right)^2 \times 0.394 = 0.7 \text{ kW}$$

$\eta_{all-day}$

$$\begin{aligned} &= \frac{(12 \times 20 + 0)}{(12 \times 20 + 0) + (12 \times 0.7) + (24 \times 0.394)} \times 100 \\ &= 93.07 \% \end{aligned}$$

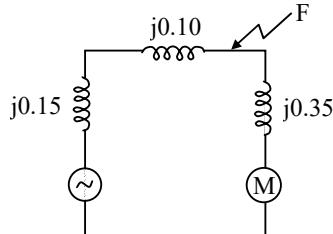**53. Ans: (A)**

**Sol:** The equivalent circuit shown below



$$\text{Current } I_L = 1 \angle 36.86^\circ$$

$$= (0.8 + j0.6) \text{ pu}$$

For the generator

$$E''_g = V_t + jI_L X_d'$$

$$\begin{aligned} &= 0.9 + (0.8 + j0.6) (j0.15) \\ &= 0.81 + j0.12 \text{ pu} \end{aligned}$$

For motor

$$\begin{aligned} E''_m &= V_t - jI_L X_d' \\ &= 0.9 - (0.8 + j0.6) (j0.45) \\ &= 1.17 - 0.36 \text{ pu} \end{aligned}$$

Sub transient current in the fault in the generator

$$\begin{aligned} I''_g &= \frac{E''_g}{X_d'} = \frac{0.81 + j0.12}{j0.25} \\ &= 0.48 - j3.24 \text{ pu} \end{aligned}$$


Sub transient current in the fault in the motor

$$\begin{aligned} I''_m &= \frac{E''_m}{X_d'} = \frac{1.17 - j0.36}{j0.35} \\ &= -1.03 - j3.34 \text{ pu} \end{aligned}$$

**54. Ans: (D)**

$$\text{Sol: } G(s) = \frac{5(1+0.1s)}{s(1+0.5s)\left[\left(\frac{s}{50}\right)^2 + \frac{s}{0.65} + 1\right]}$$

Corner frequencies = 2, 10, 50 rad/s

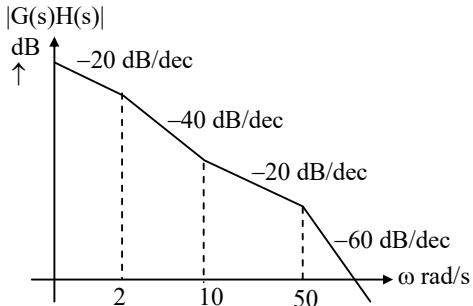

The slope change at  $\omega = 10$  rad/sec is  $-40$  dB/dec to  $-20$  dB/dec



**55. Ans: (A)**

$$\text{Sol: } x_e(t) = \frac{x(t) + x(-t)}{2} = \frac{1}{2} [e^{-2t} \cos t + e^{2t} \cos t]$$

$$x_e(t) = \frac{1}{2} \cos t [e^{2t} + e^{-2t}]$$

$$x_e(t) = \cosh(2t) \cos t$$