



# ACE

## Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

### ESE-2019 MAINS TEST SERIES Question Cum Answer Booklet (QCAB)

Electronics & Telecommunication Engineering      Test-1      Paper-I

Time Allowed: 3 Hours

Maximum Marks: 300

ACE HALL TICKET No. :

HALL TICKET No. :   
(Issued by UPSC)

NAME OF THE CANDIDATE :  NAME OF THE CENTRE :

BRANCH :  BATCH :  ROLL No. :  MOBILE No. :

TEST CODE :  DATE :  30-03-2019

#### INSTRUCTIONS TO CANDIDATES:

- This Question-cum- Answer (QCA) Booklet contains **84** pages. Immediately on receipt of booklet, please check that this QCA booklet does not have any misprint or torn or missing pages or items, etc. If so, get it replaced by a fresh QCA booklet.
- Candidates must read the instructions on this page and the following pages carefully before attempting the paper.
- Candidates should attempt all questions strictly in accordance with the specified instructions and in the space prescribed under each question in the booklet. Any answer written outside the space allotted may not be given credit.
- Question Paper in detachable form is available at the end of the QCA booklet and can be removed and taken by the candidates after conclusion of the exam

#### For filling by Examiners only

Question No.	Page No.	Marks
1	03	
2	11	
3	21	
4	30	
5	39	
6	48	
7	58	
8	69	
Grand Total		

Signature of the Invigilator

Signature of the Student

Marks Secured  
after Scrutiny

## **QUESTION PAPER SPECIFIC INSTRUCTIONS**

*Please read each of the following instructions carefully before attempting questions:*

*Answers must be written in ENGLISH only.*

*There are EIGHT questions divided in TWO sections.*

*Candidate has to attempt FIVE questions in all.*

*Questions no. 1 and 5 are compulsory and out of the remaining, THREE are to be attempted choosing at least ONE question from each section.*

*The number of marks carried by a question / part is indicated against it.*

*Wherever any assumptions are made for answering a question, they must be clearly indicated.*

*Diagrams / figures, wherever required, shall be drawn in the space provided for answering the question itself.*

*Unless otherwise mentioned, symbols and notations carry their usual standard meanings.*

*Candidates should attempt all questions in the space prescribed under each question in the Question-cum-Answer (QCA) Booklet. Any answer written outside the space allotted may not be given credit.*

*Attempts of questions shall be counted in sequential order. Unless struck off, attempt of a question shall be counted even if attempted partly. Any page or portion of the page left blank in the Question-cum-Answer Booklet must be clearly struck off.*

### ***Values of constants which may be required:***

$$\text{Electron charge} = -1.6 \times 10^{-19} \text{ Coulomb}$$

$$\text{Free space permeability} = 4\pi \times 10^{-7} \text{ Henry/m}$$

$$\text{Free space permittivity} = (1/36\pi) \times 10^{-9} \text{ Farad/m}$$

$$\text{Velocity of light in free space} = 3 \times 10^8 \text{ m/sec}$$

$$\text{Boltzmann constant} = 1.38 \times 10^{-23} \text{ J/K}$$

$$\text{Planck's constant} = 6.626 \times 10^{-34} \text{ J-s}$$

### **DONT'S:**

1. Do not write your Name or Roll number or Sr. No. of Question-Cum-Answer-Booklet anywhere inside this Booklet.  
Do not sign the "Letter Writing" questions, if set in any paper by name, nor append your roll number to it.
2. Do not write anything other than the actual answers to the questions anywhere inside your Question-Cum-Answer-Booklet.
3. Do not tear off any leaves from your Question-Cum-Answer-Booklet. If you find any page missing, do not fail to notify the Supervisor/invigilator.
4. Do not write anything on the Question Paper available in detachable form or admission certificate and write answers at the specified space only.
5. Do not leave behind your Question-Cum-Answer-Booklet on your table unattended, it should be handed over to the Invigilator after conclusion of the exam.


### **DO'S :**

1. Read the instructions on the cover page and the instructions specific to this Question Paper mentioned on the next page of this Booklet carefully and strictly follow them.
2. Write your Roll number and other particulars, in the space provided on the cover page of the Question-Cum-Answer-Booklet.
3. Write legibly and neatly. Do not write in bad/illegible handwriting.
4. For rough notes or calculations the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be valued.
6. Hand over your Question-Cum-Answer-Booklet personally to the invigilator before leaving the examination hall.
7. Candidates shall be required to attempt answer to the part/sub-part of a question strictly within the pre-defined space. Any attempt outside the pre-defined space shall not be evaluated.

**SECTION - A**


Candidates  
must not  
write on  
this margin

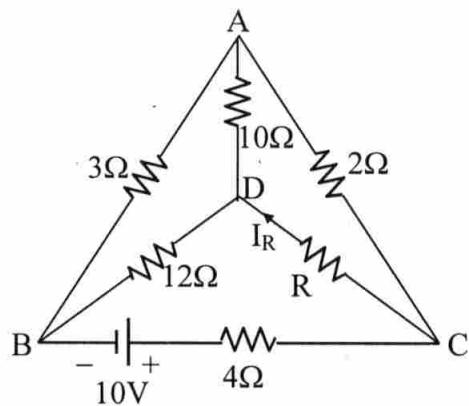- 01. (a)** Find the value of resistance  $R$  and current through it, in the circuit given below, when the branch AD carries no current.



Sol:

(12 M)

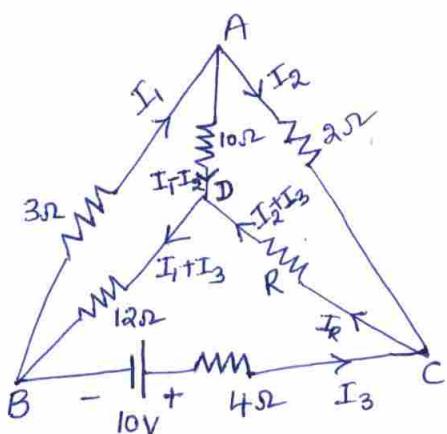

Let current  $I_1$ ,  $I_2$  and  $I_3$  flow in branches AB, AC and BC respectively. Hence, current through branches AD, CD and DB are  $I_1 - I_2$ ,  $I_2 + I_3$  and  $I_1 + I_3$  respectively.

By writing KVL equations in the three loops

$$-3I_1 - 10(I_1 - I_2) - 12(I_1 + I_3) = 0 \quad \dots \dots (1)$$

$$-2I_2 - R(I_2 + I_3) + 10(I_1 - I_2) = 0 \quad \dots \dots (2)$$

$$-R(I_2 + I_3) - 12(I_1 + I_3) + 10 - 4I_3 = 0 \quad \dots \dots (3)$$

But it is given that current through branch AB is zero

$$I_1 - I_2 = 0 \Rightarrow I_1 = I_2 \quad \dots \dots (4)$$

Using eq.(4) in eq.(1), we get

$$-3I_1 - 12(I_1 + I_3) = 0 \\ \Rightarrow I_3 = -\frac{5}{4}I_1 \quad \text{---(5)}$$

Substitute eq.(4) and eq.(5) in eq.(2)

$$-(2+R)I_1 = -R \frac{5}{4}I_1 \\ \therefore R = 8\Omega \quad \text{---(6)}$$

Substitute value of  $R$  (i.e. eq.(6)) in eq.(2) and eq.(3) and along with eq.(4), we get

$$\frac{5}{4}I_1 + I_3 = 0 \quad \text{---(7)}$$

$$20I_1 + 24I_3 = 10 \quad \text{---(8)}$$

On solving eq.(7) and (8), we get


$$I_1 = -1A ; I_3 = 1.25A \text{ and } I_2 = I_1$$

$$\therefore I_2 = -1A$$

$$\therefore \text{Current through resistor 'R' i.e. } I_R = I_3 + I_2 = -1 + 1.25 = 0.25 \text{ Amp}$$
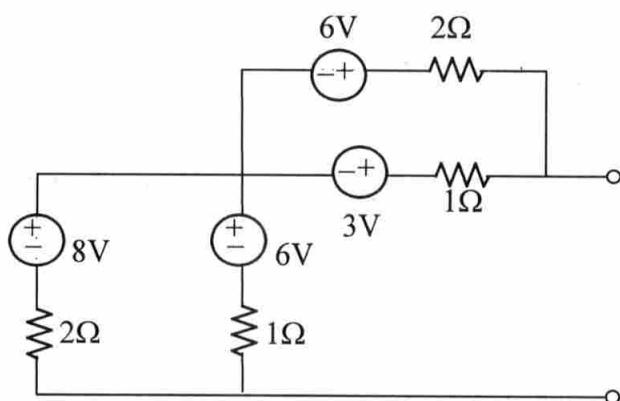
### 01. (b)

Using source transformation, deduce the circuit into its equivalent circuit with Ideal voltage source in devices with a resistance.




(12 M)


Sol:

Using Source transformation,


Step 1 :

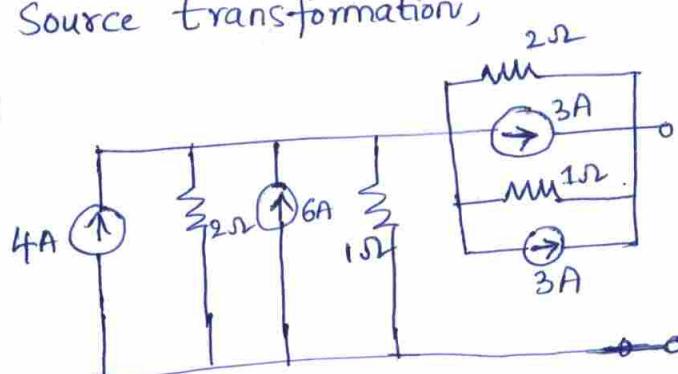


Step 2 :

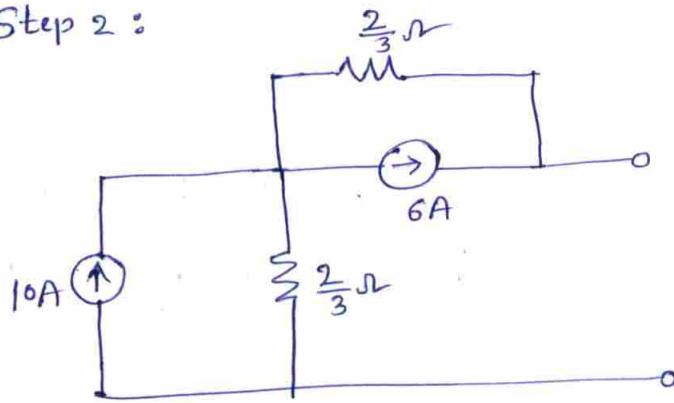

Step 3 :

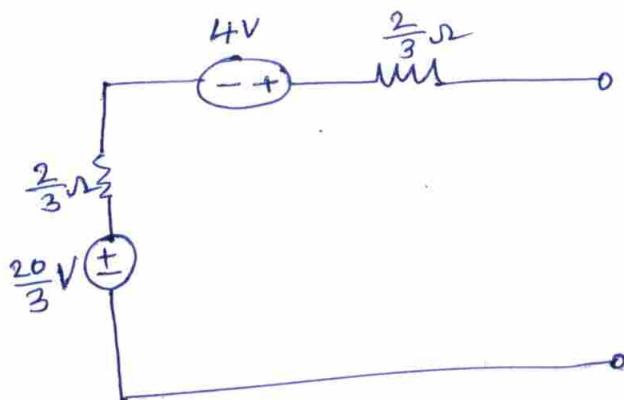

Step 4 :

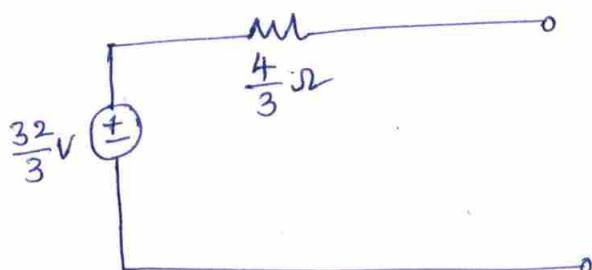

01. (c) State & explain Tellegen's theorem ?

(12 M)

Candidates  
must not  
write on  
this margin

Sol:

Tellegen's theorem states that,

"In any arbitrary jumped network, the algebraic sum of the powers in all branches at any instant is zero".

All branch currents and voltages in that network must satisfy Kirchoff's laws. Thus this theorem is based on Kirchoff's two laws (i.e KCL and KVL), but not on the type of circuit elements.

Explanation :

Consider two networks  $N_1$  and  $N_2$ , having the same graph with same reference directions assigned to branches in two networks, but with different values.

Let  $V_{ik}$ ,  $i_{ik}$  be the voltages and currents in

$N_1$  and  $V_{2k}$  and  $i_{2k}$  be voltages and currents

in  $N_2$ . By Tellegen's Theorem,

$$\sum_{k=1}^b V_{ik} \cdot i_{ak} = 0$$

and

$$\sum_{k=1}^b V_{2k} \cdot i_{ik} = 0$$

If  $t_1$  and  $t_2$  are two different times of observation,

$$\therefore \sum_{k=1}^b V_{IK}(t_1) \cdot i_{IK}(t_2) = 0$$

$\therefore$  Tellegen's Theorem depicts conservation of power.

01. (d) (i) A Si sample is doped with  $10^{18}$  As atom/cm<sup>3</sup>.

(A) what is the equilibrium hole concentration ' $P_o$ ' at 300 K?

(B) Show the position of  $E_{Fn}$  relative to  $E_i$  in band diagram.

- (ii) Find  $N_d$  for Si with  $10^{16}$  cm<sup>-3</sup> boron atoms and a certain number of donors, so that

$$E_{Fn} - E_{F_i} = 0.36\text{ev. } (\bar{K}T = 0.0259\text{ev}, n_i = 1.5 \times 10^{10} \text{cm}^{-3})$$

(6 + 6)M

Sol:

(i) (A) Given data

$$\text{for silicon at } 300\text{K, } n_i = 1.5 \times 10^{10} \text{cm}^{-3}$$

$$N_d = 10^{18} \text{cm}^{-3}.$$

Since  $N_d \gg n_i$ , we can approximate  $n_o = N_d$ .

$$\therefore \text{Hole concentration } (P_o) = \frac{n_i^2}{n_o} = \frac{n_i^2}{N_d}$$

$$= \frac{(1.5 \times 10^{10})^2}{10^{18}} = 2.25 \times 10^2 \text{cm}^{-3}.$$

(B) As we know,

$$E_{Fn} - E_i = RT \ln\left(\frac{n_0}{n_i}\right)$$

$$\Rightarrow E_{Fn} - E_i = 0.0259 \ln\left(\frac{10^{18}}{1.5 \times 10^{16}}\right)$$

$$= 0.466 \text{ eV} = 0.466 \text{ eV}$$

$\therefore$  Position of  $E_{Fn}$  relative to  $E_i$  is  $0.466 \text{ eV}$ .

$E_{Fn} - E_i = 0.466 \text{ eV}$

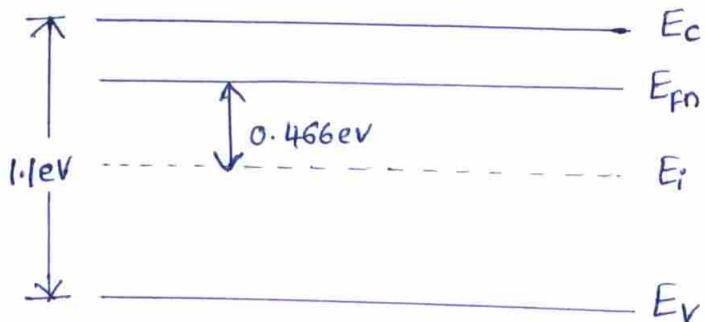


Fig. Band Diagram.

(ii)

As we know,

$$n_0 = n_i \cdot e^{\frac{E_{Fn} - E_{Fi}}{KT}}$$

$$\Rightarrow n_0 = (1.5 \times 10^{10}) \cdot e^{\frac{0.36}{0.0259}}$$

$$\Rightarrow n_0 = 1.63 \times 10^{16} \text{ cm}^{-3}$$

Again,

$$n_0 = N_d - N_A$$

$$\Rightarrow N_d = n_0 + N_A$$

$$\Rightarrow N_d = 1.63 \times 10^{16} + 10^{16}$$

$$\therefore \text{Donor Concentration } (N_d) = 2.63 \times 10^{16} \text{ cm}^{-3}$$

Candidates  
must not  
write on  
this margin

01. (e)

- (i) Show that the minimum conductivity of a semiconductor sample occurs when

$$n_{\min} = n_i \sqrt{\frac{\mu_p}{\mu_n}}$$

- (ii) What is the expression for the minimum conductivity  $\sigma_{\min}$ ?

- (iii) Calculate  $\sigma_{\min}$  for Si at 300K and compare with the intrinsic conductivity.

$$\left( \mu_n = 1350 \frac{\text{cm}^2}{\text{V-sec}}, \mu_p = 480 \frac{\text{cm}^2}{\text{V-sec}}, n_i = 1.5 \times 10^{10} \text{ cm}^{-3} \right)$$

(6 + 3 + 3)M

Sol:

(i)

The conductivity of a Semiconductor is

$$\sigma = nq\mu_n + pq\mu_p \longrightarrow ①$$

from mass-action law, we know  $np = n_i^2$

$$\Rightarrow p = \frac{n_i^2}{n}$$

$$\therefore \sigma = nq\mu_n + \frac{n_i^2}{n} q\mu_p$$

for minimum conductivity at electron concentration  $n_{min}$

$$\boxed{\frac{\partial \sigma}{\partial n} = 0}$$

$$\Rightarrow q\mu_n - \frac{n_i^2}{n_{min}^2} q\mu_p = 0.$$

$$\Rightarrow \mu_n = n_i^2 \cdot \frac{\mu_p}{\mu_n}$$

$$\Rightarrow n_{min}^2 = n_i^2 \cdot \frac{\mu_p}{\mu_n}$$

$$\Rightarrow \boxed{n_{min} = n_i \cdot \sqrt{\frac{\mu_p}{\mu_n}}}$$

$\therefore$  Minimum conductivity of a semiconductor sample

occurs when,  $n_{min} = n_i \cdot \sqrt{\frac{\mu_p}{\mu_n}}$ .

$$(ii) \quad \sigma_{min} = q \left( n_{min} \cdot \mu_n + \frac{n_i^2}{n_{min}} \cdot \mu_p \right)$$

$$\Rightarrow \sigma_{min} = q \left[ n_i \cdot \sqrt{\frac{\mu_p}{\mu_n}} \cdot \mu_n + \frac{n_i^2}{n_i} \cdot \sqrt{\frac{\mu_n}{\mu_p}} \cdot \mu_p \right]$$

$$\Rightarrow \sigma_{min} = q \left[ n_i \cdot \sqrt{\mu_n \cdot \mu_p} + n_i \cdot \sqrt{\mu_n \cdot \mu_p} \right]$$

$$\therefore \boxed{\sigma_{min} = 2q n_i \cdot \sqrt{\mu_n \cdot \mu_p}}$$

(iii) for a 'Si' semiconductor

$$\text{Intrinsic Conductivity, } \sigma_i = n_i \cdot q (\mu_n + \mu_p)$$

$$\Rightarrow \sigma_i = 1.5 \times 10^{10} \times 1.6 \times 10^{-19} (1350 + 480)$$

$$\therefore \sigma_i = 4.4 \times 10^{-6} (\Omega\text{-cm})^{-1}$$

$$\text{Minimum Conductivity, } \sigma_{\min} = 2q n_i \sqrt{\mu_n \mu_p}$$


$$\Rightarrow \sigma_{\min} = 2 \times 1.6 \times 10^{-19} \times 1.5 \times 10^{10} \times \sqrt{1350 \times 480}$$

$$\Rightarrow \boxed{\sigma_{\min} = 3.9 \times 10^{-6} (\Omega\text{-cm})^{-1}}$$

So, the minimum conductivity is less than the intrinsic conductivity for a silicon semiconductor.
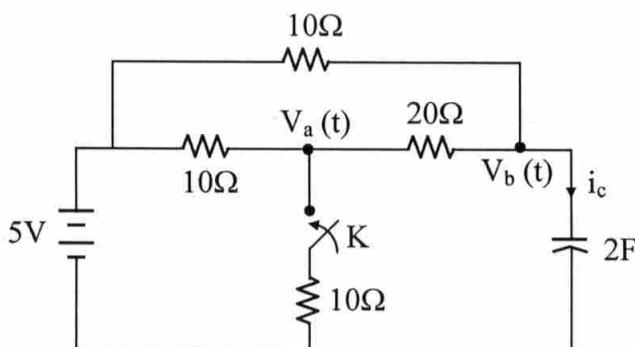
## 02. (a)

For the circuit shown, the switch K is closed at  $t = 0$ . At  $t < 0$ , the circuit is in steady state. Determine  $V_a$ ,  $V_b$ ,  $i_c$  at  $t = 0^-$ ,  $t = 0^+$ , &  $t = \infty$ .




(20 M)

Sol:

At  $t = 0^-$  circuit is in steady state,

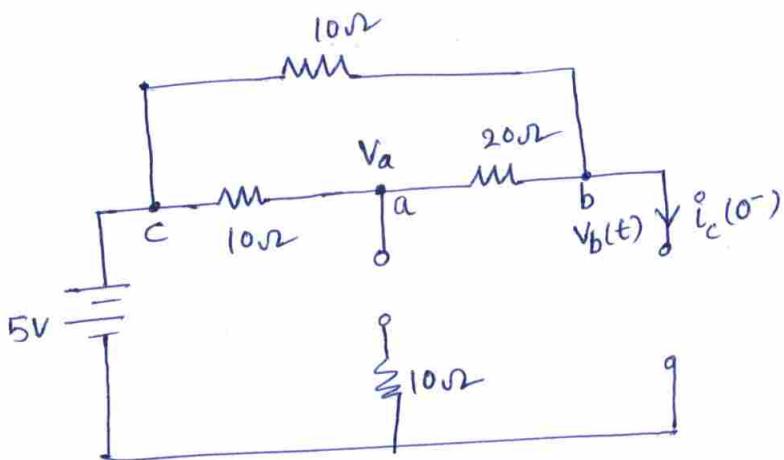( $C = \text{open}$ ,  $L = \text{short}$ ).



$$i_c(0^-) = 0 \text{ Amp.}$$

Using KCL, at node a and c

$$\frac{V_a - 5}{10} + \frac{V_a - V_b}{20} = 0 \rightarrow ①$$

$$\frac{5 - V_b}{10} + \frac{5 - V_a}{10} = 0 \rightarrow ②$$


On solving equations ① & ②

$$V_a = V_b = 5V.$$

$$\therefore V_a(0^-) = V_b(0^-) = 5V \quad \& \quad i_c(0^-) = 0A.$$

At  $t=0^+$ , the circuit is

At  $t = 0^+$ :

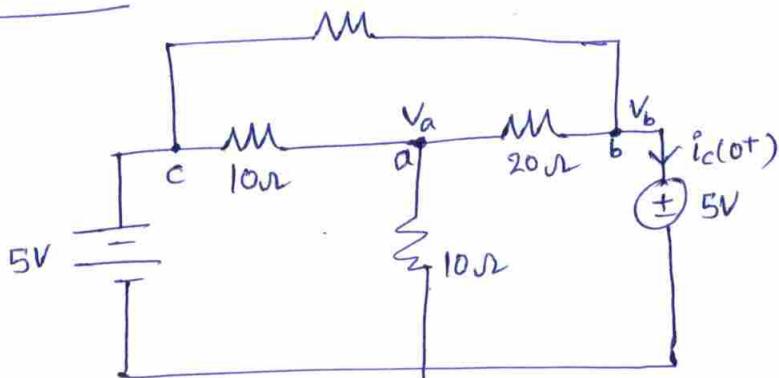

Use KCL at node a and b

$$V_b(0^+) = 5V.$$

$$\therefore i_c(0^+) = \frac{5-5}{10} + \frac{V_a-5}{20} \rightarrow ③$$


$$\frac{V_a}{10} + \frac{V_a-5}{10} + \frac{V_a-5}{20} = 0 \rightarrow ④$$

On solving equations ③ & ④, we get

$$\therefore V_a(0^+) = 3V$$

$$\therefore i_c(0^+) = -\frac{1}{10} \text{ Amp} = -0.1 \text{ Amp.}$$

At  $t = \infty$ :

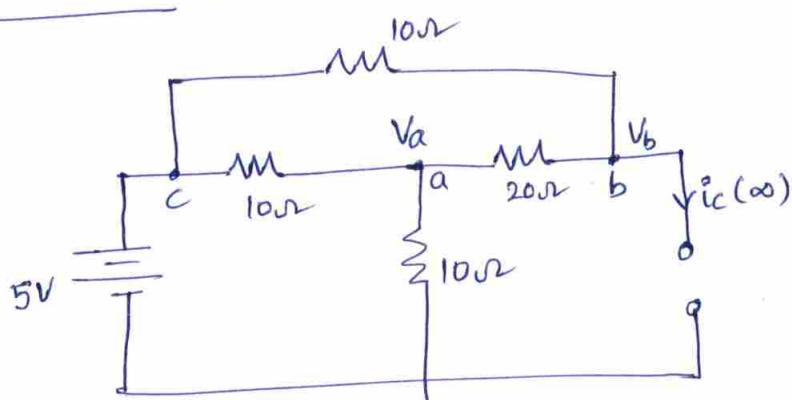

KCL at node a and c,

$$\frac{V_a - 5}{10} + \frac{V_a}{10} + \frac{V_a - V_b}{20} = 0 \rightarrow (5)$$

$$\frac{5 - V_b}{10} + \frac{5 - V_a}{10} = 0 \rightarrow (6)$$

Solving equations (5) & (6), we get

$$V_a(\infty) = \frac{20}{7} \text{ V}$$

$$V_b(\infty) = \frac{30}{7} \text{ V}$$

$$i_c(\infty) = 0 \text{ Amp.}$$

and

02. (b) (i) A voltage  $V(t) = 10\sin(\omega t)$  is applied to a series RLC circuit. At the resonant frequency of the circuit, the maximum voltage across the capacitor is 500 V. Bandwidth is 400 rad/sec and Impedance at resonance is  $100\Omega$ . Find the resonant frequency. Also find values of L&C of circuit. (12 M)

Sol:

Applied Voltage to the circuit

$$V_{\max} = 10 \text{ V}$$

$$V_{\text{rms}} = \frac{10}{\sqrt{2}} \text{ V} = 7.07 \text{ V}$$

Voltage across capacitor,

$$V_C = 500 \text{ V}$$

Magnification factor (or) Quality factor

$$Q = \frac{V_c}{V_{rms}} = \frac{500}{7.07} = 70.7$$

Band width = 400 rad/sec.

As we know that, 
$$Q = \frac{\omega_r}{BW}$$

where,  $\omega_r$  = Resonant frequency

$BW$  = Bandwidth

Substitute the given values of Bandwidth and  
Quality factor ( $Q$ ) in the above equation,

we get

$$70.7 = \frac{\omega_r}{400}$$

$$\Rightarrow \text{Resonant Frequency } (\omega_r) = 70.7 \times 400$$

$$\Rightarrow \boxed{\omega_r = 28280 \text{ rad/sec.}}$$

$$\therefore f_r = \frac{\omega_r}{2\pi} = \frac{28280}{2\pi} = 4499 \text{ Hz.}$$

$$BW = \frac{R}{L} \Rightarrow L = \frac{R}{BW} = \frac{100}{400} = 0.25 \text{ H.}$$


$$f_r = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{(2\pi f_r)^2 \times L} = 5 \text{nF.}$$

Thus,

$$\boxed{L = 0.25 \text{ H}}$$

$$\boxed{C = 5 \text{nF}}$$

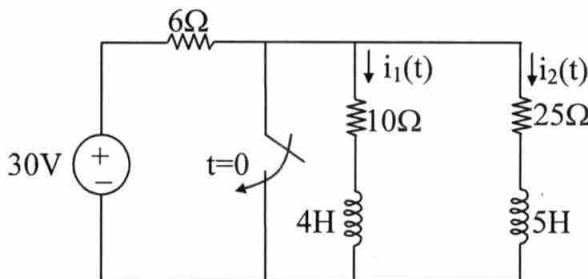(ii) Find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$  in the circuit shown below.




Candidates  
must not  
write on  
this margin

(8 M)

Sol:

Circuit at  $t < 0$ ,

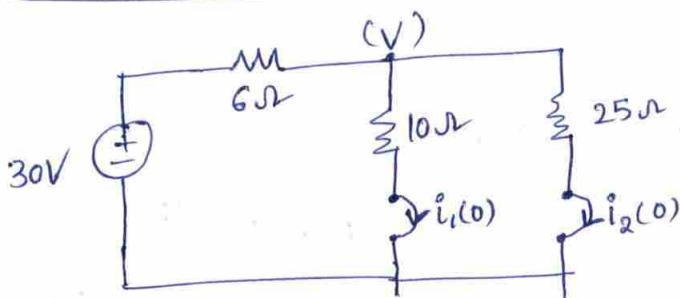

$$\text{By nodal analysis, } \frac{V-30}{6} + \frac{V}{10} + \frac{V}{25} = 0.$$

$$\Rightarrow V\left(\frac{1}{6} + \frac{1}{10} + \frac{1}{25}\right) = 5 \Rightarrow V = 16.3 \text{ Volts.}$$

$i_1(0^-) = 1.63 \text{ A}$
$i_2(0^-) = 0.652 \text{ A}$

from the circuit at  $t = \infty$

$$I_1(\infty) = 0 \text{ Amp.} \quad I_2(\infty) = 0 \text{ Amp.}$$

$$I(t) = I(\infty) + [I(0^+) - I(\infty)] \cdot e^{-t/\tau}$$

$$\text{Here } \tau_1 = \frac{4}{10} = \frac{2}{5} \text{ sec}$$

$$\tau_2 = \frac{5}{25} = \frac{1}{5} \text{ sec.}$$

$$\therefore i_1(t) = i_1(0^+) \cdot e^{-t/\tau_1} \Rightarrow i_1(t) = 1.63 e^{-2.5t} \text{ Amp.}$$

$$i_2(t) = i_2(0^+) \cdot e^{-t/\tau_2} \Rightarrow i_2(t) = 0.652 e^{-5t} \text{ Amp.}$$


Thus,

$i_1(t) = 1.63 e^{-2.5t} \text{ A}$
-------------------------------------

$i_2(t) = 0.652 e^{-5t} \text{ A}$
------------------------------------

02. (c)

(i)

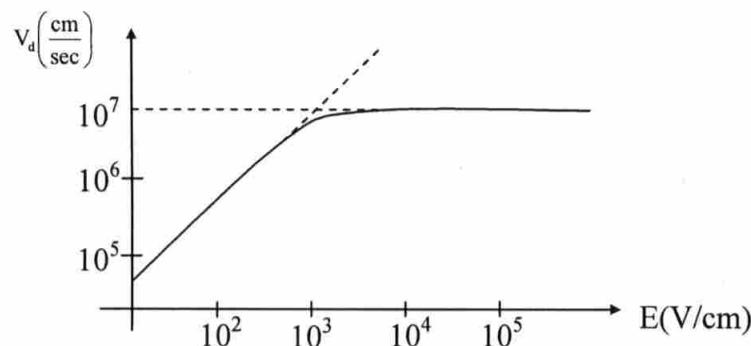

Candidates  
must not  
write on  
this margin

The above figure shows the graph between electric field (V/cm) and drift velocity  $\left(\frac{\text{cm}}{\text{sec}}\right)$ .

Refer the above figure for the below question.

A silicon bar  $1 \mu\text{m}$  long and  $100 \mu\text{m}^2$  in cross-section area is doped with  $10^{17}\text{cm}^{-3}$  phosphorus. Find the current at 300k with 10V applied voltage. **(10 M)**

Sol:

Given data

$$\begin{aligned}\text{Length, } l &= 1 \mu\text{m} \\ &= 10^{-4} \text{ cm.}\end{aligned}$$

$$\begin{aligned}\text{Area, } A &= 100 \mu\text{m}^2 = 100 \times (10^{-6})^2 \text{ m}^2 \\ &= 100 \times 10^{-12} \text{ m}^2 \\ &= 10^{-6} \text{ cm}^2\end{aligned}$$

$$\text{Applied Voltage, } V = 10 \text{ Volts}$$

$$\text{Donor concentration i.e } N_D = 10^{17} \text{ cm}^{-3}$$

$$\text{As we know, Electric field (E)} = \frac{V}{l}$$

$$\Rightarrow E = \frac{10}{10^{-4}}$$

$$\Rightarrow \boxed{E = 10^5 \text{ V/cm.}}$$

from the given graph we conclude that, with  $10^5 \text{ V/cm}$  electric field the sample is in Velocity Saturation region.

$$\therefore \text{Drift Velocity, } V_d = 10^7 \text{ cm/sec.}$$

As we know,

$$I = \sigma EA, \text{ where } \sigma = \text{Conductivity}$$

$E = \text{Electric Field}$

$A = \text{Area.}$

$$\Rightarrow I = nq\mu_n EA$$

$$\Rightarrow E = nqA V_d. \quad (\because V_d = \mu_n E)$$



$$\Rightarrow I = 1.6 \times 10^{-19} \times 10^{17} \times 10^{-6} \times 10^7$$

$$\Rightarrow I = 0.16 \text{ Amps.}$$

$\therefore$  Current at 300K with 10V applied

Voltage is,  $I = 0.16 \text{ A}$

(ii)

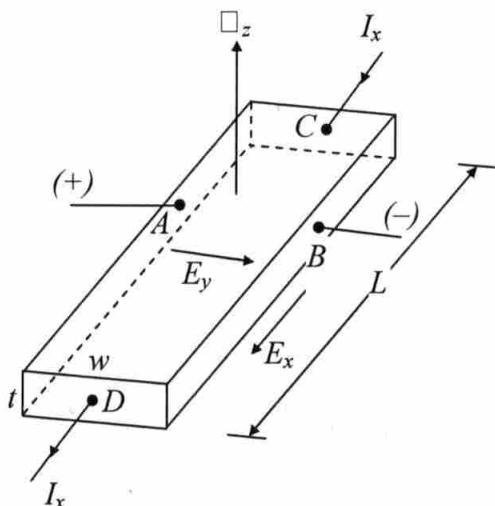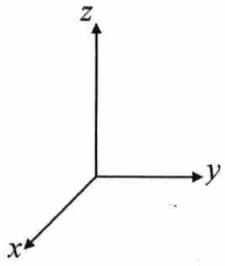Candidates  
must not  
write on  
this margin

Referring above figure, consider a semiconductor bar with  $W = 0.1\text{mm}$ ,  $t = 10\mu\text{m}$ , and  $L = 5\text{mm}$ . For magnetic flux density,  $B = 10^{-4}\text{wb/cm}^2$  in the direction shown and current of  $1\text{mA}$ , we have  $V_{AB} = -2\text{mV}$  and  $V_{CD} = 100\text{mV}$ . Find the type, concentration and mobility of the majority carrier.

(10 M)

Sol:

Given data

$$W = 0.1 \times 10^{-3} \text{ m}$$

$$= 0.1 \times 10^{-1} \text{ cm}$$

$$t = 10 \times 10^{-6} \text{ m} = 10 \times 10^{-4} = 10^{-3} \text{ cm.}$$

$$L = 5\text{mm} = 5 \times 10^{-3} \text{ m} = 5 \times 10^{-1} \text{ cm}$$

$$B = 10^{-4} \text{ wb/cm}^2$$

From the sign of  $V_{AB}$ , we can see that the majority carriers are electrons. So, the given

Specimen is n-type.

$$n_0 = \frac{I_x \cdot B_z}{q t (-V_{AB})} = \frac{10^{-3} \times 10^{-4}}{1.6 \times 10^{-19} \times 10^{-3} \times 2 \times 10^{-3}}$$

$$\Rightarrow n_0 = 3.125 \times 10^{17} \text{ cm}^{-3}$$

$$\text{Resistivity } (\rho) = \frac{R}{L/wt} = \frac{V_{CO}/I_x}{L/wt}$$

$$\Rightarrow \rho = \frac{0.1/10^{-3}}{0.5/(0.01 \times 10^{-3})}$$

$$\therefore \rho = 0.002 \text{ } (\Omega\text{-cm})$$

Mobility of electron is given as -

$$M_n = \frac{1}{\rho q n_0}$$

$$\Rightarrow M_n = \frac{1}{(0.002)(1.6 \times 10^{-19})(3.125 \times 10^{17})}$$


$$\Rightarrow M_n = 10,000 \frac{\text{cm}^2}{\text{V-sec}}$$

$\therefore$  Mobility of the majority carrier is

$$M_n = 10,000 \frac{\text{cm}^2}{\text{V-sec}}$$

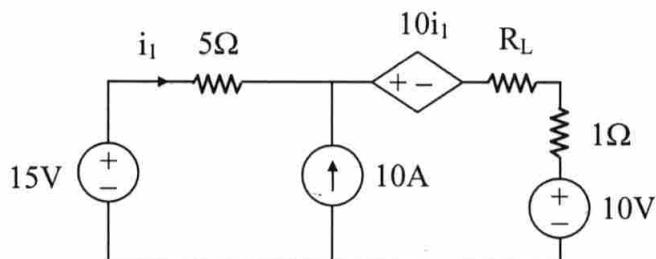03. (a)

For the network shown, determine  $R_L$  which will receive maximum power.



Candidates  
must not  
write on  
this margin

(10 M)


Sol:

Maximum power will be received by  $R_L$  when equivalent resistance of the network across  $R_L$  is equals to  $R_{Th}$ .

for this we need to find Thevenine resistance. For this we shall short all independent voltage sources & open all independent current sources.

Next we will place a voltage source of 1V in place of  $R_L$ . Then we will find I through this (Resistance) Source.

$$R_{Th} = \frac{1V}{I}$$

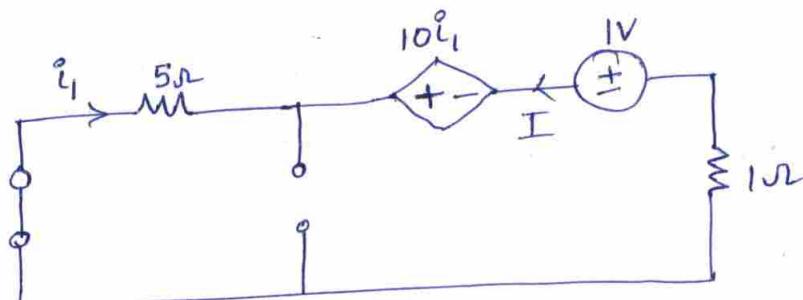

$$-I = i_1$$

$\therefore$  Use KVL,

$$-6I + 10i_1 = -1$$

$$-6(+I) + 10(-I) = -1$$

$$\Rightarrow 16I = 1 \Rightarrow I = \frac{1}{16} A$$

$$\therefore R_{th} = \frac{1}{I} = 16 \Omega$$


$\therefore$  For maximum power transfer

$$R_L = R_{th} = 16 \Omega$$
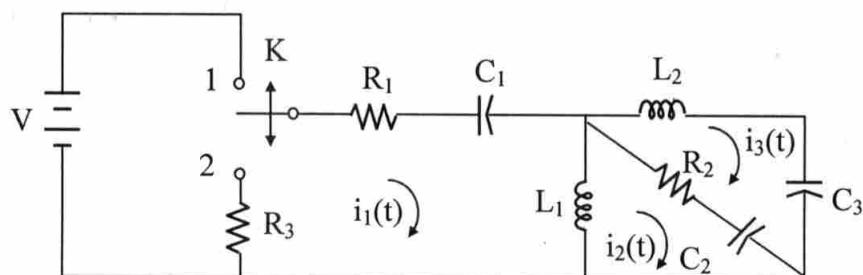
### 03. (b)

For the circuit shown, the switch K is moved from position 1 to position 2 at  $t = 0$ . At  $t < 0$  (steady state). K is at position 1.


$$\text{Show that } i_1(0^+) = i_2(0^+) = \frac{-V}{R_1 + R_2 + R_3}; i_3(0^+) = 0$$



(10 M)

Sol:

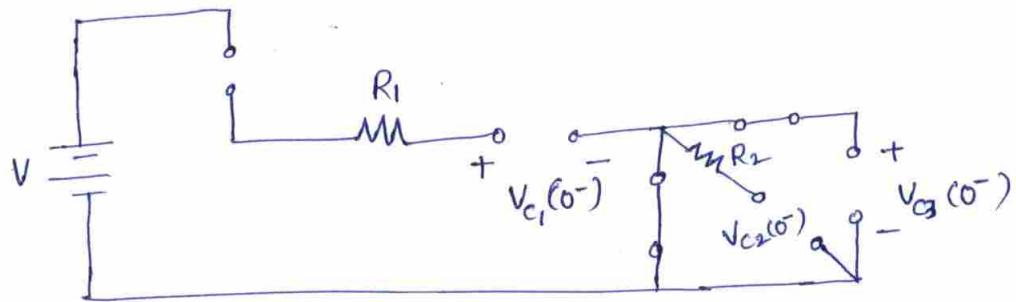
At  $t = 0^-$ , circuit is in steady state and switch K is in position 1 (capacitor: open; inductor: short).



$$\therefore V_{C1}(0^-) = V \text{ Volts}$$

$$V_{C2}(0^-) = V_{C3}(0^-) = 0$$

At  $t=0^+$

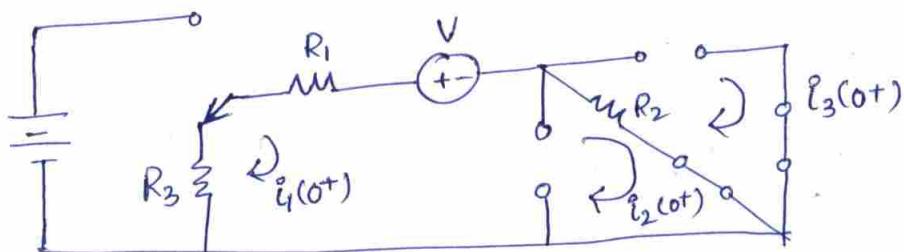

$$i_1(0^+) = i_2(0^+) ; i_3(0^+) = 0.$$


Using KVL,

$$-R_1 i_1(0^+) - V - R_2 i_2(0^+) - R_3 i_1(0^+) = 0$$

$$\therefore i_1(0^+) = i_2(0^+) = \frac{-V}{R_1 + R_2 + R_3}$$


03. (c)

Find current 'I' using Mesh Analysis

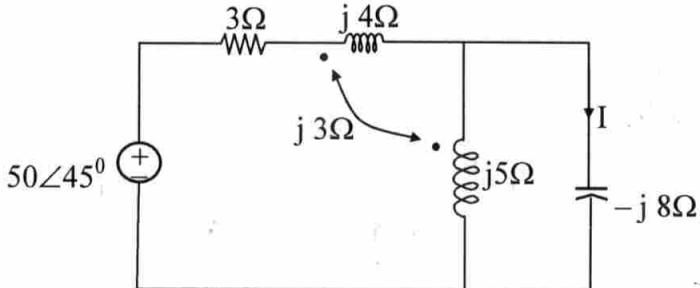

(10 M)

Sol:

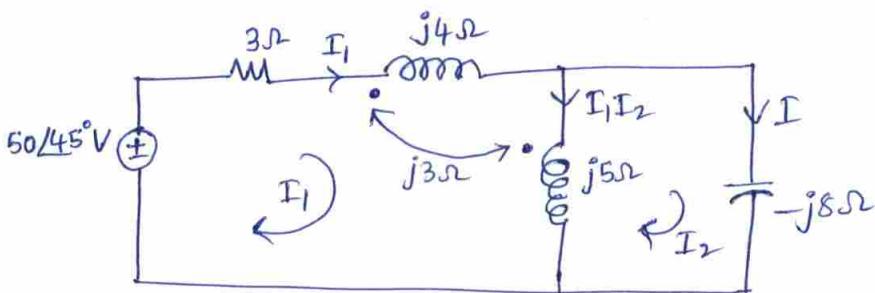

Mesh-(1) Equation :

$$- [50\angle 45^\circ] + (3+j4)I_1 + j5[I_1 - I_2] + j3[I_1 - I_2] + j3I_1 = 0$$

$$(3+j15)I_1 - j8I_2 = 50 \angle 45^\circ \rightarrow \textcircled{1}$$

Mesh-(2) Equation :

$$j5[I_2 - I_1] - j8I_2 - j3I_1 = 0$$

$$-j8I_1 - j3I_2 = 0$$

$$8I_1 + 3I_2 = 0 \rightarrow \textcircled{ii}$$

Solving  $\textcircled{1}$  &  $\textcircled{ii}$ , we get

$I = I_2 = 3.66 \angle -310.33^\circ \text{ A}$

Candidates  
must not  
write on  
this margin

- 03. (d)** A  $0.46 \mu\text{m}$  thick sample of GaAs is illuminated with monochromatic light of  $\text{h}\nu = 2\text{eV}$ . The absorption coefficient ' $\alpha$ ' is  $5 \times 10^4 \text{ cm}^{-1}$ . The power incident on the sample is  $10\text{mW}$ .
- (i) Find the total energy absorbed by the sample per second (J/s).
- (ii) Find the rate of excess thermal energy given up by the electrons to the lattice before recombination (J/s).

Candidates  
must not  
write on  
this margin

(8 + 2)M

Sol:

(i) The intensity of light transmitted through the sample of thickness is,  $I_t = I_0 e^{-\alpha l}$

Given data

$$I_0 = 10\text{mW}$$

$$= 10^{-2}\text{W}$$

$$l = 0.46\mu\text{m}$$

$$= 0.46 \times 10^{-4}\text{cm}$$

$$\alpha = 5 \times 10^4 \text{ cm}^{-1}$$

$$\therefore I_t = I_0 e^{-\alpha l}$$

$$\Rightarrow I_t = 10^{-2} \cdot e^{-[5 \times 10^4 \times 0.46 \times 10^{-4}]}$$

$$= 10^{-3}\text{W}$$

$$\Rightarrow I_t = 1\text{mW}$$

Thus the absorbed power is

$$10\text{mW} - 1\text{mW} = 9\text{mW} (\text{or}) 9 \times 10^{-3}\text{J/s}$$

(ii) The fraction of each photon energy unit which is converted to heat is

$$\frac{2 - 1.43}{2} = 0.285$$

Thus the amount of energy converted to heat per second is

$$0.285 \times 9 \times 10^{-3} = 2.57 \times 10^{-3} \text{ J/s}$$

03. (e) Draw the low frequency small signal model of FET and explain how FET is much more ideal amplifier than the conventional transistor at low frequencies ? (10 M)

Sol: The low frequency small signal model of FET has a Norton's output circuit with a dependent current generator whose current is proportional to the gate-to-source voltage.

The proportionality factor is the transconductance  $g_m$ , output resistance is  $r_d$ . The input resistance between gate and source is infinite, since it is assumed that the reverse biased gate takes no current. For the same reason the resistance between gate and drain is assumed to be infinite.

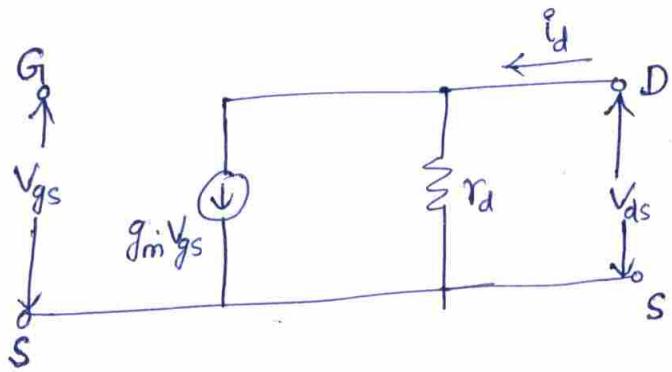


fig : Low frequency small - signal FET Model.

FET is a more ideal amplifier.

1. In a conventional transistor, current generator depends upon the input current, whereas in FET model the generator current depends upon the input Voltage.
2. There is no feedback at low frequencies from output to input in FET, whereas such feedback exists in conventional transistor through  $h_{fe}$ .
3. Input resistance of FET is almost infinite, compared to input resistance of conventional transistor. Hence, FET is a much more ideal amplifier than a conventional transistor at low frequencies.

03. (f)

Explain varactor diode. Give its equivalent circuit and mention its applications. (10 M)

Candidates  
must not  
write on  
this margin

Sol:

Diodes made especially based on the Variable-Voltage Capacitors are called Varactors, Vari caps (or) Volta caps. It is a type of diode designed to exploit the Voltage-dependent capacitance of a reverse biased pn-junction. If the Varactor diode reverse voltage is increased then the depletion region size increases. Hence by varying the reverse-bias of the Varactor diode, the capacitance be varied.

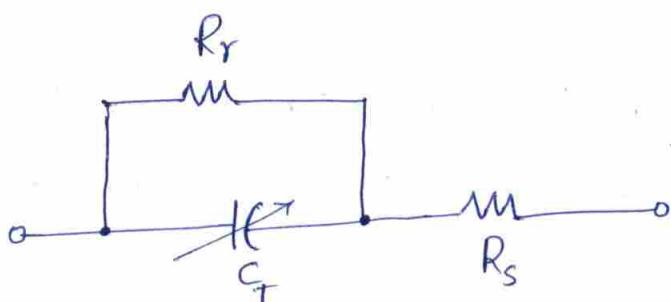


Fig. Circuit model of Varactor diode.



Fig: symbol.

The resistance  $R_s$ , represents the body (ohmic) series resistance of the diode. Typical values of  $C_f$  and  $R_s$  are  $20\text{pF}$  and  $8.5\Omega$  respectively at a reverse-bias of  $4V$ . The reverse diode resistance  $R_r$  shunting  $C_f$  is large ( $>1\text{M}\Omega$ ), and hence is usually neglected.

$$C_f = \frac{C_0}{\sqrt{V_{bi} + V_R}}$$

$C_0$  = constant


$V_{bi}$  = Built-in potential

$V_R$  = Reverse applied voltage

### Applications :


1. Voltage tuning of the LC resonant circuits in radars, televisions etc.
2. They are commonly used in voltage-controlled oscillators, parametric amplifiers, frequency multipliers, self-balancing bridge circuits and automatic frequency control circuits.

44. (a)

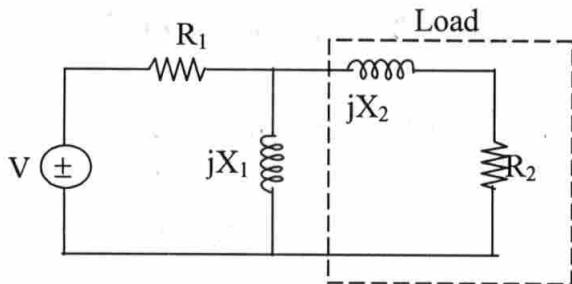(i) Find  $X_1$  and  $X_2$  in terms of  $R_1$  and  $R_2$  to give maximum power dissipation in  $R_2$ Candidates  
must not  
write on  
this margin

(10 M)

Sol:

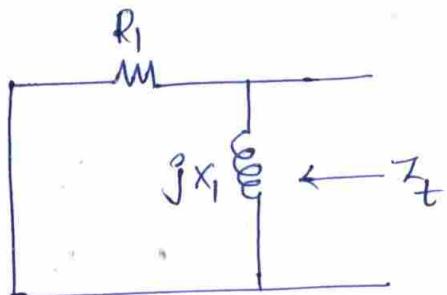

$$Z_t = \frac{R_1(jX_1)}{R_1 + jX_1} = \frac{R_1 X_1^2 + jR_1^2 X_1}{R_1^2 + X_1^2}$$

$$\therefore Z_L = Z_t^*$$

$$R_2 + jX_2 = \frac{R_1 X_1^2}{R_1^2 + X_1^2} - j \frac{R_1 X_1}{R_1^2 + X_1^2}$$

$$\text{So, } R_2 = \frac{R_1 X_1^2}{R_1^2 + X_1^2}$$

$$\text{Then } X_1 = \pm R_1 \sqrt{\frac{R_2}{R_1 - R_2}} \rightarrow ①$$

$$\text{Also } X_2 = - \frac{R_1^2 \cdot X_1}{R_1^2 + X_1^2} \rightarrow ②$$

Substitute ① in ②


$$\text{Then, } X_2 = \sqrt{R_2(R_1 - R_2)}$$

∴ The final Answer is :

$$X_1 = \pm R_1 \cdot \sqrt{\frac{R_2}{R_1 - R_2}}$$

$$X_2 = \sqrt{R_2(R_1 - R_2)}$$

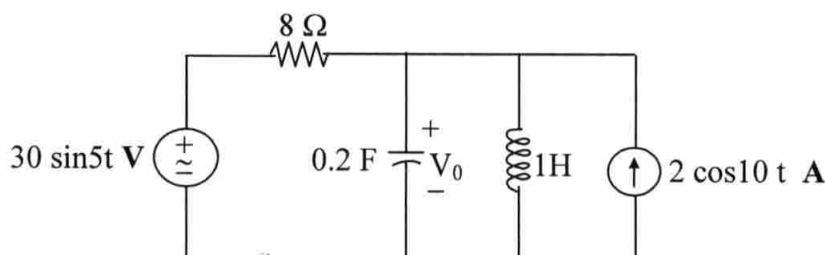(ii) In the circuit shown below, determine the value of  $V_0$ .




(10 M)

Sol:

By applying Super-position Theorem

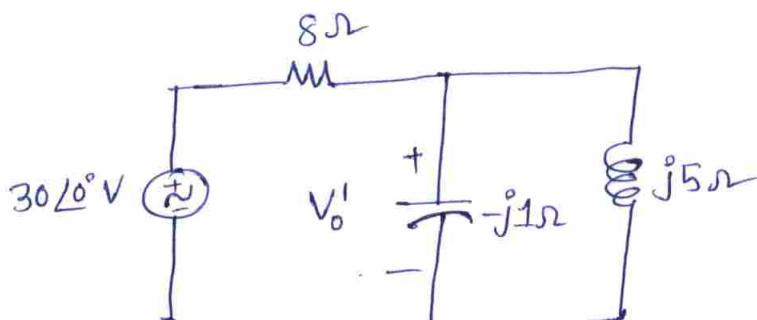Case -1 : When 'V' alone acting,  $V_o = V_o'$




Using Nodal Analysis,

$$V_o' = 4.631 \angle -81.12^\circ V$$

Case-2 : When 'Current source (I)' alone acting,

$$V_o = V_o''$$

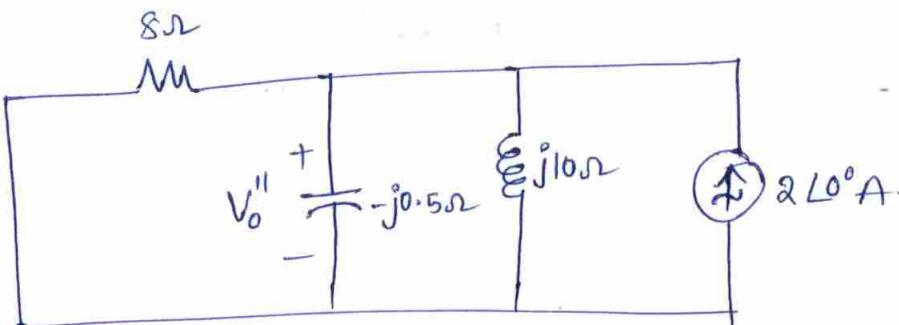

Using Nodal Analysis,

$$V_o'' = 1.051 \angle -86.24^\circ V$$


$$\therefore V_o = V_o' + V_o''$$

$$V_o = 4.631 \sin(5t - 81.12^\circ) + 1.05 \cos(10t - 86.24^\circ) V$$

Note :

Input sources are at different frequencies.

04. (b) (i)

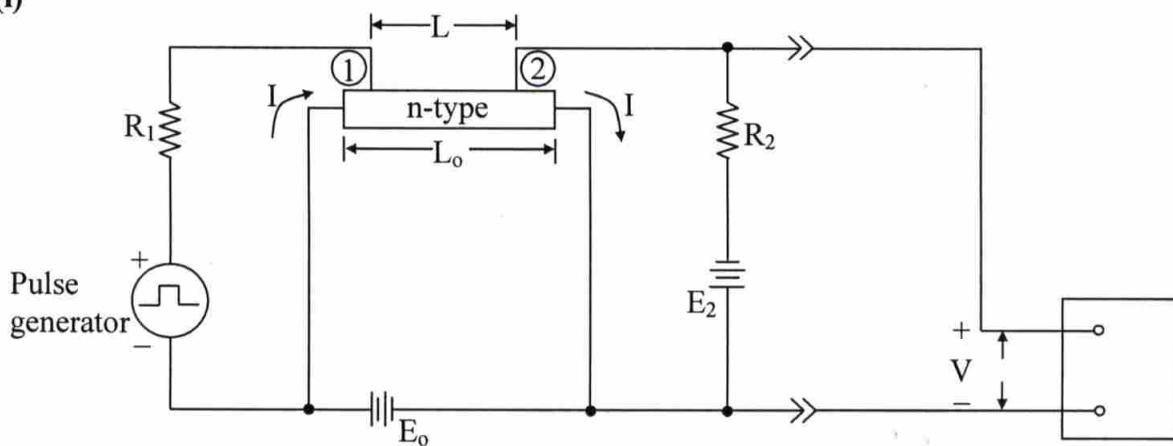Candidates  
must not  
write on  
this margin

An n-type 'Ge' sample is used in the experiment shown in the above figure. The length of the sample is 1 cm, and the probes (1) and (2) are separated by 0.95 cm. The battery voltage  $E_0$  is 2V. A pulse arrives at point (2) 0.25ms after injection at (1), the width of the pulse  $\Delta t$  is 117  $\mu$ s. Calculate the electron mobility. (8 M)

Sol:

Given data

$$L_0 = 1 \text{ cm}$$

$$L = 0.95 \text{ cm}$$

$$E_0 = 2 \text{ Volts}$$

$$\Delta t = 117 \text{ } \mu\text{sec.}$$

As we know ,

$$\text{mobility} = \frac{\text{Drift Velocity}}{\text{Electric field}}$$

(or)

$$\boxed{\mu_n = \frac{V_d}{E}}$$

$$\Rightarrow \mu_n = \frac{L / 0.25 \text{ ms}}{E_0 / L_0}$$

$$\Rightarrow \mu_n = \frac{0.95 \text{ cm} / (0.25 \times 10^{-3})}{2/1 \text{ cm}} = 1900 \frac{\text{cm}^2}{\text{V-sec}}$$

$\therefore$  Mobility of electron is,

$$\boxed{\mu_n = 1900 \frac{\text{cm}^2}{\text{V-sec}}}$$

- (ii) An n-type silicon bar of width 10mm and height 5mm with majority carrier concentration of  $10^{20} \text{ cm}^{-3}$  is placed in a transverse magnetic field of  $2.16 \frac{\text{wb}}{\text{m}^2}$ . Calculate the magnitude of the Hall voltage developed if an electric field of 6 V/cm is applied across the specimen in perpendicular to the magnetic field ( $\mu_n = 1500 \text{ cm}^2/\text{V-sec}$ ). (12 M)

Sol:

Given data,

$$\begin{aligned} \text{Width, } w &= 10 \text{ mm} \\ &= 10 \times 10^{-3} \text{ m} \\ &= 10 \times 10^{-1} \text{ cm} \end{aligned}$$

$$\begin{aligned} \text{Magnetic field, } B &= 2.16 \text{ wb/m}^2 \\ &= 2.16 \times 10^{-4} \frac{\text{wb}}{\text{cm}^2} \end{aligned}$$

$$\text{Mobility, } \mu_n = 1500 \frac{\text{cm}^2}{\text{V-sec}}$$

$$\text{Electric field, } E = 6 \frac{\text{V}}{\text{cm}}$$

$$\text{Height, } d = 5\text{mm} = 5 \times 10^{-3} \text{ cm}$$

- As we know,

$$\leftarrow \text{Hall Voltage, } V_H = \frac{BI}{\rho w}$$

$$\Rightarrow V_H = \frac{BJA}{qN_D \cdot w}, (\because I = J \cdot A, \rho = qN_D)$$

$$\Rightarrow V_H = \frac{B(\sigma E)(dxw)}{qN_D \times w}, [\because J = \sigma E, A = dxw]$$

$$\Rightarrow V_H = \frac{B(N_D q \mu_0 E)(dxw)}{qN_D \times w}, [\because \sigma = qN_D \mu_0]$$

$$\Rightarrow V_H = B \mu_0 E d$$

$$\Rightarrow V_H = (2.16 \frac{\text{wb}}{\text{m}^2}) \times (1500 \frac{\text{cm}^2}{\text{v-sec}}) \times (6 \frac{\text{V}}{\text{cm}}) \times (0.5 \text{cm})$$

$$\Rightarrow V_H = (2.16 \times 10^{-4} \frac{\text{wb}}{\text{cm}^2}) \times (1500 \frac{\text{cm}^2}{\text{v-sec}}) \times (6 \frac{\text{V}}{\text{cm}}) \times (0.5 \text{cm})$$

$$\Rightarrow V_H = 0.972 \text{ Volts.}$$

$\therefore$  Hall voltage is given as

$$V_H = 0.972 \text{ Volts}$$


04. (c)

For the circuit given, draw

(i) Thevenin's equivalent circuit at a - a'

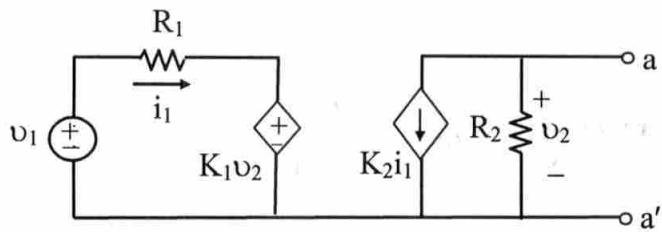(ii) Norton's equivalent circuit at a - a'


Candidates  
must not  
write on  
this margin



(12 + 8)M

Sol:

(i)

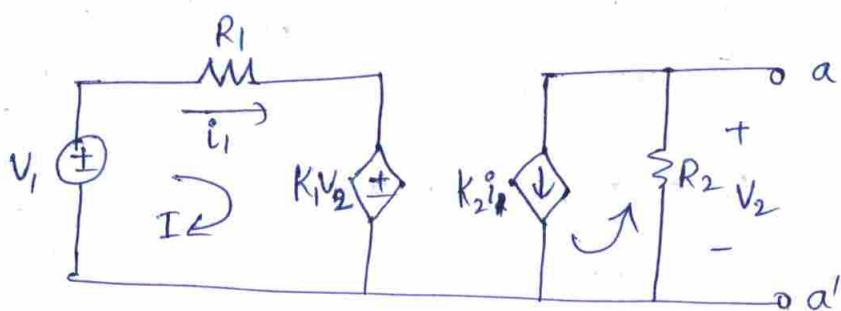

In loop I, using KVL

$$V_1 = i_1 \cdot R_1 + K_1 V_2 \rightarrow ①$$

Voltage across  $R_2$  is,  $V_2 = -K_2 \cdot i_1 \cdot R_2$

For Thevenin Voltage  $V_{th}$  across a-a',

$$V_{th} = V_2 = -K_2 \cdot i_1 \cdot R_2$$


$$i_1 = -\frac{V_{th}}{K_2 \cdot R_2} \rightarrow ②$$

Substitute eq. ② in eq. ①

$$V_1 + R_1 \left( \frac{V_{th}}{K_2 \cdot R_2} \right) - K_1 \cdot V_{th} = 0$$

$$\therefore V_{th} = \frac{K_2 \cdot R_2 \cdot V_1}{K_1 \cdot K_2 \cdot R_2 - R_1}$$

For  $Z_{th}$  across  $a-a'$ :

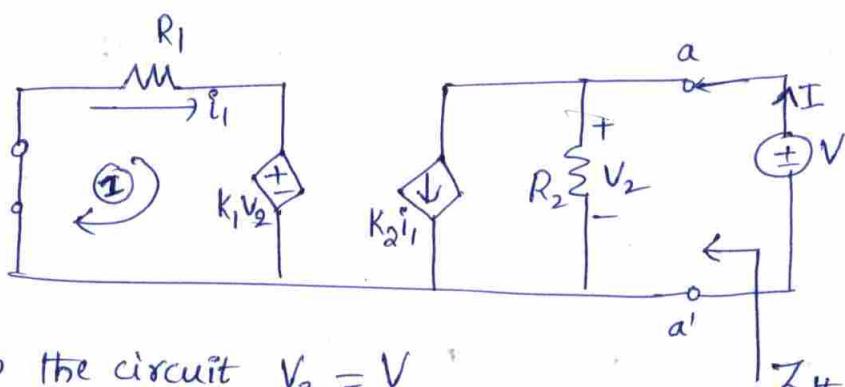

From the circuit  $V_2 = V$

From loop ①, use KVL

$$-R_1 i_1 - K_1 V_2 = 0 \Rightarrow i_1 = -\frac{K_1 V_2}{R_1} \rightarrow ③$$


$$\text{Using KCL, Current}(I) = \frac{V_2}{R_2} + K_2 i_1 \rightarrow ④$$

Substitute eq. ③ in eq. ④


$$I = \frac{V_2}{R_2} + K_2 \left[ -\frac{K_1 V_2}{R_1} \right]$$

$$\therefore \frac{V_2}{I} = \frac{V}{I} = Z_{th} = \frac{R_1 R_2}{R_1 - K_1 K_2 R_2}$$

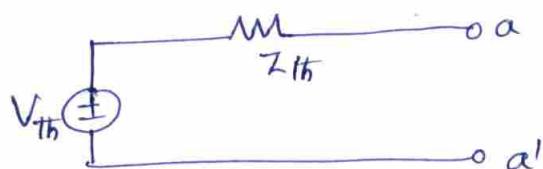$\therefore$  Thevenin Equivalent is given as



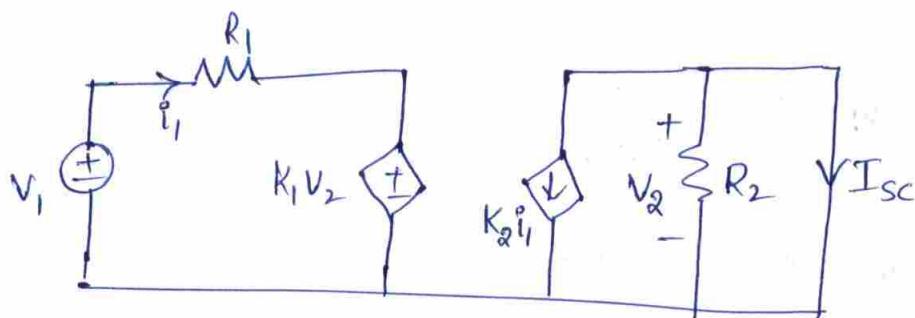
(ii) For Norton's equivalent, find  $I_{sc}$  through  $a-a'$



From above circuit, we can simply say that

$$V_2 = 0$$


$$\therefore K_1 V_2 = 0.$$

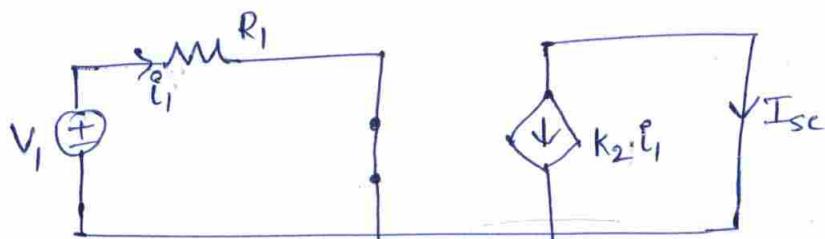

$$i_1 = \frac{V_1}{R_1} ; I_{sc} = -K_2 \cdot i_1$$

$$\therefore I_{sc} = -\frac{K_2 V_1}{R_1}$$

Norton's Equivalent is given as,

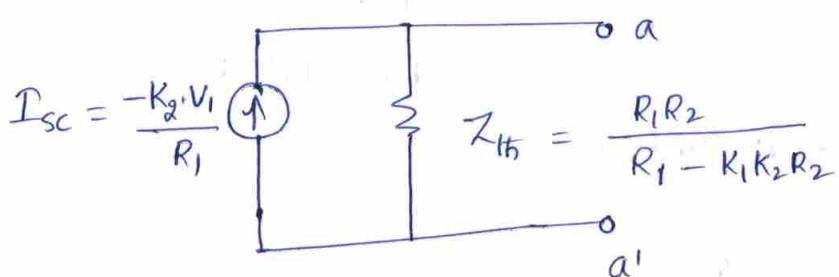

**SECTION - B**

Candidates  
must not  
write on  
this margin

**05. (a)**

A series circuit consist of two pure elements has the following current and voltage  
 $V = 100 \sin(2000t + 50^\circ) V$

$$i = 20 \cos(2000t + 20^\circ) A$$

Find the elements and their values in the circuit ?

(12 M)

Sol:

We can write ,

$$i = 20 \sin(2000t + 20^\circ + 90^\circ) \quad (\because \sin(\theta + 90^\circ) = \cos\theta)$$

$$\therefore i = 20 \sin(2000t + 110^\circ) A.$$

$\therefore$  Current leads voltage by  $110^\circ - 50^\circ = 60^\circ$ .

And the circuit must consists of resistance &  
Capacitance.

$$\tan\theta = \frac{1}{\omega CR}$$

$$\therefore \frac{1}{\omega C} = R \cdot \tan 60^\circ = 1.73 R.$$

$$Z = \frac{V_m}{I_m} = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{100}{20} = 5$$

$$\Rightarrow 5 = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$\Rightarrow R\sqrt{1+(1.73)^2} = \frac{100}{20} = 5$$


$$\Rightarrow R = \frac{5}{\sqrt{1 + (1.73)^2}}$$

$$\therefore \boxed{R = 2.5 \Omega}$$

and Capacitance ( $C$ )  $= \frac{1}{\omega(1.73R)} = 115.6 \mu F$ .


$$\therefore \boxed{C = 115.6 \mu F}$$

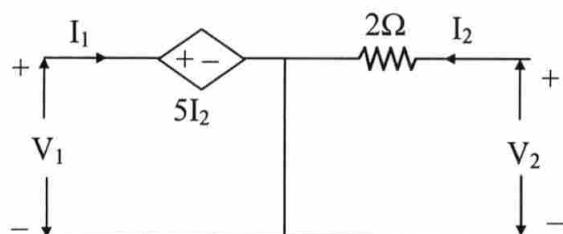05. (b) Find Y and Z parameters for the following circuit.



(12 M)

Sol:

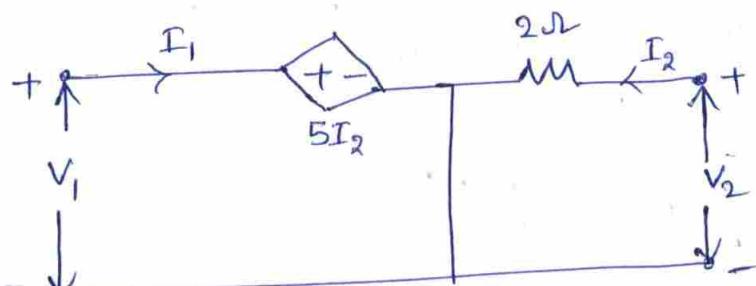

For two loops, write KVL

$$V_1 - 5I_2 = 0$$

$$V_2 - 2I_2 = 0$$

$$\therefore V_1 = (0)I_1 + 5I_2$$

$$V_2 = (0)I_1 + 2I_2$$

On comparing with,

$$V_1 = Z_{11} \cdot I_1 + Z_{12} \cdot I_2$$

$$V_2 = Z_{21} \cdot I_1 + Z_{22} \cdot I_2$$

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 0 & 5 \\ 0 & 2 \end{bmatrix}$$

$$Y\text{-Parameter} = [Y] = [Z]^{-1}$$

$$\Rightarrow [Y] = \frac{1}{|Z|} \begin{bmatrix} 2 & -5 \\ 0 & 0 \end{bmatrix}$$

Here  $|Z| = 0$ , so

$$[Y] = \begin{bmatrix} \infty & \infty \\ \infty & \infty \end{bmatrix}$$

$\therefore Y$ -parameters are undefined.

05. (c)


Derive the transfer function  $H(s) = \frac{V_o(s)}{V_i(s)}$  of series RLC circuit find the quality factor

when the transfer function is  $H(s) = \frac{10^6}{s^2 + 20s + 10^6}$  (12 M)

Candidates  
must not  
write on  
this margin

Sol:

Given series RLC circuit,

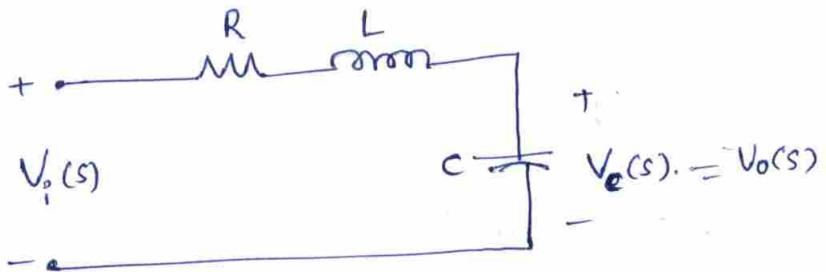

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{cs}}{R + LS + \frac{1}{sc}} = \frac{1}{Lcs^2 + RCS + 1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Compare  $H(s) = \frac{10^6}{s^2 + 20s + 10^6}$  with the above

equation ,

$$\therefore \frac{1}{LC} = 10^6 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 10^3 \text{ rad/sec}$$

$$\frac{R}{L} = 20$$

$$\therefore Q = \frac{\omega_0 \cdot L}{R} = \frac{10^3}{20} = 50.$$

From the given transfer function of Series RLC Circuit, the Quality factor is given as —


$$Q = 50$$

05. (d)

For the diode - resistance circuit in the figure, the diode cut-in voltage is 0.6 and voltage drop across a conducting diode is 0.7 V.

Calculate  $V_o$  and indicate the state of each diode for

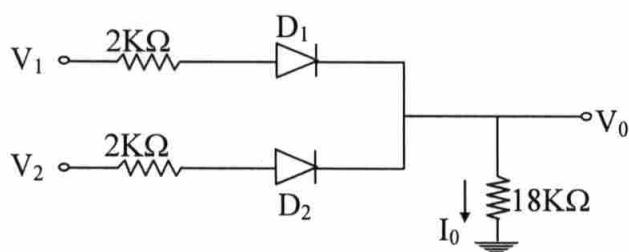- i)  $V_1 = 10 \text{ V}, V_2 = 0 \text{ V}$
- ii)  $V_1 = 10 \text{ V}, V_2 = 5 \text{ V}$
- iii)  $V_1 = V_2 = 5 \text{ V}$



(4 + 4 + 4) M

Sol:

(i)  $V_1 = 10 \text{ V}, V_2 = 0 \text{ V}$ .

$D_1$  would conduct.

$$I_0 = \frac{10 - 0.7}{(2+18) \text{ k}\Omega} = 0.465 \text{ mA}$$

$$V_0 = 0.465 \times 18 = 8.37 \text{ V.}$$

So  $D_1$  is ON and  $D_2$  is OFF.

(ii)  $V_1 = 10 \text{ V} ; V_2 = 5 \text{ V}$

Assume that  $D_1$  only conducts, Then as per part(i)

$$V_0 = 8.37 \text{ V.}$$

$$V_2 - V_0 = 5 - 8.37 = -3.37 \text{ V.}$$

So  $D_2$  does not conduct as assumed.


$$\therefore V_0 = 8.37 \text{ V.}$$

So,  $D_1$  is ON and  $D_2$  is OFF.

(iii)  $V_1 = V_2 = 5 \text{ V.}$

Considering that  $D_1, D_2$  both conduct and Output Voltage is  $V_0$ .

$$\text{Then } I_{D_1} + I_{D_2} = I_0$$

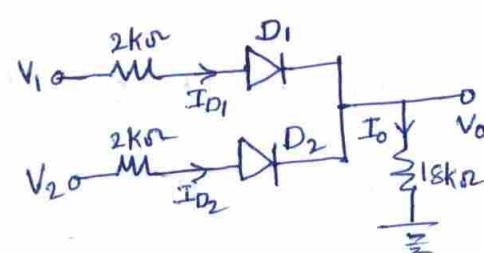

$$\text{Here, } I_{D_1} = \frac{5 - 0.7 - V_0}{2k\Omega} = \frac{(4.3 - V_0)}{2k\Omega}$$

Similarly,

$$I_{D_2} = \frac{5 - 0.7 - V_0}{2k\Omega} = \frac{4.3 - V_0}{2}$$

$$\therefore I_{D_1} = I_{D_2}$$

$$I_O = I_{D_1} + I_{D_2} = 4.3 - V_0$$

$$\text{But } I_O = \frac{V_0}{18 \times 10^3} \Rightarrow 4.3V - V_0 = \frac{V_0}{18 \times 10^3}$$

$$\Rightarrow V_0 = 4.3V$$

$$V_1 - V_0 = V_2 - V_0 = 5 - 4.3 = 0.7V > 0.6V$$

$\therefore$  Our assumption is correct i.e both diodes are conduct.


Hence  $V_0 = 4.3V$ .

So, both  $D_1$  &  $D_2$  are ON.

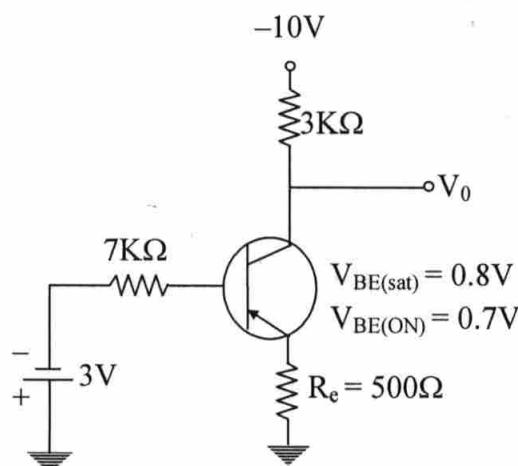05. (e)

For the circuit shown, assume  $\beta = 100$ .

- Find if the silicon Transistor is in cut-off, saturation or in active region.
- Find  $V_o$ .
- Find the minimum value of the resistor that should be added at emitter for which the transistor operates in the active region.



(5 + 2 + 5)M

Sol:

(i)

By KVL

$$-500 \times I_E - 0.7 - 7 \times 10^3 \times I_B + 3 = 0$$

$$\Rightarrow 7 \times 10^3 I_B + 500 \times 10 I_B = 2.3$$

$$\Rightarrow I_B = \frac{2.3}{7 \times 10^3 + 50.5 \times 10^3}$$

$$\Rightarrow I_B = \frac{2.3}{57.5 \times 10^3} = 40 \mu A$$

$$\therefore \beta_{dc} I_B = 4 mA$$

$$I_{c(sat)} = \frac{10 - 0.2}{3.5 \times 10^3} = \frac{9.8}{3.5 \times 10^3} = 2.8 mA$$

$\therefore$  As  $\beta_{dc} I_B > I_{c(sat)}$ , So Transistor is in

Saturation mode.


(ii)

$$V_o = V_{CE, sat} + I_E R_e = -0.2 + (-2.8 \times 0.5) \approx -1.6 V$$

$$\therefore \boxed{V_o = -1.6 V}$$

(iii)

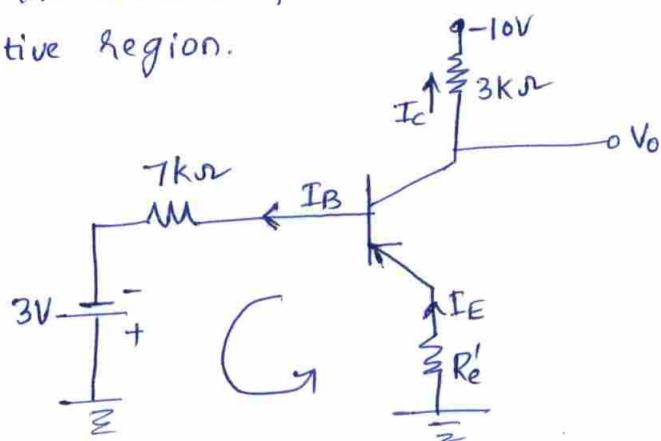Let us consider, the resistor  $R'_e$  that should be added at the emitter for which the transistor operates in active region.



By KVL,

$$-I_E \cdot R'_e - 0.7 - 7 \times 10^3 \cdot I_B + 3 = 0$$

$$\Rightarrow I_E \cdot R'_e + (10 \times 7) \cdot I_B = 2.3$$

$$\Rightarrow (1+\beta) I_B \cdot R'_e + (7 \times 10^3) I_B = 2.3$$

$$\Rightarrow I_B = \frac{2.3}{101 R'_e + (7 \times 10^3)}$$

$$\therefore I_C = \beta I_B = \frac{2.3 \times 100}{101 R'_e + 7 \times 10^3}$$

$$I_E = (1+\beta) I_B = \frac{2.3 \times 101}{101 R'_e + 7 \times 10^3}$$

By KVL,

$$-I_E \cdot R'_e - V_{EC} - I_C \times 3 \times 10^3 + 10 = 0$$

$$\Rightarrow V_{EC} = 10 - I_E \cdot R'_e - 3 \times 10^3 \cdot I_C$$

$\therefore$  for the transistor to be operate in active region,

$$V_{EC} > 0.2$$

$$\Rightarrow 10 - I_E \cdot R'_e - 3 \times 10^3 I_C > 0.2$$

$$\Rightarrow \frac{2.3 \times 101 R'_e}{101 R'_e + 7 \times 10^3} + \frac{3 \times 10^3 \times 2.3 \times 100}{101 R'_e + 7 \times 10^3} < 9.8$$

$$\Rightarrow (690 - 68.6) \times 10^3 < (989.6 - 232.3) R'_e$$

$$\Rightarrow R'_e > 820.54 \Omega$$

$$\Rightarrow R'_{e(\text{minimum})} = 821 \Omega$$

Since  $500\Omega$  resistor is already present at emitter,


$\therefore$  The minimum value of resistor to be added at emitter is  $821 - 500 = 321 \Omega$ .

06. (a)

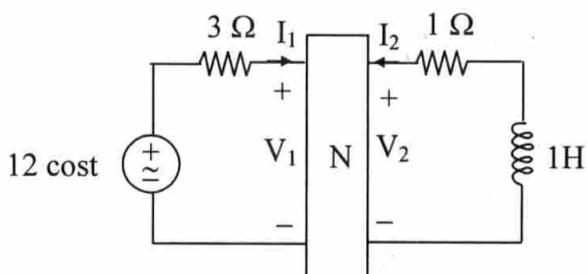(i) The Z-parameters of a two-port network 'N' are given by,

$$Z_{11} = \left[ 2s + \frac{1}{s} \right], Z_{12} = Z_{21} = 2s, Z_{22} = (2s + 4)$$


Find the T-equivalent of Network N, If network N is connected to a source and a load as shown in figure by its T-equivalent, then find  $I_1$ ,  $I_2$ ,  $V_1$  &  $V_2$ .



(15 M)

Sol:

T-Network

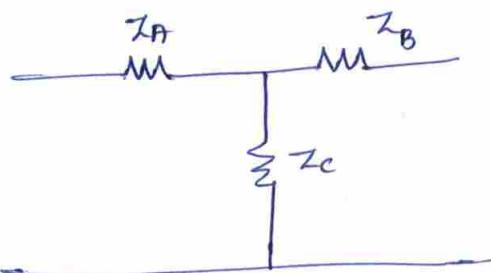

$$Z_A = Z_{11} - Z_{12} = \frac{1}{s}$$

$$Z_B = Z_{22} - Z_{21} = 4$$

$$Z_C = Z_{12} = Z_{21} = 2s.$$

$$\therefore s = j\omega = j1\text{ rad/s}$$

$$\therefore \omega = 1, \text{ from source}$$


$$Z_A = -j1\text{ rad/s}$$

$$Z_B = 4\text{ rad/s}$$

$$Z_C = +j2\text{ rad/s}$$

Candidates  
must not  
write on  
this margin

So, the total Network become

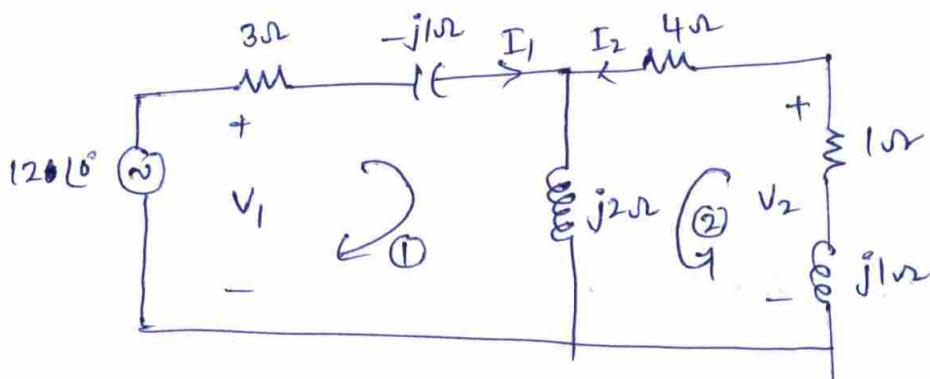

By applying mesh analysis in the above circuit  
KVL in loop ① ,

$$3I_1 - jI_1 + j2(I_1 + I_2) = 12$$

$$(3-j+2j)I_1 + j \cdot 2 \cdot I_2 = 12$$

$$(3+j)I_1 + j2I_2 = 12 \rightarrow ①$$

KVL in loop ②

$$(j+1+j)I_2 + j2(I_1 + I_2) = 0$$


$$\Rightarrow 2jI_1 + (4+j)I_2 = 0 \rightarrow ②$$

Solving ① & ② we get

$$\boxed{\begin{aligned} I_1 &= 3.29 \angle -10.2^\circ \text{ A} \\ I_2 &= 1.13 \angle -131.2^\circ \text{ A} \end{aligned}}$$



$$\begin{aligned} V_1 &= 12 - 3I_1 \Rightarrow \boxed{V_1 = 2.88 \angle 37.5^\circ \text{ Volts}} \\ V_2 &= (1+j)(-I_2) \Rightarrow \boxed{V_2 = 1.6 \angle 93.8^\circ \text{ Volts}} \end{aligned}$$

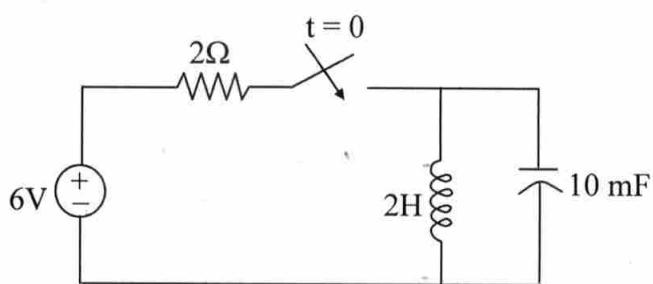(ii) Draw the Dual of the circuit shown below



(5 M)

Sol: Steps of Dual import from material

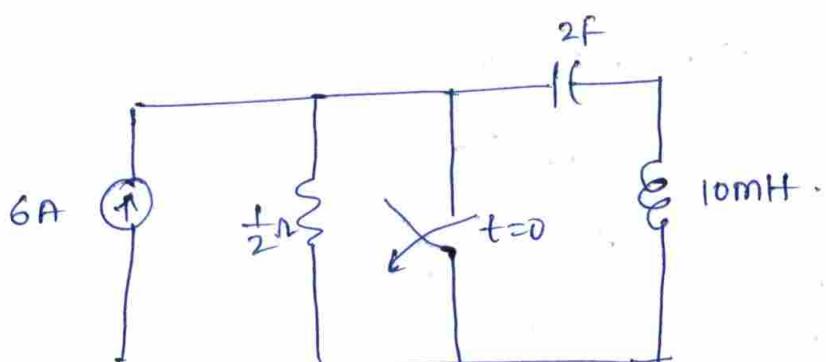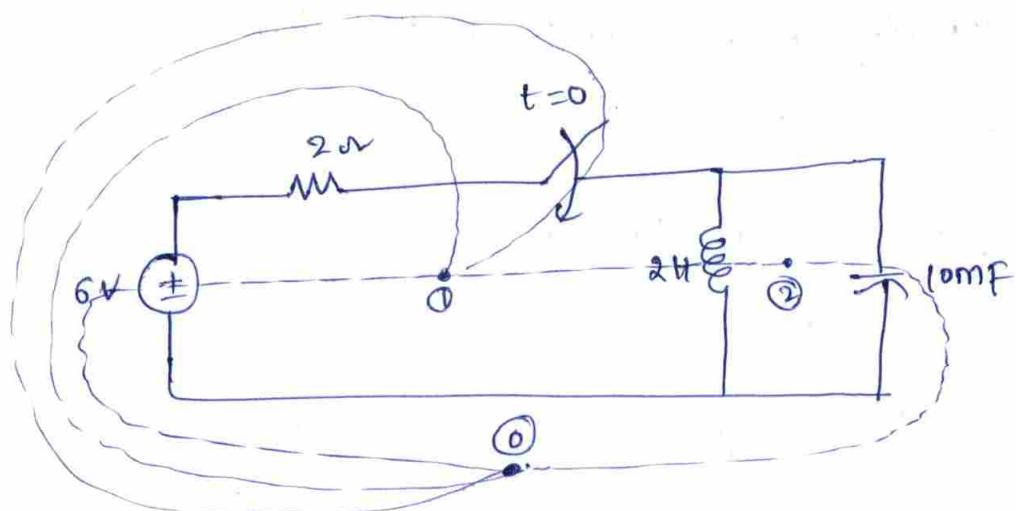


06. (b) (i) Two loads connected in parallel are respectively 2kW at a power factor of 0.75 leading and 4 kW at power factor of 0.95 lagging. Calculate the combined power factor of the two loads. Find the complex power supplied by the source.

(10 M)

Candidates  
must not  
write on  
this margin

Sol:

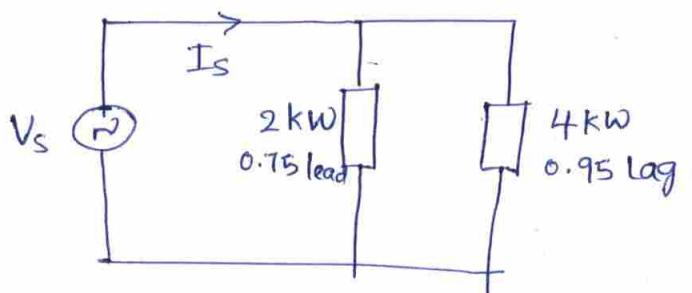

$$P_1 = 2 \text{ kW}, P_2 = 4 \text{ kW}, P_T = 6 \text{ kW}$$

$$P = S \cos\phi \Rightarrow S_1 = \frac{P_1}{\cos\phi_1} = \frac{2000}{0.75} = 2666.67 \text{ VA}$$

$$\therefore S_1 = 2666.67 \text{ VA}$$

$$\Rightarrow S_2 = \frac{P_2}{\cos\phi_2} = \frac{4000}{0.95} = 4210.52 \text{ VA}$$

$$\therefore S_2 = 4210.52 \text{ VA}$$

$$|S| = \sqrt{P^2 + Q^2}$$

$$\Rightarrow Q_1 = \sqrt{S_1^2 - P_1^2} = \sqrt{(2666.67)^2 - (2000)^2}$$

$$\therefore Q_1 = 1763 \text{ lead.}$$

$$\text{Similarly, } Q_2 = \sqrt{S_2^2 - P_2^2} = \sqrt{(4210.52)^2 - (4000)^2}$$

$$\Rightarrow Q_2 = 1314.7 \text{ lag.}$$

$$\therefore \boxed{Q_2 = 1314.7 \text{ lag.}}$$

$$S_1 = 2000 - j1763$$

$$S_2 = 4000 + j1314.7$$

$$\boxed{S_T = 6000 - j448.3}$$

$$\cos\phi = \frac{P_T}{S_T} = \frac{6000}{\sqrt{(6000)^2 + (448.3)^2}}$$

$$\Rightarrow \cos\phi = 0.9972, \text{ lead.}$$

$$\therefore \boxed{\cos\phi = 0.9972 \text{ lead.}}$$

- (ii) Consider a series-parallel circuit as shown calculate current through each resistor, the voltage across each resistor and voltage at each node of circuit.

Candidates  
must not  
write on  
this margin

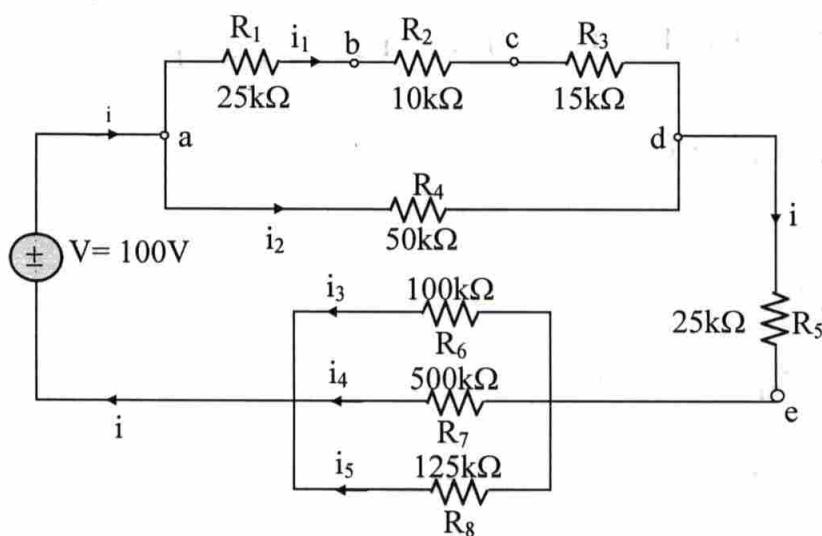


Figure: Series parallel circuit

(10 M)

Sol:

The equivalent resistance of

$$R_1, R_2 \text{ & } R_3 \text{ & } R_4 \text{ is } (50||50) = 25\text{k}\Omega$$

$$R_1, R_2 \text{ & } R_3 \text{ is } (25+10+15) = 50\text{k}\Omega$$

$$R_6, R_7, R_8 \text{ is } (100||500||125) = 50\text{k}\Omega$$

$$\text{Since } R_1 + R_2 + R_3 = R_4, \text{ we have } i_1 = i_2.$$

$$\therefore R_{\text{eq}} = (25+25+50)\text{k}\Omega = 100\text{k}\Omega$$

$$i = \frac{V}{R_{\text{eq}}} = 1\text{mA}$$

$$\text{Hence } i_1 = 0.5\text{mA} = i_2$$

To compute (calculate) the values of voltage across resistances  $R_1, R_2, R_3, R_4, R_5$  and  $R_6$

$$V_{R_1} = R_1 \times i_1 = 12.5 \text{ V}$$

Similarly,

$$V_{R_2} = 5 \text{ V}$$

$$V_{R_3} = 7.5 \text{ V}$$

$$V_{R_4} = 25 \text{ V}$$

$$V_{R_5} = R_5 \times i = 25 \text{ V}$$

$$i_3 = \frac{(100 - 25 - 25) \text{ V}}{100 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$i_4 = \frac{50 \text{ V}}{500 \text{ k}\Omega} = 0.1 \text{ mA}$$

$$i_5 = \frac{50 \text{ V}}{125 \text{ k}\Omega} = 0.4 \text{ mA}$$

$$\text{Now, } V_b = V_a - V_{R_1} = 100 - 12.5 = 87.5 \text{ V}$$

Similarly,

$$V_c = 82.5 \text{ V}, \quad V_d = 75 \text{ V}, \quad V_e = 50 \text{ V}$$

Thus,

$i_1 = i_2 = 0.5 \text{ mA}$
$i_3 = 0.5 \text{ mA}$
$i_4 = 0.1 \text{ mA}$
$i_5 = 0.4 \text{ mA}$

$V_{R_1} = 12.5 \text{ V}$
$V_{R_2} = 5 \text{ V}$
$V_{R_3} = 7.5 \text{ V}$
$V_{R_4} = 25 \text{ V}$
$V_{R_5} = 25 \text{ V}$

06. (c) (i) With proper explanation show the electron drift velocity at 300K in pure silicon for  $100 \frac{V}{cm}$  is less than thermal velocity and comment on the electron drift velocity for  $10^4 V/cm$ .  $\left( \mu_n = 1350 \frac{cm^2}{V \cdot sec}, m_0 = 9.1 \times 10^{-31} kg, k = 1.38 \times 10^{-23} J/K \right)$  (12 M)

Candidates  
must not  
write on  
this margin

Sol:

Given data

$$E = 100 \frac{V}{cm}$$

$$\mu_n = 1350 \frac{cm^2}{V \cdot sec}$$

As we know,

$$V_d = \mu_n \cdot E$$

$$\therefore \text{Drift velocity, } V_d = \mu_n \cdot E = 1350 \times 100 = 1.35 \times 10^5 \frac{cm}{sec}$$

$$\Rightarrow V_d = 1.35 \times 10^5 \frac{cm}{sec} \rightarrow ①$$

Again, As we know

$$\frac{1}{2} m_0 \cdot V_{th}^2 = KT$$

where,  $V_{th}$  = Thermal Velocity,  $K$  = Boltzmann's const.

$m_0$  = mass of electron.

$$\Rightarrow V_{th} = \sqrt{\frac{2KT}{m_0}}$$

$$\Rightarrow V_{th} = \sqrt{\frac{2 \times 1.38 \times 10^{-23} \times 300}{9.1 \times 10^{-31}}}$$

$$\Rightarrow V_{th} = 9.54 \times 10^6 \frac{\text{cm}}{\text{sec}} \rightarrow ②$$

From above two equations ① & ②, it is clear  
that the drift velocity is less than the thermal  
velocity at  $100 \frac{\text{V}}{\text{cm}}$ .

Now, Let us calculate the drift velocity and  
thermal velocity for the electric field of  $10^4 \text{ V/cm}$ .

$\therefore$  Drift velocity at  $10^4 \text{ V/cm}$ ,

$$V_d = \mu_n \cdot E$$

$$\Rightarrow V_d = 1350 \times 10^4 \text{ cm/sec}$$

$$\Rightarrow V_d = 1.35 \times 10^7 \text{ cm/sec.}$$

Comment :

The electron drift Velocity for  $10^4 \frac{\text{V}}{\text{cm}}$  is

greater than thermal Velocity.

- (ii) Calculate the intrinsic concentration of Germanium at 500K. ( $m_n = 0.55m$ ,  $m_p = 0.37m$ ) (8 M)

Sol:

As we know,

$$E_g = E_{g0} - \beta T$$

$$\text{for 'Ge', } \beta = 2.23 \times 10^{-4}$$

$$E_{g0} = 0.785 \text{ eV}$$

$$\therefore \text{At } 500\text{K, } E_g = 0.785 - (2.23 \times 10^{-4} \times 500)$$

$$\Rightarrow E_g = 0.6735 \text{ eV.}$$

$$KT = \frac{T}{11600} = \frac{500}{11600} = 4.31 \times 10^{-3} \text{ eV.}$$

We know,

$$n_i^2 = 2.33 \times 10^{31} \times \left( \frac{m_n \cdot m_p}{m^2} \right)^{\frac{3}{2}} \cdot T^3 \cdot e^{-\frac{E_g}{KT}}$$

$$\Rightarrow n_i^2 = 2.33 \times 10^{31} \times \left( \frac{0.55 \times 0.37 m^2}{m^2} \right)^{\frac{3}{2}} \cdot (500)^3 \cdot e^{-\frac{0.6735}{0.0431}}$$

$$\Rightarrow n_i^2 = 2.33 \times 10^{31} \times (0.55 \times 0.37)^{\frac{3}{2}} \times (500)^3 \times 1.635 \times 10^{-7}$$

$$\Rightarrow n_i^2 = 4.3715 \times 10^{31}$$

$$\Rightarrow n_i = 6.61 \times 10^{15} \text{ cm}^{-3}$$

$\therefore$  Intrinsic Concentration,  $n_i = 6.61 \times 10^{15} \text{ cm}^{-3}$

Candidates  
must not  
write on  
this margin

07. (a)

Reduced incidence matrix of an oriental graph is given as

$$\begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

- (i) Drawn its graph
- (ii) How many tress are possible for this graph?
- (iii) Write the tie-set Matrix ?

(15 M)

Sol:

(i) Reduced Incidence matrix

$$[A] = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

As algebraic sum of column entries of an incidence matrix is zero. So incidence matrix


Branches/Nodes	1	2	3	4	5
(1)	0	-1	1	0	0
(2)	0	0	-1	-1	-1
(3)	-1	0	0	0	1
(4)	1	1	0	1	0

$a_{ij} = 1$ , if  $j$  is oriented away from node  $i$

Candidates  
must not  
write on  
this margin

and  $a_{ij} = -1$ , if branch 'j' is Oriented toward node 'i'  
 $a_{ij} = 0$ , if branch 'j' is incident on node 'i'

$\therefore$  Graph for Incidence Matrix

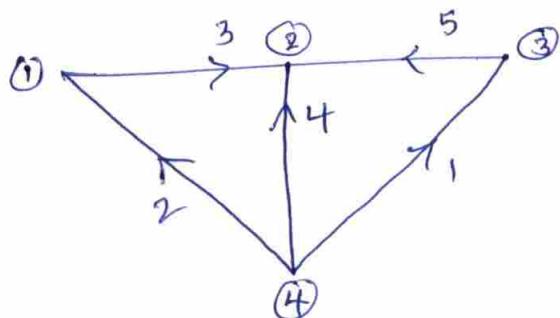

(ii)

Number of trees = Determinant  $[A] \cdot [A^T]$ .

$$[A] \cdot [A^T] = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 & -1 \\ -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$


$$\Rightarrow [A][A^T] = \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix}$$

$$\text{Det } [A][A^T] = 2(6-1) - (-1)(-2-0) + 0 \\ = 10 - 2 = 8$$



$\therefore$  Number of possible trees = 8

(iii)

Consider a tree from the graph

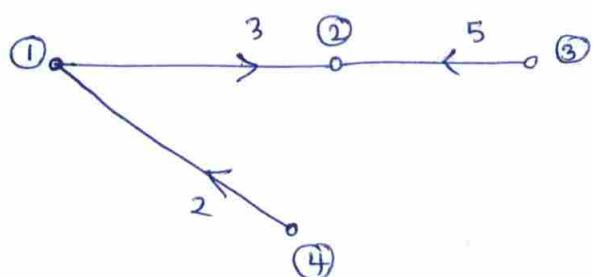Candidates  
must not  
write on  
this margin

Loop with above tree

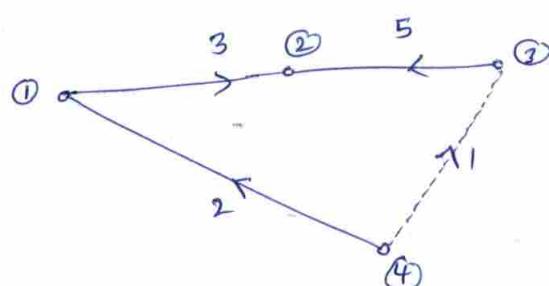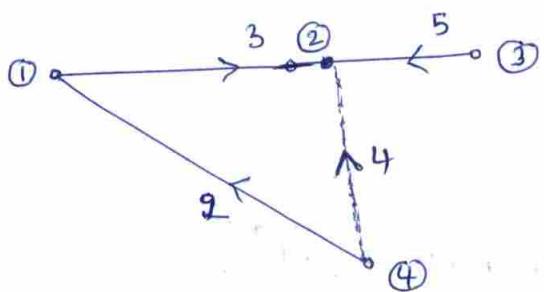


Tie-set matrix

Tiesets/Loop connect	1	2	3	4	5
$I_1$	0	1	1	-1	0
$I_2$	-1	1	1	0	1

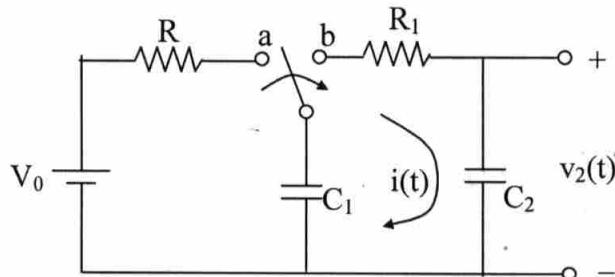07. (b)

The switch is moved from the position a to b at  $t = 0$ , having been in the position a for a long time before  $t = 0$ . The capacitor  $C_2$  is uncharged at  $t = 0$ . Find  $i(t)$  and  $v_2(t)$  for  $t > 0$ .

Candidates  
must not  
write on  
this margin



(15 M)

Sol:


At  $t=0^-$ , the network has attained steady-state condition. Hence, the capacitor acts as an open-circuit and it will charge to  $V_0$  Volts.

$$\boxed{V(0^-) = V_0}$$

Since the voltage across the capacitor does not change instantaneously.

$$\therefore V(0^+) = V_0$$

$$i(0^+) = \frac{V_0}{R_1}$$

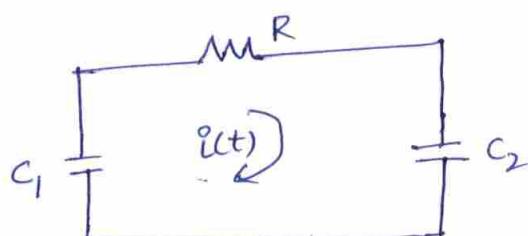

Writing KVL equation for  $t > 0$ ,

$$-\frac{1}{C_1} \int_0^t i dt + V_0 - R_1 i - \frac{1}{C_2} \int_0^t i dt = 0 \rightarrow \textcircled{1}$$

Differentiating equation ① , we get

$$-\frac{\dot{i}}{c_1} - R_1 \frac{di}{dt} - \frac{\dot{i}}{c_2} = 0$$

$$\frac{di}{dt} + \frac{1}{R_1} \left[ \frac{c_1 + c_2}{c_1 c_2} \right] i = 0$$

The solution of this differential equation is given by

$$i(t) = K \cdot e^{-\frac{1}{R_1} \left[ \frac{c_1 + c_2}{c_1 c_2} \right] t}$$

$$\text{At } t=0, \boxed{i(0) = \frac{V_0}{R_1}}$$

$$K = \frac{V_0}{R_1}$$

$$\therefore i(t) = \frac{V_0}{R_1} \cdot e^{-\frac{1}{R_1} \left[ \frac{c_1 + c_2}{c_1 c_2} \right] t}$$

$$\Rightarrow i(t) = \frac{V_0}{R_1} \cdot e^{-\frac{1}{R_1 C} t}$$

$$\text{where } C = \frac{c_1 c_2}{c_1 + c_2}$$

$$V_2(t) = \frac{1}{C_2} \int_0^t i dt$$

$$= \frac{1}{C_2} \int_0^t \frac{V_0}{R_1} \cdot e^{-\frac{1}{R_1 C} t} dt$$

$$V_2(t) = \frac{V_0}{R_1 C_2} \cdot R_1 C \left[ 1 - e^{-\frac{1}{R_1 C} t} \right]$$

$$\therefore \boxed{V_2(t) = \frac{V_0}{C_2} C \left[ 1 - e^{-\frac{1}{R_1 C} t} \right]}, \text{ for } t > 0.$$


07. (c)

- (i) Show Electron drift, electron diffusion, current diffusion density and current drift density flow in the n-type bar with respect to electric field and describe the effects on drift and diffusion current densities when,
- (A) Electron concentration is doubled.  
 (B) Constant electron concentration is added uniformly.

Candidates  
must not  
write on  
this margin

(10 M)

Sol:

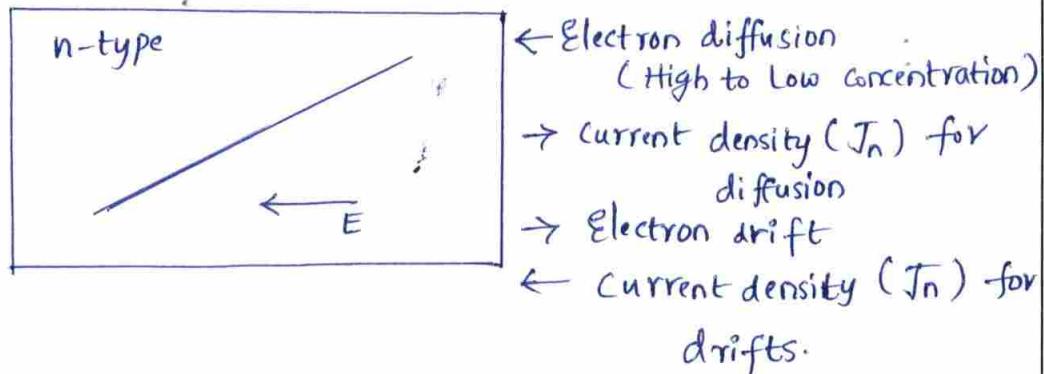

In n-type bar current flows in the opposite direction of electron flow because of negative charge.

Initially,

$$\text{Diffusion current density} = qD_n \cdot \frac{dn}{dx}$$

$$\Rightarrow J_n(\text{diffusion}) = qD_n \cdot \frac{dn}{dx}$$

$$\text{Drift current density} = qn\mu_n E$$

$$\Rightarrow J_n(\text{drift}) = qn\mu_n E$$

(A)

Doubled Electron Concentration

$$J'_n(\text{diffusion}) = \left[ qD_n \cdot \frac{d(2n)}{dx} \right]$$

$$\Rightarrow J_n'(\text{diffusion}) = 2 \left[ qD_n \frac{dn}{dx} \right]$$

$$\therefore J_n'(\text{diffusion}) = 2 J_n(\text{diffusion})$$

$$J_n'(\text{drift}) = q(n) \mu_n E = 2[qn \mu_n E]$$

$$\therefore \boxed{J_n'(\text{drift}) = 2 J_n(\text{drift})}$$

So, if we doubled the electron concentration then both drift & diffusion current density also doubles.

### (B) Add Constant Concentration ( $n_+$ )

$$\begin{aligned} J_n''(\text{diffusion}) &= qD_n \frac{d}{dx}(n+n_+) \\ &= qD_n \frac{dn}{dx} + qD_n \frac{dn_+}{dx} \end{aligned}$$

$$\Rightarrow J_n''(\text{diffusion}) = qD_n \frac{dn}{dx} \quad \left[ \because \frac{dn_+}{dx} = 0, \text{ as } 'n_+' \text{ is a constant.} \right]$$

$$\Rightarrow \boxed{J_n''(\text{diffusion}) = J_n(\text{diffusion})}$$

$$J_n''(\text{drift}) = q(n+n_+) \mu_n E$$

$$\Rightarrow J_n''(\text{drift}) = qn \mu_n E + qn_+ \mu_n E$$

$$\Rightarrow \boxed{J_n''(\text{drift}) = J_n(\text{drift}) + qn_+ \mu_n E}$$

So, if we add constant concentration ( $n_+$ ), diffusion current density remains same but drift current density will increases by  $qn_+ \mu_n E$ .

(ii) Calculate intrinsic resistivity and conductivity of silicon at room temperature.

$$\left( \mu_n = 1300 \frac{\text{cm}^2}{\text{V-sec}}, \mu_p = 500 \frac{\text{cm}^2}{\text{V-sec}}, n_i = 1.5 \times 10^{10} \text{ cm}^{-3} \right)$$

(5 M)

Candidates  
must not  
write on  
this margin

Sol:

Given data

$$\mu_n = 1300 \frac{\text{cm}^2}{\text{V-sec}}$$

$$\mu_p = 500 \frac{\text{cm}^2}{\text{V-sec}}$$

$$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$$

$$T = 300 \text{ K}$$

$$\therefore \sigma_i = n_i (\mu_n + \mu_p) q$$

$$\Rightarrow \sigma_i = 1.5 \times 10^{10} \times (1300 + 500) \times 1.6 \times 10^{-19}$$

$$\Rightarrow \sigma_i = 4.32 \times 10^{-6} (\Omega\text{-cm})^{-1}$$

$$\therefore \text{Resistivity } (f_i) = \frac{1}{\sigma_i}$$

$$\Rightarrow f_i = \frac{1}{4.32 \times 10^{-6}}$$

$$\Rightarrow f_i = 23.481 \times 10^3 (\Omega\text{-cm}).$$

$$\therefore \text{Intrinsic Conductivity } (\sigma_i) = 4.32 \times 10^{-6} (\Omega\text{-cm})^{-1}$$

$$\text{Intrinsic Resistivity } (f_i) = 23.481 \times 10^3 (\Omega\text{-cm})$$

07. (d) In a very long p-type silicon bar with Cross-section area =  $0.5 \text{ cm}^2$  and  $N_a = 10^{17} \text{ cm}^{-3}$ , we inject holes such that the steady state excess hole concentration is  $5 \times 10^{16} \text{ cm}^{-3}$  at  $x = 0$ .  
 $\left( \mu_p = 500 \frac{\text{cm}^2}{\text{V-sec}}, \tau_p = 10^{-10} \text{ sec}, E_g = 1.1 \text{ eV}, V_T = 0.0259 \text{ V}, n_i = 1.5 \times 10^{10} \text{ cm}^{-3} \right)$

Candidates  
must not  
write on  
this margin

- (i) What is the steady state separation between  $E_p$  and  $E_c$  at  $x = 1000 \text{ \AA}$ ?
- (ii) What is the hole current?
- (iii) How much is the excess stored hole charge?

(5 + 5 + 5)M

Sol:

Given data

$$\text{Cross-sectional Area} = 0.5 \text{ cm}^2$$

$$P_0 = N_a = 10^{17} \text{ cm}^{-3}$$

$$\text{Excess hole} = \Delta p = 5 \times 10^{16} \text{ cm}^{-3}$$

(i)  $D_p = \frac{KT}{q} \mu_p = 0.0259 \times 500 = 12.95 \text{ cm/s.}$

$$L_p = \sqrt{D_p \cdot T_p} = \sqrt{12.95 \times 10^{-10}} = 3.6 \times 10^{-5} \text{ cm.}$$

$$p = P_0 + \Delta p \cdot e^{-x/L_p}$$

$$\Rightarrow p = 10^{17} + (5 \times 10^{16}) \cdot e^{-\frac{x}{3.6 \times 10^{-5}}}$$

$$\Rightarrow p = 1.379 \times 10^{17} \text{ cm}^{-3}$$

As we know,

$$p = n_i \cdot e^{\frac{E_i - E_p}{KT}}$$

$$\Rightarrow E_i - E_p = KT \ln \left( \frac{p}{n_i} \right)$$

$$\Rightarrow E_i - E_p = 0.0259 \ln \left( \frac{1.379 \times 10^{17}}{1.5 \times 10^{10}} \right)$$

$$\Rightarrow E_i - E_p = 0.415 \text{ eV}$$

$$\therefore E_c - E_p = \frac{E_g}{2} + E_i - E_p$$

$$\Rightarrow E_c - E_p = \frac{1.1}{2} + 0.415$$

$$\Rightarrow \boxed{E_c - E_p = 0.965 \text{ eV}}$$

(ii) We can calculate the hole current using the equation

$$I_p = -qA D_p \frac{dp}{dx}, \quad (\text{where } p = p_0 + \Delta p \cdot e^{-x/L_p})$$

$$\Rightarrow I_p = qA \frac{D_p}{L_p} (\Delta p) \cdot e^{-x/L_p}$$

$$\Rightarrow I_p = 1.6 \times 10^{-19} \times 0.5 \times \frac{12.95}{3.6 \times 10^{-5}} \times 5 \times 10^{16} \cdot e^{-\frac{10^{-5}}{3.6 \times 10^{-5}}}$$

$$\Rightarrow I_p = 1.09 \times 10^3 \text{ A}$$

$$\therefore \boxed{\text{Hole current } (I_p) = 1.09 \times 10^3 \text{ A}}$$

(iii) The excess stored hole charge,

$$Q_p = qA (\Delta p) L_p$$


$$\Rightarrow Q_p = 1.6 \times 10^{-19} \times (0.5) (5 \times 10^{16}) (3.6 \times 10^{-5})$$

$$\Rightarrow Q_p = 1.44 \times 10^{-7} C$$

$\therefore$  Excess stored hole charge,

$$Q_p = 1.44 \times 10^{-7} C$$

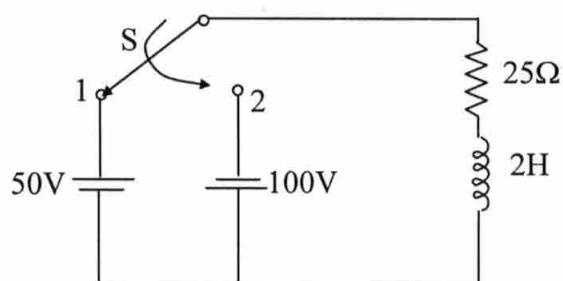
08. (a) (i) In the circuit shown below, the switch S is in position '1' long enough to establish steady - state conditions and at  $t = 0$  is switched to position '2'. Draw 's - domain' network :



(10 M)

Sol:

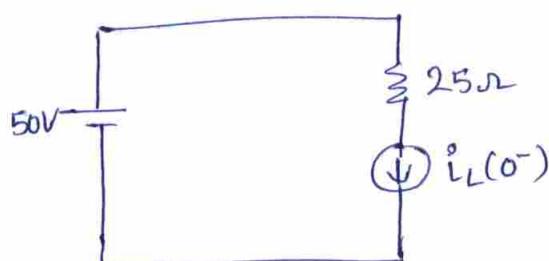When switch is in position '1' for long time, it will go to steady-state condition where inductor will acts as a short-circuit.




Current through inductor,

$$I_L = \frac{V}{R} = \frac{50}{25} = 2A$$


$$i_L(0^-) = i_L(0^+) = 2A$$

When switch moved to position (2)

Inductor acts as a current source of 2A.

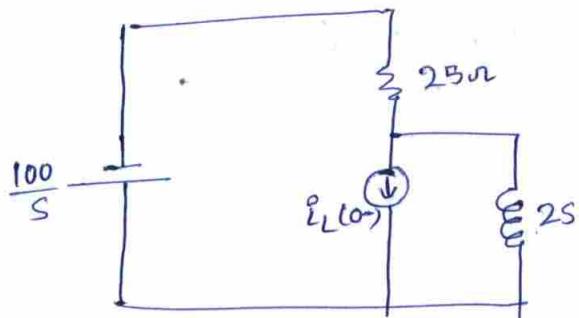


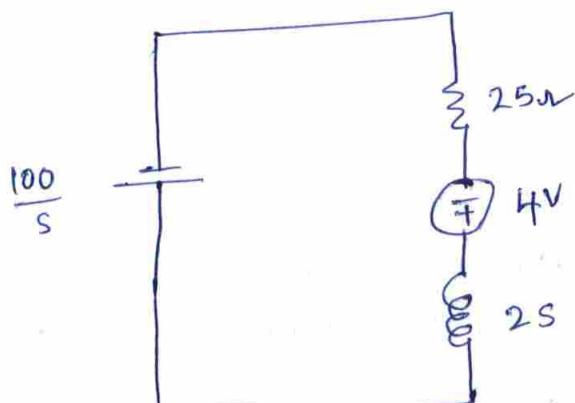By converting inductor current and inductor parallel network into series, it will look like



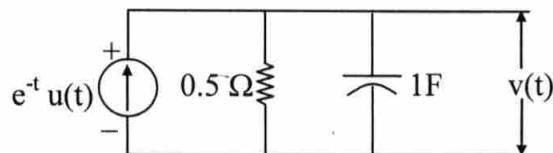
(ii) Using Laplace transform method, obtain expression for  $v(t)$  in the following network.

Candidates  
must not  
write on  
this margin



(10 M)

Sol:

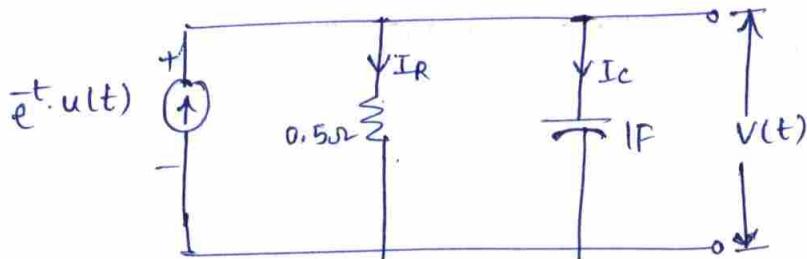

By applying KCL

$$i(t) = I_R + I_C$$

$$\text{LT}[e^{-t} u(t)] = V(s)[2+s] \rightarrow ①$$

The Laplace transform is given by

$$\text{Laplace Transform}[e^{-t} u(t)] = \frac{1}{s+1}$$

$$\text{Laplace}[v(t)] = V(s).$$

Taking the Laplace transform on both sides of eq. ①, we get

$$\frac{1}{s+1} = V(s)[2+s]$$

$$\Rightarrow V(s) = \frac{1}{(s+1)(s+2)}$$

$$\Rightarrow V(s) = \frac{1}{(s+1)} - \frac{1}{(s+2)}$$

By applying Inverse Laplace Transform on both sides, we get

$$V(t) = (\bar{e}^{-t} - \bar{e}^{-2t}) \cdot u(t)$$



08. (b) Explain clearly the construction of a p-n junction diode and its use to convert sunlight directly into electricity. What distinguishes a solar cell from a conventional p-n junction diode? (20 M)

Sol:
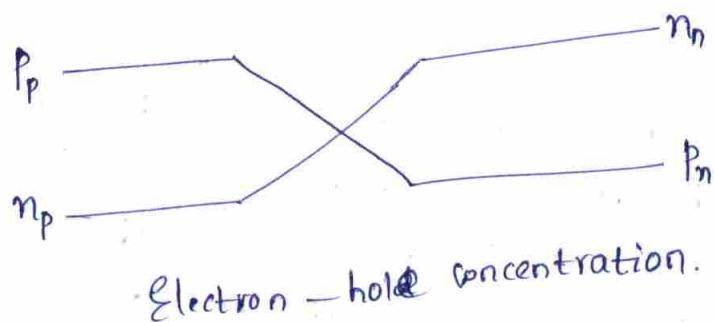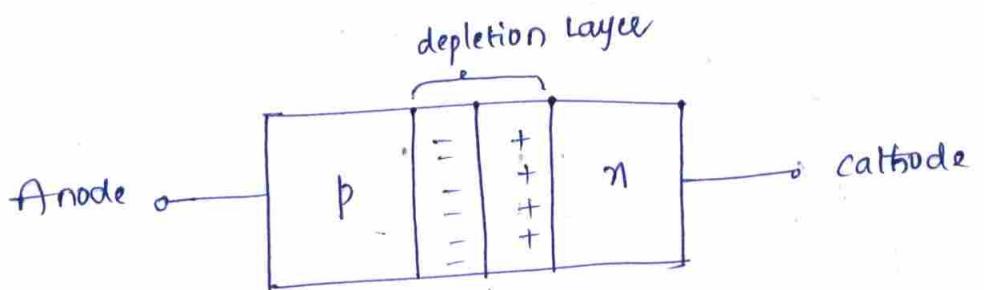
### Construction of p-n Junction %

A p-n junction diode is formed by doping one side of a piece of silicon with a p-type dopant (Boron) and other side of N-type dopant (phosphorous). Ge can be used as instead of silicon. The p-n junction is a two terminal device. This is the basic construction of the p-n junction diode. It is one of the most simplest semiconductor devices as it allows current to flow only one direction. The p-n junction is an interface between P-type and n-type regions and is used to construct diodes and transistors. At the junction, majority carriers diffuse across the junction which results

and this creates a depletion layer and a barrier potential ( $V_{\text{barrier}}$ ) across the junction. The voltage  $V_{\text{barrier}}$  causes an opposing current flow, and the two flows form an equilibrium.




#### Applications :

- p-n junction diode, in reverse biased configuration is sensitive to light from a range between 400nm - 1000nm, which includes visible light. Therefore it can be used as a photo diode.
- It can also be used as a "solar cell".
- p-n junction forward bias condition is used in all LED lighting applications.

#### Conversion of sun light into electricity :


The first photovoltaic device was built using a Si p-n junction by Russell Ohl in 1939. A silicon solar

Photo Voltaic cells converts lights (photon) energy into electric energy. The photons from the exposed light prompted electrons flowing from n-junction to p-junction i.e. electric current flow.

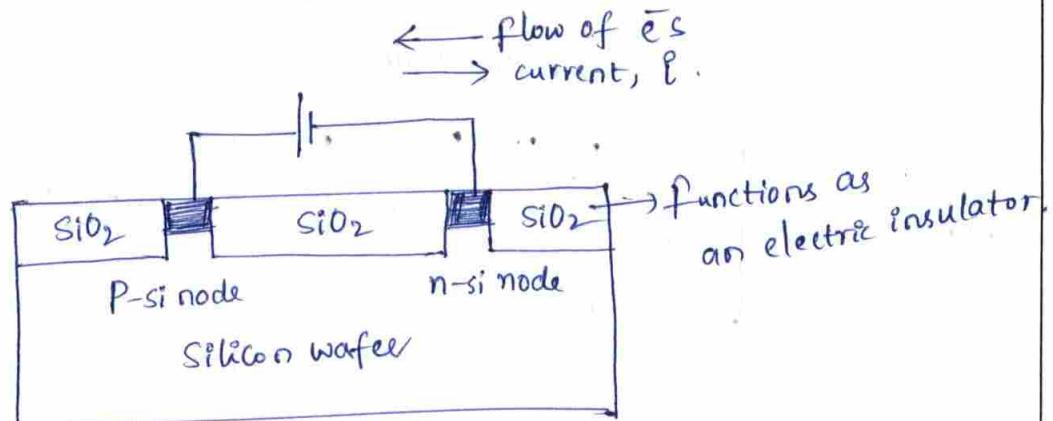
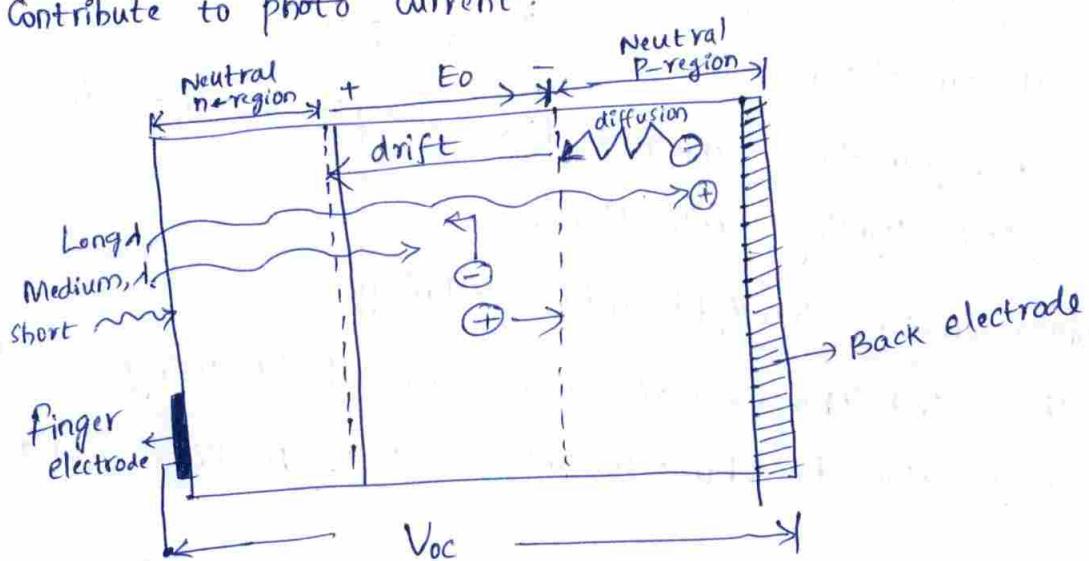
### Working Principle :

The n-region is heavily doped and thin so that the light can penetrate through it easily. The p-region is lightly doped so the most of depletion region lies in the p-side. Electron-hole pairs are generated in the depletion region and due to built-in potential & electric field, electrons moves to the n-region & holes to the p-region. When an external load is applied, the excess  $e^-$ s travel through the load to recombine with holes. EHTPs generated can contribute to photo current.



## Difference between p-n junction and Solar cell :

The solar cell is a pn-junction diode optimized to convert the incident solar radiation to electrical energy. Like wise every diode is optimized for its specific application, such as rectifier diode & zener diodes.


The major difference is the Metalization of the two electrodes. The back side of the solar cell is normally the anode is completely metalized while the front side electrode is partially metalized in the form of metal fingers & buss bars to allow light to pass to the active solar cell material absorbed in the material to generate the photo current and collecting the photo current by the metal grid to access electrically the front electrode. Normal diode is fully metalized from both sides.

08. (c) (i) Describe the constructional features of n-channel E-MOSFET. (10 M)
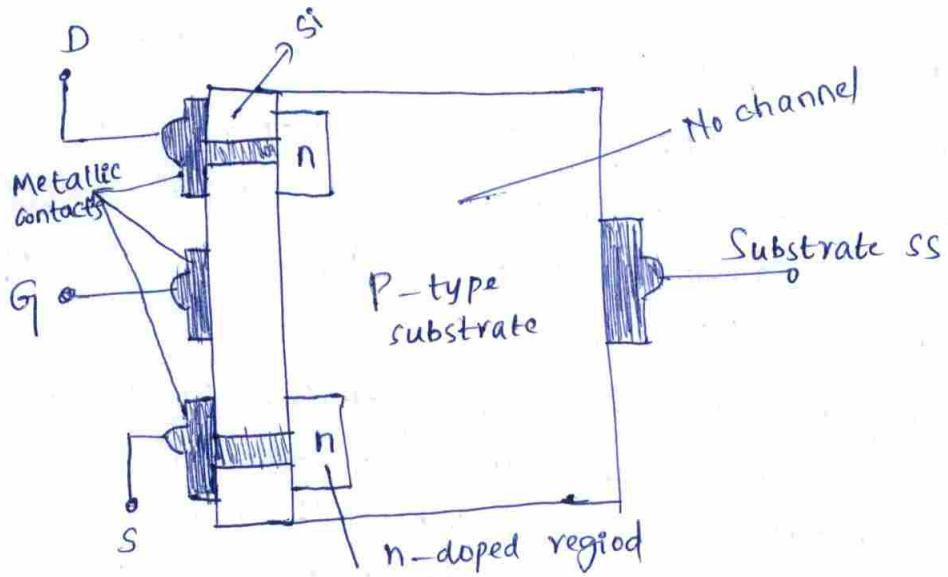
## Construction of n-channel E-MOSFET :

The Fig. (a) shows the basic construction of n-channel enhancement type MOSFET. Two lightly doped n-regions are diffused into a lightly doped p-type substrate. The source and drain are taken out through metallic contacts to n-doped regions as shown in fig (a). But the channel between two n-regions is absent in E-MOSFET.


The  $\text{SiO}_2$  layer is still present in the E-MOSFET to isolate the gate metallic platform from the region between the drain and source, but now it is simply separated from a section of the p-type material.



fig(a). Construction of n-channel EMOSFET.
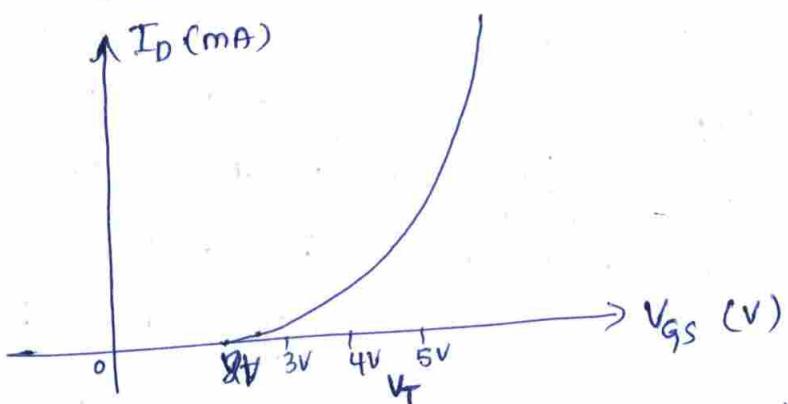
### Transfer characteristics :


Here  $V_{DS}$  is applied and  $V_{GS}$  is kept zero (by directly connecting gate to the source). At this time practically no current flows.




If we increase the magnitude of  $V_{GS}$  in the positive direction, the concentration of electrons near the  $\text{SiO}_2$  surface increases. At a particular value of  $V_{GS}$  there is a measurable current flow between drain and source. This value of  $V_{GS}$  is called Threshold voltage denoted by  $V_T$ .

Thus we can say that in an enhancement type n-channel MOSFET, a positive gate voltage above threshold value induces a channel and hence the drain current is increased by creating a thin layer of negative charges in the substrate region adjacent to the  $\text{SiO}_2$  layer.

Drain characteristics :

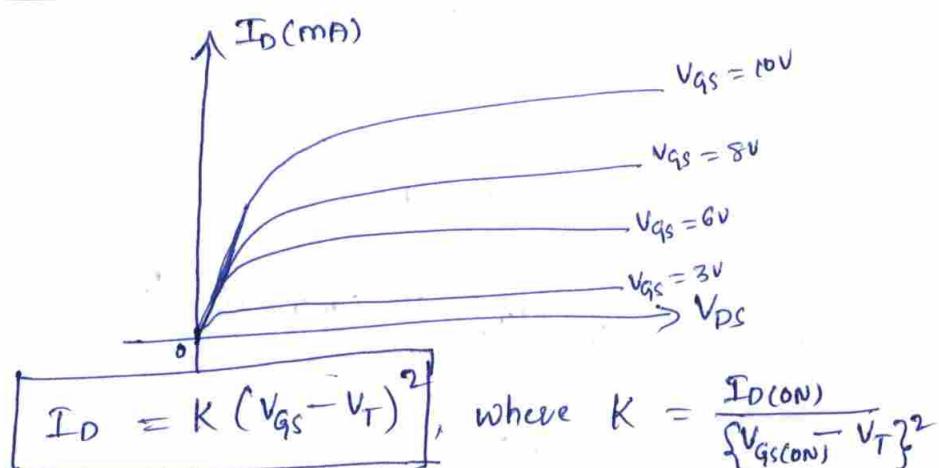

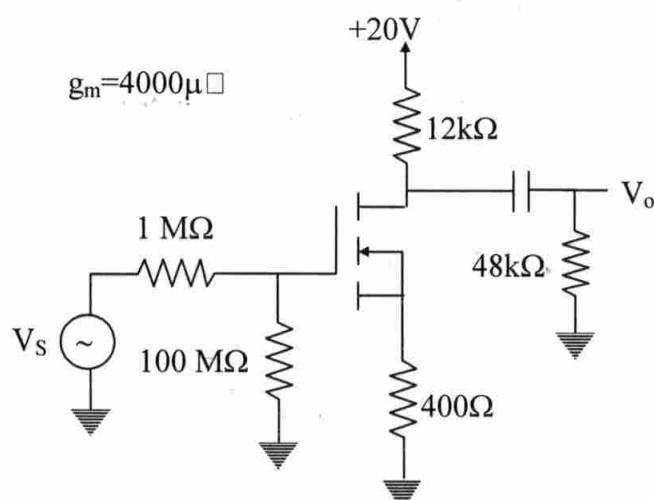- (ii) Calculate the voltage gain  $\left( \frac{V_o}{V_s} \right)$  of the circuit shown in the below figure.




(10 M)

Sol:

Given that

$$\text{Trans conductance } (g_m) = 4000 \mu\text{A/V}$$

Ac equivalent circuit

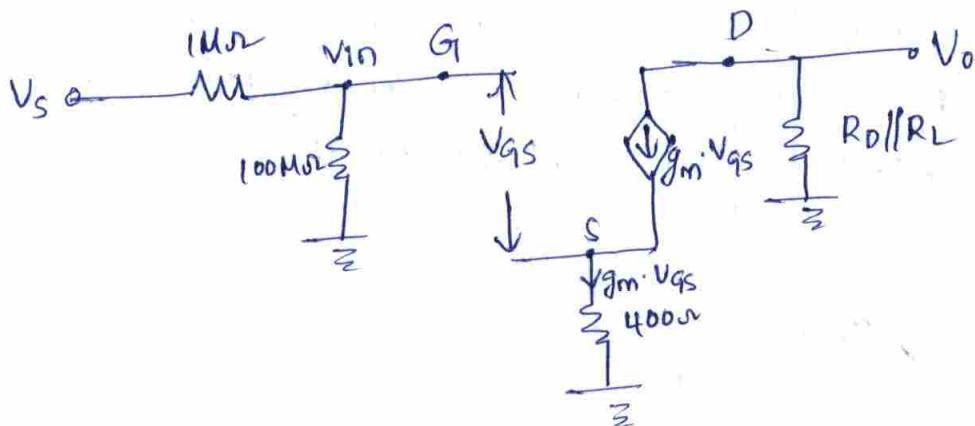

$$\begin{aligned}
 V_o &= -g_m \cdot V_{GS} (R_D \parallel R_L) \\
 &= - (12k \parallel 48k) (4000M) V_{GS} \\
 &= -38.4 V_{GS}
 \end{aligned}$$

$$\begin{aligned}
 V_{in} &= V_{GS} + g_m \cdot V_{GS} \times 400 \\
 &= V_{GS} [1 + (4000M) \times 400] \\
 &= 2.6 V_{GS}
 \end{aligned}$$

$$\frac{V_o}{V_{in}} = \frac{-38.4}{2.6} = -14.769$$

$$\text{where, } V_{in} = \frac{V_s [100M]}{1M + 100M}$$

∴ Voltage gain

$$A_v = \frac{V_o}{V_s} = -14.769 \left( \frac{100}{101} \right)$$
$$= -14.62$$

∴  $A_v = -14.62$

