



**ACE**  
**Engineering Academy**  
Leading Institute for ESE/GATE/PSUs

Hyderabad | Delhi | Ahmedabad | Bhopal | Pune | Bhubaneswar | Bengaluru  
Lucknow | Patna | Chennai | Vijayawada | Vizag | Tirupathi | Kukatpally | Kolkata

# **ESE - 2019 (MAINS)**

**Questions with Detailed Solutions**

**ELECTRONICS & TELECOMMUNICATION ENGINEERING**

## **PAPER - I**

ACE Engineering Academy has taken utmost care in preparing the **ESE-2019 MAINS** Examination solutions. Discrepancies, if any, may please be brought to our notice. ACE Engineering Academy do not owe any responsibility for any damage or loss to any person on account of error or omission in these solutions. ACE Engineering Academy is always in the fore front of serving the students, irrespective of the examination type (GATE/ESE/PSUs/PSC/GENCO/TRANSCO etc.,).

# **ELECTRONICS & TELECOMMUNICATION ENGINEERING**

## **ESE \_ MAINS \_ PAPER - I**

### **SUBJECT WISE REVIEW**

SUBJECT(S)	LEVEL	Marks
Basic Electronics Engineering	Moderate	27
Basic Electrical Engineering	Moderate	20
Materials Science	Easy	84
Electronic Measurements and Instrumentation	Moderate	84
Network Theory	Moderate	124
Analog and Digital Circuits	Moderate	141

Since 1995

**ACE**

**Subject Experts,**

**ACE Engineering Academy**

## SECTION-A

**01. (a) (i) Calculate the temperature at which silicon (Si) semiconductor tends to behave like a metal** (6 M)

**(ii) Prove that reverse saturation current approximately doubles for every 10°C rise in temperature in a semiconductor diode.** (6 M)

**Sol:**

(i)  $E_G(T) = E_{G0} - \beta T$

$$0 = 1.21 - 3.60 \times 10^{-4} \cdot T$$

$$\Rightarrow T = 3361.1^\circ\text{K}$$

**Explanation:**

Energy Band gap  $\approx 6$  eV For Insulator

$\approx 1$  eV For Semiconductor

$\approx 0$  eV For Metal

→ Energy Band is Dependent on temperature. As temperature increases energy band gap decreases. As temperature increases Valence electrons gain energy and get excited, hence making such excited electron, free is possible easily i.e., gap between conduction & valence band decreases.

→ The above equations relates energy gap versus temperature

$E_{G0}$  = Energy Gap At 0°K

$\beta$  = Constant

T = Temperature in °K

$E_G(T)$  = Energy Gap at T°K

(ii)  $I_{02} = 2^{\left(\frac{T_2-T_1}{10}\right)} \cdot I_{01}$

where,  $I_{01}$  is reverse saturation current at temperature  $T_1$

$I_{02}$  is reverse saturation current at temperature  $T_2$

$$I_{02} = 2^{\frac{\Delta T}{10}} \cdot I_{01}$$

$$\Delta T = 10^\circ\text{C}$$

$$I_{02} = 2^{\frac{10}{10}} I_{01} = 2^1 I_{01}$$

$$I_{02} = 2 I_{01}$$

∴ For every  $10^\circ\text{C}$  rise in temperature, reverse saturation current approximately double.

**01. (b) (i) Prove that when two resistors are connected in parallel, the equivalent resistance of the combination is always smaller than that of smaller resistor. (6 M)**

**(ii) A conductor has resistance  $5.4\Omega$  at  $20^\circ\text{C}$  and  $7\Omega$  at  $100^\circ\text{C}$ . Determine the resistance of the conductor at  $0^\circ\text{C}$ . (6 M)**

**Sol:**

$$(i) \frac{1}{R_{eq(n)}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$\text{If } n = 2 \text{ then } \frac{1}{R_{eq(2)}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq(2)} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq(2)} = \frac{R_1}{1 + \frac{R_1}{R_2}} = \frac{R_2}{1 + \frac{R_2}{R_1}}$$

$$\text{Since } \frac{R_1}{R_2} > 0, \text{ we see } R_{eq(2)} < R_1$$

$$\& R_{eq(2)} < R_2$$

$$\text{So, } R_{eq(2)} < \min(R_1, R_2)$$

Now suppose it is true that

$$R_{eq(n)} < \min(R_1, R_2, \dots, R_n)$$

$$\text{Consider, } \frac{1}{R_{eq(n+1)}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} + \frac{1}{R_{n+1}} = \frac{1}{R_{eq(n)}} + \frac{1}{R_{n+1}}$$

Using above result for  $n = 2$ , we find  $R_{eq(n+1)} < \min[R_{n+1}, R_{eq(n)}] < \min[R_{n+1}, \min(R_1, \dots, R_n)]$

But  $\min[R_{n+1}, \min(R_1, \dots, R_n)] = \min[R_{n+1}, R_1, \dots, R_n]$ .

So,  $R_{eq(n+1)} < \min(R_1, R_2, \dots, R_n, R_{n+1})$

(ii) Let us consider the following equation

$$R_1 = R_0[1 + \alpha (\Delta T_1)]$$

Where,  $R_1$  = Resistance at  $20^\circ\text{C}$  ( $5.4\Omega$ )

$R_0$  = Resistance at  $0^\circ\text{C}$

$$\Delta T_1 = (20^\circ\text{C} - 0^\circ\text{C}) = 20^\circ\text{C}$$

$\alpha$  = Temperature coefficient of resistance

$$\Rightarrow 5.4 = R_0[1 + 20\alpha] \dots\dots\dots (1)$$

$$R_2 = R_0[1 + \alpha (\Delta T_2)]$$

Where,  $R_2$  = Resistance at  $100^\circ\text{C}$  ( $7\Omega$ )

$$\Delta T_2 = 100^\circ\text{C} - 0^\circ\text{C} = 100^\circ\text{C}$$

$$\Rightarrow 7 = R_0[1 + 100\alpha] \dots\dots\dots (2)$$

$\therefore$  By solving above equation (1) and (2)

$$R_0 = 5\Omega \text{ and } \alpha = \left(\frac{1}{50}\right)$$

$\therefore$  Resistance of the conductor at  $0^\circ\text{C}$  is  $5\Omega$ .

### 01. (c) What is 'line imperfection defect' in crystal? How does it affect the properties of a metal?


(12 M)

**Sol:** Line imperfection defects:

- If the defect is confined to more number of atoms in a lattice is known as line defect.  
Ex; Crack formation in a material, where along the line of crack, the atoms are missing. Hence it is a line defect.
- A *dislocation* may be defined as a disturbed region between two substantially perfect parts of a crystal.
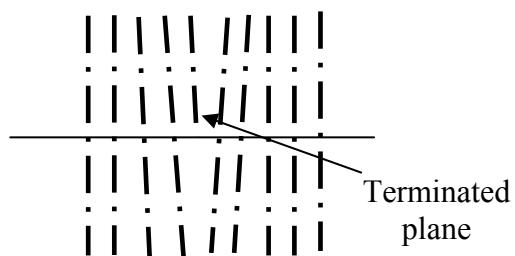
#### (a) Edge Dislocation

- By applying force on the lattice along the line of defect the lattice can break or crack easily known as edge dislocation.
- At the edge of a material, if any defects are created, then it acts as a line defect in the material.



- Edge dislocations are caused by the termination of a plane of atoms in the middle of a crystal.
- In such a case, the adjacent planes are not straight, but instead bend around the edge of the terminating plane so that the crystal structure is perfectly ordered on either side.

### (b) Screw Dislocation

- If the movement of atom planes is following a translation motion followed by rotational motion is known as screw dislocation.
- In this phenomenon the arrangement of atoms in the lattice will be in the form of circular fashion at different planes.
- Therefore screw dislocation defects will change the surface properties of the material significantly.
  - (1) Material properties depends on number of line defect and there movement.
  - (2) The dislocation (line defect) always moves in a direction and on a plane that require low energy. Combination of direction and plane is known as slip system.

Structure	Number of slip systems
HCP	8
BCC	48
FCC	12

- (3) If the number of slip system in a material is more than 5 then those materials are ductile in nature with low strength , otherwise material is brittle.
- (4) Based on strain hardening mechanism, by deforming material plastically, dislocation density increased and due to that dislocation – dislocation interaction takes place, so strength of material decreases.

# **ESE / GATE / PSUs 2020 – 2021**

## **ADMISSIONS OPEN**

### **GATE + PSUs – 2020**

Regular Batches @ Dilsukhnagar	<b>08<sup>th</sup> &amp; 22<sup>nd</sup> July, 05<sup>th</sup> &amp; 20<sup>th</sup> August 2019</b>
Regular Batch @ Kukatpally	<b>01<sup>st</sup> July 2019</b>
Regular Batches @ Pune	<b>01<sup>st</sup> &amp; 15<sup>th</sup> July 2019</b>
Weekend & Regular Batches @ Chennai	<b>06<sup>th</sup> July 2019</b>
Regular Batch @ Bengaluru	<b>08<sup>th</sup> July 2019</b>

### **ESE + GATE + PSUs – 2020**

Regular Batch @ Dilsukhnagar	<b>08<sup>th</sup> July 2019</b>
Regular Batch @ Pune	<b>01<sup>st</sup> July 2019</b>

### **GATE + PSUs – 2021**

Morning Batches @ Abids	<b>12<sup>th</sup> July &amp; 10<sup>th</sup> August 2019</b>
Morning & Evening Batches @ Dilsukhnagar	<b>12<sup>th</sup> July &amp; 10<sup>th</sup> August 2019</b>
Morning & Evening Batches @ Kukatpally	<b>12<sup>th</sup> July &amp; 10<sup>th</sup> August 2019</b>
Weekend Batches @ Pune	<b>6<sup>th</sup> July &amp; 17<sup>th</sup> August 2019</b>
Weekend Batch @ Chennai	<b>6<sup>th</sup> July 2019</b>
Weekend Batch @ Bengaluru	<b>3<sup>rd</sup> August 2019</b>
Weekend Batch @ Vijayawada	<b>7<sup>th</sup> July 2019</b>
Weekend Batch @ Tirupati	<b>13<sup>th</sup> July 2019</b>
Weekend Batch @ Vizag	<b>20<sup>th</sup> July 2019</b>

### **ESE + GATE + PSUs – 2021**

Morning Batches @ Abids	<b>12<sup>th</sup> July &amp; 10<sup>th</sup> August 2019</b>
Weekend Batches @ Pune	<b>6<sup>th</sup> July &amp; 17<sup>th</sup> August 2019</b>

### **IES GENERAL STUDIES BATCH**

Regular Batch @ Abids	<b>12<sup>th</sup> July 2019</b>
Weekend Batch @ Pune	<b>13<sup>th</sup> July 2019</b>

### **GENCO / TRANSO / DISCOMS BATCH**

Regular Batch @ Abids	<b>14<sup>th</sup> July 2019</b>
-----------------------	----------------------------------

for more batch details please visit: [www.aceenggacademy.com](http://www.aceenggacademy.com)

**01. (d) (i) Enumerate the different performance indices based on which an engineer selects an instrument. (5 M)**

**(ii) What is the SI system of units? Mention some (at least four) well-defined units maintained by the international System of Units. (7 M)**

**Sol:** (i) Different performance indices on which engineer selects an Instrument

(1) Accuracy Grade (Class) of an Instrument: If instrument has more Accuracy grade, then error in Instrument reading is less.

(2) Sensitivity of an Instrument:

If instrument has high sensitivity then loading by instrument on measuring quantity is less.

So loading error in instrument reading less

(3) Resolution of an Instrument:

If instrument has high resolution even a small variation in measuring quantity can be measured.

(4) Dynamic Error/fidelity:

If dynamic error is less, output of instrument follows similar to the input quantity.

So, instrument should be preferred more fidelity (mean less dynamic error)

(5) Speed of response:

If an instrument has more speed of response, settling time is less, with more speed of response measuring lag/delay time is less

(ii) The seven base units which from the basis of the now universally accepted international systems of Units, in their present status are defined below:

**1. Metre (m):** It is the unit of length. The metre is the length equal to 1,650,763.73 wavelengths in vacuum of radiation corresponding to the transition between the level  $2_{p10}$  and  $5_{d5}$  (orange red line) of the krypton 86 atom (excited at the triple point of nitrogen 63.15° kelvin).

**2. Kilogramme (kg):** It is the unit of mass. A kilogramme is equal to the mass of the international prototype of mass. This prototype is a cylinder of platinum iridium alloy.

**3. Second (s):** It is the unit of time. A second is defined as the duration of 9,192,631,770 periods of radiation corresponding to the transition between the two hyperfine levels of the ground state of the cesium atom.

**4. Ampere (A):** It is the unit of electric current. The ampere is that constant current which, if maintained in two straight parallel conductors of infinite length, of negligible cross-section, and placed one metre apart in vacuum, would produce between them a force equal to  $2 \times 10^7$  Newton per metre length.

**5. Kelvin (K):** It is the unit of temperature. The Kelvin, unit of thermodynamic temperature, is the fraction 1/273.16 of the thermodynamic temperature of triple point of water.

**6. Candela (Cd):** it is the unit of luminous intensity. It is the luminous intensity, in a perpendicular direction, of a surface of 1/600,000 square metre of a blackbody at the temperature of freezing platinum under a pressure of 101,325Newton per square metre.

**7. Mole (mol):** The mole is the amount of substance of a system which contains as many elementary entities as there are atoms in 0.012 kg of carbon 12. it should be noted that whenever mole is used, the elementary entities must be specified, which may be atoms, molecules, ions, electrons, other particles, or specified groups of such particles.

These definitions are adopted all over the world for purposes of science, technology, industry and commerce. The Eleventh General Conference of Weights and Measures which met in October, 1960 recommended a unified systematically constituted, coherent system of fundamental, supplementary and derived units for international use. This system, called the International system of units and designated by the abbreviation SI, system internationale 'd' units is now legally compulsory in about twenty countries. It consists of six base units, two supplementary units and 27 derived units. Principles for the use of prefixes for forming the multiples and sub-multiples of units were also laid down. The six base units have already been adopted in the standards of weights and Measures Act, 1956.



Scan QR Code  
for Website

# LONG TERM PROGRAM

## ESE+GATE+PSUs-2021

◆ Morning Batch

**12<sup>th</sup> July 2019 @ Abids (EC/EE/ME/CE)**

## GATE+PSUs-2021

◆ Morning Batches

**12<sup>th</sup> July 2019**

@ Abids (EC/EE/ME/CE/CSIT/IN)  
@ Kukatpally (EC/EE/ME/CE/CSIT/IN),  
@ Dilsukhnagar (EC/EE/ME),  
@ Kothapet (CE)

◆ Evening Batches

**12<sup>th</sup> July 2019**

@ Kukatpally (EC/EE/ME/CE/CSIT/IN)  
@ Dilsukhnagar (EC/EE/ME)  
@ Kothapet (CE)

**Head Office Address:** # 4-1-1236/1/A, Sindhu Sadan,  
King Koti, Abids, Hyderabad - 500001, Telangana, India

website: **www.aceenggacademy.com**

ABIDS

040-23234418 / 19 / 20

KUKATPALLY

040-40199966, 93476 99966

DILSUKHNAGAR


040-40209345, 40044451

KOTHAPET

040-24034418 / 19



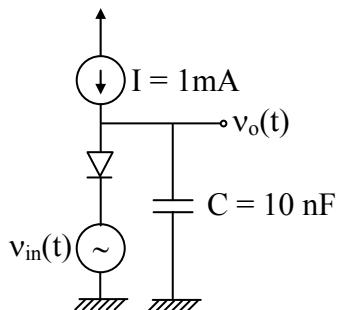01. (e) In the circuit shown in the figure below,  $I = 1\text{mA}$  is a DC current and  $v_{in}(t)$  is a sinusoidal voltage with small amplitude:




Representing the diode by its small signal resistance  $r_d$ , which is a function of  $I$ , sketch the circuit for determining  $v_o(t)$  and thus find out cutoff frequency  $f_H$ . (Assume  $V_T = 25\text{mV}$  at room temperature) (12 M)

**Sol:** Step (1):  $r_d$  (the diode small-signal resistance) is given by.

$$r_d = \frac{V_T}{I} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega \quad \text{---(1)}$$

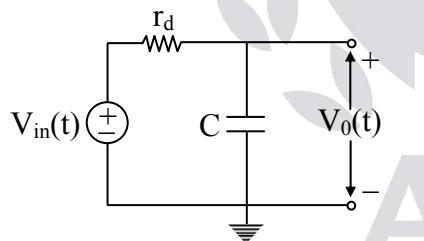Step (2): For determining  $V_0(t)$ , all the dc sources in the circuit should be considered as zero. i.e the current source  $I$  should be open from the circuit shown in bellow.



$$V_0(t) = \frac{\frac{1}{j\omega C} V_i(t)}{r_d + \frac{1}{j\omega C}} \quad \text{---(2)}$$

$$\frac{V_0(t)}{V_i(t)} = \frac{\frac{1}{j\omega C}}{\frac{1}{r_d} + \frac{1}{j\omega C}} = \frac{1}{1 + j2\pi f r_d C} \quad \text{---(3)}$$

$$= \frac{1}{1 + \frac{jf}{f_H}} \quad \text{---(4)}$$

where  $f_H$  = Upper cutoff frequency  $= \frac{1}{2\pi r_d C}$

$$\therefore \left| \frac{V_o(t)}{V_i(t)} \right| = \frac{1}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}} \quad \text{---(6)}$$

Step (3): cutoff frequency  $f_H = \frac{1}{2\pi r_d C} = \frac{1}{2\pi \times 25\Omega \times 10nF} = 636.94\text{kHz} = 0.63694\text{MHz}$  ---(7)



**ACE®**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs



Hyderabad | Ahmedabad | Pune | Delhi | Bhopal | Bhubaneswar | Bangalore | Patna | Chennai | Lucknow | Visakhapatnam | Vijayawada | Tirupati | Kolkata

New Batches for  
**GENCO / TRANSCO / DISCOMS**  
@ Hyderabad  
ELECTRICAL ENGINEERING

Batch Dates

**29<sup>th</sup> June & 14<sup>th</sup> July 2019**

Duration : **5 to 6 Months** • Timings : **4 to 6 hrs** • Fee : **45000/-** • Venue : **ABIDS**

It's exclusive for Power Generation Corporation & Power Distribution Company's of all states in India

Syllabus Included

(a). General Aptitude,  
(b). Technical Subjects (as per GATE Syllabus Except Mathematics)




Scan QR Code  
for More Information

Web: [www.aceenggacademy.com](http://www.aceenggacademy.com) | Call: 040-23234418/19/20

**02. (a)(i) Find the equilibrium hole concentration  $p_0$  at 300 K of Si sample doped with phosphorus impurity if Fermi level energy ( $E_F$ ) of doped Si is 0.407 eV more than intrinsic level energy ( $E_i$ ). Given  $n_i = 1.5 \times 10^{10}$  atoms/cm<sup>3</sup> and  $kT = 0.0259$  eV. (10 M)**

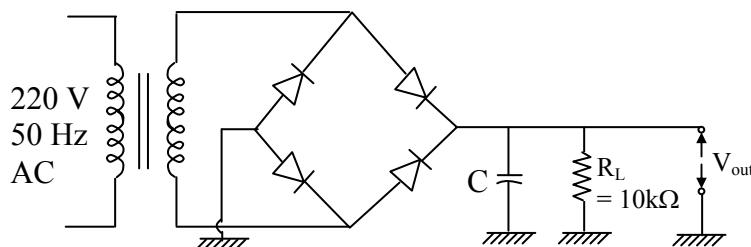**(ii) A filter capacitor C is used to smooth out the pulses from the full-wave rectifier as shown in the figure below:**




**Find the value of C so that the steady current supply to load  $R_L$  can be maintained.**

**(10 M)**

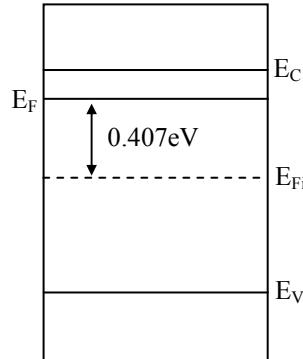**Sol:**

$$(i) E_F - E_{Fi} = KT \ell \ln \left( \frac{N_D}{n_i} \right) = KT \ell \ln \left( \frac{n}{n_i} \right)$$



$$\frac{E_F - E_{Fi}}{KT} = \ell \ln \left( \frac{n}{n_i} \right)$$

$$\Rightarrow \frac{n}{n_i} = e^{\frac{E_F - E_{Fi}}{KT}}$$

$$n = n_i e^{\left( \frac{E_F - E_{Fi}}{KT} \right)}$$

$$= 1.5 \times 10^{10} \cdot e^{\frac{0.407}{0.0259}}$$


$$= 1 \times 10^{17} / \text{cm}^3$$

$$\therefore \text{The equilibrium hole concentration, } p_0 = \frac{n_i^2}{n}$$

$$\Rightarrow p_0 = \frac{(1.5 \times 10^{10})^2}{1 \times 10^{17}}$$

$$\Rightarrow p_0 = 2246.279 \text{ cm}^{-3}$$

(ii)

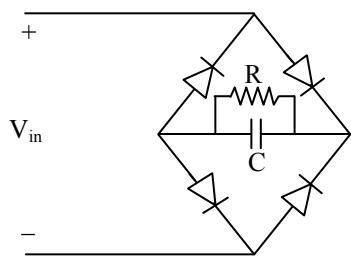


$$V_m = 220\sqrt{2} = 311.12$$

$$T = \frac{1}{f} = 0.02$$

$$R = 10K$$

For a steady current supply

Diodes are ideal

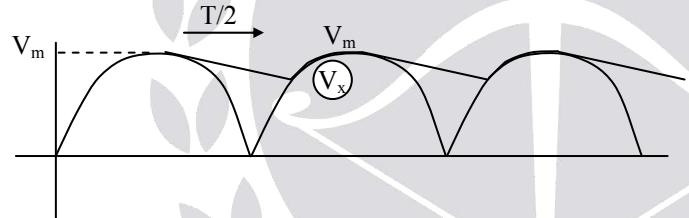

$$V_x = V_m e^{-t/RC}$$

$$\left| t = T/2 \quad RC \gg T \right.$$

$$= V_m \left( 1 - \frac{T}{2RC} \right)$$

$$\text{Ripple (r)} = V_m - V_x$$

$$r = \frac{V_m T}{2RC} = \frac{0.00031}{C}$$

'r' should be small

$\therefore C$  should be large, If  $r = 0.01V_m$

$$C = 0.1mF$$

$$\therefore C = 0.1mF$$

# **REGULAR BATCHES**

**GATE+PSUs - 2020**

**ABIDS DSNR      KOTHAPET KKP**

**24<sup>th</sup> June | 01<sup>st</sup> July | 08<sup>th</sup> July | 22<sup>nd</sup> July |  
05<sup>th</sup> August | 20<sup>th</sup> August 2019**

# **MPSC MAINS ||**

**CIVIL ENGINEERING**

**REGULAR BATCH: 15th July 2019**

**FREE ORIENTATION SESSION & DEMO CLASS**


**06th July 2019, 10am TO 1pm @ PUNE**

**02. (b) (i) What is the principle of nanomagnetism? Based on the specific properties of nanomagnetism, write its applications in engineering field. (12 M)**

**(ii) Classify insulating materials according to their temperature stability limit and give few examples of each grade. (8 M)**

**Sol:**

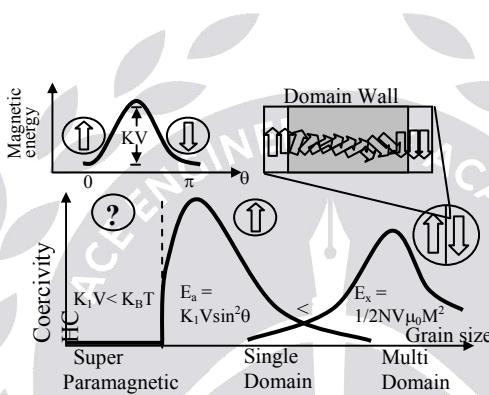- (i) When reducing the size of the magnetic material the number of domains within the material will be reduced until only a single domain is obtained. By having only single domains it is possible to produce strong permanent magnets. However if the size is reduced beyond a certain limit the sample becomes superparamagnetic and does no longer hold any ferromagnetism.



The figure illustrates the coercivity as function of magnetic particle size. As the particle shrinks fewer domains are present in the particle. At a certain size - depending in the material the magnetic particle becomes a single domain - typically in the range from 10 - 100 nm. At sizes below 10nm the particles becomes superparamagnetic. The spin is constantly changing within the particle.

To produce high performance permanent magnetic the particle size should be chosen so that the coercivity is maximized together with the remanence.

engineering application of nanomagnetism:-

- (1) MRI contrast equipment.
- (2) Biosensors.
- (3) Magnetic relaxation switches.
- (4) energy conversion.
- (5) electronic devices.

- (ii) Maximum allowable temperatures of various types of insulation

<b>Insulation Classes</b>	<b>Maximum Permissible temperature (°C)</b>
Y	90
A	105
E	120
B	130
F	155
H	180
C	Over 180

- (i) Class-Y Insulation: Withstands a temperature of up to 90°C; typically made of cotton, silk, or paper.
- (ii) Class-A Insulation: Withstands a temperature of up to 105°C; reinforced Class-Y materials with impregnated varnish or insulation oil.
- (iii) Class-E Insulation: Withstands a temperature of up to 120°C.
- (iv) Class-B Insulation: Withstands a temperature of up to 130°C; This has a form that inorganic material is hardened with adhesives. This is the first insulator using this structure.
- (v) Class-F Insulation: Withstands a temperature of up to 155°C; for example, made of Class-B materials that are upgraded with adhesives, silicone, and alkyd-resin varnish of higher thermal endurance.
- (vi) Class-H Insulation: Withstands a temperature of up to 180°C; for example, made of inorganic material glued with silicone resin or adhesives of equivalent performance
- (vii) Class-C Insulation: Withstands a temperature of up to 180°C or higher; made of 100% inorganic material.

Temperature classes of insulating material.

3Insulation type	Main	Insulation material	Adhesive, impregnant, or coating material used together with the insulator specified in column 3	Target Insulator
Y	Main	Cotton, silk, or other natural plant or animal fibers . Regenerated cellulose. Cellulose acetate. Polyamide fiber. Paper and paper goods. Press board.	None	None


**02. (c) (i) What are the signal conditioning requirements for measurements with strain gauges? How can you compensate errors due to temperature in strain gauge measurements?**

(10 M)

**(ii) A piezoelectric transducer is subjected to force of 6 N. The dimension of the transducer is given as  $6 \text{ mm} \times 6 \text{ mm} \times 1.3 \text{ mm}$ . The charge sensitivity and the dielectric constant of the transducer are given as  $160 \text{ pC/N}$  and  $1250 \times 10^{-11} \text{ F/m}$  respectively. Calculate the voltage generated and the deflection caused to the surface. The Young's modulus of elasticity of the material is given as  $12 \times 10^6 \text{ N/m}^2$ .** (10 M)

**Sol:**

**(i)**

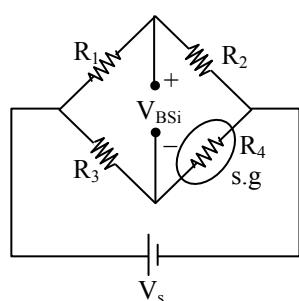

$$R_m = \infty$$

Strain gauge is a resistive transducer so the best signal conditioning is done by wheatstone bridge circuit.


$$R_1 = R_2 = R_3 = R$$


$$R_4 = R + \Delta R \text{ after stress applied}$$

$$\begin{aligned} V_{BSI} &= V_s \left\{ \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right\} \\ &= V_s \left\{ \frac{R}{R+R} - \frac{(R+\Delta R)}{R+(R+\Delta R)} \right\} \\ &= V_s \left\{ \frac{1}{2} - \frac{R+\Delta R}{2R+\Delta R} \right\} \\ &= V_s \left\{ \frac{2R+\Delta R - 2R - \Delta R}{4R+2\Delta R} \right\} \\ &= V_s \left\{ \frac{-\Delta R}{4R+2\Delta R} \right\} \\ |V_{BSI}| &= \frac{V_s \cdot \Delta R}{4R} [\because 4R \gg 2\Delta R] \end{aligned}$$


$$V_{BSI} \propto \Delta R \propto \Delta L \propto F$$

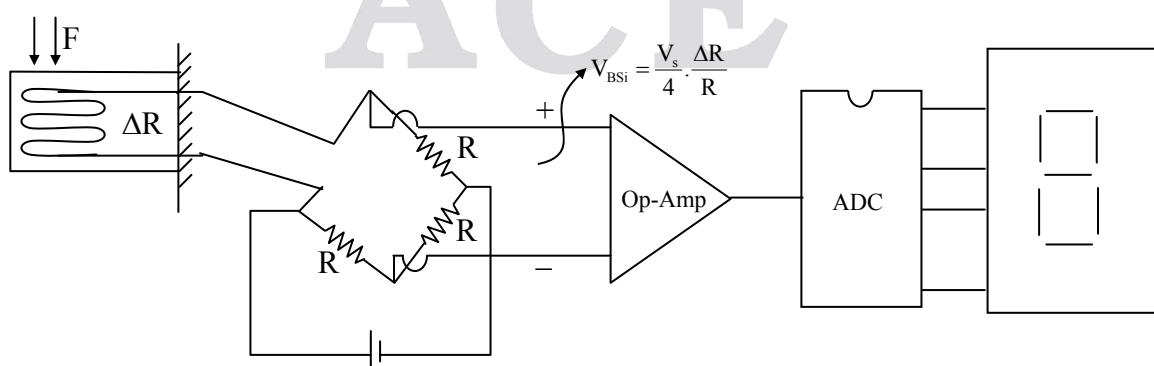The signal conditioning blocks for strain gauge



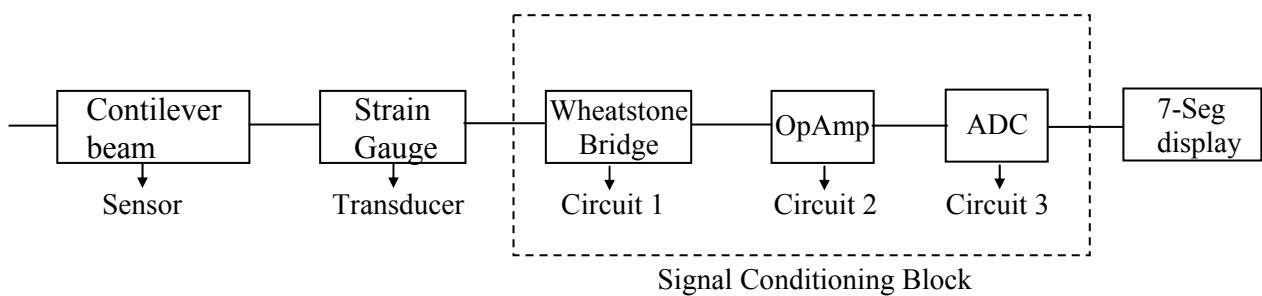

### Temperature effect on Strain Gauge

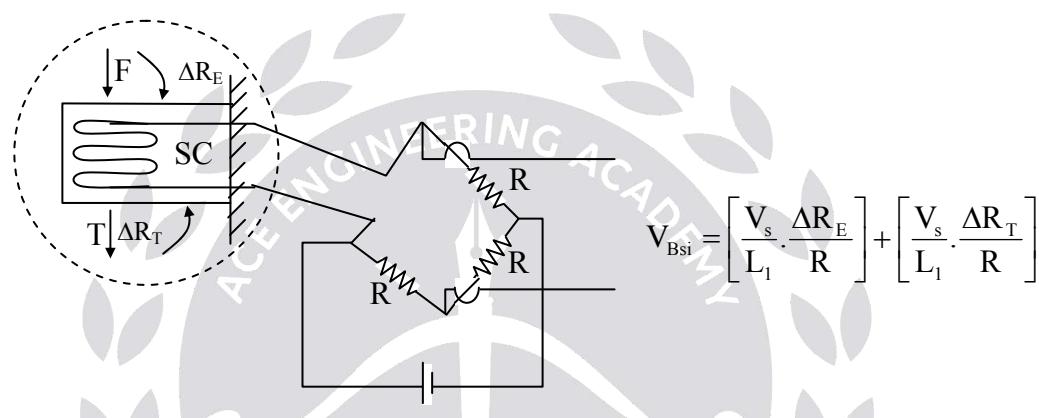

Semiconductor strain gauges are extremely sensitive for stress m/m as their gauge factor is high due to resistivity effect. But they're sensitive to temperature also; they've negative temperature coefficient of resistance,

$$V_{Bsi} = \frac{V_s}{4} \cdot \frac{\Delta R}{R}$$

$$= \frac{V_s}{4} \cdot \frac{[\Delta R_E + \Delta R_T]}{R}$$

$\Delta R_E$  = due to strain

$$V_{Bsi} = \left[ \frac{V_s}{4} \cdot \frac{\Delta R_E}{R} \right] + \left[ \frac{V_s}{4} \cdot \frac{\Delta R_T}{R} \right]$$

$\Delta R_T$  = due to temperature

True value Temperature induced error

To eliminate this error dummy strain gauges of semiconductor material have to be used as compensation element that strain gauge has to be placed on other surface and that surface has to be subjected to temperature but not to force; that's why that strain gauge is called dummy strain gauge

(ii)  $F_{i/p} = 6N$

$$\ell \times b \times h = 6mm \times 6mm \times 1.3 mm$$

$$\vec{d} [\text{charge sensitivity}] = 160 \text{ pC/N}$$

$$\epsilon [\text{dielectric constant}] = 1250 \times 10^{-11} \text{ F/m}$$

$$Y_{\text{crystal}} = 12 \times 10^6 \text{ N/m}^2$$

(1)  $E_0 = ?$

$$E_0 = \vec{g} \cdot \vec{p} \cdot t$$

$$= \left[ \frac{\vec{d}}{\epsilon} \right] \cdot \frac{F}{A} \cdot t$$

$$\Rightarrow \frac{160 \times 10^{-12}}{1250 \times 10^{-11}} \times \frac{6}{6 \times 6 \times 10^{-6}} \times 1.3 \times 10^{-3}$$

$$\Rightarrow \frac{1248 \times 10^{-15}}{45000 \times 10^{-17}}$$

$$\Rightarrow 0.0277 \times 10^{+2}$$

$$E_0 = 2.77 \text{ volts}$$

(2)  $x(\text{deflection}) = ?$

$$\frac{F}{A} = Y \cdot \frac{(\Delta t)}{t} \rightarrow x$$

$$\frac{F}{A} = Y \cdot \frac{x}{t}$$

$$\frac{F}{A} \cdot \frac{t}{Y} = x$$

$$x = \frac{6}{6 \times 6 \times 10^{-6}} \times \frac{1.3 \times 10^{-3}}{12 \times 10^6}$$

$$\Rightarrow \frac{7.8}{432} \times \frac{10^{-3}}{1}$$

$$x = 0.018 \text{ mm}$$

# **SSC-JE (Paper-I)**

## **Online Test Series**

Staff Selection Commission - Junior Engineer

**No. of Tests : 20**

Subject Wise Tests : 16 | Mock Tests - 4

**Civil | Electrical | Mechanical**

**Starts From 10<sup>th</sup> July 2019**

All tests will be available till 27<sup>th</sup> September 2019

📞 040 - 48539866 / 040 - 40136222

✉️ testseries@aceenggacademy.com

# **RRB(JE)-2019**

## **Online Test Series**

### **► STAGE - I**

Common for all Streams

No. of Tests : 20

Starts from 25<sup>th</sup> February 2019

### **► STAGE - II**

CE | ME | EC | EE


No. of Tests : 20

Starts from 6<sup>th</sup> May 2019

📞 040 - 48539866 / 040 - 40136222

✉️ testseries@aceenggacademy.com

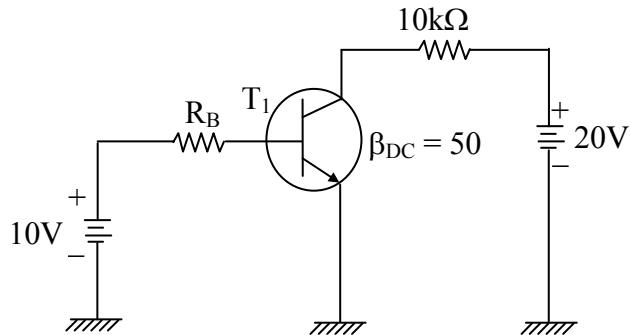03. (a)(i) Calculate the range of base resistance ( $R_B$ ) so that transistor  $T_1$  never operates in saturation region:



(10 M)

(ii) An amplifier has bandwidth of 500kHz and voltage gain of 100. What should be the amount of negative feedback if the amplifier bandwidth is extended to 5MHz? What will be the new gain after negative feedback is introduced? (10 M)

Sol:

(i) Case (i): Let  $V_{CE_{sat}} = 0.2V$  and  $V_{BE} = 0.7V$

Step (1): KVL for output section

$$20V - I_{C_{sat}} 10k\Omega - V_{CE_{sat}} = 0 \quad (1)$$

$$\Rightarrow I_{C_{sat}} = \frac{20V - 0.2V}{10k\Omega} = 1.98mA \quad (2)$$

$$\therefore I_{B_{min}} \text{ to saturate } 'T_1' = \frac{I_{C_{sat}}}{\beta_{DC}} = \frac{1.98mA}{50} = 0.0396mA \quad (3)$$


NOTE: The actual value of  $I_B$  should be less than  $I_{B_{min}}$  to ensure the transistor never operates in saturation region.

$$\text{i.e., } I_B < I_{B_{min}} \Rightarrow I_B < 0.0396mA \quad (4)$$

Step (2) KVL for input section

$$10V - I_B R_B - V_{BE} = 0 \quad (5)$$
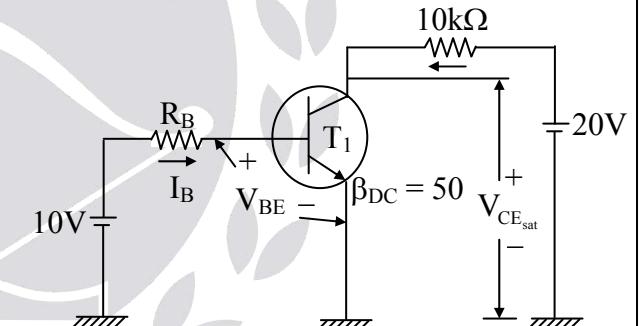
$$\Rightarrow R_B = \frac{10V - 0.7V}{I_B} \quad (6)$$



$$R_B > \frac{9.3V}{0.0396mA} \quad (7)$$

$$\therefore R_B > 234.85k\Omega \quad (8)$$

i.e. For  $R_B > 234.85k\Omega$   $T_1$  never operates in saturation

**(ii) Given**

Bandwidth before feedback,  $BW = 500kHz$

Voltage gain before feedback  $A_v = 100$

Step (1) The general formula for the bandwidth with negative feedback,

$$BW_f = BW [1 + A_v \beta]$$

$$\Rightarrow 5MHz = 500kHz [1 + 100\beta]$$

$$\Rightarrow 1 + 100\beta = \frac{5 \times 10^6 Hz}{500 \times 10^3 Hz} = 10$$

$$\Rightarrow 100\beta = 9$$

$$\therefore \beta = \frac{9}{100} = 0.09 \quad [\text{i.e } 9\%]$$

Step (2): Gain with negative feedback,

$$A_{V_f} = \frac{A_v}{1 + A_v \beta}$$

$$= \frac{100}{1 + 100 \times \frac{9}{100}}$$

$$\therefore A_{V_f} = 10$$

# **GATE - 2020**

**Online Test Series**

Starts from 2nd May 2019

**No. of Tests : 64**

**+**

**Free 52 Practice Tests of  
GATE - 2019 Online Test Series**

**Total Tests : 116**

# **ESE - 2020 PRELIMS**

**Online Test Series**

Starts from 15th May 2019

**No. of Tests : 44**

**+**

**Free 30 Practice Tests of  
ESE - 2019 Online Test Series**

**Total Tests : 74**

# **GATE+ESE - 2020**

**Online Test Series**

Combination Pack

All tests will be available till  
**GATE - 2020 & ESE -2020 (Prelims)**  
examinations respectively.

- Detailed solutions are available.

- Video solutions are also available for difficult questions.

 **040 - 48539866 / 040 - 40136222**

- All India rank will be given for each test.

- Comparison with all India toppers of ACE students.

 **testseries@aceenggacademy.com**

# **KPTCL - AE & AEE**

**Online Test Series**

Karnataka Power Transmission Corporation Limited

**No. of Tests : 16**

Subject Wise Tests : 13 | Mock Tests - 3

**Electrical Engineering**

**Starts From 8<sup>th</sup> June 2019**

All tests will be available till KPTCL Examination

 **040 - 48539866 / 040 - 40136222**

 **testseries@aceenggacademy.com**

**03. (b) (i) What are HTSC? Write the important applications of superconducting materials and HTSC.** (10 M)

**(ii) "A ceramist can alter the properties of ceramic." Justify the statement.** (10 M)

**Sol:**

- (i) High temperature superconductors:- Some of the cuprate ceramics are becoming superconductor at high temperature nearly about 100K.

Example:- Yttrium barium copper oxide-94K

Application of superconductor:

- (1) Maglev trains
- (2) loss less power transmission line.
- (3) cryotron switch
- (4) MRI scanning
- (5) Nuclear power plant.

Application of HTSC:-

- (1) Current limiter
- (2) Fusion magnets
- (3) NMR- spectrometer.
- (4) Transformers.

- (ii) In general density of ceramics are lighter than metal and heavier than polymers.

A ceramist can alter the properties of ceramic by the following method

- Make starting materials more uniform.
- Decrease grain size in polycrystalline ceramic products.
- Minimize porosity.
- introduce compressive surface stresses.
- Use fibre reinforcement.
- Heat treat.



# ACE

## Engineering College

(Approved by AICTE & Affiliated to JNTUH)

@ GHATKESAR, HYDERABAD



Scan for Experts' Advice



EAMCET CODE  
**ACEG**  
Region: Medchal-Malkajgiri

**B.Tech :** CSE\* IT ECE\* CIVIL MECH\* EEE\*



Separate Hostel Facility for Boys & Girls


EDC | Guidance for GATE and ESE |  
Centre of Excellence in AI / ML, IoT and JHUB



800+ Capacity  
Auditorium

Why ACE? **THE BUTTERFLY**

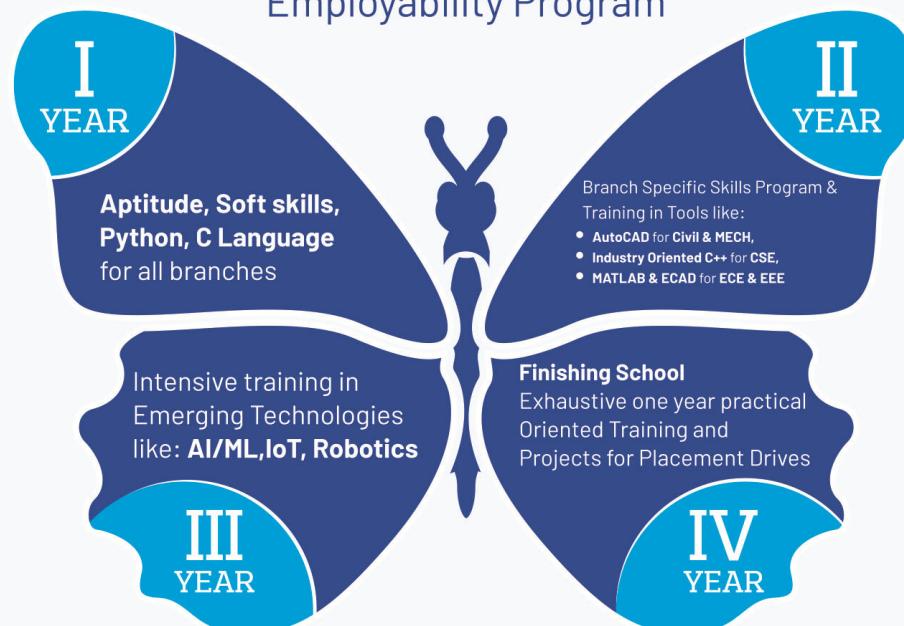Skill Development &  
Employability Program



**OUR PROMINENT RECRUITERS**  
(A.Y. 2018-19)

INFOSYS	MU SIGMA	VIRTUSA
WIPRO	COGNIZANT	OPENTEXT
TCS	CYIENT	JIO
OPTUM	HITACHI	XTREMIT
AAIC	AMAZON	HEXAWARE
XIAOMI	HP	GGK TECH
MINDTREE	TECH MAHINDRA	OPTUMRX
MI	CAPGEMINI	CORECOMPETE
SPIDERS	IBM	EPAM
SYNTEL	VALUEMOMENTUM	NINELEAPS

and many more...

More than **80%**  
PLACEMENTS of Registered Candidates

**9133308468, 9912391169, 9133308533**


Email: [admissions2019@aceec.ac.in](mailto:admissions2019@aceec.ac.in) | website: [www.aceec.ac.in](http://www.aceec.ac.in)

- 03. (c) (i)** Explain, with necessary diagrams, how you can detect the proximity of an object.(12 M)  
**(ii)** The spring constant and seismic mass of an accelerometer are  $3300 \text{ N/m}$  and  $5 \times 10^{-2} \text{ kg}$  respectively. The maximum displacement is  $\pm 0.25\text{m}$ (before the mass hits the stops). Calculate (1) the maximum measurable acceleration in g and (2) the natural frequency. (8 M)

**Sol:**

- (i) The proximity of an object can be detected by several sensor technologies such as ultrasonic sensors, capacitive, photo electric, inductive.

Inductive proximity:

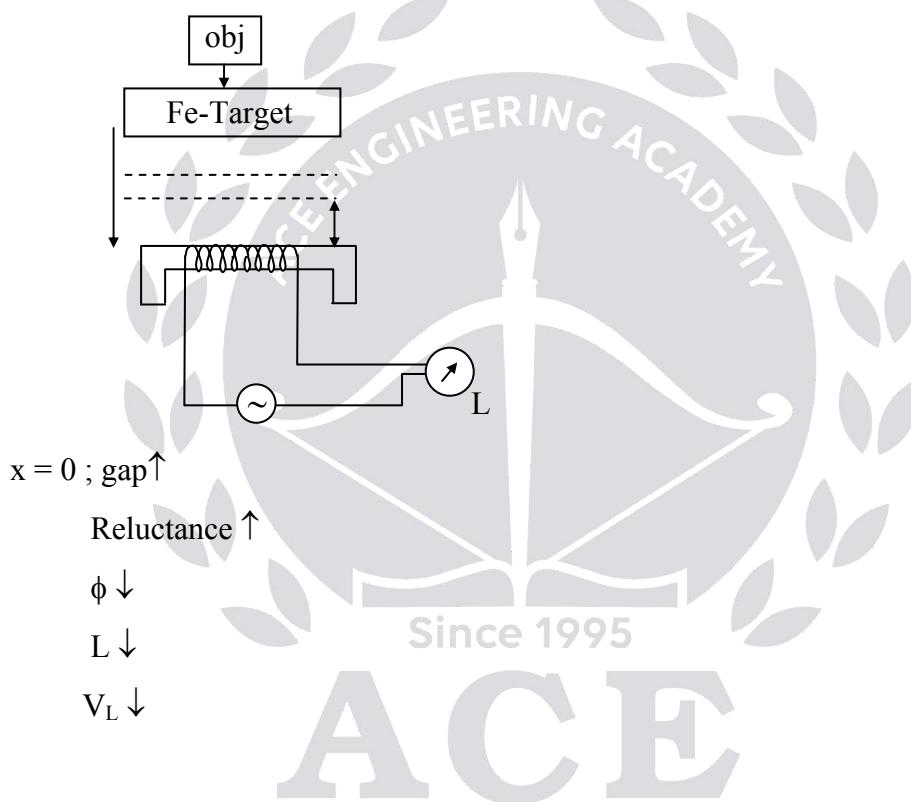

If object approaches

$x \downarrow, \text{gap} \downarrow$



Reluctance  $\downarrow$

$\phi \uparrow$


$L \uparrow$

$V_L \uparrow$

Optical proximity:

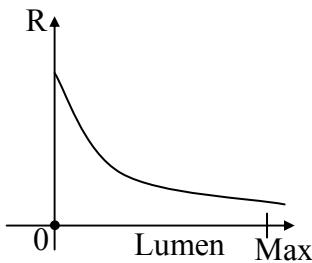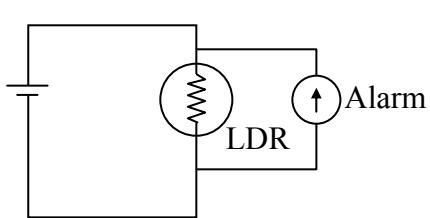


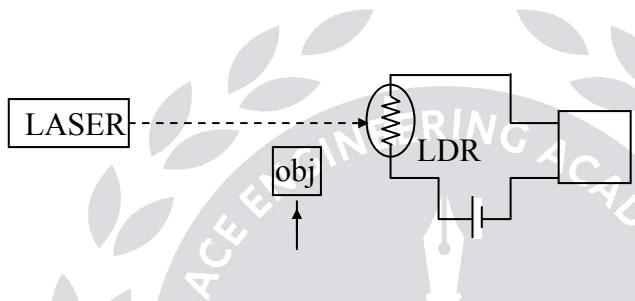LDR is a photo resistor whose resistance will decrease as the light is incident on it; when an object enters in between light source and LDR then alarm rings.



If object is not there then light hits LDR then  $R$  is less current increases, when object comes in the middle then LDR, resistance increases current decreases.

Ultrasonic proximity:

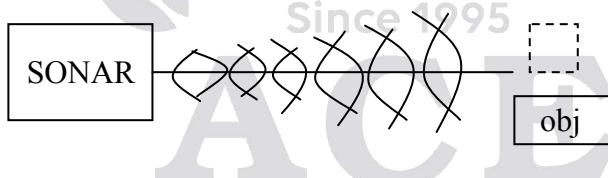

Piezo electric acts like transducer and inverse transducer also. When stress applied voltage is generated and when voltage applied it generates ultrasonic waves; when object is not there will not be any echo; if an object is present in the middle of the wave propagation then there will be echo.

(ii)  $K$  (spring constant) = 3300 N/m

$$M \text{ (Mass)} = 5 \times 10^{-2} \text{ kg}$$

$$X_0 \text{ (dispersion)} = \pm 0.25 \text{ m}$$

$$(1) \text{ Steady state sensitivity} = \frac{X_0}{\text{acc}_{i/p}} = \frac{M}{K}$$

$$X_0 = \left( \frac{M}{K} \right) \text{acc}_{i/p}$$

$$(0.25 \text{ m}) = \frac{5 \times 10^{-2}}{3300} \text{ acc}_{i/p}$$

$$\text{acc}_{i/p} = \frac{0.25 \times 3300}{5 \times 10^{-2}} = 16,500 \text{ m/s}^2$$


$$\text{In terms of 'g'} \Rightarrow 1683.67g$$

$$(2) \text{ Natural frequency } (\omega_n) = \sqrt{\frac{K}{M}}$$

$$= \sqrt{\frac{3300}{5 \times 10^{-2}}} = \sqrt{\frac{330000}{5}} = \sqrt{\frac{33}{5}} \times 100 \\ = 256.904 \text{ rad/sec}$$

$$f_n = 40.908 \text{ Hz}$$

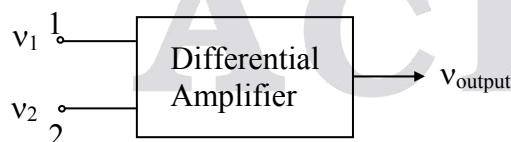**04. (a) (i) Consider a differential amplifier as shown in the figure**



Where the first set of signals is  $v_1 = 50 \mu\text{V}$ ,  $v_2 = -50 \mu\text{V}$  and the second set of signals is  $v_1 = 1050 \mu\text{V}$ ,  $v_2 = 950 \mu\text{V}$ . If the common-mode rejection ratio is 100, calculate the percentage difference in output voltage obtained for the two sets of input signals.

**(10 M)**

- (ii) (1) Repeat part (a)(i), if the common-mode rejection ratio is  $10^5$ . (3 M)  
 (2) Draw the conclusion by comparing part (a)(i) and part (a)(ii)(1). (2 M)  
 (iii) Explain photovoltaic potential in short. (5 M)

**Sol:**

- (i) Case (i): consider the first set of input signals:

$$V_1 = 50\mu V \text{ and } V_2 = -50\mu V$$

$$\text{Step (1): } V_{id} = V_1 - V_2 = 50\mu V - (-50\mu V) = 100\mu V \quad (1) \text{ [Differential mode input]}$$

$$\text{common mode input, } V_c = \frac{V_1 + V_2}{2} = \frac{50\mu V - 50\mu V}{2} = 0$$

Step (2): Total output voltage of the differential amplifier,

$$V_0^1 = A_d V_{id} + A_c V_c$$

$$= A_d V_{id} \left[ 1 + \frac{A_c}{A_d} \left( \frac{V_c}{V_{id}} \right) \right]$$

$$= A_d 100\mu V \left[ 1 + \frac{1}{CMRR} \left( \frac{V_c}{V_{id}} \right) \right]$$

$$= A_d 100\mu V [1 + 0] - (6) [\because V_c = 0]$$

$$\therefore V_0^1 = A_d 100\mu V$$

Case (ii): Consider the second set of input signals  $V_1 = 1050\mu V$  and  $V_2 = 950\mu V$

$$\text{Step (1): Differential mode input, } V_{id} = V_1 - V_2 = 1050\mu V - 950\mu V = 100\mu V$$

$$\text{common mode input, } V_c = \frac{V_1 + V_2}{2} = \frac{1050\mu V + 950\mu V}{2} = 1000\mu V$$

$$\text{Step (2): } V_0^{11} = A_d V_{id} \left[ 1 + \frac{1}{CMRR} \left( \frac{V_c}{V_{id}} \right) \right]$$

$$= A_d 100\mu V \left[ 1 + \frac{1}{100} \left( \frac{1000}{100} \right) \right]$$

$$= A_d 100\mu V [1 + 0.1]$$

$$\therefore V_0^{11} = A_d 100\mu V + A_d 10\mu V = A_d [110\mu V]$$

Step (3): % change in the output,

$$\% \Delta V_0 = \frac{V_0^{11} - V_0^1}{V_0^1} \times 100 = \frac{A_d 10\mu V}{A_d 100\mu V} \times 100$$

% change in output = 10%

(ii) (1) Case(i):  $V_{id} = 100\mu V$  and  $V_C = 0$

$$V_0^1 = A_d V_{id} = A_C V_C = A_d 100\mu V$$

Case (ii)  $V_{id} = 100\mu V$  and  $V_C = 1000\mu V$

$$V_0^{11} = A_d V_{id} \left[ 1 + \frac{1}{CMRR} \left( \frac{V_C}{V_{id}} \right) \right]$$

$$= A_d 100\mu V \left[ 1 + \frac{1}{10^5} \left( \frac{1000}{100} \right) \right]$$

$$= A_d 100\mu V + A_d 100\mu V \times \frac{1}{10000}$$

$$V_0^{11} = A_d 100\mu V + A_d 0.01\mu V = A_d 100.01 \mu V$$

$$\text{Case (iii) } \% \text{ change in output voltage} = \frac{V_0^{11} - V_0^1}{V_0^1} \times 100 = \frac{A_d \times 0.01\mu V}{A_d \times 100\mu V} \times 100$$

$$\therefore \% \Delta V_0 = 0.01\%$$

## (2) Observation

1. In part (a) (i), the percentage change in the output voltage is 10% when the CMRR value is 100.
2. In part (a)(ii) (1), when the CMRR is  $10^5$ , the percentage change in output voltage is just 0.01% only.

**Conclusion:** The error in the output of a differential amplifier due to common mode can be minimized by having high CMRR value in the amplifier (or) A differential amplifier with high CMRR value will have the less tendency to enter into common mode of operation and hence the error in the output of such an amplifier will be almost zero.

- (iii) The Photovoltaic potential is the actual usable solar energy or power once it has been transformed into electricity by photovoltaic systems.

Photovoltaic is the most direct way to convert solar radiation into electricity and is based on the photovoltaic effect. It is quite generally defined as the emergence of an electric voltage between two electrodes attached to a solid or liquid system upon shining light onto this system. Practically all photovoltaic devices incorporate a p-n junction in a semiconductor across which the photovoltage is developed. These devices are also known as solar cells. Light absorption occurs in a semiconductor material. The semiconductor material has to be able to absorb a large part of the solar spectrum. Dependent on the absorption properties of the material, the light is absorbed in a region more or less close to surface.

**04. (b) (i) What is polarization mechanism in dielectric material? Explain active and passive dielectrics with suitable example. (10 M)**

**(ii) Explain cermets. How are they different from fibre reinforced composites? Write four applications of each. (10 M)**

**Sol:**

(i) Polarization occurs due to several microscopic mechanisms and is of four types

- (1) Electronic polarization,  $\alpha_e$
- (2) Ionic polarization,  $\alpha_i$
- (3) Orientational polarization,  $\alpha_o$
- (4) Space - charge polarization,  $\alpha_s$

1) Electronic polarization,  $\alpha_e$ :

It is defined as the electric strain produced in an atom due to the relative displacement of electron cloud and the positive nucleus in electric field.

$$\text{Electronic polarizability } \alpha_e = 4\pi\epsilon_0 R^3$$

$$F-m^2 \quad (R - \text{Radius of the atom})$$

Thus it is proportional to the volume of the atom and is independent of temperature. It is present in all materials and is fastest of all polarizabilities.

2) Ionic polarization,  $\alpha_i$  :

It occurs in ionic solids only and is due to the displacement of cations and anions in opposite directions to the applied field.

$$\alpha_i = \frac{\mu}{E} = \frac{e^2}{\omega_0^2} \left[ \frac{1}{M} + \frac{1}{m} \right]$$

OR  $\alpha_i = \frac{e^2}{\omega_0^2 m^*}$

$\alpha_i$  is inversely proportional to the square of the natural frequency of the ionic molecule and to its reduced mass and is independent of temperature.

3) Orientational polarization,  $\alpha_o$ :

This occurs in polar solids only and is due to the presence of polar molecules in the dielectric. These molecules posses permanent dipole moments even without field. But they are randomly oriented. When an external field is applied these dipoles try to align themselves in the direction of the field giving rise to Orientational Polarization.

$$\alpha_o = \frac{\mu^2}{3kT}$$

Where  $\mu$  is dipole moment of each atom.

Thus it is inversely proportional to absolute temperature.

4) Space - charge polarization,  $\alpha_s$ :

Space - charge polarization occurs due to the accumulation of charges at the electrodes or at the interfaces in a multi phases material. The ions diffuse over appreciable distances in response to the applied field, giving rise to redistribution of charges in the dielectric medium. It is found in ferrites and semiconductors and is negligibly small.

Therefore, total polarizability of the material is

$$\begin{aligned} \alpha &= \alpha_e + \alpha_i + \alpha_o \\ &= 4\pi\epsilon_0 R^3 + \frac{e^2}{\omega_0^2} \left[ \frac{1}{M} + \frac{1}{m} \right] + \frac{\mu^2}{3KT} \end{aligned}$$

We have  $\mu_e = \alpha_e E$

where  $\alpha_e$  is the electronic polarizability.

$$\alpha_e = 4\pi\epsilon_0 R^3$$

$$\text{Polarization, } P_e = N\mu_e = N\alpha_e E$$

Where 'N' is the number of atoms/ m<sup>3</sup>

$$P_e = \epsilon_0 E (\epsilon_r - 1) = N\alpha_e E$$

$$(\epsilon_r - 1) = \frac{N\alpha_e}{\epsilon_0}$$

$$\alpha_e = \frac{\epsilon_e (\epsilon_r - 1)}{N}$$

S.No	Active dielectric	Passive dielectric
1.	Dielectric which can easily adapt itself to store the electrical energy in it is called active dielectric	Dielectric which restricts the flow of electrical energy in it are called passive dielectrics.
2.	Examples: Piezo electric, Ferro electrics	Examples: Glass, mica, plastic
3.	It is used in the production of ultrasonics.	It is used in the production of sheets pipes, etc.,

(ii) Cermets:- cermets are compounds of ceramics and metals. cermets are composite material. A cermet is designed to have the optical properties of both a ceramics, such as high temperature resistance and hardness, and those of a metal, such as ability to undergo plastic deformation.

Application of cermets:

- (1) resistor, capacitor and vacuum tubes.
- (2) space craft shields
- (3) transport vehicle breaks and clutches.
- (4) storage of nuclear waste, fabrication of nuclear reactor.

Fiber reinforced composites:- In fiber reinforced composites, the reinforcement phase materials are in the form of wires, fibers and whiskers surrounded by these fibers polymer matrix phase present.

Application of Fiber reinforced composites:

- (1) optical fiber (GFRP)
- (2) Transportation vehicle glasses (GFRP)
- (3) Sports goods (CFRP)
- (4) bullet proof jackets (AFRP)

**04. (c) (i) What are the elements of a generalized data acquisition system? Draw a multi-channel data acquisition system using single A/D converter and briefly explain its working.**

**(14 M)**

**(ii) Explain, with a diagram, the operation of a force balance current telemetering system.**

**(6 M)**

**Sol:**

(i) **DAQ:** Data Acquisition is a process of achieving the information of a process variable (like temperature, press, flows etc) in the required format.

A DAQ system typically consists of there following elements

- (1) Transducers
- (2) Signal conditioning equipment
- (3) Multiplexer
- (4) Signal converter
- (5) A/D converter
- (6) Auxillary equipment
- (7) Digital recorders
- (8) Digital printers.


(1) **Transducers:** They convert a physical quantity into an electrical signal which is acceptable by the data acquisition system.

Eg: Thermocouple, strain gauge

(2) **Signal conditioning equipment:** Signal conditioning equipment provides any equipment that assists in transforming the output of transducers to the desired magnitude or form required by the next stage of the DAQ system. They may include devices for amplifying, refining, attenuation, altering.

Eg: Op-Amp, Divider, Filter

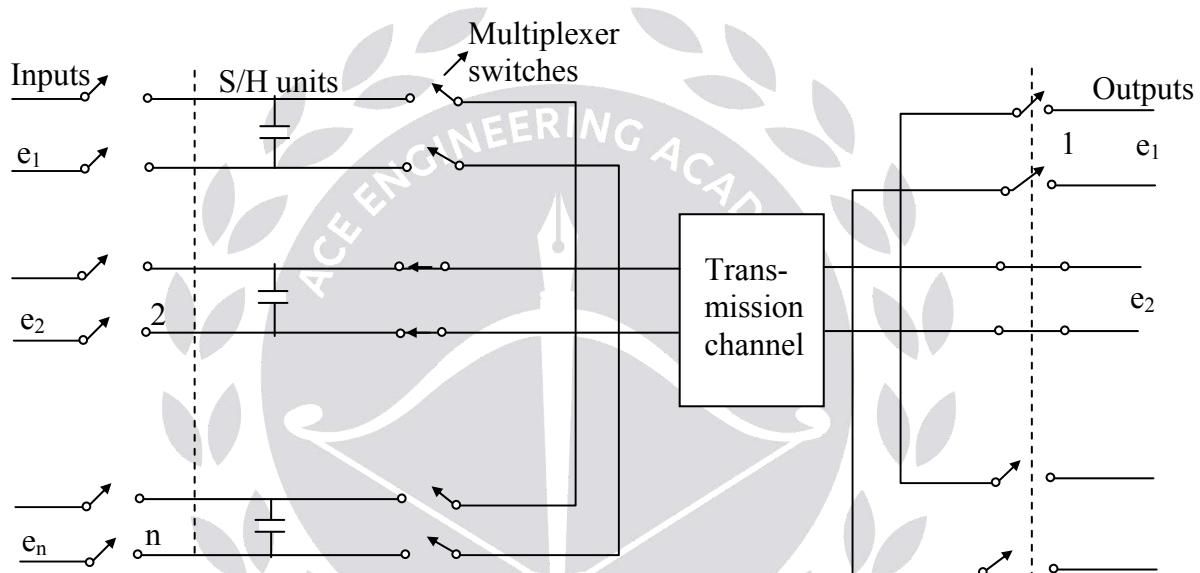(3) **Multiplexer:** Multiplexing is the process of sharing a single channel with more than one output. Thus a multiplexer accepts analog inputs and connects them sequentially to one measuring instrument another name for a multiplexer is “scanner”.



(4) **A/D converter:** ADC will convert analog voltage to its equivalent digital form.


(5) **Auxiliary equipment:** This contains devices for system programming functions and digital processing. Some of typical functions done by auxiliary equipment are linearization and limit comparison of signals.

(6) **Digital recorders:** Records information in digital form.

Eg: Floppy disks, magnetic tapes

(7) **Digital printers:** A digital printer can be specified to interface with an electronic instrumentation system in codes to perform this work.

### Multichannel DAQ system:

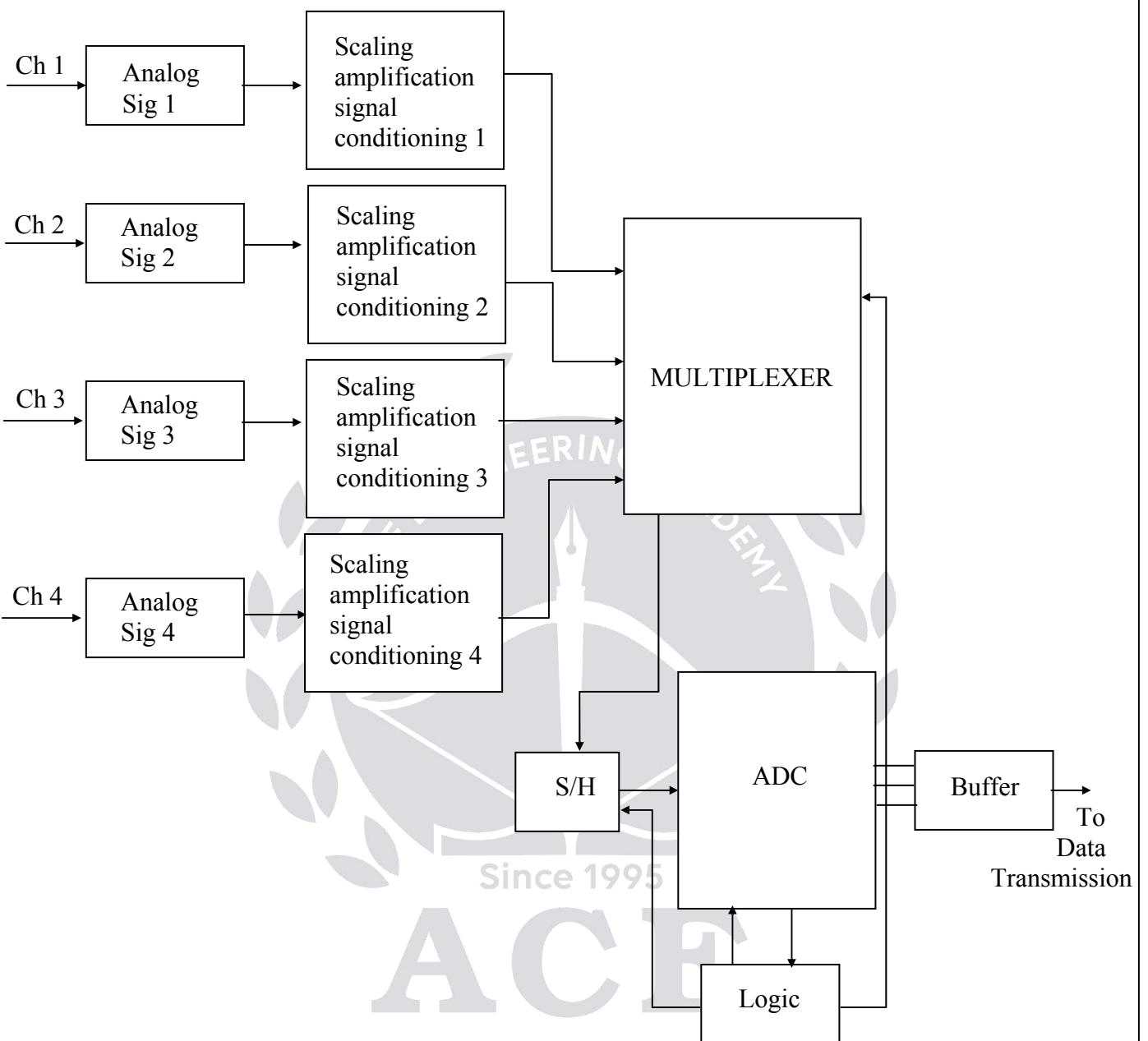

There will be many systems in DAQ. They can be time shared by two or more input devices.


The above figure shows a multichannel DAQ system. It has a signal ADC preceeded by multiplexer.

As shown in figure, there are 4 channels analog in nature. There can be number of input's. Each signal is given to individual amplifiers. The output of the amplifiers is given to signal condition circuits. From the output of signal conditioning circuits the signals go to the multiplexer. The multiplexer output is converted into digital signals by A/D converter sequentially.

The multiplexer stores the data say of the first channel in the sample hold circuit. It then seeks the second channel. During this interval the data of the first channel will be converted into digital form. This permits utilization of time more efficiently.

When once conversion is complete the status line from the converter causes the sample/hold circuit to return to the sample mode. It then accepts the signal of next channel. After acquisition of data either immediately or on a command the S/H circuit will be switched to hold mode. Now conversion begins and MUX selects the next channel.
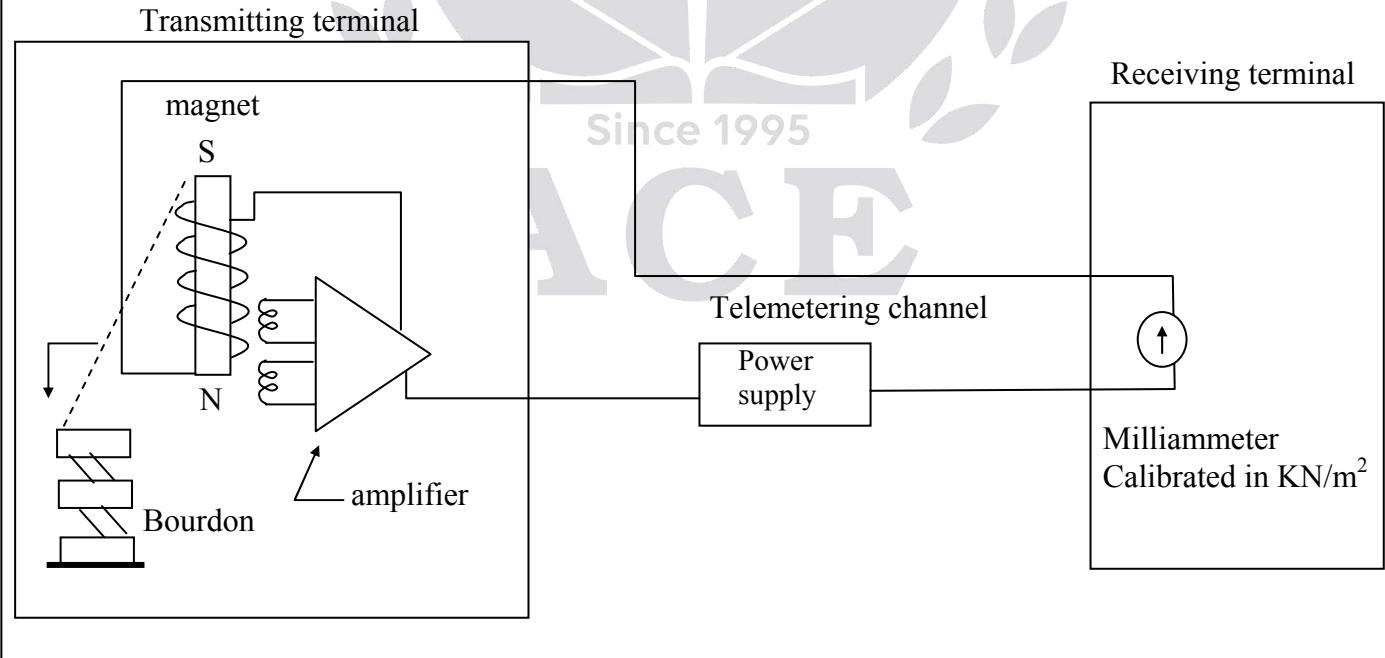
## (ii) Force Balance Current Telemetry System:




A Force Balance System, in this system a part of the current output is feedback to oppose the motion of the input variable. The system is operated by the bourdon tube which rotates the feedback coil which in turn changes the flux linkages between the primary and secondary coils. The change in flux linkages varies the amplitude of amplifier. The output signal is connected to the feedback force coil which produces a force opposing the bourdon tube input.

A force balance system increases the accuracy as smaller motions are required which result in better linearity.


## SECTION-B

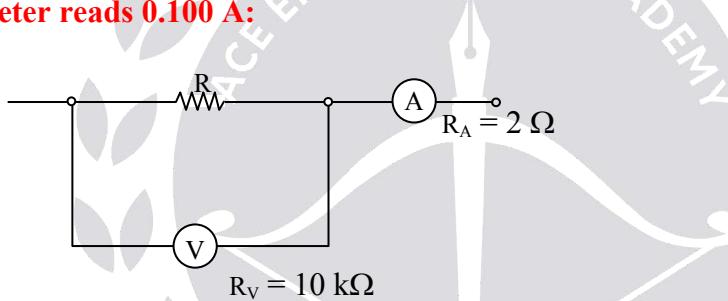**05. (a) (i) Find the value of resistance  $R$  in the figure below if the voltmeter reads 12 V and ammeter reads 0.100 A:**



(6 M)

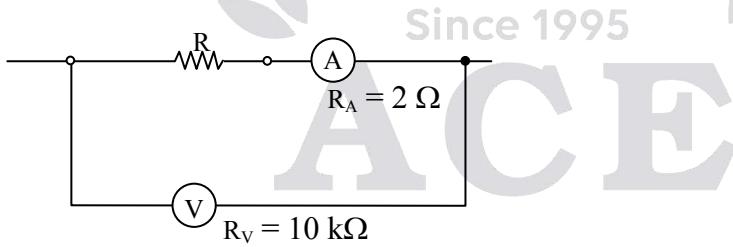**(ii) Repeat part (a)(i) for the circuit arrangement given in the figure below**



(6 M)


**Sol:**

(i) Given data,

Voltmeter reading = 12V

ammeter reading = 0.100A

The given circuit can be redrawn as

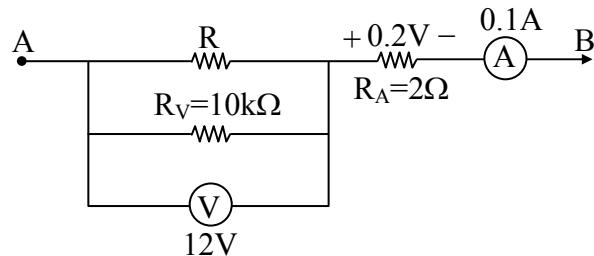

$\therefore$  Total voltage drop across the terminal AB =  $12 + 0.2 = 12.2\text{V}$

Total resistance across the terminal AB =  $(R//10\text{k}) + 2$

$$\therefore \text{Current flowing through terminal AB} = \frac{\text{Voltage drop}}{\text{Total Resistance}}$$

$$\Rightarrow 0.1 = \frac{12.2}{2 + (R//10\text{k})}$$

$$\Rightarrow 2 + \frac{10^4 R}{10^4 + R} = 122$$


$$\Rightarrow \frac{10^4 R}{10^4 + R} = 120$$

$$\Rightarrow \frac{10^4 + R}{R} = \frac{10^4}{120}$$

$$\Rightarrow \frac{10^4}{R} + 1 = \frac{10^4}{120}$$

$$\Rightarrow \frac{10^4}{R} = \frac{10^4}{120} - 1 \Rightarrow R = 121.45\Omega$$

(ii) Redraw the given circuit

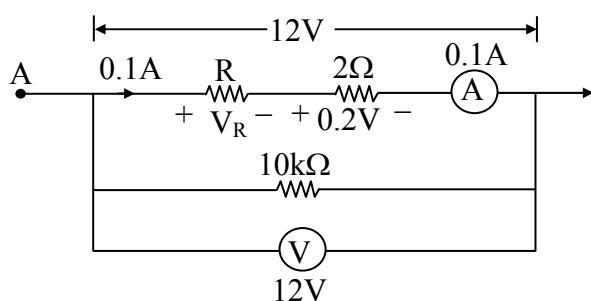

$$\therefore V_R = 12 - 0.2$$

$$\Rightarrow V_R = 11.8V$$

$$\therefore R = \frac{V_R}{0.1A}$$

$$\Rightarrow R = \frac{11.8}{0.1}$$


$$\Rightarrow R = 118\Omega$$

**05. (b) Copper has an atomic radius of 0.1278 nm. Calculate the atomic density (number of atoms per unit) in (1 0 0) plane of copper (FCC). (12 M)**

**Sol:** Cu is FCC structure material .

$$4R = \sqrt{2} a$$
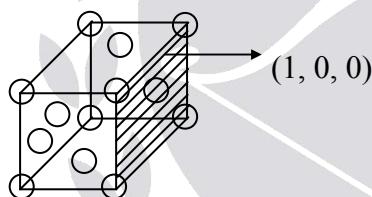
$$a = \frac{4R}{\sqrt{2}} = \frac{4 \times 0.1278}{\sqrt{2}} \text{ nm} = 0.36147 \text{ nm}$$



Number of atoms in (100) = 2

$$\text{Planar density} = \frac{2}{a^2} = \frac{2}{(0.3614)^2} = \frac{2}{0.13066} = 15.306 \text{ atoms/nm}^2$$

**05. (c) How can you convert a galvanometer into an ammeter and a voltmeter? A PMMC galvanometer of  $6 \Omega$  resistance reads up to 60 mA. Determine the value of the resistance (i) when connected in parallel to enable the instrument to read up to 1.20 A and (ii) when connected in series to enable it to read 12 V. (12 M)**

**Sol:** A Galvanometer can be converted into an ammeter by connecting a small value resistance in parallel.


A Galvanometer can be converted into a voltmeter by connecting a high value resistance in series.

$$\text{Galvanometer resistance } (R_m) = 6\Omega$$


$$\text{Current } (I_{fsd}) = 60 \text{ mA} \quad (0 - 60 \text{ mA})$$

$$\text{Galvanometer Voltage } (V_m) = I_{fsd} R_m = 60 \text{ mA} \times 6 = 360 \text{ mV} \quad (0 - 360 \text{ mV})$$

**(i)** As a Ammeter Conversion

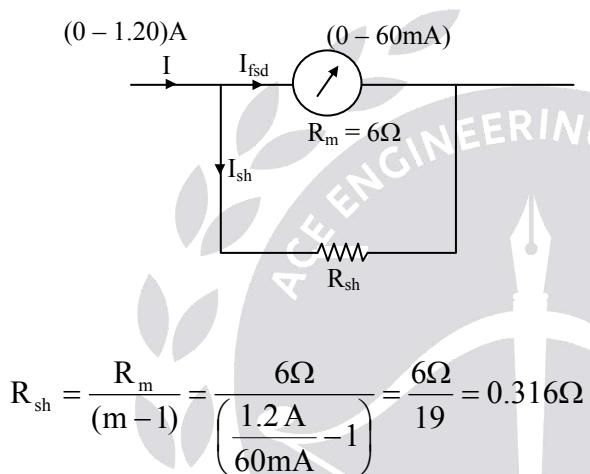

**(ii)** As a Voltmeter Conversion

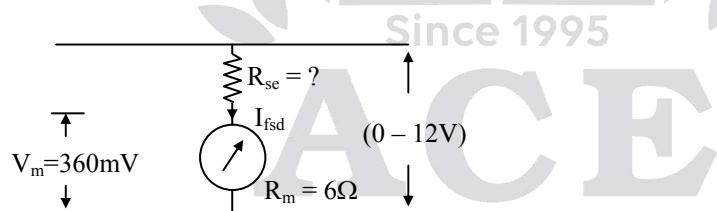

$$R_{se} = R_m(m-1) \Rightarrow R_{se} = 6\Omega \left( \frac{12 \text{ V}}{360 \text{ mV}} - 1 \right) = 194\Omega$$



www.aceenggacademy.com



**ACE**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs

**GATE 48**  
All India 1<sup>st</sup> Ranks

**ESE 11**  
All India 1<sup>st</sup> Ranks

LAUNCHING



## DIGITAL CLASSES

for GENERAL STUDIES &amp; ENGINEERING APTITUDE - ESE

### New Batches @ HYDERABAD

#### GATE+PSUS – 2020

Regular Batches : 24<sup>th</sup> June, 01<sup>st</sup>, 08<sup>th</sup>, 22<sup>nd</sup> July, 5<sup>th</sup> & 20<sup>th</sup> Aug 2019  
Spark Batch : 24<sup>th</sup> June, 2019

#### ESE+GATE+PSUS – 2020

Spark Batch : 24<sup>th</sup> June, 2019  
Regular Batches : 24<sup>th</sup> June & 8<sup>th</sup> July 2019  
General Studies Batch : 12<sup>th</sup> July 2019

#### GATE+PSUS – 2021

Morning & Evening  
Batches : 12<sup>th</sup> July & 10<sup>th</sup> August 2019

#### ESE+GATE+PSUS – 2021

Morning Batches :  
12<sup>th</sup> July & 10<sup>th</sup> August 2019

#### GENCO / TRANSCO

29<sup>th</sup> June 2019

#### HEAD OFFICE

# 4-1-1236/1A, Sindhu Sadan, King Koti, Abids, Hyderabad – 500001.  
040-23234418, 19, 20, 040-24750437  
hyderabad@aceenggacademy.com  
www.aceenggacademy.com

DILSUKH NAGAR : 040-40044451, 40209345

KUKATPALLY : 040-40199966, 93476 99966

KOTHAPET : 040 – 24034418/19

### OUR GATE – 2019 TOPPERS



and many more...

G	TOP 10	TOP 100	E	TOP 10	TOP 100	G	TOP 10	TOP 100	M	TOP 10	TOP 100	C	TOP 10	TOP 100	I	TOP 10	TOP 100	P	TOP 10	TOP 100
9	74	7	7	71	5	44	6	60	5	28	10	74	10	49						

### OUR ESE – 2018 TOP RANKERS



and many more...

TOTAL SELECTIONS : 350 | E&amp;T : 89 | EE : 80 | CE : 92 | ME : 89



TO WIN THE RACE...  
JOIN ACE...



Scan for New Batches

HYDERABAD | AHMEDABAD | DELHI | BHOPAL | PUNE | BHUBANESWAR | LUCKNOW | PATNA | BENGALURU | CHENNAI | VIJAYAWADA | VIZAG | TIRUPATHI | KOLKATA



with 3.20 CGPA



B.Tech Courses\*



**ACE**  
Engineering College  
(Approved by AICTE & Affiliated to JNTUH)

EAMCET CODE  
**ACEG**

📍 Ghatkesar, Hyderabad ☎ 9133308468, 9912391169, 9133308533 ✉ aceenggcollege@gmail.com 🌐 www.aceec.ac.in



Scan QR Code for more details

On-Campus  
Hostel Facility  
for Boys & Girls

Sponsored by : Yadala Satyanarayana Memorial Educational Society | Powered by : ACE Engineering Academy (Leading Institute for ESE / GATE / PSUs)

### COURSES OFFERED


B.Tech (UG) CSE\* 180 ECE\* 180 CIVIL 120 MECH\* 120 EEE\* 60 IT\*\* 60

\*\* Subject to Approval of JNTUH

### WHY ACE..?

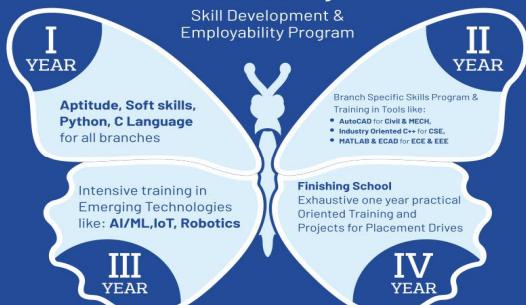
#### The Butterfly

Skill Development &amp; Employability Program



Entrepreneurship Development Cell | Guidance for GATE, GRE, TOEFL, GMAT and CAT  
Centre of Excellence in AI / ML, IoT and JHUB | National Service Scheme (NSS)

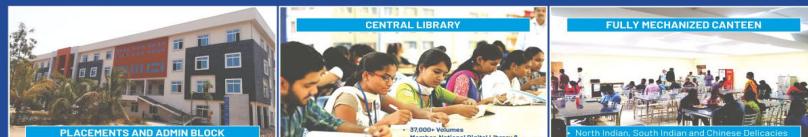Department Technical Clubs: •CIVIL-Spanzors •EEE-Phasor •MECH-Mechizaya •ECE-Tektronix •CSE-Cybernetics



#### OUR EMINENT RECRUITERS (A.Y. 2018-19)

- TCS - 21
- Wipro - 18
- Amazon - 16
- Cognizant - 13
- Cyient - 03
- Xiaomi - 31
- Mu Sigma - 01
- Hitachi - 02
- AAIC - 05
- Infosys - 01
- Optum - 03

and many more..

#### INDUSTRY ASSOCIATION WITH

- AICTE-BENNET University
- Microsoft Innovation Centre
- TCS-IDN Program
- HCL Technologies Pvt.Ltd.
- Larsen Toubro (L&T)
- Cyient
- Aspiring Minds
- eCubes
- eLitmus
- TASK

and many more..





# MPSC (MES) MAINS 2019

(Civil Engineering)

Regular Batch starts on **15th July 2019**

## DISCOUNTS AVAILABLE

For ACE students of 2018-19 Session	50%
For ACE students of 2017-18 Session	30%
For ACE students of 2016 earlier	20%

# MPSC (MES) MAINS FREE Orientation & Demo

On 6<sup>th</sup> July 2019

IES GENERAL STUDIES BATCH				
Type of Batch	Timings	Date	Duration	Venue
Weekend Batch	6 to 8 hours of classes Sat: 10am to 7pm & Sun 8am to 6pm	13 <sup>th</sup> July 2019	4 to 5 Months	@ Pune



Ranks in  
**Top 1000**  
from **Pune**




Ranks in  
**Top 2000**  
from **Pune**



Ranks in  
**Top 3000**  
from **Pune**

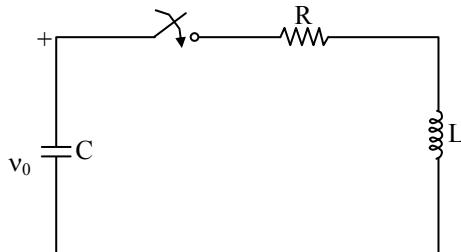05. (d) In the circuit below,  $v_C(0^-) = v_0$ , while the inductor is no charged. The switch that is initially open is closed at  $t = 0$ . Also  $L = C$  in terms of numerical value. Find  $R$  (positive value) so that the circuit is critically damped (12 M)




**Sol:** Given data,

$$V_0(0^-) = V_0$$

$$L = C$$

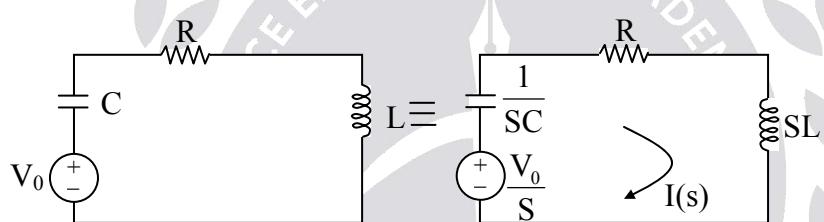The given circuit for  $t > 0$  is shown below



$$\begin{aligned} \therefore I(s) &= \frac{V_0 / S}{R + SL + \frac{1}{SC}} \\ &= \frac{V_0}{SR + S^2L + \frac{1}{C}} \\ &= \frac{V_0}{LS^2 + SR + \frac{1}{C}} \\ &= \frac{V_0}{L\left(S^2 + S\frac{R}{L} + \frac{1}{LC}\right)} \end{aligned}$$

$$\Rightarrow I(s) = \frac{V_0 / L}{S^2 + \frac{R}{L}S + \frac{1}{LC}} \quad \dots\dots(1)$$

∴ The characteristics equation for equation (1) is  $S^2 + \frac{R}{L}S + \frac{1}{LC} = 0$

Now if we compare equation (1) with standard equation  $S^2 + 2\xi\omega_n S + \omega_n^2 = 0$

$$\omega_n^2 = \frac{1}{LC} \text{ and } 2\xi\omega_n = \frac{R}{L} \Rightarrow \xi = \frac{R}{L(2\omega_n)}$$

$$\Rightarrow \omega_n = \frac{1}{\sqrt{LC}}$$

$$\therefore \xi = \frac{R}{L} \times \frac{\sqrt{LC}}{2}$$


$$\Rightarrow \xi = \frac{R}{2} \sqrt{\frac{C}{L}} \quad \dots\dots\dots(2)$$

∴ for critically damped,  $\xi = 1$

∴ From equation (2)

$$\frac{R}{2} \sqrt{\frac{C}{L}} = 1$$
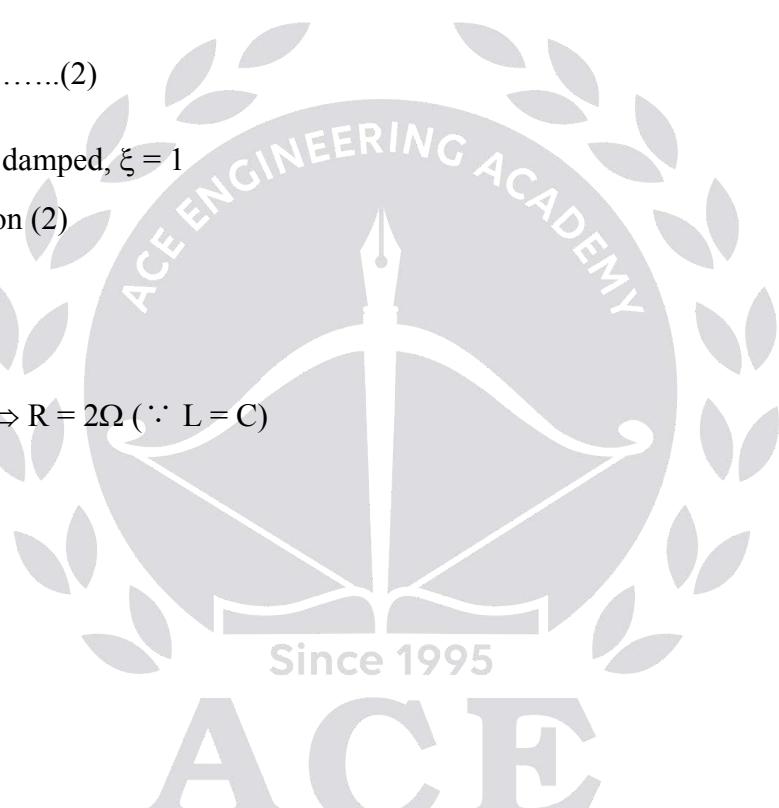
$$\Rightarrow R = 2\sqrt{\frac{L}{C}} \Rightarrow R = 2\Omega \quad (\because L = C)$$



**ACE**



## Hearty Congratulations to our **GATE-2019 TOPPERS**

AIR

**1**



PRAKHAR  
SINGH  
CE

AIR

**1**



RAJAT  
SONI  
EC

AIR

**1**



PRANAV  
SHARMA  
CSIT

AIR

**1**



SHASHANK  
MANGAL  
IN

AIR

**1**



SURYA  
NARAYANA  
PI

and many more...

### GATE-2019 TOPPERS from Pune Classroom Program



SAISH KALASKAR  
IN-AIR-07



RANJIT KUMAR  
ECE-AIR-08



GAURAV JADHAV  
ME-AIR-11



OMKAR LATUR  
ME-AIR-12



RUCHA JOSHI  
ECE-AIR-40



MANASWINEE THAKUR  
ECE-AIR-49



TAHAA SHABBIR  
ME-AIR-52



SHUBHAM SHUKLA  
ECE-AIR-72



OMKAR THORAT  
ECE-AIR-97



SHRADDHA PANDEY  
CSIT-AIR-98



SAMADHAN BORKAR  
ME-AIR-104



K N PRIYAPRAVAS  
PI-AIR-105



AKASH D SHINDE  
CE-AIR-106



SS DESHMUKH  
XE-AIR-111



KRISHNA CHAITANYA  
ME-AIR-133



VAIBHAV BANAJWADE  
EE-AIR-140



ASHUTOSH AGARWAL  
CE-AIR-147



ABRUTI A. PANDA  
ECE-AIR-158



ADITYA KOLTE  
IN-AIR-160



KAGESH PIMPARKAR  
IN-AIR-171



B D PRADEEP  
IN-AIR-222



SIDDHESH BORSE  
IN-AIR-229



SANDESH GAIKWAD  
ME-AIR-268



ASHISH K. SHISODE  
IN-AIR-277



RIZWAN K.M.  
ME-AIR-294



MAYUR VISHE  
EE-AIR-339



SHUBHAM DANKONDWAR  
CSIT-AIR-350



SHWETA KULKARNI  
ECE-AIR-444



AAYUSH CHAUDHARY  
CSIT-AIR-465



SAURABH BHAVISKAR  
ME-AIR-471

and many more...

### MPSC (MES) 2018 Qualified Students from Pune

MPSC (MES)



CE  
AJIT WAOLVE



CE  
BHUSHAN KHANDARE



CE  
PAYAL DIVE



CE  
GANESH PATIL



CE  
GAURAV MALVE



CE  
SUHAS GAVIT



CE  
PANKAJ GOSAVI



CE  
VISHAL KARAD



CE  
VINOD KHADE



CE  
MINAL PAWAR



CE  
NITIN SONWANE



CE  
KUNAL PAKAL



CE  
SHRADDHA KULKARNI



CE  
VANASHRI DHAYTADAK

ESE+GATE  
+PSUs-2020  
Streams: CE/ME/EC/EE

GATE+PSUs  
2020  
Streams: CE/ME/EC/EE

ESE+GATE  
+PSUs-2021  
(Two Years Integrated program)  
Streams: CE/ME/EC/EE/IN/CS/IT/PI

83

Ranks in  
Top 1000  
from Pune

121

Ranks in  
Top 2000  
from Pune

153

Ranks in  
Top 3000  
from Pune

Regular Batches  
Commence

01<sup>st</sup> July 2019

Regular Batches  
Commence

1<sup>st</sup> July 2019  
15<sup>th</sup> July 2019

Weekend Batches  
Commence

6<sup>th</sup> July &  
17<sup>th</sup> August  
2019

### MPSC (MES) MAINS 2019

(Civil Engineering)

Regular Batch starts on **15th July 2019**


• 020- 25535950, 09343499966

• [www.aceenggacademy.com](http://www.aceenggacademy.com)


INTERVIEWS

05. (e) In the feedback circuit shown in the figure below,  $h_{fe}$  is very large. Identify the type of feedback, and (i) find the feedback factor  $\beta$  and overall transresistance with feedback and

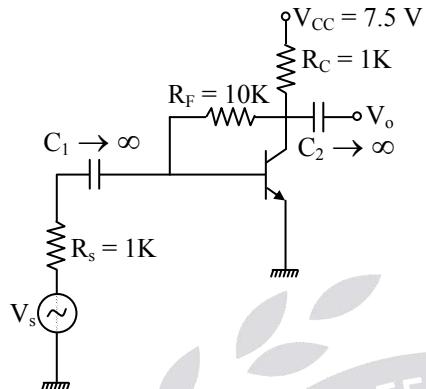(ii) overall voltage gain,  $A_{vs} = \frac{V_o}{V_s}$ : (12 M)



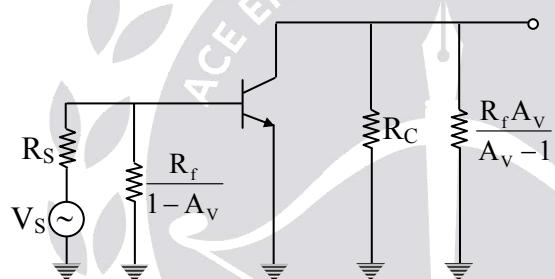**Sol:** The given circuit can be redrawn as shown below using miller's theorem: (AC model)




**NOTE:** In the given circuit output is voltage and feedback signal is current.

Hence it is voltage-shunt (or) shunt-shunt type of feedback

(i) Step (1)  $R_L = R_C // R_f \frac{A_v}{A_v - 1} = R_C // R_f$  (1) [ $\because h_{fe}$  is large,  $A_v$  is large]

$$\Rightarrow R_L = 1k // 10k = 0.9k\Omega \quad (2)$$

Step (2): small signal model

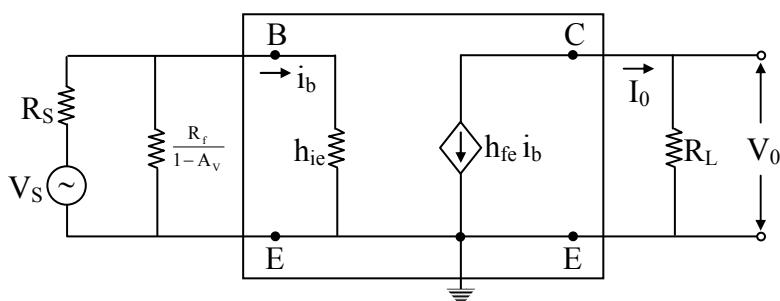

Transresistance gain without feedback,

$$R_M = \frac{V_0}{i_b} = -\frac{h_{fe} i_b R_L}{i_b} = -h_{fe} R_L \quad (3)$$

$$\text{Feed back factor, } \beta = \frac{I_f}{V_0} \quad (4)$$

KVL for (Base) B to (Collector)C loop of BJT

$$V_i - I_f R_f - V_0 = 0 \quad (5)$$

$$I_f R_f = V_i - V_0 \approx -V_0 \quad (6) \quad [\because V_i \ll V_0]$$

$$\therefore \frac{I_f}{V_f} = \beta = -\frac{1}{R_f} = -\frac{1}{10k\Omega} \quad (7)$$

Step (3):

$$\text{Overall transresistance with feedback, } R_{M_f} = \frac{R_M}{1 + R_M \beta} \quad (8)$$


$$= \frac{-h_{fe} R_L}{1 + \left( -h_{fe} R_L \left( -\frac{1}{R_f} \right) \right)} \quad (9)$$

$$= \frac{-h_{fe} R_L}{h_{fe} \frac{R_L}{R_f}} \quad (10) \quad [\because h_{fe} \text{ is large}]$$

$$= -\frac{0.9k\Omega}{0.9k\Omega} \quad (11)$$

$$\therefore R_{M_f} = \frac{V_0}{I_s} = -10k\Omega \quad (12)$$

(ii) Consider the given circuit

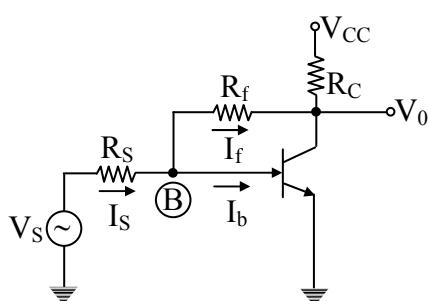

Method (1):

Step (1) KCL at node (B):

$$I_S = I_f + i_b \approx I_f \quad (1) \quad [\because h_{fe} \text{ is large } i_b \approx 0]$$

$$\Rightarrow \frac{V_s - V_b}{R_s} = \frac{V_b - V_0}{R_f} \quad (2)$$

step (2): In a BJT, the AC voltage at base and Emitter is always equal i.e  $V_b = V_e \quad (3)$


in the given circuit,  $V_b = V_e = 0 \quad (4) \quad [\because \text{Emitter is grounded}]$

Step (3): Equation (4) in equation (2)

$$\frac{V_s - 0}{R_s} = \frac{0 - V_0}{R_f} \quad (5)$$

$$\frac{V_0}{V_s} = A_{v_s} = -\frac{R_f}{R_s} = \frac{-10k\Omega}{1k\Omega} = -10 \quad (6)$$

Method: (2)

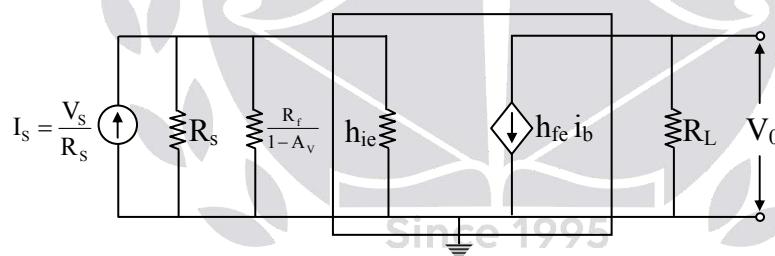

$$A_{v_s} = \frac{V_0}{V_s} = \left( \frac{V_0}{I_s R_s} \right) = \frac{R_{M_f}}{R_s} = \frac{-10k\Omega}{1k\Omega} = -10 \quad (1) \quad \left[ \because R_{M_f} = \frac{V_0}{I_s} = -10k \right]$$



## New Batches @ Bengaluru

### Regular Batches For GATE + PSUs – 2020

Type of Batch	Timings	Date	Duration	Venue
Regular Batch	Six Days a Week 6 to 8 Hours Per Day	8 <sup>th</sup> July 2019	5 to 6 Months	@ Bengaluru

### INTEGRATED PROGRAM GATE + PSUs – 2021

Type of Batch	Timings	Date	Duration	Venue
Weekend Batch	Sat 2:30 pm to 7:30 pm Sun 8am to 8pm	3 <sup>rd</sup> August 2019	14 to 16 Months	@ Bengaluru

## KPTCL - AE & AEE **Online** Test Series

Karnataka Power Transmission Corporation Limited

**No. of Tests : 16**

Subject Wise Tests : 13 | Mock Tests - 3


**Electrical Engineering**

Starts From **8<sup>th</sup> June 2019**

All tests will be available till KPTCL Examination

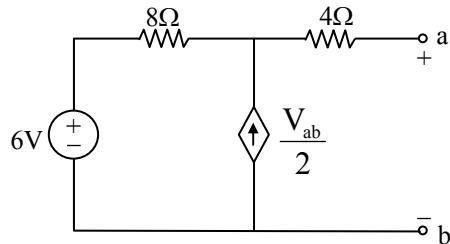
**06. (a) (i)** A voltage source delivers 4 A when the load connected is  $5\Omega$  and 2 A when the load is  $20\Omega$ . What is the maximum power it can deliver? Also calculate power transfer efficiency with  $R_L = 5\Omega$  and power transfer efficiency when it delivers 50 W. (10 M)

**(ii)** Find the thevenin equivalent of the circuit at a-b :



(10 M)

**Sol:**

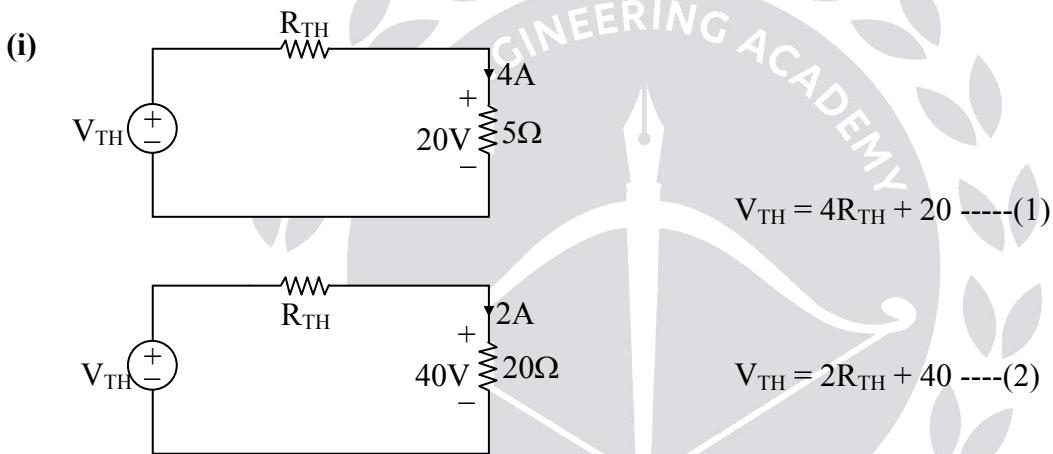

$$V_{TH} = 4R_{TH} + 20 \quad \dots(1)$$

$$V_{TH} = 2R_{TH} + 40 \quad \dots(2)$$

$$\text{equation (2)} - \text{equation (1)}$$

$$-2R_{TH} + 20 = 0 \Rightarrow 2R_{TH} = 20$$

$$R_{TH} = 10\Omega$$

Now, put the value of  $R_{TH} = 10\Omega$  in equation (1)


$$\therefore V_{TH} = 4(10) + 20$$

$$\Rightarrow V_{TH} = 60 \text{ Volts}$$

The maximum power that can be delivered,  $P_{max} = \frac{V_{TH}^2}{4R_{TH}}$

$$\Rightarrow P_{max} = \frac{(60)^2}{4 \times 10} = 90 \text{ Watts}$$
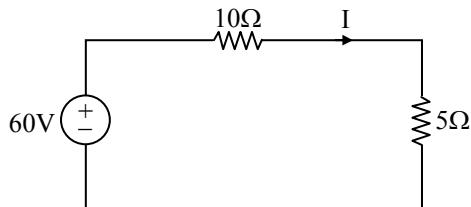
### Power transfer efficiency with $R_L = 5\Omega$ :-



$$I = \frac{60}{15} = 4A$$


$$P_{in} = (60)(4) = 240$$

$$P_{out} = (4)^2(5) = 80$$

$$\text{Power transfer efficiency } (\eta) = \frac{P_{out}}{P_{in}} \times 100 = \frac{80}{240} \times 100$$

$$\eta = 33.33\%$$
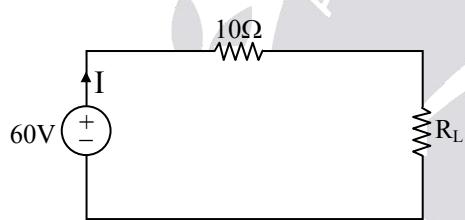
### Power transfer efficiency for 50W delivery:-



$$P_{deli} = 50W \quad (P_{in} = 50W)$$

$$\Rightarrow 50 = 60 I$$

$$\Rightarrow I = \frac{5}{6} A$$

$$\text{By KVL, } 60 - 10I - R_L I = 0$$

$$\Rightarrow 60 = \frac{50}{6} + \frac{5R_L}{6}$$

$$\Rightarrow 360 = 50 + 5R_L$$


$$\Rightarrow R_L = 62\Omega$$

$$\therefore P_{out} = I^2 R_L = \left(\frac{5}{6}\right)^2 \times 62$$

$$\Rightarrow P_{\text{out}} = 43.05 \text{ Watts}$$

$$\therefore \text{Power transfer efficiency } (\eta) = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100 = \frac{43.05}{50} \times 100 = 86.11\%$$

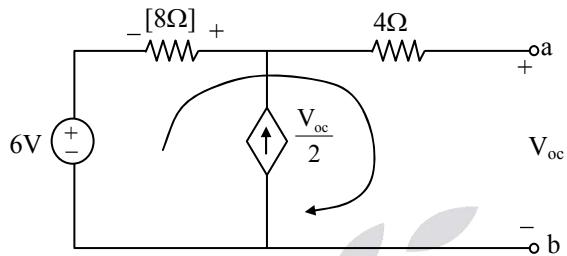**(ii) Calculation of  $V_{\text{oc}}$ :**




$$\text{KVL, } -6 - \frac{V_{\text{oc}}}{2}(8) + V_{\text{oc}} = 0$$

$$V_{\text{oc}} - 4V_{\text{oc}} = 6$$

$$-V_{\text{oc}} = 6 \Rightarrow V_{\text{oc}} = -2 \text{ volts}$$


**Calculation of  $I_{\text{SC}}$ :**

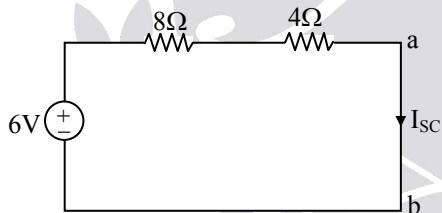

$$I_{\text{sc}} = \frac{6}{12} = \frac{1}{2} \text{ A}$$

$$R_{\text{TH}} = \frac{V_{\text{oc}}}{I_{\text{sc}}} = \frac{-2}{1/2} = -4\Omega$$

**Thevenin equivalent circuit:**

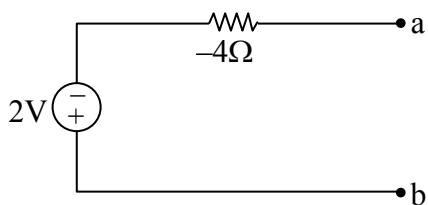



## New Batches @ Hyderabad

### Regular Batches For GATE + PSUs – 2020

Type of Batch	Timings	Date	Duration	Streams & Venue
Regular Batch	4 to 6 Hours	8 <sup>th</sup> July 2019	5 to 6 Months	CS (Abids)
		22 <sup>nd</sup> July 2019		CE (Kothapet, Kukatpally)
		05 <sup>th</sup> August 2019		IN, PI (Dilsukhnagar)
		20 <sup>th</sup> August 2019		EC, EE, ME (DSNR, KKP)

### Regular Batches For ESE + GATE + PSUs – 2020

Type of Batch	Timings	Date	Duration	Streams & Venue
Regular Batch	6 to 8 Hours	8 <sup>th</sup> July 2019	7 to 9 Months	EC, EE (DSNR) ME, CE (Kothapet)

### IES GENERAL STUDIES BATCH

Type of Batch	Timings	Date	Duration	Venue
Regular Batch	4 to 6 hours	12 <sup>th</sup> July 2019	55 to 60 Days	@ Abids


### Long Term Program for GATE + PSUs – 2021

Type of Batch	Timings	Date	Duration	Streams & Venue
Morning Batch	6 am to 8 am	12 <sup>th</sup> July & 10 <sup>th</sup> August 2019	15 to 16 Months	EC, EE, CE, ME, CSIT & IN @ Abids
Morning Batch	6 am to 8 am	12 <sup>th</sup> July & 10 <sup>th</sup> August 2019	15 to 16 Months	EC, EE, ME @ Dilsukhnagar
Evening Batch	6 pm-8.30 Pm	12 <sup>th</sup> July & 10 <sup>th</sup> August 2019	15 to 16 Months	EC, EE, ME @ Dilsukhnagar
Morning Batch	6 am to 8 am	12 <sup>th</sup> July & 10 <sup>th</sup> August 2019	15 to 16 Months	CE @ Kothapet
Evening Batch	6 pm-8.30 Pm	12 <sup>th</sup> July & 10 <sup>th</sup> August 2019	15 to 16 Months	CE @ Kothapet
Morning Batch	6 am to 8 am	12 <sup>th</sup> July & 10 <sup>th</sup> August 2019	15 to 16 Months	EC, EE, CE, ME, CSIT & IN @ Kukatpally
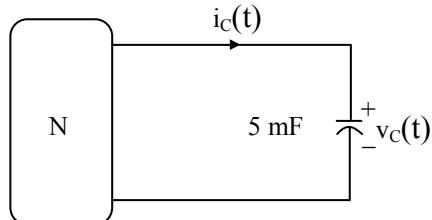
## MPSC (MES) MAINS 2019 (CE)


Regular Batch starts on **15th July 2019**

**06 (b) (i)** For the circuit shown in the figure below, it is known that the voltage across the capacitor is  $v_c(t) = 20 \sin\left(2t + \frac{\pi}{6}\right) V$  for  $t \geq 0$ . Compute and plot the instantaneous power absorbed by the capacitor and energy stored by the capacitor over  $[0, t]$ :



(8 M)

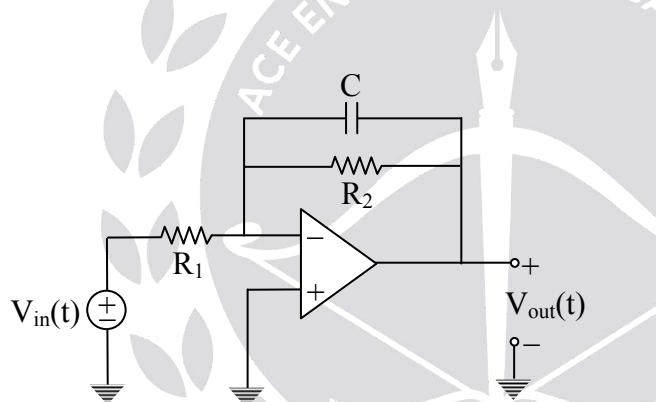**(ii)** The op-amp in the figure assumed to be ideal  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 40 \text{ k}\Omega$  and  $C = 10 \mu\text{F}$ :



- (1) Use nodal to construct a first-order differential equation describing the input-output relationship of the voltage.
- (2) Laplace transform your equation of (1) and solve  $V_{out}(s)$  in terms of  $V_{in}(s)$  and  $V_C(0^-)$ .
- (3) If  $V_{in}(t) = 2e^{-2t}u(t) \text{ V}$  and  $V_C(0) = 0$ , find  $V_{out}(t)$ .

(12 M)

**Sol:**

(i)  $v_c(t) = 20 \cdot \sin\left(2t + \frac{\pi}{6}\right) \text{ for } t \geq 0$

$c = 5 \text{ mF}$

$$i_c(t) = c \cdot \frac{dv_c(t)}{dt}$$

$$= 5 \times 10^{-3} \times \frac{d}{dt} \left( 20 \sin \left( 2t + \frac{\pi}{6} \right) \right)$$

$$= 10^{-1} \times \cos \left( 2t + \frac{\pi}{6} \right) \quad (2)$$

$$i_c(t) = 0.2 \cos \left( 2t + \frac{\pi}{6} \right)$$


$$\text{Instantaneous power } P_i(t) = v_c(t) \cdot i_c(t) = 20 \sin \left( 2t + \frac{\pi}{6} \right) \times 0.2 \cos \left( 2t + \frac{\pi}{6} \right)$$

$$= 4 \sin \left( 2t + \frac{\pi}{6} \right) \cdot \cos \left( 2t + \frac{\pi}{6} \right)$$


$$= 2 \left( 2 \sin \left( 2t + \frac{\pi}{6} \right) \cdot \cos \left( 2t + \frac{\pi}{6} \right) \right)$$

$$= 2 \left( \sin \left( 4t + \frac{\pi}{3} \right) \right)$$
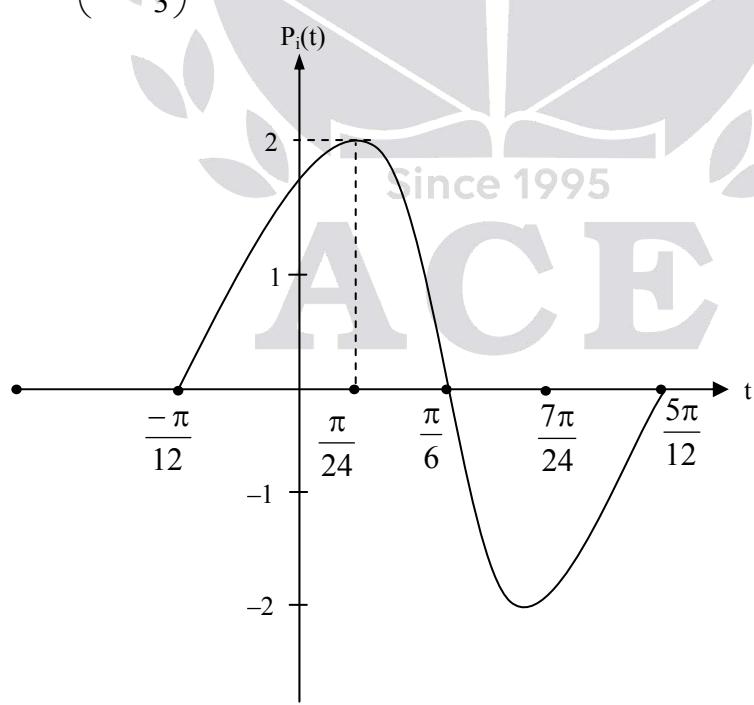
$$P_i(t) = 2 \sin \left( 4t + \frac{\pi}{3} \right)$$



$$\begin{aligned}
 E &= \frac{1}{2} CV^2(t) \\
 &= \frac{1}{2} \times 5 \times 10^{-3} \left\{ 20 \sin\left(2t + \frac{\pi}{6}\right) \right\}^2 \\
 &= \frac{5 \times 10^{-3}}{2} \times 20 \times 20 \times \sin^2\left(2t + \frac{\pi}{6}\right) \\
 &= 1 \sin^2\left(2t + \frac{\pi}{6}\right) \\
 &= \frac{1 - \cos\left(4t + \frac{\pi}{3}\right)}{2} \\
 &= 0.5 - 0.5 \cos\left(4t + \frac{\pi}{3}\right)
 \end{aligned}$$

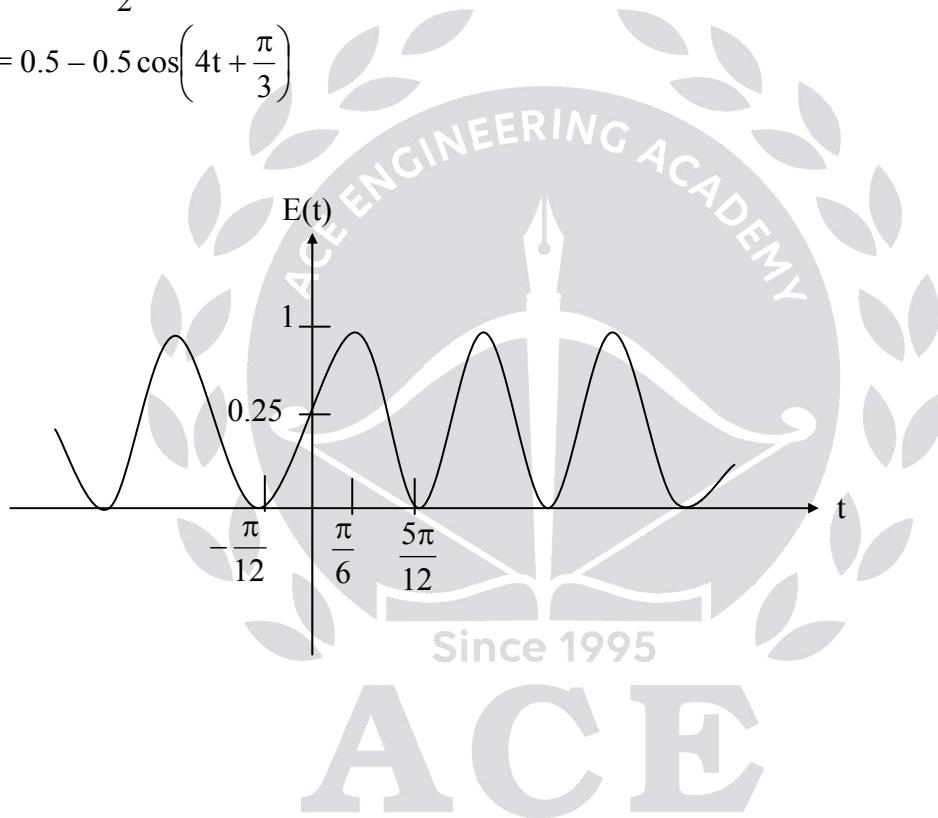

(ii) (1) Step (1): KCL at ( $V_2$ )

$$I_i + I_{f_1} + I_{f_2} = 0 \quad (1)$$

$$\Rightarrow \frac{V_i(t)}{R_1} + \frac{V_o(t)}{R_2} + \frac{CdV_o(t)}{dt} = 0 \quad (2) [\because V_1 = 0 \Rightarrow V_2 = 0]$$

$$\Rightarrow \frac{CdV_o(t)}{dt} + \frac{V_o(t)}{R_2} = -\frac{V_i(t)}{R_1}$$

$$\Rightarrow \frac{d}{dt}V_o(t) + \frac{1}{CR_2}V_o(t) = -\frac{1}{R_1C}V_i(t)$$

This is first order linear differential equation describing input-output relationship of the voltage.

#### NOTE:

The solution for the above first order linear differential equation

$$V_o(t) = -\frac{e^{-\frac{t}{CR_2}}}{CR_1} \int \frac{t}{e^{CR_2}} V_i(t) dt + K e^{-\frac{t}{CR_2}}$$

(2) From the circuit given

$$\frac{V_i(s)}{R_1} + \frac{V_o(s)}{R_2} + C s V_o(s) = 0$$

$$\Rightarrow V_o(s) \left[ sC + \frac{1}{R_2} \right] = -\frac{V_i(s)}{R_1}$$

$$\Rightarrow V_o(s) \left[ \frac{1+sCR_2}{R_2} \right] = -\frac{V_i(s)}{R_1}$$

$$\therefore V_o(s) = -\frac{R_2}{R_1} \frac{V_i(s)}{1+sCR_2}$$

(3) Consider the equation for output voltage obtained in (1) [equation (5)]

$$V_o(t) = -\frac{e^{-\frac{t}{R_2C}}}{R_1C} \int e^{\frac{t}{R_2C}} V_i(t) dt + K e^{-\frac{t}{R_2C}} \quad (9)$$

$$= -\frac{e^{-\frac{t}{R_2C}}}{R_1C} \int e^{\frac{t}{R_2C}} [2e^{-2t}] dt + K e^{-\frac{t}{R_2C}} \quad (10)$$

$$= -\frac{2e^{-\frac{t}{R_2C}}}{R_1C} \int e^{\left(\frac{1}{R_2C}-2\right)t} dt + Ke^{-t/R_2C} \quad (11)$$

$$= -\frac{2e^{-\frac{t}{R_2C}}}{R_1C} \left[ \frac{e^{\left(\frac{1}{R_2C}-2\right)t}}{\left(\frac{1}{R_2C}-2\right)} \right] + Ke^{-t/R_2C} \quad (12)$$

$$= -\frac{2e^{-\frac{t}{R_2C}}}{R_1C} \frac{e^{\left(\frac{1}{R_2C}-2\right)t}}{1-2R_2C} + Ke^{-t/R_2C} \quad (13)$$

$$\therefore V_0(t) = -\frac{2R_2}{R_1} \left[ \frac{e^{-2t}}{1-2R_2C} \right] + Ke^{-t/R_2C} \quad (14)$$


$$= -2 \left( \frac{40k}{20k} \right) \left[ \frac{e^{-2t}}{1-2 \times 40k \times 10\mu F} \right] + Ke^{-t/R_2C} \quad (15)$$

$$= -\frac{4e^{-2t}}{1-0.8} + ke^{-t/R_2C} \quad (16)$$

$$\therefore V_0(t) = -20e^{-2t} + ke^{-t/R_2C} \quad (17)$$

$$\Rightarrow V_0(t) = -10 V_i(t) \quad (18) \quad [\because V_i(t) = 2e^{-2t} \text{ and } V_C(0) = 0]$$

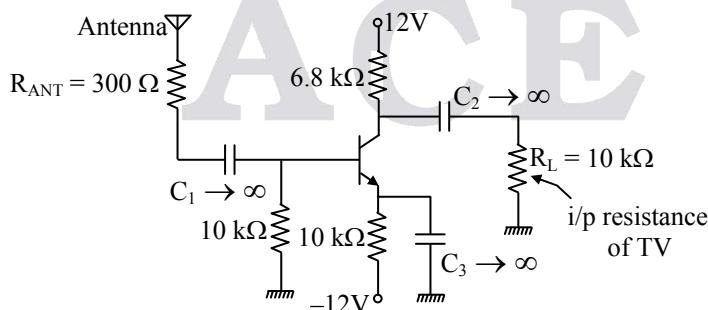**06. (c) A certain person with poor television reception and no access to cable TV intends to use the amplifier in the figure shown below as booster amplifier between his antenna and his television:**




The transistor has high frequency capacitances with  $C_{bc} = 4 \text{ pF}$ ,  $C_{be} = 2 \text{ pF}$ ,  $C_{ce} = 1 \text{ pF}$  and  $\beta \geq 100$ . Calculate low-pass dominant pole frequency and determine whether this amplifier performs adequately. (Assume  $V_T = 26 \text{ mV}$  at room temperature) (20 M)

**Sol:** Case (i):

DC model

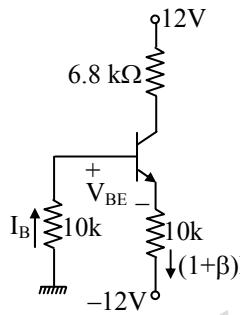1. All Ac sources = 0
2.  $X_C = \infty$  (All capacitors open)



KVL for input loop

$$0 - I_B 10k - V_{BE} - (1+\beta) I_B 10k + 12V = 0 \quad (1)$$

$$\Rightarrow I_B = \frac{12V - 0.7V}{10k + 101 \times 10k} = 0.011mA \quad (2)$$


$$\Rightarrow I_E = (1 + \beta) I_B = 1.11mA \quad (3)$$

$$\Rightarrow g_m = \frac{I_E}{V_T} = \frac{1.11mA}{26mV} = 0.0427 \text{ S} \quad (4)$$

$$\therefore h_{ie} = r_\pi = \frac{\beta}{g_m} = 2.34k\Omega \quad (5)$$


Case (ii): AC model

1. All DC sources = 0
2.  $X_C = 0$

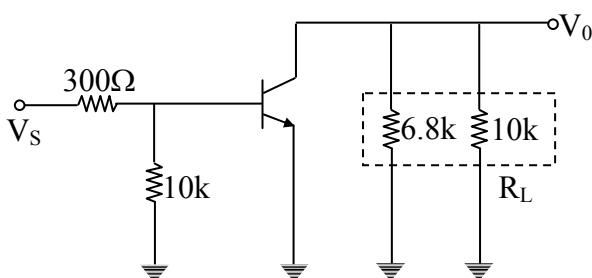


Step (1):  $R_L^1 = 6.8k \parallel 10k = 4.0476k$

Small-signal model at high frequencies:

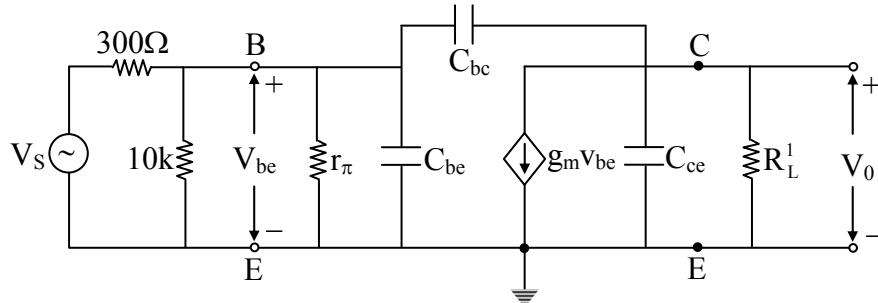

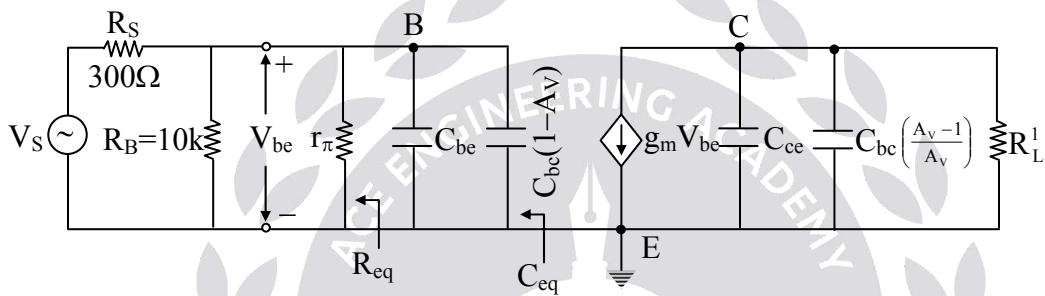Modified Small-Signal model using Millers theorem:



Step (2):  $C_{eq} = C_{be} + C_{bc} [1 + g_m R_L^1] \quad (2)$

$$= 2\text{pF} + 4\text{pF} [1 + 0.0427 \times 4.0476 \times 10^3 \Omega] \quad (3)$$

$$= 697.33\text{pF} \quad (4)$$

Step (3):  $R_{eq} = 300\Omega \parallel 10k \parallel r_\pi \quad (5)$

$$= 0.3k\Omega \parallel 10k \parallel 2.34k\Omega \quad (6)$$

$$= 259\Omega$$

Step (4): Low pass dominant pole frequency

$$f_H = \frac{1}{2\pi R_{eq} C_{eq}} \quad (8)$$

$$= \frac{1}{2\pi \times 259\Omega \times 697.33 \times 10^{-12} \text{F}} \quad (9)$$

$$f_H = 0.88166\text{MHz} \quad (10)$$


Step (5):  $|A_{V_M}| = \frac{R_B}{R_B + R_S} \left[ \frac{r_\pi}{r_\pi + R_B \parallel R_S} \right] (g_m R_L^1) \quad (11)$

$$= \left( \frac{10k}{10k + 0.3k} \right) \left( \frac{2.34k}{2.34k + 10k // 0.3k} \right) (0.0427\text{U} \times 4.0476 \times 10^3 \Omega) \quad (12)$$

$$= 149.154 \quad (13)$$

**Conclusion:** The amplifier used between antenna and TV can amplify the signals upto 0.88166 MHz by 149.154 times approximately. As the frequency of signals received through cable TV is in the range of 41MHz to 250MHz, the amplifier used will not perform adequately.

07. (a) In the circuit shown in the figure below,  $|V_1| = 200$  V,  $V_2 = 200 \angle 0^\circ$  V and  $|I| = 12$  A. The total power absorbed by the circuit is 1.8 kW. Find  $R_1$ ,  $X_1$  and  $X_2$ :

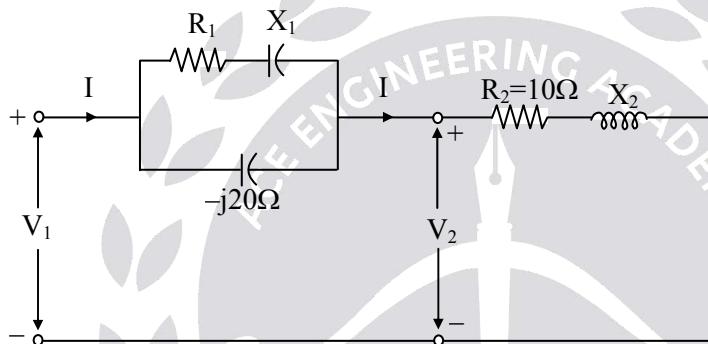

(20 M)

Sol:  $V_1 = 200$  V

$V_2 = 200$  V

Power absorbed by  $10 \Omega$  resistor  $= R \times |I|^2 = 10 \times (12)^2 = 1440$  W

$P = V_2 \times I \cos\phi_2$

$1440 = 200 \times 12 \times \cos\phi_2$

$\cos\phi_2 = 0.6 \Rightarrow \sin\phi_2 = 0.8$

$\phi_2 = 53.13^\circ$

Angle between  $I$  and  $V_2$  is  $53.13^\circ$ . Since  $V_2 = 200 \angle 0^\circ$ ,  $I = 12 \angle -53.13^\circ$

We know that  $X_2 = Z_2 \cdot \sin\phi_2$  -----(1)

$$R_2 = Z_2 \cdot \cos\phi_2$$

$$Z_2 = \frac{R_2}{\cos\phi_2} = \frac{10}{0.6} = 16.66\Omega$$

From (1)  $\Rightarrow X_2 = Z_2 \cdot \sin\phi_2 = 16.66 \times 0.8$

$$X_2 = 13.328\Omega$$

$$P_1 = V_1 \times I \times \cos\phi_1 \quad (\because P_1 = 1.8\text{kW})$$

$$\cos\phi_1 = \frac{1800}{200 \times 12}$$

$$\cos\phi_1 = 0.75$$

$$\phi_1 = 41.4^\circ \quad (\sin\phi_1 = \sin 41.4^\circ)$$

That is angle between current I and voltage  $V_1$  is  $41.4^\circ$

$$V_1 = 200\angle -11.73^\circ \text{ V} \quad (\because -53.13^\circ + 41.4^\circ = 11.73^\circ)$$

$$V_1 - V_2 = 200\angle -11.73^\circ - 200\angle 0^\circ$$

$$V_1 - V_2 = 40.87\angle -95.86^\circ$$

$$\text{Current through the capacitor } I_c = \frac{V_1 - V_2}{jX_c} = \frac{40.87\angle -95.86^\circ}{20\angle -90^\circ}$$

$$I_c = 2.0436\angle -5.86^\circ$$

$$\text{Now, current through } R_1 \text{ & } X_1 \text{ are } I_1 = I - I_c = 12\angle -53.13^\circ - 2.04\angle -5.86^\circ$$


$$I_1 = 10.718\angle 61.18^\circ$$

$$Z_1 = \frac{V_1 - V_2}{I_1} = \frac{40.87\angle -95.86^\circ}{10.718\angle -61.18^\circ}$$

$$Z_1 = 3.13 - j 2.119 \Rightarrow R_1 - j 1$$


$$R_1 = 3.13\Omega \quad X_1 = 2.169\Omega$$

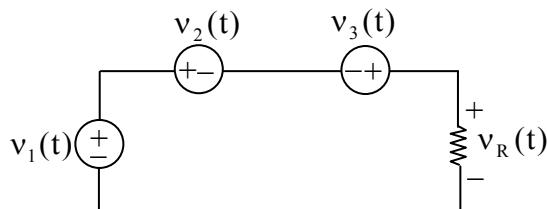- 07. (b) (i) Determine the voltage across the resistor in the circuit of the figure shown below using phasor concept for  $v_1(t) = 20 \cos(\omega t + 53.13^\circ)\text{V}$ ,  $v_2(t) = 19.68 \sin(\omega t + 152.8^\circ)\text{V}$  and  $v_3(t) = 4.215 \cos(\omega t + 71.61^\circ)\text{V}$ :**




(6 M)

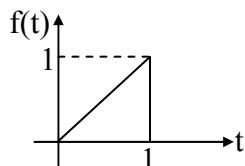(ii) Find the Laplace transform of the sawtooth sketched in the figure below:



(4 M)

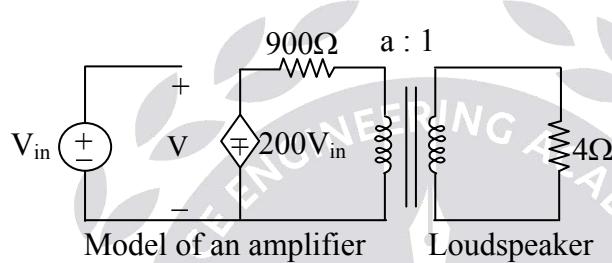(iii) The figure below shows a simplified model of an audio amplifier containing an ideal transformer. The input voltage is at 2kHz with a magnitude 1V r.m.s. The load is a loudspeaker, represented by  $4\Omega$  resistance:



- (1) Find the average power delivered to the  $4\Omega$  load if it is directly connected to the amplifier (i.e., with the transformer removed)
- (2) With the transformer connected and with turns ratio  $a = 5$ , find the average power delivered to the load.

(10 M)

Sol:

$$(i) \bar{V}_1 = 20 \angle 90^\circ + 53.13^\circ = 20 \angle 143.13^\circ \text{ V}$$

$$\bar{V}_2 = 19.68 \angle 152.8^\circ \text{ V}$$

$$\bar{V}_3 = 4.215 \angle 90^\circ + 71.61^\circ = 4.215 \angle 161.61^\circ \text{ V}$$

KVL


$$-\bar{V}_1 + \bar{V}_2 - \bar{V}_3 + \bar{V}_R = 0$$

$$\bar{V}_R = \bar{V}_1 - \bar{V}_2 + \bar{V}_3$$

$$\bar{V}_R = [20 \angle 143.13^\circ] - [19.68 \angle 152.8^\circ] + 4.215 \angle 161.6^\circ \text{ V}$$

$$\bar{V}_R = 5 \angle 119.93^\circ$$

(ii)

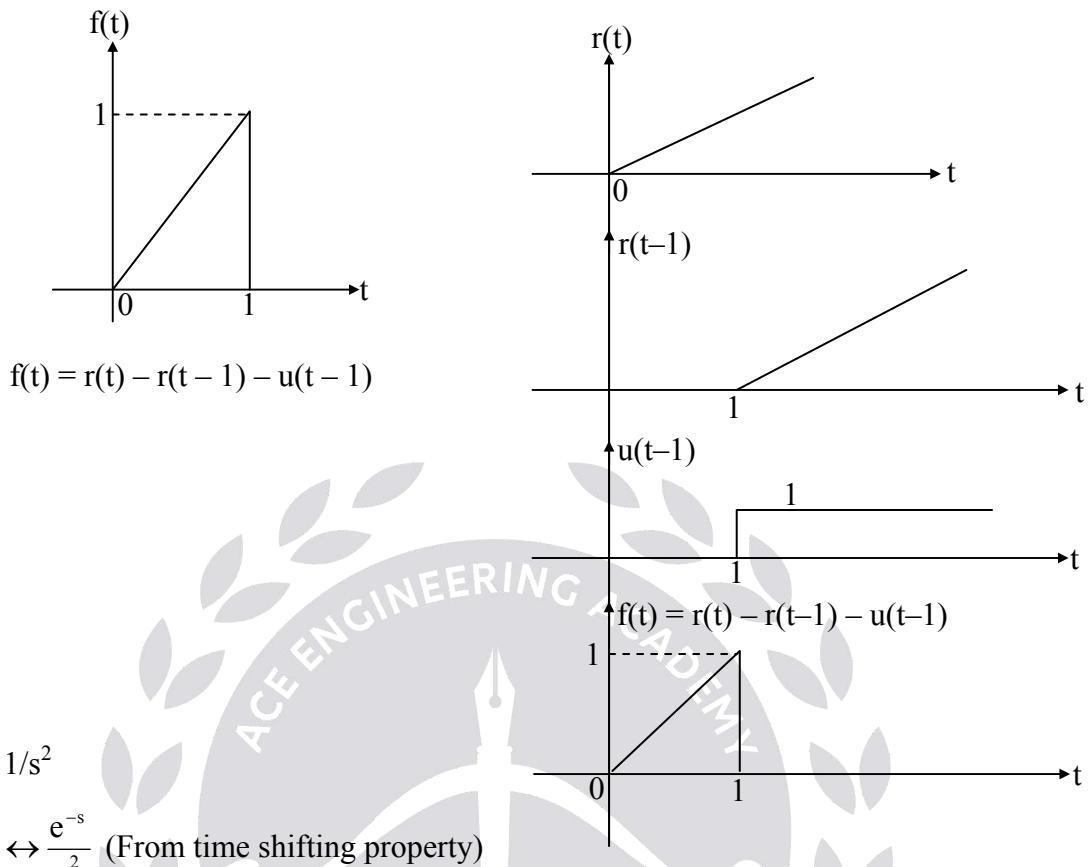

$$r(t) \leftrightarrow 1/s^2$$

$$r(t-1) \leftrightarrow \frac{e^{-s}}{s^2} \text{ (From time shifting property)}$$

$$u(t) \leftrightarrow \frac{1}{s}$$

$$u(t-1) \leftrightarrow \frac{e^{-s}}{s} \text{ (From time shifting property)}$$

$$F(s) = \frac{1}{s^2} - \frac{e^{-s}}{s^2} - \frac{e^{-s}}{s}$$

ACE

(OR)


$$f(t) = t[u(t) - u(t-1)] = tu(t) - tu(t-1)$$

$$= tu(t) - (t-1+1)u(t-1)$$


$$= tu(t) - (t-1)u(t-1) - u(t-1)$$

$$F(s) = \frac{1}{s^2} - \frac{e^{-s}}{s^2} - \frac{e^{-s}}{s}$$

(iii)

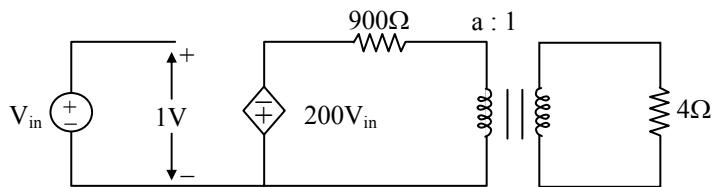

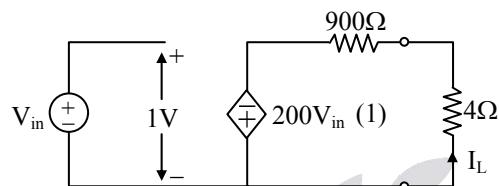
(1) The average power delivered to the  $4\Omega$  load if it is directly connected




$$I_L = \frac{200(1)}{900 + 4} = \frac{200}{904} = 0.2214$$

$$P_{avg} = I_L^2 (4) = 0.1957 = 195.8 \text{ mW}$$

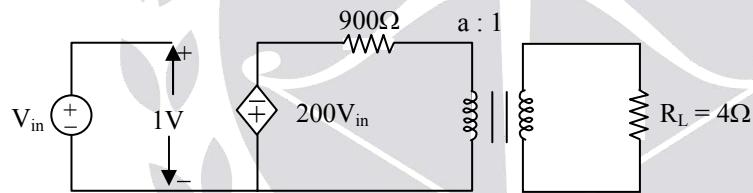(2) With the transformer Connected and with turns ratio  $a = 5$


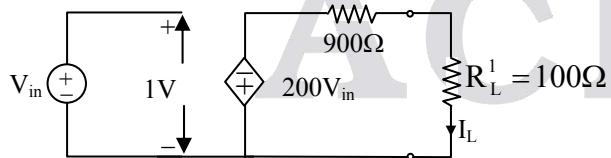
$$K = \frac{1}{a} = \frac{1}{5} \quad R_L^1 = \frac{R_L}{K^2} = \frac{4}{\left(\frac{1}{5}\right)^2} = 100\Omega$$



$$I_L = \frac{200(1)}{900 + 100} = \frac{1}{5} \text{ A}$$

$$P_{avg} = I_L^2 (100) = \left(\frac{1}{5}\right)^2 100 = 4 \text{ W}$$

07. (c) (i) Implement the logic function shown below with a static CMOS gate  
 $\text{Out} = \overline{\overline{ABC} + ABC + \overline{ABC}}$ .


(ii) A certain counting type 12-bit ADC operates with FSR = 0 to 10 V, clock frequency  $f_{\text{clk}} = 1\text{MHz}$ . Determine the dynamic range of converter, conversion time, conversion rate and Nyquist frequency of converter. (20 M)

Sol: (i)  $\text{Out} = \overline{\overline{ABC} + ABC + \overline{ABC}}$

$$= \overline{\overline{ABC} + ABC + ABC + \overline{ABC}}$$

$$= \overline{AB + BC}$$

$$\text{Out} = \overline{B(A + C)}$$

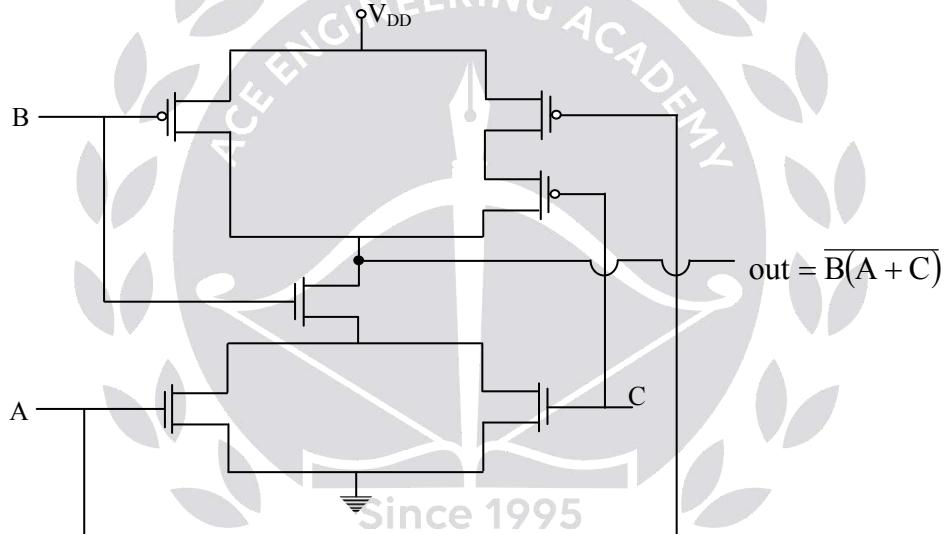

(ii) Given 12-bit counter Type ADC  $\Rightarrow N = 12$

$\text{FSR} = 0 \text{ to } 10\text{V}$

$$f_{\text{clock}} = 1\text{MHz} \Rightarrow \text{Clock period } T = \frac{1}{f_{\text{clock}}} = 1\mu\text{s}$$

$$(a) \text{Dynamic range} = 20 \log \left[ \frac{\text{max voltage}}{\text{min voltage other than 0}} \right]$$

$$\begin{aligned}
 &= 20 \log \left[ \frac{(2^N - 1) \times \text{stepsize}}{\text{stepsize}} \right] \\
 &= 20 \log 2^N \\
 &= 20 N \log 2 \\
 &= 20(N) 0.301 \\
 &= 6.02N = 6.02(12) \\
 &= 72.247 \text{ dB}
 \end{aligned}$$

(b) Max conversion time =  $(2^N - 1)T$

$$= (2^{12} - 1) 1\mu\text{s} = (2047) (1\mu\text{s}) \approx 2 \text{ ms}$$

(c) Sampling period  $T_s \geq$  max conversion time

$$T_s \geq 2 \times 10^{-3} \text{ Sec}$$

(d) Conversion rate  $f_s = \frac{1}{T_s} = \frac{1}{2 \times 10^{-3} \text{ s}} \Rightarrow f_s = 500 \text{ Hz}$

(e) As  $f_s = 500 \text{ Hz}$

$$\text{Nyquist frequency of the converter} = \frac{f_s}{2} = 250 \text{ Hz}$$

**08. (a)** A shunt generator delivers 50kW at 250V when running at 400 r.p.m. The armature and field resistance are  $0.02\Omega$  and  $50\Omega$  respectively. Calculate the speed of the machine when running as a shunt motor and taking 50kW, 250V. Given, total voltage drop in the brushes is 2V. (20 M)

**Sol:** Generating mode:-


$$\begin{aligned}
 P_{\text{out}} &= VI_L = 50 \text{ kW} \\
 &= (250)I_L = 50 \text{ kW}
 \end{aligned}$$

$$I_L = 200 \text{ A}$$

$$I_f = \frac{V}{r_f} = \frac{250}{50} = 5 \text{ A}$$

$$I_a = I_L + I_f = 200 \text{ A} + 5 \text{ A} = 205 \text{ A}$$
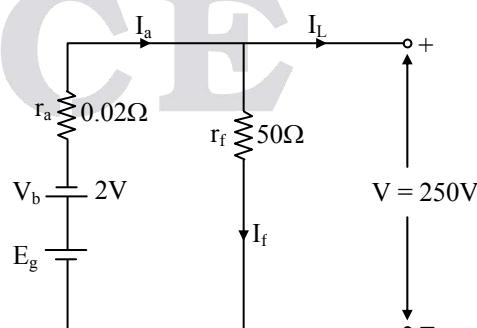
$$\begin{aligned}
 E_g &= V_b + V + I_a r_a \\
 &= 2 + 250 + (205)(0.02)
 \end{aligned}$$



$$E_g = 256.1 \text{ V}$$

$$N_1 = 400 \text{ rpm} = N_s$$

Motoring mode:-

$$I_f = 5 \text{ A}$$

$$P_{in} = 50 \text{ kW}$$

$$V \cdot I_L = 50 \text{ kW}$$

$$(250)I_L = 50 \text{ kW}$$

$$I_L = 200 \text{ A}$$

$$I_a = I_L - I_f = 195 \text{ A}$$

$$I_a = 195 \text{ A}$$

$$E_b = V - I_a r_a - V_b$$



$$= 250 - (195)(0.02) - 2$$

$$E_b = 244.1 \text{ V}$$


$$\frac{E_g}{E_b} = \frac{N_s}{N_m}$$

$$\frac{256.1}{244.1} = \frac{400}{N_m}$$

$$N_m = 381.26 \text{ rpm}$$

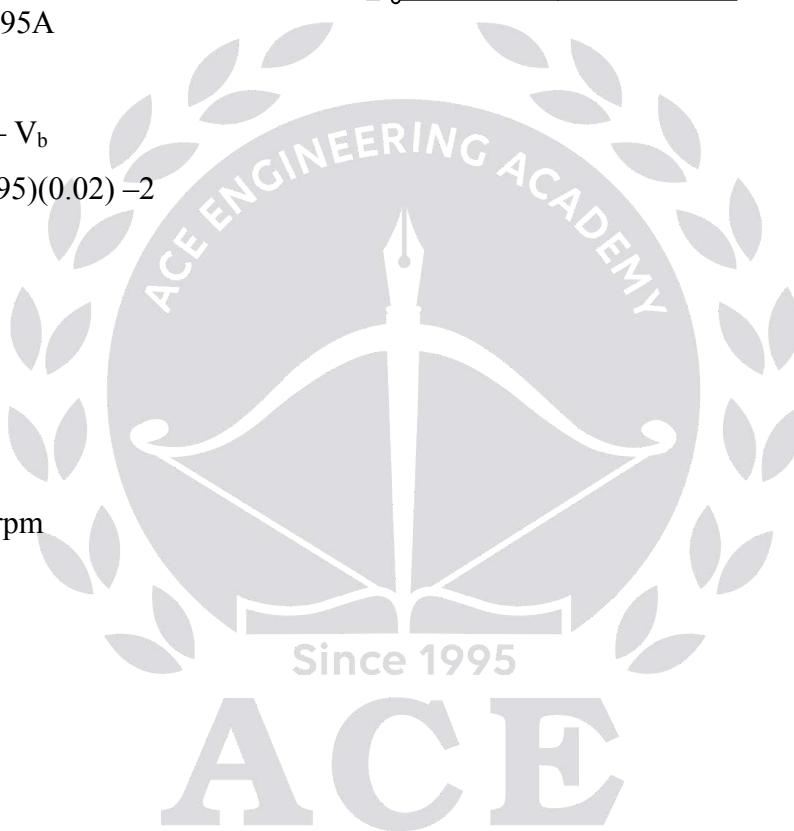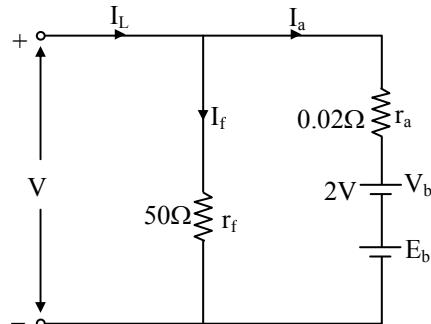

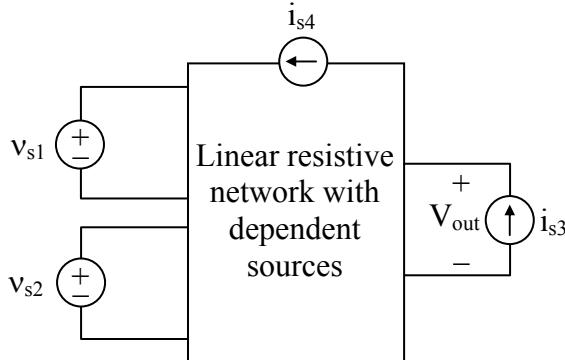08. (b) (i) The linear resistive circuit shown in the figure below has four independent sources. Three of them have fixed value, only one,  $i_{s3}$  is adjustable:




The table shows the four sets of measurements taken in a laboratory:

$i_{s3}$ (mA)	$V_{out}$ (V)
1	6
2	10
5	?
?	0

Complete the last two rows of the table. For the data in row 3, find the power delivered by the current source  $i_{s3}$ . (12 M)

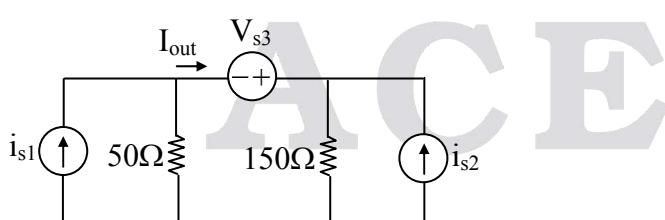(ii) Consider the three-source circuit of the figure below:



Compute  $I_{out}$  using superposition theorem. (8 M)

Sol:

$$(i) \quad V_{out} = k_1 V_{s1} + k_2 V_{s2} + k_3 i_{s4} + k_4 i_{s3}$$

$\underbrace{\qquad\qquad}_{\rightarrow \text{Constant} \rightarrow k_o}$

$$V_{out} = k_0 + k_4 i_{s3}$$

$$10 = k_0 + k_4 (2m)$$

$$6 = k_0 + k_4 (1m)$$

---


$$4 = k_4 (1m)$$

$$\Rightarrow k_4 = 4000$$

$$\text{So, } 6 = K_0 + 4 \rightarrow k_0 = 2$$

$$\text{So, } V_{out} = 2 + (4000)i_{s3}$$

Now from table

$$\text{if } i_{s3} = 5\text{mA, } V_{out} = 2 + (4k)(5m)$$

$$V_{out} = 22 \text{ volts}$$


$$\text{If } V_{out} = 0, 0 = 2 + 4k(i_{s3})$$

$$i_{s3} = -0.5\text{mA}$$

Now for data in Row - 3,  $i_{s3} = 5\text{mA}$  &  $V_{out} = 22 \text{ V}$

Power delivered is,  $(V_{out})(i_{s3}) = 110\text{mW}$

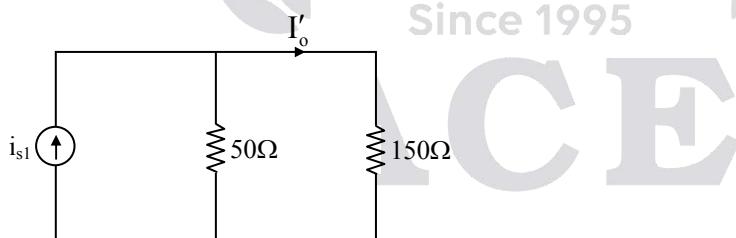- (ii)** Consider source ' $i_{s1}$ ' ( $V_{s3}$  = short circuited,  $i_{s2}$  = open circuited)




$$\therefore I'_o = \frac{i_{s1} \times 50}{50 + 150}$$

$$\Rightarrow I'_o = \frac{50i_{s1}}{200}$$

$$\Rightarrow I'_o = 0.25i_{s1}$$

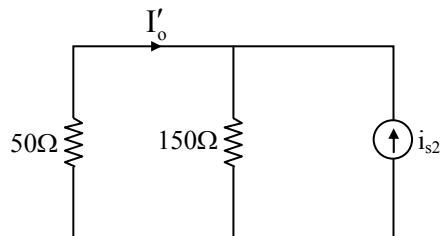
Consider source ' $i_{s2}$ ' ( $V_{s3} = S.C.$ ,  $i_{s1} = 0.C.$ )



$$\therefore I''_o = \frac{-i_{s2} \times 150}{50 + 150}$$

$$\Rightarrow I''_o = -0.75i_{s2}$$

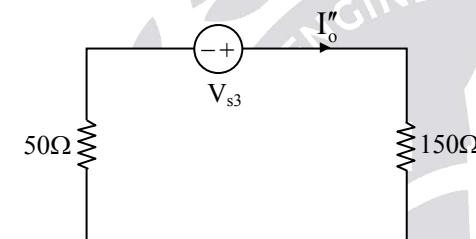Consider source  $V_{s3}$  ( $i_{s1} = 0.C.$ ,  $i_{s2} = 0.C.$ )



$$\therefore I'''_o = \frac{V_{s3}}{200}$$


$$\Rightarrow I'''_o = 0.005V_{s3}$$

$\therefore$  using superposition theorem

$$I_{out} = I'_o + I''_o + I'''_o$$

$$\Rightarrow I_{out} = 0.25i_{s1} - 0.75i_{s2} + 0.005V_{s3}$$

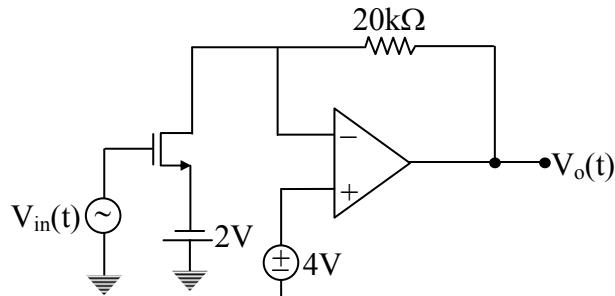08. (c) (i) For the circuit shown in the figure below, determine the output voltage if the input  $V_{in}(t) = 100 \sin(2\pi \times 10^3 t)$  mV. Assume that the op-amp is an ideal op-amp and MOSFET parameters are  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$ ,  $V_{tn} = 1\text{V}$ ,  $W = 10\mu\text{m}$  and  $L = 2.5\mu\text{m}$ :




(15 M)

(ii) Draw a block diagram of a 4 to 2 encoder. Label all inputs and outputs. How is the 4 to 2 encoder different from 4 to 1 multiplexer? (5 M)

Sol:

(i)

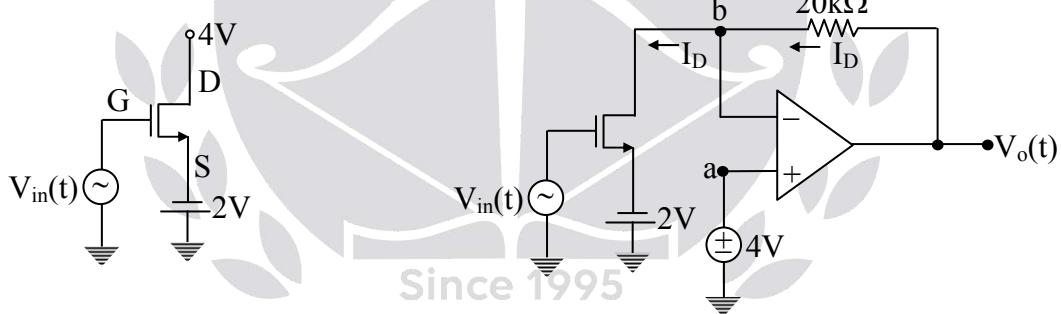Since  $V_d = 0$ 

$$V_a = V_b = 4\text{V}$$

$$V_D = 4\text{V}, V_s = -2\text{V}, V_G = V_{in}(t)$$

$$V_{DS} = 6\text{V}, V_{DS(\text{sat})} = V_{GS} - V_{tn} = V_{in}(t) + 2 - 1 = V_{in}(t) + 1 \quad (\text{range} \Rightarrow 1.1\text{V to } 0.9\text{V})$$

$$\text{As } V_{DS} > V_{DS(\text{sat})} \rightarrow \text{MOSFET in saturation region then } I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) [V_{GS} - V_{tn}]^2$$

$$= \frac{1}{2} (100 \times 10^{-6}) \left( \frac{10}{2.5} \right) [V_{in}(t) + 1]^2$$

$$I_D = 200 \times 10^{-6} [V_{in}(t) + 1]^2$$

Then from op-amp circuit

$$V_0(t) - V_b = 20 \times 10^3 I_D$$

$$V_0(t) = V_b + 20 \times 10^3 \times 200 \times 10^{-6} (V_{in}(t)+1)^2$$

$$= 4 + 4 (V_{in}(t)+1)^2$$

$$= 4 + 4 [0.1\sin\omega t + 1]^2$$

$$= 4 + 4 [0.01\sin^2\omega t + 0.2\sin\omega t + 1]$$

$$V_0(t) = 8 + 0.8 \sin(2\pi 10^3 t) + 0.04 \sin^2(2\pi \times 10^3 t)$$

## (ii) 4 to 2 Encoder

Encoder produces a binary code for the selected input, the relation between n and m is  $2^m = n$

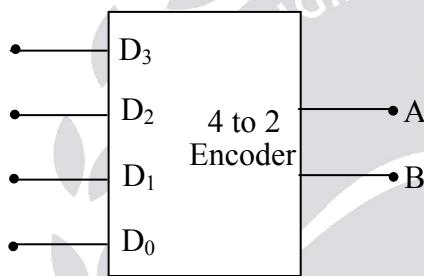



Table: Encoder Function:

D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A	B
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

The limitation of encoder is the coding process is incorrect if more than one input is selected. To overcome this, we use priority encoder, where inputs are given with priorities.


\* A multiplexer is a many to one circuit. It selects one of the inputs based on the selection line value. For a N:1 MUX, the number of selection lines are ' $\log_2 N$ '.

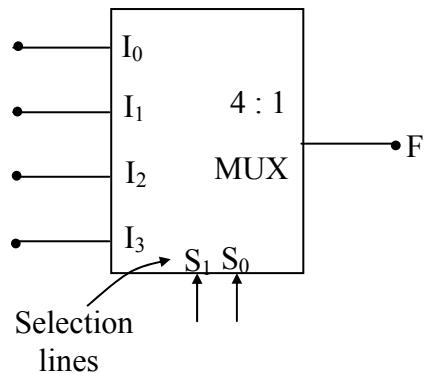Consider a 4:1 MUX. It has 4 inputs, 2 selection lines and one output.



$S_1 \quad S_0$	F
0 0	$I_0$
0 1	$I_1$
1 0	$I_2$
1 1	$I_3$
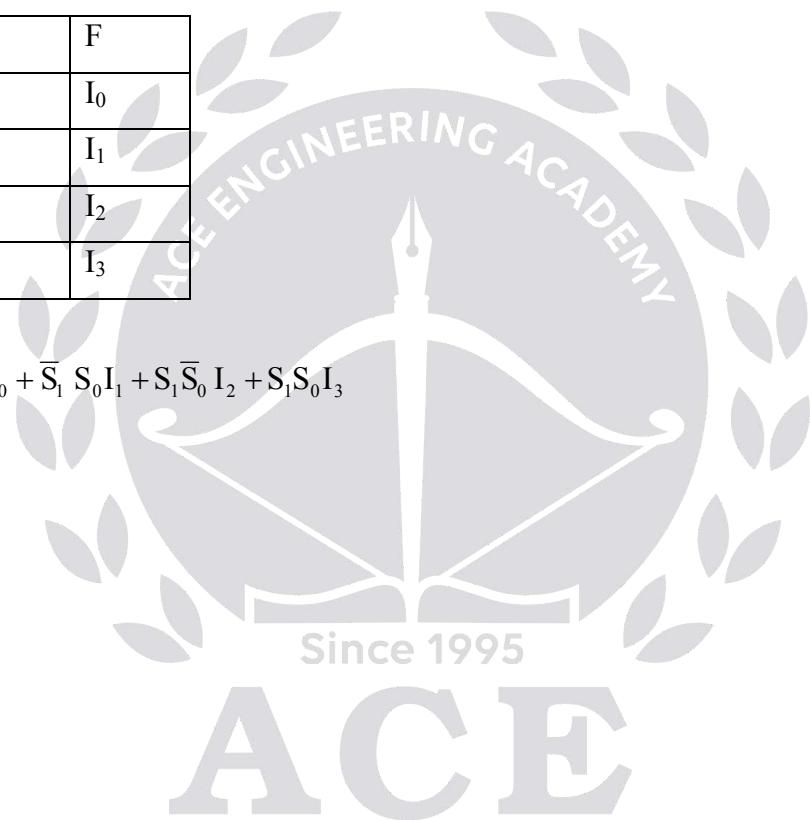
$$F = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$





## Hearty Congratulations to our **GATE-2019 Toppers**



and many more...

## Hearty Congratulations to our **ESE-2018 Toppers**



& MANY MORE...

**48** AIR 1<sup>st</sup> in **GATE**

**11** AIR 1<sup>st</sup> in **ESE**

Subscribe to our **Youtube Channel**

[www.youtube.com/aceacademyhyd](https://www.youtube.com/aceacademyhyd)

for Latest Videos on

Preparation Strategy & Tips

for **ESE | GATE | PSUs**



By Prof. Y.V. Gopala Krishna Murthy

® [www.aceenggacademy.com](http://www.aceenggacademy.com)  
Contact: **040-23234418,19,20 - 24750437**