



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad – 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Branch: Electrical Engineering

Mock-B - Solutions

GATE-2020 General Aptitude (GA)

01. Ans: (D)

Sol: (PART AND THE WHOLE) A fragment is a piece of broken bone; a shard is a piece of broken pottery. (D)

02. Ans: (A)

03. Ans: (D)

Sol: irretrievably means impossible to recover or get back, so irrevocably is the correct synonym, which means not capable of being changed : impossible to revoke.

04. Ans: (B)

Sol: Indiscriminate (adj.) means not discriminating or choosing randomly; haphazard; without distinction.

05. Ans: (A)

Sol: $a_0 = 1$; $a_n = 2a_{n-1}$ if n is odd

$a_n = a_{n-1}$ if n is even

$a_{100} = a_{100-1} = a_{99} = 2.a_{99-1} = 2.a_{99} = 2.a_{98-1}$

$= 2a_{97}$

$= 2.2a_{97-1} = 2^2.a_{96} \dots\dots\dots 2_{50}.a_0 = 2^{50}$

06. Ans: (C)

Sol: $A = 1$; $B = 1$

(a) $B = B + 1 = 2$

(b) & (c) $A = A \times B = 1 \times 2 = 2$

Step 2: $B = 2 + 1 = 3$; $A = A \times B = 2 \times 3 = 6$

Step 3: $B = 3 + 1 = 4$; $A = A \times B = 6 \times 4 = 24$

Step 4: $B = 4 + 1 = 5$; $A = 24 \times 5 = 120$

Step 5: $B = 5 + 1 = 6$; $A = 120 \times 6 = 720$

07. Ans: (A)

Sol: Ratio of efficiency (P & Q) = 2 : 1

Ratio of efficiency (P + Q, R) = 3 : 1

If R does 1 unit work, then P & Q together do 3 units.

Out of 3 units, P does 2 units and Q does 1 unit.

\therefore Ratio of efficiency (P, Q & R) = 2 : 1 : 1

Hence, earnings should be divided in the ratio is 2 : 1 : 1

08. Ans: (C)

Sol: In 1972, A was as old as the number formed by the last two digits of his year of birth.

So, A was born in 1936 (as in 1972, he is 36 yrs older also, last two digits of 1936 are 36).

Hence, B was born in $1936 + 15 = 1951$ so, he is 21 yrs old in 1972

09. Ans: (B)

Sol: Difference (in thousands) between the numbers of customers in the 2 complexes in:

January: $22 - 20 = 2$

February: $25 - 24 = 1$

March: $20 - 15 = 5$

April: $28 - 25 = 3$

May: $20 - 14 = 6$ [Max]

June: $20 - 15 = 5$

10. Ans: (B)

Sol: The issue is more about punishing criminals, and so punishment is more important than crime prevention (correct answer B).

Specialization (EE)

01. Ans: 24

Sol: Given that $F(x) = f(g(x))$

$$\Rightarrow F^1(x) = f^1(g(x)) \cdot g^1(x) \quad (\because \text{by chain rule})$$

$$\Rightarrow F^1(5) = f^1(g(5)) \cdot g^1(5)$$

$$\Rightarrow F^1(5) = f^1(-2) \cdot 6$$

$$\therefore F^1(5) = (4) (6) = 24$$

02. Ans: 16.5 to 16.7


Sol: $\frac{V_0}{V_{dc}} = \frac{1}{1-D} \Rightarrow \frac{15}{5} = \frac{1}{1-D}$, hence $D = \frac{2}{3}$

$$\Delta V_0 = 0.01 \times 15 = 0.15 \text{ V}$$

As $\Delta I_L = 2 \text{ A}$ given, the capacitor current waveform is redrawn as shown below:

$$\Delta V_0 = \frac{\Delta Q}{C} \Rightarrow 0.15 = \frac{2.5 \times 10^{-6}}{C}$$
, hence $C =$

$$16.67 \mu\text{F}$$

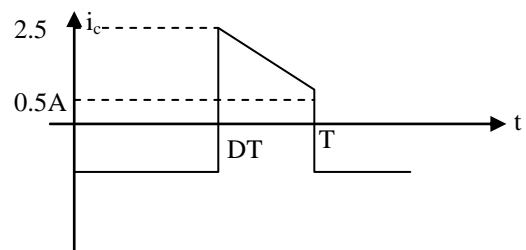

03. Ans: (D)

Sol: We know that,

$$P(A \cap B) \leq \min \{P(A), P(B)\}$$

$$\Rightarrow P(A \cap B) \leq 0.25 \dots\dots\dots (1)$$

we have, $P(A \cup B) \leq P(S)$

$$\Rightarrow \{P(A) + P(B) - P(A \cap B)\} \leq 1$$

$$\Rightarrow \{0.25 + 0.8 - P(A \cap B)\} \leq 1$$

$$\Rightarrow 0.05 \leq P(A \cap B) \dots\dots\dots (2)$$

From (1) and (2), we have

$$0.05 \leq P(A \cap B) \leq 0.25$$

04. Ans: (A)

Sol: $|\text{adj}A| = |A|^{n-1}$

$$\Rightarrow -11(4-6) + 3(4-6) = |A|^2$$

$$\Rightarrow 22 - 6 = |A|^2$$

$$\therefore |A| = \pm 4$$

05. Ans: (B)

Sol: Mod-n ring counter is designed by using 'n' flipflops

Mod-2n Johnson counter is designed by using 'n' flipflops.

So, mod-8 ring counter requires 8 flipflops and mod-8 Johnson counter requires 4 flipflops.

06. Ans: 1

Sol: If rank of A is 2, then $|A| = 0$

$$\Rightarrow (x-1)(x^2+x+1) = 0$$

$$\Rightarrow x = 1, \frac{-1 \pm \sqrt{3}i}{2}$$

$$\therefore x = 1$$

07. Ans: (c)

Sol: The slip at 415 V is,

$$s = \frac{N_s - N_r}{N_s} = \frac{1000 - 950}{1000} = 0.05$$

When the voltage rise to 440 V, the load torque and rotor resistance remains the same, consequently

We have, $s_{\text{new}} = s_{\text{old}} \left(\frac{E_{2(\text{old})}}{E_{2(\text{new})}} \right)^2$

$$E_{2(\text{new})} = \frac{440}{\sqrt{3}} \text{ and } E_{2(\text{old})} = \frac{415}{\sqrt{3}}$$

$$s_{\text{new}} = 0.05 \left(\frac{415/\sqrt{3}}{440/\sqrt{3}} \right)^2 = 0.0444$$

$$\begin{aligned} N_r &= N_s (1 - s_{\text{new}}) \\ &= 1000 (1 - 0.0444) \\ &= 955.5 \end{aligned}$$

08. Ans (d)

Sol: Energy consumed in 100 seconds, by a load of 450W

$$= \frac{P \times \text{hours}}{1000} = \frac{450 \times 100}{1,000 \times 3600} = \frac{1}{80} \text{ kWh}$$

Meter constant in revolutions/kWh

$$= \frac{\text{Revolutions made by disc}}{\text{Energy consumed}} = \frac{10}{1/80} = 800$$

09. Ans (d)

Sol: We know for dual slope DVM

$$\frac{V_i \times t_{\text{ON}}}{RC} = \frac{V_{\text{ref}} \times t_{\text{ref}}}{RC}$$

$$\Rightarrow t_{\text{ref}} = \frac{V_i \times t_{\text{ON}}}{V_{\text{ref}}} = \frac{8}{10} = 0.8 \text{ sec}$$

10. Ans: 388.488 (Range 387 to 390)

Sol: $i(t) = 4 + 3 \cos(10t - 30^\circ) + 4 \sin(10t + 30^\circ)$
 $= 4 + 3 \cos(10t - 30^\circ) + 4 \cos(10t + 30^\circ - 90^\circ)$
 $= 4 + 3 \cos(10t - 30^\circ) + 4 \cos(10t - 60^\circ)$
 $= 4 + 3 \angle -30^\circ + 4 \angle -60^\circ$

$$= 4 + 3 \cos 30^\circ - j3 \sin 30^\circ + 4 \cos 60^\circ - j4 \sin 60^\circ$$

$$= 4 + \left[\frac{4 + 3\sqrt{3}}{2} - j \frac{3 + 4\sqrt{3}}{2} \right]$$

$$= 4 + 6.766 \angle -47.24^\circ$$

$$= 4 + 6.76 \angle -47.24$$

$$i(t) = 4 + 6.76 \cos(10t - 47.24)$$

$$I_{\text{rms}} = \sqrt{4^2 + \left(\frac{6.76}{\sqrt{2}} \right)^2} = \sqrt{38.84}$$

$$\begin{aligned} \text{Power dissipated in } 10\Omega \text{ is } P &= I_{\text{rms}}^2 \times R \\ &= (\sqrt{38.84})^2 \times 10 \\ &= 38.84 \times 10 \\ P &= 388.4 \text{ watts} \end{aligned}$$

11. Ans : (B)

Sol: Given: $\rho_s = \frac{1}{9\pi} \text{ nC/m}^2$ located at $z = 5\text{m}$

Field point (1,1,-1)

z-coordinate of field point ($z = -1$) is less than z-coordinate of source point ($z = 5$), hence

$$\vec{E} = \frac{\rho_s}{2\epsilon_0} (-\hat{a}_z) = \frac{1}{2 \times \frac{10^{-9}}{36\pi}} \times 10^{-9} (-\hat{a}_z)$$

$$\therefore \vec{E} = -2\hat{a}_z \text{ V/m}$$

12. Ans: 397.5 range(396 to 398)

Sol: G_1 : Full load voltage drop = $400 \times \frac{3}{100} = 12 \text{ V}$

G_2 : Full load voltage drop = $400 \times \frac{6}{100} = 24 \text{ V}$

$$G_1: I_{f1} = \frac{250 \times 10^3}{400} = 625 \text{ A}$$

$$G_2: I_{f2} = \frac{150 \times 10^3}{400} = 375 \text{ A}$$

Voltage of G_1 at load current I_1

$$V_1 = 410 - \left(\frac{12}{625} \right) I_1$$

$$V_2 = 420 - \left(\frac{24}{375} \right) I_2$$

Load on generation in parallel $I_L = I_1 + I_2 = 1000 \text{ A}$

Bus voltage = V

$$V_1 = V_2 = V$$

$$410 - \left(\frac{12}{625} \right) I_1 = 420 - \left(\frac{24}{375} \right) I_2$$

$$0.064 I_2 - 0.0192 I_1 = 10$$


$$I_1 + I_2 = 1000$$

$$I_1 = 649 \text{ A}, I_2 = 351 \text{ A}$$

$$\begin{aligned} \text{Bus voltage } V &= 410 - \left(\frac{12}{625} \right) \times 649 \\ &= 397.5 \text{ V} \end{aligned}$$

13. Ans: (A)

Sol:

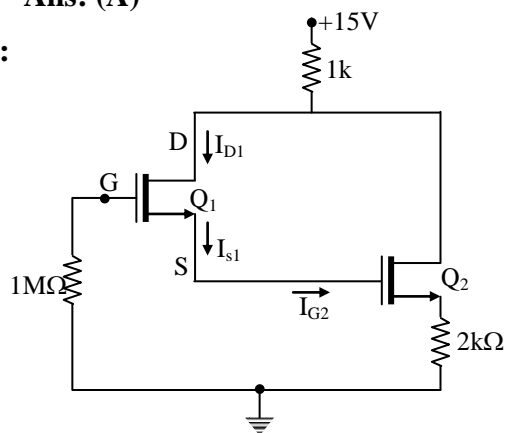


Step(1): From the circuit,

$$I_{S1} = I_{G2} = 0 \quad \text{---(1)} \quad [\because I_G = 0 \text{ in MOSFETs}]$$

$$\Rightarrow I_{D1} = I_{S1} = 0 \quad \text{---(2)} \quad [\because I_D = I_S \text{ in MOSFETs}]$$

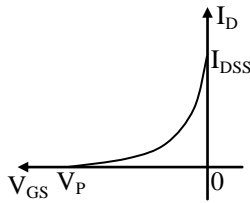Step(2): Consider the transfer characteristics of a DMOSFET



Case (i): $I_D = I_{DSS}$ at $V_{GS} = 0$ ___(3)


Case (ii): $I_D = 0$ at $V_{GS} = V_P$ ___(4)

$$\Rightarrow V_{GSQ1} = V_P = -4V \quad \text{---(5)}$$

$\therefore I_{D1} = 0$ in the ckt given

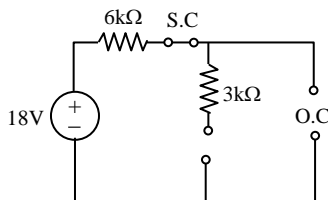14. Ans: - 60 V/sec (No Range)

Sol: At time $t = 0^-$ switch is in open condition



So, L is short circuit, C is open circuit

$$i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 18V$$

At $t = 0^+$ switch is closed


$$I_C(0^+) = C \frac{dv(0^+)}{dt}$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C}$$

$$i_C(0^+) = -6 \times 10^{-3} A$$

$$\frac{dv(0^+)}{dt} = \frac{-6 \times 10^{-3}}{100 \times 10^{-6}}$$

$$\frac{dv(0^+)}{dt} = -60V/sec$$

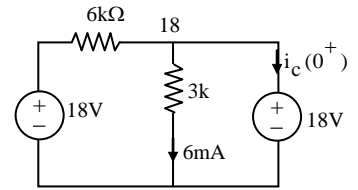

15. Ans: (B)

Sol: In 180° mode, $(I_{sw})_{rms} = \left[\frac{V_{dc} \sqrt{2}}{3R} \right]$

$$70 = \frac{V_{dc} \sqrt{2}}{3R}$$

$$\frac{V_{dc}}{R} = \left(\frac{210}{\sqrt{2}} \right)$$

In 120° mode, $(I_{sw})_{rms} = \left[\frac{V_{dc}}{\sqrt{6R}} \right]$

$$\Rightarrow \frac{210}{\sqrt{12}} = 60.62A$$

16. Ans: (D)

Sol:

$$i/p = 5\sin\omega t \quad \longrightarrow \quad \boxed{\phantom{\text{Block}}} \quad \longrightarrow \quad o/p = 10\cos\omega t = 5A \sin(\omega t + \phi)$$

$$10\cos\omega t = 5A \sin(\omega t + \phi)$$

$$A = 2, \phi = 90^\circ$$

If input = $10\cos\omega t$

$$\begin{aligned} \text{Output} &= (10) (2) \cos(\omega t + 90^\circ) \\ &= -20\sin\omega t \end{aligned}$$

17. Ans: (D)

Sol: $(1+t) \frac{dy}{dt} = 4y$

$$\int \frac{1}{y} dy = \int \frac{4}{1+t} dt$$

Log y = 4 log (1+t) + log c

$y = c(1+t)^4$

$y(0) = 1 \Rightarrow 1 = c(1+0)^4 \Rightarrow c = 1$

$\Rightarrow y = (1+t)^4$

18. Ans: 224 (No range)

Sol: Number of P specified = 124

Number of Q specified = 100

\therefore Total number of equation

= size of Jacobian matrix

= 124 + 100

= 224

19. Ans: (D)

Sol: $\frac{E}{R} = \frac{1}{1 - \left[\frac{4}{s+1} - \frac{4}{s+1} \right]} = \frac{s+1}{s+9}$

20. Ans: (c)

Sol: Given $y(n) - \frac{1}{4} y(n-1) = x(n)$

Apply z transform

$$Y(z) - \frac{1}{4} z^{-1} Y(z) = X(z)$$

$$Y(z) = \frac{X(z)}{1 - \frac{1}{4} z^{-1}}$$

$x(n) = \delta(n-1)$

$X(z) = z^{-1}$

$$Y(z) = \frac{z^{-1}}{1 - \frac{1}{4} z^{-1}}$$

Apply inverse z transform

$$\left(\frac{1}{4}\right)^n u(n) \leftrightarrow \frac{1}{1 - \frac{1}{4} z^{-1}}$$


From time shifting property

$$\left(\frac{1}{4}\right)^{n-1} u(n-1) \leftrightarrow \frac{z^{-1}}{1 - \frac{1}{4} z^{-1}}$$

So, $y(n) = \left(\frac{1}{4}\right)^{n-1} u(n-1)$

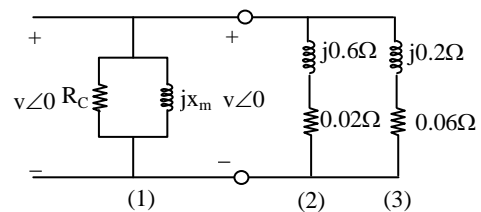21. Ans: 24.8 (Range: 24 to 25)

Sol: Equivalent-circuit (per ph) of the double-cage motor is as shown.



(1): Magnetizing current & core losses branch.

(2): low resistance, high reactance, inner cage.

(3): High resistance, low reactance, outer cage.

At starting, torque due to inner cage

$$= \frac{3V^2(0.02)}{\omega_s [0.02^2 + 0.6^2]}$$

Torque due to outer cage

$$= \frac{3V^2(0.06)}{\omega_s [0.06^2 + 0.2^2]}$$

$$\frac{\text{Torque due to outer cage}}{\text{Torque due to inner cage}} = \frac{0.06(0.02^2 + 0.6^2)}{(0.06^2 + 0.2^2)(0.02)}$$

$$= 3 \times \frac{0.3604}{0.0436}$$

$$= 24.8$$

22. Ans: (c)

Sol: $H_1(z) = \frac{z^2 + 1.5z - 1}{z^2}$ and

$$H_2(z) = z^2 + 1.5z - 1$$

∴ The zeros of the functions will be identical but not the poles

23. Ans: (D)


Sol: During positive cycle D_3 is FB, D_4 is RB.

Hence C_1 gets charged to V_m

During Negative cycle D_1 is FB, D_2 is RB.

Hence C_2 gets charged to $-V_m$

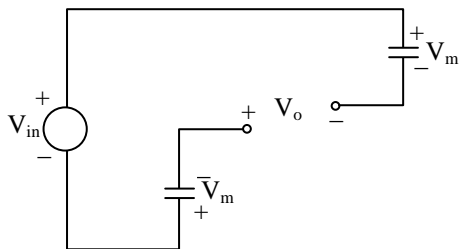After the capacitors are charged, the diodes will remain reverse biased




$$\text{KVL: } -V_{in} + V_m - V_o - V_m = 0$$

$$V_o = -V_{in}$$

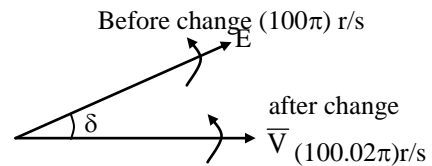24. Ans: 3.6 (No range)

Sol: In figure \bar{V} is the bus voltage and \bar{E} is the induced emf in the machine.



Bus frequency is always fixed at $f = 50\text{Hz}$.

so \bar{V} rotates in the anticlockwise direction at $\frac{2\pi N}{60} = 100\pi$ r/sec. Before the change in

the prime mover input, \bar{E} also rotates in the anticlockwise direction at 100π r/sec. So \bar{E} and \bar{V} are stationary with respect to each other, and the torque angle (or) load angle or power angle δ remains constant.

Now, after the change, \bar{V} continues at $100\pi\omega$ r/sec (anticlockwise) but \bar{E} rotates at 100.02π r/s anticlockwise. So relative speed $= 0.02\pi$ r/s $= 0.02 \times 180 = 3.6^\circ$ elec.

25. Ans: 55 (range 54.90 to 55)

Sol: Compensator $D(s) = \frac{0.4s + 1}{0.04s + 1} = \frac{1 + aTs}{1 + Ts}$

$$aT = 0.4$$

$$T = 0.04$$


$$\therefore a = 10$$

Maximum phase angle,


$$\phi_m = \sin^{-1} \left(\frac{a-1}{a+1} \right) = 55^\circ$$

26. Ans: (B)

Sol:

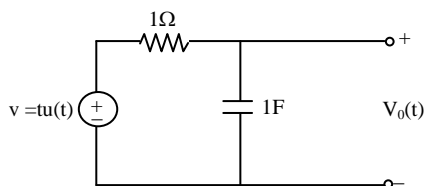

Converting into Laplace domain we get

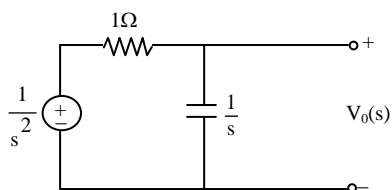

$$V_o(s) = \frac{\frac{1}{s} \times \frac{1}{s^2}}{1 + \frac{1}{s}} = \frac{1}{s^3 \left(\frac{s+1}{s} \right)} = \frac{1}{s^2(s+1)}$$

$$V_o(s) = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{s+1}$$

$$B = \frac{1}{s+1} \Big|_{s=0} = 1$$

$$A = \frac{dB}{ds} \Big|_{s=0} = \frac{(s+1) \times 0 - 1}{(s+1)^2} \Big|_{s=0} = -1$$

$$C = \frac{1}{s^2} \Big|_{s=-1} = 1$$

$$V_o(s) = \frac{-1}{s} + \frac{1}{s^2} + \frac{1}{s+1}$$

Apply inverse Laplace transform on both sides

$$V_o(t) = -u(t) + tu(t) + e^{-t} u(t)$$

$$V_o(t) = ((t-1) + e^{-t})u(t), t > 0$$

27. Ans: (B)

Sol: • (SP) = 8086H

• (DE) = 8085H

• (HL) exchanged with (DE)

After execution

(HL) = 8085H, (DE) = ~~xxxx~~H

(HL) = 8085H = 1000 0000 1000 0101

(SP) = 8086H = 1000 0000 1000 0110

(HL) = 010BH = 0000 0001 0000 1011

• (HL) = 010BH copied into (SP)

⇒ (SP) = 010BH

• 8085 microprocessor calls delay subroutine and after execution of subroutine, microprocessor returns to main program.

SP contents decremented by 2 for CALL operation

SP contents incremented by 2 for RETURN operation

i.e., (SP) = 010BH - 2 + 2

= 010BH

• 8085 microprocessor pushes DE pair contents to stack. SP contents will be decremented by 2 for PUSH operation.

(SP) = 010BH - 2 = 0109H

• 8085 microprocessor executes RST 7 software interrupt where it calls

respective ISR and returns to main execution.

$$(SP) = 0109H - 2 + 2 = 0109H$$

- 8085 microprocessor contents of top 2 stack locations back into PSW. SP contents will be incremented by 2 for POP operation.

$$(SP) = 0109H + 2 = 010BH$$

$$(SP) = 010BH$$

28. Ans: (D)

Sol: Given curve 'C' is a closed curve.

So, we have to evaluate the integral by using Green's theorem.

By Green's theorem, we have

$$\oint_C (M dx + N dy) = \iint_R \left(\frac{\partial N}{\partial x} - \frac{\partial M}{\partial y} \right) dx dy$$

$$\text{Now, } \oint_C [(x - y)dx + (x + 3y) dy]$$

$$= \iint_R \left[\frac{\partial}{\partial x} [x + 3y] - \frac{\partial}{\partial y} (x - y) \right] dx dy$$

$$= \iint_R [1 - (-1)] dx dy$$

$$= 2 \iint_R 1 dx dy = 2(\text{Area of the circle 'C'})$$

$$= 2(\pi r^2)_{r=4} = 32 \pi$$

29. Ans: 18

Sol: As \vec{G} is irrotational and hence $\nabla \times \vec{G} = 0$

$$\text{i.e. } \begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ (ax + bz^3) & (3x^2 - cz) & (3xz^2 - y) \end{vmatrix} = 0 \cdot \hat{a}_x + 0 \cdot \hat{a}_y + 0 \cdot \hat{a}_z$$

$$\text{So, } -1 + c = 0 \Rightarrow c = 1$$

$$3z^2 - 3bz^2 = 0 \Rightarrow b = 1$$

$$6x - ax = 0 \Rightarrow a = 6$$

$$\therefore a = 6, b = 1, c = 1$$

$$\nabla \cdot \vec{G} = \frac{\partial G_x}{\partial x} + \frac{\partial G_y}{\partial y} + \frac{\partial G_z}{\partial z}$$

$$= ay + 6xz$$

$$\nabla \cdot \vec{G} \Big|_{(1,1,2)} = 6 \times 1 + 6(1)(2)$$

$$\therefore \nabla \cdot \vec{G} = 18$$

30. Ans: (B)

Sol: At no load power supplied

$$P_{in0} = VI_{L0} = 400 \times 2 = 800 \text{ W}$$

$$\text{Shunt field current } I_{sh} = \frac{V}{R_{sh}} = \frac{400}{800} = 0.5 \text{ A}$$

$$\text{Armature current } I_{a0} = I_{L0} - I_{sh}$$

$$= 2 - 0.5 = 1.5 \text{ A}$$

No load armature Cu loss

$$= I_{a0}^2 R_a + I_{a0} \times \text{brush drop}$$

$$= (1.5)^2 \times 0.6 + 1.5 \times 2 = 4.35 \text{ W}$$

Constant losses

$$P_c = P_{in0} - \text{no load armature copper loss}$$

$$= 800 - 4.35 = 795.65 \text{ W}$$

At full load

$$\text{Output power } P_{out} = 18000 \text{ W}$$

Let the armature current on full load be 'I_a' amp

$$P_{in} = V \times (I_a + I_{sh}) = 400(I_a + 0.5)$$

$$P_{in} = P_{out} + \text{armature Cu loss} + \text{constant loss}$$

$$400 (I_a + 0.5) = 18,000 + I_a^2 (0.6) + 795.65 + 2I_a$$

$$400 I_a + 200 = 18,000 + I_a^2 (0.6) + 795.65 + 2I_a$$

$$0.6I_a^2 - 398I_a + 18595.65 = 0$$


$$I_a = 612.75 \text{ A impractical}$$

$$I_a = 50.579 \text{ A}$$


$$\begin{aligned} \text{Motor } \eta &= \frac{\text{motor output}}{\text{motor int put}} \times 100 \\ &= \frac{18000}{20431.6} \times 100 = 88.09 \end{aligned}$$

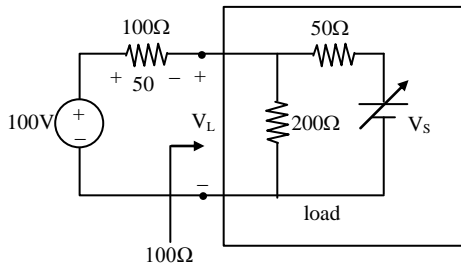31. Ans: 37.5 (Range 37 to 38)

Sol: Applying thevenin's theorem in the source side, the circuit can be redrawn as



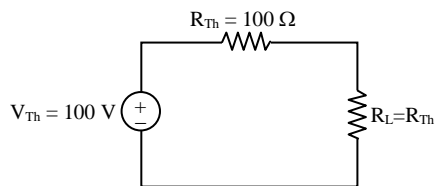We know that for maximum power transform, the load resistance is equal to thevenin's resistance.



$$\text{Voltage drop across load, } V_L = \frac{V_{Th} \times R_{Th}}{R_{Th} + R_L}$$

$$\Rightarrow V_L = \frac{V_{Th} \times R_{Th}}{2R_{Th}}$$

$$V_L = \frac{V_{Th}}{2}$$

Consider above figure, for maximum power transferred to load

$$V_L = \frac{V_{TH}}{2} = \frac{100}{2} = 50 \text{ Volts}$$

Applying nodal analysis, we get

$$\Rightarrow \frac{50}{100} = \frac{50}{200} + \frac{50 - V_s}{50}$$


$$\Rightarrow \frac{50 - V_s}{50} = \frac{1}{4}$$

$$\Rightarrow 50 - V_s = 12.5$$

$$\Rightarrow V_s = 37.5 \text{ V}$$

32. Ans: (C)

Sol:

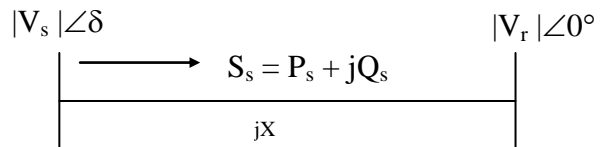

At sending end side, complex power (S_s)

$$S_s = V_s \cdot I_s^*$$

$$= |V_s| \angle \delta \left[\frac{|V_s| \angle \delta - |V_r| \angle 0^\circ}{X \angle 90^\circ} \right]^*$$

$$P_s + jQ_s = \frac{|V_s|^2}{X} \angle 90^\circ - \frac{|V_s||V_r|}{X} \angle 90^\circ + \delta$$

Sending end reactive power

$$Q_s = \frac{|V_s|^2}{X} \sin 90^\circ - \frac{|V_s||V_r|}{X} \sin (90^\circ + \delta)$$

$$Q_s = \frac{|V_s|^2}{X} - \frac{|V_s||V_r|}{X} \cos \delta$$

During maximum power transfer $\delta = 90^\circ$

$$\therefore Q_s = \frac{|V_s|^2}{X}$$

$$Q_s = \frac{|V_r|^2}{X} \quad (\because |V_s| = |V_r|)$$

At receiving end side, complex power (S_r)

$$S_r = V_r \cdot I_r^* \\ = |V_r| \angle 0^\circ \left[\frac{|V_s| \angle \delta - |V_r| \angle 0^\circ}{|X| \angle 90^\circ} \right]^*$$

$$P_r + j Q_r = \frac{|V_r||V_s|}{|X|} \angle 90^\circ - \delta - \frac{|V_r|^2}{X} \angle 90^\circ$$

Receiving end reactive power

$$Q_r = \frac{|V_r||V_s|}{|X|} \cos \delta - \frac{|V_r|^2}{X} \sin 90^\circ$$

During maximum power transfer $\delta = 90^\circ$

$$Q_r = -\frac{V_r^2}{X} \text{ i.e., load must be able to deliver}$$

the reactive power.

So, During maximum power transfer condition, sink of the reactive power is only transmission line.

Total reactive power absorbed by the transmission line is

$$Q_{\text{line}} = Q_s - Q_r \\ = \left(\frac{V_r^2}{X} \right) - \left(-\frac{V_r^2}{X} \right) \\ Q_{\text{line}} = \frac{2V_r^2}{X} \quad (\because |V_r| = |V_s| = V) \\ Q_{\text{line}} = \frac{2V^2}{X}$$

33. Ans: (B)

Sol: $f(t) = \left(-\frac{t}{T} + 1 \right) [u(t) - u(t - T)]$

$$f(t) = \left(-\frac{t}{T} \right) [u(t) - u(t - T)] + [u(t) - u(t - T)]$$

$$[u(t) - u(t - T)] \leftrightarrow \frac{1}{s} - \frac{e^{-sT}}{s}$$

From differentiation in s-domain property


$$\left(-\frac{t}{T} \right) [u(t) - u(t - T)] \leftrightarrow \frac{1}{T} \frac{d}{ds} \left(\frac{1}{s} - \frac{e^{-sT}}{s} \right) \\ = \frac{1}{T} \left[\frac{-1}{s^2} - \frac{(se^{-sT}(-T) - e^{-sT})}{s^2} \right]$$

$$\left(-\frac{t}{T} \right) [u(t) - u(t - T)] \leftrightarrow \frac{1}{T} \left[\frac{-1}{s^2} + T \frac{e^{-sT}}{s} + \frac{e^{-sT}}{s^2} \right] \\ = \frac{e^{-sT}}{s} + \frac{e^{-sT}}{Ts^2} - \frac{1}{s^2T}$$

$$F(s) = \frac{1}{s} - \frac{e^{-sT}}{s} + \frac{e^{-sT}}{s} + \frac{e^{-sT}}{Ts^2} - \frac{1}{s^2T} \\ = \frac{1}{s} + \frac{e^{-sT}}{Ts^2} - \frac{1}{s^2T} = \frac{1}{s^2T} [sT - 1 + e^{-sT}]$$

34. Ans: 4.92 (4.5 to 5.5)

Sol:

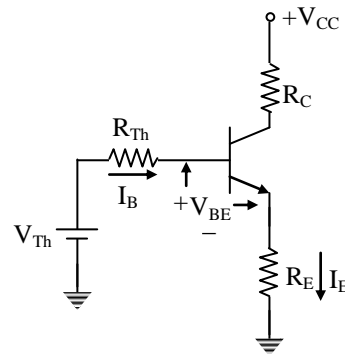

fig(a): Thevenin equivalent of the given circuit

Step(1):

KVL for the input loop of circuit shown in fig(a)

$$V_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0 \text{ ----- (1)}$$

$$I_E = \frac{V_{Th} - V_{BE}}{R_E + \frac{R_{Th}}{1 + \beta}} \text{ ---- (2) } [\because I_B = \frac{I_E}{1 + \beta}]$$

$$V_{Th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_{Th} = R_1 // R_2$$

Step (2):

$$\text{But } I_E R_E = \frac{V_{CC}}{3} = \left[\frac{V_{Th} - V_{BE}}{R_E + \frac{R_{Th}}{1 + \beta}} \right] R_E \text{ ----- (3)}$$

$$(\because \text{ Given that voltage drop across } R_E = \frac{V_{CC}}{3})$$

$$\left\{ \frac{(V_{Th} - V_{BE})}{R_E \left[1 + \left(\frac{R_{Th}}{R_E} \right) \left(\frac{1}{1 + \beta} \right) \right]} \right\} R_E = \frac{V_{CC}}{3} \text{ ----- (4)}$$

$$V_{Th} = \frac{V_{CC}}{3} \left[1 + \left(5.73 \times \frac{1}{101} \right) \right] + V_{BE} \text{ ----- (5)}$$

$$V_{Th} = 4.92693V \text{ ----- (6)}$$

35. Ans: 0.0045 (Range: 0.004 TO 0.005)

Sol: Let X = number of accidents between 5 P.M and 6 P.M.

For Poisson distribution,

$$\lambda = np = (1000)(0.0001) = 0.1$$

$$P(X=x) = \frac{e^{-\lambda} \lambda^x}{x!} \quad (x = 0, 1, 2, \dots)$$

Required Probability = $P(X \geq 2)$

$$= 1 - P(X < 2)$$


$$= 1 - \{P(X=0) + P(X=1)\}$$

$$= 1 - e^{-0.1} (1 + 0.1)$$

$$= 0.0045$$

36. Ans: (B)

Sol: Reactance of a pressure coil = 0.2% of its resistance
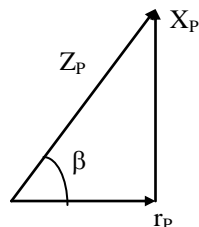
$$\tan \beta = \frac{X_p}{r_p} = \frac{0.002 r_p}{r_p}$$


$$\beta = \tan^{-1}(0.002)$$

$$= 0.1145 \text{ rad}$$

$$\cos \phi = 0.707$$

$$\phi = \cos^{-1}(0.707) = 45^\circ$$

$$\text{Correction factor} = \frac{\cos \phi}{\cos \beta \cos(\phi - \beta)}$$

$$= \frac{0.707}{\cos(6.56) \cos(45^\circ - 6.56)}$$

$$= 0.9085$$

\therefore Correction factor = 0.9085

37. Ans: 33.66 (33.40 to 33.80)

Sol: Fig.1. Shows the circuit of the transmission line, transformer equivalent circuit referred.

hv and load referred hv. Numerical values are calculated using given data.

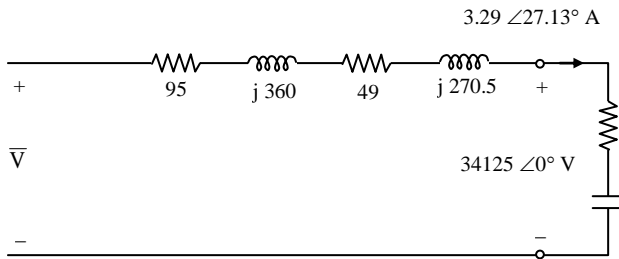


Fig.1

$$\text{Transformation ratio } k = \left(\frac{35000}{2400} \right) = 14.58$$

Equivalent impedance of transformer referred hv = $(0.23 + j1.27)k^2 = 49 + j270.5$

Load 100 kW at 0.89 leading & 2340 V

Load voltage referred to hv

$$= 2340 \times \frac{35000}{2400} = 34,125 \text{ V}$$

$$P = VI \cos\phi$$

$$34125 \times I \times 0.89 = 100 \times 10^3$$

$$I = \frac{100 \times 10^3}{34125 \times 0.89} = 3.29 \text{ A}$$

Phase angle, $\cos^{-1} 0.89 = 27.13$

$$\bar{V} = 34125 + 3.29 \angle 27.13^\circ [144 + j630.5]$$

$$\bar{V} = 34125 + [2.92 + j1.5] [144 + j630.5]$$

$$= 34125 - 524.28 + j2062.15$$

$$= 33600 + j2062$$

Magnitude = 33663 = 33.66 kV

38. Ans: (B)

Sol: For break point,

$$\frac{dk}{ds} = 0$$

$$\frac{d}{ds} \left(\frac{1}{G(s)H(s)} \right) = 0$$

$$\frac{d}{ds} (s(s+6)(s^2+4s+13)) = 0$$

$$(s^2+6s)[2s+4] + (s^2+4s+13)[2s+6] = 0$$

$$2s^3 + 16s^2 + 24s + 2s^3 + 6s^2 + 8s^2 + 24s + 26s + 78 = 0$$

$$4s^3 + 30s^2 + 74s + 78 = 0$$

$$f(s) = 2s^3 + 15s^2 + 37s + 39 = 0 \text{ -----(1)}$$

$$f(-5) = -21$$

$$f(-4) = 3$$

$$f(-3) = 9$$

As there is a sign change in between -5, -4, one root is on real axis, which is in between -5, -4. Three real axis break points is not possible

39. Ans: (C)

Sol: $I_a = 1000 \angle 0^\circ \text{ A}, I_b = I_c = 0$

Zero sequence component

$$I_{a0} = I_{b0} = I_{c0} = \frac{1}{3} [I_a + I_b + I_c]$$

$$= \frac{1}{3} [1000 \angle 0^\circ]$$

$$= 333.3 \angle 0^\circ$$

$$I_{a1} = \frac{1}{3} [I_a + aI_b + a^2I_c] = 333.3 \angle 0^\circ \text{ A}$$

$$I_{b1} = a^2 I_{a1} = 333.3 \angle 240^\circ \text{ A}$$

$$I_{c1} = a I_{a1} = 333.3 \angle 120^\circ \text{ A}$$

$$I_{a2} = \frac{1}{3} [I_a + a^2I_b + aI_c] = 333.3 \angle 0^\circ \text{ A}$$


$$I_{b_2} = a I_{a_2} = 333.3 \angle 120^\circ$$

$$I_{c_2} = a^2 I_{a_2} = 333.3 \angle 240^\circ$$

Hence option 'c' is correct.


40. Ans: (B)

Sol:

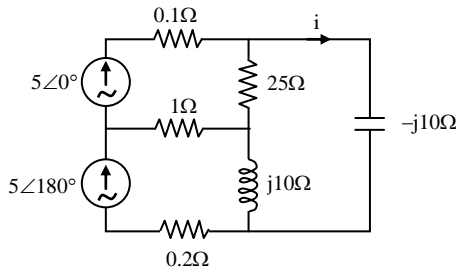


By super position principle $i = i_1 + i_{11}$

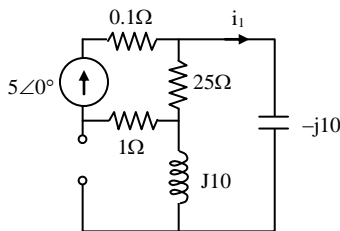
Current i_1 : $5 \angle 0^\circ$ source acting alone



$-j10 + j10 = 0 \Omega$ (short circuit)

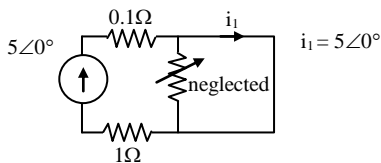

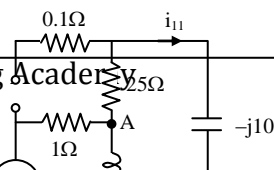Current i_{11} : $5 \angle 180^\circ$ source acting alone



By current division rule at node A

$$i_{11} = 5 \angle 180^\circ \times \frac{j10}{25 + j10 - j10}$$

$$= 2j \angle 180^\circ$$

$$= -2j$$

$$\therefore i = i_1 + i_{11} = 5 - 2j \text{ A}$$

41. Ans: 16 (Range: 15.9 to 16.2)

Sol: $G(s) H(s) = \frac{10}{(s+2)^4}$

$$\angle G(j\omega) H(j\omega) = \angle \frac{10}{(j\omega+2)^4}$$

Gain margin (GM) = 20 log

$$\frac{1}{|G(j\omega)H(j\omega)|_{\omega=\omega_{pc}}}$$

$$\angle G(j\omega)H(j\omega)_{\omega=\omega_{pc}} = -180^\circ$$

$$\angle \frac{10}{(j\omega+2)^4} \Big|_{\omega=\omega_{pc}} = -180^\circ$$

$$-4 \tan^{-1} \frac{\omega_{pc}}{2} = -180^\circ$$

$$\Rightarrow \omega_{pc} = 2$$

$$|G(j\omega)H(j\omega)|_{\omega=\omega_{pc}} = \left| \frac{10}{(j(2)+2)^4} \right|$$

$$= \frac{10}{(\sqrt{2^2+2^2})^4} = \frac{10}{64}$$

$$\begin{aligned} \text{Gain margin} &= 20 \log \frac{64}{10} \\ &= 20[\log 64 - \log 10] \\ &= 20 [6 (0.3) - 1] \\ &= 16 \text{ (Range: 15.9 to 16.2)} \end{aligned}$$

42. Ans: (C)

Sol: By giving different sets of input values and Q(t) (present state) we have to determine next state Q(t+1)

X	Y	Q(t)	S	R	Q(t+1)
0	0	0	1	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	1	1	×
1	1	1	1	1	×

K-map for Q (t + 1)

		YQ(t)			
		00	01	11	10
X	0	1	1		
	1		1	×	×

$$\begin{aligned} \therefore Q(t+1) &= \bar{X}\bar{Y} + \bar{Y}Q(t) \quad \text{or} \\ Q(t+1) &= \bar{X}\bar{Y} + XQ(t) \end{aligned}$$

43. Ans: 0.2

Sol: Given that $\frac{dy}{dx} = x^3 - 2y$ ($\because \frac{dy}{dx} = f(x, y)$)

with $y(0) = 0.25$ ($\because y(x_0) = y_0$)

Let $x_0 = 0, y_0 = 0.25$ & $h = 0.1$

Then $x_1 = x_0 + h = 0.1$

The formula for Euler's forward method is

$$y(x_1) \approx y_1 = y_0 + h f(x_0, y_0)$$

$$\Rightarrow y(0.1) \approx y_1 = 0.25 + (0.1) (x_0^3 - 2y_0)$$

$$\Rightarrow y(0.1) \approx y_1 = 0.25 + (0.1) [0 - 2(0.25)]$$

$$\therefore y(0.1) \approx y_1 = 0.25 - (0.1) (0.5) = 0.25 - 0.05 = 0.2$$

44. Ans: 0 (No range)

Sol: $\delta(t^2 - a^2) = \frac{1}{2|a|} [\delta(t+a) + \delta(t-a)]$

$$I = \int_{-1}^1 \frac{1}{4} [\delta(t-2) + \delta(t+2)] dt$$

$$I = \frac{1}{4} \int_{-1}^1 \delta(t-2) dt + \frac{1}{4} \int_{-1}^1 \delta(t+2) dt$$

From sifting property

$$\int_{t_1}^{t_2} x(t) \delta(t - t_0) dt = x(t_0) \quad t_1 \leq t_0 \leq t_2$$

$$= 0 \text{ otherwise}$$

$$I = 0 + 0 = 0$$

45. Ans: 86.8°

Sol: The given output voltage waveform is having quarter wave symmetry,

$$\therefore a_n = 0$$

$$\text{And } b_n = \frac{1}{\pi} \int_0^{2\pi} f(t) \sin(n\omega t) d\omega t$$

$$= \frac{2}{\pi} \int_0^{\pi} f(t) \sin(n\omega t) d\omega t$$

For fundamental $n = 1$

$$\therefore b_1 = \frac{2V_{dc}}{\pi} \left[\int_0^{\alpha} \sin \omega t d\omega t - \int_{\alpha}^{\pi-\alpha} \sin \omega t d\omega t + \int_{\pi-\alpha}^{\pi} \sin \omega t d\omega t \right]$$

$$= \frac{2V_{dc}}{\pi} \left[-\cos \omega t \Big|_0^{\alpha} + \cos \omega t \Big|_{\alpha}^{\pi-\alpha} - \cos \omega t \Big|_{\pi-\alpha}^{\pi} \right]$$

$$= \frac{2V_{dc}}{\pi} [2 - 4 \cos \alpha]$$

RMS value of fundamental output voltage can be

$$\Rightarrow \frac{2V_{dc}}{\pi\sqrt{2}} [2 - 4 \cos \alpha] = 120 \text{ V}$$

$$\Rightarrow \cos \alpha = 0.056 \Rightarrow \alpha = 86.8^\circ$$

46. Ans: (D)

Sol: $X(\omega) = \frac{1}{(2 + j\omega)^2}$

$$H(\omega) = \frac{1}{4 + j\omega}$$

$$Y(\omega) = X(\omega) \cdot H(\omega) = \frac{1}{(4 + j\omega)(2 + j\omega)^2}$$


$$= \frac{1/4}{4 + j\omega} - \frac{1/4}{2 + j\omega} + \frac{1/2}{(2 + j\omega)^2}$$

$$y(t) = \frac{1}{4} e^{-4t} u(t) - \frac{1}{4} e^{-2t} u(t) + \frac{1}{2} t e^{-2t} u(t)$$

$$y(3) = \frac{1}{4} e^{-12} - \frac{1}{4} e^{-6} + \frac{3}{2} e^{-6} = \frac{1}{4} e^{-12} + \frac{5}{4} e^{-6}$$

47. Ans: 2.19 (2.18 to 2.20)

Sol: Apply KCL at V_a

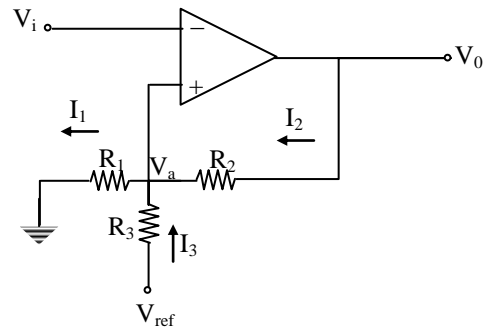

$$I_1 = I_2 + I_3$$

$$\frac{V_a}{R_1} = \frac{V_{ref} - V_a}{R_3} + \frac{V_0 - V_a}{R_2}$$

$$V_a \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_{ref}}{R_3} + \frac{V_0}{R_2}$$

$$V_a = V_{UTP} \text{ when } V_0 = +V_{sat}$$

$$V_a = V_{LTP} \text{ when } V_0 = -V_{sat}$$

$$V_a = \frac{\frac{V_{ref}}{R_3} + \frac{V_{sat}}{R_2}}{\left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]}$$

$$V_{UTP} = \frac{\frac{-10}{10} + \frac{12}{50}}{\left[\frac{1}{10} + \frac{1}{10} + \frac{1}{50} \right]} = -3.4545 \text{ V}$$

$$V_{LTP} = -5.6363 \text{ V}$$

$$V_H = V_{UTP} - V_{LTP}$$

$$V_H \approx 2.19$$

48. Ans: 8021 (Range 8015 to 8030)

Sol: Given data: Number of poles = 12

Reactances of $X_d = 5\Omega$, $X_q = 3\Omega$.

Power factor is unity

$$S = \sqrt{3} V_L I_L$$

$$\Rightarrow 20 \times 10^6 = \sqrt{3} \times 11 \times 10^3 I_a$$

$$I_a = \frac{20 \times 10^3}{\sqrt{3} \times 11 \times 10^3} = 1049.72 \text{ A}$$

At unity power factor

$$V \sin \delta = I_q X_q$$

$$I_q = I_a \cos \delta$$

$$I_d = I_a \sin \delta$$

$$\therefore V \sin \delta = (I_a \cos \delta) X_q$$

$$\tan \delta = \frac{I_a X_q}{V} = \frac{1049.7 \times 3}{(11 \times 10^3) / \sqrt{3}} = 0.49585$$

$$\delta = 26.4^\circ$$

$$I_q = I_a \cos \delta = 1049.72 \cos 26.4^\circ = 940.3$$

$$I_d = I_a \sin \delta = 1049.72 \sin 26.4^\circ = 466.7$$

Excitation voltage per phase,

$$E = V \cos \delta + I_d X_d$$

$$= \frac{11 \times 10^3}{\sqrt{3}} \cos 26.4^\circ + 466.7 \times 5$$

$$= 5688 + 2333.5$$

$$= 8021.5 \text{ V}$$

49. Ans: (B)

Sol: Given $v = y + e^{-x} \cos y$

$$\Rightarrow v_x = -e^{-x} \cos(y) \text{ and } v_y = 1 - e^{-x} \sin(y)$$

$$\text{Consider } du = (u_x) dx + (u_y) dy$$

$$= (v_y) dx + (-v_x) dy$$

$$\Rightarrow du = (1 - e^{-x} \sin y) dx + (e^{-x} \cos y) dy$$

$$\Rightarrow \int du = \int (1 - e^{-x} \sin y) dx + \int 0 dy + k$$

$$\Rightarrow u = x + e^{-x} \sin y + k$$

Now the required analytic function $f(z)$ is given by $f(z) = u + iv$

$$\Rightarrow f(z) = (x + e^{-x} \sin y + k) + i(y + e^{-x} \cos y)$$

$$\therefore f(z) = z + ie^{-z} + k$$

50. Ans: (D)

Sol: From Poisson's equation, we have

$$\nabla^2 V = -\frac{\rho_v}{\epsilon_0}$$

$$\rho_v = -\epsilon_0 \nabla^2 V$$

$$\frac{\partial V}{\partial r} = \frac{-100 \sin \theta}{r^3}$$

$$\frac{dV}{d\theta} = \frac{50 \cos \theta}{r^2}, \frac{\partial V}{\partial \phi} = 0$$

So,

$$\nabla^2 V = \frac{1}{r^2} \frac{\partial}{\partial r} \left(r^2 \frac{\partial V}{\partial r} \right) + \frac{1}{r^2 \sin \theta} \frac{\partial}{\partial \theta} \left(\sin \theta \frac{\partial V}{\partial \theta} \right) + 0$$

$$= \frac{1}{r^2} \frac{\partial}{\partial r} \left(r^2 \times -\frac{100 \sin \theta}{r^3} \right) + \frac{1}{r^2 \sin \theta} \frac{\partial}{\partial \theta} \left(\frac{\sin \theta \times 50 \cos \theta}{r^2} \right)$$

$$= \frac{1}{r^2} \times \frac{100 \sin \theta}{r^2} + \frac{1}{r^4 \sin \theta} \times 50 \cos 2\theta$$

$$= \frac{100 \sin \theta}{r^4} + \frac{50(1 - 2 \sin^2 \theta)}{r^4 \sin \theta}$$

$$= \frac{50}{r^4 \sin \theta}$$

$$\text{Now, } \rho_v = -\epsilon_0 \nabla^2 V = -\epsilon_0 \frac{50}{r^4 \sin \theta}$$

$$\text{So, } Q = \int \rho_v dv$$

$$= \int_0^{2\pi} \int_0^{2\pi} \int_0^1 -\epsilon_0 \frac{50}{r^4 \sin \theta} \times r^2 \sin \theta dr d\theta d\phi$$

$$\begin{aligned}
 &= -50\epsilon_0 \int_1^2 \frac{dr}{r^2} \int_0^\pi d\theta \int_0^{2\pi} d\phi \\
 &= -50\epsilon_0 \left[\frac{-1}{r} \right]_1^2 [\pi] [2\pi] \\
 &= -50\epsilon_0 \times \frac{1}{2} \times 2\pi^2 \\
 &= -50\epsilon_0 \pi^2 = -50 \times \frac{10^{-9}}{36\pi} \times \pi^2 \\
 &= -\frac{50\pi}{36} \text{ nC} = -4.36 \text{ nC}
 \end{aligned}$$

51. (Range: 608 to 612)

Sol: Given:

Rating of transformers = 100 MVA at 220 kV

Magnetizing current interrupted at 44% of its peak value.

Capacitance = 2000 μ F

And inductance L = 35 H

Full load transformer current

$$I_{fl} = \frac{100 \times 1000}{\sqrt{3} \times 220} = 262.43 \text{ A}$$

$$\begin{aligned}
 \text{Magnetizing current } I_\mu &= \frac{4}{100} \times I_n \\
 &= \frac{4}{100} \times 262.43 \\
 &= 10.49 \text{ A}
 \end{aligned}$$

Magnetizing current at the moment of


$$\begin{aligned}
 \text{interruption } i &= \frac{44}{100} \times I_\mu \\
 &= \frac{44 \times 10.49 \text{ A}}{100} = 4.61 \text{ A}
 \end{aligned}$$

Now if V is the voltage that may appear across the circuit breaker contacts, then

$$\begin{aligned}
 V &= i \sqrt{\frac{L}{C}} = 4.61 \sqrt{\frac{35}{2000 \times 10^{-6}}} \\
 &= 609.8 \text{ V}
 \end{aligned}$$

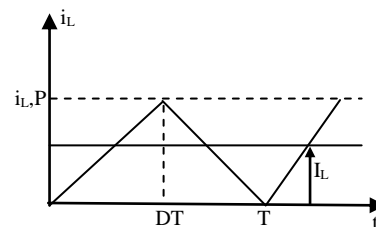52. Ans: (D)

Sol: At boundary conditions, inductor current waveform is shown below:



$$I_L = \frac{1}{2} i_{L,p} = \frac{10}{2} = 5 \text{ A}$$

Average output voltage, $V_o = D \times V_{dc} = 0.2 \times 500 = 100 \text{ V}$. As average inductor voltage is zero, $E = V_o = 100 \text{ V}$

Power delivered to the battery = $I_L \times E = 5 \times 100 = 500 \text{ W}$

From 0 to DT, inductor current slope, $\frac{V_{dc} - E}{L} = \frac{i_{L,p}}{DT}$


Conduction time of the switch,

$$DT = \frac{0.06 \times 10}{500 - 100} = 1.5 \text{ ms}$$

53. Ans: 171 (Range: 165 to 175)

Sol: Now 1V is applied at primary side a-a'

$$R = \frac{1}{i}$$

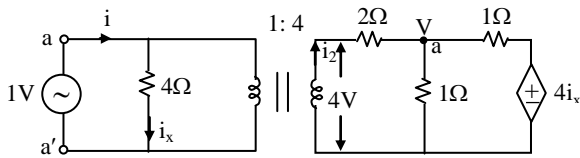

By transformation ratio

$$K = \frac{4}{1} = 4$$

$$\frac{V_2}{V_1} = k = 4$$

$$V_2 = 4V$$

$$i_x = \frac{1}{4}A$$

Apply KCL at node-a,

$$\frac{V-4}{2} + \frac{V}{1} + \frac{V-4i_x}{1} = 0$$

$$V-4+2V + 2V -8i_x = 0$$

$$5V = 4+8i_x = 4 + 8 \times \frac{1}{4} = 6$$

$$V = \frac{6}{5}V$$

i_2 is current flows through secondary winding then

$$i_2 = \frac{4 - \frac{6}{5}}{2} = \frac{14}{10} = 1.4A$$

This i_2 transferred to primary then

$$i'_2 = 1.4 \times 4$$


$$\therefore i = i_x + i'_2$$

$$= \frac{1}{4} + 1.4 \times 4 = 5.85 A$$

$$\therefore R = \frac{1}{i} = \frac{1}{5.85} = 171 \text{ m}\Omega$$

54. Ans: (C)

Sol:

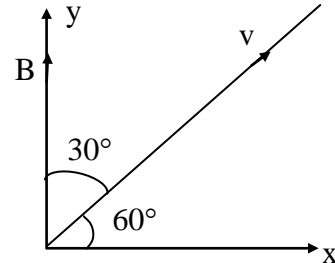


Angle between the B and v is 30° , so the path of the particle is helix.

$$T = \frac{2\pi m}{Bq} = \frac{2\pi \times 1.67 \times 10^{-27}}{0.104 \times 1.6 \times 10^{-19}} = 2\pi \times 10^{-7} \text{ sec}$$

$$r = \frac{mv \sin \theta}{Bq} = \frac{1.67 \times 10^{-27} \times 2 \times 10^6}{1.6 \times 10^{-19} \times 0.104} \times \sin 30^\circ = 0.1m$$

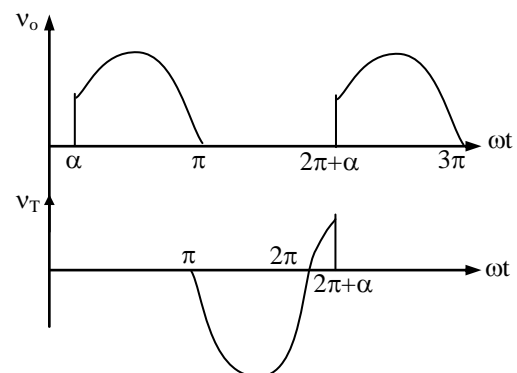55. Ans: 231.5 to 232.5

Sol: $V_S = 300 V$ $R_L = 100\Omega$ $\alpha = 60^\circ$



Moving Iron voltmeter reads r.m.s value of voltage

When thyristor is 'ON' reading is zero

When thyristor is off

$$\begin{aligned}
 V_{r.m.s} &= \left[\frac{1}{2\pi} \int_{\pi}^{2\pi+\alpha} V_m^2 \sin^2 \omega t \, d\omega t \right]^{\frac{1}{2}} \\
 &= \left[\frac{V_m^2}{2\pi} \int_{\pi}^{2\pi+\alpha} \frac{1 - \cos 2\omega t}{2} \, d\omega t \right]^{\frac{1}{2}} \\
 &= \frac{V_m}{2\sqrt{\pi}} \left[\pi + \alpha - \frac{1}{2} \left(\sin 2(2\pi + \alpha) - \frac{1}{2} \sin 2\pi \right) \right]^{\frac{1}{2}} \\
 &= \frac{V_m}{2\sqrt{\pi}} \left[(\pi + \alpha) - \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}} \\
 &= \frac{300 \times \sqrt{2}}{2\sqrt{\pi}} \left[(\pi + 60^\circ) \times \frac{\pi}{180} - \frac{1}{2} \sin \frac{2\pi}{3} \right]^{\frac{1}{2}} \\
 &= 231.94 \text{ V}
 \end{aligned}$$