

GATE-2020 General Aptitude (GA)

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Shubaneswar | Lucknow | Patna | Sengaluru | Chennal | Vijayawada | Vizag | Tirupati | Kukatpaliy | Kolkata | Ahmedabad

Branch: Electrical Engineering Mock-A - Solutions

07. Ans: (B)

=

	I I I I I I I I I I				
01.	Ans: (A)	Sol: Let principle be 4. Then amount = $4 \times \frac{7}{4} = 7$			
Sol:	Vulgarity (n.) means offensive speech or	Interest = $7 - 4 = 3$			
	conduct.	Rate of interest $=\frac{3\times100}{4\times4}=18\frac{3}{4}\%$			
02.	Ans: (A) 03. Ans: (B)				
04.	Ans: (A)	08. Ans: (C) Sol: Net part filled in 1 hour =			
Sol:	Cylinder volume = $\pi r^2 h = \frac{22}{7} \times 10 \times 10 \times$	$\frac{1}{10} + \frac{1}{12} - \frac{1}{20} = \frac{6+5-3}{60} = \frac{11-3}{60} = \frac{8}{60} = \frac{2}{15}$			
	$14 = 4400 \text{ m}^3$	The tank will be full in $\frac{15}{2}$ hrs			
05.	Ans: (D)	= 7 hrs.30 min.			
Sol:	Speed = 10 kmph = $10 \times \frac{5}{18} m/\text{sec}$ =	09 Ans. (A)			
	$\frac{50}{18}$ m/sec	Sol: Share of wealth that C gets (in Rs lakhs) =			
	Man walks 50 m in 18 sec.	20 $Tax = 40%$			
06.	Ans: (D)	\Rightarrow Wealth tax (in Rs lakhs) that C has to pay			
Sol:	Rate downstream = $(24/2)$ kmph = 12 kmph.	$=\frac{40}{100}\times 20=8$			
	Rate upstream = $(24/4)$ kmph = 6 kmph.	100			
	Therefore, speed in still water = $1/2^*$ (12 +				
	6) = 9 kmph.				



10. Ans: (A)

Sol: Note that an assumption is like a premise in that if it is wrong the argument is invalid, and if it is right it supports the conclusion. If the statement in (A) is correct, it supports the idea that point and shoot is not art, but if it is wrong, and choosing what to point the camera at involves art, then the argument is invalid. Hence, (A) is an assumption.

Specialization (EE)

01. Ans: (D)



Fourier transform of periodic signal x(t) is

$$X(\omega) = 2\pi \sum_{n=-\infty}^{\infty} C_n \,\delta(\omega - n\omega_s)$$

Where $C_n = \frac{1}{T} \int_0^T x(t) e^{-jn\omega_0 t} dt$
$$= \frac{1}{2} \int_0^2 \delta(t) e^{-jn\pi t} dt = \frac{1}{2}$$
$$X(\omega) = \frac{2\pi}{2} \sum_{n=-\infty}^{\infty} \delta(\omega - n\pi)$$
$$X(\omega) = \pi \sum_{n=-\infty}^{\infty} \delta(\omega - n\pi)$$

02. Ans: (D)

$$P(x = 1) = 0.5 P(x = 2)$$

 $\lambda e^{-\lambda} = 1 \lambda^2 e^{-\lambda}$

$$\frac{\lambda e}{1!} = \frac{1}{2} \frac{\lambda e}{2!}$$

$$\Rightarrow \lambda = 4$$

P (x = 4) = $\frac{\lambda^4 e^{-\lambda}}{4!} = \frac{4^4 e^{-4}}{24} = \frac{32}{3} e^{-4}$



Three non touch loop gains = $G_1 H_1 G_3 H_3 G_5 H_4$ = $G_1 H_1 G_3 H_3 G_6 H_5$

06. Ans: (D)
Sol:
$$I_0 = C$$

 $I_1 = D$
 $I_2 = \overline{C}$
 $I_3 = \overline{C} \ \overline{D}$



S ₁	S ₀	
Α	B	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

F(A, B, C, D)

$$= \overline{A} \ \overline{B} \ C + \overline{A} \ BD + A \ \overline{B} \ \overline{C} + AB(\overline{C} \ \overline{D})$$

$$= \overline{A} \ \overline{B} \ C(D + \overline{D}) + \overline{A} \ B(C + \overline{C}) D$$

$$+ A \overline{B} \overline{C} (D + \overline{D}) + AB \overline{C} \overline{D}$$

$$= \overline{A} \ \overline{B} \ CD + \overline{A} \ \overline{B} \ C\overline{D}$$

$$+\overline{A} BCD + \overline{A} B\overline{C} D + A\overline{B}\overline{C} D$$

$$+A \overline{B} \overline{C} \overline{D} + AB \overline{C} \overline{D}$$

$$\mathbf{F} = \sum \mathbf{m}(2, 3, 5, 7, 8, 9, 12)$$

07. Ans: 0.5 (No range)

Sol: Starting current $I_{st (s,DOL)} = I_{sc}$ (with rated voltage).

With V_1 (Reduced voltage) (40% of V)

$$I_{sc1} = 2.5 I_{f1}$$

$$0.4V \propto 2.5 I_{f1}$$

$$\frac{0.4V}{V} = \frac{2.5I_{f1}}{I_{sc}}$$

$$I_{sc} = \frac{2.5}{0.4} I_{f1} = \frac{25}{4} I_{f1}$$

Auto transformer starting line current, $I_{st} \label{eq:s,A.T}_{(s,A.T)}$ = $k^2 \; I_{st(DOL)}$

1.5
$$I_{f1} = K^2 \cdot \frac{25}{4} \cdot I_{f1}$$

 $K^2 = \frac{1.5 \times 4}{25} = \frac{6}{25}$
Transformation

ratio, K =
$$\sqrt{\frac{6}{25}} = 0.489$$

Sol:
$$G(s) = \frac{300}{s(s+1)(s+15)(s+20)}$$

= $\frac{300}{s(1+s)15(1+\frac{s}{15})20(1+\frac{s}{20})}$
= $\frac{1}{s(s+1)(1+\frac{s}{15})(1+\frac{s}{20})}$

Approximate transfer function (considering dominant pole only) of system is

$$G(s) = \frac{1}{s(1+s)}$$

09. Ans: (C)

Sol: In order to eliminate seventh order harmonic,

the pulse width is equal to
$$2d = \frac{2\pi}{n}$$
,
 $\frac{4\pi}{n}, \frac{6\pi}{n}, \frac{8\pi}{n}, \dots$
Hence, $2d = \frac{2\pi}{n} = \frac{2\pi}{7} = 51.43$, 102.86, 154.3...

ACE Engineering Publications

10. Ans: (B)

Sol: Find Thevenin's equivalent circuit. With 2 Ω acting, voltage across it V =6V With 4 Ω acting, voltage across it V=11V Difference in voltage is 5V

11. Ans: 123 (Range from 120 to 125)

Sol: At no load

$$I_{s} = C \cdot \frac{V_{sph}}{A}$$
$$|I_{s}| = \frac{1}{Z_{c}} \sin \beta \ell \cdot \frac{1}{\cos \beta \ell} \cdot V_{sph}$$
$$\lambda = \frac{3 \times 10^{8}}{50}$$
$$= \frac{1}{Z_{c}} Tan \beta \ell \cdot V_{sph}$$
$$\beta = \frac{2\pi}{\lambda}$$
$$= \frac{1}{400} \times tan \left(1.047 \times 10^{-3} \times 200 \times \frac{180}{\pi} \right) \times \frac{400}{\sqrt{3}} \text{ kA}$$
$$= 0.1227 \text{ kA}.$$

12. Ans: (d)

Sol: Generalized Maxwell's equations are

1.
$$\nabla \times \vec{E} = -\frac{\partial \overline{B}}{\partial t}$$

2. $\nabla \cdot \vec{D} = \rho_v$
3. $\nabla \times \vec{H} = J_c + \frac{\partial \overline{D}}{\partial t}$
4. $\nabla \cdot \vec{B} = 0$
For static fields $\frac{\partial}{\partial t}(*) = 0$

1.
$$\nabla \times \vec{E} = 0$$

2. $\nabla . \vec{D} = \rho_v$
3. $\nabla \times \vec{H} = J_c$
4. $\nabla . \vec{B} = 0$

13. Ans: 10 (no range)

Sol: Circuit at $t = 0^{-}$ is



By KVL
$$\Rightarrow 40 - V_C(0^-) - 4 = 0$$

 $\Rightarrow V_C(0^-) = 36 \text{ V} = V_C(0^-)$
 $i_L(0^-) = 0 \text{ A} = i_L(0^+)$
Circuit at $t = 0^+$ is



So, from the circuit $i(0^+) = 10 \text{ A}$

14. Ans: (A)

Sol: Energy stored $\frac{1}{2}$ J $\omega^2 = 4000 \times 100$ Nm or Joules

$$\omega = \frac{2\pi \times 600}{60} = 20\pi \text{ rad}/\text{sec}$$



$$J = \frac{4000 \times 100 \times 2}{(20\pi)^2} = 202.64 \text{ kg} - \text{m}^2$$

For dc motor, the dynamic equation is

$$T_{e} = J \frac{d\omega}{dt} + T_{L}$$
$$dt = \frac{J}{T_{e} - T_{L}} .d\omega$$
$$t = \frac{J}{T_{e} - T_{L}} .\omega$$

Given T_L = motor full load torque, T_{efl}

$$T_{\rm efl} = \frac{100 \times 746}{20 \pi} \, \mathrm{N.m}$$

As current during starting is limited to 1.5 time, the full load current, the starting torque.

$$T_{est} = 1.5 T_{efl}$$

$$t = \frac{J}{T_{est} - T_{efl}} .\omega = \frac{202.64 \times 20\pi}{0.5 \times 100 \times 746} \times 20\pi$$

$$t = 21.44 \text{ sec}$$

15. Ans: (B)

Sol:
$$G(j\omega) = \frac{3(2-j\omega)}{(j\omega+1)(j\omega+5)}$$

 $\Rightarrow M = \frac{3\sqrt{4+\omega^2}}{\sqrt{\omega^2+1}\sqrt{\omega^2+25}}$
 $\omega = 0$ magnitude M =1.2
 $\Rightarrow \phi = -\tan^{-1}\left(\frac{\omega}{2}\right) - \tan^{-1}(\omega) - \tan^{-1}\left(\frac{\omega}{5}\right)$
 $\omega = 0$ ------ $\phi = 0^{\circ}$
 $\omega = \infty$ ------ $\phi = -270^{\circ}$
The polar starts at $1.2 \angle 0^{\circ}$ and ends at $0 \angle -270^{\circ}$

16. Ans: 0 Reasons \Rightarrow the given wave has half wave symmetry

17. Ans: 40 (No Range) Sol:

$$I_{sh} = 0.01\Omega$$

$$M_{sh} = 0.01\Omega$$

$$V_{m} = V_{sh}$$

$$V_{m} = 400 \text{mV}$$

$$I_{sh} = \frac{V_{m}}{R_{sh}} = \frac{400 \times 10^{-3}}{0.01}$$

$$I_{sh} = 40 \text{A}$$

18. Ans: (B)

Sol: Relationship between impulse response and step response is

$$h(t) = \frac{d}{dt} s(t)$$

Given, $s(t) = 2e^{-3t} u(t)$
$$h(t) = 2 [e^{-3t} \delta(t) - 3 e^{-3t} u(t)]$$

$$= 2e^{-3t} \delta(t) - 6 e^{-3t} u(t)$$

But $e^{-3t} \delta(t) = 1 \delta(t)$
 $\therefore h(t) = 2\delta(t) - 6 e^{-3t} u(t)$

19. Ans: 10 (no range)

Sol: Given data; B = 110 MW/Hz R = 0.01 Hz/MW D = ? $B = D + \frac{1}{R}$ GATE-2020 Electrical Engineering (EE)

 $110 = D + \frac{1}{0.01} \Longrightarrow D = 10 \, MW/Hz$

20. Ans: 12

- Sol: Given CMRR = 80dB = 10⁴ & A_C = 1.5 Step(1): CMRR = $\frac{A_d}{A_c} \Rightarrow A_d = 1.5 \times 10^4$ (1) Step(2): V_o = A_dV_{id} + A_CV_C (2) \therefore V_{id} = V₁ - V₂, V_C = $\frac{V_1 + V_2}{2}$ = 1.5 × 10⁴ (100.5 - 99.5)mV + 1.5 $\left(\frac{100.5 + 99.5}{2}\right)$ mV (3) = 1.5 × 10⁴ × 1 × 10⁻³ V + 1.5 × 100 × 10⁻³ V (4)
 - =15.15V___(5)

NOTE: The maximum possible output voltage in an op-amp circuit is $\leq V_{sat}$

$$\therefore V_{o} = +12V_{o}$$
 (6)

Т

21. Ans: (B)

Sol:
$$\overline{B} = \nabla \times \overline{A} = \frac{1}{\rho} \begin{vmatrix} \hat{\rho} & \rho \hat{\phi} & \hat{z} \\ \frac{\partial}{\partial \rho} & \frac{\partial}{\partial \phi} & \frac{\partial}{\partial z} \\ \rho^2 & \rho \cdot \frac{\rho}{2} & 0 \end{vmatrix}$$
$$= \frac{1}{\rho} \Big[\hat{\rho} (0 - 0) - \rho \hat{\phi} (0 - 0) + \hat{z} \Big(\frac{2\rho}{2} - 0 \Big) \Big]$$
$$= \frac{1}{\rho} \Big[\rho \hat{z} \Big] = \hat{z} W b / m^2$$

T

22. Ans: -1 (No Range)
Sol:
$$X(z) = \frac{2+3z}{1-z+3z^2} = 2+5z-z^2+---$$

So, $x(-2) = -1$

23 Ans: (C)

Sol:
$$\frac{dy}{dx} = 4x^3 e^{-y}$$

Using variable separable method $e^{y} = x^{4} + c$ at x =1, y =0, \Rightarrow c=0

$$\Rightarrow e^y = x^4$$

24. Ans: (c) Sol: LXI B, 0010H : $(BC) \leftarrow 0010H$ LOOP: DCX B : $(BC) \leftarrow (BC)-1$ MOV A, B : $(A) \leftarrow (B)$ ORA C : $(A) \leftarrow (A)V(C)$: This logical operation sets

'Z' Flag

JNZ LOOP

: when (BC)
becomes 0000H
: Branch to
"LOOP" if Z =0
: LOOP will be

continued for 16 times

25. Ans: (**D**) **Sol:** $z^2 + 9 = 0 \Rightarrow z = \pm 3i$

 $z_0 = 3i$ lies inside the circle.





$$\therefore I = 2\pi i \lim_{z \to 3i} \frac{(z - 3i)}{(z + 3i)(z - 3i)}$$
$$= 2\pi i \cdot \frac{1}{6i} = \frac{\pi}{3}$$

Q. 26 – Q. 55 carry TWO marks each.

26. Ans: 7.07V (Range: 6.5to7.5)

Sol: Vertical sensitivity = 4 V/cm

Peak to peak amplitude = 5 cm

 $\therefore V_{p-p} = (vertical sensitivity) \times (distance$

between peak to peak)

$$V_{pp} = 4 \times 5 = 20V$$
$$V_{p} = \frac{V_{pp}}{2} = \frac{20}{2} = 10V$$
$$V_{rms} = \frac{V_{p}}{\sqrt{2}} = \frac{10}{\sqrt{2}}$$
$$\Rightarrow V_{rms} = 7.07 V$$

27. Ans: 379.26 (Range: 378 to 381)

Sol: Step (1): From the circuit, $V_0 = 10V + 0.7V$

 $= 10.7 V = V_{CE}$ (1)





$$\Rightarrow I_{L} = \frac{V_{0}}{1k} = 10.7 \text{mA} _ (2)$$
Step (2): KVL for input loop
$$I_{S} = \frac{20V - 10.7V}{200\Omega} = 46.5 \text{mA} _ (3)$$
Step (3): KCL at node V₀

$$I_{S} = I_{Z} + I_{C} + I_{L} = I_{B} + I_{C} + I_{L} _ (4)$$
[:: I_B = I_Z]
$$\Rightarrow$$

$$I_{C} \left[1 + \frac{1}{\beta} \right] = 46.5 \text{mA} - 10.7 \text{mA} = 35.8 \text{mA} _ (5)$$

$$\Rightarrow I_{C} = 35.445 \text{mA} _ (6)$$
Step(4): P_C = V_{CE} I_C

= 379.26mW____(7)

28. Ans: 224.17 (Range 222 to 226)

Sol: When source inductance is not taken into account, each diode will conduct for 180° . When source inductance is taken into account, each diode will conduct for $(180 + \mu)^{\circ}$

Where μ is overlap angle and can be determined as follows:

$$\cos \mu = 1 - \frac{2\omega L_s}{V_m} I_o$$

$$\Rightarrow \cos \mu = 1 - \frac{2 \times 100\pi \times 10 \times 10^{-3}}{220\sqrt{2}} \times 14 = 0.71727$$

$$\Rightarrow \mu = 44.17^\circ$$

$$\therefore \text{ Conduction angle for } D_i \text{ is } 180 + 44.17$$

 $\therefore \text{ Conduction angle for } D_1 \text{ is } 180 + 44.17$ $= 224.17^{\circ}$



29. Ans: (B)

Sol: $g(x) = \frac{f(x)}{x+1}$ g(x) in continuous and differentiable in [0, 5]. By Lagrange's theorem, there exists a value

$$g^{1}(c) = \frac{g(5) - g(0)}{5 - 0}$$
$$= \frac{\left(-\frac{1}{6}\right) - 4}{5} = \frac{-5}{6}$$

 $c \in (0, 5)$, such that

30. Ans: (C)

Sol:
$$P_{m1} = \frac{EV}{X_{eq}} = \frac{1.0 \times 1.0}{0.5} = 2.0$$

 $P_{m2}=0$

 $P_{m3} = 0.75 \ P_{m1} = 1.5$

$$\delta_0 = \sin^{-1} \left(\frac{\mathbf{P}_{s}}{\mathbf{P}_{m1}} \right) = 30$$

 $\delta_0(rad) = 0.523$

$$\delta_{\rm m} = 180 - \sin^{-1} \left(\frac{{\rm P}_{\rm s}}{{\rm P}_{\rm m3}} \right)$$
$$= 180 - \sin^{-1} \left(\frac{1.0}{1.5} \right) = 138.2^{\rm o}$$

 $\delta_{\rm m}({\rm rad}) = 2.41$

$$\delta_{c} = \cos^{-1} \left(\frac{P_{s}(\delta_{m} - \delta) + P_{m3} \cos \delta_{m}}{P_{m3}} \right)$$

$$=$$

$$\cos^{-1}\left[\frac{1.0(2.41 - 0.523) + 1.5\cos 138.2)}{1.5}\right]$$

$$= \cos^{-1} \left[\frac{1.0(2.41 - 0.523) - 1.118}{1.5} \right]$$
$$= \cos^{-1} (0.512) = 59.2^{\circ}$$

31. Ans: 99.8 (Range: 99 to 100)

Sol:





Step (1):

From the small signal model shown in

fig(a)

$$V_{i} = -h_{fe}i_{b}R_{C}$$

$$= -100 \times 1k\Omega \quad i_{b}$$

$$V_{o} = AV_{i}$$

$$= 1000 \times 100 \times 1k \Omega \quad i_{b}$$

$$V_{f} = \beta V_{o} = \beta AV_{i}$$

$$= \frac{1}{100} \times (-1000) \times (-100) \times 1k\Omega \quad i_{b}$$

$$= 1000 \times 1k\Omega \quad i_{b}$$
(2):

Step (2):

KVL for input loop $V_s = i_b [R_s+h_{ie}]+V_f$ $= i_b[R_s+h_{ie}+1000\times 1k\Omega]$

ACE Engineering Academy



$$= i_b [2k\Omega + 1000k\Omega]$$

Step (3): $\frac{V_0}{V_s} = \frac{1000 \times 100 \times 1k\Omega i_b}{1002 k\Omega i_b}$
$$= 99.8$$

32. Ans: (C)

Sol: $\omega_0 = \text{GCD}(4, 12) = 4$

 $\begin{aligned} x(t) &= 3 \sin (\omega_0 t + 20^\circ) - 4 \cos(3\omega_0 t - 40^\circ) \\ x(t) &= 3 \sin (\omega_0 t + 20^\circ) + \end{aligned}$

$$4\cos(3\omega_0t + 140^{\circ})$$

The phase of III harmonic is 140°

33. Ans: 1334 (Range 1130 to 1340)

Sol: Given data, $P=4,\,V_L=440$ V, $R_2=0.1\Omega$,

 $X_2 = 0.8 \ \Omega, \ K = 1.3$

For maximum mechanical power output



$$R_{2}\left(\frac{1}{s}-1\right) = \sqrt{R_{2}^{2} + X_{2}^{2}}$$
$$\frac{1}{s}-1 = \frac{\sqrt{(0.1)^{2} + (0.8)^{2}}}{0.1}$$
$$\frac{1}{s}-1 = 8.062$$
$$\frac{1}{s} = 9.062$$
$$s = 0.1103$$
(i) Nr = Ns (1 - s)

= 1500 (1 – 0.1103) = 1334 rpm

34. Ans: (D)

Sol: [A/B] =

[1	2	3	14		1	2	3	14
1	4	7	30	~	0	2	4	16
1	1	1	λ		0	0	0	$2\lambda - 12$

To be consistent Rank of augmented matrix $(\rho(A/B))$ and Rank of A matrix should be equal.

 $\rho(A/B) = \rho(A) = 2\lambda - 12 = 0 \Longrightarrow \lambda = 6$

35. Ans: (C)

Sol: $x(t) = C_{12} (A \cos t) 0 < t < 2\pi$

$$C_{12} = \frac{\int_{t_1}^{t_2} x(t) A \cos t}{\int_{t_1}^{t_2} (A \cos t)^2 d t}$$

= $\frac{\int_{0}^{\pi/2} A^2 \cos t + \int_{\pi/2}^{3\pi/2} -A^2 \cos t + \int_{3\pi/2}^{2\pi} A^2 \cos t}{\int_{0}^{2\pi} A^2 \cos^2 t d t}$
$$C_{12} = \frac{4}{\pi}$$

So, $x(t) = \frac{4A}{\pi} \cos t \quad 0 < t < 2\pi$



36. Ans: (A)

Sol:



$$X_{1eq} = \frac{j0.2}{2} = j0.1$$

$$X_{2eq} = \frac{j0.2}{2} = j0.1$$

$$X_{0eq} = X_0 + 3X_n + 3X_F$$

$$= 0.05 + 3 \times 0.05 + 3 \times 0.05$$

$$= 0.35$$

$$I_{R_0} = I_{R_1} = \frac{E_{R_1}}{Z_{1eq} + Z_{2eq} + Z_{0eq}}$$

$$= \frac{1.0}{j0.1 + j0.1 + j0.35}$$

$$I_{R_0} = I_{R_1} = \frac{1.0}{j0.1 + j0.1 + j0.35}$$

$$I_{R_0} = I_{R_1} = \frac{1.0}{j \, 0.55} = 1.82 \angle -90^{\circ}$$
$$V_{R_0} = -I_{R_0} X_{_{0eq}} = -1.82 \angle -90^{\circ} \times 0.2 \angle 90^{\circ}$$
$$V_{R_0} = -0.364 = 0.364 \text{ pu}$$

$$V_{R_0} = 0.364 \times \frac{13.2}{\sqrt{3}} = 2.77 \, kV$$

37. Ans: (C)

Sol: Number of ways we can distribute 5 red balls into 3 numbered boxes

= C(3-1+5, 5) = 21

Similarly we can distribute 5 white balls in 21 ways and 5 blue balls in 21 ways. By product rule, required number of ways =

(21)(21)(21) = 9261

38. Ans: (B)

Sol: In buck boost converter, $V_T = V_0 + V_{dc} = \frac{V_0}{D}$

$$\left[\because \mathbf{V}_{o} = \mathbf{V}_{dc} \left(\frac{\mathbf{D}}{1 - \mathbf{D}} \right) \right]$$

and $I_{T} = I_{L} = \frac{I_{0}}{1 - D}$ (symbols have their

usual meaning)

Therefore,
$$\frac{P_0}{P_T} = \frac{V_0 I_0}{\left(\frac{V_0}{D}\right) \times \left(\frac{I_0}{1-D}\right)} = D(1-D)$$

It has maximum value at D = 0.5 and the maximum value of 0.25.

39. Ans: (B)

Sol: Total marbles = 10 + 30 + 20 + 15 = 75
P[both are white] = P[first is white and
second is white]

$$=\frac{30}{75}\times\frac{30}{75}=\frac{4}{25}$$



40. Ans: (B)

Sol:



$$V_{\text{test}} = 10 + j\omega L + \frac{1}{j\omega C} \times 6$$
$$Z_{\text{in}} = \frac{V_{\text{test}}}{1} = 10 + j \left(\omega L - \frac{6}{\omega C}\right)$$

At resonance, imaginary part of Z_{in} is zero

$$\omega_0 L - \frac{6}{\omega_0 C} = 0$$

$$\omega_0^2 LC = 6$$

$$\omega_0^2 = \frac{6}{LC}$$

$$\omega_0 = \sqrt{\frac{6}{LC}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{6}{LC}} = \frac{1}{2\pi} \sqrt{\frac{6}{1m \times 50 n}}$$

$$f_0 = 55 \text{ kHz}$$

41. Ans: (D)

Sol: Let voltage drop across the switch = V_t and voltage drop across the diode = V_d

When the switch is ON (0 to DT):

$$L\frac{di_{L}}{dt} = V_{dc} - V_{t}$$

When the switch is OFF (DT to (1-D)T):

$$L\frac{di_{L}}{dt} = V_{dc} - V_{0} - V_{d}$$

Apply volt-sec balance equation:

$$(V_{dc} - V_t)DT + (V_{dc} - V_o - V_d)(1 - D)T = 0$$

$$\Rightarrow V_0 = \left[\frac{V_{dc}}{1 - D}\right] \left[1 - D\frac{V_t}{V_{dc}} - \left(\frac{1 - D}{D}\right)\frac{V_d}{V_{dc}}\right]$$

$$\Rightarrow V_0 = \left[\frac{50}{1 - 0.5}\right] \left[1 - 0.5 \times \frac{0.5}{50} - \left(\frac{1 - 0.5}{0.5}\right)\frac{0.4}{50}\right]$$

$$= 100 \times 0.987 = 98.7V$$

42. Ans: (A)



The equivalent circuit is







Fig.1

From fig, assuming the transformer to be ideal,

(i)
$$\bar{I}_2 = \frac{240 \angle 0^\circ}{20 \angle 36.86^\circ}$$

= $12 \angle -36.86^\circ = 9.6 - j7.2A$
(ii) $\bar{I}_x = \frac{120 \angle 0^\circ}{10 \angle 0^\circ} = 12 \angle 0^\circ A$

$$\bar{I}_x = \bar{I}_3 - \bar{I}_2 \Longrightarrow 12 \angle 0^\circ = \bar{I}_3 - 12 \angle -36.86$$
$$\implies \bar{I}_3 = 21.6 - j7.2 A$$

(iii) The number of turns of each winding must be as marked in the fig.

For Amp-turn balance,

$$\overline{I}_{1}(20N) = (\overline{I}_{2}N) + (\overline{I}_{3}N) \quad \dots \dots \quad (1)$$

(Since \overline{I}_1 enters its winding at dot and \overline{I}_2 and \overline{I}_3 leave their respective windings at dots, a component of \overline{I}_1 must be in phase with \overline{I}_2 and another component of \overline{I}_1 must be in phase with \overline{I}_3 by dot convention).

$$\bar{I}_{1} = \frac{\bar{I}_{2} + \bar{I}_{3}}{20} = \frac{1}{20} [31.2 - j14.3] A$$
$$= 1.718 \angle -24.76 \circ A$$
Magnitude = 1.718
Power factor = 0.908

44. Ans: (D)

Q₃

Sol: It is a 3 bit shift Register, for each clk pulse

45. Ans: 459.8 (Range: 457.50 – 461.50) Sol:



Line constants are L = 1 mH/km

C = 9.7 nF/km

Length of transmission line, l = 300 km Let us take equivalent – π model in standard form.

In this model $\frac{Y'}{2}$ has to be calculated

For this model $A = 1 + \frac{Z'Y'}{2}, B = Z'$

From these two equation, $\frac{\mathbf{Y}'}{2} = \frac{\mathbf{A} - 1}{\mathbf{B}}$

Where 'A' and 'B' for lossless long line given in the data. For lossless long line. A = $\cos\beta l$, B = jz_c $\sin\beta l$ $\beta = \omega\sqrt{LC} = 2\pi \times 50 \times \sqrt{1 \times 10^{-3} \times 9.7 \times 10^{-9}}$ = 0.978×10⁻³ rad/km $Z_c = \sqrt{\frac{L}{C}} = \sqrt{\frac{1 \times 10^{-3}}{9.7 \times 10^{-4}}} = 321.08\Omega$ Now for line, A = $\cos(0.978 \times 10^{-3} \times 300)$ = 0.9573 B = j 321.08 × $\sin(0.978 \times 10^{-3} \times 300)$ = j92.86 Ω $\frac{Y'}{2} = \frac{A-1}{B} = j4.598 \times 10^{-4} \text{ U}$ From given model $\frac{Y'}{2} = jB$ $\Rightarrow B = 459.8\mu\text{U} = 459.8\mu\text{U}$

46. Ans: 0.5

Sol: CE is
$$|SI - A| = 0$$

 $\begin{vmatrix} s & -1 & 0 \\ 0 & s & -1 \\ 1 & k & s+2 \end{vmatrix} = 0$
 $s [s^{2} + 2s + k] + [1] = 0$
 $s^{3} + 2s^{2} + sk + 1 = 0$
RH criteria
 $s^{3} \begin{vmatrix} 1 & k \\ 2 & 1 \\ s^{1} \end{vmatrix} \begin{vmatrix} \frac{2k - 1}{2} \\ 1 \end{vmatrix}$

The value of k for system becomes just

stable is 2k - 1 = 0 2k = 1 $\therefore k = 1/2$

47. Ans: (B)

Sol:



 $K \bigg|_{s = s_1} = \frac{\text{Product of distance vectors from}}{\frac{\text{various poles of } G(s)H(s) \text{ to } s = s_1}{\text{Product of distance vectors from}}}$ various zeroes of G(s) H(s) to s = s_1

$$k = \frac{\sqrt{80} \times \sqrt{80}}{5} = 16$$

K > 16 the system is over damped.

48. Ans: Range: [6.60 to 7.05]

Sol:







X_{ij} = reactance of line connected between				
bus 'i' and 'j'				
$V_1 \angle \delta_1 = 1 \angle 0^\circ; \qquad \qquad V_3 \angle \delta_3 = 0.98 \angle 8^\circ$				
$V_2 \angle \delta_2 = 0.95 \angle 10^\circ;$ $V_4 \angle \delta_4 = 1.05 \angle -10^\circ$				
$\mathbf{P}_{31} = \frac{\mathbf{V}_3 \mathbf{V}_1}{\mathbf{X}_{31}} \times \sin(\delta_3 - \delta_1)$				
$P_{31} = \frac{0.98 \times 1}{0.05} \times \sin(8^{\circ} - 0^{\circ})$				
$P_{31} = 2.7278 \text{ pu}$				
$\mathbf{P}_{32} = \frac{\mathbf{V}_3 \mathbf{V}_2}{\mathbf{X}_{32}} \times \sin(\delta_3 - \delta_2)$				
$=\frac{0.98\times0.95}{0.2}\times\sin(8^{\circ}-10^{\circ})$				
$P_{32} = -0.1624 \text{ pu}$				
$\mathbf{P}_{34} = \frac{\mathbf{V}_3 \mathbf{V}_4}{\mathbf{X}_{34}} \times \sin(\delta_3 - \delta_4)$				
$P_{34} = \frac{0.98 \times 1.05}{0.1} \times \sin \left[8^{\circ} - \left(-10^{\circ} \right) \right]$				
$P_{34} = 3.1798 \text{ pu}$				
Active power balance at bus (3)				
$P_{g3} = P_{32} + P_{31} + P_{34} + P_{load3}$				
= 2.7278 - 0.1624 + 3.1798 + 1				

$$\begin{split} P_{g3} &= P_{32} + P_{31} + P_{34} + P_{load3} \\ &= 2.7278 \ -0.1624 + 3.1798 + 1 \\ P_{g3} &= 6.7452 \end{split}$$

49. Ans: 2.203 (2.0 to 2.3)

Sol:
$$Z_{in} = j\omega L \parallel \left(R + \frac{1}{j\omega C}\right)$$

$$Z_{in} = \frac{j\omega L \left(R + \frac{1}{j\omega C}\right)}{R + j\omega L + \frac{1}{j\omega C}} = \frac{\frac{L}{C} + j\omega LR}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

$$Z_{in} = \frac{\left(\frac{L}{C} + j\omega LR\right)\left(R - j\left(\omega L - \frac{1}{\omega C}\right)\right)}{R^{2} + \left(\omega L - \frac{1}{\omega C}\right)^{2}}$$

To have a resistive impedance, $Im(Z_{in}) = 0$. Hence,

$$\omega LR^{2} - \left(\frac{L}{C}\right) \left(\omega L - \frac{1}{\omega C}\right) = 0$$

$$\omega R^{2}C = \omega L - 1/\omega C$$

$$\omega^{2}R^{2}C^{2} = \omega^{2}LC - 1$$

$$L = \frac{\omega^{2}R^{2}C^{2} + 1}{\omega^{2}C}$$

Now we can solve for L.

$$L = R^{2}C + 1/(\omega^{2}C)$$

$$= (200^{2})(50 \times 10^{-9}) + 1/[(2\pi \times 50,000)^{2}(50 \times 10^{-9})]$$

$$= 2 \times 10^{-3} + 0.2026 \times 10^{-3}$$

$$= 2.203 \text{mH}$$

50. Ans: 1.515 (1.45 to 1.65)

Sol: Capacitance between two concentric spheres

is

$$C = \frac{4\pi\epsilon ab}{b-a}$$

$$\varepsilon_{0}, \sigma = 10^{-3} \text{U/m}$$



and conductance is given as $G = \frac{\sigma}{\epsilon}C$ $\therefore R = \frac{1}{G} = \frac{\epsilon}{\sigma C} = \frac{\epsilon(b-a)}{\sigma 4\pi\epsilon ab}$ $\therefore R = \frac{b-a}{4\pi\sigma ab} = \frac{(7-3)\times10^{-2}}{4\pi\times10^{-3}\times21\times10^{-4}}$ $=1515.76\Omega$ $=1.515k\Omega$

51. Ans: 50.1Ω [49 to 51]

Sol: When bridge is balanced $V_a = V_b$



$$V_{a} = \frac{10 \times 100}{200} = 5V$$

$$V_{a} = V_{b} = 5V$$

$$I_{R} = \frac{V_{b}}{150} = \frac{1}{30}A$$

$$10 - 100I - 100\left(I - \frac{1}{30}\right) = 0$$

$$I = \frac{1}{15}A$$

$$V_{c} = \left[\frac{1}{15} - \frac{1}{30}\right] \times 100 = 3.33V$$

$$|\mathbf{R}| = \frac{\mathbf{V}_{b} - \mathbf{V}_{c}}{\mathbf{I}_{R}} = \frac{5 - 3.33}{\left[\frac{1}{30}\right]} = 50.1\Omega$$

52. Ans: 0.75

Sol: TF = L[IR] =
$$\frac{2}{(s+2)^2+2^2}$$

$$=\frac{2}{s^2+4s+8}=\frac{C(s)}{R(s)}$$

Steady state error $(e_{ss}) = \lim_{t \to \infty} e(t)$

$$= \underset{s \to 0}{\text{Lt } sE(s)}$$
$$= \underset{s \to 0}{\text{Lt } s}[R(s) - C(s)H(s)]$$
$$e_{ss} = \underset{s \to 0}{\text{Lt } s}[R(s) - C(s)] \quad [\because H(s) = 1]$$
$$= \underset{s \to 0}{\text{Lt } s}[\frac{1}{s} - \frac{2}{s^2 + 4s + 8} \times \frac{1}{s}]$$
$$= 1 - \frac{1}{4} = \frac{3}{4} = 0.75$$

53. Ans: 2 (No range)

Sol:



or $-3I_1 + 3I_2 + 3I_3 - 2I_4 = -5$ (3) At node c, $I_2 = I_3 + 1$ (4) Solving (1), (2), (3) and (4) yields $I_1 = 4$ A, $I_2 = 3$ A, $I_3 = 2$ A, and $I_4 = 4$ A At node b, $i_1 = I_2 - I_1 = -1$ A At node a, $i_2 = 4 - I_4 = 0$ A At node 0, $i_3 = I_4 - I_3 = 2$ A $i_2 + i_3 = 0 + 2 = 2A$

54. Ans: 6. 7 (Range: 6 to 7)

Sol: When a 3-phase synchronous machine is operating on an infinite bus, we can show that

P = power per phase

$$= \frac{\mathrm{EV}}{\mathrm{X}_{\mathrm{d}}} \sin \delta + \frac{\mathrm{V}^2}{2} \left(\frac{1}{\mathrm{X}_{\mathrm{q}}} - \frac{1}{\mathrm{X}_{\mathrm{d}}} \right) \sin 2\delta$$

Where all symbols have their usual meanings.

The term
$$\frac{V^2}{2} \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\delta$$
 is called the

reluctance power P_{rel} . It exist even when there is no excitation; but it is non zero only for salient pole machines where $X_d > X_q$. (For non-salient pole rotor machines, $X_d = X_q = X_s =$ synchronous reactance).

In the problem;
$$P_{rel}/ph = \frac{V^2}{2} \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\delta$$
.

For maximum $P_{rel}(as \ \delta \ varies)$; $\frac{dp_{rel}}{d\delta} = 0$.

Which gives
$$\delta = \left(\frac{\pi}{4}\right) rad$$

$$P_{rel}/ph = \frac{1}{2} \left(\frac{400}{\sqrt{3}}\right)^2 \left(\frac{1}{4} - \frac{1}{6}\right) W$$

Maximum reluctance power fall 3 phases = 6666.66

55. Ans: (a)

Sol:



From boundary condition, $D_{1n}=D_{2n}$ and

$$\frac{D_{1t}}{D_{2t}} = \frac{\varepsilon_1}{\varepsilon_2} \text{ or } D_{2t} = \frac{\varepsilon_2}{\varepsilon_1} D_{1t}$$

$$D_{1n} = D_1 \cos \theta_1 \text{ and } D_{1t} = D_1 \sin \theta_1, \quad \text{where}$$

$$D_1 = \left| \overline{D}_1 \right|.$$
Hence $D_{2n} = D_1 \cos \theta_1$

$$\mathbf{D}_{2t} = \frac{\varepsilon_2}{\varepsilon_1} \mathbf{D}_{1t} = \frac{\varepsilon_2}{\varepsilon_1} \mathbf{D}_1 \sin \theta_1$$

Now

$$D_{2} = \sqrt{(D_{2n})^{2} + (D_{2t})^{2}}$$
$$= \sqrt{(D_{1}\cos\theta_{1})^{2} + \left(\frac{\varepsilon_{2}}{\varepsilon_{1}}D_{1}\sin\theta_{1}\right)^{2}}$$
$$= D_{1}\sqrt{\cos^{2}\theta_{1} + \left(\frac{\varepsilon_{2}}{\varepsilon_{1}}\sin\theta_{1}\right)^{2}}$$

ACE Engineering Academy

