



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad


Branch: Electronics & Communication Engineering - SOLUTIONS

01. Ans: 24 (No range)

Sol: Given that $F(x) = f(g(x))$
 $\Rightarrow F'(x) = f'(g(x)) \cdot g'(x)$ (\because by chain rule)
 $\Rightarrow F'(5) = f'(g(5)) \cdot g'(5)$
 $\Rightarrow F'(5) = f'(-2) \cdot 6$
 $\therefore F'(5) = (4)(6) = 24$

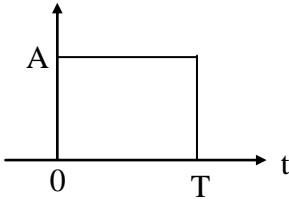02. Ans: (c)

Sol: $E = A^2 T$
 $\frac{S}{N} = \frac{2E}{N_0} = \frac{2A^2 T}{N_0}$



03. Ans: (d)

Sol:

$$\text{i/p} = 5\sin\omega t \quad \boxed{\text{ }} \quad \text{o/p} = 10\cos\omega t$$

$$= 5A \sin(\omega t + \phi)$$

$$10\cos\omega t = 5A \sin(\omega t + \phi)$$

$$A = 2, \phi = 90^\circ$$

If input = $10\cos\omega t$
output = $(10)(2) \cos(\omega t + 90^\circ)$
 $= -20\sin\omega t$

04. Ans: (d)

Sol: We know that,

$$P(A \cap B) \leq \min \{ P(A), P(B) \}$$

$$\Rightarrow P(A \cap B) \leq 0.25 \dots\dots\dots (1)$$

We have, $P(A \cup B) \leq P(S)$

$$\Rightarrow \{P(A) + P(B) - P(A \cap B)\} \leq 1$$

$$\Rightarrow \{0.25 + 0.8 - P(A \cap B)\} \leq 1$$

$$\Rightarrow 0.05 \leq P(A \cap B) \dots\dots\dots (2)$$

From (1) and (2), we have
 $0.05 \leq P(A \cap B) \leq 0.25$

05. Ans: 113.09 (Range: 112.5 to 113.5)

Sol: $D_{\max} = \frac{4\pi}{\lambda^2} A_e$
 $D_{\max} = \frac{4\pi}{\lambda^2} (3\lambda)^2 = 36\pi = 113.09$

06. Ans: 14.66 (14 to 15)

Sol: Transition capacitance

$$C_T = \frac{k}{(V_0 + V_R)^n}$$

When reverse bias voltage V_R is 4V,
 $C_T = 18 \text{ pF}$

$$\text{So, } 18 \times 10^{-12} = \frac{k}{(4.7)^{\frac{1}{3}}}$$

$$k = 18 \times 10^{-12} \times (4.7)^{\frac{1}{3}}$$

When reverse bias voltage V_R is 8V, let the capacitance be C ,

$$C = \frac{k}{(8.7)^{\frac{1}{3}}}$$

$$C = \frac{18 \times 10^{-12} \times (4.7)^{\frac{1}{3}}}{(8.7)^{\frac{1}{3}}}$$

$$C = 14.66 \text{ pF}$$

07. Ans: 388.488 (Range: 387 to 390)

Sol: $i(t) = 4 + 3 \cos(10t - 30^\circ) + 4 \sin(10t + 30^\circ)$
 $= 4 + 3 \cos(10t - 30^\circ) + 4 \cos(10t + 30^\circ - 90^\circ)$
 $= 4 + 3 \cos(10t - 30^\circ) + 4 \cos(10t - 60^\circ)$
 $= 4 + 3 \angle -30^\circ + 4 \angle -60^\circ$
 $= 4 + 3 \cos 30^\circ - j 3 \sin 30^\circ + 4 \cos 60^\circ - j 4 \sin 60^\circ$
 $= 4 + \left[\frac{4 + 3\sqrt{3}}{2} - j \frac{3 + 4\sqrt{3}}{2} \right]$



$$\begin{aligned}
 &= 4 + 6.766 \angle -47.24^\circ \\
 &= 4 + 6.76 \angle -47.24 \\
 i(t) &= 4 + 6.76 \cos(10t - 47.24) \\
 I_{\text{rms}} &= \sqrt{4^2 + \left(\frac{6.76}{\sqrt{2}}\right)^2} \\
 &= \sqrt{38.84}
 \end{aligned}$$

Power dissipated in 10Ω is


$$\begin{aligned}
 P &= I_{\text{rms}}^2 \times R = (\sqrt{38.84})^2 \times 10 \\
 &= 38.84 \times 10 \\
 P &= 388.4 \text{ watts}
 \end{aligned}$$

08. Ans: (b)


$$\begin{aligned}
 \text{Sol: } E_{Fn} - E_{Fi} &= KT \ln \left(\frac{N_D}{n_i} \right) \\
 0.3eV &= 0.02586 \ln \left(\frac{N_D}{n_i} \right) \\
 N_D &= 1.6379 \times 10^{15}/cm^3 \\
 J_n &= nq\mu_n E \\
 &\simeq N_D q\mu_n E \\
 &\simeq 1.6379 \times 10^{15} \times 1.6 \times 10^{-19} \times 1300 \times 10 \\
 &\simeq 3.407 A/cm^2 \\
 &= 3407 \times 10^{-3} A/cm^2
 \end{aligned}$$

09. Ans: (b)

Sol:

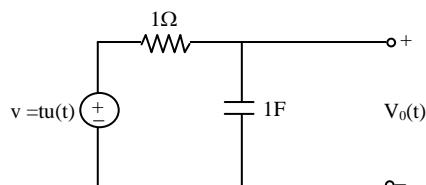

Converting into Laplace domain we get

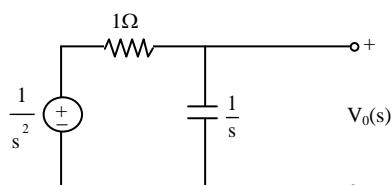

$$\begin{aligned}
 V_0(s) &= \frac{\frac{1}{s} \times \frac{1}{s^2}}{1 + \frac{1}{s}} = \frac{1}{s^3 \left(\frac{s+1}{s} \right)} \\
 &= \frac{1}{s^2 (s+1)}
 \end{aligned}$$

$$V_0(s) = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{s+1}$$

$$B = \left. \frac{1}{s+1} \right|_{s=0} = 1$$

$$A = \left. \frac{dB}{ds} \right|_{s=0} = \left. \frac{(s+1) \times 0 - 1}{(s+1)^2} \right|_{s=0} = -1$$

$$C = \left. \frac{1}{s^2} \right|_{s=-1} = 1$$

$$V_0(s) = \frac{-1}{s} + \frac{1}{s^2} + \frac{1}{s+1}$$

Apply inverse Laplace transform on both sides

$$V_0(t) = -u(t) + tu(t) + e^{-t} u(t)$$


$$V_0(t) = ((t-1) + e^{-t})u(t), t > 0$$

10. Ans: (d)

$$\begin{aligned}
 \text{Sol: } &\text{If } V_A > V_B \text{ all diodes are forward biased hence } R_{AB} = 0. \text{ If } V_A < V_B, D_1 D_3 \text{ RB \&} \\
 &D_2 \text{ FB} \\
 &\therefore R_{AB} = 36 \Omega + 18 \Omega \\
 &\quad = 54 \Omega
 \end{aligned}$$

11. Ans: -4 (No range)

Sol:

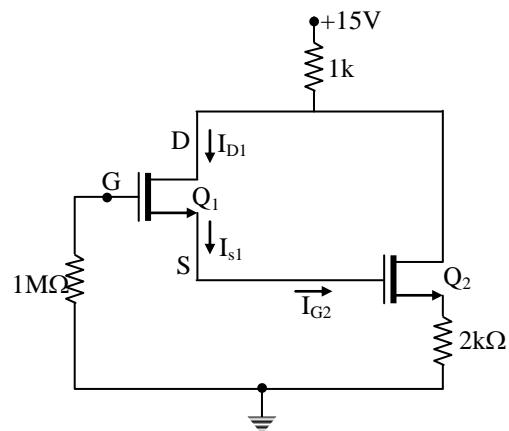



Step(1): From the circuit,

$$I_{S1} = I_{G2} = 0 \quad (1) \quad [\because I_G = 0 \text{ in MOSFETs}]$$

$$\Rightarrow I_{D1} = I_{S1} = 0 \quad (2) \quad [\because I_D = I_S \text{ in MOSFETs}]$$


Step(2): Consider the transfer characteristics of a DMOSFET

$$\text{Case (i): } I_D = I_{DSS} \text{ at } V_{GS} = 0 \quad (3)$$

$$\text{Case (ii): } I_D = 0 \text{ at } V_{GS} = V_P \quad (4)$$

$$\Rightarrow V_{GSQ1} = V_P = -4V \quad (5)$$
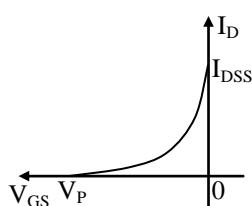
$$\therefore I_{D1} = 0 \text{ in the ckt given}$$




12. Ans: (b)

Sol: MOD-n ring counter is designed by using 'n' flipflops.

MOD-2n Johnson counter is designed by using 'n' flipflops.

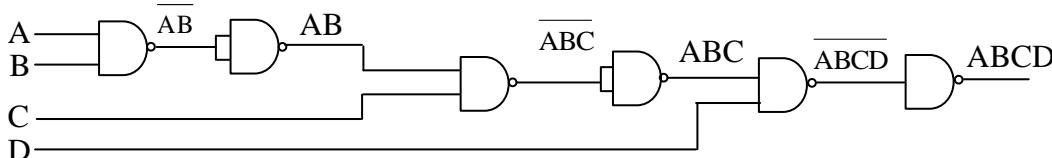15. Ans: 6 (No range)

$$\overline{\overline{Y}} = ABCD = \overline{A} \overline{B} \overline{C} \overline{D}$$



\therefore 6 NAND gates are required.

16. Ans: (a)

$$\text{Sol: } |\text{adj A}| = |A|^{n-1}$$

$$\Rightarrow 1(12 - 12) - 11(4 - 6) + 3(4 - 6) = |A|^2$$

$$\Rightarrow 22 - 6 = |A|^2$$

$$\therefore |A| = \pm 4$$

So, MOD-8 ring counter requires 8 flipflops and MOD-8 Johnson counter requires 4 flipflops.

13. Ans: 8.33 (Range: 8 to 8.6)

Sol: According to the concept of virtual ground

$$V_1 = V_2$$

$$\Rightarrow 5V = \frac{30kV_0}{30k + 20k}$$

$$\therefore V_0 = \frac{5V \times 50k}{30k} = 8.33V$$

14. Ans: 54.4 (54.2 to 54.6)

Sol: Given $B = 4000 \text{ Hz}$, $S = 0.1 \times 10^{-3} \text{ W}$
 $N = 10^{-12} \times 2 \times 4000 = 8 \times 10^{-9} \text{ W}$

$$\frac{S}{N} = 1.25 \times 10^4$$

$$C = B \log_2 [1 + \frac{S}{N}]$$

$$\begin{aligned} C &= 4000 \log_2 [1 + 1.25 \times 10^4] \\ &= 54.4 \times 10^3 \text{ bps} \\ &= 54.4 \text{ kbps} \end{aligned}$$

17. Ans: 55 (Range: 54.90 to 55)

$$\text{Sol: Compensator } D(s) = \frac{0.4s + 1}{0.04s + 1} = \frac{1 + aTs}{1 + Ts}$$

$$aT = 0.4$$

$$T = 0.04$$

$$\therefore a = 10$$

Maximum phase angle,

$$\phi_m = \sin^{-1} \left(\frac{a-1}{a+1} \right) = 55^\circ$$



18. Ans: (c)

Sol: Given $y(n) - \frac{1}{4}y(n-1) = x(n)$

Apply z transform

$$Y(z) - \frac{1}{4}z^{-1}Y(z) = X(z)$$

$$Y(z) = \frac{X(z)}{1 - \frac{1}{4}z^{-1}}$$

$$x(n) = \delta(n-1)$$

$$X(z) = z^{-1}$$

$$Y(z) = \frac{z^{-1}}{1 - \frac{1}{4}z^{-1}}$$

Apply inverse z transform

$$\left(\frac{1}{4}\right)^n u(n) \leftrightarrow \frac{1}{1 - \frac{1}{4}z^{-1}}$$

From time shifting property

$$\left(\frac{1}{4}\right)^{n-1} u(n-1) \leftrightarrow \frac{z^{-1}}{1 - \frac{1}{4}z^{-1}}$$

$$\text{So, } y(n) = \left(\frac{1}{4}\right)^{n-1} u(n-1)$$

19. Ans: 4 (no range)

Sol: $\frac{1}{T_s} = 8000$

$$\text{So, } T_s = 125\mu\text{sec}$$

The separation between samples is $5\mu\text{sec}$
As the sample is represented by a pulse of $1\mu\text{sec}$ duration. The separation between two successive pulses is $4\mu\text{sec}$.

20. Ans: (d)

Sol: $(1+t)\frac{dy}{dt} = 4y$

$$\int \frac{1}{y} dy = \int \frac{4}{1+t} dt$$

$$\log y = 4 \log(1+t) + \log(c)$$

$$y = c(1+t)^4$$

$$y(0) = 1 \Rightarrow 1 = c(1+0)^4 \Rightarrow c = 1$$

$$\Rightarrow y = (1+t)^4$$

21. Ans: (c)

Sol: $H_1(z) = \frac{z^2 + 1.5z - 1}{z^2}$ and

$$H_2(z) = z^2 + 1.5z - 1$$


\therefore The zeros of the functions will be identical but not the poles.

22. Ans: (d)

Sol: $\frac{E}{R} = \frac{1}{1 - \left[-\frac{4}{s+1} - \frac{4}{s+1} \right]} = \frac{s+1}{s+9}$

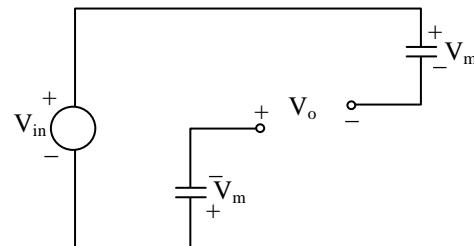23. Ans: (d)

Sol: During positive cycle D_3 is FB, D_4 is RB.
Hence C_1 gets charged to V_m
During Negative cycle D_1 is FB, D_2 is RB.
Hence C_2 gets charged to $-V_m$
After the capacitors are charged, the diodes will remain reverse biased



KVL

$$-V_{in} + V_m - V_o - V_m = 0$$

$$V_o = -V_{in}$$

24. Ans: 1 (No range)

Sol: If rank of A is 2, then $|A| = 0$

$$\Rightarrow x^3 - 1$$

$$(x-1)(x^2 + x + 1) = 0$$

$$\Rightarrow x = 1, \frac{-1 \pm \sqrt{3}i}{2}$$

$$\therefore x = 1$$



25. Ans: (b)

Sol: $\bar{E} = \cos(\omega t + \beta z)\hat{a}_x + \sin(\omega t + \beta z)\hat{a}_y$

Phase difference = 90°

And amplitude of both components are equal

\therefore Circularly polarized.


Let $Z = 0$

$$\bar{E} = \cos(\omega t)\hat{a}_x + \sin(\omega t)\hat{a}_y$$

$$\omega t = 0 \Rightarrow \bar{E} = \hat{a}_x$$

$$\omega t = 90^\circ \Rightarrow \bar{E} = \hat{a}_y$$

\therefore Anti-Clockwise direction

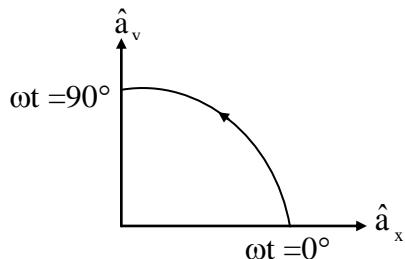

\Rightarrow left circularly polarized.

26. Ans: (d)

Sol: Given curve 'C' is a closed curve.

So, we have to evaluate the integral by using Green's theorem.

By Green's theorem, we have

$$\oint_C (M dx + N dy) = \iint_R \left(\frac{\partial N}{\partial x} - \frac{\partial M}{\partial y} \right) dx dy$$

$$\text{Now, } \oint_C [(x-y)dx + (x+3y)dy]$$

$$= \iint_R \left[\frac{\partial}{\partial x} [x+3y] - \frac{\partial}{\partial y} [x-y] \right] dx dy$$

$$= \iint_R [1 - (-1)] dx dy$$

$$= 2 \iint_R 1 dx dy$$


= 2(Area of the circle 'C')

$$= 2(\pi r^2)_{r=4}$$

$$= 32\pi$$

27. Ans: (c)


Sol:

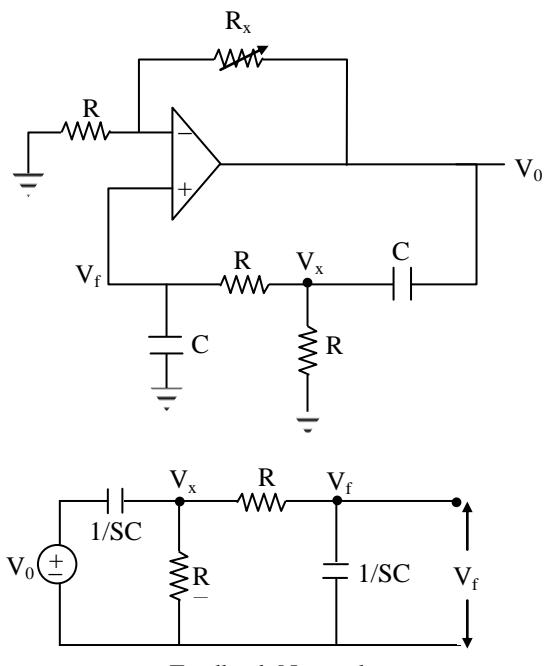

$$\frac{V_0 - V_x}{\frac{1}{SC}} = \frac{V_x}{R} + \frac{V_x - V_f}{R} \quad \dots\dots (1)$$

$$\text{and } \frac{V_x - V_f}{R} = \frac{V_f}{\frac{1}{SC}} \quad \dots\dots (2)$$
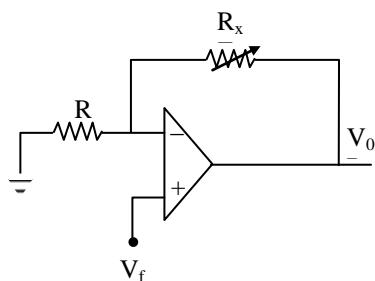
$$\therefore V_x = (1 + SRC) V_f \quad \dots\dots (3)$$





$$\Rightarrow \beta = \frac{V_f}{V_0} = \frac{\text{SCR}}{S^2 C^2 R^2 + 3\text{SCR} + 1}$$

[\because from equation (1), (2) & (3)]

$$\therefore \beta = \frac{1}{3 + j \left[\omega CR - \frac{1}{\omega CR} \right]}$$

$$\frac{V_0}{V_f} = 1 + \frac{R_x}{R}$$

Since for sustained oscillations $\beta A = 1$

$$\Rightarrow A = \frac{1}{\beta}$$

$$\therefore 1 + \frac{R_x}{R} = 3 + j \left[\omega CR - \frac{1}{\omega CR} \right]$$

Equating img., parts

$$\Rightarrow \omega CR - \frac{1}{\omega CR} = 0$$

$$\Rightarrow f = \frac{1}{2\pi RC} \text{ Hz}$$

$$\& 1 + \frac{R_x}{R} = 3$$

$$\therefore R_x = 2R$$

28. Ans: 4.5 (No range)

Sol: Given $f = 250\text{MHz}$

Beam area Ω_A = product of half power widths

$$D = \frac{4\pi}{\Omega_A} = \frac{41259}{30^\circ \times 35^\circ} = 39.29$$

$$D = \frac{4\pi}{\lambda^2} A_e$$

(or)

$$A_e = \frac{\lambda^2}{4\pi} D$$

$$\lambda = \frac{3 \times 10^8}{250 \times 10^6}$$

$$\lambda = 1.2\text{m}$$

$$A_e = \frac{(1.2)^2}{(4\pi)} \times (39.29)$$

$$\therefore A_e \simeq 4.5\text{m}^2$$

29. Ans: 0.2

Sol: Given that $\frac{dy}{dx} = x^3 - 2y$ ($\because \frac{dy}{dx} = f(x, y)$)

$$\text{with } y(0) = 0.25 \quad (\because y(x_0) = y_0)$$

$$\text{Let } x_0 = 0, y_0 = 0.25 \text{ & } h = 0.1$$

$$\text{Then } x_1 = x_0 + h = 0.1$$

The formula for Euler's forward method is

$$y(x_1) \simeq y_1 = y_0 + h f(x_0, y_0)$$

$$\Rightarrow y(0.1) \simeq y_1 = 0.25 + (0.1) (x_0^3 - 2y_0)$$

$$\Rightarrow y(0.1) \simeq y_1 = 0.25 + (0.1) [0 - 2(0.25)]$$


$$\therefore y(0.1) \simeq y_1 = 0.25 - (0.1)(0.5)$$

$$= 0.25 - 0.05$$

$$= 0.2$$


30. Ans: (b)

Sol:

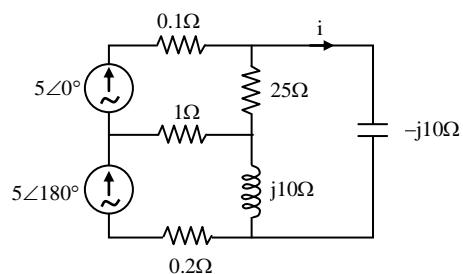


By super position principle $i = i_1 + i_{11}$

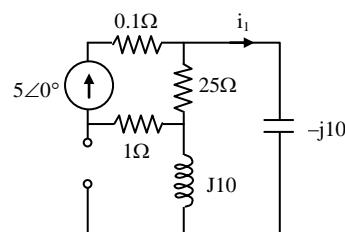Current i_1 : $5\angle 0^\circ$ source acting alone





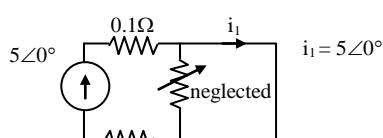
$$-j10 + j10 = 0 \Omega \text{ (short circuit)}$$



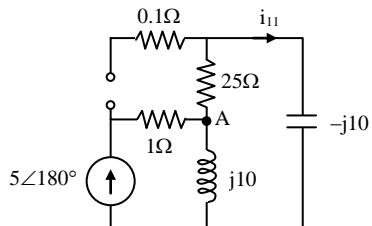Current i_{11} : $5\angle 180^\circ$ source acting alone



By current division rule at node A

$$\begin{aligned} i_{11} &= 5\angle 180^\circ \times \frac{j10}{25 + j10 - j10} \\ &= 2j\angle 180^\circ \\ &= -2j \end{aligned}$$


$$\therefore I = i_1 + i_{11} = 5 - 2j \text{ A}$$

31. Ans: 31.6 (Range: 31 to 32)

$$\begin{aligned} \text{Sol: } P_e &= Q \left[\sqrt{\frac{2A^2 T_b}{N_0}} \right] = 7.8 \times 10^{-4} \\ \sqrt{\frac{2A^2 T_b}{N_0}} &= \sqrt{10} \\ A^2 &= \frac{5 \times 2 \times 10^{-9}}{10^{-5}} = 10^{-3} \\ A &= 31.6 \times 10^{-3} \text{ V} = 31.6 \text{ mV} \end{aligned}$$

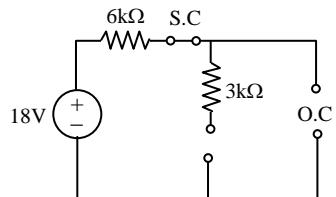32. Ans: -60 (No Range)

Sol: At time $t = 0^-$ switch is in open condition



So, L is short circuit, C is open circuit

$$i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 18 \text{ V}$$

At $t = 0^+$ switch is closed

$$\begin{aligned} I_C(0^+) &= C \frac{dv(0^+)}{dt} \\ \frac{dv(0^+)}{dt} &= \frac{i_C(0^+)}{C} \\ i_C(0^+) &= -6 \times 10^{-3} \text{ A} \end{aligned}$$

$$\begin{aligned} \frac{dv(0^+)}{dt} &= \frac{-6 \times 10^{-3}}{100 \times 10^{-6}} \\ \frac{dv(0^+)}{dt} &= -60 \text{ V/sec} \end{aligned}$$

33. Ans: 16 (Range: 15.9 to 16.2)

$$\text{Sol: } G(s) H(s) = \frac{10}{(s+2)^4}$$

$$\angle G(j\omega) H(j\omega) = \angle \frac{10}{(j\omega+2)^4}$$

$$\text{Gain margin(GM)} = 20 \log \frac{1}{|G(j\omega)H(j\omega)|_{\omega=\omega_{pc}}}$$

$$\angle G(j\omega) H(j\omega) \Big|_{\omega=\omega_{pc}} = -180^\circ$$

$$\angle \frac{10}{(j\omega+2)^4} \Big|_{\omega=\omega_{pc}} = -180^\circ$$

$$-4 \tan^{-1} \frac{\omega_{pc}}{2} = -180^\circ$$

$$\Rightarrow \omega_{pc} = 2$$

$$\begin{aligned} |G(j\omega)H(j\omega)|_{\omega=\omega_{pc}} &= \left| \frac{10}{(j(2)+2)^4} \right| \\ &= \frac{10}{(\sqrt{2^2+2^2})^4} = \frac{10}{64} \end{aligned}$$

$$\text{Gain margin} = 20 \log \frac{64}{10}$$

$$= 20[\log 64 - \log 10]$$

$$= 20 [6(0.3) - 1]$$

$$= 16 \text{ (Range: 15.9 to 16.2)}$$



34. Ans: 1.69 (Range: 1.45 to 1.85)

Sol: The value of K can be determined from the following equation:

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$

$$= \frac{10\text{mA}}{(10\text{V} - 1.5\text{V})^2} = 1.38 \times 10^{-1} \text{mA/V}^2$$

$$[\because V_{GS(on)} = 10\text{V}]$$

From the circuit, the source voltage is seen to be 0V.

$$\text{Therefore, } V_{GS} = V_G - V_S = V_G - 0 = V_G.$$

The value of V_G ($= V_{GS}$) is given by:

$$V_G (\text{or } V_{GS}) = \frac{V_{DD}}{R_1 + R_2} \times R_2$$

$$= \frac{10\text{V}}{(1+1)\text{M}\Omega} \times 1\text{M}\Omega = 5\text{V}$$

$$I_D = K (V_{GS} - V_{GS(th)})^2$$

$$= (1.38 \times 10^{-1} \text{mA/V}^2) (5\text{V} - 1.5\text{V})^2$$

$$= 1.69\text{mA}$$

35. Ans: 0.0045 (Range: 0.004 to 0.005)

Sol: Let X = number of accidents between 5 P.M and 6 P.M.

For Poisson distribution,

$$\lambda = np = (1000)(0.0001) = 0.1$$

$$P(X=x) = \frac{e^{-\lambda} \lambda^x}{x!} \quad (x = 0, 1, 2, \dots)$$

Required Probability = $P(X \geq 2)$

$$= 1 - P(X < 2)$$


$$= 1 - \{P(X = 0) + P(X = 1)\}$$

$$= 1 - e^{-0.1} (1 + 0.1)$$

$$= 0.0045$$

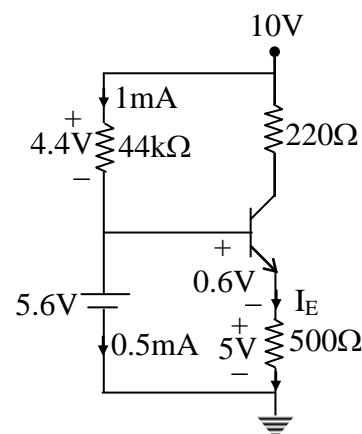36. Ans: 0.95 (No range)

Sol: Zener diode is in breakdown, replace it with a voltage source of value $V_Z = 5.6\text{V}$ & $V_{BE} = 0.6\text{V}$



Applying KCL at Base, we get

$$-1\text{mA} + 0.5\text{mA} + I_B = 0$$

$$I_B = 0.5\text{mA}$$

$$I_E = \frac{5}{500\Omega} = 10\text{mA}$$

$$I_E = (\beta + 1) I_B$$

$$\beta + 1 = \frac{I_E}{I_B}$$

$$\beta + 1 = \frac{10}{0.5}$$

$$\beta + 1 = 20$$


$$\beta = 19$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{19}{20} = 0.95$$

37. Ans: 171 (Range: 165 to 175)

Sol: Now 1V is applied at primary side a-a'

$$R = \frac{1}{i}$$

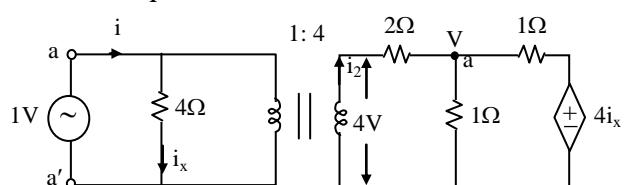

By transformation ratio

$$K = \frac{4}{1} = 4$$

$$\frac{V_2}{V_1} = k = 4$$



$$V_2 = 4V$$

$$i_x = \frac{1}{4}A$$

Apply KCL at node-a,

$$\frac{V-4}{2} + \frac{V}{1} + \frac{V-4i_x}{1} = 0$$

$$V - 4 + 2V + 2V - 8i_x = 0$$

$$5V = 4 + 8i_x = 4 + 8 \frac{1}{4} = 6$$

$$V = \frac{6}{5}V$$

i_2 is current flows through secondary winding then

$$i_2 = \frac{4 - \frac{6}{5}}{2} = \frac{14}{10} = 1.4A$$


This i_2 transferred to primary then $i'_2 = 1.4 \times 4$

$$\therefore i = i_x + i'_2 = \frac{1}{4} + 1.4 \times 4 = 5.85 A$$

$$\therefore R = \frac{1}{i} = \frac{1}{5.85} = 171 m\Omega$$

38. 4.92 (Range: 4.8 to 5.1)

Sol:

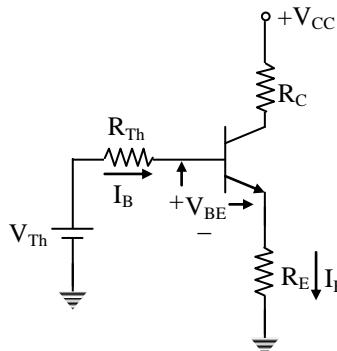

fig(a): Thevenin equivalent of the given circuit

Step (1):

KVL for the input loop of circuit shown in fig (a)

$$V_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0 \quad \text{----- (1)}$$

$$I_E = \frac{V_{Th} - V_{BE}}{R_E + \frac{R_{Th}}{1+\beta}} \quad \text{---- (2) } [\because I_B = \frac{I_E}{1+\beta}]$$

$$V_{Th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_{Th} = R_1 // R_2$$

Step (2):

$$\text{But } I_E R_E = \frac{V_{CC}}{3} = \left[\frac{V_{Th} - V_{BE}}{R_E + \frac{R_{Th}}{1+\beta}} \right] R_E \quad \text{---- (3)}$$

(\because Given that voltage drop across $R_E = \frac{V_{CC}}{3}$)

$$\left\{ \frac{(V_{Th} - V_{BE})}{R_E \left[1 + \left(\frac{R_{Th}}{R_E} \right) \left(\frac{1}{1+\beta} \right) \right]} \right\} R_E = \frac{V_{CC}}{3} \quad \text{---- (4)}$$

$$V_{Th} = \frac{V_{CC}}{3} \left[1 + \left(5.73 \times \frac{1}{101} \right) \right] + V_{BE} \quad \text{---- (5)}$$

$$V_{Th} = 4.92693V \quad \text{----- (6)}$$

39. Ans: (b)

Sol: Given $v = y + e^{-x} \cos y$

$$\Rightarrow v_x = -e^{-x} \cos(y) \text{ and } v_y = 1 - e^{-x} \sin(y)$$

$$\text{Consider } du = (u_x) dx + (u_y) dy$$

$$= (v_y) dx + (-v_x) dy$$

$$\Rightarrow du = (1 - e^{-x} \sin y) dx + (e^{-x} \cos y) dy$$

$$\Rightarrow \int du = \int (1 - e^{-x} \sin y) dx + \int 0 dy + k$$

$$\Rightarrow u = x + e^{-x} \sin y + k$$

Now the required analytic function $f(z)$ is given by $f(z) = u + iv$

$$\Rightarrow f(z) = (x + e^{-x} \sin y + k)$$

$$+ i (y + e^{-x} \cos y)$$

$$\therefore f(z) = z + ie^{-z} + k$$



40. Ans: (b)

Sol: For break point,

$$\frac{dk}{ds} = 0$$

$$\frac{d}{ds} \left(\frac{1}{G(s)H(s)} \right) = 0$$

$$\frac{d}{ds} (s(s+6)(s^2+4s+13)) = 0$$

$$(s^2+6s)[2s+4] + (s^2+4s+13)[2s+6] = 0$$

$$2s^3+16s^2+24s+2s^3+6s^2+8s^2+24s+26s+78 = 0$$

$$4s^3 + 30s^2 + 74s + 78 = 0$$

$$f(s) = 2s^3 + 15s^2 + 37s + 39 = 0 \quad \dots\dots\dots(1)$$

$$f(-5) = -21$$

$$f(-4) = 3$$

$$f(-3) = 9$$

As there is a sign change in between $-5, -4$, one root is on real axis, which is in between $-5, -4$. Three real axis break points is not possible.

41. Ans: (b)

$$\text{Sol: } f(t) = \left(-\frac{t}{T} + 1 \right) [u(t) - u(t-T)]$$

$$f(t) = \left(-\frac{t}{T} \right) [u(t) - u(t-T)] + [u(t) - u(t-T)]$$

$$[u(t) - u(t-T)] \leftrightarrow \frac{1}{s} - \frac{e^{-sT}}{s}$$

From differentiation in s-domain property

$$\left(-\frac{t}{T} \right) [u(t) - u(t-T)] \leftrightarrow \frac{1}{T} \frac{d}{ds} \left(\frac{1}{s} - \frac{e^{-sT}}{s} \right) = \frac{1}{T} \left[\frac{-1}{s^2} - \frac{(se^{-sT}(-T) - e^{-sT})}{s^2} \right]$$

$$\left(-\frac{t}{T} \right) [u(t) - u(t-T)] \leftrightarrow \frac{1}{T} \left[\frac{-1}{s^2} + T \frac{e^{-sT}}{s} + \frac{e^{-sT}}{s^2} \right] = \frac{e^{-sT}}{s} + \frac{e^{-sT}}{Ts^2} - \frac{1}{s^2 T}$$

$$F(s) = \frac{1}{s} - \frac{e^{-sT}}{s} + \frac{e^{-sT}}{s} + \frac{e^{-sT}}{Ts^2} - \frac{1}{s^2 T} = \frac{1}{s} + \frac{e^{-sT}}{Ts^2} - \frac{1}{s^2 T} = \frac{1}{s^2 T} [sT - 1 + e^{-sT}]$$

42. Ans: 3 (No range)

$$\text{Sol: } J_0 = \bar{Q}_1; K_0 = 1; J_1 = Q_0; K_1 = 1$$

J ₀	K ₀	J ₁	K ₁	Q ₀ Q ₁
				0 0
1	1	0	1	1 0
1	1	1	1	0 1
0	1	0	1	0 0
1	1	0	1	1 0

→ It is a mod-3 counter.

43. Ans: 0.707 (Range: 0.70 to 0.80)

Sol: Propagation constant

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{(30 + j2\pi \times 10^3 \times 100 \times 10^{-3})(j2\pi \times 10^3 \times 20 \times 10^{-6})}$$

$$= \sqrt{(30 + j200\pi)(j0.04\pi)}$$

$$= \sqrt{(-78.95 + j3.76)}$$

$$\gamma = 8.889 \angle 88.63^\circ$$

$$\gamma = \alpha + j\beta = [0.212 + j8.887] \text{ km}^{-1}$$

$$\beta = 8.887 \text{ rad/km}$$

$$\text{Phase velocity, } v_p = \frac{\omega}{\beta}$$



$$= \frac{2\pi \times 10^3}{(8.887)} \cdot \frac{10^3}{10^3}$$

$$v_p = 0.707 \times 10^6$$


$$\therefore v_p = 0.707 \text{ Mm/sec}$$

44. Ans: (c)

Sol: By giving different sets of input values and $Q(t)$ (present state) we have to determine next state $Q(t+1)$

X	Y	$Q(t)$	S	R	$Q(t+1)$
0	0	0	1	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	1	1	x
1	1	1	1	1	x

K-map for $Q(t+1)$

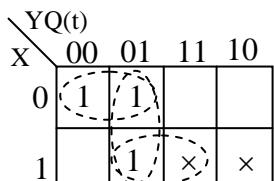

$$\therefore Q(t+1) = \bar{X} \bar{Y} + \bar{Y} Q(t) \quad \text{or}$$

$$Q(t+1) = \bar{X} \bar{Y} + XQ(t)$$

45. Ans: 0.5

Sol: Given $y(n)$ be a 4 point circular convolution of $x(n)$ & $h(n)$

$$y(n) = x(n) \text{ circular convolution } h(n)$$

Apply DFT

$$Y(k) = X(k) H(k)$$

$$Y(k) = \{1, -2, 1, -2\} \cdot \{1, j, 1, -j\}$$

$$= \{1, -2j, 1, 2j\}$$

$$\text{IDFT } y(n) = \frac{1}{N} \sum_{k=0}^{N-1} Y(k) e^{\frac{j2\pi n k}{N}}$$


$$y(0) = \frac{1}{N} \sum_{k=0}^{N-1} Y(k)$$

$$N = 4$$


$$y(0) = \frac{1}{4} \sum_{k=0}^3 Y(k) = \frac{1}{4} [1 - 2j + 1 + 2j] = \frac{2}{4} = \frac{1}{2}$$

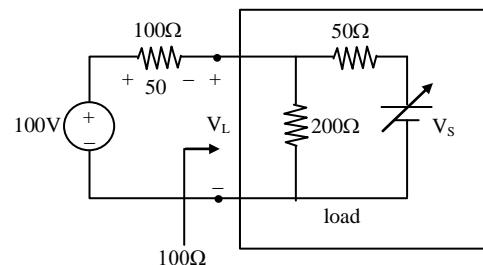46. Ans: 37.5 (Range: 37 to 38)

Sol: Applying thevenin's theorem in the source side, the circuit can be redrawn as



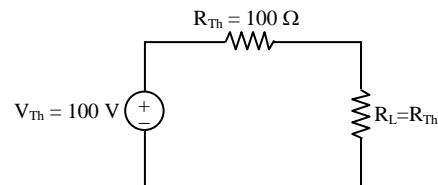We know that for maximum power transform, the load resistance is equal to Thevenin's resistance.



$$\text{Voltage drop across load, } V_L = \frac{V_{Th} \times R_L}{R_{Th} + R_L}$$

$$\Rightarrow V_L = \frac{V_{Th} \times R_L}{2R_{Th}}$$

$$V_L = \frac{V_{Th}}{2}$$

Consider above figure, for maximum power transferred to load



$$V_L = \frac{V_{TH}}{2} = \frac{100}{2} = 50 \text{ Volts}$$

Applying nodal analysis, we get

$$\Rightarrow \frac{50}{100} = \frac{50}{200} + \frac{50 - V_s}{50}$$

$$\Rightarrow \frac{50 - V_s}{50} = \frac{1}{4}$$

$$\Rightarrow 50 - V_s = 12.5$$

$$\Rightarrow V_s = 37.5 \text{ V}$$

47. Ans: (c)

Sol: $A_c \cos 2\pi f_c t + \frac{A_c \mu}{2} \cos 2\pi(f_c + f_m)t + \frac{A_c \mu}{2} \cos 2\pi(f_c - f_m)t$

USB is attenuated by a factor of '2'

$$= A_c \cos 2\pi f_c t + \frac{A_c \mu}{4} \cos 2\pi(f_c + f_m)t + \frac{A_c \mu}{2} \cos 2\pi(f_c - f_m)t$$

$$= \cos 2\pi f_c t + \frac{1}{8} \cos 2\pi(f_c + f_m)t + \frac{1}{4} \cos 2\pi(f_c - f_m)t$$

The inphase component is

$$\left[1 + \frac{1}{8} \cos 2\pi f_m t + \frac{1}{4} \cos 2\pi f_m t \right] \cos 2\pi f_c t = \left[1 + \frac{3}{8} \cos 2\pi f_m t \right]$$

48. Ans: (b)

Sol: • (SP) = 8086H

- (DE) = 8085H

- (HL) exchanged with (DE)

After execution

$$(HL) = 8085H, (DE) = \times \times \times H$$

- (HL) = 8085H = 1000 0000 1000 0101

$$(SP) = 8086H = 1000 0000 1000 0110$$

$$(HL) = 010BH = 0000 0001 0000 1011$$

- 8085 microprocessor pushes DE pair contents to stack. SP contents will be decremented by 2 for PUSH operation.

$$(SP) = 010BH - 2 = 0109H$$

- 8085 microprocessor executes RST 7 software interrupt where it calls respective ISR and returns to main execution.

$$(SP) = 0109H - 2 + 2 = 0109H$$

- (HL) = 010BH copied into (SP)

$$\Rightarrow (SP) = 010BH$$

- 8085 microprocessor calls delay subroutine and after execution of subroutine, microprocessor returns to main program.

SP contents decremented by 2 for CALL operation

SP contents incremented by 2 for RETURN operation

$$\text{i.e., } (SP) = 010BH - 2 + 2 \\ = 010BH$$

- 8085 microprocessor contents of top 2 stack locations back into PSW. SP contents will be incremented by 2 for POP operation.

$$(SP) = 0109H + 2 = 010BH$$

- (SP) = 010BH




49. Ans: 2.19 (2.18 to 2.20)

Sol: Apply KCL at V_a

$$I_1 = I_2 + I_3$$
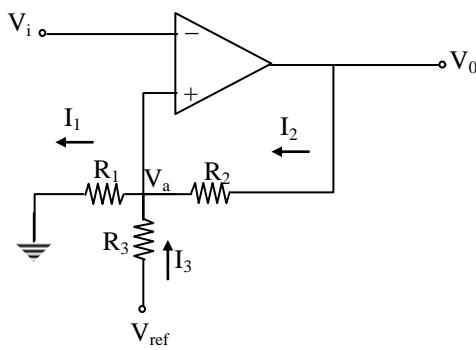
$$\frac{V_a}{R_1} = \frac{V_{ref} - V_a}{R_3} + \frac{V_0 - V_a}{R_2}$$



$$V_a \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_{ref}}{R_3} + \frac{V_0}{R_2}$$

$V_a = V_{UTP}$ when $V_0 = +V_{sat}$

$V_a = V_{LTP}$ when $V_0 = -V_{sat}$

$$V_a = \frac{\frac{V_{ref}}{R_3} + \frac{V_{sat}}{R_2}}{\left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]}$$

$$V_{UTP} = \frac{-10 + 12}{\frac{10}{10} + \frac{50}{50}} = -3.4545 \text{ V}$$

$V_{LTP} = -5.6363 \text{ V}$

$V_H = V_{UTP} - V_{LTP}$

$V_H \approx 2.19$

50. Ans: (d)

$$\text{Sol: } X(\omega) = \frac{1}{(2 + j\omega)^2}$$

$$H(\omega) = \frac{1}{4 + j\omega}$$

$$Y(\omega) = X(\omega) \cdot H(\omega) = \frac{1}{(4 + j\omega)(2 + j\omega)^2}$$

$$= \frac{1/4}{4 + j\omega} - \frac{1/4}{2 + j\omega} + \frac{1/2}{(2 + j\omega)^2}$$

$$y(t) = \frac{1}{4}e^{-4t}u(t) - \frac{1}{4}e^{-2t}u(t) + \frac{1}{2}te^{-2t}u(t)$$

$$y(3) = \frac{1}{4}e^{-12} - \frac{1}{4}e^{-6} + \frac{3}{2}e^{-6} = \frac{1}{4}e^{-12} + \frac{5}{4}e^{-6}$$

51. Ans: (a)

Sol: Given that $\beta = 1$

$$\text{loss tangent } \frac{\sigma}{\omega \in} = \tan[2 \text{phase} \eta]$$

$$= \tan(60)$$

$$= \sqrt{3}$$

$$\frac{\alpha}{\beta} = \frac{\sqrt{\mu \in}}{2} \left(\sqrt{1 + \left(\frac{\sigma}{\omega \in} \right)^2} - 1 \right)^{1/2}$$

$$\frac{\alpha}{\beta} = \frac{\sqrt{\mu \in}}{2} \left(\sqrt{1 + \left(\frac{\sigma}{\omega \in} \right)^2} + 1 \right)^{1/2}$$



By solving this

$$\frac{\alpha}{\beta} = \frac{[2-1]^{1/2}}{[2+1]^{1/2}} = \frac{1}{\sqrt{3}}$$

$$\alpha = \frac{1}{\sqrt{3}} \quad [\because \beta = 1]$$

52. Ans: (d)

Sol:

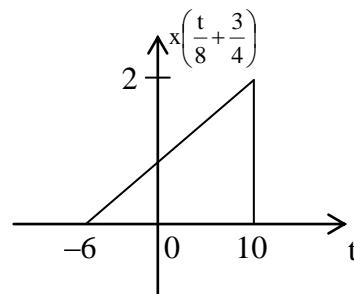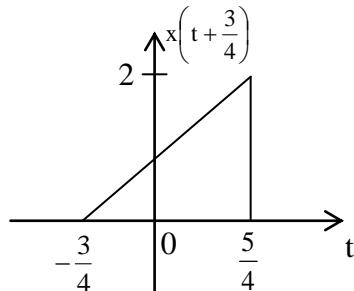



53. Ans: (a)

Sol: Given $(2xy - 9x^2)dx + (2y + x^2 + 1)dy = 0$
Here, $M = 2xy - 9x^2$ and $N = 2y + x^2 + 1$

$$\text{Now, } \frac{\partial M}{\partial y} = 2x = \frac{\partial N}{\partial x}$$

∴ The given D.E is exact

Now the general solution of the given D.E is
 $\int(2xy - 9x^2)dx + \int(2y + 0 + 1)dy = C$

$$\Rightarrow x^2y - 9\frac{x^3}{3} + y^2 + y = C \dots\dots\dots (1)$$

but $y = -3$ at $x = 0$

Now (1) becomes

$$0 - 0 + 9 - 3 = C$$

$$\Rightarrow C = 6$$

∴ The solution of a given D.E is

$$x^2y - 3x^3 + y^2 + y = 6$$

54. Ans: 31 (No range)

Sol: $P = \text{Signal power}$

$$= E[x^2(t)] = 2 \int_0^1 x^2(-x+1)dx = \frac{1}{6}W$$

$$\text{Figure of merit} = \frac{\frac{1}{6}}{1 + \frac{1}{6}} = \frac{1}{7}$$

$$\left(\frac{S}{N}\right)_o = 40 \text{ dB}$$

$$\frac{S_i}{n_i} = 7 \times 10^4$$

$$S_i = 7 \times 10^4 \times 2 \times 10^{-12} \times 4 \times 10^3$$

$$= \frac{A_c^2}{2} [1 + K_a^2 P]$$

$$K_a = \mu / A_m = 1$$

$$A_c = 31 \text{ mV}$$

55. Ans: 0 (No range)

Sol: $\delta(t^2 - a^2) = \frac{1}{2|a|} [\delta(t+a) + \delta(t-a)]$

$$I = \int_{-1}^1 \frac{1}{4} [\delta(t-2) + \delta(t+2)] dt$$

$$I = \frac{1}{4} \int_{-1}^1 \delta(t-2) dt + \frac{1}{4} \int_{-1}^1 \delta(t+2) dt$$

From sifting property

$$\int_{t_1}^{t_2} x(t) \delta(t - t_0) dt = x(t_0) \quad t_1 \leq t_0 \leq t_2 \\ = 0 \quad \text{otherwise}$$

$$I = 0 + 0 = 0$$

56. Ans: (d)

Sol: (PART AND THE WHOLE) A fragment is a piece of broken bone; a shard is a piece of broken pottery. (d)

57. Ans: (a)

58. Ans: (d)

Sol: irretrievably means impossible to recover or get back, so irrevocably is the correct synonym, which means not capable of being changed : impossible to revoke.

59. Ans: (b)

Sol: Indiscriminate (adj.) means not discriminating or choosing randomly; haphazard; without distinction.

60. Ans: (a)

Sol: $a_0 = 1; a_n = 2a_{n-1}$ if n is odd

$a_n = a_{n-1}$ if n is even

$$a_{100} = a_{100-1} = a_{99} = 2.a_{99-1}$$

$$= 2.a_{99} = 2.a_{98-1} = 2a_{97}$$

$$= 2.2a_{97-1} = 2^2.a_{96} \dots\dots\dots 2_{50}.a_0 = 2^{50}$$



61. Ans: (c)

Sol: $A = 1; B = 1$

(a) $B = B + 1 = 2$

(b) & (c) $A = A \times B = 1 \times 2 = 2$

Step 2: $B = 2 + 1 = 3; A = A \times B = 2 \times 3 = 6$

Step 3: $B = 3 + 1 = 4; A = A \times B = 6 \times 4 = 24$

Step 4: $B = 4 + 1 = 5; A = 24 \times 5 = 120$

Step 5: $B = 5 + 1 = 6; A = 120 \times 6 = 720$

62. Ans: (a)

Sol: Ratio of efficiency ($P & Q$) = $2 : 1$

Ratio of efficiency ($P + Q, R$) = $3 : 1$

If R does 1 unit work, then $P & Q$ together do 3 units.

Out of 3 units, P does 2 units and Q does 1 unit.

∴ Ratio of efficiency ($P, Q & R$) = $2 : 1 : 1$

Hence, earnings should be divided in the ratio is $2 : 1 : 1$

63. Ans: (c)

Sol: In 1972, A was as old as the number formed by the last two digits of his year of birth.
So, A was born in 1936 (as in 1972, he is 36 yrs older also, last two digits of 1936 are 36).

Hence, B was born in $1936 + 15 = 1951$ so, he is 21 yrs old in 1972

64. Ans: (b)

Sol: Difference (in thousands) between the numbers of customers in the 2 complexes in:

January: $22 - 20 = 2$

February: $25 - 24 = 1$

March: $20 - 15 = 5$

April: $28 - 25 = 3$

May: $20 - 14 = 6$ [Max]

June: $20 - 15 = 5$

65. Ans: (b)

Sol: The issue is more about punishing criminals, and so punishment is more important than crime prevention (correct answer B).