



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Branch: Electrical Engineering Mock-D - Solutions

GATE-2020 General Aptitude (GA)

01. Ans: (B)

Sol: (so) is wrong because they mean the same.

02. Ans: (C) 03. Ans: (A)

04. Ans: (D)

Sol: Capacity of the tank = $(12 \times 13.5) = 162$ litres

Capacity of each bucket = 9 litres.

Number of buckets needed = $162/9 = 18$

05. Ans: (D)

Sol: Volume of Cuboid = length \times breadth \times height

Number of cuboids

$$= \frac{(\text{Volume of cuboids}) \text{ formed from}}{(\text{Volume of cuboids}) \text{ taken}}$$

$$\frac{18 \times 15 \times 12}{5 \times 3 \times 2} = 108$$

06. Ans: (B)

Sol: **At the most case:** Let the numbers be $\{-45, 1, 1, 1, \dots, 1\}$.

Average is 0. So, at the most 44 numbers may be > 0 .

At the least case: Let the numbers be $\{45, -1, -1, -1, \dots, -1\}$.

Average is 0. So, at the least 1 number may be > 0 .

07. Ans: (B)

Sol: Perimeter = Distance covered in 8 min. =

$$12000 \times \frac{8}{60} \text{ m} = 1600 \text{ m.}$$

Let length = $3x$ metres and breadth = $2x$ metres.

Then, $2(3x + 2x) = 1600$ or $x = 160$.

\therefore Length = 480 m and Breadth = 320 m

$$\therefore \text{Area} = (480 \times 320) \text{ m}^2 = 153600 \text{ m}^2$$

08. Ans: B

Sol: Consider CP as 100%.

Loss 15% \Rightarrow So, SP = 85%

Gain 15 % \Rightarrow So, New SP = 115%

Given $115\% - 85\% = 30\% = 450$

$$\frac{100}{30} \times 450 = 1500$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



48 ALL INDIA 1st RANKS IN GATE **15** ALL INDIA 1st RANKS IN ESE

ESE - MAINS

Classes Start from:

13th FEB 2020



(@ DELHI)

(@ HYDERABAD)



**Students who Qualify in Prelims
can avail 100 % Fee Waiver**

ESE-2018, 2019 Prelims Qualified Students are also eligible

for more details Contact: **040-23234418/19/20**, Email: hyderabad@aceenggacademy.com

www.aceenggacademy.com

HYDERABAD | AHMEDABAD | DELHI | PUNE | BHUBANESWAR | LUCKNOW | KOLKATA | VIJAYAWADA | VIZAG | TIRUPATI | CHENNAI | BENGALURU



COAL INDIA LIMITED (CIL)

Management Trainees

Online Test Series

6 Full Length Mock Tests

Civil | Electrical | Mechanical

Starts From 10th Jan 2020

All tests will be available till 28th February 2020

COAL INDIA

040 - 48539866 / 040 - 40136222

testseries@aceenggacademy.com

09. Ans: (A)

Sol: GDP at the beginning of 2013 is equal to the GDP at the end of 2012

$$\Rightarrow \text{GDP growth rate in 2012} = 7\%$$


GDP at the end of 2011 = GDP at the beginning of 2012 = \$1 trillion

\therefore GDP at the beginning of 2013 =

$$\frac{100+7}{100} \times 1 \text{ trillion} = \frac{107}{100} = \$1.07 \text{ trillion}$$

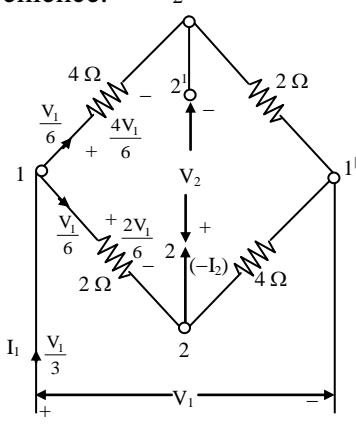10. Ans: (A)**Specialization (EE)****01. Ans: (C)**

Sol: The circuit is redrawn as a planar circuit for convenience.



$$\text{We have } V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

With port 2 open; between 1 & 1' there is a 6 Ω path (1– 2' –1') and another 6 Ω path (1–2–1').

\therefore Effective resistance between 1 and 1' = 3 Ω

$$I_1 = V_1/3$$


With port 2 open; $I_2 = 0$. Currents and voltage drops across different resistors are shown in above figure.

$$\text{By KVL; } \frac{4V_1}{6} = \frac{2V_1}{6} + V_2$$

$$V_2 = \frac{V_1}{3} \quad \left. \frac{V_1}{V_2} \right|_{I_2=0} = A = 3$$

$$\text{Also, } \left. \frac{I_1}{V_2} \right|_{I_2=0} = C = \frac{\frac{V_1}{3}}{\frac{V_1}{3}} = 1 \Omega$$

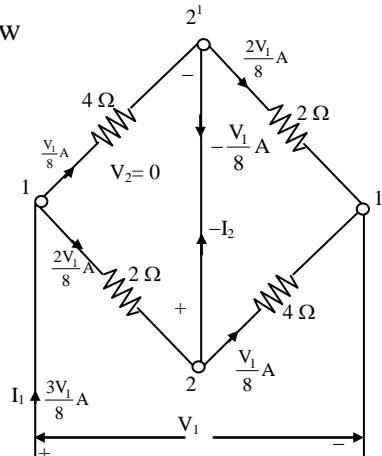With port 2 shorted, the figure is redrawn below



Between 1 and 1'; we have $(4 \Omega // 2 \Omega)$ in series with $(4 \Omega // 2 \Omega) = \frac{8}{3} \Omega$

$$I_1 = \frac{3V_1}{8} \text{ A. From figure, where currents are}$$

$$\text{marked, } (-I_2) = \frac{V_1}{8} \text{ A}$$

$$B = \left. \frac{V_1}{(-I_2)} \right|_{V_2=0} = \frac{V_1}{\frac{V_1}{8}} = 8 \Omega$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{\frac{3V_1}{8}}{\left(\frac{V_1}{8} \right)} = 3$$

02. Ans: (B)

Sol: $\nabla \times \vec{A} = \frac{1}{r} \frac{\partial}{\partial \phi} (5r \sin \phi) \hat{a}_r - \frac{\partial}{\partial r} (5r \sin \phi) \hat{a}_\phi$

$$= 5 \cos \phi \hat{a}_r - 5 \sin \phi \hat{a}_\phi$$

At $(4, \pi, 0)$

$$\nabla \times \vec{A} = -5 \hat{a}_r$$

03. Ans: (A)

Sol: The efficiency at any load is given by,

$$\% \eta = \frac{n \times VA \cos \phi}{n \times VA \cos \phi + n^2 (P_{cu})_{F,L} + P_i} \times 100$$

Where n = Fraction of full load

$1\frac{1}{4}$ th of full load, $n = 1.25$ at power factor

$$\cos \phi = 1$$


$$\% \eta = \frac{1.25 \times 100 \times 10^3 \times 1}{1.25 \times 100 \times 10^3 \times 1 + (1.25)^2 \times 1000 + 1000} \times 100 \\ = 97.991\%$$

04. Ans: (D)

Sol: For $V_i < 4V$, the diode is ON and the output

$$V_0 = 4V$$

For $V_i > 4V$, the diode is OFF and the output $V_0 = V_i$

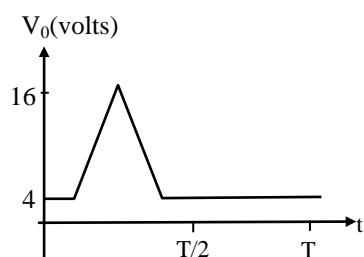**05. Ans: (A)**

Sol: For first wire, resistivity of conducting material is

$$\rho = \frac{RA}{l} = \frac{0.56 \times 2 \times 10^{-6}}{50} = 2.24 \times 10^{-8} \Omega \cdot m$$

∴ Cross-sectional area of second wire is

$$A = \frac{\rho l}{R} = \frac{(2.24 \times 10^{-8})(100)}{2} = 1.12 \times 10^{-6} m^2$$

$$\text{Diameter}(d) = 2\sqrt{\frac{A}{\pi}} = 2\sqrt{\frac{1.12 \times 10^{-6}}{\pi}} \\ = 1.19 \times 10^{-3} m \approx 1.2 mm$$

06. Ans: 2 no range

Sol: The probability density function of uniform distribution is

$$f(x) = \begin{cases} 1, & 0 < x < 1 \\ 0, & \text{otherwise} \end{cases}$$

$$E(y) = E[-2 \log_e x]$$

$$= \int_0^1 -2 \log_e x f(x) dx$$

$$= -2 \int_0^1 \log_e x dx$$

$$= -2 \{x \log_e x - x\} \Big|_0^1$$

$$= -2 \{(0-1) - (0)\} = 2$$

07. Ans: (C)

Sol: $\because \lim_{x \rightarrow 0} \frac{\tan(ax)}{x} = a$

$$\text{Now, } \lim_{x \rightarrow 0} \frac{\tan(4x)}{4x} = \frac{1}{4} \lim_{x \rightarrow 0} \frac{\tan(4x)}{x}$$

$$\therefore \lim_{x \rightarrow 0} \frac{\tan(4x)}{4x} = \frac{1}{4}(4) = 1$$

08. Ans: (B)**09. Ans: (C)**

Sol: Option (a):- Due to multiplication of input terms it is nonlinear, but it is TIV.

Option (b):- Due to multiplication of time variant term ($n - 2$) it is TV., but linear

Option (c) :- It is linear and TIV.

Option (d) :- $2^{x_1(n)+x_2(n)} \neq 2^{x_1(n)} + 2^{x_2(n)}$. So, nonlinear and TIV system

10. Ans: 0.0625 (no range)

$$\text{Sol: } G(z) = z^{-3} \cdot \frac{1}{1 - \frac{1}{4}z^{-1}}$$

$$\text{Let, } x(n) \leftrightarrow X(z) = \frac{1}{1 - \frac{1}{4}z^{-1}}$$

$$\therefore x(n) = \left(\frac{1}{4}\right)^n u(n)$$

By Time shifting property,

$$x(n-3) \xleftarrow{\text{ZT}} z^{-3}X(z)$$

$$\left(\frac{1}{4}\right)^{n-3} u(n-3) \xleftarrow{\text{Z.T.}} z^{-3} \cdot \frac{1}{1 - \frac{1}{4}z^{-1}} = G(z)$$

$$\therefore z^{-1}\{G(z)\} = g(n) = \left(\frac{1}{4}\right)^{n-3} u(n-3)$$

Put $n = 5$

$$g(5) = \left(\frac{1}{4}\right)^{5-3} = \left(\frac{1}{4}\right)^2$$

$$g(5) = \frac{1}{16} = 0.0625$$

11. Ans: 5.6568 (Range: 5.5 to 5.75)

Sol: $\bar{E} = -\nabla V$

$$= -\left[\frac{\partial V}{\partial x} \hat{a}_x + \frac{\partial V}{\partial y} \hat{a}_y \right]$$

$$= -[2xy \hat{a}_x + x^2 \hat{a}_y]$$

$$\therefore \bar{E} \text{ at } x = 2, y = 1 \text{ is } = -[4\hat{a}_x + 4\hat{a}_y]$$

$$\therefore \text{Magnitude of } \bar{E} = \sqrt{16+16} = 4\sqrt{2}$$


$$= 5.6568 \text{ V/m}$$

12. Ans: (A)

Sol: 1: a tap changing transformer has Y_{Bus} as,

$$Y_{\text{Bus}} = \begin{matrix} (1) & \begin{bmatrix} y & -\frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \\ (2) & \end{matrix}$$

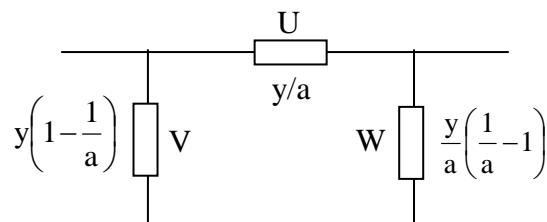The equivalent - π model from Y_{Bus} will be



As $a > 1$,

'U' is inductive nature

'W' is capacitive nature

'V' is inductive nature.

13. Ans: 1280 no range

Sol: Given that $|A_{4 \times 4}| = 5$

$$\because |KA_{n \times n}| = K^n |A_{n \times n}|$$

$$\Rightarrow |(-4)A| = (-4)^4 |A_{4 \times 4}| \text{ for } n = 4$$

$$\Rightarrow |(-4)A_{4 \times 4}| = (256)(5)$$

$$\therefore |(-4)A_{4 \times 4}| = 1280$$

TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2020

Date of Exam : **18th January 2020**
Last Date to Apply : **31st December 2019**

Highlights:

- Get real-time experience of **GATE-20** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post **GATE** guidance sessions by experts.
- Encouraging awards for **GATE-20** toppers.

PAN INDIA

PRESENCE AVAILABLE IN MORE THAN



SSC-JE (Paper-I)

Online Test Series

Staff Selection Commission - Junior Engineer

No. of Tests : 20

Subject Wise Tests : 16 | Mock Tests - 4

Civil | Electrical | Mechanical

AVAILABLE NOW

All tests will be available till **SSC 2019 Examination**

14. Ans: (C)

Sol: Given $R_{ds} = 0.15 \Omega$, $V_{ON} = 0.6 \text{ V}$

$$I_{RMS}^2 = I_{RMS1}^2 + I_{RMS2}^2$$

$$I_{RMS1}^2 = \frac{10^2}{3} \times \frac{2}{8} = \frac{25}{3}$$

$$I_{RMS2}^2 = 10^2 \times \frac{2}{8} = 25$$

$$I_{RMS}^2 = \frac{25}{3} + 25 = \frac{100}{3} \text{ A}$$

$$I_{avg} = \frac{\frac{1}{2} \times 2 \times 10 + 2 \times 10}{8} = \frac{30}{8} \text{ A}$$

$$P_{loss} = I_{RMS}^2 R_{ds} + I_{avg} V_{ON} =$$

$$\frac{100}{3}(0.15) + \frac{30}{8}(0.6)$$

$$= 5 + 2.25 = 7.25 \text{ W}$$

15. Ans: (B)

Sol: The condition for exactness of a differential equation

$$M(x, y) dx + N(x, y) dy = 0 \text{ is } \frac{\partial M}{\partial y} = \frac{\partial N}{\partial x}$$

Given that $M(x, y) = 3xy^2 + k^2 x^2 y$ and $N(x, y) = kx^3 + 3x^2 y$

$$\text{Consider } \frac{\partial M}{\partial y} = \frac{\partial N}{\partial x}$$

$$\Rightarrow 6xy + k^2 x^2 = 3kx^2 + 6xy$$

$$\Rightarrow k^2 = 3k \text{ (or) } k^2 - 3k = 0$$

$$\Rightarrow k = 0, 3$$

\therefore The non zero value of k is 3

16. Ans: 0.25 no range

Sol: Given

$$\int_0^x f(t) dt = -2 + \frac{x^2}{2} + 4x \sin(2x) + 2 \cos(2x)$$

Differentiating both sides of above w.r.t 'x', we get

$$\begin{aligned} \frac{d}{dx} \left[\int_0^x f(t) dt \right] &= -0 + \frac{2x}{2} + 4 \sin(2x) \\ &\quad + 8x \cos(2x) - 4 \sin(2x) \\ &\Rightarrow \left(\frac{d}{dx}(x) \right) [f(x)] - \left(\frac{d}{dx}(0) \right) [f(0)] \\ &= x + 8x \cos(2x) \end{aligned}$$

$$\Rightarrow f(x) = x + 8x \cos(2x)$$

$$\begin{aligned} \therefore \frac{1}{\pi} f\left(\frac{\pi}{4}\right) &= \frac{1}{\pi} \left[\frac{\pi}{4} + 8\left(\frac{\pi}{4}\right) \cdot \cos\left(\frac{2\pi}{4}\right) \right] \\ &= \frac{1}{4} = 0.25 \end{aligned}$$

17. Ans: 10 (no range)

Sol: Resolution = $\Delta V_i = 5 \text{ mV}$

Maximum Analog input = $V_{i(max)} = 5 \text{ V}$

$$\Delta V_i = \frac{1}{2^n - 1} \times 5$$

$$2^n - 1 = 1000$$

$$2^n = 1001$$

$$n \approx 10$$

18. Ans: (B)

Sol: Given that $A = (a_{ij})_{n \times n}$,

$$\text{where } a_{ij} = \begin{cases} (n+1)^2 - i, & \forall i = j \\ 0 & , \forall i \neq j \end{cases}$$

$$\Rightarrow A = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

$$= \begin{bmatrix} 15 & 0 & 0 \\ 0 & 14 & 0 \\ 0 & 0 & 13 \end{bmatrix}_{3 \times 3} \quad \text{for } n = 3$$

$\Rightarrow A_{3 \times 3}$ is a diagonal matrix & its eigen values are its diagonal elements 15, 14, 13. If $\lambda_1, \lambda_2, \lambda_3$ are the eigen values of $A_{3 \times 3}$ matrix then the eigen values of matrix $A_{3 \times 3}^2$ are λ_1^2, λ_2^2 and λ_3^2 .

\therefore The eigen values of a required matrix A^2 are $(15)^2, (14)^2$ and $(13)^2$ (i.e., 225, 196, 169)

19. Ans: (D)

Sol: Frequency of rotor currents and voltages = sf
 $= -0.01 \times 50 = -0.5$ Hz. Rotating magnetic field produced by the rotor currents rotates at a speed of $120 (sf)/P = 15$ RPM (in magnitude) with respect to the rotor.

The field due to stator currents rotates at $120 \times 50/4 = 1500$ RPM with respect to stator say in clock-wise direction.

Rotor field rotates at 1500 RPM with respect to stator.

Rotor field rotates at 15 RPM with respect to rotor.

20. Ans: (C)

Sol: Given data:

$$i(t) = \left[-6\sqrt{2} \sin(100\pi t) + 6\sqrt{2} \cos\left(300\pi t + \frac{\pi}{4}\right) + 6\sqrt{2} \right] A$$

A true rms ammeter measures I_{rms} of $i(t)$

$$I_{rms} = \sqrt{\left(6\sqrt{2}\right)^2 + \frac{(-6\sqrt{2})^2}{2} + \frac{(6\sqrt{2})^2}{2}} A$$

$$= \sqrt{36 \times 2 + 36 + 36} A$$


$$= \sqrt{36 \times 4} A = 12 A$$

21. Ans: (B)

Sol: Conductor voltage, $V_{ph} = \frac{33}{\sqrt{3}}$ kV

$$= 19.052 \text{ kV}$$

Equivalent capacitor arrangement will be

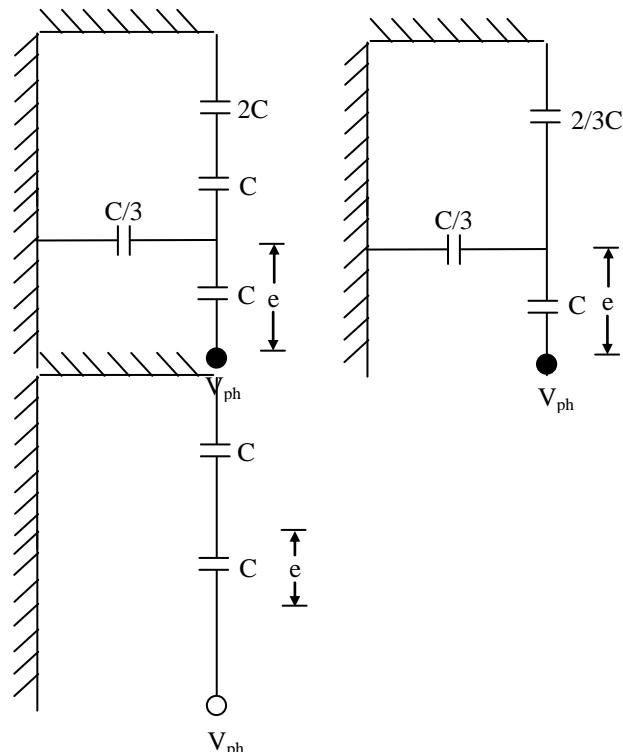


$$e = \frac{V_{ph}}{2} = 9.53 \text{ kV}$$

22. Ans: (C)



Sol: OLTF = $\frac{K}{s-a}$ ($a > 0$)

$$= \frac{K}{j\omega - a} = \frac{K}{\sqrt{\omega^2 + a^2}} \angle -\left(180^\circ - \tan^{-1} \frac{\omega}{a}\right)$$

The Polar plot is

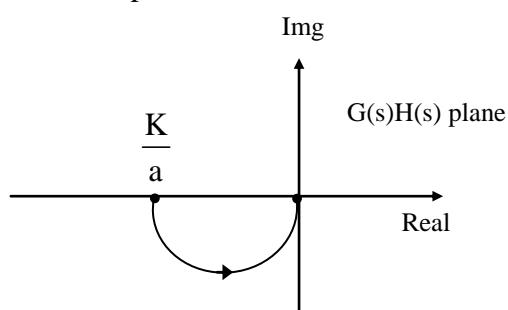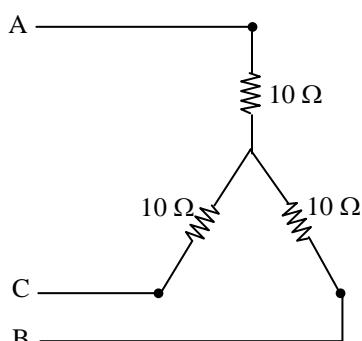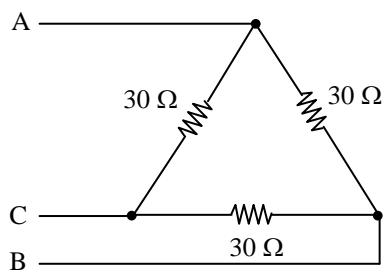**23. Ans: (B)**

Sol: Convert delta connected load into star connected load.



\therefore In 120° conduction scheme,

$$V_{ph} = \frac{V_{dc}}{\sqrt{6}} = 163.3 \text{ V}$$

3- ϕ load power

$$P_o = 3 \left[\frac{V_{ph}^2}{R} \right] = 3 \times \frac{163.3^2}{10} = 8 \text{ kW}$$


24. Ans: (C)

Sol: T. F = $\frac{Y(s)}{U(s)} = C(sI - A)^{-1} B$,

$$u(t) = \delta(t) \xrightarrow{LT} U(s) = 1$$

$$Y(s) = C(sI - A)^{-1} B$$

$$y(t) = C e^{At} B, \text{ as } e^{At} \xrightarrow{LT} (sI - A)^{-1}$$

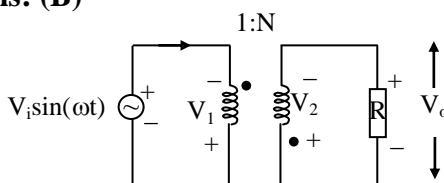25. Ans: (B)**Sol:**

$$\frac{V_2}{V_1} = N$$

$$V_2 = NV_1 = NV_i \sin \omega t$$

$$\text{So } V_0 = -NV_i \sin \omega t.$$

(According to dot polarity)

26. Ans: 425.8 (Range: 424 to 426)**Sol:** Given,


$$\text{Terminal voltage } (V_t) = 440 \text{ V}$$

$$\text{Armature resistance } (r_a) = 0.8 \Omega$$

$$\text{Field resistance } (r_f) = 200 \Omega$$

$$\text{Efficiency } (\eta) = 85\%$$
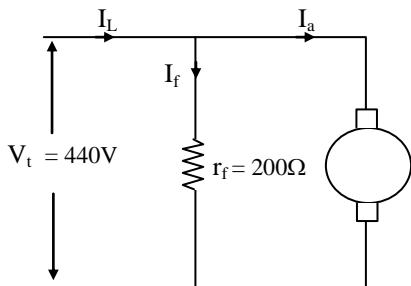
$$\text{Power output } (P_o) = 7.46 \text{ kW}$$



$$\text{Efficiency } (\eta) = \frac{\text{Power output } (P_o)}{\text{Power input } (P_i)}$$

$$\Rightarrow \frac{85}{100} = \frac{7.46 \times 10^3}{P_i}$$

$$\Rightarrow P_i = 8776.5 \text{ W}$$

$$\text{Power input } (P_i) = V_t \times I_L$$

$$\Rightarrow 8776 \text{ W} = 440 \times I_L$$

$$\Rightarrow I_L = 19.95 \text{ A}$$

$$I_f = \frac{V_t}{r_f} = \frac{440}{200}$$

$$I_f = 2.2 \text{ A}$$

For a shunt motor,

$$I_a = I_L - I_f$$

$$I_a = 19.95 - 2.2$$

$$I_a = 17.75 \text{ A}$$

For a shunt motor

$$\text{Back emf } (E_a) = V_t - I_a r_a$$

$$E_a = 440 - (17.75) \times (0.8)$$

$$\Rightarrow E_a = 425.8 \text{ V}$$

∴ Back Emf for the given shunt motor is 425.8 V

27. Ans: (A)

$$\text{Sol: CLTF} = \frac{G(s)}{1 + G(s)}$$

$$= \frac{k(s+4)}{s(s+1)+k(s+4)} \Rightarrow \frac{k(s+4)}{s^2 + (k+1)s + 4k}$$

By comparing with standard form of second order characteristic equation

$$2\omega_n = (k+1) \text{ and } \omega_n = \sqrt{4k}$$

$$2\omega_n = k+1 \quad \therefore \zeta = 1$$


$$2 \times \sqrt{4k} = k+1 \Rightarrow 16k = k^2 + 2k + 1$$

$$\Rightarrow k^2 - 14k + 1 = 0$$

$$\Rightarrow k = 0.071 \text{ & } 13.92$$

28. Ans: (C)

Sol:

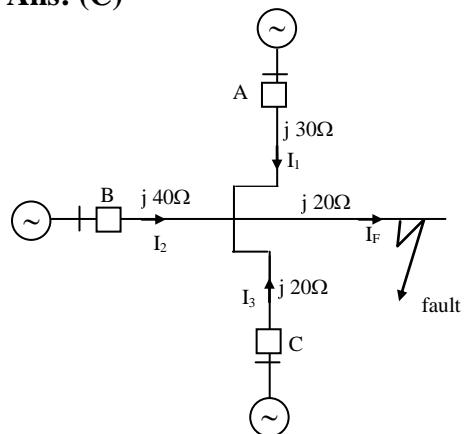

$$I_1 = 1540 \text{ A}, I_2 = 1150 \text{ A}, I_F = 5000 \text{ A}$$

$$\text{Now, } I_3 = I_F - I_1 - I_2$$

$$= 2310 \text{ A}$$

* Voltage at 'A' ,

$$V_A = I_1 \times j30 + I_F \times j20$$

Impedance measured by 'A' ,

$$Z_A = \frac{V_A}{I_1} = j30 + j20 \times \frac{I_F}{I_1}$$

$$= j30 + j64.92$$

$$= j 94.9 \Omega$$

* Voltage at 'B' ,

$$V_B = j40 \times I_2 + j20 \times I_F$$

Impedance measured by 'B',

$$Z_B = \frac{V_B}{I_2} = j40 + j86.95 \\ = j 126.95 \Omega$$

* Voltage at 'C' ,

$$V_C = I_3 \times j20 + I_F \times j20$$

Impedance measured by 'C',

$$Z_C = \frac{V_C}{I_3} = j20 + j43.29 = j 63.29 \Omega$$


As reach = 100 Ω

Relays 'A' and 'C' operates first after this operation, impedance measured by 'B' will be $Z_B = j60\Omega$ and it is lower than reach.

\Rightarrow Later on 'B' also operates.

29. Ans: 3 (2.9 to 3.1)

Sol:

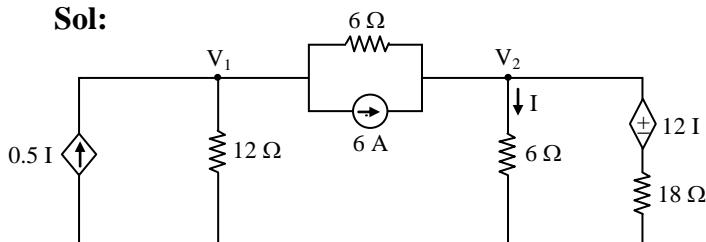

$$\text{Here, } I = \frac{V_2}{6}$$

Dependent current source supplies current of $0.5I$

$$\text{i.e., } 0.5 \left(\frac{V_2}{6} \right) = \frac{V_2}{12}$$

dependent voltage source supplies voltage of $12I$ i.e., $12 \left(\frac{V_2}{6} \right) = 2V_2$

Apply KCL at Node (1)

$$-\frac{V_2}{12} + \frac{V_1}{12} + \frac{V_1 - V_2}{6} = -6$$

$$\Rightarrow 3V_1 - 3V_2 = -72 \dots\dots\dots(1)$$

Apply KCL at Node (2),

$$\frac{V_2 - V_1}{6} + \frac{V_2}{6} + \frac{V_2 - 2V_2}{18} = 6$$

$$-3V_1 + 5V_2 = 108 \dots\dots\dots(2)$$

Adding (1) & (2), we get

$$V_2 = 18 \text{ V}$$

$$I = \frac{V_2}{6} = \frac{18}{6} = 3 \text{ A}$$

30. Ans: k = 10

Sol: Put $s = z - 1$

$$CE = 1 + \frac{k}{(z-1)(z-1+3)(z-1+4)} = 0$$

$$z^3 + 4z^2 + z + k - 6 = 0$$


$$\begin{array}{r|rr} z^3 & 1 & 1 \\ z^2 & 4 & k-6 \\ z^1 & \hline 10-k & 4 \\ z^0 & k-6 & \end{array}$$

$$10 - k = 0 \Rightarrow k = 10$$

31. Ans: (C)

Sol:

P.S	i/p	FF i/ps	N.S
Q ₁ Q ₂	x	J ₁ K ₁ J ₂ K ₂	Q ₁ Q ₂
0 0	0	0 0 0 0	0 0
0 0	1	0 0 1 1	0 1
0 1	0	0 0 0 0	0 1
0 1	1	1 1 1 1	1 0
1 0	0	0 0 0 0	1 0
1 0	1	0 0 1 1	1 1
1 1	0	0 0 0 0	1 1
1 1	1	1 1 1 1	0 0

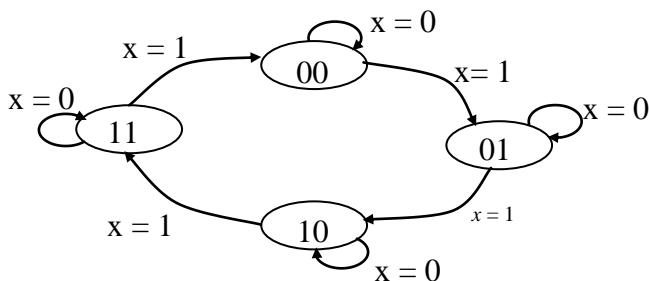

32. Ans: 2 no range

Sol: Given that $f(x, y) = x^2 + 2y^2 \dots\dots\dots (1)$

with $y - x^2 + 1 = 0 \dots\dots\dots (2)$

From (2), we write $y = x^2 - 1 \dots\dots\dots (3)$

Put (3) in (1), we get

$$\begin{aligned} f(x, y) &= x^2 + 2y^2 = x^2 + 2(x^2 - 1)^2 \\ &= x^2 + 2[x^4 - 2x^2 + 1] \end{aligned}$$

Let $g(x) = 2x^4 - 3x^2 + 2$

Then $g'(x) = 8x^3 - 6x$ and $g''(x) = 24x^2 - 6$

Consider $g'(x) = 0$

$$\Rightarrow 8x^3 - 6x = 0$$

$\therefore x = 0, \frac{\sqrt{3}}{2}, -\frac{\sqrt{3}}{2}$ are stationary points.

At $x = 0, g''(0) = -6 < 0$

$$\text{At } x = \pm \frac{\sqrt{3}}{2}, g''\left(\pm \frac{\sqrt{3}}{2}\right) = 12 > 0$$



$\therefore x = 0$ is a local point of maxima.

Hence, the maximum value of the function $f(x, y)$ at $x = 0$ is

$$\begin{aligned} f(x, y) &= f(x, x^2 - 1) = f(0, -1) \\ &= 0 + 2[0 - 0 + 1] = 2 \end{aligned}$$

33. Ans: (C)

Sol:

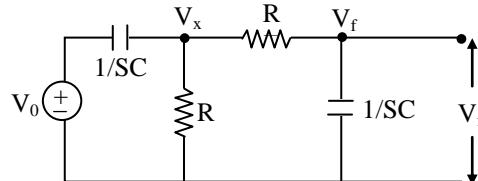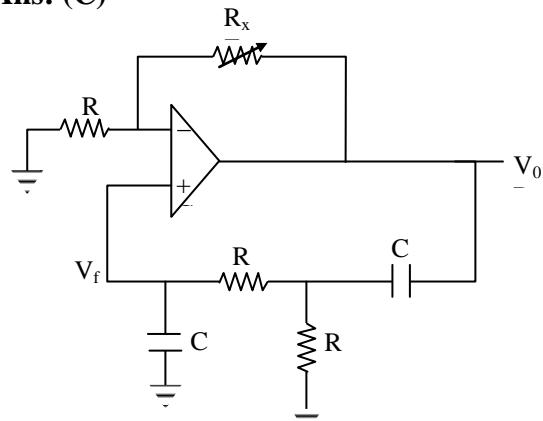

KCL at node V_x .


$$\frac{V_0 - V_x}{R} = \frac{V_x}{R} + \frac{V_x - V_f}{R} \quad \dots\dots\dots (1)$$

$$\text{and } \frac{V_x - V_f}{R} = \frac{V_f}{\frac{1}{SC}} \quad \dots\dots\dots (2)$$

$$\therefore V_x = (1+SRC) V_f \quad \dots\dots\dots (3)$$

$$\Rightarrow \beta = \frac{V_f}{V_0} = \frac{SCR}{S^2 C^2 R^2 + 3SCR + 1} \quad [\because \text{from equation (1), (2) \& (3)}]$$
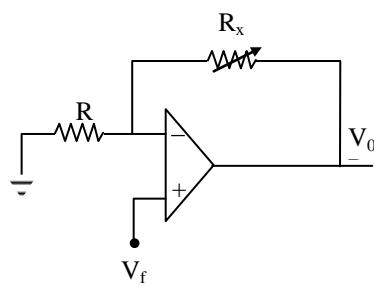
$$\therefore \beta = \frac{1}{3 + j \left[\omega CR - \frac{1}{\omega CR} \right]}$$



$$\frac{V_0}{V_f} = 1 + \frac{R_x}{R}$$

Since for sustained oscillations $\beta A = 1$

$$\Rightarrow A = \frac{1}{\beta}$$

$$\therefore 1 + \frac{R_x}{R} = 3 + j \left[\omega CR - \frac{1}{\omega CR} \right]$$

Equating img., parts

$$\Rightarrow \omega CR - \frac{1}{\omega CR} = 0$$

$$\Rightarrow f = \frac{1}{2\pi RC} \text{ Hz}$$

$$\& 1 + \frac{R_x}{R} = 3$$

$$\therefore R_x = 2R$$

34. Ans: 2.22 (Range: 2.15 to 2.25)

Sol: E_2 = stand-still rotor voltage/phase

$$= \frac{60}{\sqrt{3}} = 34.6 \text{ V.}$$

Rotor impedance at 4% slip


$$= \frac{0.6}{0.04} + j4 = 15 + j4 \Omega$$

$$|Z| = 15.5 \Omega$$


$$\text{current} = \frac{34.6}{15.5} = 2.22 \text{ Amp}$$

35. Ans: (*)


Sol:

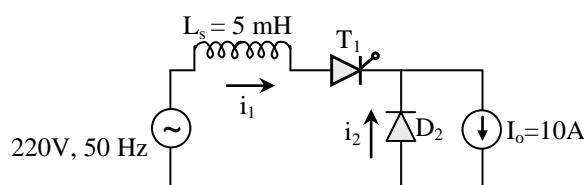

$$i_1 + i_2 = I_o$$

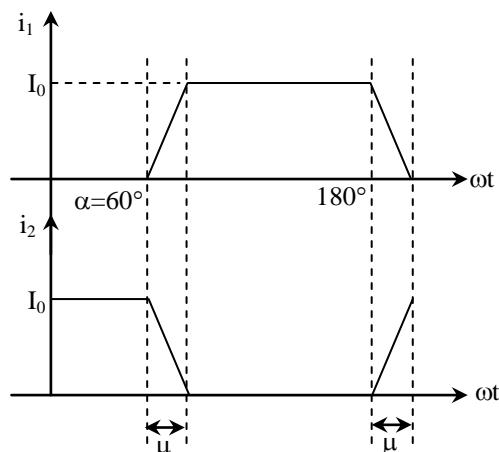

During overlap period

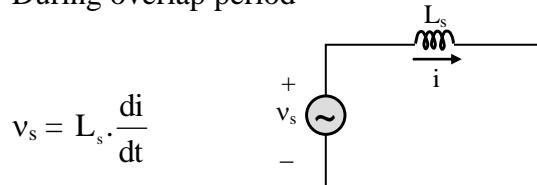

$$\int_{-I_0}^{I_0} di = \frac{1}{L_s} \int_{\frac{\alpha}{\omega}}^{\frac{\alpha+\mu}{\omega}} V_m \sin \omega t dt$$

$$2I_0 = \frac{V_m}{\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$I_0 = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\cos(\alpha + \mu) = \cos \alpha - \frac{2\omega L_s}{V_m} I_0$$

$$\cos(\alpha + \mu) =$$

$$\cos 60^\circ - \frac{2 \times 2\pi \times 50 \times 5 \times 10^{-3} \times 10}{220\sqrt{2}}$$

$$\cos(\alpha + \mu) = 0.399$$

$$\alpha + \mu = 66.479^\circ$$

$$\mu = 6.479^\circ$$

$$\text{Conduction angle of } T_1 = 120^\circ + \mu$$

$$= 120^\circ + (6.48)$$

$$= 126.48^\circ$$

HEARTY CONGRATULATIONS TO OUR ESE - 2019 TOP RANKERS



KARTIKEYA SINGH EE AIR 10



RAJAT SONI E&T AIR 10



HARSHAL BHOSALE ME AIR 10



ABUZAR GAFFARI CE AIR 10



SHAMBHANI EE AIR 2



ANKUR MANLA E&T AIR 2



SAHIL GOYAL ME AIR 2



ABHISHEK KHANDO EE AIR 3



ROHIT KUMAR E&T AIR 3



KUMAR CHANDAN ME AIR 3



AMRITJEET CE AIR 3



ANKIT TAYAL EE AIR 4



AMIR KHAN E&T AIR 4



SAURAV ME AIR 4



AMAN GULIA CE AIR 4



KUMAN PURIYAN EE AIR 5



RISHABH CHANDRA CE AIR 5



NITISH LALWANI EE AIR 6



PUSHPAK ME AIR 6



KARAN SINGH CE AIR 6



KARTIKEY SINGH EE AIR 7



RAHUL JAIN E&T AIR 7



MANISH RAJPUT ME AIR 7



KULDEEP KUMAR E&T AIR 8



HEMANT KUMAR ME AIR 8



TUSHAR KUMAR CE AIR 8



DEEPITA ROY EE AIR 9



BHUPESH KARMAKAR E&T AIR 9




G. BABAPARA ME AIR 9



ANKIT KUMAR CE AIR 9



ANJALI SHARMA EE AIR 10

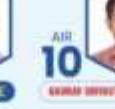

GEETA DEEWALI E&T AIR 10



SUMIT BHANDOO ME AIR 10

and many more...

TOTAL SELECTIONS in Top 10: **33**

(EE: **9**, E&T: **8**, ME: **9**, CE: **7**)

and many more...



DIGITAL CLASSES

for

ESE 2020/2021

General Studies &
Engineering Aptitude

GATE 2020/2021

Computer Science &
Information Technology

Access the Course at

www.deep-learn.in

36. Ans: (D)

Sol: Energy consumed = $VI \cos\phi \times t$

$$= \frac{230 \times 40 \times 0.4 \times 1}{1000}$$

$$= 3.68 \text{ kWh}$$

Actual number of revolution

$$= 3.68 \times 100$$

$$= 368 \text{ revolutions}$$

$$\% \text{ Error} = \frac{360 - 368}{368} \times 100$$

$$= 2.17\% \text{ low}$$

37. Ans: 91 (range: 88 to 93)

Sol: Total energy = $E_{x(t)} = \int_0^{\infty} e^{-2t} dt = \frac{1}{2}$

$$\text{Given, } x(t) = e^{-t} u(t)$$

$$X(\omega) = \frac{1}{1 + j\omega}$$

$$|X(\omega)|^2 = \frac{1}{1 + \omega^2}$$

Using parseval's theorem Energy contained

$$\text{in } |\omega| \leq 7 \text{ rad/sec} = \frac{1}{2\pi} \int_{-7}^{7} |X(\omega)|^2 d\omega$$

$$= \frac{1}{2\pi} \int_{-7}^{7} \frac{1}{1 + \omega^2} d\omega = \frac{1}{2\pi} \tan^{-1}(\omega) \Big|_{-7}^{7}$$

$$= \frac{2}{2\pi} \tan^{-1}(7) = 0.4548$$

Percentage of energy

$$= \frac{0.4548}{0.5} = 0.9096 \times 100$$

$$= 90.96\% \approx 91\%$$

38. Ans: 1.52 no range

Sol: Consider $\int_C \bar{f} \cdot d\bar{r} = \int_{(0,0)}^{(1,1)} [\sqrt{x} dx + (x + y^3) dy]$

$$\dots\dots\dots (1)$$

$$\text{Given that } C: x = t^2, y = t^3, 0 \leq t \leq 1 \quad \} \quad .. (2)$$

$$\Rightarrow dx = 2t dt, dy = 3t^2 dt$$

Using (2), (1) becomes

$$\int_C \bar{f} \cdot d\bar{r} = \int_{t=0}^1 [(t)(2t) dt + (t^2 + t^9)(3t^2) dt]$$

$$\Rightarrow \int_C \bar{f} \cdot d\bar{r} = \int_{t=0}^1 [2t^2 + 3t^4 + 3t^{11}] dt$$

$$\Rightarrow \int_C \bar{f} \cdot d\bar{r} = \left(\frac{2t^3}{3} + \frac{3t^5}{5} + \frac{3t^{12}}{12} \right)_0^1$$

$$\therefore \int_C \bar{f} \cdot d\bar{r} = \left(\frac{2}{3} + \frac{3}{5} + \frac{3}{12} \right) = 1.52$$

39. Ans: (B)

Sol: Given $\frac{d}{dx} \left(x \frac{dy}{dx} \right) = x \dots\dots\dots (1)$

$$\text{With } y(1) = 0 \dots\dots\dots (2)$$

$$\text{And } y'(1) = 0 \dots\dots\dots (3)$$

Now, integrating on both sides of (1), we get

$$x \frac{dy}{dx} = \frac{x^2}{2} + C_1$$

$$\Rightarrow \frac{dy}{dx} = \frac{x}{2} + \frac{C_1}{x} \dots\dots\dots (4)$$

Using (3), (4) becomes

$$0 = \frac{1}{2} + \frac{C_1}{1} \quad (\text{or}) \quad C_1 = -\frac{1}{2} \dots\dots\dots (5)$$

Using (5), (4) becomes

$$\frac{dy}{dx} = \frac{x}{2} - \frac{1}{2x}$$

$$\Rightarrow y = \frac{x^2}{4} - \frac{1}{2} \log x + C \quad \dots \dots \dots \quad (6)$$

Using (2), (6) becomes

$$0 = \frac{1}{4} - \frac{1}{2}(0) + C \quad (\text{or}) \quad C = \frac{-1}{4} \quad \dots \dots \dots \quad (7)$$

\therefore The solution of (1) from (6) and (7) is

$$y = y(x) = \frac{x^2}{4} - \frac{1}{2} \log(x) - \frac{1}{4}$$

$$\text{Hence, } y(2) = 1 - \frac{1}{2} \log(2) - \frac{1}{4}$$

$$= \frac{3}{4} - \frac{1}{2} \log(2)$$

40. Ans: 0.672 (Range: 0.66 to 0.68)

Sol: $I_0 = 20 \text{ A}$

$$V_0 = \frac{3V_m}{2\pi} (1 + \cos \alpha)$$

$$E = 200 \text{ V}$$

$$I_0 = \frac{V_0 - E}{R} = \frac{\frac{3V_m}{2\pi} (1 + \cos \alpha) - E}{R}$$

$$20 = \frac{\frac{3 \times 230 \times \sqrt{2}}{2\pi} (1 + \cos \alpha) - 200}{0.5}$$

$$\alpha = 69.37^\circ$$

$$\begin{aligned} \text{Displacement power factor} &= \cos \frac{\alpha}{2} \\ &= \cos 34.685 \\ &= 0.822 \end{aligned}$$

$$\text{Distortion factor DF} = \frac{I_{s1}}{I_{sr}}$$

$$I_{s1} = \frac{\sqrt{6}}{\pi} I_0 \cos \frac{\alpha}{2}$$

$$= \frac{\sqrt{6}}{\pi} \times 20 \times 0.822 = 12.818 \text{ A}$$

$$\begin{aligned} I_{sr} &= I_0 \sqrt{\frac{\pi - \alpha}{\pi}} \quad (\because \alpha \geq 60^\circ) \\ &= 15.679 \end{aligned}$$


$$DF = \frac{I_{s1}}{I_{sr}} = \frac{12.818}{15.679} = 0.817$$

$$\begin{aligned} \text{Supply power factor} &= DPF \times DF \\ &= 0.822 \times 0.817 \\ &= 0.672 \end{aligned}$$

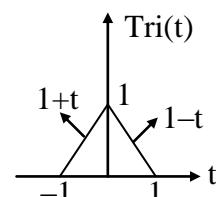41. Ans: 0.67 (range: 0.6 to 0.7)

Sol: $\text{Tri}(t) \leftrightarrow \text{Sinc}^2(f)$

$$x(t) = \text{Tri}(t), X(f) = \text{Sinc}^2(f)$$



Using parseval's theorem

$$\int_{-\infty}^{\infty} |x(t)|^2 dt = \int_{-\infty}^{\infty} |X(f)|^2 df$$

$$\int_{-\infty}^{\infty} \text{Sinc}^2(f) \text{Sinc}^2(f) df = \int_{-\infty}^{\infty} \text{Tri}(t) \text{Tri}(t) dt$$

$$\int_{-\infty}^{\infty} \text{Sinc}^4(f) df = \int_{-\infty}^{\infty} \text{Tri}(t) \text{Tri}(t) dt$$

$$= \int_{-1}^0 (t+1)^2 dt + \int_0^1 (1-t)^2 dt$$

$$= \frac{1}{3} + \frac{1}{3} = \frac{2}{3}$$

42. Ans: (B)

Sol: From Poisson's equation

$$\nabla^2 V = \frac{-\rho_v}{\epsilon}$$

for free space $\epsilon = \epsilon_0$

$$\frac{\partial^2 V}{\partial x^2} = \frac{-1}{\epsilon_0} \frac{x}{6\pi} \times 10^{-9}$$

$$\frac{\partial^2 V}{\partial x^2} = -6x$$

$$V(x) = -x^3 + C_1 x + C_2 \dots \dots \dots (1)$$

Given: $V(1) = -50$ and

$$V(4) = 50$$

Using $V(1) = -50$ in equation (1), we get

$$-50 = -1 + C_1 + C_2$$

$$C_1 + C_2 = -49$$

Using $V(4) = 50$ in equation (1), we get

$$4C_1 + C_2 = 114$$

By solving the above equations

$$C_1 = 54.33 \text{ and } C_2 = -103.33$$

$$V(x) = -x^3 + 54.33x - 103.33$$

$$V(2) = -8 + 108.66 - 103.33$$

$$\therefore V(2) = -2.67 \text{ Volt}$$

43. Ans: (A)

$$\text{Sol: } \frac{2L}{RT} = \frac{2 \times 500 \times 10^{-6}}{50 \times 50 \times 10^{-6}} = 0.4$$

$$1 - D = 1 - 0.5 = 0.5$$

$\frac{2L}{RT} < 1 - D$, Circuit is operating in


discontinuous mode

$$\frac{2L}{RT} = \beta(\beta - D)$$

$$0.4 = \beta(\beta - 0.5)$$

$$\beta^2 - 0.5\beta - 0.4 = 0$$

$$\beta = 0.93$$

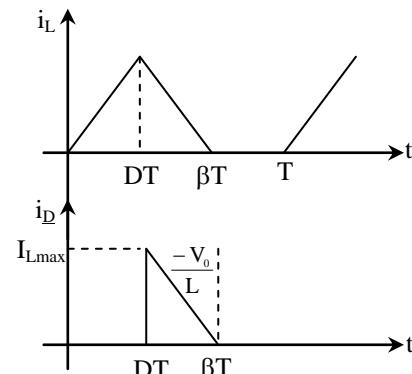

$$\frac{V_0}{L} = \frac{I_{L_{max}}}{(\beta - D)T}$$

$$I_{L_{max}} = \frac{V_0}{L} (\beta - D) T$$

$$= \frac{16.128}{500 \times 10^{-6}} (0.93 - 0.5) \times 50 \times 10^{-6}$$

$$= 1.6128(0.43)$$

$$= 0.693$$

$$I_{D_{rms}}^2 = \frac{I_{L_{max}}^2}{3} \times (\beta - D)$$

$$I_{D_{rms}}^2 = \frac{(0.693)^2}{3} \times 0.43$$

$$= 0.068 \text{ A}$$

$$I_{D_{rms}} = 0.262 \text{ A}$$

44. Ans: 3.2 (3.1 to 3.3)

$$\text{Sol: } Y_{eq} = \frac{1}{2+j4} + \frac{1}{R} = \left(\frac{1}{10} + \frac{1}{R} - \frac{j}{5} \right) \cup$$

For 0.9 lagging, angle of admittance must be
 $\cos^{-1}(0.9) = -25.84^\circ$

$$\text{Thus, } \frac{1/5}{1/10 + 1/R} = \tan 25.84 = 0.482$$

$$\Rightarrow R = 3.2 \Omega$$

45. Ans: (B)

Sol: No. of horizontal touches $n_x = 5$

No. of vertical touches $n_y = 3$

$$n_x f_x = n_y f_y$$

$$\frac{5 \times 60}{3} = f_y$$

$$\therefore f_y = 100 \text{ Hz}$$

46. Ans: 0.11**Range: 0.1 to 0.2**

Sol: Total possible outcomes for both faces even
 $= (2, 2), (2, 4), (2, 6), (4, 2), (4, 4), (4, 6),$
 $(6, 2), (6, 4), (6, 6) = 9$

Total favorable outcome for sum smaller than 6 $= (2, 2)$

P (sum is less than 6 given both faces are even) $= \frac{1}{9} = 0.11$

47. Ans: (C)

$$\text{Sol: } W_E = \frac{1}{2} \epsilon E^2$$

$$= \frac{1}{2} \times \epsilon_0 \times \epsilon_r \times E^2$$

Given: $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$ and $\epsilon_r = 4$

$$\bar{E} = 6\hat{a}_x + 8\hat{a}_y \text{ kV/mm}$$

$$= (6\hat{a}_x + 8\hat{a}_y) \times 10^6 \text{ V/m.}$$

$$|\bar{E}| = 10^7 \text{ V/m.}$$

$$W_E = \frac{1}{2} \times 4 \times 8.85 \times 10^{-12} \times (10^7)^2$$

$$= 1770 \text{ J/m}^3$$

Energy stored = Energy density \times volume

$$= 1770 \times 500 \times 10^{-3} \times 500 \times 10^{-3} \times 0.4$$

$$= 177 \text{ J}$$

48. Ans: 31 (Range: 30 to 32)

$$\text{Sol: } Z = \frac{\text{Open circuit voltage}}{\text{Short circuit current}} = \frac{450}{200} = 2.25 \Omega$$

$$X = \sqrt{Z^2 - R^2} = \sqrt{2.25^2 - 0.2^2} = 2.24 \Omega$$

Full load current

$$I = \frac{55 \times 1000}{550} = 100 \text{ A}$$

With I as reference

$$\bar{V} = 550 (0.8 + j0.6) = 440 + j330 \text{ V}$$

$$I \bar{Z} = 100 (0.2 + j2.24) = 20 + j224$$

$$\bar{E} = \bar{V} + I \bar{Z} = 440 + j330 + 20 + j224$$

$$= 720 \angle 50^\circ$$

$$\text{Regulation} = \frac{720 - 550}{550} \times 100 = 31\%$$

49. Ans: (D)

Sol: Initial energy (W_i)

$$= \frac{1}{2} C_1 V^2 = \frac{1}{2} \times 100 \times 10^{-6} \times 100 \times 100$$

$$= 0.5 \text{ J}$$

When connected in parallel, the initial charge $Q_i = C_1 V$

$= 100 \times 10^{-6} \times 100 = 10 \text{ mC}$ is redistributed in parallel combination of $C = C_1 + C_2$

$$= (100+400)\mu\text{F}$$

\therefore Common voltage becomes

$$V = \frac{Q}{C} = \frac{10 \times 10^{-3}}{500 \times 10^{-6}} = 20 \text{ V}$$

$$W_1 = \frac{1}{2} C_1 V^2 = \frac{1}{2} \times 100 \times 10^{-6} \times (20)^2 = 0.02 \text{ J}$$


$$W_2 = \frac{1}{2} C_2 V^2 = \frac{1}{2} \times 400 \times 10^{-6} \times (20)^2 = 0.08 \text{ J}$$

Final energy (W_f) = $W_1 + W_2 = 0.1 \text{ J}$

Energy dissipated = $W_i - W_f = 0.5 - 0.1 = 0.4 \text{ J}$

50. Ans: 592.96 [Range: 592 to 594]

Sol:

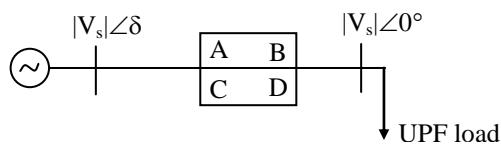

$$P_r = P_{\text{load}}$$

$$Q_r = 0$$

Reactive power equation,

$$\begin{aligned} Q_r &= \frac{|V_s| |V_r|}{|B|} \sin(\beta - \delta) - \frac{|A|}{|B|} |V_r|^2 \sin(\beta - \alpha) \\ &= \frac{|V_s| |V_r|}{|B|} \sin(90^\circ - \delta) - \frac{|A|}{|B|} |V_r|^2 \sin(90^\circ - 0^\circ) \\ |V_s| \cos \delta &= |A| |V_r| \Rightarrow |V_r| = \frac{|V_s| \cos \delta}{|A|}. \quad (1) \end{aligned}$$

Real

power,

$$P_r = \frac{|V_s| |V_r|}{|B|} \cos(\beta - \delta) - \frac{|A|}{|B|} |V_r|^2 \cos(\beta - \alpha)$$

$$P_r = \frac{|V_s| |V_r|}{|B|} \cos(90^\circ - \delta) - \frac{|A|}{|B|} |V_r|^2 \cos(90^\circ - 0^\circ)$$

$$P_r = \frac{|V_s| |V_r|}{|B|} \sin \delta$$

$$P_r = \frac{|V_s| |V_r| \cos \delta}{|A| |B|} \cdot \sin \delta$$

$$P_{(3-\phi)} = \frac{(400)^2 \times \cos 15^\circ \times \sin 15^\circ}{0.973 \times 69.33} \text{ MW}$$

$$= 592.96 \text{ MW}$$

51. Ans: (C)

Sol: Given $\frac{d^2y(t)}{dt^2} + \frac{dy(t)}{dt} - 2y(t) = x(t)$.

Apply L.T

$$s^2 Y(s) + sY(s) - 2Y(s) = X(s)$$

$$H(s) = \frac{1}{s^2 + s - 2} = \frac{1}{(s+2)(s-1)} = \frac{-1/3}{s+2} + \frac{1/3}{s-1}$$


Given that system is stable. So, ROC must include $j\omega$ axis.

So, ROC $-2 < \sigma < 1$.

$$h(t) = \frac{-1}{3} e^{-2t} u(t) - \frac{1}{3} e^t u(-t)$$

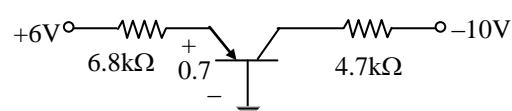52. Ans: 140.4 [Range: 138 to 142]

Sol: DC analysis: Open circuit the capacitor



$$I_E = \frac{6 - 0.7}{6.8k\Omega} = 0.779 \text{ mA}$$


$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.998}{1-0.998} = 499$$

$$I_C = \frac{\beta}{1+\beta} I_E = 0.777 \text{ mA}$$

$$g_m = \frac{I_c}{V_T} = \frac{I_c}{26 \text{ mV}} = \frac{0.777}{26}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{499}{0.777} \times 26 = 16.7 \text{ k}\Omega$$

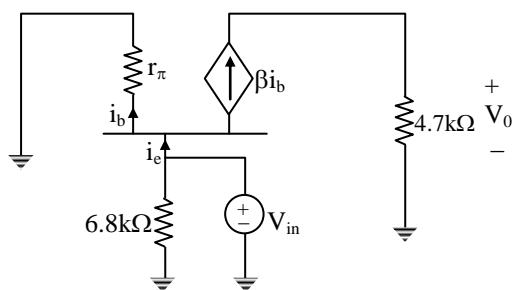AC analysis: short circuit DC voltage source and replace the transistor with its equivalent π -model



$$V_0 = \beta i_b (4.7 \text{ k}\Omega)$$

$$V_{in} = i_b \times r_\pi$$

$$A_v = \frac{V_0}{V_{in}} = \frac{\beta i_b (4.7 \text{ k}\Omega)}{i_b r_\pi} = 140.4 \text{ V/V}$$

53. Ans: 0

$$\text{Sol: } TF = K \frac{\left(1 + \frac{s}{0.5}\right)^2}{\left(1 + \frac{s}{10}\right)^3}$$

It is type 0 system

Velocity error coefficient

$$K_v = \lim_{s \rightarrow 0} s G(s) H(s)$$

$$= 0$$

54. Ans: (C)

Sol: MVI B, 0AH

7T

LOOP: MVI C, 50H

7T

DCR C

4T

DCR B

4T

JNZ LOOP

10T/7T

B register initialized with 0AH i.e., 10d.

Effect on zero flag due to "DCR B" instruction will be verified by "JNZ LOOP" instruction in iteration.

Therefore LOOP gets executed for 10 times. The only instruction outside the LOOP is MVI B, 0AH which gets executed for only 1 time.

All the instructions inside the loop gets executed for 10 times.

\therefore Total T - states

$$= 1 \times 7T + 10 \times [7T + 4T + 4T + 10T] - 3T$$

$$= 7T + 10 \times 25T - 3T$$

$$= 4T + 250T$$


$$= 254T$$

55. Ans: 1.33 p.u. (Range : 1.2 to 1.4)

Sol: $Z_{1eq} = j0.3 + j0.2 = j0.5 \text{ p.u.}$

$Z_{2eq} = j0.2 + j0.2 = j0.4 \text{ p.u.}$

$Z_{0eq} = \infty$

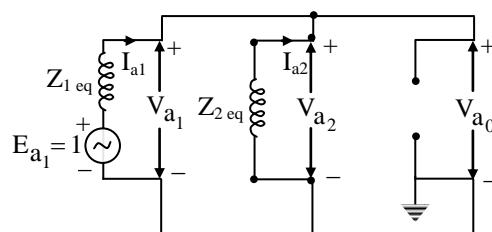

$$I_{a1} = \frac{E_{a1}}{Z_{1\text{eq}} + Z_{2\text{eq}}}$$

$$= \frac{1}{j0.5 + j0.4}$$

$$= -j1.111 \text{ p.u.}$$

$$V_{a1} = E_{a1} - I_{a1}Z_{1\text{eq}}$$

$$= 1 - (-j1.111) \times j0.5$$

$$= 0.4445 \text{ p.u.}$$

$$V_a = V_{a1} + V_{a2} + V_{a0}$$

$$= 3V_{a1}$$

$$= 3 \times 0.4445$$

$$= 1.333 \text{ p.u.}$$

ISRO

इसरो ISRO

ONLINE TEST SERIES

No. of Tests : 15

Subject Wise Tests : 12 | Mock Tests : 3

Indian Space Research Organisation (ISRO)

Recruitment of Scientist/Engineer 'SC'

ELECTRONICS | MECHANICAL | COMPUTER SCIENCE

Starts from **5th November 2019**

All tests will be available till 12-01-2020.

© 040 - 48539866 / 040 - 40136222 ✉ testseries@aceenggacademy.com

