



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.


Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad


Branch: Instrumentation Engineering - SOLUTIONS

01. Ans: (C)

Sol:

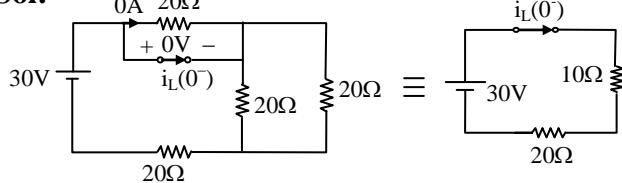
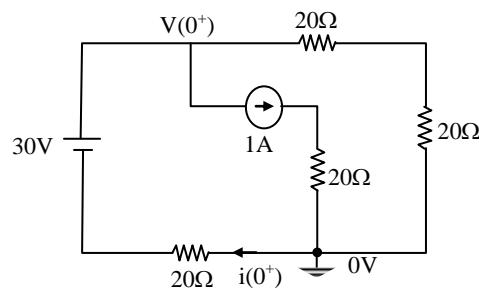
$$\text{So, } i_L(0^-) = \frac{30}{30} = 1\text{A} = i_L(0^+)$$



$$\text{Nodal: } \frac{V_L(0^+) - 30}{20} + 1 + \frac{V_L(0^+)}{40}$$

$$= 0 \Rightarrow V_L(0^+) = \frac{20}{3} \text{V}$$

$$\text{So, } i(0^+) = \frac{30 - V_L(0^+)}{20} = \frac{7}{6} \text{A}$$

02. Ans: - 3.33 (Range -3 to -4)

Sol: $A_V \approx -g_m R_D$

$$g_m = \sqrt{2I_D \mu_n C_{ox} \left(\frac{W}{L}\right)} = \frac{1}{300}$$

$$A_V = -3.33$$

03. Ans: 4

$$\text{Sol: } G(s) = \frac{\left(1 + \frac{s}{2}\right)2}{\left(1 + \frac{s}{8}\right)8} = \left(\frac{1}{4}\right) \frac{\left(1 + \frac{s}{2}\right)}{\left(1 + \frac{s}{8}\right)}$$

$$\text{But } G(s) = \frac{1+s\tau}{1+\alpha s\tau}$$


$$\text{By comparing } \tau = \frac{1}{2}$$

$$\alpha\tau = \frac{1}{8} \Rightarrow \alpha = \frac{1}{4}$$

$$\omega_m = \frac{1}{\tau\sqrt{\alpha}} = \frac{1}{\frac{1}{2}\sqrt{\frac{1}{4}}} = 4 \text{ rad/sec}$$

04. Ans: (a)

Sol:

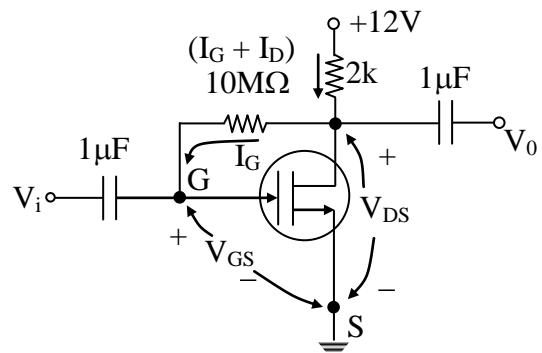

$$\text{Step (1): Consider } k = \frac{I_{D(ON)}}{[V_{GS(ON)} - V_{Th}]^2}$$



ESE - MAINS

Classes Start from:

13th FEB 2020



@ DELHI

(@ HYDERABAD)



**Students who Qualify in Prelims
can avail 100 % Fee Waiver**

ESE-2018, 2019 Prelims Qualified Students are also eligible

for more details Contact: **040-23234418/19/20**, Email: hyderabad@aceenggacademy.com

www.aceenggacademy.com

[HYDERABAD](#) | [AHMEDABAD](#) | [DELHI](#) | [PUNE](#) | [BHUBANESWAR](#) | [LUCKNOW](#) | [KOLKATA](#) | [VIJAYAWADA](#) | [VIZAG](#) | [TIRUPATI](#) | [CHENNAI](#) | [BENGALURU](#)

$$= \frac{6\text{mA}}{(8\text{V} - 3\text{V})^2} = 0.24\text{mA/V}^2 \quad (1)$$

$$\begin{aligned} \text{Step (2): } I_D &= k(V_{GS} - V_{Th})^2 \quad \dots (2) \\ &= (0.24 \text{mA/V}^2)[6.4V - 3V]^2 \\ &\quad \dots (3) \\ \therefore I_{D_0} &= 2.7744 \text{mA} \quad \dots (4) \end{aligned}$$

Step (3): KVL for output section

$$V_{DS} = 12V - (I_D + I_G) 2k = 0 \quad \underline{\hspace{1cm}} \quad (5)$$

$$\therefore V_{DS_0} = 6.45 \text{ V} \quad (7)$$

05. Ans: (c)

Sol: Electronic voltmeters offer very high input impedance than non-electronic voltmeters


because of existence of solid state electronic device at i/p side.

06. Ans: 170 (range: 169 to 171)

$$\textbf{Sol: } 2mH \rightarrow j\omega L = j(10 \times 10^3)(2 \times 10^{-3}) = j20$$

$$1\mu F \rightarrow \frac{1}{j\omega C} = \frac{1}{j(10 \times 10^3)(1 \times 10^{-6})}$$

$$\equiv -j100$$

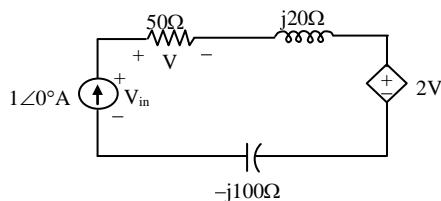

$$V = (1 \angle 0^\circ) (50) = 50$$

$$V_{in} = (1 \angle 0^\circ) (50 + j20 - j100) + (2) (50)$$



$$V_{in} = 50 - j80 + 100 = 150 - j80$$

$$Z_{in} = \frac{V_{in}}{1 \angle 0^\circ} = 150 - j80\Omega \\ = 170\Omega$$

07. Ans: (b)

Sol: The L.T of periodic signal $x(t)$, with period 'T' is

$$X(s) = \frac{1}{1 - e^{-sT}} \int_0^T x(t)e^{-st} dt$$

08. Ans: 2.585 (2.3 to 2.8)

Sol: Here monostable multivibrator is implemented with 555 timer,
pulse width = $1.1RC$
= $1.1 \times 4.7K \times 0.5\mu$
= 2.585ms

09. Ans: (c)

$$\text{Sol: } G(s) = \frac{k(s+2)(s+3)}{(s+1)(s+4)}$$

$$\text{CLTF} = \left. \frac{G(s)}{1+G(s)} \right|_{k=1} = \frac{(s+2)(s+3)}{(s+1)(s+4)+(s+2)(s+3)}$$

10. Ans: 2.12 (Range: 2 to 2.3)

$$\text{Sol: } \frac{d\phi}{ds} = \hat{a} \cdot \text{grad } \phi$$

$$\phi = 2y + z$$

$$\hat{a} = \hat{j} + \hat{k}$$

$$\hat{a} = \frac{\bar{a}}{|\bar{a}|} = \frac{j+k}{\sqrt{1^2 + 2^2}} = \frac{j+k}{\sqrt{2}}$$

$$\text{grad } \phi = \nabla \phi = \left(i \frac{\partial}{\partial x} + j \frac{\partial}{\partial y} + k \frac{\partial}{\partial z} \right) (2y + z)$$

$$= j(2y) + k(z)$$

$$\frac{d\phi}{ds} = \frac{(j+k)}{\sqrt{2}} \{ 2y \hat{j} + \hat{k} z \} = 2\hat{j} + \hat{k}$$

$$= \frac{\hat{j} + \hat{k}}{\sqrt{2}} (2\hat{j} + \hat{k}) = \frac{3}{\sqrt{2}}$$

$$= 2.12$$

11. Ans: (b)

$$\text{Sol: } f(A, B, C, D) = A + B\bar{C} + A\bar{B}\bar{D} + ABCD \\ = AB\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}CD \\ + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + ABCD \\ + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + AB\bar{C}D \\ = \sum m(4, 5, 8, 9, 10, 11, 12, 13, 14, 15) \\ = \prod M(0, 1, 2, 3, 6, 7)$$

12. Ans: (b)

Sol: For $t \geq 0^+$; KVL gives

$$E = \frac{1}{C} \int_{0^-}^t i(t) dt + (E/2)$$

$$\text{Laplace transforming, } \frac{1}{Cs} I(s) + \frac{E}{2} \frac{1}{s} = E \frac{1}{s};$$

$$\text{from which } I(s) = \frac{CE}{2}$$

$$\text{Hence } i(t) = \frac{CE}{2} \delta(t) \text{ A.}$$

13. Ans: (c)

$$\text{Sol: } \beta_1 = 2 \quad f_{m_1} = 1 \text{ kHz}$$

$$\beta_2 = 4 \quad f_{m_2} = 10 \text{ kHz}$$

$$\beta_3 = 5 \quad f_{m_3} = 20 \text{ kHz}$$

$$\Delta f = \beta_1 f_{m_1} + \beta_2 f_{m_2} + \beta_3 f_{m_3}$$

$$= 2 \text{ kHz} + 40 \text{ kHz} + 100 \text{ kHz} = 142 \text{ kHz}$$

14. Ans: (b)

Sol: A thermocouple pair (A,B), the extension wires (C,D) should have identical temperature-emf relationship.



15. Ans: 1.22 (No range)

Sol: $\frac{dy}{dx} = y + x$

$$x_0 = 0, y_0 = 1$$

$$x_1 = x_0 + h = 0.1$$

$$x_2 = x_0 + 2h = 0.2$$

$$y_1 = y_0 + h f(x_0, y_0) = 1 + (0.1)(1+0) \\ = 1.1$$

$$y_2 = y_1 + h f(x_1, y_1) \\ = 1.1 + 0.1 [0.1 + 1.1] \\ = 1.1 + 0.12 \\ = 1.22$$

16. Ans: (a)

Sol: $X(s) = \frac{2s e^{-2s}}{s^2 + 4s + 3}$

$$\text{Assume } X_1(s) = \frac{2s}{s^2 + 4s + 3} = \frac{2s}{(s+1)(s+3)} \\ = \frac{-1}{s+1} + \frac{3}{s+3}$$

Apply ILT

$$x_1(t) = -e^{-t} u(t) + 3e^{-3t} u(t)$$

$$X(s) = e^{-2s} \cdot X_1(s)$$

Apply ILT

$$x(t) = x_1(t-2)$$


$$x(t) = -e^{-(t-2)} u(t-2) + 3e^{-3(t-2)} u(t-2)$$

17. Ans: (a)

Sol: Differential arrangement for a capacitance transducer is preferred, because it reduces non-linearity.

18. Ans: 19.5

Sol:

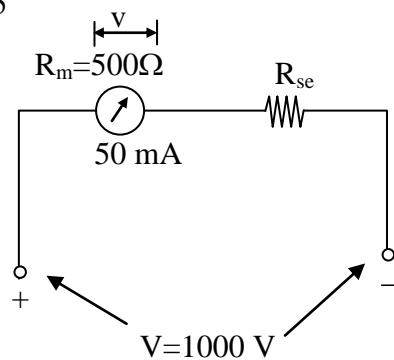

$$R_{se} = R_m (m-1)$$

$$m = \frac{V}{v} = \frac{1000}{500 \times 50 \times 10^{-3}} = 40$$

$$R_{se} = 500 (40-1)$$

$$= 500 \times 39$$

$$= 19500 \Omega$$

$$R_{se} = 19.5 \text{ k}\Omega$$

19. Ans: (b)

Sol: Let X = Amount the player wins in rupees
The probability distribution for X is given below.

Number of heads	0	1	2
X	x	1	3
P(X)	$\frac{1}{4}$	$\frac{2}{4}$	$\frac{1}{4}$

For the game to be fair we have to find x , so that $E(X) = 0$

$$\Rightarrow x \cdot \left(\frac{1}{4}\right) + 1 \cdot \left(\frac{2}{4}\right) + 3 \cdot \left(\frac{1}{4}\right) = 0$$

$$\Rightarrow x = -5$$

∴ Number of rupees, the player has to lose if no head occur = 5.

20. Ans: 6.2 (no range)

Sol: $V_{out} = 0.4V$ for input $(00010)_2 = (2)_{10}$

$$\text{Step size} = \frac{0.4}{2} = 0.2$$

$$V_{out} \text{ for input } (11111)_2 = 0.2 \times 31_{10} = 6.2V$$

21. Ans: 4 No range

Sol: The constant term in the characteristic equation of a matrix is equal to the determinant of a matrix

$$\therefore \det(A) = 4$$

22. Ans: (d)

Sol: Frequency deviation = $\frac{f_{\max} - f_{\min}}{2}$

$$f_{\max} = 100.01 \text{ MHz}$$

$$f_{\min} = 99.97 \text{ MHz}$$



$$\begin{aligned}
 &= \left(\frac{100.01 - 99.97}{2} \right) \text{MHz} \\
 &= 0.02 \times 10^6 \\
 &= 20 \text{ kHz}
 \end{aligned}$$

23. Ans: 2.83 (2.80 to 2.85)

$$\text{Sol: } R_\chi = \frac{R_2 R_3}{R_1} = \frac{800 \times 1200}{1500} = 640 \Omega$$


$$\begin{aligned}
 L_\chi &= R_2 C_1 R_3 \\
 &= 800 \times 0.15 \times 10^{-6} \times 1200
 \end{aligned}$$

$$L_\chi = 0.144 \text{ H}$$

$$\begin{aligned}
 \text{Q factor} &= \frac{\omega L_\chi}{R_\chi} \\
 &= \frac{2\pi \times 2 \times 10^3 \times 0.144}{640} \\
 &= 2.83
 \end{aligned}$$

24. Ans: (a)

Sol:

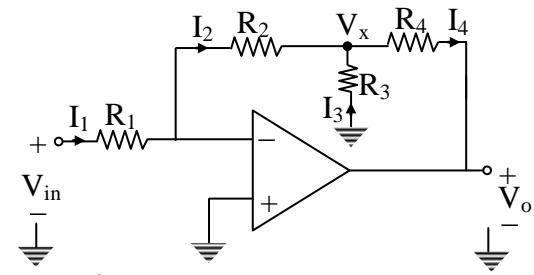

$$V^- = V^+ = 0 \quad [\because \text{Virtual ground}]$$

$$I_1 = \frac{V_{in}}{R_1} \quad (1)$$

$I_1 = I_2$ [\because current entering into the inverting terminal is zero]

$$I_2 + I_3 = I_4 \quad (2) \text{ and}$$

$$V_x = 0 - I_2 R_2 = -\frac{R_2}{R_1} V_{in} \quad (3)$$

$$\frac{V_{in}}{R_1} + \frac{0 - V_x}{R_3} = \frac{V_x - V_0}{R_4} \quad (4)$$

Solving (3) and (4), we get

$$\frac{V_0}{V_{in}} = -\frac{R_2}{R_1} \left[1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$

25. Ans: 24 No range

Sol: Given that $F(x) = f(g(x))$

$$\Rightarrow F'(x) = f'(g(x)) \cdot g'(x) \quad (\because \text{by chain rule})$$

$$\Rightarrow F'(5) = f'(g(5)) \cdot g'(5)$$

$$\Rightarrow F'(5) = f'(-2) \cdot 6$$


$$\therefore F'(5) = (4)(6) = 24$$

26. Ans: 25 (range: 25 to 25)

Sol: Maximum power transferred to load resistance R_L is

$$= \frac{V_{Th}^2}{4R_{Th}}$$

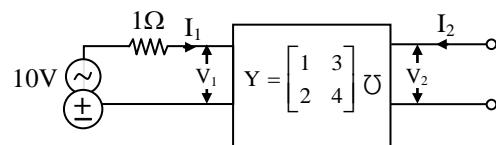Calculation of V_{Th} : (open the load resistance)



From Y-parameters

$$I_1 = V_1 + 3V_2 \quad \dots \dots \dots (1)$$

$$I_2 = 2V_1 + 4V_2 \quad \dots \dots \dots (2)$$

But $I_2 = 0$, so $-2V_1 = 4V_2$

$$V_1 = -2V_2 \quad \dots \dots \dots (3)$$

$$\text{And } I_1 = 10 - V_1$$

$$\text{From}(1), 10 - V_1 = V_1 + 3V_2$$


$$10 - 2V_1 = 3V_2$$

$$\text{From}(3), 10 - 2(-2V_2) = 3V_2$$

$$V_2 = -10V$$

Calculation of R_{Th} : (deactivate all independent sources)

if 1V is applied across a-b then

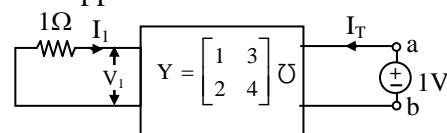

TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2020

Date of Exam : **18th January 2020**
Last Date to Apply : **31st December 2019**

Highlights:

- Get real-time experience of **GATE-20** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post **GATE** guidance sessions by experts.
- Encouraging awards for **GATE-20** toppers.

PAN INDIA

PRESENCE AVAILABLE IN MORE THAN



SSC-JE (Paper-I)

Online Test Series

Staff Selection Commission - Junior Engineer

No. of Tests : 20

Subject Wise Tests : 16 | Mock Tests - 4

Civil | Electrical | Mechanical

AVAILABLE NOW

All tests will be available till **SSC 2019 Examination**



$$I_2 = I_T$$

$$V_2 = 1V$$

From (1) & (2)

$$I_1 = V_1 + 3(1) \dots\dots\dots(4)$$

$$I_T = 2V_1 + 4(1) \dots\dots\dots(5)$$

But $V_1 = -I_1$, $I_1 = -V_1$

$$-V_1 = V_1 + 3$$


$$V_1 = \frac{-3}{2}$$

$$\text{From (5)} I_T = 2\left(\frac{-3}{2}\right) + 4$$

$$I_T = 1$$

$$R_{Th} = \frac{1}{I_T} = 1\Omega$$

∴

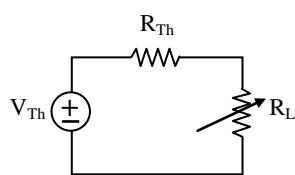

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{100}{4 \times 1} = 25 W$$

27. Ans: 175 (172 to 179)

Sol: at $10^\circ C \rightarrow$

$$R_{T_1} = R_o e^{\beta \left(\frac{1}{T} - \frac{1}{T_o} \right)}$$

$$= 10k\Omega e^{3500 \left(\frac{1}{10+273} - \frac{1}{25+273} \right)}$$

$$R_{T_1} = 18.64 k\Omega$$

At $20^\circ C$

$$R_{T_2} = R_o e^{\beta \left(\frac{1}{T_2} - \frac{1}{T_o} \right)}$$

$$= 10k\Omega \times e^{3500 \left(\frac{1}{20+273} - \frac{1}{25+273} \right)}$$

$$R_{T_2} = 12.22 k\Omega$$

$$V_{T_1} = \frac{18.64k}{18.64k + 10k} \times 5 = 3.25V$$

$$V_{T_2} = \frac{12.22k}{12.22k + 10k} \times 5 = 2.75V$$

$$\frac{\Delta V}{\Delta T} = \frac{V_{T_2} - V_{T_1}}{T_2 - T_1} = \frac{2.75 - 3.25}{20 - 10}$$

$$= -50 \left(\frac{mV}{^\circ C} \right)$$

$$V_{out} = -50 \left(\frac{mV}{^\circ C} \right) \times \left(1 + \frac{25k}{10k} \right)$$

$$V_{out} = -175 \left(\frac{mV}{^\circ C} \right)$$

28. Ans: (a)

$$\text{Sol: } \frac{E(s)}{R(s)} = \frac{\frac{1}{R(s)} \left\{ 1 - \left\{ \frac{2}{3} - \frac{3}{2} \right\} + \left\{ \frac{2}{3} \times \frac{-3}{2} \right\} \right\}}{1 - \left\{ \frac{2}{3} - \frac{3}{2} - 3 \right\} + \left\{ \frac{2}{3} \times \frac{-3}{2} \right\}}$$

$$= \frac{1 \left\{ 1 - \frac{2}{3} + \frac{3}{2} - 2 \times 3 \times \frac{1}{2} \times \frac{1}{3} \right\}}{1 - \frac{2}{3} + \frac{3}{2} + 3 - 2 \times 3 \times \frac{1}{2} \times \frac{1}{3}}$$

$$= \frac{1 + \frac{5}{6} - 1}{1 + \frac{5}{6} + 3 - 1}$$

$$\frac{E(s)}{R(s)} = \frac{5}{23}$$

29. Ans: (b)

Sol: line equation of AB is,

Here A = (1, 1) B = (3, 2)

$$y - 1 = \frac{1}{2}(x - 1) \Rightarrow y = \frac{x + 1}{2}$$

$$dy = \frac{dx}{2}$$

$$\therefore \int_C \operatorname{Re} z \, dz = \int_1^3 x(dx + idy)$$



$$= \int_1^3 x \left(dx + i \frac{dx}{2} \right) = \left(1 + \frac{i}{2} \right) \left[\frac{x^2}{2} \right]_1^3 \\ = 4 + 2i$$

30. Ans: (C)

Sol: $s \omega(s) = -\omega(s) + i_a(s)$

$$\Rightarrow \omega(s)[s+1] = i_a(s) \Rightarrow \omega(s) = \frac{i_a(s)}{s+1} \dots (1)$$

$$s i_a(s) = -\omega(s) - 10 i_a(s) + 10 U(s)$$

$$i_a(s)[s+10] + \omega(s) = 10 U(s)$$

$$i_a(s) \left[s + 10 + \frac{1}{s+1} \right] = 10 U(s) [\because \text{eq (1)}]$$

$$\Rightarrow \frac{i_a(s)}{U(s)} = \frac{10(s+1)}{s^2 + 11s + 11}$$

31. Ans: (c)

$$\frac{I}{P} = \frac{\eta e \lambda}{hc}$$

η = quantum efficiency = 0.65

λ = wavelength = 900nm

P = power = 0.5 μ W

I = unknown current in A

e = 1.6×10^{-19} C

c = 3×10^8 (m/sec)

$h = 6.624 \times 10^{-34}$ (Js)

$$I = \frac{0.5 \times 10^{-6} \times 0.65 \times 1.6 \times 10^{-19} \times 900 \times 10^{-9}}{6.624 \times 10^{-34} \times 3 \times 10^8}$$

I = 0.2355 (μ A)


Multiplication factor

$$m = \frac{10 \times 10^{-6}}{I} = \frac{10 \times 10^{-6}}{0.236 \times 10^{-6}}$$

m = 42.373 \cong 43

32. Ans: (C)

Sol:

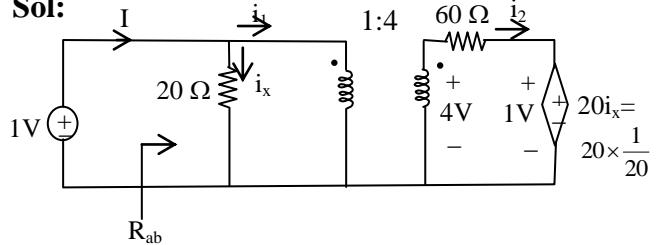

$$i_x = 1/20$$

$$i_2 = \frac{4-1}{60} = \frac{3}{60} = \frac{1}{20}$$

$$\frac{i_1}{i_2} = 4 \Rightarrow i_1 = \frac{4}{20}$$

$$I = \frac{1}{20} + \frac{4}{20} = \frac{1}{4}$$

$$R_{ab} = 4 \Omega$$

33. Ans: (d)

$$\text{Sol: } h(n) = 2^n u(n) - \left(\frac{1}{2} \right)^n u(-n-1)$$

$$\text{ROC1 is } |z| > 2 \quad \text{ROC2 is } |z| < \frac{1}{2}$$

$$\text{R.O.C. of } H(z) = R = R_1 \cap R_2 = \{ \} = \emptyset$$

\therefore There is no R.O.C. of H(z)

\therefore H(z) does not exist.

34. Ans: 25.06 (Range 24.5 to 25.5)

Sol: W = 4.5 kHz

$$NR = 2W = 9 \text{ kHz}$$

$$SR = 2(N.R) = 2 \times 9 \text{ kHz} \\ = 18 \text{ k samples / sec}$$

L = number of quantization levels = 128

Number of bits n = $\log_2 L = \log_2 128 = 7$

$$\text{SNR (dB)} = 10 \log_{10} \text{SNR}$$

$$\text{SNR} \Rightarrow 10^{15/10}$$

$$\text{SNR} = 31.62$$

$$R_b = \text{bit rate} = nf_s \\ = n \times (SR)$$



$= 7 \times 18000$
 $= 126000 \text{ bps}$
 $R_b = 126 \text{ kbps}$
 Shannon Hartley law
 $C = B \log_2 (1 + S/N)$
 B = transmission bandwidth of channel
 For error free transmission of messages
 $C \geq R_b$
 $\text{Blog}_2 (1+S/N) \geq 126 \text{ kbps}$
 $B \geq \frac{126 \text{ kbps}}{\log_2 (1+S/N)} \Rightarrow B \geq 25.06 \text{ kHz}$
 $B_{\min} = 25.06 \text{ kHz}$

35. Ans: (a)

Sol: $J_1 = X, K_1 = \bar{X}$
 from the truth table of JK flip-flop

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

When $X = 0 J_1 = 0, K_1 = 1 Q_{n+1} = 0 = X$
 When $X = 1 J_1 = 1, K_1 = 0 Q_{n+1} = 1 = X$

X	Q_1	Q_2	Q_3	Z
0	0	0	0	0
1	1	1	1	1

Finally $Z = X$, the given circuit is a shift register.

36. Ans: 71.56 (70 to 73)

Sol:

$$\begin{aligned} \frac{30\angle 0 + \bar{V}_{NS}}{-j30} + \frac{30\angle -120^\circ + \bar{V}_{NS}}{30} + \frac{30\angle 120^\circ + \bar{V}_{NS}}{30} \\ = 0 \end{aligned}$$

$$\bar{V}_{NS} \left[\frac{1}{15} + j \frac{1}{30} \right] = -30 \left[1\angle -120^\circ + 1\angle 120^\circ + j1 \right]$$

$$= -30[-1\angle 0 + j1] = 1 - j1$$

$$\bar{V}_{NS} = \frac{30(1 - j1)}{\frac{1}{15} + j \frac{1}{30}} \quad \angle \bar{V}_{NS} = -45^\circ - \tan^{-1} \frac{1}{2} = 71.56^\circ$$

37. Ans: 70 (No range)


Sol: $X(e^{j\omega}) = e^{6j\omega} - 3e^{-j2\omega} + 5e^{j\omega} + 5 - 2e^{-j6\omega} - 3e^{-j4\omega}$
 Apply IDTFT
 $x(n) = \{1, 0, 0, 0, 0, 5, 5, 0, -3, 0, -3, 0, -2\}$
 $x(4) = -3;$

$$\sum_{n=-\infty}^{\infty} |x(n)|^2 = 1 + 25 + 25 + 9 + 9 + 4$$

 $= 50 + 18 + 5 = 73$
 $x(4) + \sum_{n=-\infty}^{\infty} |x(n)|^2 = -3 + 73 = 70$

38. Ans: (d)

Sol:

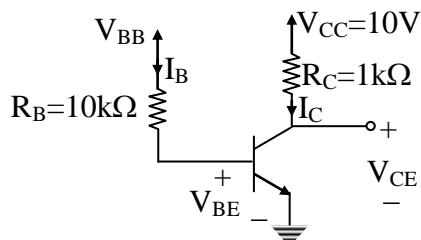

- i) Operating at the edge of saturation is obtained with $V_{CE} = 0.3V$. Thus

$$I_C = \frac{10 - 0.3}{1k\Omega} = 9.7 \text{ mA}$$

Since, at the edge of saturation, I_C and I_B are still related by β ,

$$I_B = \frac{9.7 \text{ mA}}{50} = 0.194 \text{ mA}$$

$$V_{BB} = (0.194 \times 10) + 0.7 = 2.64 \text{ V}$$

- ii) To operate deep in saturation,

$$V_{CE} = V_{CESat} \approx 0.2 \text{ V}$$

$$I_C = \frac{10 - 0.2}{1k\Omega} = 9.8 \text{ mA}$$

TEST YOUR PREP

IN A REAL TEST ENVIRONMENT

Pre GATE - 2020

Date of Exam : **18th January 2020**
Last Date to Apply : **31st December 2019**

Highlights:

- Get real-time experience of **GATE-20** test pattern and environment.
- Virtual calculator will be enabled.
- Post exam learning analytics and All India Rank will be provided.
- Post **GATE** guidance sessions by experts.
- Encouraging awards for **GATE-20** toppers.

PAN INDIA

PRESENCE AVAILABLE IN MORE THAN



SSC-JE (Paper-I)

Online Test Series

Staff Selection Commission - Junior Engineer

No. of Tests : 20

Subject Wise Tests : 16 | Mock Tests - 4

Civil | Electrical | Mechanical

AVAILABLE NOW

All tests will be available till **SSC 2019 Examination**



$$I_B = \frac{I_C}{\beta_{\text{forced}}} = \frac{9.8}{10} = 0.98 \text{mA}$$

$$V_{BB} = (0.98 \times 10) + 0.7 = 10.5 \text{V}$$

39. Ans: (a)

Sol:

ABC	D = 0	D = 1	
000	(0)	(1)	= 1 = I ₀
001	(2)	(3)	= 1 = I ₁
010	(4)	5	= \bar{D} = I ₂
011	6	7	= 0 = I ₃
100	8	9	= 0 = I ₄
101	(10)	(11)	= 1 = I ₅
110	12	13	= 0 = I ₆
111	(14)	(15)	= 1 = I ₇

40. Ans: 0.75 (No range)

Sol: From the given circuit

$$\rightarrow V_C = 2 \text{V}$$

$$I_C = \frac{10 - V_C}{R_{C1}}$$

$$R_{C1} = \frac{10 - 2}{I_C} = \frac{8}{I_C}$$

$$\rightarrow V_C = 4 \text{V}$$

$$I_C = \frac{10 - V_C}{R_{C2}}$$

$$R_{C2} = \frac{10 - 4}{I_C} = \frac{6}{I_C}$$

$$\frac{R_{C2}}{R_{C1}} = \frac{\frac{6}{I_C}}{\frac{8}{I_C}} = \frac{6}{8} = \frac{3}{4} = 0.75$$

41. Ans: (d)

Sol: $\rightarrow (A) = XXH \oplus XXH = 00H$

$$\rightarrow (HL) = 4000H$$

$$\rightarrow (SP) = 3000H$$

$$\rightarrow (A) = 35 \text{ H}$$

$$\rightarrow (M) = (4000H) = 36H$$

$$\rightarrow (A) = 35H = 0011\ 0101$$

$$(M) = 36H = 0011\ 0110$$

$$(A) = 6BH = 0110\ 1011$$

$$CY = 0, P = 0, AC = 0, Z = 0, S = 0$$

→ Decimal Adjust Accumulator

06H is added to lower digit since it is > 9

$$(A) = 6BH = 0110\ 1011$$

$$= 06H = 0000\ 0110$$

$$(A) = 71H = 0111\ 0001$$

$$CY = 0, P = 1, AC = 1, Z = 0, S = 0$$

$$(PSW) = 0111\ 0001\ 0001\ 0100$$

$$= 7114H$$

42. Ans: (a)

Sol: Output voltage of electromagnetic transducer

$$= B/V$$

$$= 1.1 \times 100 \times 10^{-3} \times 50 \times 10^{-3} = 5.5(\text{mV})$$

op-amp output voltage

$$V_0 = \frac{e_0 \times 10^6 \times 100}{10^6 + (0.1 \times 10^6)} = \frac{e_0 100}{1 + 0.1} = \frac{e_0 \times 100}{1.1}$$

$$= 5.5 \times 10^{-3} \times \frac{100}{1.1} \Rightarrow V_0 = 0.5V$$

43. Ans: (c)

Sol: To obtain the loop gain, we break the positive feedback at the positive input terminal of the op-amp where the input impedance is infinite, apply an input voltage V_i , and find its output voltage, V_0

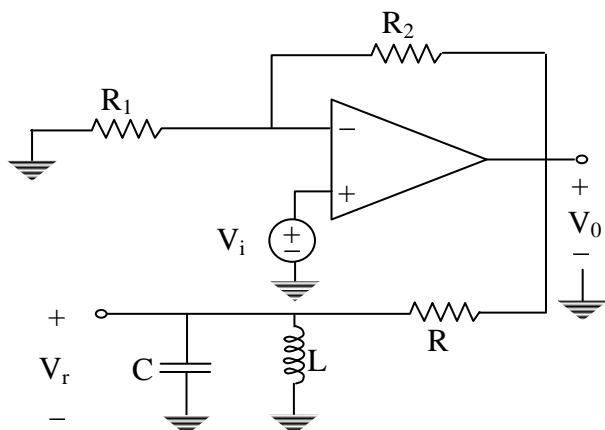


Fig. Breaking the feedback loop at the input of the op-amp

$$A(s) = \frac{V_0}{V_i} = 1 + \frac{R_2}{R_1}$$

$$\beta(s) = \frac{V_r}{V_0} = \frac{s \frac{1}{CR}}{s^2 + s \frac{1}{CR} + \frac{1}{LC}}$$

$$A(s)\beta(s) = \frac{s \frac{1}{CR} \left(1 + \frac{R_2}{R_1}\right)}{s^2 + s \frac{1}{CR} + \frac{1}{LC}}$$

$$A(j\omega)\beta(j\omega) = \frac{j \frac{\omega}{CR} \left(1 + \frac{R_2}{R_1}\right)}{\left(-\omega^2 + \frac{1}{LC}\right) + j \frac{\omega}{CR}}$$

From this expression, we see that the phase angle of $A(j\omega)\beta(j\omega)$ will be zero at the value of ω that makes the real part of denominator zero,

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

At this frequency, the magnitude of the loop gain is given by


$$|A(j\omega_0)\beta(j\omega_0)| = 1 + \frac{R_2}{R_1} = 1 + \frac{10k}{1k} = 11$$

44. Ans: 1

Sol: $\text{Sinc}(t) \leftrightarrow \text{rect}(f)$


$\text{Sinc}(t/2) \leftrightarrow 2 \text{ rect}(2f)$

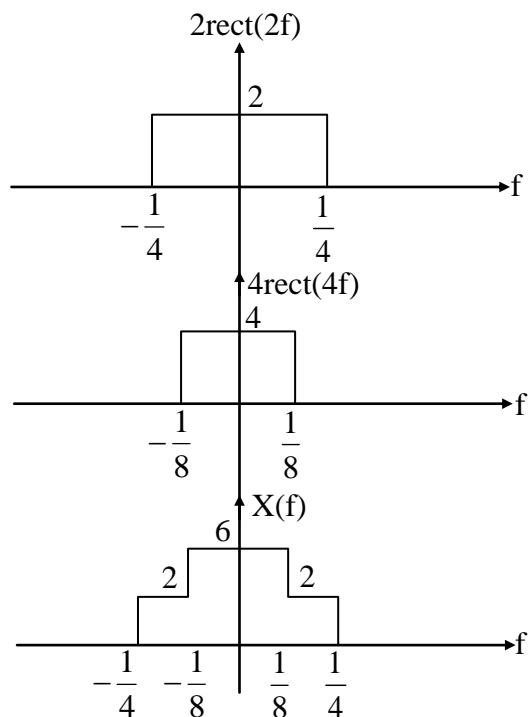$\text{Sinc}(t/4) \leftrightarrow 4 \text{ rect}(4f)$



Given $h(t) = A \text{ Sinc}(\alpha t)$
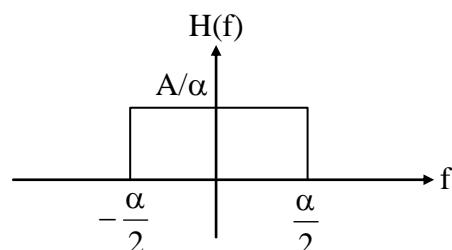
$$H(f) = \frac{A}{\alpha} \text{ rect}\left(\frac{f}{\alpha}\right)$$



$Y(f) = X(f) \cdot H(f) = X(f)$ only when

$$\frac{-\alpha}{2} = \frac{-1}{4} \Rightarrow \alpha = \frac{1}{2}$$

$$\frac{A}{\alpha} = 1 \Rightarrow A = \alpha = \frac{1}{2}$$

$$A + \alpha = 1$$

HEARTY CONGRATULATIONS TO OUR ESE - 2019 TOP RANKERS



KARTIKEYA SINGH EE AIR 10



RAJAT SONI E&T AIR 10



HARSHAL BHOSALE ME AIR 10



ABUZAR GAFFARI CE AIR 10



SHAMBHANI EE AIR 2



ANKUR MANLA E&T AIR 2



SAHIL GOYAL ME AIR 2



ABHISHEK KHANDO EE AIR 3



ROHIT KUMAR E&T AIR 3



KUMAR CHANDAN ME AIR 3



AMARJEET CE AIR 3



ANKIT TAYAL EE AIR 4



AMIR KHAN E&T AIR 4



SAURAV ME AIR 4



AMAN GULIA CE AIR 4



KUMAN PURIYAN EE AIR 5



RISHABH CHANDRA CE AIR 5



NITISH LALWANI EE AIR 6



PUSHPAK ME AIR 6



KARAN SINGH CE AIR 6



KARTIKEY SINGH EE AIR 7



RAHUL JAIN E&T AIR 7



MANISH RAJPUT ME AIR 7



KULDEEP KUMAR E&T AIR 8



HEMANT KUMAR ME AIR 8



TUSHAR KUMAR CE AIR 8




DEEPITA ROY EE AIR 9



BHUPESH KARMAKAR E&T AIR 9



S. BABAPARA ME AIR 9

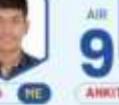

ANKIT KUMAR CE AIR 9



ANKALI SHARMA EE AIR 10



GEETA DEEWALI E&T AIR 10



SUMIT BHANDOO ME AIR 10

and many more...

TOTAL SELECTIONS in Top 10: **33**

(EE: **9**, E&T: **8**, ME: **9**, CE: **7**) and many more...



DIGITAL CLASSES

for

ESE 2020/2021

General Studies &
Engineering Aptitude

GATE 2020/2021


Computer Science &
Information Technology

Access the Course at



45. Ans: 6.83 (6.75 to 6.9)

Sol:

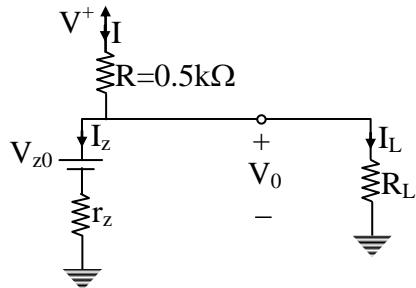

$$V_z = V_{z0} + r_z I_z$$

$$6.8 = V_{z0} + (20\Omega \times 5\text{mA})$$

$$\Rightarrow V_{z0} = 6.7\text{V} \quad (1)$$

With no load connected, the current through the zener is given by

$$I_z = I = \frac{V^+ - V_{z0}}{R + r_z} = \frac{10 - 6.7}{0.5\text{k} + 0.02\text{k}}$$

$$I_z = 6.35\text{mA} \quad (2)$$

$$\rightarrow V_0 = V_{z0} + I_z r_z = 6.7 + (6.35 \times 0.02) \\ = 6.83\text{V}$$

46. Ans: 3750

Sol: Give data:

$$\lambda = 9000\text{A}^\circ$$

$$\Delta = 2\%$$

$$\mu_{\text{core}} = 1.6 = n_1$$

$$\pi = 3$$

$$V = 8$$

$$V = \frac{2\pi r}{\lambda} n_1 \sqrt{2\Delta}$$


$$8 = \frac{2 \times 3 \times r}{9000 \times 10^{-10}} \times 1.6 \sqrt{2 \times \frac{2}{100}}$$

$$r = 3750\text{nm}$$

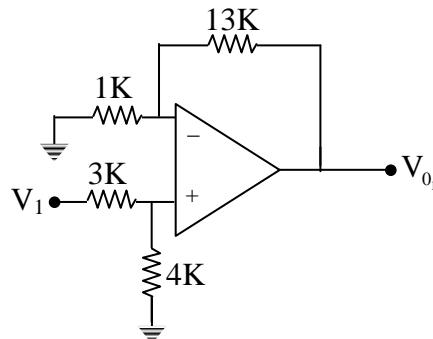47. Ans:-28

Sol: Using superposition principle,

Case (1): consider only V_1 and make $V_2 = 0$




$$\text{So, } V_{01} = V_+ \left(1 + \frac{13}{1} \right) = 14(V_+)$$

$$\text{Now, } V_+ = V_1 \left(\frac{4\text{K}}{7\text{K}} \right) = \frac{4V_1}{7}$$

$$\text{So, } V_{01} = 14 \left(\frac{4V_1}{7} \right) = 8V_1$$

Case (2):

Consider only V_2 and make $V_1 = 0$

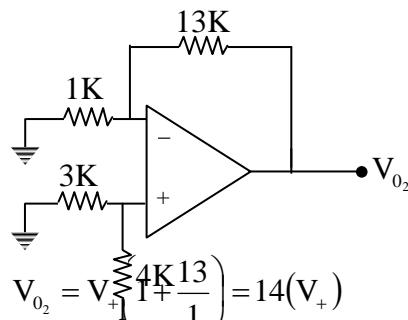

$$V_{02} = V_+ \left(1 + \frac{13}{1} \right) = 14(V_+)$$

$$\text{Now, } V_+ = \frac{V_2(3\text{K})}{7\text{K}} = \frac{3V_2}{7}$$

$$\text{So, } V_{02} = 14 \left(\frac{3V_2}{7} \right) = 6V_2$$

So, overall output voltage $V_0 = V_{01} + V_{02}$

$$\text{So, } V_0 = 8V_1 + 6V_2$$

On comparing A = 8, B = 6



$$\text{So, } (B + A)(B - A) = (6 + 8)(6 - 8) \\ = -28$$


48. Ans: 4 (No range)

$$\text{Sol: } X(k) = \sum_{n=0}^{N-1} x(n) e^{-j2\pi kn/N} \\ = \sum_{n=0}^{\frac{N}{2}-1} x(2n) e^{-j2\pi k(2n)/N} + \sum_{n=0}^{\frac{N}{2}-1} x(2n+1) e^{-j2\pi k(2n+1)/N} \\ = \sum_{n=0}^{\frac{N}{2}-1} x(2n) W_N^{kn} + W_N^k \sum_{n=0}^{\frac{N}{2}-1} x(2n+1) W_N^{kn} \\ X(0) = \sum_{n=0}^{\frac{N}{2}-1} x(2n) W_{N/2}^0 + W_N^0 \sum_{n=0}^{\frac{N}{2}-1} x(2n+1) W_{N/2}^0$$

$$X(0) = \sum_{n=0}^{\frac{N}{2}-1} x(2n) + \sum_{n=0}^{\frac{N}{2}-1} x(2n+1) \\ X(N/2) = \sum_{n=0}^{\frac{N}{2}-1} x(2n) W_{N/2}^{Nn} + W_N^{\frac{N}{2}} \sum_{n=0}^{\frac{N}{2}-1} x(2n+1) W_{N/2}^{Nn} \\ = \sum_{n=0}^{\frac{N}{2}-1} x(2n) - \sum_{n=0}^{\frac{N}{2}-1} x(2n+1) \\ X(0) + X(N/2) = 2 \sum_{n=0}^{\frac{N}{2}-1} x(2n) \\ \Rightarrow \sum_{n=0}^3 x(2n) = \frac{1}{2}[X(0) + X(N/2)] = \frac{1}{2}[X(0) + X(4)] \\ = \frac{1}{2}[(0 + 8)] = 4$$

49. Ans: 25 (No range)

Sol:

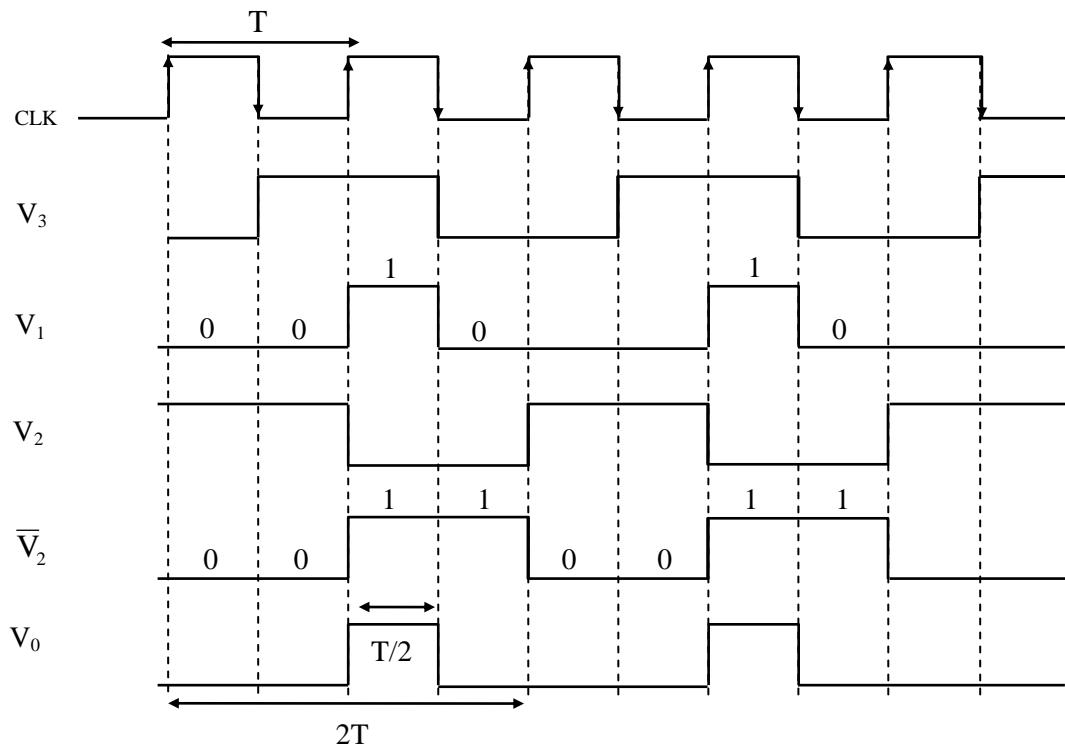


$$\text{Duty cycle} = \frac{T}{2T} \times 100 = 25\%$$



50. Ans: (c)

Sol:

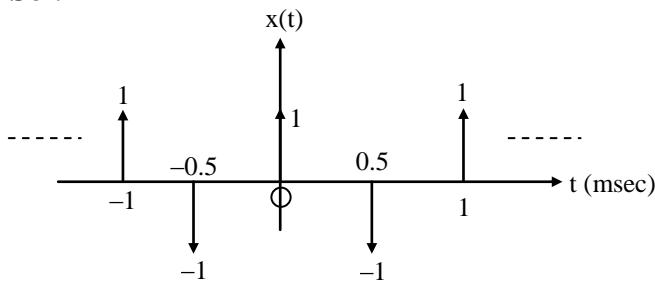

$$C_n = \frac{1}{T_0} \int_0^{T_0} x(t) e^{-jn\omega_0 t} dt$$

$$C_n = \frac{1}{1 \times 10^{-3}} \left[\int_0^1 x(t) e^{-jn\omega_0 t} dt \right]$$

$$C_n = 10^3 [1 - e^{-jn\omega_0 (0.5 \times 10^{-3})}]$$

$$C_n = 10^3 \left[1 - e^{-jn \left(\frac{2\pi}{1 \times 10^{-3}} \right) (0.5 \times 10^{-3})} \right]$$

$$C_n = 10^3 [1 - e^{-jn\pi}] = 1000 [1 - (-1)^n]$$

Fourier transform of periodic signal is


$$X(\omega) = 2\pi \sum_{n=-\infty}^{\infty} C_n \delta(\omega - n\omega_0)$$

$$X(\omega) = 2000\pi \sum_{n=-\infty}^{\infty} [1 - (-1)^n] \delta(\omega - 2000n\pi)$$

$$X(\omega) = 2000\pi [\dots, 2\delta(\omega + 2000\pi) + 2\delta(\omega - 2000\pi) + \dots]$$

$$x(t) = 4000\pi [\delta(\omega + 2000\pi) + \delta(\omega - 2000\pi) + \dots]$$
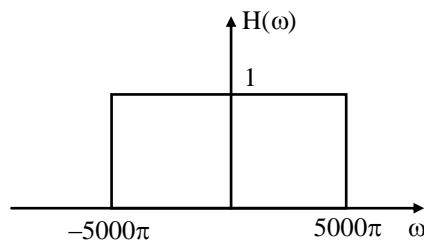
$$X(\omega) = 4000[\cos(2000\pi t) + \cos(6000\pi t) + \dots]$$



The output of low pass filter is
 $y(t) = 4000 \cos(2000\pi t)$

51. Ans: 1200

$$\text{Sol: } m(t) = \sin(250\pi t) + \cos(250\pi t) = \sqrt{2} \cos[250\pi t - 45^\circ]$$

$$f_m = \frac{250\pi}{2\pi} = 125 \text{ Hz}$$

$$\begin{aligned} \text{SR} &= 1.2 (\text{NR}) \\ &= 1.2 \times 2 \times 125 \\ &= 300 \text{ samples/sec} \end{aligned}$$

Step size $\Delta = 0.4$

$$\frac{\Delta}{2} = Q_e = \frac{(V_{\max} - V_{\min})}{2^n};$$

$$0.40 = \frac{\sqrt{2} - (-\sqrt{2})}{2^n}$$

$$2^n = \frac{2\sqrt{2}}{0.4}$$

$$n = 3.82 \Rightarrow n = 4$$

$$\therefore R_b = n f_s = 4 \times 300 \text{ bps} = 1200 \text{ bps}$$

$$R_b = 1200 \text{ bps}$$

52. Ans:(a)

Sol: The energy of each photon will be

$$hv = h \frac{c}{\lambda_0} = \frac{(6.6 \times 10^{-34}) \times (3 \times 10^8)}{0.5 \times 10^{-6}} = 4 \times 10^{-19} \text{ J}$$



So, the number of photons emitted per second = $\frac{1\text{W}}{4 \times 10^{-19}\text{J}} = 2.5 \times 10^{18}$

53. Ans: (b)

Sol: For eigen vector, $AX = \lambda X$

$$\begin{bmatrix} 1 & 1 & 3 \\ 1 & 5 & 1 \\ 3 & 1 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = (-2) \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

$$\Rightarrow x_1 + x_2 + 3x_3 = -2x_1 \rightarrow (1)$$

$$\Rightarrow x_1 + 5x_2 + x_3 = -2x_2 \rightarrow (2)$$

$$\Rightarrow 3x_1 + x_2 + x_3 = -2x_3 \rightarrow (3)$$

$$(1) \Rightarrow 3(x_1 + x_3) = -x_2 \rightarrow (4)$$

$$(2) \Rightarrow x_1 + x_3 = -7x_2 \rightarrow (5)$$

$$(3) \Rightarrow 3(x_1 + x_3) = -x_2 \rightarrow (6)$$

$$\text{From (4)&(5)} \rightarrow x_1 + x_3 - 7(3(x_1 + x_3)) = 0$$

$$\Rightarrow x_1 + x_3 = 0$$

$$\text{Suppose } x_1 = k \Rightarrow x_3 = -k$$

$$\therefore x_2 = -3(x_1 + x_3) = 0$$

$$\therefore \text{Eigen vector } \begin{bmatrix} k \\ 0 \\ -k \end{bmatrix}$$

$$\text{For } k = 1 \Rightarrow \text{eigen vector} = \begin{bmatrix} 1 \\ 0 \\ -1 \end{bmatrix}$$

54. Ans: 45°

$$\text{Sol: } \left| \frac{(50)\sqrt{50}}{(j\omega_{gc} + 5)^3} \right| = 1$$

$$\left(\sqrt{\omega_{gc}^2 + 5^2} \right)^3 = 50\sqrt{50}$$

$$\omega_{gc} = 5 \text{ rad/sec}$$

$$PM = 180^\circ + \angle G(j\omega_{gc})H(j\omega_{gc})$$

$$= 180^\circ - 3 \tan^{-1} \frac{\omega_{gc}}{5} = 180 - 135 = 45^\circ$$

55. Ans: 0.2 No range

Sol: Given that $\frac{dy}{dx} = x^3 - 2y$ ($\because \frac{dy}{dx} = f(x, y)$)

with $y(0) = 0.25$ ($\because y(x_0) = y_0$)

Let $x_0 = 0, y_0 = 0.25$ & $h = 0.1$

Then $x_1 = x_0 + h = 0.1$

The formula for Euler's forward method is

$$y(x_1) \approx y_1 = y_0 + h f(x_0, y_0)$$

$$\Rightarrow y(0.1) \approx y_1 = 0.25 + (0.1)(x_0^3 - 2y_0)$$

$$\Rightarrow y(0.1) \approx y_1 = 0.25 + (0.1)[0 - 2(0.25)]$$

$$\therefore y(0.1) \approx y_1 = 0.25 - (0.1)(0.5) \\ = 0.25 - 0.05 = 0.2$$

56. Ans: (a)

Sol: The right choice is 'on'. 'Tell on' means 'to affect'. 'Tell against' means 'to go against'. 'Tell of' means 'to tell about something'.

57. Ans: (c)

Sol: 'is' tired verb must agree with the first subject when 'as well as' is used.

58. Ans: (a)

59. Ans: (d)

$$\text{Sol: } L = \frac{5}{2} B$$

$$\text{Area} = L \times B = 1000$$

$$L \times \frac{2L}{5} = 1000$$

$$L^2 = 2500 \Leftrightarrow L = 50 \text{ m}$$

60. Ans: (b)

Sol: Supplement of $80^\circ = 180^\circ - 80^\circ = 100^\circ$.

SSC-JE (Paper-II) MAINS 2018

OFFLINE TEST SERIES

Streams: Civil | Electrical | Mechanical

FULL LENGTH MOCK TEST-1

Exam Date: **01.12.2019**

Exam Timing: **6:00 pm to 8:00 pm**

FULL LENGTH MOCK TEST-2

Exam Date: **15.12.2019**

Exam Timing: **6:00 pm to 8:00 pm**

- All tests will be conducted in **Question Paper Booklet** format.
- Test Series will be conducted at all our centres.

Hyderabad | Delhi | Pune | Bhubaneswar | Bengaluru | Chennai | Vijayawada | Vizag | Tirupathi | Kukatpally | Kollam | Ahmedabad

 040 - 48539866 / 040 - 40136222  testseries@aceenggacademy.com

ISRO ONLINE TEST SERIES

No. of Tests : 15

Subject Wise Tests : 12 | Mock Tests : 3

Indian Space Research Organisation (ISRO)
Recruitment of Scientist/Engineer 'SC'

ELECTRONICS | MECHANICAL | COMPUTER SCIENCE

Starts from **5th November 2019**

All tests will be available till **12-01-2020**.

 © 040 - 48539866 / 040 - 40136222  testseries@aceenggacademy.com




61. Ans: (d)

Sol: Let the height of tower be 'PQ', 'QR' be the length of shadow to tower in ΔPQR .


$$\tan \theta = \frac{PQ}{QR} = \frac{h}{4h}$$
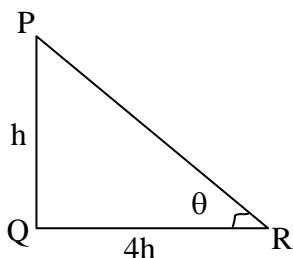
$$\therefore \theta = \tan^{-1}\left(\frac{1}{4}\right)$$



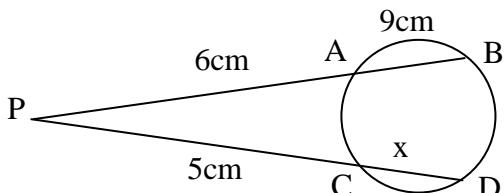62. Ans: (a)

Sol: If two chords of a circle, intersect inside a circle (outside a circle) at any point. Then,



$$PA \times PB = PC \times PD$$

$$\Rightarrow 6 \times 15 = 5 \times (x + 5)$$

$$\Rightarrow x + 5 = 18 \Rightarrow x = 13 \text{ cm}$$

63. Ans: (a)

Sol: Total time between 10 pm to 6 am = 8 hours
% time spent in Light sleep or in Extreme sleep = $30 + 25 = 55\%$

$$\Rightarrow \text{Time spent in Light sleep or in Extreme sleep} = \frac{55}{100} \times 8$$

$$\Rightarrow \frac{22}{5} = 4.4 \text{ hours}$$

64. Ans: (b)

Sol: Total cost of mobiles = 99×15000
= Rs. 14,85,000

$$\text{Total cost of cameras} = 53 \times 13000$$

$$= \text{Rs. } 6,89,000$$

$$\text{Total cost of TVs} = 29 \times 59000$$

$$= \text{Rs. } 17,11,000$$

$$\text{Total cost of Refrigerator} = 21 \times 56000$$

$$= \text{Rs. } 11,76,000$$

$$\text{Total cost of AC} = 97 \times 25000$$

$$= \text{Rs. } 24,25,000$$

$$\begin{aligned} \text{Total cost} &= 14,85,000 + 6,89,000 \\ &+ 17,11,000 + 11,76,000 \\ &+ 24,25,000 = \text{Rs. } 74,86,000 \end{aligned}$$

Total cost in lakhs = Rs. 74.86 lakhs

65. Ans: (a)

Sol: An assumption is an unstated premise. So, we are looking for something that is implied in the argument, and if wrong, will undermine the argument. All that the speaker implies is that Josh is efficient because he has twenty years of practice, and so answer (A) is correct.