



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Branch: Electronics & Communication Engineering - SOLUTIONS

01. Ans: 496 (No Range)

Sol: For n-bit comparator,
Number of combinations for which $A > B$
is $\frac{2^{2n} - 2^n}{2}$


Here $n = 5$. (It is a 4 bit magnitude comparator)

$$= \frac{2^{2 \times 5} - 2^5}{2} = 496$$

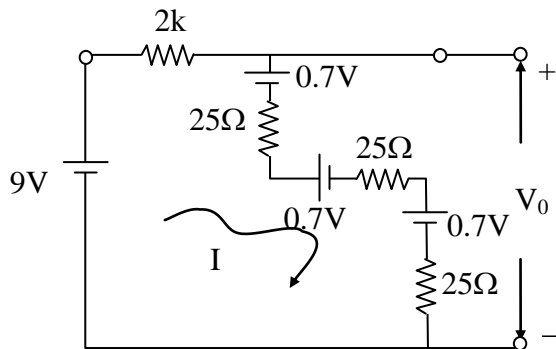02. Ans: (a)

Sol: In the given circuit D_1 , zener & $D_4 \rightarrow F.B$
 D_3 & $D_2 \rightarrow R.B \rightarrow O.C$

When zener F.B it behaves like a pn diode



Then the equation for the circuit is
 $-9 + I(2k) + 0.7 + I(25) + 0.7$
 $+ I(25) + 0.7 + I(25) = 0$

From the above circuit I is given by

$$I = 3.325 \text{ mA}$$

$$\begin{aligned} V_0 &= (0.7 + 25I)3 \\ &= 2.1 + 75 \times 3.325 \times 10^{-3} \\ &= 2.1 + 0.249 \\ &= 2.35 \text{ V} \end{aligned}$$

03. Ans: (a)

Sol: For series RLC transient current to be oscillatory

$$\xi < 1$$

$$\frac{R}{2} \sqrt{\frac{C}{L}} < 1$$

$$R < 2 \sqrt{\frac{L_{eq}}{C_{eq}}}$$

$$R < 2 \sqrt{\frac{1}{9}}$$

$$R < \frac{2}{3} \Omega$$

04. Ans: 1 (No range)

Sol: Let $A = \begin{bmatrix} 1 & 2 & 0 \\ 0 & 1 & 3 \\ 0 & 0 & 1 \end{bmatrix}$

A is the upper triangular matrix eigen value is 1 only

Consider $(A - I) = \begin{bmatrix} 0 & 2 & 0 \\ 0 & 0 & 3 \\ 0 & 0 & 0 \end{bmatrix}$

Clearly rank of $(A - I) = 2$

Geometric multiplicity of eigen value 1 =

No. of linearly independent eigen vectors

$$= n - r$$

$$= 3 - 2 = 1$$

05. Ans: 10.5 (no range)

Sol: The average current

$$I_{CC} = \frac{I_{CCH} + I_{CCL}}{2} = \frac{2.4 + 1.8}{2} = 2.1 \mu A$$

The average power dissipation

$$P_D = V_{CC} \times I_{CC} = 5V \times 2.1 \mu A = 10.5 \mu W$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

ESE - MAINS

Classes Start from: **13th FEB 2020**



@ DELHI



Students who Qualify in Prelims
can avail **100 % Fee Waiver**



@ HYDERABAD

ESE-2018, 2019 Prelims Qualified Students are also eligible for Fee Discounts



/aceacademy



/ACE_Enggacademy




/aceenggacademy

- H.O. # 4-1-1236/1/A, Sindhu Sadan, King Koti Road, Abids, Hyderabad - 500001, Telangana, India.
- Ph: 040-23234418/19/20 , 040-24750437.
- Email: hyderabad@aceenggacademy.com
- **www.aceenggacademy.com**



06. Ans: (d)

Sol:

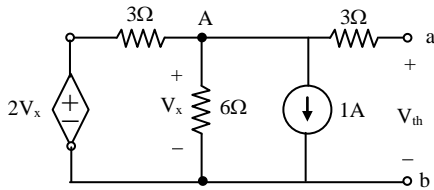

Current flowing through 3Ω is zero so $V_{th} = V_x$


Apply KCL at node A, then

$$\frac{V_x - 2V_x}{3} + \frac{V_x}{6} + 1 = 0$$

$$-2V_x + V_x + 6 = 0$$

$$V_x = 6V$$

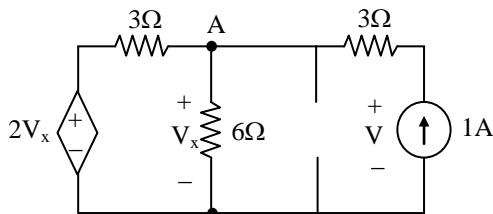R_{th} can be find out by exciting the circuit with 1A, replace all independent sources by their internal resistances



By KCL at node A

$$\frac{V_x}{6} + \frac{(V_x - 2V_x)}{3} - 1 = 0$$

$$V_x - 2V_x - 6 = 0$$

$$V_x = -6V$$

$$V = 3 + V_x = 3 - 6 = -3V$$

$$R_{th} = \frac{V}{I} = \frac{-3}{1} = -3\Omega$$

07. Ans: (c)

$$\begin{aligned} \text{Sol: } \% \eta_{FM} &= (1 - J_0^2(\beta)) \times 100 \\ &= (1 - 0.5^2) \times 100 \\ &= 75\% \end{aligned}$$

08. Ans: (a)

Sol: We have

$$\begin{aligned} \rho_v &= \nabla \cdot \vec{D} = \frac{\partial D_z}{\partial z} = \frac{\partial}{\partial z} (z^3 \rho \cos^2 \phi) \\ &= 3z^2 \rho \cos^2 \phi \end{aligned}$$

$$\text{Now, } Q = \int_V \rho_v dv$$

$$\begin{aligned} &= \int_V 3z^2 \rho \cos^2 \phi \times \rho d\phi d\rho dz \\ &= 3 \int_{z=-2}^2 z^2 dz \int_{\phi=0}^{2\pi} \cos^2 \phi d\phi \int_{\rho=0}^1 \rho^2 d\rho \\ &= \frac{3}{3} \times 16 \times \pi \times \frac{1}{3} = \frac{16}{3} \pi C \end{aligned}$$

09. Ans: (a)

Sol: Given $x(t) = 3e^{-t}u(t)$, $h(t) = 2e^{-2t}u(t)$

Apply L.T

$$X(s) = \frac{3}{s+1}, H(s) = \frac{2}{s+2}$$

$$Y(s) = X(s)H(s) = \frac{6}{(s+1)(s+2)}$$

$$Y(s) = \frac{6}{s+1} - \frac{6}{s+2}$$

Apply ILT

$$y(t) = 6 [e^{-t} - e^{-2t}]u(t)$$

10. Ans: (d)

$$\text{Sol: } F = \Sigma m(0,2,3,4,6)$$

$$= \Sigma m(1,5,7)$$

$$= \Pi M(0,2,3,4,6)$$

QP		R			
		00	01	11	10
R	0	0		0	0
	1	0			0

$$F = P[R + \overline{Q}]$$

11. Ans: 7 (No range)

$$\text{Sol: } d_{\min} = 2t + 1$$

$$t = 3$$

$$d_{\min} = 7$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



Hyderabad | Ahmedabad | Pune | Delhi | Bhubaneswar | Bangalore | Chennai | Lucknow | Visakhapatnam | Vijayawada | Tirupati | Kolkata

Head Office Address: # 4-1-1236/1/A, Sindhu Sadan, King Koti, Abids, Hyderabad - 500001, Telangana, India.

SUMMER

SHORT TERM BATCHES GATE + PSUs - 2021

@ HYDERABAD

Streams: EC, EE, ME, CE, CSIT, IN & PI

28th April, 5th May,
10th May, 17th May, 25th May,
1st June, 8th June, 2020

Course Duration: 55 to 60 Days

☎ 040-23234418/19/20, 040-24750437

✉ hyderabad@aceenggacademy.com

@ DELHI

Streams: EC, EE, ME, CE, IN & PI

10th & 20th
May 2020

Course Duration: 60 to 70 Days

☎ 7838971777 (Call or Whatsapp)

✉ delhi@aceenggacademy.com

Early Bird Offer Rs. 3,000/- Register before 31st March 2020

Upcoming Batches @ HYDERABAD

GATE+PSUs-2021

Spark Batches : 10th May, 8th & 23rd June 2020.

Regular Batches : 26th April, 10th, 24th May, 8th, 23rd June, 7th, 22nd July,
5th & 20th August 2020.

ESE+GATE+PSUs-2021

Spark Batches : 10th May, 8th & 23rd June 2020.

Regular Batches : 29th March, 26th April, 10th, 24th May,
8th, 23rd June & 7th July 2020.

Upcoming Batches @ DELHI

GATE+PSUs-2021

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

Regular Batches : 17th Feb, 7th March, 10th & 20th May 2020.

ESE+GATE+PSUs-2021

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

Regular Batches : 17th Feb, 7th March, 10th & 20th May 2020.

GATE+PSUs-2022

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

ESE+GATE+PSUs-2022

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

SSC-JE Batches @ Hyderabad

New Batch Starts from: 10th May 2020

for Civil, Mechanical & Electrical



Scan QR Code for
Upcoming Batches
Details

☎ www.aceenggacademy.com


follow us on:





12. Ans: 6 (No range)

Sol:

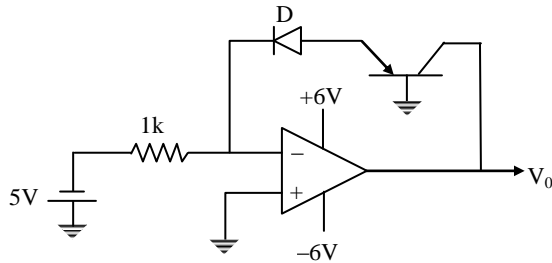

In this circuit diode tries to conduct but the transistor which is in cut-off region does not allow

any current and hence negative feedback does not exist.

Therefore op-amp acts as comparator. So output voltage $V_0 = +6V$

13. Ans: (a)

Sol: We have for lossy medium

$$|\eta| = \frac{\sqrt{\frac{\mu}{\epsilon}}}{\left[1 + \left(\frac{\sigma}{\omega\epsilon}\right)^2\right]^{1/4}} \quad \text{and} \quad \tan 2\theta_n = \frac{\sigma}{\omega\epsilon}$$

For good conductor

$$\frac{\sigma}{\omega\epsilon} \gg 1$$

$$\text{So, } |\eta| = \frac{\sqrt{\frac{\mu}{\epsilon}}}{\left(\left(\frac{\sigma}{\omega\epsilon}\right)^2\right)^{1/4}} = \frac{\sqrt{\frac{\mu}{\epsilon}}}{\sqrt{\frac{\sigma}{\omega\epsilon}}} = \sqrt{\frac{\mu}{\epsilon}} \times \sqrt{\frac{\omega\epsilon}{\sigma}} = \sqrt{\frac{\omega\mu}{\sigma}}$$

$$\theta_n = \frac{1}{2} \tan^{-1}\left(\frac{\sigma}{\omega\epsilon}\right) = \frac{1}{2} \times 90^\circ = 45^\circ \quad \left(\because \frac{\sigma}{\omega\epsilon} \gg 1\right)$$

For good conductor skin depth

$$\delta = \frac{1}{\alpha} = \frac{1}{\beta} = \frac{1}{\sqrt{\frac{\omega\mu\sigma}{2}}}$$

So, intrinsic impedance

$$\begin{aligned} \eta &= |\eta| e^{j\theta_n} \\ &= \sqrt{\frac{\omega\mu}{\sigma}} e^{j\pi/4} \\ &= \sqrt{\frac{\omega\mu\sigma}{2}} \times \frac{1}{\sigma} \times \sqrt{2} e^{j\pi/4} \\ &= \frac{1}{\delta} \times \frac{1}{\sigma} \times \sqrt{2} \times e^{j\pi/4} \\ &= \frac{1}{\sigma\delta} \times \sqrt{2} \left(\cos \frac{\pi}{4} + j \sin \frac{\pi}{4} \right) \\ &= \frac{1}{\sigma\delta} \times \sqrt{2} \left(\frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \right) \\ &= \frac{1}{\sigma\delta} (1 + j) \end{aligned}$$

14. Ans: 0 (No range)

$$\text{Sol: } \text{Grad}(\ln r) = \frac{1}{r} \frac{1}{r} \vec{r} = \frac{\vec{r}}{r^2}$$

$$\begin{aligned} \text{Curl}(r^2 \text{ grad } \ln r) &= \text{curl} \left(r^2 \frac{\vec{r}}{r^2} \right) \\ &= \text{curl}(\vec{r}) = 0 \end{aligned}$$

15. Ans: 0.4 (No range)

$$\begin{aligned} \text{Sol: } \frac{4s+10}{s} &= 4 + \frac{10}{s} = 4 \left[1 + \frac{10}{4s} \right] \\ &= 4 \left[1 + \frac{1}{\frac{4}{10}s} \right] \\ &= 4 \left[1 + \frac{1}{0.4s} \right] \\ &= 4 \left[1 + \frac{1}{T_I s} \right] \end{aligned}$$

$$\therefore T_I = \text{reset time} = 0.4 \text{ sec}$$

16. Ans: 53 (No range)

$$\begin{aligned} \text{Sol: } V(2x + 3y) &= 2^2 V(x) + 3^2 V(y) \\ &= (4 \times 2) + (9 \times 5) \\ &= 53 \end{aligned}$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

48
ALL INDIA
1st RANKS IN GATE

15
ALL INDIA
1st RANKS IN ESE

Hyderabad | Ahmedabad | Kothapet | Kukatpally | Delhi | Pune | Bhubaneswar | Lucknow | Bengaluru | Chennai | Vijayawada | Vizag | Tirupathi | Kolkata

ESE / GATE / PSUs LONG TERM PROGRAM @ HYDERABAD

Batches Start From



19th JAN 2020



25th FEB 2020

Streams Offered : EC | EE | ME | CE | CSIT | IN & PI


MORNING BATCHES



EVENING BATCHES



WEEKEND BATCHES

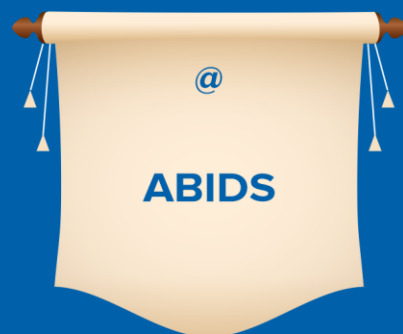

COURSES OFFERED:

- Classroom Coaching
- Postal Coaching
- Online Test Series
- Interview Guidance
- Digital Classes

New Batches for

ESE + GATE + PSUs - 2022

GATE + PSUs - 2022

Starts from:

19th JAN 2020

25th FEB 2020

New Batches for

ESE + GATE + PSUs - 2021

Morning Batches @ Abids

28th DEC & 19th JAN 2020



Scan QR CODE for
New Batch Details

Hearty Congratulations to our **ESE 2019 Top Rankers**



our **GATE-2019 Rankers**



ABIDS

KUKATPALLY

DILSUKHNAGAR

☎ 040-23234418,19,20, 040-24750437

☎ 040-40199966, 93476 99966

☎ 040-40209345, 040-40044451

www.aceenggacademy.com

follow us on:





17. Ans: 5 (No range)

Sol: $Z_{11} = 6\Omega, Z_{12} = Z_{21} = 4\Omega$

For symmetrical network, $Z_{11} = Z_{22} = 6\Omega$

ABCD parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

Now from Z – parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 = 6I_1 + 4I_2 \dots\dots (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 = 4I_1 + 6I_2 \dots\dots (2)$$

By putting $V_2 = 0$ in equation (2)

$$4I_1 = -6I_2$$

Put value of I_1 in equation (1) than

$$V_1 = 6 \left(-\frac{6}{4} I_2 \right) + 4I_2$$

$$= I_2 \left[\frac{-36}{4} + 4 \right] = -5I_2$$

$$\text{So } \frac{V_1}{I_2} = -5$$

$$B = -(-5) = 5\Omega$$

18. Ans: (b)

Sol: Given $f_i = 100 \text{ kHz}$

$$\text{Frequency at A} = f_A = \frac{100\text{kHz}}{10} = 10\text{kHz}$$

$$\text{Frequency at B} = f_B = \frac{10\text{kHz}}{20} = 500\text{Hz}$$

$$\text{Frequency at C} = f_C = \frac{500\text{Hz}}{16} = 31.25\text{Hz}$$

$$\text{Frequency at D} = f_D = \frac{31.25\text{Hz}}{8} = 3.9\text{Hz}$$

19. Ans: (d)

Sol: Bag -1

Bag- 2

5 Red

4 Red

7 Green

8 Green

$$\begin{aligned} \text{By total probability} &= \frac{1}{2} \times \frac{7}{12} + \frac{1}{2} \times \frac{8}{12} \\ &= \frac{15}{24} \end{aligned}$$

20. Ans: 36 (No range)

Sol: To get the peak current both NMOS and PMOS are operated in saturation at switching threshold $V_m = \frac{V_{DD}}{2}$ and the peak current is given by

$$\begin{aligned} I_{\text{peak}} &= \frac{1}{2} \mu_n C_{\text{ox}} \left(\frac{W}{L} \right)_n \left(\frac{V_{DD}}{2} - V_{tn} \right)^2 \\ &= \frac{1}{2} \times 300 \times 10^{-6} \times 1.5 \times (0.9 - 0.5)^2 \\ &= 36\mu\text{A} \end{aligned}$$

21. Ans: (d)

Sol: $G = kD$

$$= k \times \frac{4\pi}{\lambda^2} \times A_e \quad (k \text{ is the efficiency factor})$$

$$= 1 \times \frac{4\pi}{\lambda^2} \times \frac{\pi}{4} 3^2 \quad (\text{for loss less antenna } k=1)$$

$$= \frac{9\pi^2}{\lambda^2}$$

$$= \frac{9\pi^2}{(1)^2} \quad (\because \lambda = \frac{3 \times 10^8}{300 \times 10^6} = 1\text{m})$$

22. Ans: (c)

$$\text{Sol: } S_{AM}(t) = 10 \cos(198\pi t) + 40 \cos(200\pi t) + 10 \cos(202\pi t)$$

Carrier term is $= 40 \cos(200\pi t)$

$$A_C = 40, f_C = 100$$

LSB term: $10 \cos(198\pi t)$

$$\frac{A_C \mu}{2} = 10 \quad f_C - f_m = 99$$

$$\mu = \frac{2 \times 10}{40} = 0.5, f_m = 1$$

message signal: $A_m \cos(2\pi f_m t)$

$$\frac{A_m}{A_C} = \mu \Rightarrow A_m = \mu \cdot A_C = 0.5 \times 40 = 20$$

$$m(t) = 20 \cos(2\pi t)$$

23. Ans: (c)

Sol: By observing the N-MOS circuit, C is in parallel to the series combination of A and B. Thus, $\bar{Y} = AB + C$



24. Ans: (c)

Sol: Given $f_c = 1000\text{Hz}$ and $f_s = 1500\text{Hz}$

$$\Omega_c = 2\pi f_c$$

$$\Omega_s = 2\pi f_s$$

$$\Omega_c = 2000\pi$$

$$\Omega_s = 3000\pi$$

For attenuation of -20dB

$$-20 \log_{10}(x) = 20$$

$$\Rightarrow x = 10^{-1} = 0.1$$

$$\text{Here, } x = \delta_s = 0.1$$

Now,

$$N = \frac{\log_{10} \left[\frac{1}{\delta_s^2} - 1 \right]}{2 \log_{10} (\Omega_s / \Omega_c)}$$

$$N = \frac{\log_{10}(100 - 1)}{2 \log_{10}(1.5)} = 5.67$$


$$N = 6$$

25. Ans: -1 (No range)

$$\begin{aligned} \text{Sol: } \lim_{x \rightarrow 0} \frac{\sin x}{x(x-1)} &= \lim_{x \rightarrow 0} \frac{1}{x-1} \cdot \lim_{x \rightarrow 0} \frac{\sin x}{x} \\ &= -1 \times 1 \\ &= -1 \end{aligned}$$

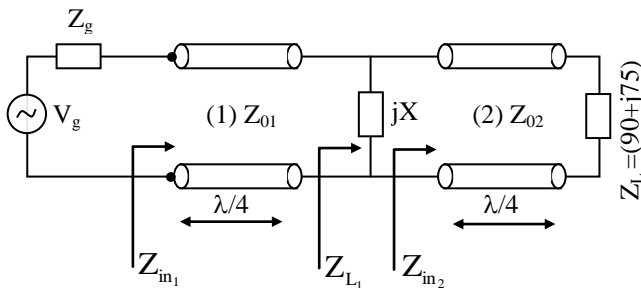26. Ans: (a)

Sol: For maximum power to be delivered to the load, the power delivered to the input terminals of line (1) must be maximum, so, the equivalent input impedance of the transmission line must be equal to its source impedance.



$$Z_{in2} = \frac{Z_{02}^2}{Z_L}$$

$$Z_{L1} = (jX // Z_{in2})$$

$$\frac{1}{Z_{L1}} = \frac{1}{jX} + \frac{1}{Z_{in2}}$$

$$\frac{1}{Z_{L1}} = \frac{1}{jX} + \frac{Z_L}{Z_{02}^2} \rightarrow (1)$$

$$Z_{in1} = \frac{Z_{01}^2}{Z_{L1}}$$

$$= \frac{Z_{in1}}{Z_{01}^2} = \frac{1}{Z_{L1}} \rightarrow (2)$$

From equation (1) and (2)

$$\frac{Z_{in1}}{Z_{01}^2} = \frac{1}{jX} + \frac{Z_L}{Z_{02}^2}$$

$Z_{in1} = Z_g^*$ (from maximum power transfer theorem)

$$Z_{in1} = 40 - j50$$

$$\frac{40 - j50}{50^2} = \frac{-j}{X} + \frac{90 + j75}{Z_{02}^2}$$

Equating real parts,

$$\frac{40}{50^2} = \frac{90}{Z_{02}^2}$$

$$Z_{02} = 75\Omega$$

Equating Imaginary parts,

$$\frac{-50}{50^2} = \frac{-1}{X} + \frac{75}{Z_{02}^2}$$

$$X = 30\Omega$$

27. Ans: (b)

Sol: Given $f(D) y = Q(x) \dots\dots\dots(1)$

$$\text{where } f(D) = D^2 + 3D + 2$$

$$\text{and } Q(x) = \cos(x)$$

C.F: Consider A.E, $f(m) = 0$

$$\Rightarrow m^2 + 3m + 2 = 0$$

$$\Rightarrow m = -1, -2$$

$$\therefore y_c = c_1 e^{-x} + c_2 e^{-2x}$$

P.I: Here, $Q(x) = \cos(x) = \cos(ax+b)$

$$\text{and } f(D) = \phi(D^2) = \phi(-a^2) = \phi(-1)$$

$$= (-1) + 3D + 2 = 1 + 3D \neq 0$$



Now,

$$y_p = \frac{1}{1+3D} \times \frac{1-3D}{1-3D} \cos(x) = \frac{1-3D}{1-9D^2} \cos(x)$$

$$\Rightarrow y_p = (1-3D) \left[\frac{1}{1-9(-1)} \cos(x) \right]$$

$$= (1-3D) \left(\frac{1}{10} \cos(x) \right)$$

$$\therefore y_p = \frac{\cos(x)}{10} + \frac{3}{10} \sin x$$


Hence, the general solution of (1) is

$$y = y_c + y_p$$

$$\text{i.e., } y = c_1 e^{-x} + c_2 e^{-2x} + \frac{\cos(x)}{10} + \frac{3}{10} \sin x$$

28. Ans: (c)

Sol:

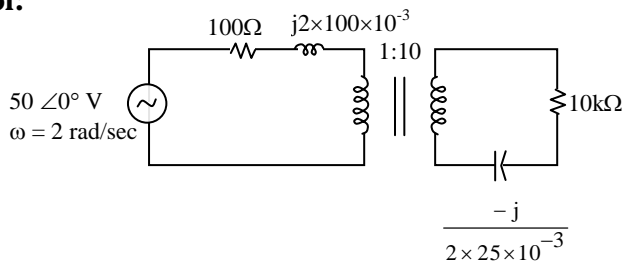

By transferring secondary impedance to primary then

$$z'_2 = \frac{Z_2}{k^2} \quad k = \frac{10}{1} = 10$$

$$z'_2 = \frac{10k\Omega - \frac{j}{2 \times 25 \times 10^{-3}}}{100}$$

$$= 100 - \frac{j}{5} = 100 - j0.2$$

$$I_1 = \frac{50}{100 + j0.2 + 100 - j0.2}$$

$$= \frac{50}{200} = \frac{1}{4} = 250 \text{ mA}$$

$$I_2 = \frac{I_1}{k} = \frac{I_1}{10} = 25 \text{ mA}$$

So power dissipated in the 10kΩ resistor is

$$P = (25 \times 10^{-3})^2 \cdot 10k\Omega$$

$$= 6.25 \text{ W}$$

29. Ans: (a)

Sol: $\angle G(s) = -3 \omega_{pc} - 90^\circ = -180^\circ$

$$\Rightarrow \omega_{pc} = 30^\circ = \frac{\pi}{6}$$

$$\text{Magnitude (a)} = \frac{k}{\omega_{pc}} = \frac{6k}{\pi}$$

For stability $a < 1$

$$\Rightarrow k < \frac{\pi}{6}$$

Therefore Range is $0 < k < \frac{\pi}{6}$

30. Ans: (a)

Sol: Given $x(n) = \frac{3^n}{n!}$

$$X(z) = \sum_{n=-\infty}^{\infty} x(n) z^{-n}$$

$$\text{Let } g(n) = \frac{1}{n!}$$

$$\therefore G(z) = Z\{g(n)\} = Z\left\{\frac{1}{n!}\right\}$$

$$G(z) = Z\left\{\frac{1}{n!}\right\} = \sum_{n=0}^{\infty} \frac{1}{n!} z^{-n}$$

$$G(z) = 1 + \frac{(1/z)}{1!} + \frac{(1/z)^2}{2!} + \frac{(1/z)^3}{3!} + \dots$$

$$G(z) = Z\left\{\frac{1}{n!}\right\} = e^{1/z} \dots (1)$$

By property,

$$a^n g(n) \leftrightarrow G\left(\frac{z}{a}\right)$$

$$3^n \frac{1}{n!} \leftrightarrow e^{3/z}$$

$$\therefore X(z) = Z\left\{\frac{3^n}{n!}\right\} = e^{3/z}$$

31. Ans: (a)

Sol: Given $f(D)y = Q(x) \dots (1)$

$$\text{where } f(D) = D^2 + 4D + 4$$

$$\& Q(x) = x^4 e^{-2x} = e^{-2x} \cdot x^4 = e^x \cdot V(x)$$



$$\text{Now, } y_p = \frac{1}{f(D)} [e^{-2x} x^4]$$

$$\Rightarrow y_p = e^{-2x} \left[\frac{1}{f(D-2)} x^4 \right]$$


$$\Rightarrow y_p = e^{-2x} \left[\frac{1}{(D-2)^2 + 4(D-2) + 4} x^4 \right]$$

$$\Rightarrow y_p = e^{-2x} \left[\frac{1(x^4)}{D^2} \right]$$


$$\therefore y_p = e^{-2x} \cdot \frac{x^6}{30}$$

32. Ans: 0.275 {Range: 0.25 to 0.29}


Sol:

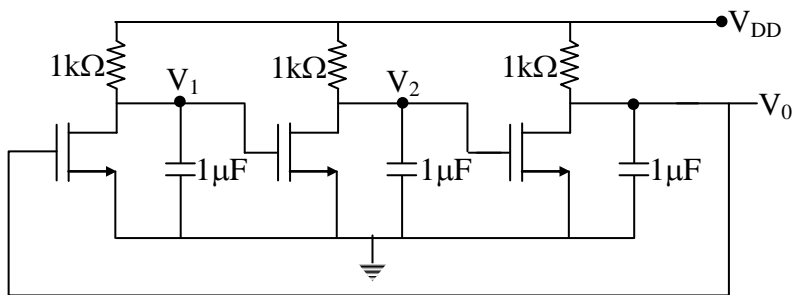

Consider a single-stage:

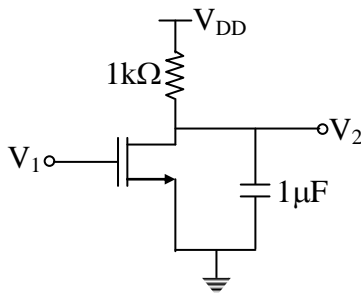

small-signal equivalent:

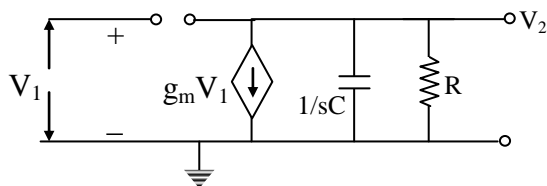

$$V_2 = -g_m V_1 (R // (1/sC))$$

$$\frac{V_2}{V_1} = -g_m [R // (1/sC)]$$

$$\text{So, similarly } \frac{V_1}{V_0} = \frac{V_0}{V_2} = \frac{V_2}{V_1} = -g_m \{R // (1/sC)\}$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



48
ALL INDIA
1st RANKS IN GATE



15
ALL INDIA
1st RANKS IN ESE

HYDERABAD | TIRUPATI | DELHI | PUNE | BHUBANESWAR | BENGALURU | LUCKNOW | CHENNAI | VIJAYAWADA | VIZAG | KOLKATA | AHMEDABAD

DIGITAL CLASSES

for

ESE

GS & Engg. Aptitude

250+

Hours of Classes
with Quizzes

GATE

CS & IT

450+

Hours of Classes
with Quizzes

Launching Soon! for ECE | EEE | MECH | CE | IN



Erudite &
Experienced
Faculty



Free Online
Test Series



Relevant Study Material
by Post



Doubt Clearing
Available



Access the Lectures
from anywhere
and Unlimited Times



Write & Store
Your Notes Online



EMI Option
Available

DEEP LEARN

Access The Course at
www.deep-learn.in



For oscillators, loop gain = 1

$$\frac{V_1}{V_0} \times \frac{V_2}{V_1} \times \frac{V_0}{V_2} = 1$$

$$\text{i.e., } \{-g_m[R/(1/sC)]\}^3 = 1$$

$$\Rightarrow -\left[\frac{g_m R}{1 + R s C}\right]^3 = 1$$

Put $s = j\omega$

$$\Rightarrow -\left[\frac{g_m R}{1 + j\omega RC}\right]^3 = 1$$

$$\Rightarrow -\left[\frac{(g_m R)^3}{(1 + j\omega RC)^3}\right] = 1$$

Equating angle condition i.e., angle = 360° for sustained oscillations

$$\text{i.e., } 180^\circ - 3\tan^{-1}(\omega RC) = 0^\circ$$

$$\tan^{-1}(\omega RC) = 60^\circ$$

$$\omega = \frac{\sqrt{3}}{RC}$$

$$f = \frac{\sqrt{3}}{2\pi RC} = 0.2756 \text{ kHz}$$

33. Ans: (b)

Sol: $\int_{-\infty}^{\infty} x e^{-x^2} dx$

Let $f(x) = x e^{-x^2}$

$$f(-x) = -x e^{-x^2} = -f(x)$$

$\therefore f(x)$ is odd function

\therefore The value of given integral is zero.

34. Ans: (c)

Sol: From parseval's theorem

$$2\pi \int_{-\infty}^{\infty} |x(t)|^2 dt = \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$$

$$x(t) = \begin{cases} t+1 & ; -1 < t < 0 \\ -t+1 & ; 0 < t < 2 \\ t-3 & ; 2 < t < 3 \end{cases}$$



$$\begin{aligned} \int_{-\infty}^{+\infty} |X(\omega)|^2 d\omega &= 2\pi \left[\int_{-1}^0 (t^2 + 2t + 1) dt + \int_0^2 (t^2 - 2t + 1) dt + \int_2^3 (t^2 - 6t + 9) dt \right] \\ &= 2\pi \left[\left(\frac{t^3}{3} + t^2 + t \right)_{-1}^0 + \left(\frac{t^3}{3} - t^2 + t \right)_0^2 + \left(\frac{t^3}{3} - 3t^2 + 9t \right)_2^3 \right] \\ &= 2\pi \left[\frac{1}{3} - 1 + 1 + \frac{8}{3} - 4 + 2 + 9 - 27 + 27 - \frac{8}{3} + 12 - 18 \right] = 8\pi/3 \end{aligned}$$

35. Ans: 25 (No range)

Sol: Method: I

$$\begin{aligned} \text{Closed loop gain } A_f(s) &= \frac{A_0(s)}{1 + \beta A_0(s)} \\ &= \frac{\frac{250}{s}}{1 + \frac{(2\pi \times 100)}{(0.8)(250)}} \\ &= \frac{250}{1 + \frac{s}{(2\pi \times 100)}} \end{aligned}$$

Low frequency gain/DC gain

$$= \frac{250}{1 + (0.8)(250)}$$

Band width = $100(1 + (0.8)(250))$

Gain \times Bandwidth = $250 \times 100 = 25 \times 10^3$ Hz

Method: 2

$$\text{If } A(s) = \frac{A_0}{1 + j\left(\frac{f}{f_H}\right)}$$

Then Gain (DC gain) = A_0

BW = f_H

Gain \times BW = $A_0 f_H$

Gain BW is constant {i.e., same for open loop as well as feedback closed loop amplifier}

$$A_0(s) = \frac{250}{1 + \frac{j\omega}{2\pi \times 100}} = \frac{250}{1 + j\left(\frac{f}{100}\right)}$$

Gain = 250

BW = 100

So, Gain \times BW = $250 \times 100 = 25 \times 10^3$ Hz

36. Ans: (d)

Sol: The power decays as $P e^{-2\alpha z}$
at $z = d$ power is attenuated to $10^{-12}P$
 $\therefore P e^{-2\alpha d} = 10^{-12}P$

$$-2\alpha d = \ln(10^{-12})$$

$$\alpha d = 13.8155$$

$$d = \frac{13.8155}{\alpha} \text{ ----(1)}$$

Since $f < f_{cmn}$, γ_{mn} must be real

$$\therefore \gamma_{mn} = \alpha = \beta \sqrt{\left(\frac{f_{cmn}}{f}\right)^2 - 1}$$

$$\lambda f = 3 \times 10^8 \text{ m/sec}$$

$$\lambda = \frac{3 \times 10^8}{10^9} = 0.3 \text{ m}$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{0.3} = 20.94 \text{ rad/m}$$

$$\begin{aligned} \therefore \gamma_{mn} = \alpha &= 20.94 \sqrt{(1.5)^2 - 1} \\ &= 23.41 \text{ Np/m} \end{aligned}$$

substitute α value in equation (1)

$$d = \frac{13.8155}{23.411} = 0.590 \text{ m}$$

$$d = 0.590 \text{ m}$$

37. Ans: (d)

Sol:

$$\tan 60^\circ = \frac{\sqrt{3}}{x} \Rightarrow x = 1$$



Pole is at $s = -1$

$$\text{Open loop TF } G(s) = \frac{K}{(s+1)^3}$$

$$\text{Closed loop TF} = \frac{G(s)}{1+G(s)H(s)}$$

$$H(s) = 1, K = 2$$

$$\text{CLTF} = \frac{\frac{2}{(s+1)^3}}{1 + \frac{2}{(s+1)^3}} = \frac{2}{s^3 + 3s^2 + 3s + 3}$$

38. Ans: (b)

$$\text{Sol: } P(T_1/R_1) = \frac{P(R_1/T_1) \times P(T_1)}{P(R_1)}$$

$$P(R_1) = P(T_1) P(R_1/T_1) + P(T_0) P(R_1/T_0)$$

$$= 0.4(0.92) + 0.6(0.1) = 0.428$$

$$\therefore P(T_1/R_1) = \frac{0.92 \times 0.4}{0.428} = 0.8598 \approx 0.86$$

39. Ans: (d)

Sol: \rightarrow (HL) = 4000H

\rightarrow (SP) = 2500H

\rightarrow (A) = AAH

\rightarrow (A) = AAH \oplus AAH = 00H

\Rightarrow (A) = 00H

\rightarrow PSW contents pushed on to top of stack

\rightarrow HL pair contents i.e., 4000H is exchanged with contents of top of stack
Top of stack contains 4000H.


\rightarrow Contents of top of stack i.e., 4000H popped back into PSW

\Rightarrow (PSW) = 4000H

Then flag register contents are 00H.

40. Ans: (b)

Sol:

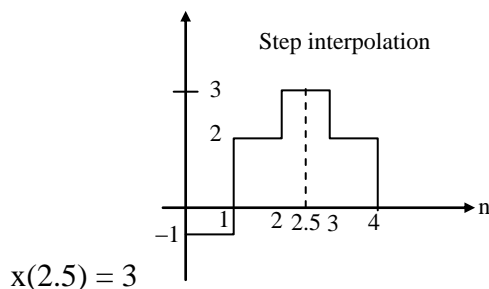

41. Ans: 1.93 (Range: 1.8 to 2.05)

$$\text{Sol: } P_e = Q \left(\sqrt{\frac{A_c^2 T_b}{N_0} \cos^2 \phi} \right)$$

$$\therefore P_{e(\text{BPSK})} = Q \left(\sqrt{\frac{10^{-4} \times 3}{10^4 \times 2 \times 10^{-9} \times 4}} \right)$$

$$= Q(1.93)$$

42. Ans: (a)

$$\text{Sol: } \frac{P_R}{P_T} = G_T G_R \left(\frac{\lambda}{4\pi R} \right)^2$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{75 \times 10^6} = 4\text{m}$$

$$\lambda = 4\text{m}, \frac{\ell}{\lambda} = \frac{1}{2}$$

$$\ell = \frac{\lambda}{2}$$

Half wave dipole

So, $D = 1.64$

$$\therefore \frac{P_R}{P_T} = \frac{1.64 \times 1.64 \times 4^2}{16\pi^2 \times 10^6}$$

$$\frac{P_R}{P_T} = 27.25 \times 10^{-8}$$

43. Ans: 0.25 (No range)

$$\text{Sol: } BW = \frac{R_b}{2} [1 + \alpha]$$

$$4.5 \times 10^3 = \frac{7200}{2} [1 + \alpha]$$


$$\alpha = 0.25$$

44. Ans: 1 (No range)

Sol: Given

V_i = Halfwave rectified output of $5\sin\omega t$.

Representing V_i in graph

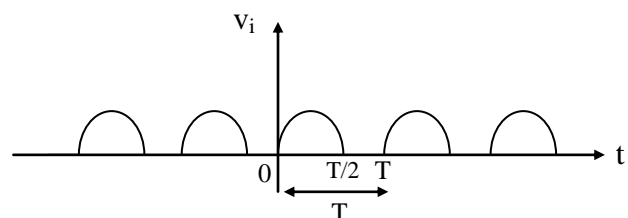



From the given transfer characteristics, we can conclude that

If $V_i > +3 \Rightarrow V_0$ changes from -10 to $+10$

$V_i < -3 \Rightarrow V_0$ changes from $+10$ to -10


Given at $t = 0^- \Rightarrow V_0 = -10V$

Now starting from $t = 0^-$

$\Rightarrow V_0 = -10V, V_i = 0V$

Now as $V_i > +3$

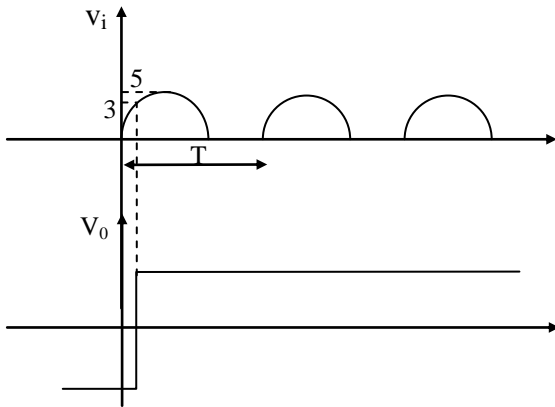$\Rightarrow V_0$ changes from -10 to $+10$



and Now if V_0 becomes $+10V$, it will never come back to $-10V$ since for that to happen V_i should be less than -3 but given V_i is always positive, so number of transitions is 1.

45. Ans: (b)

Sol: Given $y''(t) - y'(t) - 6y(t) = e^t u(t)$

Apply L.T

$$s^2 Y(s) - sy(0) - y'(0) - sY(s) + y(0) - 6Y(s) = \frac{1}{s-1}$$

Given $y(0) = 1, y'(0) = 0$

$$s^2 Y(s) - s - sY(s) + 1 - 6Y(s) = \frac{1}{s-1}$$

$$Y(s)[s^2 - s - 6] = s - 1 + \frac{1}{s-1}$$

$$Y(s)[s^2 - s - 6] = \frac{s^2 - 2s + 2}{s-1}$$

$$Y(s) = \frac{s^2 - 2s + 2}{(s-1)(s-3)(s+2)}$$

$$Y(s) = \frac{A}{s-1} + \frac{B}{s-3} + \frac{C}{s+2}$$

$$Y(s) = -\frac{1}{6} \frac{1}{s-1} + \frac{1}{2} \frac{1}{s-3} + \frac{2}{3} \frac{1}{s+2}$$

Apply ILT

$$y(t) = -\frac{1}{6} e^t + \frac{1}{2} e^{3t} + \frac{2}{3} e^{-2t} \quad t > 0$$

46. Ans: 258.85 (Range 255 to 265)

Sol: Since, $N_{AB} = n_p [x = x_B] = n_{p_0} \exp\left(\frac{V_{BC}}{V_T}\right)$


Where,

$$n_{p_0} = \frac{n_i^2}{N_{AB}} = \frac{(1.5 \times 10^{10})^2}{10^{16}} = 2.25 \times 10^4 / \text{cm}^3$$

$$n_p [x = x_B] = 2.25 \times 10^4 \times \exp\left[\frac{0.6}{0.0259}\right] = 258.85 \times 10^{12} / \text{cm}^3$$

47. Ans: 10(No range)

Sol: $c(t) = 12.5e^{-6t} \sin 8t$

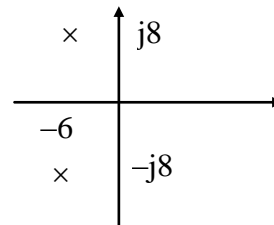

ω_n is radial distance from origin

$$\omega_n = \sqrt{6^2 + 8^2}$$


$$\omega_n = 10 \text{ rad/sec}$$

48. Ans: 0.03 (Range: 0.028 to 0.032)

Sol: Since, Dynamic conductance, $g = \frac{I_C}{V_T}$,

$$\therefore I_E = \frac{6 - 0.7}{6.8} \text{ mA} = 0.779 \text{ mA}$$
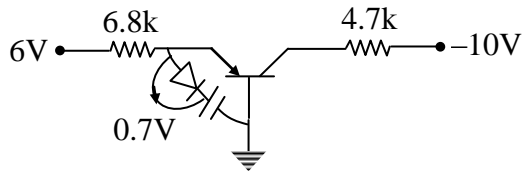
$$\therefore \beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}} = \frac{0.998}{1 - 0.998} = 499$$



$$\therefore I_B = \frac{I_E}{1 + \beta_{dc}} = 1.55 \mu A$$

\therefore Transconductance,

$$g = \frac{I_C}{V_T} \approx \frac{I_E}{26mV} = \frac{0.779}{26} = 0.03 \text{ } \Omega$$

49. Ans: 9 (No range)

Sol: Forward paths: $M_1 = G_1 G_2 G_3 G_4 G_5 G_6$

$$M_2 = G_1 G_2 G_7 G_6$$

$$M_3 = G_1 G_2 G_3 G_4 G_8$$

Loops: $L_1 = G_4 H_2$

$$L_2 = G_5 G_6 H_3$$

$$L_3 = G_1 G_2 G_3 G_4 G_5 G_6 H_1$$

$$L_4 = G_1 G_2 G_7 G_6 H_1$$

$$L_5 = G_1 G_2 G_3 G_4 G_8 H_1$$

$$L_6 = G_8 H_3$$

50. Ans: (d)

Sol: Given that 8 KB ROM & 8 KB RAM interfaced to 8085.

ROM is selected when A_{15} is 0

RAM is selected when A_{15} is 1

A_{13} & A_{14} are unused.

MVI A, 00H ; (A) = 00H

STA 8080H ; (8080H) \leftarrow (A) = 00H

DCR A ; (A) = FFH

STA C080H ; (C080H) \leftarrow (A) = FFH


; (8080H) \leftarrow (A) = 00H

RET ; (PC) \leftarrow (TOS)

Contents of memory location 8080H is 00H.

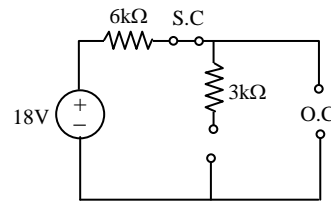51. Ans: - 60 (No Range)

Sol: At time $t = 0^-$ switch is in open condition




So, L is short circuit, C is open circuit

$$i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 18V$$

At $t = 0^+$ switch is closed

$$I_C(0^+) = C \frac{dv(0^+)}{dt}$$

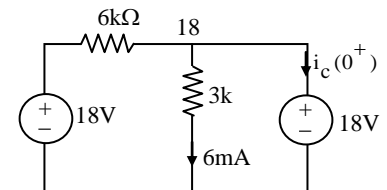

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

$$i_c(0^+) = -6 \times 10^{-3} \text{ A}$$

$$\frac{dv(0^+)}{dt} = \frac{-6 \times 10^{-3}}{100 \times 10^{-6}}$$

$$\frac{dv(0^+)}{dt} = -60 \text{ V/sec}$$

52. Ans: (c)

Sol: Given

$$f(x) = \frac{\pi^2}{3} - 4 \left(\frac{\cos x}{1^2} - \frac{\cos 2x}{2^2} + \dots \right)$$

clearly $f(x)$ is continuous at $x = 0$

($\because \lim_{x \rightarrow 0} f(x) = 0$) the four series converges

to $f(0)$

$$\frac{\pi^2}{3} - 4 \left(\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots \right) = 0$$


$$\frac{\pi^2}{3} - 4 \left(\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots \right) = 0$$

$$\frac{1}{1^2} + \frac{1}{2^2} - \frac{1}{3^2} + \dots = \frac{\pi^2}{12}$$



53. Ans: 68.57 (Range: (67.5 to 69.5V))

Sol:

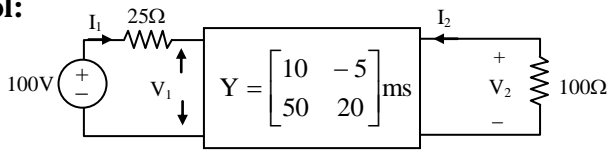

By applying at KVL input side

$$V_1 = 100 - 25I_1 \dots\dots\dots (1)$$

$$V_2 = -100 I_2 \dots\dots\dots (2)$$

From Y-parameters

$$I_1 = (10 \times 10^{-3}) V_1 - (5 \times 10^{-3}) V_2 \dots\dots\dots (3)$$

$$I_2 = (50 \times 10^{-3}) V_1 + (20 \times 10^{-3}) V_2 \dots\dots\dots (4)$$

By putting value of V_2 in equation (4)

$$I_2 = (50 \times 10^{-3}) V_1 + (20 \times 10^{-3}) (-100 I_2)$$

$$= (50 \times 10^{-3}) V_1 - 2I_2$$

$$3I_2 = (50 \times 10^{-3}) V_1$$

And from equation (3)

$$I_1 = (10 \times 10^{-3}) V_1 - (5 \times 10^{-3}) (-100 I_2)$$

$$= (10 \times 10^{-3}) V_1 + (5 \times 10^{-3} \times 100) \left(\frac{50 \times 10^{-3}}{3} \right) V_1$$

$$= (10 \times 10^{-3}) V_1 + \frac{25}{3} \times 10^{-3} V_1$$

$$= \frac{55}{3} \times 10^{-3} V_1$$

$$\therefore V_1 = 100 - [25 \times I_1]$$

$$V_1 = 100 - \left[25 \times \frac{55}{3} \times 10^{-3} V_1 \right]$$

$$V_1 \left[1 + 25 \times \frac{55}{3} \times 10^{-3} \right] = 100$$

$$V_1 = \frac{100}{1.458} = 68.57V$$

54. Ans: 19.23 (Range 19 to 20)

Sol: Since, $N_{AB} \ll N_{DC} \Rightarrow \frac{1}{N_{AB}} + \frac{1}{N_{DC}} = \frac{1}{N_{AB}}$

As at early effect, $[V_j]_{B-C} = V_{punch}$ and $[W_{dep}]_{B-C} = W_B$ (base width).

$$\therefore [W_{dep}]_{B-C} = W = W_B = \sqrt{\frac{2\varepsilon}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) [V_{punch}]}$$

$$= \sqrt{\frac{2\varepsilon}{q} \frac{1}{N_A} V_{punch}}$$

$$\therefore V_{punch} = \frac{q N_A W_B^2}{2\varepsilon},$$

where $\varepsilon = \varepsilon_0 \varepsilon_r$ and $[\varepsilon_r]_{Si} = 11.7$

Now given,

$$\rho_B = 0.5 \Omega \text{cm} = \frac{1}{\sigma_B} \approx \frac{1}{N_A q \mu_p} \text{ and it is given}$$

$$\text{that, } [\mu_p]_{Si, 300^\circ K} = 500 \text{cm}^2 / \text{V sec}$$

$$\therefore N_{DB} = N_{DA} = 2.5 \times 10^{16} / \text{cm}^3$$

$$\therefore V_{punch} = \frac{1.6 \times 10^{-19} \times 2.5 \times 10^{16} \times (10^{-4})^2}{2 \times 1.04 \times 10^{-12}}$$

$$= 19.23V$$

55. Ans: (d)

Sol: In hamming code, K parity bits are added to an n-bit data word, forming a new word of n + K bits.

The bit positions are numbered in sequence from 1 to n + K. Those positions numbered as a power of 2 are reserved for the parity bits.

Step-1: Finding the value of K:

$$2^K - 1 - K \geq n$$

$$\text{For } K = 3, n \leq 4$$

$$\text{For } K = 4, n \leq 11$$

$$\text{Thus, } K = 4$$

Step-2: The 4 parity bits, P_1, P_2, P_4 and P_8 are in positions 1, 2, 4 and 8 respectively.

$$P_1 = \text{XOR of bits } (3, 5, 7, 9, 11) = 0$$

$$P_2 = \text{XOR of bits } (3, 6, 7, 10, 11) = 0$$

$$P_4 = \text{XOR of bits } (5, 6, 7, 12) = 1$$

$$P_8 = \text{XOR of bits } (9, 10, 11, 12) = 1$$

Therefore, the 12-bit word is

$$P_1 P_2 D_0 P_4 D_1 D_2 D_3 P_8 D_4 D_5 D_6 D_7$$

$$= 0 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 0$$



56. Ans: (d)

Sol: 'Cut out for' means designed to be so. 'Cut up' means 'to be emotionally upset'. 'Cut down' means 'to kill somebody' or 'to make something fall down by cutting it at the base'. 'Cut off' means 'separated from the rest of the world'.

57. Ans: (c)

58. Ans: (a)

59. Ans: (d)

Sol: Let principle be 1.
then amount after 10 years = $3 \times 1 = 3$
 \therefore Simple interest = $3 - 1 = 2$
 \therefore Rate of interest = $\frac{2 \times 100}{1 \times 10} = 20\%$

60. Ans: (c)

Sol: Note that $20 - 14 = 6$; $25 - 19 = 6$;
 $35 - 29 = 6$; $40 - 34 = 6$.

$$\begin{aligned} 20 &= 2 \times 2 \times 5 \\ 25 &= 5 \times 5 \\ 35 &= 1 \times 5 \times 7 \\ 40 &= 2 \times 2 \times 2 \times 5 \end{aligned}$$

Required number


$$\begin{aligned} &= \text{L.C.M. of } (20, 25, 35 \text{ and } 40) - 6. \\ &= (2 \times 2 \times 2 \times 5 \times 5 \times 7) - 6 \\ &= 1400 - 6 = 1394 \end{aligned}$$

61. Ans: (c)

Sol: The angle subtended by an arc at the centre of the circle is twice the angle subtended by the arc at any point on the remaining part of the circle.

$$\therefore \angle BOC = 2\angle BAC = 2 \times 50^\circ = 100^\circ$$

Now in $\triangle BOC$

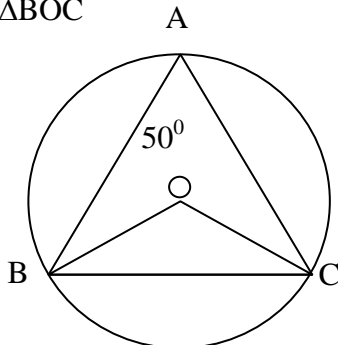

$OB = OC$ [radii of circumcentre]

$$\therefore \angle OBC = \angle OCB = x \text{ (let)}$$

$$\therefore x + x + 100^\circ = 180^\circ$$

$$\Rightarrow 2x = 80^\circ$$

$$\Rightarrow x = 40^\circ$$

62. Ans: (a)

Sol: At 4:10 the hour hand is a head of minute hand

Given that $n = 4$ and $x = 10$

Then according to the formula required angle

$$\begin{aligned} &= \left\{ 30 \left(n - \frac{x}{5} \right) + \frac{x}{2} \right\}^\circ \\ &= \left\{ 30 \left(4 - \frac{10}{5} \right) + \frac{10}{2} \right\}^\circ \\ &= \{ (30 \times 2) + 5 \}^\circ = (60 + 5)^\circ \\ &= 65^\circ \end{aligned}$$

63. Ans: (b)

Sol: Total cost (in Rs) of journey to Town A
 $= 4300 + 3100 + 4000 + 6000 = 17400$

$$\text{Average cost} = \frac{17400}{4} = \text{Rs. } 4350$$

64. Ans: (a)

Sol: Maximum cost (in Rs) of journey from Delhi to town A = By Train 4 = Rs. 6000

Similarly, for town B = Rs. 6300

Town C = Rs. 5600 and

Town D = Rs. 5700

$$\begin{aligned} \Rightarrow \text{Maximum cost} &= 6000 + 6300 + 5600 \\ &= \text{Rs. } 23600 \end{aligned}$$

65. Ans: (d)

UPCOMING BATCHES @ PUNE

(Streams: ME / CE / EC / EE / CS / IT / IN / PI)

LONG TERM PROGRAM

GATE+PSUs 2021

Weekend Batches:

28th December 2019

01st February 2020

Evening Batch

10th February 2020

MPSC

PRELIMS (CE/ME/EE)

Evening Batch

20th January 2020

TWO YEARS PROGRAM

GATE+PSUs 2022

Weekend Batch

01st February 2020

ESE+GATE+PSUs 2022

Weekend Batch

01st February 2020

Branch Office: #302, Venkatest Villa, CTS 1204/9, Upstairs: Janata Sahakari Bank,
Ghole Road, Mahatma Phule Museum, Shivaji Nagar, Pune - 411005.

Call: 020-25535950, 9343499966 | Web: www.aceenggacademy.com