



ACE

Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad - 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

Branch: Electrical Engineering Mock- E - Solutions

GATE-2020 General Aptitude (GA)

01. Ans: (C)

Sol: (passive voice - verb in past participle form).

02. Ans: (C)

Sol: 'between.... to' is wrong. 'between.....and'.

03. Ans: (D)

Sol: Suggestion is friendly/ smooth

Demand is unfriendly/Rough

Take is smooth

Grab is Rough

04. Ans: (C)

Sol: Let the four numbers be x , $x + 2$, $x + 4$, and $x + 6$.

$$\Rightarrow x + x + 2 + x + 4 + x + 6 = 36$$

$$\Rightarrow 4x + 12 = 36$$

$$\Rightarrow x = 6$$

Therefore, the numbers are 6, 8, 10 & 12.

Therefore, the sum of their squares = $6^2 + 8^2 + 10^2 + 12^2 = 36 + 64 + 100 + 144 = 344$.

05. Ans: (A)

Sol: We know that an ordinary year has 1 odd day and a leap year has 2 odd days.

During this period, namely 2005, 2006, 2007, 2008, 2009, 2010.

Total number of odd days = $(1 + 1 + 1 + 2 + 1 + 1) \text{ days} = 7 = 0 \text{ odd days}$.

Hence, the calendar for 2005 will serve for the year 2011 too.

06. Ans: (D)

Sol: The solution to this problem can be obtained only with more information like ratio of the length of the rectangle to its breadth.

07. Ans: (B)

Sol: Amount = $\left[7500 \times \left(1 + \frac{4}{100} \right)^2 \right]$

$$= \left(7500 \times \frac{26}{25} \times \frac{26}{25} \right)$$

$$= 8112$$

So, compound interest = $(8112 - 7500)$

$$= 612$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



48 ALL INDIA 1st RANKS IN GATE **15** ALL INDIA 1st RANKS IN ESE

ESE - MAINS

Classes Start from:

13th FEB 2020



(@ DELHI)

(@ HYDERABAD)



**Students who Qualify in Prelims
can avail 100 % Fee Waiver**

ESE-2018, 2019 Prelims Qualified Students are also eligible

for more details Contact: **040-23234418/19/20**, Email: hyderabad@aceenggacademy.com

www.aceenggacademy.com

HYDERABAD | AHMEDABAD | DELHI | PUNE | BHUBANESWAR | LUCKNOW | KOLKATA | VIJAYAWADA | VIZAG | TIRUPATI | CHENNAI | BENGALURU



COAL INDIA LIMITED (CIL)

Management Trainees

Online Test Series

6 Full Length Mock Tests

Civil | Electrical | Mechanical

Starts From 10th Jan 2020

All tests will be available till 28th February 2020

COAL INDIA

040 - 48539866 / 040 - 40136222

testseries@aceenggacademy.com

08. Ans: (C)

Sol: Let their present ages be $6x$ and $7x$ respectively. Then, their age difference = 'x' years

$$\text{i.e. } 4 = 'x' \text{ years}$$

\therefore Their present ages are 24 & 28 respectively

$$\begin{aligned} \text{Ratio of ages after 4 years} &= 24 + 4 : 28 + 4 \\ &= 7 : 8 \end{aligned}$$

09. Ans: (B)

Sol: Expenditure in year 2016 (in 000') = 3800

Expenditure in year 2015 (in 000') = 3075

\Rightarrow Required % increase

$$\begin{aligned} &= \frac{(3800 - 3075)}{3075} \times 100 \\ &= \frac{725}{30.75} = \frac{29}{1.23} = 23.57\% \end{aligned}$$

10. Ans: (B)**Specialization (EE)****01. Ans: 120 (No Range)**

Sol: For fan load, $T \propto N_r^2$; $P \propto N_r^3$

$$N_r \propto N_s \propto \frac{1}{P_{ok}}$$

$$P \propto \left(\frac{1}{P_{ok}} \right)^3$$

$$\Rightarrow 15 \times (8)^3 = P_2 (4)^3$$

$$P_2 = 120 \text{ kW}$$

02. Ans: (A)

$$\text{Sol: } P_{max} = \frac{|V_s||V_r|}{X_L} = \frac{1 \times 1}{0.1} = 10 \text{ p.u}$$

$$\text{For } P_{max} \delta = 90^\circ$$

$$(Q_r)_{pmax} = \frac{-V_r^2}{X_L} = \frac{-1^2}{0.1} = 10 \text{ p.u}$$

Line expecting reactive power from receiving end. So receiving end power factor is leading

$$P.f_r = \cos \tan^{-1} \left(\frac{Q_r}{P_{rmax}} \right)$$

$$\begin{aligned} Pf_r &= \cos \left(\tan^{-1} \left(\frac{10}{10} \right) \right) \\ &= 0.707 \text{ lead} \end{aligned}$$

03. Ans: (B)

Sol: $R_1 = 100 \Omega \pm 10\% = 100 \pm 10 \Omega$

$R_2 = 200 \Omega \pm 10\% = 200 \pm 20 \Omega$

If two resistances are connected in series,

$$\text{Total resistance } R_T = R_1 + R_2$$

$$= 300 \pm 30 \Omega$$

04. Ans: 0 (Zero)

$$\text{Sol: } V_0 = \sum_{n=1,3,5}^{\infty} \frac{2V_s}{n\pi} \cdot \sin(n\omega t)$$

$$V_{04} = 0$$

05. Ans: (A)

Sol: Here, element cannot be resistor as V and i are not proportional. Required element is inductor

For $0 < t < 2 \text{ ms}$

$$\frac{di}{dt} = 5 \times 10^3 \text{ A/s} \text{ and } V = 15 \text{ V}$$

$$\therefore L = \frac{V}{\frac{di}{dt}} = 3 \text{ mH}$$

06. Ans: (C)

Sol: $\rho_v = \nabla \cdot \vec{D}$

$$= \frac{1}{r^2 \sin \theta} \left[\frac{\partial}{\partial r} \left[r^2 \sin \theta \left(\frac{3r}{r^2 + 1} \right) \right] \right]$$

$$= \frac{1}{r^2} \left[\frac{(r^2 + 1)9r^2 - 3r^3(2r)}{(r^2 + 1)^2} \right]$$

$$= \frac{3(r^2 + 3)}{(r^2 + 1)^2} \text{ C/m}^3$$

$$\rho_v \text{ at } \left(1, \frac{\pi}{3}, \frac{\pi}{2} \right) = 3 \text{ C/m}^3$$

07. Ans: 2


Sol: $p = 3, z = 1$

No. of asymptotes

$$= |p - z| = 2$$

08. Ans: 5.7 (5.5 to 6.0)

Sol:

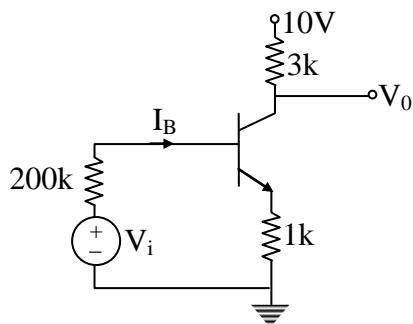

$$I_B = \frac{V_i - V_{BE}}{[200 + 1(1+\beta)] \times 10^3}$$

$$= 14.28 \mu\text{A}$$

$$I_C = \beta I_B = 1.428 \text{ mA}, I_E = (1+\beta)I_B$$

$$= 1.4428 \text{ mA}$$

$$V_0 = 10 - 3 I_C = 5.716 \text{ V}$$

$$\therefore V_0 = 5.716 \text{ V}$$

09. Ans: (D)

Sol: $\overline{\overline{X + \overline{Y} + \overline{X}}} = \overline{\overline{XY} + \overline{X}} = X$

10. Ans: (A)

Sol: It is a finite duration signal extending from 0 to 4.

All finite duration signals are energy signals but not vice-versa.

11. Ans: (D)

12. Ans: (D)

Sol:

- ◆ Closed loop systems accuracy is very high due to correction of any arising error.
- ◆ Closed loop systems have high bandwidth, i.e., high operating frequency zone.
- ◆ Tendency towards oscillations if feedback is not properly utilised.

13. Ans: (B)

Sol: $\because L^{-1}\left\{\frac{\bar{f}(S)}{S}\right\} = \int_0^t L^{-1}\{\bar{f}(S)\} dt$

Now,

$$L^{-1}\left\{\frac{1}{S(S-1)}\right\} = L^{-1}\left\{\frac{1}{S}\right\} - L^{-1}\left\{\frac{1}{S-1}\right\} = \int_0^t L^{-1}\left\{\frac{1}{S-1}\right\} dt$$

$$\Rightarrow L^{-1}\left\{\frac{1}{S(S-1)}\right\} = \int_0^t e^t dt$$

$$\therefore L^{-1}\left\{\frac{1}{S(S-1)}\right\} = (e^t)_0^t = e^t - 1$$

14. Ans: (C)

Sol: Given $x(t) = 3 \sin(2t)$

Input frequency is $\omega = 2$

$$H(2) = \frac{4}{2+j2} = 1.4142 \angle -45^\circ$$

If input is the form $x(t) = A \sin(\omega_0 t + \phi)$.

Then output is the form

$$y(t) = A|H(\omega_0)| \sin(\omega_0 t + \phi + \angle H(\omega_0))$$

$$y(t) = (3)(1.4142) \sin(2t - 45^\circ) = 4.2426 \sin(2t - 45^\circ)$$

15. Ans: 125 no range

Sol: Given that $|A_{4 \times 4}| = 5$

$$\because |\text{adj}(A_{n \times n})| = |A|^{n-1}$$

$$\Rightarrow |\text{adj}(A_{4 \times 4})| = |A|^{4-1} \quad \text{for } n = 4$$

$$\therefore |\text{adj}(A_{4 \times 4})| = |A|^3 = 5^3 = 125$$

16. Ans: (A)

Sol: At normal excitation, no load condition $\delta = 0, E = V$

As load increases ' δ ' increases then

$E \cos \delta < V \Rightarrow$ under excitation

\therefore Lagging pf, absorb Reactive power.

17. Ans: 1.8

$$H_{\text{eq}} = \frac{KE_1 + KE_2}{G_{\text{base}}} = \frac{500 + 400}{500} = 1.8 \text{ MJ / MVA}$$

18. Ans: (B)

Sol: Given

$$(4) \frac{\partial^2 u}{\partial x^2} + (-3) \frac{\partial^2 u}{\partial x \partial y} + (1) \frac{\partial^2 u}{\partial y^2} + (5)u = 0$$

If we compare the given partial differential equation with general partial differential equation

$$A \frac{\partial^2 u}{\partial x^2} + B \frac{\partial^2 u}{\partial x \partial y} + C \frac{\partial^2 u}{\partial y^2} + D \frac{\partial u}{\partial x} + E \frac{\partial u}{\partial y} + Fu = Q$$

then

we get $A = 4, B = -3$ and $C = 1$

If $B^2 - 4AC < 0$ then the partial differential equation is said to be elliptic type.

$$\text{Here, } B^2 - 4AC = (-3)^2 - 4(4)(1) = -7 < 0$$

\therefore The given partial differential equation is elliptic type.

19. Ans: 10 A

Sol: for $t \geq 0$

$$i_c = V_{\text{co}} \sqrt{\frac{C}{L}} \sin \frac{t}{\sqrt{LC}}$$

$$I_c = 10 \sin(10^4 t)$$

Peak value = 10 A

20. Ans: (D)

Sol: $\vec{E} = -\nabla V$

$$= -V_0 \left[\left(\frac{\pi}{4} \right) e^{-z} \cos\left(\frac{\pi y}{4}\right) \hat{a}_y + (-1) e^{-z} \sin\left(\frac{\pi y}{4}\right) \hat{a}_z \right]$$

$$= V_0 \left[-e^{-z} \left(\frac{\pi}{4} \right) \cos\left(\frac{\pi y}{4}\right) \hat{a}_y + e^{-z} \sin\left(\frac{\pi y}{4}\right) \hat{a}_z \right]$$

∴ Electric field intensity at (0, 1, 1) is given by


$$\vec{E} = \frac{V_0}{\sqrt{2}} e \left[\hat{a}_z - \frac{\pi}{4} \hat{a}_y \right] \text{ V/m}$$

21. Ans: 0.38 (Range: 0.37 to 0.39)

$$\text{Sol: } \frac{C}{R} = \left(\frac{8}{1+8(2)} \right) \left(\frac{4}{1+4} \right) = \frac{32}{85} = 0.376$$

22. Ans: (C)

Sol:

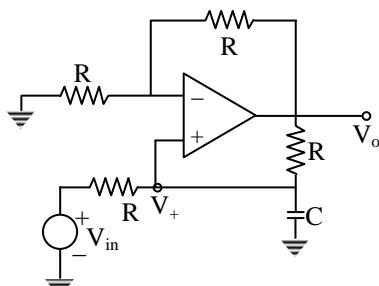

$$V_- = V_+ = \frac{V_o}{2}$$

KCL

$$\frac{(V_+) - V_{in}}{R} + \frac{V_+}{\frac{1}{SC}} + \frac{(V_+) - V_o}{R} = 0$$

$$\rightarrow \frac{V_o}{V_{in}} = \frac{2}{SCR}$$

This is a non inverting integrator

23. Ans: (D)

$$\text{Sol: } \omega_0 = \frac{3\pi^2}{4}$$

$$\frac{\omega_0}{2\pi} = \frac{3\pi}{8}$$

It is a irrational number.

So, non periodic signal.

24. Ans: (C)

$$\text{Sol: Given that } u = \frac{x^{3/2} + y^{3/2}}{4x - y}$$

⇒ $u(x, y)$ is a homogenous function with

$$\text{degree } n = \frac{3}{2} - 1 = \frac{1}{2}$$

By Euler's theorem for homogeneous functions, we have the following result.

If $u = f(x, y)$ is a homogeneous function with degree 'n' in x and y then

$$x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = n.u$$

$$\therefore x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \frac{1}{2} u$$

25. Ans: (B)

$$\text{Sol: } P(x = 2) = P(x = 3)$$

$$\frac{\lambda^2 e^{-\lambda}}{2!} = \frac{\lambda^3 e^{-\lambda}}{3!}$$

$$\frac{\lambda^2 e^{-\lambda}}{2} = \frac{(\lambda^2)(\lambda)e^{-\lambda}}{6}$$

$$\Rightarrow \lambda = 3$$

$$P(x \neq 0) = 1 - P(x = 0)$$

$$= 1 - \frac{\lambda^0 e^{-\lambda}}{0!} = 1 - e^{-3}$$



Hyderabad | Ahmedabad | Pune | Delhi | Bhubaneswar | Bangalore | Chennai | Lucknow | Visakhapatnam | Vijayawada | Tirupati | Kolkata

Head Office Address: # 4-1-1236/1/A, Sindh Sadan, King Koti, Abids, Hyderabad - 500001, Telangana, India.

SUMMER

SHORT TERM BATCHES GATE + PSUs - 2021

@ HYDERABAD

Streams: EC, EE, ME, CE, CSIT, IN & PI

28th April, 5th May,
10th May, 17th May, 25th May,
1st June, 8th June, 2020

Course Duration: 55 to 60 Days

✉ 040-23234418/19/20, 040-24750437

✉ hyderabad@aceenggacademy.com

Early Bird Offer Rs. 3,000/- Register before 31st March 2020

Upcoming Batches @ HYDERABAD

GATE+PSUs-2021

Spark Batches : 10th May, 8th & 23rd June 2020.

Regular Batches : 26th April, 10th, 24th May, 8th, 23rd June, 7th, 22nd July, 5th & 20th August 2020.

ESE+GATE+PSUs-2021

Spark Batches : 10th May, 8th & 23rd June 2020.

Regular Batches : 29th March, 26th April, 10th, 24th May, 8th, 23rd June & 7th July 2020.

SSC-JE Batches @ Hyderabad

New Batch Starts from: 10th May 2020

for Civil, Mechanical & Electrical

@ DELHI

Streams: EC, EE, ME, CE, IN & PI

10th & 20th
May 2020

Course Duration: 60 to 70 Days

✉ 7838971777 (Call or Whatsapp)

✉ delhi@aceenggacademy.com

Upcoming Batches @ DELHI

GATE+PSUs-2021

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

Regular Batches : 17th Feb, 7th March, 10th & 20th May 2020.

ESE+GATE+PSUs-2021

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

Regular Batches : 17th Feb, 7th March, 10th & 20th May 2020.

GATE+PSUs-2022

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

ESE+GATE+PSUs-2022

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.



Scan QR Code for
Upcoming Batches
Details

26. Ans: 88.29 (Range: 88 to 89)

Sol: Torque constant $T_2 = T_1$

$$\phi_2 I_{a_2} = \phi_1 I_{a_1}$$

$$\Rightarrow I_{sh_2} I_{a_2} = I_{sh_1} I_{a_1}$$

$$I_{sh_1} = \frac{V}{R_{sh}} = \frac{250}{250} = 1A$$

$$I_{sh_2} I_{a_2} = 1 \times 20$$

$$I_{a_2} = \frac{20}{I_{sh_2}}$$

$$E_{b_1} = V - I_{a_1} R_a = 250 - 20 \times 0.5 = 240 A$$

$$E_{b_2} = V - I_{a_2} R_a = 250 - \frac{20}{I_{sh_2}} \times 0.5$$

$$= 250 - \frac{10}{I_{sh_2}}$$

$$\frac{E_{b_2}}{E_{b_1}} = \frac{I_{sh_2} \times N_2}{I_{sh_1} \times N_1} \Rightarrow \frac{250 - \frac{10}{I_{sh_2}}}{240} = \frac{I_{sh_2} \times 800}{1 \times 600}$$

$$= 250 - \frac{10}{I_{sh_2}} = 320 I_{sh_2}$$

$$\Rightarrow 32 I_{sh_2}^2 - 25 I_{sh_2} + 1 = 0$$

$$I_{sh_2} = \frac{25 \pm \sqrt{25^2 - 4 \times 32 \times 1}}{2 \times 32}$$

$$I_{sh_2} = 0.739 A \text{ or } (0.0422 A \text{ is too low})$$

$$I_{sh_2} = 0.739 A = \frac{V}{R_{sh_2}} = \frac{250}{R_{sh_2}}$$

$$R_{sh_2} = \frac{250}{0.739} = 338.29 \Omega$$

$$\begin{aligned} \text{Resistance to be added} &= 338.29 - 250 \\ &= 88.29 \Omega \end{aligned}$$

27. Ans: (B)

$$\text{Sol: } S_{IL_1} = \frac{V^2}{Z_{c1}} = 640 \text{ MW}$$

$$S_{IL_2} = \frac{V^2}{Z_{c2}} = 640 \times 1.3 \text{ MW}$$

$$\frac{V^2}{Z_{c1} \cdot \sqrt{\frac{1-k_{se}}{1-k_{sh}}}} = 640 \times 1.3$$

$$\sqrt{\frac{1-k_{se}}{1-k_{sh}}} = \frac{1}{1.3}$$

$$= 0.769$$

To meet this equation $k_{sh} = 0, k_{se} \neq 0$


$$\text{So, } \sqrt{1-k_{se}} = 0.769$$

$$K_{se} = 0.408$$

% series compensation = 40.8%

28. Ans: (C)

Sol: Base: 50 MVA, 13.8 kV

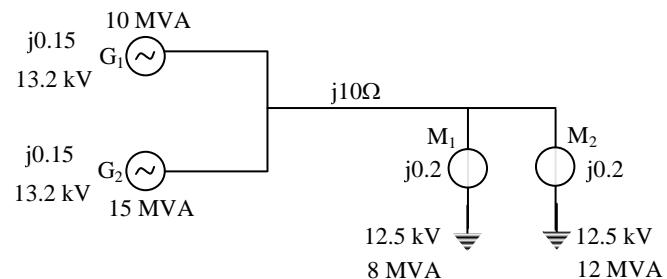


$$X_{G_1} = j0.15 \times \frac{50}{10} \times \left(\frac{13.2}{13.8} \right)^2 = j0.686$$

$$X_{G_2} = j0.15 \times \frac{50}{15} \times \left(\frac{13.2}{13.8} \right)^2 = j0.457$$

$$X_{T,L} = \frac{10 \times 50}{(13.8)^2} = 2.625$$

$$X_{M_1} = 0.2 \times \left(\frac{50}{8} \right) \times \left(\frac{12.5}{13.8} \right)^2 = 1.02$$

$$X_{M_2} = 0.2 \times \left(\frac{50}{12} \right) \times \left(\frac{12.5}{13.8} \right)^2 = 0.683$$

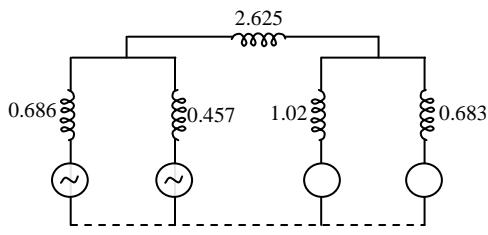
29. Ans: 0.36 (Range: 0.2 to 0.5)

Sol: $I = 0.3 \text{ A}$, $M = 800 \sin\left(\theta - \frac{2\pi}{9}\right) \mu\text{H}$.

$$\theta = 100^\circ = \frac{5\pi}{9} \text{ rad}$$

For EDM instrument, $T_d = I^2 \frac{dM}{d\theta}$

$$= (0.3)^2 \times 800 \cos\left(\frac{5\pi}{9} - \frac{2\pi}{9}\right)$$

$$= 36 \mu\text{Nm}.$$

Now, controlling torque $T_C = K\theta$

At balance condition, $T_d = T_C$

$$K = \frac{36}{100} \mu\text{Nm/degree}$$

$$= 0.36 \mu\text{Nm/degree}$$

30. Ans: 30 Amp

Sol: $\Rightarrow V_0 = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times 200\pi}{\pi} \cos 120^\circ$

$$V_0 = -200 \text{ volt}$$

$$P_0 = V_0 I_0 = 6000 \text{ W}$$

$$I_0 = \frac{6000}{200} = 30 \text{ Amp}$$

31. Ans: (D)

Sol: Let $f(z) = \frac{e^z + \sin(z)}{\left(z - \frac{\pi}{2}\right)^4} = \frac{\phi(z)}{(z - z_o)^{n+1}}$

Then the singular point of $f(z)$ is $z = \frac{\pi}{2}$

Here, the singular point $z = \frac{\pi}{2}$ lies in the

given region $\left|z - \frac{\pi}{2}\right| = 4$

Now, we can evaluate the given integral by using Cauchy's integral formula

$$\text{i.e. } \oint_C f(z) dz = \oint_C \frac{\phi(z)}{(z - z_o)^{n+1}} dz = \frac{2\pi i}{n!} \phi^{(n)}(z_o)$$

$$\Rightarrow \oint_C f(z) dz = \oint_C \frac{e^z + \sin(z)}{\left(z - \frac{\pi}{2}\right)^{3+1}} dz$$

$$\Rightarrow \oint_C f(z) dz = \frac{2\pi i}{3!} \phi''' \left(\frac{\pi}{2} \right) = \frac{2\pi i}{6} (e^z - \cos z) \Big|_{z=\frac{\pi}{2}}$$

$$\therefore \oint_C f(z) dz = \frac{\pi i}{3} e^{\pi/2}$$

32. Ans: (A)

Sol: Given that $\bar{f} = x^2 \bar{i} + y^2 \bar{j} + z^2 \bar{k}$

New, (W.D) Work done

$$= \int_C \bar{f} \cdot d\bar{r} \quad \text{where } \bar{f} = f_1 \bar{i} + f_2 \bar{j} + f_3 \bar{k} \text{ &}$$

$$\bar{r} = x \bar{i} + y \bar{j} + z \bar{k}$$

$$\Rightarrow \text{W.D} = \int_A^B [f_1 dx + f_2 dy + f_3 dz]$$

$$\Rightarrow \text{W.D} = \int_{(0,0,0)}^{(3,6,10)} [x^2 dx + y^2 dy + z^2 dz]$$


$$\Rightarrow W.D = \left(\frac{x^3}{3} + \frac{y^3}{3} + \frac{z^3}{3} \right)_{(0,0,0)}^{(3,6,10)}$$

$$= \frac{(3)^3}{3} + \frac{(6)^3}{3} + \frac{(10)^3}{3}$$


$$\therefore W.D = \frac{1243}{3}$$

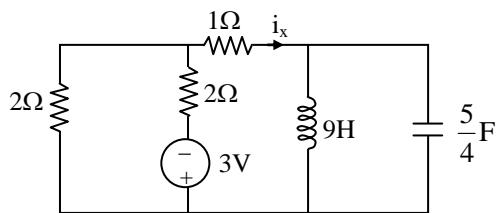33. Ans: (D)

Sol: At $t = 0^-$, the circuit is as shown below



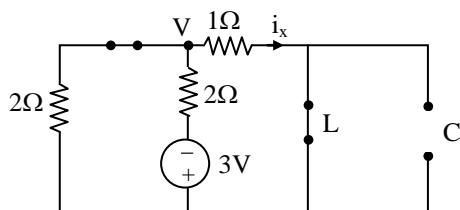Assume up to $t = 0^-$, the circuit is in steady state then the equivalent circuit is



Applying nodal analysis,


$$\Rightarrow \frac{V}{2} + \frac{V+3}{2} + \frac{V}{1} = 0$$

$$\Rightarrow V = \frac{-3}{4} V$$

$$\therefore i_x = \frac{V}{1} = \frac{-3}{4} A$$

$$\Rightarrow i_L(0^-) = i_x = \frac{-3}{4} A \text{ and } V_c(0^-) = 0V$$

At $t = 0^+$ the circuit becomes

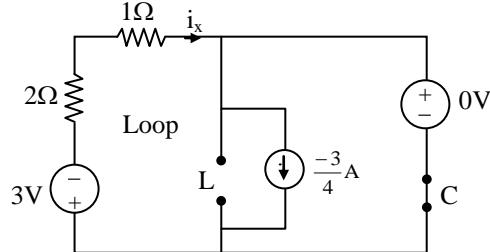

Applying kVL for the outer loop

$$\Rightarrow 3 + 3i_x + 0 = 0$$


$$\Rightarrow i_x = -1A$$

$\therefore i_x$ at $t = 0^+$ is $-1A$

34. Ans: 14

Sol: $\tau = R_{eq} C \text{ sec}$

Evaluation of R_{eq} :

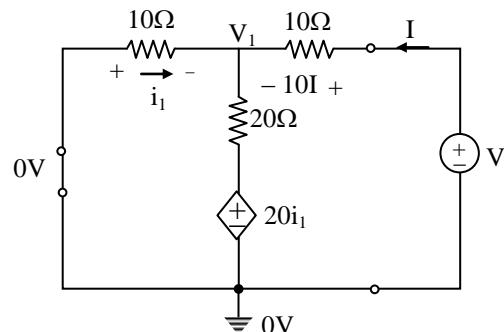

$$\text{By KVL} \Rightarrow 0 - 10i_1 - V_1 = 0 \Rightarrow V_1 = -10i_1 \quad \dots\dots (1)$$

$$\text{By KVL} \Rightarrow V_1 + 10I - V = 0 \Rightarrow V_1 = V - 10I \quad \dots\dots (2)$$

$$\text{Nodal} \Rightarrow -i_1 + \frac{V_1 - 20i_1}{20} - I = 0$$

$$\Rightarrow -40i_1 + V_1 = 20I$$

$$\Rightarrow V_1 = 4I$$

$$\Rightarrow V - 10I = 4I \Rightarrow V = 14I \Rightarrow \frac{V}{I} = R_{eq} = 14$$

$$\text{So, } \tau = R_{eq}C = 14 \times 1 \mu\text{F} = 14 \mu\text{sec}$$

35. Ans: (A)**Sol:**

$$\begin{bmatrix} D_x \\ D_y \\ D_z \end{bmatrix} = \varepsilon_0 \begin{bmatrix} 3 & 1 & 1 \\ 1 & 3 & 1 \\ 1 & 1 & 3 \end{bmatrix} \begin{bmatrix} 2 \\ 2 \\ 0 \end{bmatrix}$$

$$D_x = \varepsilon_0 [6+2]$$

$$D_y = \varepsilon_0 [2+6]$$

$$D_z = \varepsilon_0 [2+2]$$

$$\Rightarrow D = D_x + D_y + D_z$$

$$= 8\varepsilon_0 \hat{a}_x + 8\varepsilon_0 \hat{a}_y + 4\varepsilon_0 \hat{a}_z$$

36. Ans: 0.43 (range 0.42 to 0.44)

$$\text{Sol: } \frac{C(s)}{R(s)} = \frac{1}{1+Ts}$$

$$C(s) = \frac{6}{1+Ts}$$

$$C(t) = \frac{6}{T} e^{-t/T}$$

$$\text{At } t=0, C(t) = 6/T = 4 \Rightarrow T = 3/2$$

$$\text{At } t=t_1,$$


$$3 = \frac{6}{T} e^{-t_1/T}$$

$$3 = \frac{2}{3} \times 6 e^{-t_1/3}$$

$$3 = \frac{2}{3} \times 6 e^{-t_1^{2/3}}$$

$$\frac{3}{4} = e^{-2t_1/3}$$


$$\Rightarrow t_1 = 0.43 \text{ sec.}$$

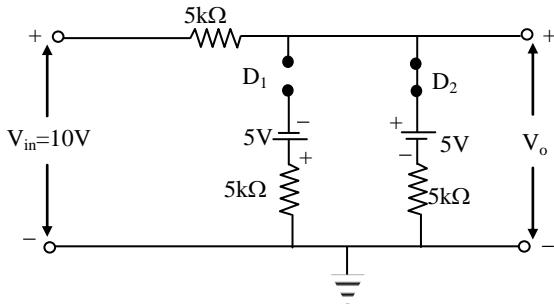37. Ans: 0.5**Sol:** When $V_{in}=10V$, 'D₁' OFF & 'D₂' ON

$$\therefore I_{D_2} = \frac{10-5}{10k} = 0.5 \text{ mA}$$

$$\Rightarrow V_o = 5 + 5k \cdot I_{D_2} = 5 + 5k \cdot (0.5 \text{ mA}) = 7.5V$$

When $V_{in} = 15V$, 'D₁' ON & 'D₂' OFF

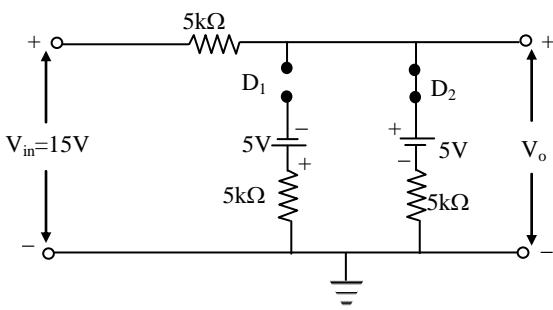


$$\therefore I_{D_2} = \frac{15-5}{10k} = \frac{10}{10k} = 1 \text{ mA}$$

$$\Rightarrow V_o = 5 + 5k (I_{D_2})$$

$$= 5 + 5k (1 \text{ mA})$$

$$= 5 + 5$$

$$\therefore V_o = 10V$$

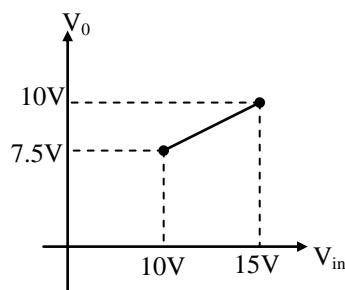

The slope of transfer characteristics

$$= \frac{10 - 7.5}{15 - 10} = \frac{1}{2} = 0.5$$

$$\Rightarrow x = -1 \text{ & } y = 2$$

$\therefore (x, y) = (-1, 2)$ is a critical point of $f(x, y)$

At $(x, y) = (-1, 2)$, $r = 8$, $s = 0$ & $t = 18$

$$\text{Here, } rt - s^2 = (8)(18) - (0)^2 = 144$$

$$\text{and } r = 8 > 0$$

$\therefore (x, y) = (-1, 2)$ is a local point of minima.

Hence, the minimum value of the function

$$f(x, y) \text{ at } (-1, 2) \text{ is } f(-1, 2) = -16$$

42. Ans: 3

$$\text{Sol: } n = \frac{T_{\text{sweep}}}{T_{\text{signal}}}$$

$$= \frac{\text{Total} 10 \text{ div} \times 3 \frac{\text{ms}}{\text{div}}}{\frac{1}{100 \text{ Hz}}}$$

$$(\because 200 \pi \text{ means } f_{\text{signal}} = 100 \text{ Hz})$$

$$= 10 \text{ div} \times 3 \frac{\text{msec}}{\text{div}} \times 100 \frac{\text{cycles}}{\text{sec}}$$

$$= 3000 \times 10^{-3} \text{ cycles}$$

$$= 3 \text{ cycles}$$

43. Ans: (A)

$$\text{Sol: } P(P) = P(Q) = P(R) = P(S) = \frac{1}{6}$$

$$P = P(P^C)P(Q^C)P(R^C)P(S) +$$

$$P(P^C)P(Q^C)P(R^C)P(S^C)P(P^C)P(Q^C)P(R^C)P(S)$$

+

$$= \frac{1}{6} \left(\frac{5}{6} \right)^3 + \left(\frac{1}{6} \right) \left(\frac{5}{6} \right)^7 +$$

$$= \left(\frac{1}{6} \right) \left(\frac{5}{3} \right)^3 \left\{ 1 + \left(\frac{5}{6} \right)^4 + \left(\frac{5}{6} \right)^8 +\right\}$$

$$= \left(\frac{1}{6} \right) \left(\frac{5}{6} \right)^3 \left\{ \frac{1}{1 - \left(\frac{5}{6} \right)^4} \right\}$$

$$= \left(\frac{1}{6} \right) \left(\frac{5}{6} \right)^3 \left\{ \frac{6^4}{6^4 - 5^4} \right\}$$

$$= \left(\frac{1}{6} \right) \left(\frac{5^3}{6^3} \right) \left\{ \frac{6^4}{6^4 - 5^4} \right\}$$

$$= \frac{125}{671}$$

44. Ans: (A)

Sol: MMF balance requires that

$$N_1 \bar{I}_1 = N_2 \bar{I}_2 + N_3 \bar{I}_3$$

$$N_1 \bar{I}_1 = N_1 \bar{I}_2 + \frac{1}{2} N_1 \bar{I}_3$$

Or

$$\bar{I}_1 = \bar{I}_2 + \frac{1}{2} \bar{I}_3 \dots\dots\dots (1)$$

Since the value of flux through all three coils is identical, $\bar{V}_1 = \bar{V}_2 = 2\bar{V}_3$.

$$\text{By Ohm's law, } \bar{I}_2 = \frac{\bar{V}_2}{R} = \frac{\bar{V}_1}{R} \dots\dots\dots (2)$$

$$\bar{I}_3 = \frac{\bar{V}_3}{R} = \frac{\bar{V}_1}{2R} \dots\dots\dots (3)$$

Use (2) and (3) in (1) to find

$$\bar{I}_1 = \frac{\bar{V}_1}{R} + \frac{\bar{V}_1}{4R} = \frac{5\bar{V}_1}{4R}$$

Hence,

$$Z_1 = \frac{\bar{V}_1}{\bar{I}_1} = \frac{4}{5} R$$

HEARTY CONGRATULATIONS TO OUR ESE - 2019 TOP RANKERS



KARTIKEYA SINGH EE AIR 10



RAJAT SONI E&T AIR 10



HARSHAL BHOSALE ME AIR 10



ABUZAR GAFFARI CE AIR 10



SHAMBHANI EE AIR 2



ANKUR MANLA E&T AIR 2



SAHIL GOYAL ME AIR 2



ABHISHEK KHANDO EE AIR 3



ROHIT KUMAR E&T AIR 3



KUMAR CHANDAN ME AIR 3



AMRITJEET CE AIR 3



ANKIT TAYAL EE AIR 4



AMIR KHAN E&T AIR 4



SAURAV ME AIR 4



AMAN GULIA CE AIR 4




KUMAN PURIYAN EE AIR 5



RISHABH CHANDRA CE AIR 5



NITISH LALWANI EE AIR 6

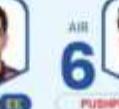

PUSHPAK ME AIR 6



KARAN SINGH CE AIR 6



KARTIKEY SINGH EE AIR 7



RAHUL JAIN E&T AIR 7



MANISH RAJPUT ME AIR 7



KULDEEP KUMAR E&T AIR 8



HEMANT KUMAR ME AIR 8



TUSHAR KUMAR CE AIR 8




DEEPITA ROY EE AIR 9



BHUPESH KARMAKAR E&T AIR 9



G. BABAPARA ME AIR 9

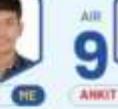

ANKIT KUMAR CE AIR 9



ANJALI SHARMA EE AIR 10



GEETA DEEWALI E&T AIR 10



SUMIT BHANDOO ME AIR 10

and many more...

TOTAL SELECTIONS in Top 10: **33**

(EE: **9**, E&T: **8**, ME: **9**, CE: **7**)

and many more...



DIGITAL CLASSES

for

ESE 2020/2021

General Studies &
Engineering Aptitude

GATE 2020/2021

Computer Science &
Information Technology

Access the Course at

www.deep-learn.in

45. Ans: 52.35 Range (50 to 55)

Sol: Without capacitor:

$$\text{Total } P_{\text{old}} = 150 \text{ kW}$$

$$\begin{aligned} \text{Total } Q_{\text{old}} &= \frac{100}{0.8} \times 0.6 + \frac{50}{0.707} \times 0.707 \\ &= 125 \text{ kVAr} \end{aligned}$$

To make overall pf to be 0.9 lag, after keeping capacitor

$$\cos \phi_{\text{new}} = \frac{P}{\sqrt{P^2 + Q_{\text{new}}^2}}$$

$$0.9 = \frac{150}{\sqrt{150^2 + Q_{\text{new}}^2}}$$

$$Q_{\text{new}} = 72.65 \text{ kVAr}$$

$$\begin{aligned} \text{Now capacitor bank rating, } Q_c &= Q_{\text{old}} - Q_{\text{new}} \\ &= 52.35 \text{ kVAr} \end{aligned}$$

46. Ans: (B)

Sol: Conduction of FD each time = conduction of each SCR


$$\alpha - 30 = 150 - \alpha$$

$$\alpha = 90^\circ$$

$$\frac{(i_T)_{\text{rms}}}{(i_{FD})_{\text{rms}}} = \frac{I_0 \sqrt{\frac{150 - \alpha}{360}}}{I_0 \sqrt{\frac{\alpha - 30}{120}}} = \frac{1}{\sqrt{6}} = \frac{1}{\sqrt{2}\sqrt{3}} = \frac{1}{\sqrt{3}}$$

47. Ans: (A)

Sol:

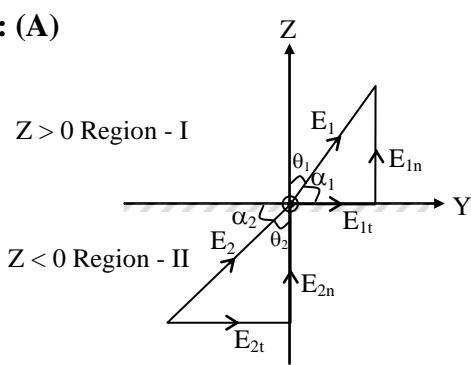

The tangential component in region I is

$$\bar{E}_{1t} = 3\hat{a}_x + 5\hat{a}_y$$

The normal component in region I is

$$\bar{E}_{1n} = 2\hat{a}_z$$

The tangential component of the second region is

$$\bar{E}_{2t} = \bar{E}_{1t} = 3\hat{a}_x + 5\hat{a}_y$$

For free of charge $\bar{D}_{2n} = \bar{D}_{1n}$

$$\epsilon_{r_2} \bar{E}_{2n} = \epsilon_{r_1} \bar{E}_{1n}$$

$$\bar{E}_{2n} = \frac{\epsilon_{r_1}}{\epsilon_{r_2}} \bar{E}_{1n}$$

$$= \frac{2}{4} \times 2\hat{a}_z$$

$$\therefore \hat{E}_{2n} = 1\hat{a}_z$$

$$\tan \theta_2 = \frac{E_{2t}}{E_{2n}} = \frac{\sqrt{3^2 + 5^2}}{1} = \sqrt{34}$$

$$\therefore \theta_2 = \tan^{-1}(\sqrt{34}) = 80.27^\circ$$

$$\therefore \alpha_2 = 90 - \theta_2 = 9.73^\circ$$

$$\tan \alpha_1 = \frac{E_{1n}}{E_{1t}} = \frac{2}{\sqrt{3^2 + 5^2}} = \frac{2}{\sqrt{34}} = 0.343$$

$$\therefore \alpha_1 = \tan^{-1}(0.343) = 18.93^\circ$$

$$\therefore \alpha_1 = 18.93^\circ, \alpha_2 = 9.73^\circ$$

48. Ans: (D)

Sol: Select line from ω_2 rise to 100 rad/sec.

$$\text{Slope} = \left(\frac{M_2 - M_1}{\log \omega_2 - \log \omega_1} \right)$$

$$\Rightarrow -20 = \left(\frac{0 - 6}{\log 100 - \log \omega_2} \right)$$

$$\Rightarrow \log 100 - \log \omega_2 = \frac{-6}{-20} = 0.3$$

$$-\log \omega_2 = 0.3 - 2$$

$$\log \omega_2 = 1.7$$

$$\omega_2 = 50.11 \approx 50 \text{ rad/sec}$$

$$\Rightarrow TFG(s)H(s) = \frac{K(1+S/20)}{S(1+S/50)(1+S/100)}$$

$$\omega_{gc} = 100 \text{ rad/sec} \text{ [from figure]}$$

$$PM = 180^\circ + \angle G(j\omega)H(j\omega)|_{\omega_{gc}}$$

$$= 180^\circ + \left[-90^\circ + \tan^{-1}\left(\frac{\omega_{gc}}{20}\right) - \tan^{-1}\left(\frac{\omega_{gc}}{50}\right) - \tan^{-1}\left(\frac{\omega_{gc}}{100}\right) \right]$$

$$PM = 180^\circ + \left[-90^\circ + \tan^{-1}\left(\frac{100}{20}\right) - \tan^{-1}\left(\frac{100}{50}\right) - \tan^{-1}\left(\frac{100}{100}\right) \right] \\ = 60^\circ$$


49. Ans: (B)

$$\text{Sol: } G(s)H(s) = \frac{k}{(s+2)^{10}}$$

$$\text{Centroid} = \frac{\sum \text{poles} - \sum \text{zeroes}}{p-z}$$

$$= \frac{(-2)10 - 0}{10} = -2$$
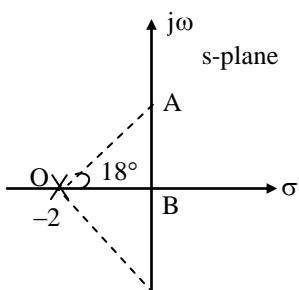
$$\text{Angle of asymptotes} = \frac{(2q+1)\pi}{p-z} \\ = 18^\circ, 54^\circ \dots \dots$$



$$\cos 18^\circ = \frac{OB}{OA}$$


$$\Rightarrow OA = \frac{OB}{\cos 18^\circ} = \frac{2}{0.95} = 2.105$$

Maximum value of k for stability

$$= \frac{\text{product of distance from poles}}{\text{product of distance from zeroes}} \\ = (2.105)^{10}$$

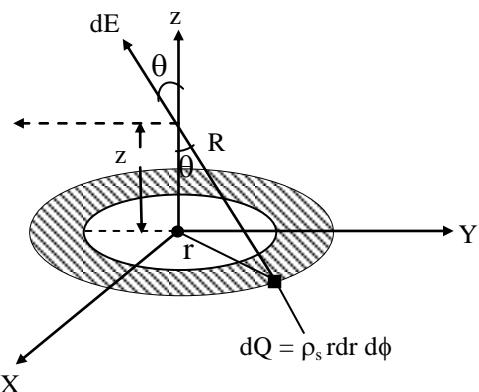50. Ans: 54.63 (53 to 56)

Sol: From fig. by symmetry only the z-components of the field exists along the z-axis.



$$dQ = \rho_s r dr d\phi$$

$$\cos \theta = \frac{z}{R}, R = \sqrt{r^2 + z^2}$$

Hence

$$dE_z = \frac{dQ}{4\pi \epsilon_0 R^2} \cos \theta$$

$$= \frac{\rho_s r dr d\phi}{4\pi \epsilon_0 (r^2 + z^2)} \cdot \frac{z}{\sqrt{r^2 + z^2}}$$

$$= \frac{\frac{100 \times 10^{-6}}{r} \times r dr d\phi \times z}{4\pi \times \frac{1}{36\pi} \times 10^{-9} (r^2 + z^2)^{3/2}}$$

At $z = 10 \text{ m}$

$$E_Z = 9 \times 10^6 \int_{r=1}^2 \int_{\phi=0}^{2\pi} \frac{dr d\phi}{(r^2 + 100)^{\frac{3}{2}}}$$

$$= 18\pi \times 10^6 \int_{r=1}^2 \frac{dr}{(r^2 + 100)^{3/2}}$$

$$= 18\pi \times 10^6 \left. \frac{r}{100\sqrt{r^2 + 100}} \right|_{r=1}^2$$

$$= 54.63 \text{ kV/m}$$

51. Ans: (A)

Sol: $T = 1 \text{ msec}$

$$R = 5\Omega$$

$$L = 0.2 \text{ H}$$

$$T_a = \frac{L}{R} = 0.04$$

$$\frac{T_{OFF}}{T_{ON}} = \frac{(1-D)T}{DT} = 1 = D = 0.5$$

$$T_{ON} = DT = 0.5 \text{ m}$$

$$V_0 = DV_s$$

$$V_0 = 0.5 \times 100$$

$$V_0 = 50\text{V}$$

$$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-\frac{T_{ON}}{T_a}}}{1 - e^{-\frac{T}{T_a}}} \right] = 10.062 \text{ A}$$

$$I_{min} = \frac{V_s}{R} \left[\frac{e^{\frac{T_{ON}}{T_a}} - 1}{e^{\frac{T}{T_a}} - 1} \right] = 9.938 \text{ A}$$

$$\Delta i_0 = I_{max} - I_{min}$$

$$\Delta i_0 = 0.125 \text{ A}$$

ISRO



ONLINE TEST SERIES

No. of Tests : 15

Subject Wise Tests : 12 | Mock Tests : 3

**Indian Space Research Organisation (ISRO)
Recruitment of Scientist/Engineer 'SC'**

ELECTRONICS | MECHANICAL | COMPUTER SCIENCE

Starts from **5th November 2019**

All tests will be available till 12-01-2020.

040 - 48539866 / 040 - 40136222 | testseries@aceenggacademy.com



52. Ans: (B)

Sol: $X(z) = \frac{z}{(z-1)^3}$

$$\Rightarrow z^{n-1}X(z) = \frac{z^n}{(z-1)^3}$$

Poles of $z^{n-1} X(z)$ are given by,

$$(z-1)^3 = 0$$

$$z = 1, z = 1, z = 1$$

i.e., 'z = 1' is a repeated pole of index 'm + 1 = 3'

Now,

Residue of $z^{n-1} X(z)$ at repeated pole 'z = a' of index 'm + 1'

$$= \frac{1}{m!} \lim_{z \rightarrow a} \frac{d^m}{dz^m} (z-a)^{m+1} z^{n-1} X(z)$$

∴ Residue of $z^{n-1} X(z)$ at repeated pole 'z =

$$1' of index '3' = \frac{1}{2!} \lim_{z \rightarrow 1} \frac{d^2}{dz^2} (z-1)^3 \frac{z^n}{(z-1)^3}$$

$$R = \frac{1}{2} \lim_{z \rightarrow 1} \frac{d^2}{dz^2} z^n$$

$$R = \frac{1}{2} \lim_{z \rightarrow 1} n(n-1)z^{n-2}$$

$$R = \frac{1}{2} n(n-1)u(n)$$

Now, By Residue method,

$Z^{-1}\{X(z)\}$ = Sum of all the residues of $z^{n-1}X(z)$

$$Z^{-1}\left\{\frac{z}{(z-1)^3}\right\} = \frac{n(n-1)}{2} u(n)$$

53. Ans: 87.6 (Range: 86 to 89)

Sol: $P_s = P_e = 1.0$

$$P_{M_1} = \frac{EV}{X_{I_{eq}}} = (EV)y_{eq} = 2.0 (1.2 \times 1.0) = 2.4$$

$$\delta_0 = \sin^{-1} \left(\frac{P_s}{P_{M_1}} \right)$$

$$= \sin^{-1} \left(\frac{1.0}{2.4} \right) \text{ele.deg ree} \Rightarrow 24.62^\circ$$

$$\delta_{0(\text{rad})} = \delta_0 \times \frac{\pi}{180} = 0.429$$

Fault: $P_{e_2} = 0, P_{m_2} = 0$

$$\delta_m = 180^\circ - \sin^{-1} \left(\frac{P_s}{P_{m_3}} \right)$$

$$P_{m_3} = P_{m_1}$$

$$\delta_m = 180^\circ - \sin^{-1} \left(\frac{1.0}{2.4} \right)$$

$$= 180^\circ - 24.62^\circ = 155.38^\circ$$

$$\delta_{m(\text{rad})} = \delta_m \times \frac{\pi}{180} = 2.711$$

$$\delta_c = \cos^{-1} \left[\frac{P_s(\delta_m - \delta_e) + P_{m_3} \cos \delta_m}{P_{m_3}} \right]$$

$$\delta_c = \cos^{-1} \left[\frac{1.0(\delta_m - \delta_e) + 2.4 \cos \delta_m}{2.4} \right] \text{ele.deg ree}$$

$$\delta_c = \cos^{-1} \left[\frac{1.0(2.711 - 0.429) + 2.4 \cos(155.38)}{2.4} \right]$$

$$= 87.6^\circ$$

54. Ans: (A)

Sol: $tu(t) \leftrightarrow \frac{1}{s^2}$

$$(t-2)u(t-2) \leftrightarrow \frac{e^{-2s}}{s^2} [\because x(t-t_0) \leftrightarrow e^{-st_0} X(s)]$$

$$e^{-t}(t-2)u(t-2) \leftrightarrow \frac{e^{-2(s+1)}}{(s+1)^2} [\because e^{s_0 t} x(t) \leftrightarrow X(s-s_0)]$$

55. Ans: (D)

Sol: $\rightarrow (HL) = 1000H$

$$\rightarrow (A) = 45H$$

$$\rightarrow (B) = 96H$$

$\rightarrow (HL) = 1000H$ pushed to top of stack

$$\rightarrow (A) = 45H = 0100\ 0101$$

$$(B) = 96H = 1001\ 0110$$

$$\underline{\underline{(A) = DBH = 1101\ 1011}}$$

$$\overline{CY} = 0, P = 0, AC = 0, Z = 0, S = 1$$

$$\rightarrow (HL) = 1000H - 1 = 0FFFH$$

$\rightarrow (TOS) = 1000H$ popped into DE pair

$$(DE) = 1000H$$

\rightarrow Decimal Adjust Accumulator After
Addition

$$\begin{array}{r} (A) = DBH = 1101\ 1011 \\ + 66H = 0110\ 0110 \end{array}$$

$$(A) = 41H = 0100\ 0001$$

$$CY=1, P=1, AC=1, Z=0, S=0$$

\rightarrow Double Add HL to DE

$$(HL) = 0FFFH$$

$$(DE) = 1000H$$

$$\underline{\underline{(HL) = 1FFFH}}$$

$$\rightarrow (\text{flag register}) = 00 \times 1 \times 1 \times 0 = 0001\ 0100$$

$$= 04H$$

$$(HL) = 1FFFH \& (PSW) = 4114H$$