



# ACE

## Engineering Academy

Head Office : Sree Sindhi Guru Sangat Sabha Association, # 4-1-1236/1/A, King Koti, Abids, Hyderabad – 500001.

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Lucknow | Patna | Bengaluru | Chennai | Vijayawada | Vizag | Tirupati | Kukatpally | Kolkata | Ahmedabad

### Branch: Instrumentation Engineering - SOLUTIONS

**01. Ans: 496 (No Range)**

**Sol:** For n-bit comparator,  
Number of combinations for which  $A > B$

$$\text{is } \frac{2^{2n} - 2^n}{2}$$

Here,  $n = 5$ .


(It is a 4 bit magnitude comparator)

$$= \frac{2^{2 \times 5} - 2^5}{2} = 496$$

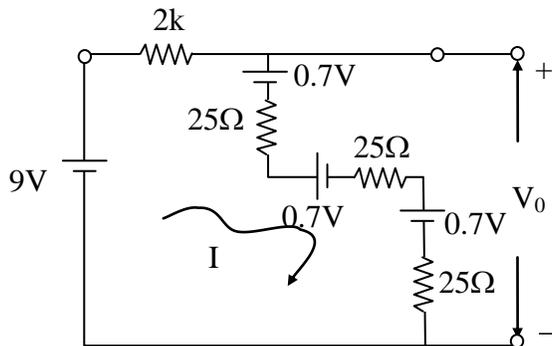**02. Ans: (a)**

**Sol:** In the given circuit  $D_1$ , zener &  $D_4 \rightarrow$  F.B  
 $D_3$  &  $D_2 \rightarrow$  R.B

When zener F.B it behaves like a pn diode



Then the equation for the circuit is

$$-9 + I(2k) + 0.7 + I(25) + 0.7 + I(25) + 0.7 + I(25) = 0$$

From the above circuit I is given by

$$I = 3.325 \text{ mA}$$

$$\begin{aligned} V_0 &= (0.7 + 25I)3 \\ &= 2.1 + 75 \times 3.325 \times 10^{-3} \\ &= 2.1 + 0.249 \\ &= 2.35 \text{ V} \end{aligned}$$

**03. Ans: (a)**

**Sol:** For series RLC transient current to be oscillatory

$$\xi < 1$$

$$\frac{R}{2} \sqrt{\frac{C}{L}} < 1$$

$$R < 2 \sqrt{\frac{L_{eq}}{C_{eq}}}$$

$$R < 2 \sqrt{\frac{1}{9}}$$

$$R < \frac{2}{3} \Omega$$

**04. Ans: 1 (No range)**

**Sol:** Let  $A = \begin{bmatrix} 1 & 2 & 0 \\ 0 & 1 & 3 \\ 0 & 0 & 1 \end{bmatrix}$

A is the upper triangular matrix eigen value is 1 only

$$\text{Consider } (A - I) = \begin{bmatrix} 0 & 2 & 0 \\ 0 & 0 & 3 \\ 0 & 0 & 0 \end{bmatrix}$$

Clearly rank of  $(A - I) = 2$

Geometric multiplicity of eigen value 1

= No. of linearly independent eigen vectors

$$= n - r$$

$$= 3 - 2 = 1$$

**05. Ans: 10.5 (no range)**

**Sol:** The average current

$$I_{CC} = \frac{I_{CCH} + I_{CCL}}{2} = \frac{2.4 + 1.8}{2} = 2.1 \mu\text{A}$$

The average power dissipation

$$P_D = V_{CC} \times I_{CC} = 5 \text{ V} \times 2.1 \mu\text{A} = 10.5 \mu\text{W}$$



**ACE**<sup>®</sup>  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs



# ESE - MAINS

Classes Start from: **13<sup>th</sup> FEB 2020**



@ DELHI



Students who Qualify in Prelims  
can avail **100 % Fee Waiver**



@ HYDERABAD

ESE-2018, 2019 Prelims Qualified Students are also eligible for Fee Discounts



/aceacademy



/ACE\_Enggacademy




/aceenggacademy

- H.O. # 4-1-1236/1/A, Sindhu Sadan, King Koti Road, Abids, Hyderabad - 500001, Telangana, India.
- Ph: 040-23234418/19/20 , 040-24750437.
- Email: hyderabad@aceenggacademy.com
- [www.aceenggacademy.com](http://www.aceenggacademy.com)



06. Ans: (d)

Sol:

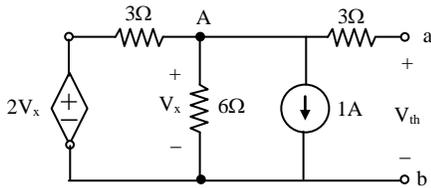

Current flowing through  $3\Omega$  is zero so  $V_{th} = V_x$


Apply KCL at node A, then

$$\frac{V_x - 2V_x}{3} + \frac{V_x}{6} + 1 = 0$$

$$-2V_x + V_x + 6 = 0$$

$$V_x = 6V$$

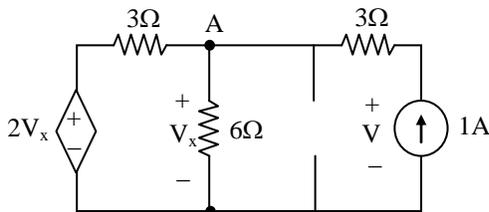$R_{th}$  can be find out by exciting the circuit with 1A, replace all independent sources by their internal resistances



By KCL at node A

$$\frac{V_x}{6} + \frac{(V_x - 2V_x)}{3} - 1 = 0$$

$$V_x - 2V_x - 6 = 0$$

$$V_x = -6V$$

$$V = 3 + V_x = 3 - 6 = -3V$$

$$R_{th} = \frac{V}{I} = \frac{-3}{1} = -3\Omega$$

07. Ans: (c)


Sol:  $\% \eta_{FM} = (1 - J_0^2(\beta)) \times 100$

$$= (1 - 0.5^2) \times 100$$

$$= 75\%$$

08. Ans: 40 (no range)

Sol:

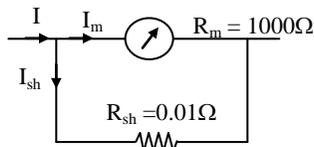

$$V_m = V_{sh}$$

$$V_m = 400mV$$

$$I_{sh} = \frac{V_m}{R_{sh}} = \frac{400 \times 10^{-3}}{0.01}$$

$$I_{sh} = 40A$$

09. Ans: (a)

Sol: Given  $x(t) = 3e^{-t}u(t)$ ,  $h(t) = 2e^{-2t}u(t)$

Apply L.T

$$X(s) = \frac{3}{s+1}, H(s) = \frac{2}{s+2}$$

$$Y(s) = X(s)H(s) = \frac{6}{(s+1)(s+2)}$$

$$Y(s) = \frac{6}{s+1} - \frac{6}{s+2}$$

Apply ILT

$$y(t) = 6 [e^{-t} - e^{-2t}]u(t)$$

10. Ans: (d)

Sol:  $F = \Sigma m(0,2,3,4,6)$

$$= \Sigma m(1,5,7)$$

$$= \Pi M(0,2,3,4,6)$$

QP				
R	00	01	11	10
0	0		0	0
1	0			0

$$F = P[R + \bar{Q}]$$

11. Ans: 7.07 (Range: 6.5to7.5)

Sol: Vertical sensitivity = 4 V/cm

Peak to peak amplitude = 5 cm

$\therefore V_{p-p} = (\text{vertical sensitivity})$

$\times (\text{distance between peak to peak})$

$$V_{pp} = 4 \times 5 = 20V$$

$$V_p = \frac{V_{PP}}{2} = \frac{20}{2} = 10V$$




$$V_{\text{rms}} = \frac{V_p}{\sqrt{2}} = \frac{10}{\sqrt{2}}$$

$$\Rightarrow V_{\text{rms}} = 7.07 \text{ V}$$

**12. Ans: 6 (No range)**

**Sol:**

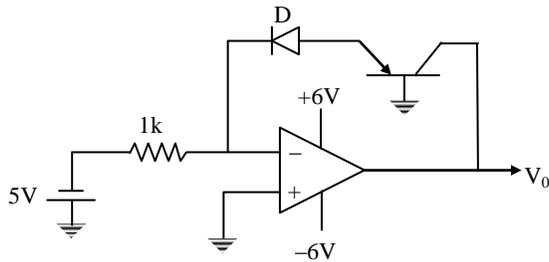

In this circuit diode tries to conduct but the transistor which is in cut-off region does not allow

any current and hence negative feedback does not exist.

Therefore op-amp acts as comparator. So output voltage  $V_0 = +6\text{V}$

**13. Ans: 0.36**

**Sol:**  $C = \frac{2x}{\Delta t}$

$C = \text{velocity of light} = 3 \times 10^8 \text{ (m/sec)}$

$x = \text{distance that can be measured by laser ranging}$

$\Delta t = \text{time distance resolved}$

$$x = \frac{C \times \Delta t}{2} = \frac{3 \times 10^8 \times 2.4 \times 10^{-9}}{2}$$

$$x = 0.36 \text{ m}$$

**14. Ans: 0 (No range)**

**Sol:**  $\text{Grad}(\ln r) = \frac{1}{r} \frac{1}{r} \vec{r} = \frac{\vec{r}}{r^2}$

$$\text{Curl} (r^2 \text{ grad } \ln r) = \text{curl} \left( r^2 \frac{\vec{r}}{r^2} \right)$$

$$= \text{curl} (\vec{r}) = 0$$

**15. Ans: 0.4 (No range)**

**Sol:**  $\frac{4s+10}{s} = 4 + \frac{10}{s} = 4 \left[ 1 + \frac{10}{4s} \right]$

$$= 4 \left[ 1 + \frac{1}{\frac{4}{10}s} \right]$$

$$= 4 \left[ 1 + \frac{1}{0.4s} \right]$$

$$= 4 \left[ 1 + \frac{1}{T_1 s} \right]$$

$$\therefore T_1 = \text{reset time} = 0.4 \text{ sec}$$

**16. Ans: 53 (No range)**

**Sol:**  $V(2x + 3y) = 2^2 V(x) + 3^2 V(y)$

$$= (4 \times 2) + (9 \times 5)$$

$$= 53$$

**17. Ans: 5 (No range)**

**Sol:**  $Z_{11} = 6\Omega, Z_{12} = Z_{21} = 4\Omega$

For symmetrical network,  $Z_{11} = Z_{22} = 6\Omega$

ABCD parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

Now from Z-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 = 6I_1 + 4I_2 \dots\dots (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 = 4I_1 + 6I_2 \dots\dots (2)$$

By putting  $V_2 = 0$  in equation (2)

$$4I_1 = -6I_2$$

Put value of  $I_1$  in equation (1) than

$$V_1 = 6 \left( -\frac{6}{4} \right) I_2 + 4I_2$$

$$= I_2 \left[ \frac{-36}{4} + 4 \right] = -5I_2$$

$$\text{So } \frac{V_1}{I_2} = -5$$

$$B = -(-5) = 5\Omega$$



**ACE<sup>®</sup>**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs



**48**  
ALL INDIA  
1<sup>st</sup> RANKS IN GATE

**15**  
ALL INDIA  
1<sup>st</sup> RANKS IN ESE

Hyderabad | Ahmedabad | Pune | Delhi | Bhubaneswar | Bangalore | Chennai | Lucknow | Visakhapatnam | Vijayawada | Tirupati | Kolkata

Head Office Address: # 4-1-1236/1/A, Sindhu Sadan, King Koti, Abids, Hyderabad - 500001, Telangana, India.

# SUMMER

## SHORT TERM BATCHES GATE + PSUs - 2021

### @ HYDERABAD

Streams: EC, EE, ME, CE, CSIT, IN & PI

28<sup>th</sup> April, 5<sup>th</sup> May,  
10<sup>th</sup> May, 17<sup>th</sup> May, 25<sup>th</sup> May,  
1<sup>st</sup> June, 8<sup>th</sup> June, 2020

Course Duration: 55 to 60 Days

☎ 040-23234418/19/20, 040-24750437  
✉ hyderabad@aceenggacademy.com

### @ DELHI

Streams: EC, EE, ME, CE, IN & PI

10<sup>th</sup> & 20<sup>th</sup>  
May 2020

Course Duration: 60 to 70 Days

☎ 7838971777 (Call or Whatsapp)  
✉ delhi@aceenggacademy.com

**Early Bird Offer Rs. 3,000/- Register before 31<sup>st</sup> March 2020**

### Upcoming Batches @ HYDERABAD

#### GATE+PSUs-2021

Spark Batches : 10<sup>th</sup> May, 8<sup>th</sup> & 23<sup>rd</sup> June 2020.  
Regular Batches : 26<sup>th</sup> April, 10<sup>th</sup>, 24<sup>th</sup> May, 8<sup>th</sup>, 23<sup>rd</sup> June, 7<sup>th</sup>, 22<sup>nd</sup> July,  
5<sup>th</sup> & 20<sup>th</sup> August 2020.

#### ESE+GATE+PSUs-2021

Spark Batches : 10<sup>th</sup> May, 8<sup>th</sup> & 23<sup>rd</sup> June 2020.  
Regular Batches : 29<sup>th</sup> March, 26<sup>th</sup> April, 10<sup>th</sup>, 24<sup>th</sup> May,  
8<sup>th</sup>, 23<sup>rd</sup> June & 7<sup>th</sup> July 2020.

### Upcoming Batches @ DELHI

#### GATE+PSUs-2021

Weekend Batches : 28<sup>th</sup> Dec, 11<sup>th</sup> Jan & 8<sup>th</sup> Feb 2020.  
Regular Batches : 17<sup>th</sup> Feb, 7<sup>th</sup> March, 10<sup>th</sup> & 20<sup>th</sup> May 2020.

#### ESE+GATE+PSUs-2021

Weekend Batches : 28<sup>th</sup> Dec, 11<sup>th</sup> Jan & 8<sup>th</sup> Feb 2020.  
Regular Batches : 17<sup>th</sup> Feb, 7<sup>th</sup> March, 10<sup>th</sup> & 20<sup>th</sup> May 2020.

#### GATE+PSUs-2022

Weekend Batches : 28<sup>th</sup> Dec, 11<sup>th</sup> Jan & 8<sup>th</sup> Feb 2020.

#### ESE+GATE+PSUs-2022

Weekend Batches : 28<sup>th</sup> Dec, 11<sup>th</sup> Jan & 8<sup>th</sup> Feb 2020.

### SSC-JE Batches @ Hyderabad

New Batch Starts from: 10<sup>th</sup> May 2020

for Civil, Mechanical & Electrical



Scan QR Code for  
Upcoming Batches  
Details

☎ [www.aceenggacademy.com](http://www.aceenggacademy.com)

follow us on:    



**18. Ans: (b)**

**Sol:** Given  $f_i = 100 \text{ kHz}$

$$\text{Frequency at A} = f_A = \frac{100\text{kHz}}{10} = 10\text{kHz}$$

$$\text{Frequency at B} = f_B = \frac{10\text{kHz}}{20} = 500\text{Hz}$$

$$\text{Frequency at C} = f_C = \frac{500\text{Hz}}{16} = 31.25\text{Hz}$$

$$\text{Frequency at D} = f_D = \frac{31.25\text{Hz}}{8} = 3.9\text{Hz}$$

**19. Ans: (d)**

**Sol: Bag -1**

**Bag- 2**

5 Red

4 Red

7 Green

8 Green

$$\begin{aligned} \text{By total probability} &= \frac{1}{2} \times \frac{7}{12} + \frac{1}{2} \times \frac{8}{12} \\ &= \frac{15}{24} \end{aligned}$$

**20. Ans: 36 (No range)**

**Sol:** To get the peak current both NMOS and PMOS are operated in saturation at switching threshold  $V_m = \frac{V_{DD}}{2}$  and the peak current is given by

$$\begin{aligned} I_{\text{peak}} &= \frac{1}{2} \mu_n C_{\text{ox}} \left( \frac{W}{L} \right)_n \left( \frac{V_{DD}}{2} - V_m \right)^2 \\ &= \frac{1}{2} \times 300 \times 10^{-6} \times 1.5 \times (0.9 - 0.5)^2 \\ &= 36 \mu\text{A} \end{aligned}$$

**21. Ans: (d)**

**Sol:** 0 m corresponds to 0V

2m corresponds  $\rightarrow$

$$\begin{aligned} P = \rho gh &= 1.3 \times 10^3 \times 9.81 \times 2 \\ &= 25.506 \text{ (kPa)} \end{aligned}$$

Sensor output will be

$$V = 25 \left( \frac{\text{mV}}{\text{kPa}} \right) \times 25.506 \text{ (kPa)} = 0.638 \text{ V}$$

$$\text{Sensitivity of level measurement} = \frac{0.638 \text{ (V)}}{2 \text{ (m)}}$$

$$= 0.319 \left( \frac{\text{V}}{\text{m}} \right) = 3.19 \left( \frac{\text{mV}}{\text{cm}} \right)$$

**22. Ans: (c)**

$$\text{Sol: } S_{\text{AM}}(t) = 10 \cos(198\pi t) + 40 \cos(200\pi t) + 10 \cos(202\pi t)$$

Carrier term is  $= 40 \cos(200\pi t)$

$$A_C = 40, f_C = 100$$

LSB term:  $10 \cos(198\pi t)$

$$\frac{A_C \mu}{2} = 10 \quad f_C - f_m = 99$$

$$\mu = \frac{2 \times 10}{40} = 0.5, f_m = 1$$

message signal:  $A_m \cos(2\pi f_m t)$

$$\frac{A_m}{A_C} = \mu \Rightarrow A_m = \mu \cdot A_C = 0.5 \times 40 = 20$$

$$m(t) = 20 \cos(2\pi t)$$

**23. Ans: (c)**

**Sol:** By observing the N-MOS circuit, C is in parallel to the series combination of A and B. Thus,  $\bar{Y} = AB + C$

**24. Ans: (c)**

**Sol:** Given  $f_c = 1000\text{Hz}$  and  $f_s = 1500\text{Hz}$

$$\Omega_c = 2\pi f_c$$

$$\Omega_s = 2\pi f_s$$

$$\Omega_c = 2000\pi$$

$$\Omega_s = 3000\pi$$

For attenuation of  $-20\text{dB}$

$$-20 \log_{10}(x) = 20$$

$$\Rightarrow x = 10^{-1} = 0.1$$

$$\text{Here, } x = \delta_s = 0.1$$

Now,

$$N = \frac{\log_{10} \left[ \frac{1}{\delta_s^2} - 1 \right]}{2 \log_{10} \left( \frac{\Omega_s}{\Omega_c} \right)}$$

$$N = \frac{\log_{10}(100 - 1)}{2 \log_{10}(1.5)} = 5.67$$

$$N = 6$$



25. Ans: -1 (No range)


Sol: 
$$\lim_{x \rightarrow 0} \frac{\sin x}{x(x-1)} = \lim_{x \rightarrow 0} \frac{1}{x-1} \cdot \lim_{x \rightarrow 0} \frac{\sin x}{x}$$

$$= -1 \times 1$$

$$= -1$$

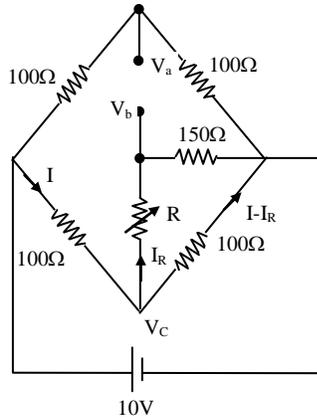26. Ans: 50.1Ω [49 to 51]

Sol: When bridge is balanced  $V_a = V_b$



$$V_a = \frac{10 \times 100}{200} = 5V$$

$$V_a = V_b = 5V$$

$$I_R = \frac{V_b}{150} = \frac{1}{30} A$$

$$10 - 100I - 100\left(I - \frac{1}{30}\right) = 0$$

$$I = \frac{1}{15} A$$

$$V_c = \left[\frac{1}{15} - \frac{1}{30}\right] \times 100 = 3.33V$$

$$|R| = \frac{V_b - V_c}{I_R} = \frac{5 - 3.33}{\left[\frac{1}{30}\right]} = 50.1\Omega$$

27. Ans: (b)

Sol: Given  $f(D)y = Q(x)$  .....(1)

where  $f(D) = D^2 + 3D + 2$

and  $Q(x) = \cos(x)$

C.F: Consider A.E,  $f(m) = 0$

$$\Rightarrow m^2 + 3m + 2 = 0$$

$$\Rightarrow m = -1, -2$$

$$\therefore y_c = c_1 e^{-x} + c_2 e^{-2x}$$

P.I: Here,  $Q(x) = \cos(x) = \cos(ax+b)$

and  $f(D) = \phi(D^2) = \phi(-a^2) = \phi(-1)$

$$= (-1) + 3D + 2 = 1 + 3D \neq 0$$

Now,

$$y_p = \frac{1}{1+3D} \times \frac{1-3D}{1-3D} \cos(x) = \frac{1-3D}{1-9D^2} \cos(x)$$

$$\Rightarrow y_p = (1-3D) \left[ \frac{1}{1-9(-1)} \cos(x) \right]$$

$$= (1-3D) \left( \frac{1}{10} \cos(x) \right)$$

$$\therefore y_p = \frac{\cos(x)}{10} + \frac{3}{10} \sin x$$


Hence, the general solution of (1) is

$$y = y_c + y_p$$

$$\text{i.e., } y = c_1 e^{-x} + c_2 e^{-2x} + \frac{\cos(x)}{10} + \frac{3}{10} \sin x$$

28. Ans: (c)

Sol:

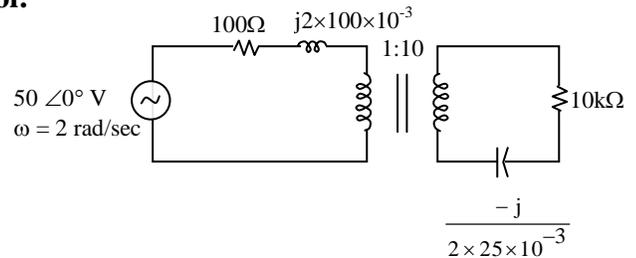

By transferring secondary impedance to primary then

$$z'_2 = \frac{z_2}{k^2} \quad k = \frac{10}{1} = 10$$

$$z'_2 = \frac{10k\Omega - \frac{j}{2 \times 25 \times 10^{-3}}}{100}$$

$$= 100 - \frac{j}{5} = 100 - j0.2$$

$$I_1 = \frac{50}{100 + j0.2 + 100 - j0.2}$$

$$= \frac{50}{200} = \frac{1}{4} = 250 \text{ mA}$$

$$I_2 = \frac{I_1}{k} = \frac{I_1}{10} = 25 \text{ mA}$$

So power dissipated in the 10kΩ resistor is

$$P = (25 \times 10^{-3})^2 \times 10k\Omega$$

$$= 6.25 \text{ W}$$



**ACE**<sup>®</sup>  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs

**48**  
ALL INDIA  
1<sup>st</sup> RANKS IN GATE

**15**  
ALL INDIA  
1<sup>st</sup> RANKS IN ESE

Hyderabad | Ahmedabad | Kothapet | Kukatpally | Delhi | Pune | Bhubaneswar | Lucknow | Bengaluru | Chennai | Vijayawada | Vizag | Tirupathi | Kolkata

# ESE / GATE / PSUs LONG TERM PROGRAM @ HYDERABAD

Batches Start From



**19<sup>th</sup> JAN 2020**



**25<sup>th</sup> FEB 2020**

Streams Offered : EC | EE | ME | CE | CSIT | IN & PI


## MORNING BATCHES



## EVENING BATCHES



## WEEKEND BATCHES

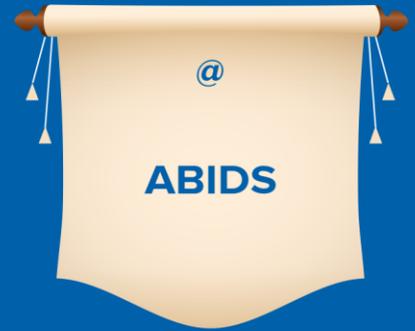

## COURSES OFFERED:

- Classroom Coaching
- Postal Coaching
- Online Test Series
- Interview Guidance
- Digital Classes

### New Batches for

**ESE + GATE + PSUs - 2022**

**GATE + PSUs - 2022**

Starts from:

**19<sup>th</sup> JAN 2020**

**25<sup>th</sup> FEB 2020**

### New Batches for

**ESE + GATE + PSUs - 2021**

Morning Batches @ Abids

**28<sup>th</sup> DEC & 19<sup>th</sup> JAN 2020**



Scan QR CODE for  
New Batch Details

### Hearty Congratulations to our ESE 2019 Top Rankers



### our GATE-2019 Rankers



**ABIDS**

☎ 040-23234418,19,20, 040-24750437

**KUKATPALLY**

☎ 040-40199966, 93476 99966

**DILSUKHNAGAR**

☎ 040-40209345, 040-40044451

[www.aceenggacademy.com](http://www.aceenggacademy.com)

follow us on:





**29. Ans: (a)**

**Sol:**  $\angle G(s) = -3 \omega_{pc} - 90^\circ = -180^\circ$

$$\Rightarrow \omega_{pc} = 30^\circ = \frac{\pi}{6}$$

$$\text{Magnitude (a)} = \frac{k}{\omega_{pc}} = \frac{6k}{\pi}$$

For stability  $a < 1$

$$\Rightarrow k < \frac{\pi}{6}$$

Therefore Range is  $0 < k < \frac{\pi}{6}$

**30. Ans: (a)**

**Sol:** Given  $x(n) = \frac{3^n}{n!}$

$$X(z) = \sum_{n=-\infty}^{\infty} x(n)z^{-n}$$

$$\text{Let } g(n) = \frac{1}{n!}$$

$$\therefore G(z) = Z\{g(n)\} = Z\left\{\frac{1}{n!}\right\}$$

$$G(z) = Z\left\{\frac{1}{n!}\right\} = \sum_{n=0}^{\infty} \frac{1}{n!} z^{-n}$$

$$G(z) = 1 + \frac{(1/z)}{1!} + \frac{(1/z)^2}{2!} + \frac{(1/z)^3}{3!} + \dots$$

$$G(z) = Z\left\{\frac{1}{n!}\right\} = e^{1/z} \dots \dots (1)$$

By property,

$$a^n g(n) \leftrightarrow G\left(\frac{z}{a}\right)$$

$$3^n \frac{1}{n!} \leftrightarrow e^{3/z}$$

$$\therefore X(z) = Z\left\{\frac{3^n}{n!}\right\} = e^{3/z}$$

**31. Ans: (a)**

**Sol:** Given  $f(D)y = Q(x) \dots \dots \dots (1)$

where  $f(D) = D^2 + 4D + 4$

&  $Q(x) = x^4 e^{-2x} = e^{-2x} \cdot x^4 = e^x \cdot V(x)$

Now,  $y_p = \frac{1}{f(D)} [e^{-2x} x^4]$

$$\Rightarrow y_p = e^{-2x} \left[ \frac{1}{f(D-2)} x^4 \right]$$


$$\Rightarrow y_p = e^{-2x} \left[ \frac{1}{(D-2)^2 + 4(D-2) + 4} x^4 \right]$$

$$\Rightarrow y_p = e^{-2x} \left[ \frac{1(x^4)}{D^2} \right]$$

$$\therefore y_p = e^{-2x} \cdot \frac{x^6}{30}$$


**32. Ans: 0.275 {Range: 0.25 to 0.29}**

**Sol:**

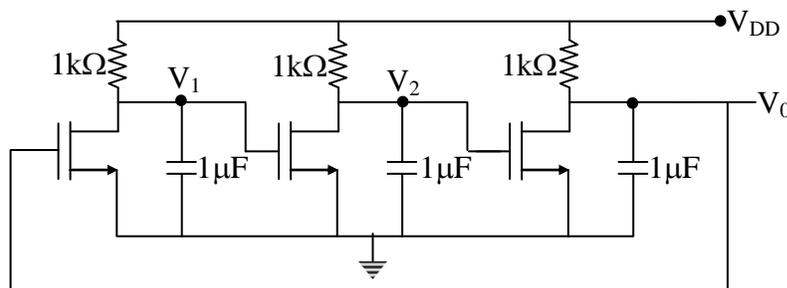




Consider a single-stage:

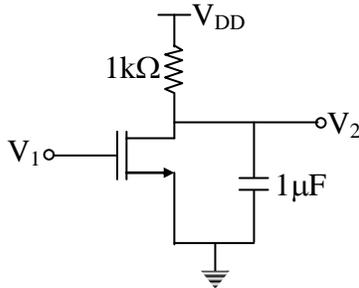

**small-signal equivalent:**

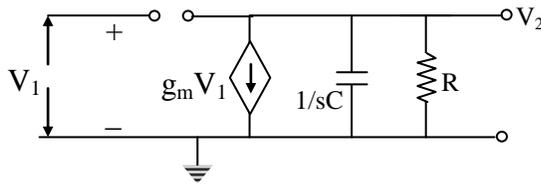

$$V_2 = -g_m V_1 (R // (1/sC))$$

$$\frac{V_2}{V_1} = -g_m [R // (1/sC)]$$

$$\text{So, similarly } \frac{V_1}{V_0} = \frac{V_0}{V_2} = \frac{V_2}{V_1} = -g_m \{R // (1/sC)\}$$

For oscillators, loop gain = 1

$$\frac{V_1}{V_0} \times \frac{V_2}{V_1} \times \frac{V_0}{V_2} = 1$$

$$\text{i.e., } \{-g_m [R // (1/sC)]\}^3 = 1$$

$$\Rightarrow -\left[ \frac{g_m R}{1 + R s C} \right]^3 = 1$$

Put  $s = j\omega$

$$\Rightarrow -\left[ \frac{g_m R}{1 + j\omega RC} \right]^3 = 1$$

$$\Rightarrow -\left[ \frac{(g_m R)^3}{(1 + j\omega RC)^3} \right] = 1$$

Equating angle condition i.e., angle =  $360^\circ$  for sustained oscillations

$$\text{i.e., } 180^\circ - 3 \tan^{-1}(\omega RC) = 0^\circ$$

$$\tan^{-1}(\omega RC) = 60^\circ$$



$$\omega = \frac{\sqrt{3}}{RC}$$

$$f = \frac{\sqrt{3}}{2\pi RC} = 0.2756 \text{ kHz}$$

**33. Ans: (b)**

**Sol:**  $\int_{-\infty}^{\infty} x e^{-x^2} dx$

Let  $f(x) = x e^{-x^2}$

$$f(-x) = -x e^{-x^2} = -f(x)$$

∴  $f(x)$  is odd function

∴ The value of given integral is zero.

**34. Ans: (c)**

**Sol:** From parseval's theorem

$$2\pi \int_{-\infty}^{\infty} |x(t)|^2 dt = \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$$

$$x(t) = \begin{cases} t+1 & ; -1 < t < 0 \\ -t+1 & ; 0 < t < 2 \\ t-3 & ; 2 < t < 3 \end{cases}$$

$$\begin{aligned} \int_{-\infty}^{+\infty} |X(\omega)|^2 d\omega &= 2\pi \left[ \int_{-1}^0 (t^2 + 2t + 1) dt + \int_0^2 (t^2 - 2t + 1) dt + \int_2^3 (t^2 - 6t + 9) dt \right] \\ &= 2\pi \left[ \left( \frac{t^3}{3} + t^2 + t \right)_{-1}^0 + \left( \frac{t^3}{3} - t^2 + t \right)_0^2 + \left( \frac{t^3}{3} - 3t^2 + 9t \right)_2^3 \right] \\ &= 2\pi \left[ \frac{1}{3} - 1 + 1 + \frac{8}{3} - 4 + 2 + 9 - 27 + 27 - \frac{8}{3} + 12 - 18 \right] = 8\pi/3 \end{aligned}$$

**35. Ans: 25 (No range)**

**Sol:** Method: I

$$\text{Closed loop gain } A_f(s) = \frac{A_0(s)}{1 + \beta A_0(s)}$$

$$\begin{aligned} & \frac{250}{1 + \frac{s}{(2\pi \times 100)}} \\ &= \frac{250}{1 + \frac{(0.8)(250)}{1 + \frac{s}{(2\pi \times 100)}}} \end{aligned}$$

Low frequency gain/DC gain

$$= \frac{250}{1 + (0.8)(250)}$$



Band width =  $100(1+(0.8)(250))$   
Gain  $\times$  Bandwidth =  $250 \times 100 = 25 \times 10^3$  Hz

**Method: 2**

$$\text{If } A(s) = \frac{A_0}{1 + j \left( \frac{f}{f_H} \right)}$$

Then Gain (DC gain) =  $A_0$

BW =  $f_H$

Gain  $\times$  BW =  $A_0 f_H$

Gain BW is constant {i.e., same for open loop as well as feedback closed loop amplifier}

$$A_0(s) = \frac{250}{1 + \frac{j\omega}{2\pi \times 100}} = \frac{250}{1 + j \left( \frac{f}{100} \right)}$$

Gain = 250

BW = 100

So, Gain  $\times$  BW =  $250 \times 100 = 25 \times 10^3$  Hz

**36. Ans: 40.32 (range 40 to 41)**

**Sol:** Efficiency,  $\eta = \frac{I_p / q}{P_{opt} / hf} = \frac{I_p}{P_{opt}} \left( \frac{hf}{q} \right)$

$$\eta = R \left( \frac{h \times c}{q} \right) \frac{1}{\lambda}$$

$$R = \eta \cdot \frac{\lambda(\mu\text{m})}{1.24}$$


$$R = 1 \cdot \left( \frac{50}{1.24} \right)$$

( $\because \eta = 100\%$ )

$$R = \frac{50}{1.24} = 40.32$$

**37. Ans: (d)**

**Sol:**

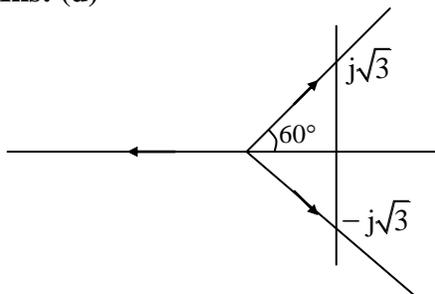

$$\tan 60^\circ = \frac{\sqrt{3}}{x} \Rightarrow x = 1$$

Pole is at  $s = -1$

$$\text{Open loop TF } G(s) = \frac{K}{(s+1)^3}$$

$$\text{Closed loop TF} = \frac{G(s)}{1 + G(s)H(s)}$$

$H(s) = 1, K = 2$

$$\text{CLTF} = \frac{\frac{2}{(s+1)^3}}{1 + \frac{2}{(s+1)^3}} = \frac{2}{s^3 + 3s^2 + 3s + 3}$$

**38. Ans: (b)**

**Sol:**  $P(T_1 / R_1) = \frac{P(R_1 / T_1) \times P(T_1)}{P(R_1)}$

$$P(R_1) = P(T_1) P(R_1 / T_1) + P(T_0) P(R_1 / T_0)$$

$$= 0.4(0.92) + 0.6(0.1) = 0.428$$

$$\therefore P(T_1 / R_1) = \frac{0.92 \times 0.4}{0.428} = 0.8598 \approx 0.86$$

**39. Ans: (d)**

**Sol:**  $\rightarrow$ (HL) = 4000H

$\rightarrow$ (SP) = 2500H

$\rightarrow$ (A) = AAH

$\rightarrow$ (A) = AAH  $\oplus$  AAH = 00H

$\Rightarrow$ (A) = 00H

$\rightarrow$  PSW contents pushed on to top of stack

$\rightarrow$  HL pair contents i.e., 4000H is

exchanged with contents of top of stack

Top of stack contains 4000H.

$\rightarrow$  Contents of top of stack i.e., 4000H


popped back into PSW

$\Rightarrow$ (PSW) = 4000H

Then flag register contents are 00H.

**40. Ans: (b)**

**Sol:**

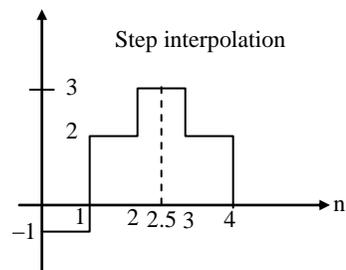



$$x(2.5) = 3$$

41. Ans: (d)

$$\text{Sol: Range ability } R = \frac{Q_{\max}}{Q_{\min}} = \frac{50(\text{cm}^3/\text{sec})}{2(\text{cm}^3/\text{sec})}$$

$$R = 25$$

The flow at 1cm opening is

$$Q = Q_{\min} R^{(s/s_{\max})}$$

$$Q = 2 \left( \frac{\text{cm}^3}{\text{sec}} \right) \times (25)^{(1\text{cm}/3\text{cm})}$$

$$Q = 5.85 \text{ (cm}^3/\text{sec)}$$

42. Ans: (b)

Sol:

Current (I)	4mA	20mA
Motor speed rpm (R)	140 rpm	600 rpm

Now by using this table we make equation of straight line.

$$\frac{I - 4\text{mA}}{20\text{mA} - 4\text{mA}} = \frac{R - 140}{600 - 140}$$

$$I = \left( \frac{R - 140}{460} \right) \times 16\text{mA} + 4\text{mA}$$

$$I = 9.913 \text{ (mA)}$$

The current 9.913mA expressed as percentage of controller output is

$$= \frac{I - I_{\min}}{I_{\max} - I_{\min}} \times 100 = \frac{I - 4\text{mA}}{20\text{mA} - 4\text{mA}} \times 100$$

$$= \frac{9.913\text{mA} - 4\text{mA}}{20\text{mA} - 4\text{mA}} \times 100 = 36.9\%$$

43. Ans: 0.25 (No range)

$$\text{Sol: } BW = \frac{R_b}{2} [1 + \alpha]$$

$$4.5 \times 10^3 = \frac{7200}{2} [1 + \alpha]$$


$$\alpha = 0.25$$

44. Ans: 1 (No range)

Sol: Given

$V_i$  = Halfwave rectified output of  $5\sin\omega t$ .

Representing  $V_i$  in graph

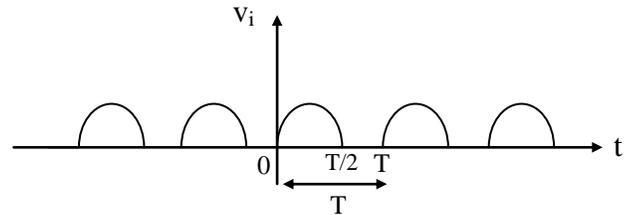

From the given transfer characteristics, we can conclude that

If  $V_i > +3 \Rightarrow V_0$  changes from  $-10$  to  $+10$


$V_i < -3 \Rightarrow V_0$  changes from  $+10$  to  $-10$

Given at  $t = 0^- \Rightarrow V_0 = -10\text{V}$

Now starting from  $t = 0^-$   
 $\Rightarrow V_0 = -10\text{V}, V_i = 0\text{V}$

Now as  $V_i > +3$

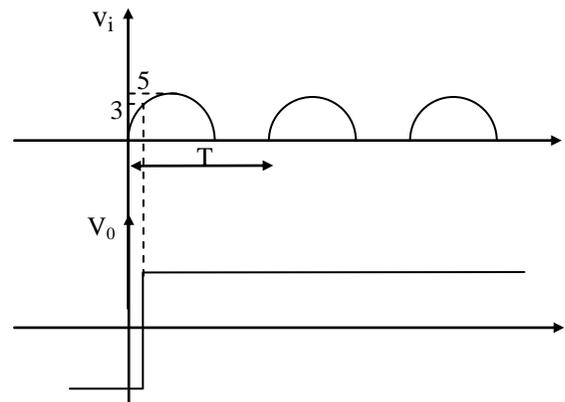$\Rightarrow V_0$  changes from  $-10$  to  $+10$



and Now if  $V_0$  becomes  $+10\text{V}$ , it will never come back to  $-10\text{V}$  since for that to happen  $V_i$  should be less than  $-3$  but given  $V_i$  is always positive, so number of transitions is 1.

45. Ans: (b)

Sol: Given  $y''(t) - y'(t) - 6y(t) = e^t u(t)$

Apply L.T

$$s^2 \cdot Y(s) - sy(0) - y'(0) - sY(s) + y(0) - 6Y(s) = \frac{1}{s-1}$$



Given  $y(0) = 1, y'(0) = 0$

$$s^2 Y(s) - s - s Y(s) + 1 - 6 Y(s) = \frac{1}{s-1}$$

$$Y(s)[s^2 - s - 6] = s - 1 + \frac{1}{s-1}$$

$$Y(s)[s^2 - s - 6] = \frac{s^2 - 2s + 2}{s-1}$$

$$Y(s) = \frac{s^2 - 2s + 2}{(s-1)(s-3)(s+2)}$$

$$Y(s) = \frac{A}{s-1} + \frac{B}{s-3} + \frac{C}{s+2}$$

$$Y(s) = -\frac{1}{6} \frac{1}{s-1} + \frac{1}{2} \frac{1}{s-3} + \frac{2}{3} \frac{1}{s+2}$$

Apply ILT

$$y(t) = -\frac{1}{6} e^t + \frac{1}{2} e^{3t} + \frac{2}{3} e^{-2t} \quad t > 0$$

**46. Ans: 200**

**Sol:** Given data:

$\Delta x$  = movement of movable mirror =  $50 \mu\text{m}$

$\lambda$  = wavelength of light used =  $500 \text{nm}$

We know the relation in Michelson interferometer

$$n\lambda = 2\Delta x$$


$n$  = number of fringes

$$n = \frac{2\Delta x}{\lambda} = \frac{2 \times 50 \times 10^{-6}}{500 \times 10^{-9}}$$

$$n = 200$$

**47. Ans: 10(No range)**

**Sol:**  $c(t) = 12.5e^{-6t} \sin 8t$

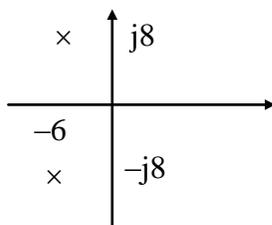

$\omega_n$  is radial distance from origin

$$\omega_n = \sqrt{6^2 + 8^2}$$

$$\omega_n = 10 \text{ rad/sec}$$

**48. Ans: (a)**

**Sol:** from given data we can write

High flow rate  $Q_A, Q_B, Q_C$

Low flow rate  $\bar{Q}_A, \bar{Q}_B, \bar{Q}_C$

High pressure  $P$

Low pressure  $\bar{P}$

High level  $L$

Low level  $\bar{L}$

Condition-Either input flow rate is high

$$Q_A \bar{Q}_B + \bar{Q}_A Q_B$$

Low output flow  $\bar{Q}_C$

Low pressure  $\bar{P}$

High level  $L$

$$\text{Overfill alarm condition} = (Q_A \bar{Q}_B + \bar{Q}_A Q_B) \bar{Q}_C \bar{P} L$$

**49. Ans: 9 (No range)**

**Sol:** Forward paths:  $M_1 = G_1 G_2 G_3 G_4 G_5 G_6$

$$M_2 = G_1 G_2 G_7 G_6$$

$$M_3 = G_1 G_2 G_3 G_4 G_8$$

Loops:  $L_1 = G_4 H_2$

$$L_2 = G_5 G_6 H_3$$

$$L_3 = G_1 G_2 G_3 G_4 G_5 G_6 H_1$$

$$L_4 = G_1 G_2 G_7 G_6 H_1$$

$$L_5 = G_1 G_2 G_3 G_4 G_8 H_1$$

$$L_6 = G_8 H_3$$

**50. Ans: (d)**

**Sol:** Given that 8 KB ROM & 8 KB RAM interfaced to 8085.

ROM is selected when  $A_{15}$  is 0

RAM is selected when  $A_{15}$  is 1

$A_{13}$  &  $A_{14}$  are unused.

MVI A, 00H ; (A) = 00H

STA 8080H ; (8080H) ← (A) = 00H

DCR A ; (A) = FFH

STA C080H ; (C080H) ← (A) = FFH

; (8080H) ← (A) = 00H

RET ; (PC) ← (TOS)

Contents of memory location 8080H is 00H.



**ACE**<sup>®</sup>  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs



**48**  
ALL INDIA  
1<sup>st</sup> RANKS IN GATE



**15**  
ALL INDIA  
1<sup>st</sup> RANKS IN ESE

HYDERABAD | TIRUPATI | DELHI | PUNE | BHUBANESWAR | BENGALURU | LUCKNOW | CHENNAI | VIJAYAWADA | VIZAG | KOLKATA | AHMEDABAD

# DIGITAL CLASSES

for

## ESE

GS & Engg. Aptitude

### 250+

Hours of Classes  
with Quizzes

## GATE

CS & IT

### 450+

Hours of Classes  
with Quizzes

**Launching Soon!** for ECE | EEE | MECH | CE | IN



Erudite &  
Experienced  
Faculty



Free Online  
Test Series



Relevant Study Material  
by Post



Doubt Clearing  
Available



Access the Lectures  
from anywhere  
and Unlimited Times



Write & Store  
Your Notes Online



EMI Option  
Available


# DEEP LEARN

Access The Course at  
[www.deep-learn.in](http://www.deep-learn.in)



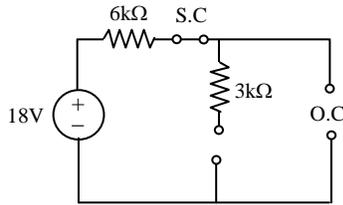**51. Ans: - 60 (No Range)**

**Sol:** At time  $t = 0^-$  switch is in open condition




So, L is short circuit, C is open circuit

$$i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 18V$$

At  $t = 0^+$  switch is closed

$$I_C(0^+) = C \frac{dv(0^+)}{dt}$$

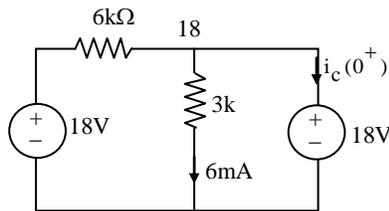

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C}$$

$$i_C(0^+) = -6 \times 10^{-3} \text{ A}$$

$$\frac{dv(0^+)}{dt} = \frac{-6 \times 10^{-3}}{100 \times 10^{-6}}$$

$$\frac{dv(0^+)}{dt} = -60 \text{ V/sec}$$

**52. Ans: (c)**

**Sol:** Given

$$f(x) = \frac{\pi^2}{3} - 4 \left( \frac{\cos x}{1^2} - \frac{\cos 2x}{2^2} + \dots \right)$$

clearly  $f(x)$  is continuous at  $x = 0$

( $\because \lim_{x \rightarrow 0} f(x) = 0$ ) the four series converges

to  $f(0)$


$$\frac{\pi^2}{3} - 4 \left( \frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots \right) = 0$$

$$\frac{\pi^2}{3} - 4 \left( \frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots \right) = 0$$

$$\frac{1}{1^2} + \frac{1}{2^2} - \frac{1}{3^2} + \dots = \frac{\pi^2}{12}$$

**53. Ans: 68.57 (Range: (67.5 to 69.5V))**

**Sol:**

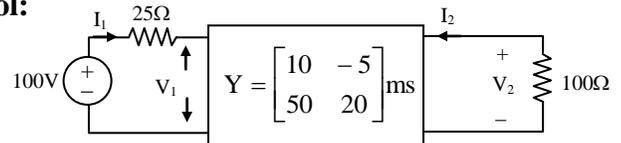

By applying at KVL input side

$$V_1 = 100 - 25I_1 \dots \dots (1)$$

$$V_2 = -100 I_2 \dots \dots (2)$$

From Y-parameters

$$I_1 = (10 \times 10^{-3}) V_1 - (5 \times 10^{-3}) V_2 \dots \dots (3)$$

$$I_2 = (50 \times 10^{-3}) V_1 + (20 \times 10^{-3}) V_2 \dots \dots (4)$$

By putting value of  $V_2$  in equation (4)

$$I_2 = (50 \times 10^{-3}) V_1 + (20 \times 10^{-3}) (-100 I_2)$$

$$= (50 \times 10^{-3}) V_1 - 2I_2$$

$$3I_2 = (50 \times 10^{-3}) V_1$$

And from equation (3)

$$I_1 = (10 \times 10^{-3}) V_1 - (5 \times 10^{-3}) (-100 I_2)$$

$$= (10 \times 10^{-3}) V_1 + (5 \times 10^{-3} \times 100) \left( \frac{50 \times 10^{-3}}{3} \right) V_1$$

$$= (10 \times 10^{-3}) V_1 + \frac{25}{3} \times 10^{-3} V_1$$

$$= \frac{55}{3} \times 10^{-3} V_1$$

$$\therefore V_1 = 100 - [25 \times I_1]$$

$$V_1 = 100 - \left[ 25 \times \frac{55}{3} \times 10^{-3} V_1 \right]$$

$$V_1 \left[ 1 + 25 \times \frac{55}{3} \times 10^{-3} \right] = 100$$

$$V_1 = \frac{100}{1.458} = 68.57 \text{ V}$$



54. Ans: (d)

Sol:  $t_{\text{measured}} = 1650^\circ\text{C} = 1923 \text{ k}$

$$\varepsilon_1 = 0.85, \varepsilon_2 = 0.75$$


$$T_{\text{actual}} = T_{\text{measured}} \times \left( \frac{\varepsilon_1}{\varepsilon_2} \right)^{0.25}$$

$$= 1923 \times \left( \frac{0.85}{0.75} \right)^{0.25} = 1984.12 \text{ k}$$

$$T_{\text{actual}} = 1984.12 - 273 = 1711.12^\circ\text{C}$$

55. Ans: 33.33 (33.0 to 33.8)

Sol:

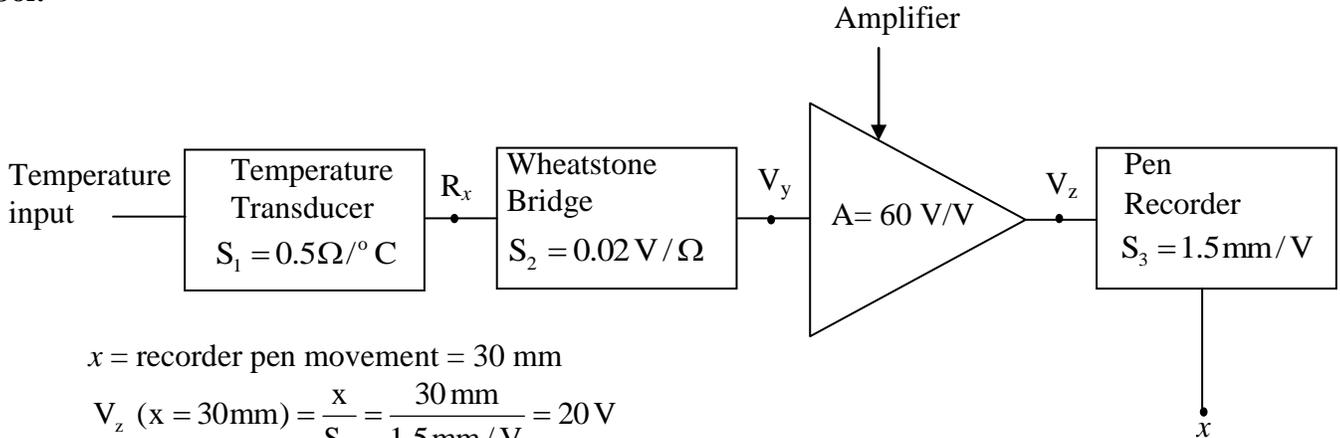

$x = \text{recorder pen movement} = 30 \text{ mm}$

$$V_z (x = 30\text{mm}) = \frac{x}{S_3} = \frac{30 \text{ mm}}{1.5 \text{ mm/V}} = 20 \text{ V}$$

$$V_y = \frac{V_z}{60} = \frac{20}{60} = \frac{1}{3} \text{ V}$$

$$R_x = \frac{V_y}{S_2} = \frac{V_3 \text{ V}}{0.02 \text{ V}/\Omega} = \frac{50}{3} \Omega$$

Temperature input for  $n = 30 \text{ mm}$  displacement

$$= \frac{R_x}{S_1} = \frac{50/3 \Omega}{0.5 \Omega/^\circ\text{C}} = \frac{50/3 \Omega}{0.5 \Omega/^\circ\text{C}} = \frac{100}{3}^\circ\text{C} = 33.33^\circ\text{C}$$

56. Ans: (d)

Sol: 'Cut out for' means designed to be so. 'Cut up' means 'to be emotionally upset'. 'Cut down' means 'to kill somebody' or 'to make something fall down by cutting it at the base'. 'Cut off' means 'separated from the rest of the world'.

57. Ans: (c)

58. Ans: (a)

59. Ans: (d)

Sol: Let principle be 1.

then amount after 10 years  $= 3 \times 1 = 3$

$\therefore$  Simple interest  $= 3 - 1 = 2$

$\therefore$  Rate of interest  $= \frac{2 \times 100}{1 \times 10} = 20\%$

60. Ans: (c)

Sol: Note that  $20 - 14 = 6$ ;  $25 - 19 = 6$ ;  
 $35 - 29 = 6$ ;  $40 - 34 = 6$ .

$$\begin{aligned} 20 &= 2 * 2 * 5 \\ 25 &= 5 * 5 \\ 35 &= 1 * 5 * 7 \\ 40 &= 2 * 2 * 2 * 5 \end{aligned}$$



Required number


$$\begin{aligned}
 &= \text{L.C.M. of } (20, 25, 35 \text{ and } 40) - 6. \\
 &= (2 \times 2 \times 2 \times 5 \times 5 \times 7) - 6 \\
 &= 1400 - 6 = 1394
 \end{aligned}$$

**61. Ans: (c)**

**Sol:** The angle subtended by an arc at the centre of the circle is twice the angle subtended by the arc at any point on the remaining part of the circle.

$$\therefore \angle BOC = 2\angle BAC = 2 \times 50^\circ = 100^\circ$$

Now in  $\triangle BOC$

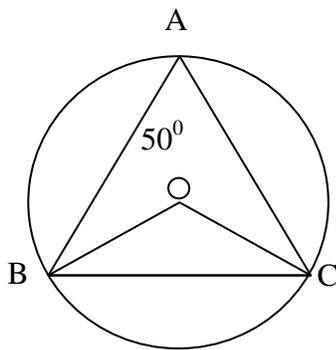

$OB = OC$  [radii of circumcentre]

$$\therefore \angle OBC = \angle OCB = x \text{ (let)}$$

$$\therefore x + x + 100^\circ = 180^\circ$$

$$\Rightarrow 2x = 80^\circ$$

$$\Rightarrow x = 40^\circ$$

**62. Ans: (a)**

**Sol:** At 4:10 the hour hand is a head of minute hand

Given that  $n = 4$  and  $x = 10$

Then according to the formula required angle

$$\begin{aligned}
 &= \left\{ 30 \left( n - \frac{x}{5} \right) + \frac{x}{2} \right\}^\circ \\
 &= \left\{ 30 \left( 4 - \frac{10}{5} \right) + \frac{10}{2} \right\}^\circ \\
 &= \{ (30 \times 2) + 5 \}^\circ = (60 + 5)^\circ \\
 &= 65^\circ
 \end{aligned}$$

**63. Ans: (b)**

**Sol:** Total cost (in Rs) of journey to Town A  
 $= 4300 + 3100 + 4000 + 6000 = 17400$

$$\text{Average cost} = \frac{17400}{4} = \text{Rs. } 4350$$

**64. Ans: (a)**

**Sol:** Maximum cost (in Rs) of journey from Delhi to town A = By Train 4 = Rs. 6000

Similarly, for town B = Rs. 6300

Town C = Rs. 5600 and

Town D = Rs. 5700

$$\Rightarrow \text{Maximum cost} = 6000 + 6300 + 5600 = \text{Rs. } 23600$$

**65. Ans: (d)**