



PRE-GATE-2020

Instrumentation Engineering

(Questions with Detailed Solutions)

GENERAL APTITUDE

Q. 1 – Q. 5 carry one mark each.

01. Fill in the blank with an appropriate phrase

Jobs are hard to _____ these days

- (A) Come by (B) Come down
(C) Come of (D) Come from

01. Ans: (A)

Sol: 'Come by' means to manage to get something.

02. The question below consists of a pair of related words followed by four pairs of words. Select the pair that best expresses the relation in the original pair.

MONKEY : TROOP :

- (A) sheep : hard
(B) elephant : Parliament
(C) bacteria : Colony
(D) wolves : School

02. Ans: (C)

Sol: Troop consists of monkeys just as a colony consists of bacteria.

03. Choose the most appropriate word from the options given below to complete the following sentence:

If you had gone to see him, he _____ delighted.

- (A) Would have been
(B) Will have been
(C) Had been
(D) Would be

03. Ans: (A)

Ans: 'A' conditional tense type 3 grammatical code is

If +had+V3, would +have+V3

04. Which of the following options is closest in meaning to the underlined word?

European intellectuals have long debated the consequences of the hegemony of American popular culture around the world.

- (A) regimen (B) vastness
(C) dominance (D) popularity

04. Ans: (C)

Sol: Dominance means influence or control over another country, a group of people etc.



05. How many one-rupee coins, 50 paise coins, 25 paise coins in total of which the numbers are proportional to 5, 7 and 12 are together work ₹115?

- (A) 50, 70, 120 (B) 60, 70, 11
(C) 70, 80, 90 (D) None of these

05. Ans: (A)

Sol: $(5 \times 1 + 7 \times 0.5 + 12 \times 0.25)x = 115$

$$(5 + 3.5 + 3)x = 115$$

$$11.5x = 115$$

$$x = 10$$

$$\therefore \text{Number of one rupee coin} = 5x$$

$$= 5 \times 10 = 50$$

$$\text{Number of 5-paise coin} = 7x = 7 \times 10 = 70$$

$$\begin{aligned} \text{Number of 25-paise coin} &= 12x \\ &= 12 \times 10 = 120 \end{aligned}$$

Q. 6 – Q. 10 carry Two marks each.

06. Critical reading is a demanding process. To read critically, you must slow down your reading and, with pencil in hand, perform specific operations on the text mark up the text with your reactions, conclusions, and questions, then you read, become an active participant. This passage best supports the statement that

- (A) Critical reading is a slow, dull but essential process.
(B) The best critical reading happens at critical times in a person's life.
(C) Readers should get in the habit of questioning the truth of what they read.
(D) Critical reading requires thoughtful and careful attention.

06. Ans: (D)

Sol: Choice (A) is incorrect because the author never says that reading is dull.

Choice (B) and (C) are not support by the paragraph.

Choice (D) is correct as it is implied in the entire passage.


07. Anil's house faces east from the back-side of the house, he walks straight 50 metres, then turns to the right and walks 50m again finally, he turns towards left and stops after walking 25 m. Now Anil is in which direction from the starting point?

- (A) South-east
(B) South-west
(C) North-east
(D) North- west



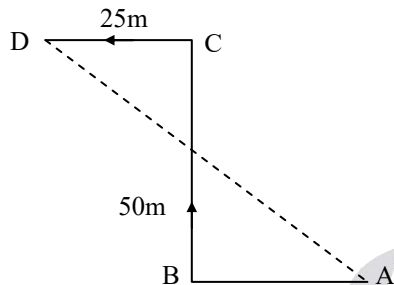07. Ans: (D)

Sol: The movement of Anil are shown in the adjoining figure



He starts walking from back of his house (i.e) towards west now, the final position is D, which is to the north west of his starting point A.

- 08.** A and B enter into a partnership, A puts in ₹50 and B puts in ₹45. At the end of 4 months, A withdraws half his capital and at the end of 5 months B withdraws $\frac{1}{2}$ of his, C then enters with a capital of ₹70 at the end of 12 months, the profit of concern is ₹254, how can the profit be divided among A, B and C ?
- (A) ₹76, ₹80 and ₹98
- (B) ₹80, ₹76 and ₹98
- (C) ₹76, ₹98 and ₹80
- (D) ₹80, ₹98 and ₹76

08. Ans: (B)

Sol:

A's share : B's share : C's share

$$(50 \times 4 + 25 \times 8) : (45 \times 5 + 22.5 \times 7) : (70 \times 7)$$

$$400 : 382.5 : 490$$

$$800 : 765 : 980$$

$$160 : 153 : 196$$

$$\text{Total profit} = ₹254$$

$$\text{Profit of A} = \frac{160}{160 + 153 + 196} \times 254$$

$$= \frac{160}{509} \times 254$$

$$= ₹79.8 \approx ₹80$$

$$\text{Profit of B} = \frac{153}{509} \times 254$$

$$= ₹76.34$$

$$\approx ₹76$$

$$\text{Profit of C} = \frac{196}{509} \times 254$$

$$= ₹97.8$$

$$\approx ₹98$$

∴ Hence option 'B' is correct.



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

ESE - MAINS

Classes Start from: **13th FEB 2020**



@ DELHI



Students who Qualify in Prelims
can avail **100 % Fee Waiver**



@ HYDERABAD

ESE-2018, 2019 Prelims Qualified Students are also eligible for Fee Discounts



/aceacademy



/ACE_Enggacademy



/aceenggacademy

- H.O. # 4-1-1236/1/A, Sindhu Sadan, King Koti Road, Abids, Hyderabad - 500001, Telangana, India.
- Ph: 040-23234418/19/20 , 040-24750437.
- Email: hyderabad@aceenggacademy.com
- www.aceenggacademy.com




09. A sum of ₹25400 was lent out in two parts, one of 12% and the other at $12\frac{1}{2}\%$. If the total annual income is ₹3124.2, the money lent at 12% is _____.

(A) ₹15240 (B) ₹25400
(C) ₹10160 (D) ₹31242

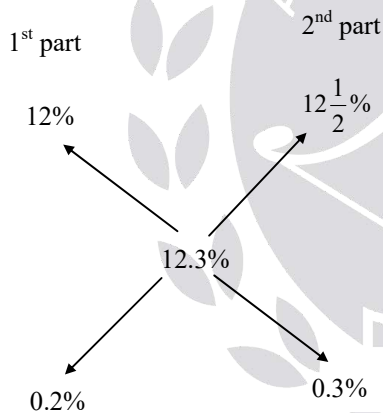09. Ans: (C)

Sol: Overall rate of interest

$$\frac{3124.2}{25400} \times 100 = 12.3\%$$



∴ The sum will be divided in the ratio 0.2:0.3 (or) 2:3

$$\begin{aligned} \therefore \text{The sum lent at } 12\% &= 25400 \times \frac{2}{5} \\ &= ₹10160. \end{aligned}$$

10. The following question is to be answered on the basis of the table given below.

Category of personnel	Number of staff in the year-1990	Number of staff in the year-1995
Data preparation	18	25
Data control	5	8
Operators	18	32
Programmers	21	26
Analysts	15	31
Managers	3	3
Total	80	135

What is the increase in the sector angle for operators in the year 1995 over the sector angle for operators in the year 1990?

(A) 4° (B) 3°
(C) 2° (D) 1°

10. Ans: (A)

Sol: Sector angle for operators in the year 1990

$$= \frac{18}{80} \times 360^\circ = 81^\circ$$

Sector angle for operators in the year 1995

$$\begin{aligned} &= \frac{32}{135} \times 360^\circ \\ &= 85.33 \\ &\approx 85\% \end{aligned}$$

$$\therefore \text{Required difference} = 85^\circ - 81^\circ = 4^\circ$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



Hyderabad | Ahmedabad | Pune | Delhi | Bhubaneswar | Bangalore | Chennai | Lucknow | Visakhapatnam | Vijayawada | Tirupati | Kolkata

Head Office Address: # 4-1-1236/1/A, Sindhu Sadan, King Koti, Abids, Hyderabad - 500001, Telangana, India.



SUMMER



SHORT TERM BATCHES GATE + PSUs - 2021

@ HYDERABAD

Streams: EC, EE, ME, CE, CSIT, IN & PI

28th April, 5th May,
10th May, 17th May, 25th May,
1st June, 8th June, 2020

Course Duration: 55 to 60 Days

☎ 040-23234418/19/20, 040-24750437

✉ hyderabad@aceenggacademy.com

@ DELHI

Streams: EC, EE, ME, CE, IN & PI

10th & 20th
May 2020

Course Duration: 60 to 70 Days

☎ 7838971777 (Call or Whatsapp)

✉ delhi@aceenggacademy.com

Early Bird Offer Rs. 3,000/- Register before 31st March 2020

Upcoming Batches @ HYDERABAD

GATE+PSUs-2021

Spark Batches : 10th May, 8th & 23rd June 2020.

Regular Batches : 26th April, 10th, 24th May, 8th, 23rd June, 7th, 22nd July,
5th & 20th August 2020.

ESE+GATE+PSUs-2021

Spark Batches : 10th May, 8th & 23rd June 2020.

Regular Batches : 29th March, 26th April, 10th, 24th May,
8th, 23rd June & 7th July 2020.

Upcoming Batches @ DELHI

GATE+PSUs-2021

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

Regular Batches : 17th Feb, 7th March, 10th & 20th May 2020.

ESE+GATE+PSUs-2021

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

Regular Batches : 17th Feb, 7th March, 10th & 20th May 2020.

GATE+PSUs-2022

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

ESE+GATE+PSUs-2022

Weekend Batches : 28th Dec, 11th Jan & 8th Feb 2020.

SSC-JE Batches @ Hyderabad

New Batch Starts from: 10th May 2020

for Civil, Mechanical & Electrical



Scan QR Code for
Upcoming Batches
Details

☎ www.aceenggacademy.com

follow us on:






INSTRUMENTATION ENGINEERING

Q. 11 – Q. 35 carry one mark each.


11.

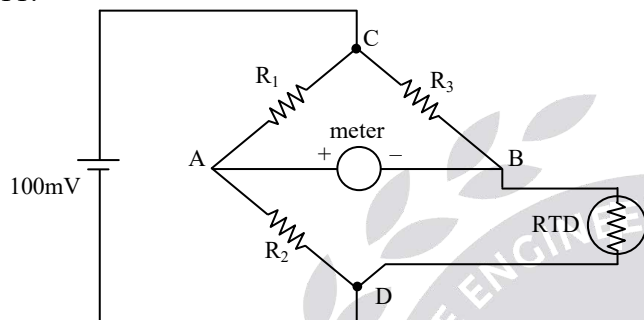

Suppose the meter in given Wheatstone bridge circuit is “pegged” even when the RTD is at 0°C (When the bridge should be balanced) with the polarity across the indicating voltmeter terminals as shown. Using digital multi meter we measured voltage between test point C and B. If RTD failed shorted then the magnitude reading of digital multi meter in mV is

11. Ans: 100 [Range: 99.9 to 100.1]

Sol:

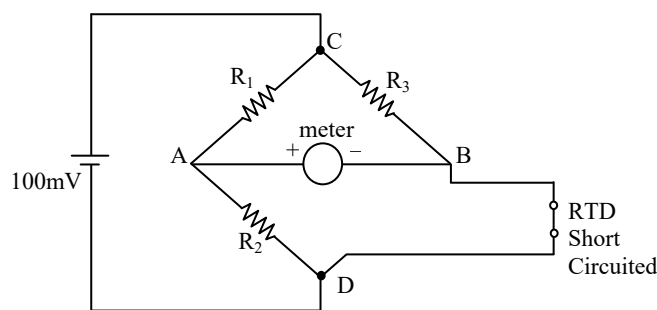

From above diagram we can say that all supply voltage will come across resistance R_3 so digital multi meter connected between test point C and B measure 100 mV.

12. A 1 k Ω strain gauge having gauge factor $G_f = 2.0$ is attached to a load cell ($E = 100 \times 10^3$ MPa). The cross sectional area of the load cell A is 200 mm². The change in resistance ΔR (in Ω), when the load cell supports a 1000 kg load (Consider $g = 10$ m/s²)

12. Ans: 1 [Range: 0.9 to 1.1]

Sol: We know

$$\Delta R = G_f \epsilon R \quad (1)$$

$$\epsilon = \frac{\text{stress}}{E} = \frac{F/A}{E} = \frac{F}{AE}$$

$$\epsilon = \frac{Mg}{AE}$$

Equation (1) becomes

$$\Delta R = G_f \times \frac{Mg}{AE} \times R$$

$$= 2 \times \frac{1000 \times 10}{200 \times 10^{-6} \times 100 \times 10^3 \times 10^6} \times 1000$$

$$\Delta R = 1 \Omega$$



13. If directional derivative of $\phi = 2xz - y^2$, at the point (1, 3, 2) becomes maximum in the direction of \vec{a} , then magnitude of \vec{a} is _____

13. Ans: 7.48 [Range: 7.4 to 7.5]

Sol: Given $\phi = 2xz - y^2$

$$\begin{aligned}\nabla\phi &= \frac{\partial\phi}{\partial x}\vec{i} + \frac{\partial\phi}{\partial y}\vec{j} + \frac{\partial\phi}{\partial z}\vec{k} \\ &= 2z\vec{i} - 2y\vec{j} + 2x\vec{k}\end{aligned}$$

\therefore Required direction vector $= \vec{a} = (\nabla\phi)$ at (1, 3, 2) $= (4\vec{i} - 6\vec{j} + 2\vec{k})$

$$\begin{aligned}\text{Magnitude of } \vec{a} &= \sqrt{16 + 36 + 4} \\ &= \sqrt{56} \\ &= 7.48\end{aligned}$$

14. A sinusoidal carrier is frequency modulated by a sinusoidal signal with the frequency deviation of 10 kHz. If the message signal frequency is 5 kHz, then the fraction of carrier power P_{fc} to the total power P_t is _____
(Given that $J_0(2) = 0.224$, $J_0(5) = -0.178$ & $J_0(8) = 0.172$)

14. Ans: 0.0501 [Range: 0.0490 to 0.0510]

Sol: Given $\Delta f = 10\text{kHz}$ and $f_m = 5\text{kHz}$

$$\beta = \frac{\Delta f}{f_m} = \frac{10\text{k}}{5\text{k}} = 2$$

$$\beta = 2$$

$$P_{fc} = \frac{A_c^2}{2} J_0^2(2)$$

$$P_t = \frac{A_c^2}{2}$$

$$\frac{P_{fc}}{P_t} = J_0^2(2) = 0.0501$$

15. A photomultiplier has a current gain of 3×10^6 . A weak light beam produces 50 electrons per second at the photocathode. The anode to ground resistance (in $\text{k}\Omega$) must be used to get 12 μV voltage from this light source (The charge on an electron is $1.6 \times 10^{-19} \text{C}$).

15. Ans: 500 [Range: 495 to 505]

Sol: The current is found from the gain of the PMT and the charge of an electron as:

$$\begin{aligned}I &= 3 \times 10^6 \times 50 \left(\frac{e}{\text{sec}} \right) \times 1.6 \times 10^{-19} \left(\frac{\text{C}}{e} \right) \\ &= 3 \times 10^6 \times 50 \times 1.6 \times 10^{-19} \left(\frac{\text{C}}{\text{sec}} \right) \\ &= 24(\text{pA})\end{aligned}$$

$$\begin{aligned}\text{Anode to ground resistance} &= \frac{12 \times 10^{-6}}{24 \times 10^{-12}} \\ &= 0.5 \times 10^6 \\ &= 500 \text{ k}\Omega\end{aligned}$$



16. A numerical solution of the equation $f(x) = x + \sqrt{x} - 3 = 0$ can be obtained using Newton - Raphson method. If the starting value is $x = 2$ for the iteration then the value of x that is to be used in the next step is _____

16. Ans: 1.69 [Range: 1.4 to 1.8]

Sol: Given $f(x) = x + \sqrt{x} - 3 = 0$ and $x_0 = 2$


$$f'(x) = 1 + \frac{1}{2\sqrt{x}}$$

Newton - Raphson formula is

$$x_{n+1} = x_n - \frac{f(x_n)}{f'(x_n)}$$

$$\begin{aligned} \Rightarrow x_1 &= x_0 - \frac{f(x_0)}{f'(x_0)} \\ &= 2 - \frac{(2 + \sqrt{2} - 3)}{\left(1 + \frac{1}{2\sqrt{2}}\right)} \\ &= 1.6939 \end{aligned}$$

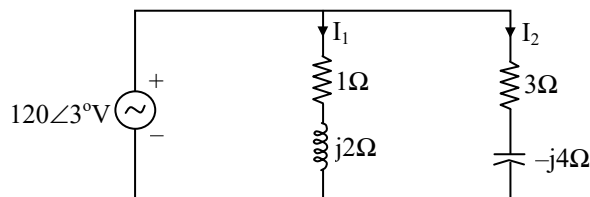17. Consider the following circuit. The behaviour of parallel circuit with the power factor of _____ lagging




17. Ans: 0.8 [Range: 0.77 to 0.83]

Sol: Total admittance

$$\begin{aligned} Y &= Y_1 + Y_2 = \frac{1}{Z_1} + \frac{1}{Z_2} \\ &= \frac{1}{1 + j2} + \frac{1}{3 - j4} = \frac{1 - j2}{5} + \frac{3 + j4}{25} \\ Y &= \frac{5 - j10 + 35 + j4}{25} = \frac{(8 - j6)}{25} \text{ U} \end{aligned}$$

$$Y = \left(\frac{8}{25}\right) - j\left(\frac{6}{25}\right)$$

$$Y = G - jB$$

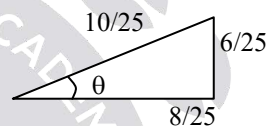

$$\cos\theta = 0.8$$

0.8 lagging power factor.

18. Given $X(z) = \frac{z^2 + z}{z^3 - 3z^2 + 3z - 1}$; $|z| > 1$, then $x(n)$ value at $n = 2$ is _____

18. Ans: 4

Sol: $X(z) = \frac{z^{-1} + z^{-2}}{1 - 3z^{-1} + 3z^{-2} - z^{-3}}$

$$\begin{aligned} &(1 - 3z^{-1} + 3z^{-2} - z^{-3})z^{-1} + z^{-2}(z^{-1} + 4z^{-2} + \dots) \\ &\frac{z^{-1} - 3z^{-2} + 3z^{-3} - z^{-4}}{4z^{-2} - 3z^{-3} + z^{-4}} \\ &\frac{4z^{-2} - 12z^{-3} + 12z^{-4} - 4z^{-5}}{\vdots} \end{aligned}$$

$$X(z) = z^{-1} + 4z^{-2} + \dots$$

Apply inverse z-transform


$$\delta(n - n_0) \leftrightarrow z^{-n_0}$$

$$x(n) = \delta(n - 1) + 4\delta(n - 2) + \dots$$

$$x(2) = 4$$



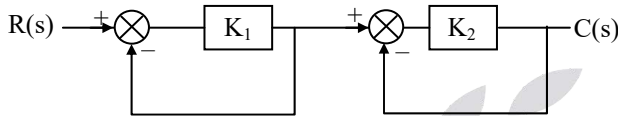19. A control system is represented by the block diagram shown in figure. The nominal values of the parameters are $K_1 = 1$ and $K_2 = 10$. Then Sensitivity of the transfer function with respect to K_1 is _____



19. **Ans: 0.5**

Sol: Transfer function,

$$\frac{C(s)}{R(s)} = \left(\frac{K_1}{1+K_1} \right) \left(\frac{K_2}{1+K_2} \right) = \left(\frac{10K_1}{11+11K_1} \right)$$

$$S_{K_1}^T = \left(\frac{\partial T / T}{\partial K_1 / K_1} \right) = \left(\frac{K_1}{T} \right) \left(\frac{\partial T}{\partial K_1} \right)$$

$$= \left(\frac{K_1}{\frac{10K_1}{11+11K_1}} \right) \times \left[\frac{10(11+11K_1) - 10K_1(11)}{(11+11K_1)^2} \right]$$

$$= \left(\frac{11}{11+11K_1} \right) \Rightarrow (S_{K_1}^T)_{K_1=1} = \frac{11}{22} = 0.5$$

20. A butter worth LPF is to meet the following specifications pass band ripple = 1dB for $\Omega \leq 4\text{rad/sec}$ and stop band attenuation $\geq 20\text{ dB}$ for $\Omega \geq 8\text{ rad/sec}$. The minimum order required for butterworth filter is _____

20. **Ans: 5**


Sol: Given $\delta_p = 1\text{dB}$, $\Omega_p = 4\text{rad/sec}$, $\delta_s = 20\text{dB}$ and $\Omega_s = 8\text{ rad/sec}$

$$n = \frac{1}{2} \frac{\log \left[\frac{10^{0.1\delta_s\text{dB}} - 1}{10^{0.1\delta_p\text{dB}} - 1} \right]}{\log \left(\frac{\Omega_s}{\Omega_p} \right)}$$

$$= \frac{1}{2} \frac{\log \left[\frac{10^{0.1(20)} - 1}{10^{0.1(1)} - 1} \right]}{\log \left(\frac{8}{4} \right)}$$


$$= 4.289 \approx 5$$

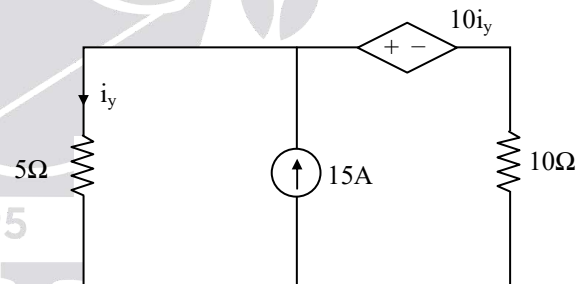21. In the given circuit, the power (in kiloWatts) delivered by the dependent source is _____



21. **Ans: 4.5**

Sol:

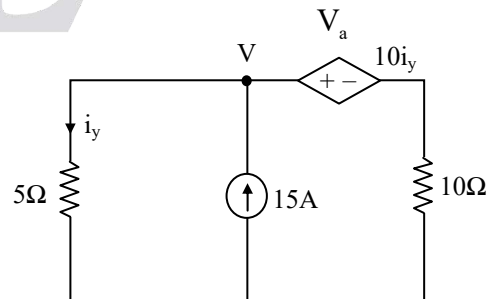

By KCL at node 'V'

$$\frac{V}{5} + \frac{V - 10i_y}{10} = 15 \Rightarrow 2V + V - 10i_y = 150$$



$$3V - 10i_y = 150$$

$$3V - 10\left(\frac{V}{5}\right) = 150 \Rightarrow V = 150 \text{ Volts}$$

$$\text{and } i_y = \frac{V}{5} = 30 \text{ A}$$

Power delivered by the dependent source

$$P_d = V_a I_d = (10i_y) \left(\frac{10i_y - V}{10} \right)$$

$$= 10 \times 30 \left(\frac{10(30) - 150}{10} \right)$$

$$= 300(15) = 4500 \text{ Watts}$$

$$= 4.5 \text{ kW}$$

22. Simplify the following Boolean expression $F = \overline{\overline{X\overline{Y}} + XYZ + X(Y + X\overline{Y})}$ and the number of literals in the simplified expression are _____

Ans: 0

Sol: $F = \overline{\overline{X\overline{Y}} + XYZ + X(Y + X\overline{Y})}$

$$= \overline{\overline{X(\overline{Y} + YZ)} + X(Y + X)(Y + \overline{Y})}$$

[\because distributive law $A + BC$

$$= (A + B)(A + C)]$$

$$= \overline{\overline{X(\overline{Y} + Z)} + X(X + Y)}$$

$$= \overline{X(\overline{Y} + Z).X(1 + Y)} \quad [\because A + \overline{A} = 1]$$

$$= \overline{X(\overline{Y} + Z).X(1 + Y)} \quad [\because \overline{\overline{A}} = A]$$

$$= \overline{X(\overline{Y} + Z).X} = 0$$

$$[\because A(1+B) = A, A.\overline{A} = 0]$$

23. A base band signal band limited to 5 MHz is to be transmitted using VSB modulation. The percentage of vestige bandwidth allowed is 20% of USB bandwidth. The bandwidth saving (in MHz) due to VSB modulation when compared to DSB-SC modulation is _____

Ans: 4

Sol: Given $W = 5 \text{ MHz}$

BW of USB is 5 MHz


BW of vestige is 20% of 5 MHz = 1 MHz

$$\begin{aligned} \text{BW of VSB signal} &= 5 \text{ MHz} + 1 \text{ MHz} \\ &= 6 \text{ MHz} \end{aligned}$$

$$\begin{aligned} \text{BW of the DSB-SC signal} &= 2W \\ &= 10 \text{ MHz} \end{aligned}$$

So, the BW saving is 4 MHz.

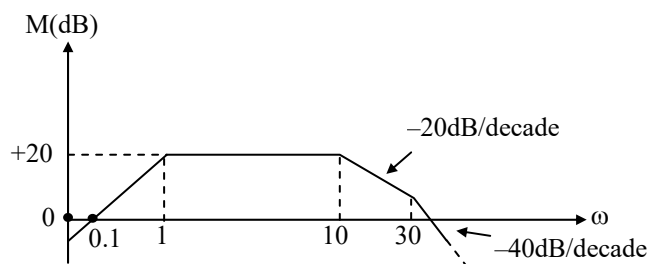24. The asymptotic magnitude plot of a minimum phase system is shown in figure. The transfer function of a given system is





- (A) $\frac{10s}{(s+1)(s+10)(s+30)}$
 (B) $\frac{3000s}{(s+1)(s+10)(s+30)}$
 (C) $\frac{3000s^2}{(s+1)^2(s+10)(s+30)}$
 (D) $\frac{300s}{(s+1)(s+10)(s+30)}$

24. Ans: (B)

Sol: Calculations for initial slope

$$\Rightarrow S = \frac{M_2 - M_1}{\log \omega_2 - \log \omega_1} \Rightarrow S = \frac{20 - 0}{\log 1 - \log 0.1}$$

$$\Rightarrow S = \frac{20}{0+1} = +20 \text{ dB/dec}$$

Transfer function,

$$G(s)H(s) = \frac{K s}{(1+s)(1+s/10)(1+s/30)}$$

Calculations for K:

$$M|_{\omega=0.1} = 20 \log K + 20 \log \omega$$

$$0 = 20 \log K - 20 \log 0.1$$





$$0 = 20 \log K - 20$$


$$20 = 20 \log K \Rightarrow K = 10$$

$$G(s)H(s) = \frac{10s}{(1+s)(1+s/10)(1+s/30)}$$

$$= \frac{3000s}{(s+1)(s+10)(s+30)}$$

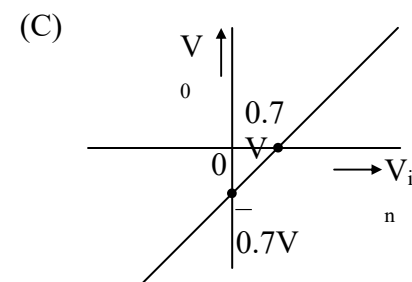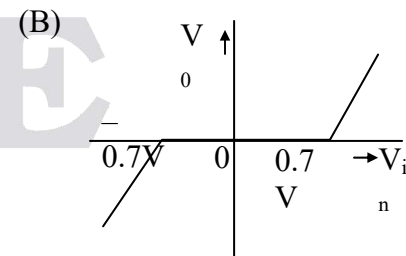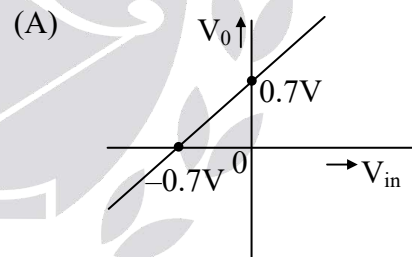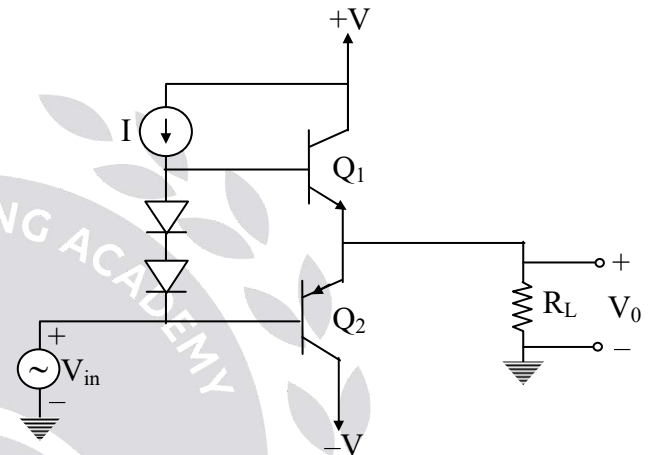25. Consider the following circuit. The diode forward drop and base-to-emitter forward drop is considered to be 0.7V. $[V_{BE(ON)} = V_{D(ON)} = 0.7V]$. Sketch the transfer characteristics?




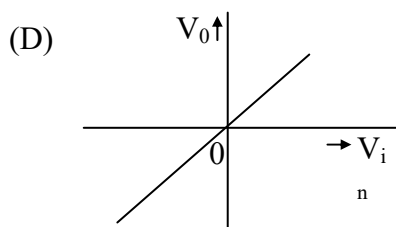

25. **Ans: (A)**

Sol:

V_{in}	V_{B1}	V_0
0V	1.4V	0.7V
-0.7V	0.7V	0V

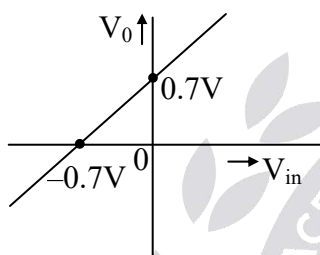

26. For the function $f(x, y) = x^2 - y^2$, the point (0, 0) is

- (A) a local minimum
- (B) a saddle point
- (C) a local maximum
- (D) not a stationary point

26. **Ans: (B)**

Sol: Given $f(x, y) = x^2 - y^2$

$$\Rightarrow f_x = 2x, f_y = -2y \text{ and}$$

$$f_{xx} = 2, f_{xy} = 0, f_{yy} = -2$$

Consider $f_x = 0$ and $f_y = 0$

$$\Rightarrow 2x = 0 \text{ and } -2y = 0$$

$\Rightarrow (0, 0)$ is a stationary point

$$\text{At } (0, 0), f_{xx} f_{yy} - (f_{xy})^2 = -4 < 0$$

$\therefore f(x, y)$ has neither a maximum nor minimum at (0, 0).

27. A synchronous counter built using T flip-flops, the flip-flop inputs are $T_2 = Q_2 \oplus Q_1$; $T_1 = Q_1 \oplus Q_0$; $T_0 = Q_2 \odot Q_0$. Determine the counter state after 2 pulses if the present state is 110.

(Assume Q_2 as MSB, Q_0 as LSB)

- (A) 000
- (B) 110
- (C) 100
- (D) None

27. **Ans: (A)**

Sol: $T_2 = Q_2 \oplus Q_1$; $T_1 = Q_1 \oplus Q_0$;

$$T_0 = Q_2 \odot Q_0$$

CLK	P.S			FF Inputs			N.S		
	Q_2	Q_1	Q_0	T_2	T_1	T_0	Q_2	Q_1	Q_0
1	1	1	0	0	1	0	1	0	0
2	1	0	0	1	0	0	0	0	0

28. A system is described by the impulse response $h(n) = (-1)^n u(n)$. The difference equation of the inverse of this system is

- (A) $y(n) + y(n-1) = x(n)$
- (B) $y(n) - y(n-1) = x(n)$
- (C) $y(n) = x(n) + x(n-1)$
- (D) $y(n) = x(n) - x(n-1)$

28. **Ans: (C)**

Sol: Given $h(n) = (-1)^n u(n)$

$$(a)^n u(n) \xrightarrow{z.T} \frac{1}{1 - az^{-1}} \quad H(z) = \frac{1}{1 + z^{-1}}$$




$$H_{\text{inv}}(z) = \frac{1}{H(z)} = 1 + z^{-1} = \frac{Y(z)}{X(z)}$$

$$Y(z) = X(z) + z^{-1}X(z)$$

Apply inverse z-transform

$$y(n) = x(n) + x(n-1]$$

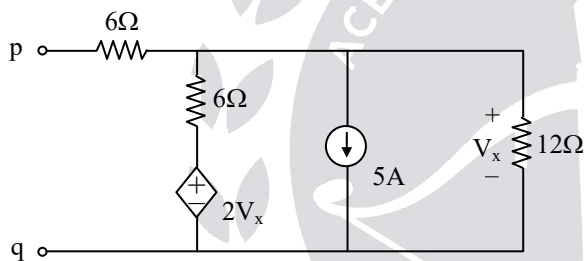
29. In the following circuit, the thevenin's voltage and resistance looking into terminals p & q respectively are.



- (A) 40V, 6Ω (B) 60V, 12Ω
(C) 40V, -12Ω (D) 60V, -6Ω

29. Ans: (D)

Sol: V-I method

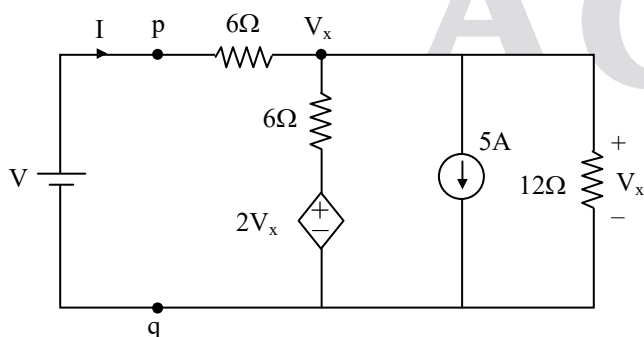

By KCL at V_x

$$I = \frac{V_x - 2V_x}{6} + 5 + \frac{V_x}{12}$$

$$I = \frac{-V_x}{6} + 5 + \frac{V_x}{12} = \frac{-2V_x + 60 + V_x}{12}$$

$$12I = 60 - V_x$$

$$12I = 60 - (V - 6I) \quad \left[\begin{array}{l} I = \frac{V - V_x}{6} \\ V_x = V - 6I \end{array} \right]$$

$$12I = 60 - V + 6I$$


$$V = -6I + 60$$

$$V = R_{\text{th}}I + V_{\text{th}}$$

$$V_{\text{th}} = 60 \text{ Volts}$$

$$R_{\text{th}} = -6\Omega$$

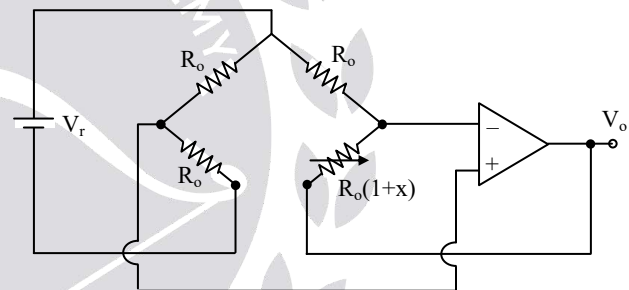30. A modified bridge circuit includes a single linear sensor $R_o(1+x)$.




The output voltage V_o is

- (A) $-\frac{V_r}{2}$ (B) $-\frac{V_r x}{2}$
(C) $\frac{V_r x}{2}$ (D) 0

30. Ans: (B)

Sol:

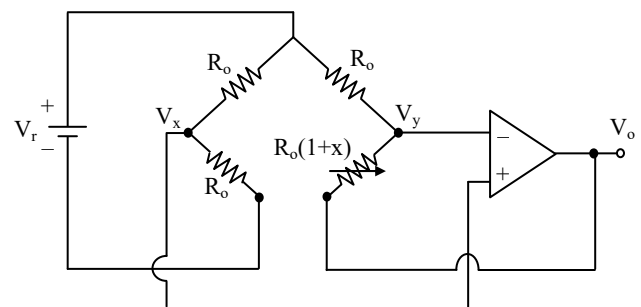



Apply voltage division rule at V_x

$$V_x = \frac{V_r}{2}$$

$$\text{By VG, } V_y = V_x = \frac{V_r}{2}$$

Apply KCL at V_y

$$\frac{V_y - V_r}{R_o} + \frac{V_y - V_o}{R_o(1+x)} = 0$$

$$V_o = -\frac{V_r}{2}x$$

31. An LED with an external quantum efficiency of 0.012 is coupled to an optical fiber of NA = 0.15 (with air between them). The overall source-fiber coupling efficiency is

- (A) 2.25×10^{-2} (B) 2.7×10^{-4}
(C) 1.2×10^{-2} (D) 1.8×10^{-3}

31. Ans: (B)

Sol: Overall source fiber coupling efficiency
= External quantum efficiency \times optical fiber efficiency
= $0.012 \times (\text{NA})^2$
= $0.012 \times (0.15)^2$
= 2.7×10^{-4}

32. A continuous random variable X has a probability density function

$f(x) = e^{-x}$, $0 < x < \infty$. Then $P(X > 2)$ is

- (A) 0.1353 (B) 0.2354
(C) 0.2343 (D) 1.1353

32. Ans: (A)

Sol: $P(X > 2) = \int_2^{\infty} f(x) \cdot dx$

$$= \int_2^{\infty} e^{-x} dx = \frac{e^{-x}}{-1} \Big|_2^{\infty}$$

$$= e^{-2} = 0.1353$$

33. A time varying voltage signal $V(t) = X + Y \sin \omega t$ is measured by a single channel Analog CRO (operated with coupling mode set to DC) and also by Dual slope integrating DMM (operated with voltage Range set to AC). After measurement, DMM and CRO will display _____ and _____ respectively.

- (A) $\sqrt{\left(\frac{X}{\sqrt{2}}\right)^2 + \left(\frac{Y}{\sqrt{2}}\right)^2}$ & $X + Y \sin \omega t$
(B) X & $X + Y \sin \omega t$
(C) $\sqrt{X^2 + \left(\frac{Y}{\sqrt{2}}\right)^2}$ & $Y \sin \omega t$
(D) X & $Y \sin \omega t$

33. Ans: (B)

Sol: * DMM measures average value.
Therefore displays X)
* In DC coupling, the sensed signal as it is reaches to Y-input of CRO and hence displayed as $X + Y \sin \omega t$.



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

48
ALL INDIA
1st RANKS IN GATE

15
ALL INDIA
1st RANKS IN ESE

Hyderabad | Ahmedabad | Kothapet | Kukatpally | Delhi | Pune | Bhubaneswar | Lucknow | Bengaluru | Chennai | Vijayawada | Vizag | Tirupathi | Kolkata

ESE / GATE / PSU_s

LONG TERM PROGRAM

@ HYDERABAD

Batches Start From



19th JAN 2020



25th FEB 2020

Streams Offered : EC | EE | ME | CE | CSIT | IN & PI

MORNING BATCHES



EVENING BATCHES



WEEKEND BATCHES



COURSES OFFERED:

- Classroom Coaching
- Postal Coaching
- Online Test Series
- Interview Guidance
- Digital Classes

New Batches for

ESE + GATE + PSU_s - 2022

GATE + PSU_s - 2022

Starts from:

19th JAN 2020

25th FEB 2020

New Batches for

ESE + GATE + PSU_s - 2021

Morning Batches @ Abids

28th DEC & 19th JAN 2020



Scan QR CODE for
New Batch Details

Hearty Congratulations to our **ESE 2019 Top Rankers**



our **GATE-2019 Rankers**



ABIDS

☎ 040-23234418,19,20, 040-24750437

KUKATPALLY

☎ 040-40199966, 93476 99966

DILSUKHNAGAR

☎ 040-40209345, 040-40044451

www.aceenggacademy.com

follow us on:





34. In a counter type ADC the clock frequency is 1 MHz and threshold voltage is 10 mV. The DAC has full scale output of 20.46V and resolution of 10 bits. Find the conversion time for analog input of 3.728V.

(A) 1023 μ s (B) 511.5 μ s
(C) 190 μ s (D) 187 μ s

34. Ans: (D)

Sol: Step size = $\frac{20.46}{2^{10}-1} = \frac{20.46}{1023} = 20\text{mV}$.

Given $V_{in} = 3.728\text{V}$, then V_d has to be =
3.728 + 10mV

$$V_d = 3.728 + 0.01 = 3.738\text{V}$$

$$= \frac{3.738}{20 \times 10^{-3}} = 186.9 = 187_{10}$$

$$= 010111011_2$$

Conversion time is $\Rightarrow 187 \times 1\mu\text{s} = 187\mu\text{s}$.

35. The solution to $x^2 y^{11} + xy^1 - y = 0$ is

(A) $y = C_1 x^2 + C_2 x^{-3}$

(B) $y = C_1 + C_2 x^{-2}$

(C) $y = C_1 x + \frac{C_2}{x}$

(D) $y = C_1 x + C_2 x^4$

35. Ans: (C)

Sol: Put $\ln x = t$ so that $x = e^t$ and

$$\text{let } x \frac{dy}{dx} = Dy, \quad x^2 \frac{d^2 y}{dx^2} = D(D-1)y$$

$$\text{where } D = \frac{d}{dt}$$

Given differential equation is

$$x^2 y^{11} + xy^1 - y = 0$$

$$\Rightarrow D(D-1)y + Dy - y = 0$$

$$\Rightarrow (D^2 - 1)y = 0$$

Consider Auxiliary equation $f(D) = 0$

$$\Rightarrow D^2 - 1 = 0$$


$$\Rightarrow D = 1, -1 \text{ are different real roots}$$

\therefore The general solution of given equation is

$$y = C_1 e^t + C_2 e^{-t} = C_1 x + \frac{C_2}{x}$$

Q. 36 – Q. 65 carry Two marks each.

36.

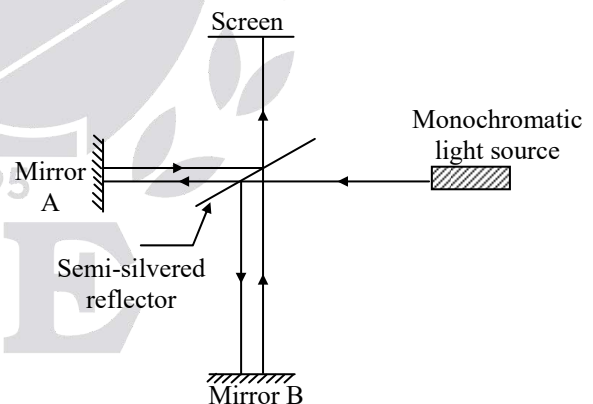

The interferometer as shown in the above figure. Two monochromatic light rays that are initially coming from same source (and hence being initially in phase) travel the two different paths and finally we look at them on the screen and find an interference pattern.



Suppose we change the position of one of the mirrors (mirror A in the figure) by 0.0125 mm & find that the bright and dark fringes change into each other 100 times during this process.

The frequency of the light ray in THz is

36. Ans: 600 [Range: 592 to 610]

Sol: Let we change position of one of the mirrors by d such that $2d = \frac{\lambda}{2}$, then a bright fringe changes into dark fringe and dark fringe change into bright fringe. The dark & bright fringes change into each other 100 times during the process, then the distance D by which mirror has been displaced must be 100 times d .


$$D = 100d = 100 \times \frac{\lambda}{4} = 25\lambda$$

$$\lambda = \frac{D}{25} = \frac{1.25 \times 10^{-5}}{25} = 500 \text{ nm}$$

$$\text{We know } f = \frac{c}{\lambda} = \frac{3 \times 10^8}{5 \times 10^{-7}} = 6 \times 10^{14} \text{ Hz}$$


$$= 600 \times 10^{12} \text{ Hz} = 600 \text{ THz}$$

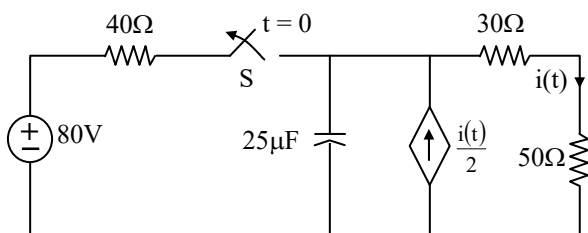37. The circuit is under steady state for $t < 0$, the switch is opened at $t = 0$. The value of $i(t)$ (in milliamperes) at $t = 4 \text{ msec}$ is _____.




37. Ans: 294.303 [Range: 292 to 296]

Sol:

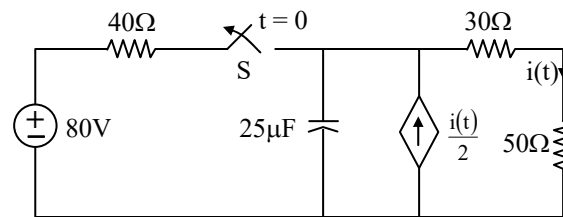

For $t < 0$, S is closed at $t = 0^-$

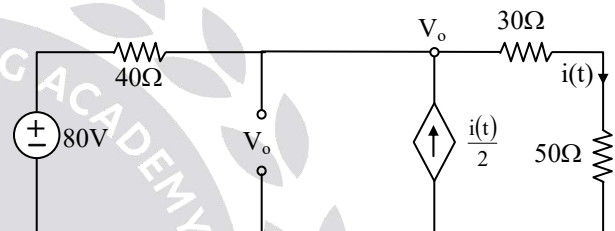Circuit is in steady state condition and capacitor acts as open circuit



By KCL at V_0 ,


$$\frac{V_0 - 80}{40} + i(t) = \frac{i(t)}{2} \Rightarrow \frac{V_0 - 80}{40} + \frac{i(t)}{2} = 0$$

$$\Rightarrow \frac{V_0 - 80}{40} + \frac{1}{2} \left(\frac{V_0}{80} \right) = 0$$


$$4V_0 - 320 + V_0 = 0 \Rightarrow 5V_0 = 320 \text{ V}$$

$$V_0 = 64 \text{ Volts}$$

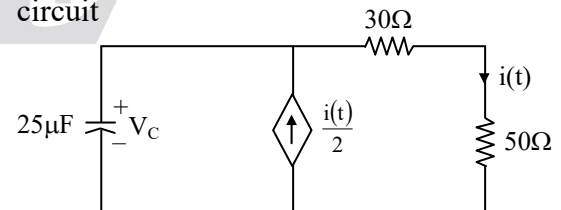For $t > 0$, S is opened, R-C source free circuit



For Req

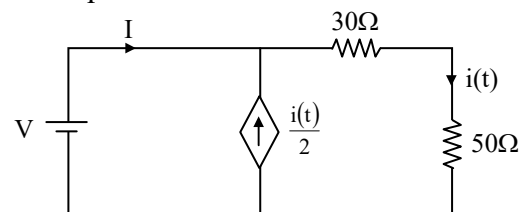



$$\tau = R_{eq}C$$

$$I + \frac{i(t)}{2} = i(t)$$

$$\Rightarrow \frac{i(t)}{2} = I$$

$$\Rightarrow \frac{V}{80 \times 2} = I$$

$$\Rightarrow R_{eq} = \frac{V}{I} = 160\Omega$$

Voltage across capacitor is given by,


$$V_C(t) = V_0 e^{\frac{-t}{\tau}} = 64e^{-250t}$$

$$i(t) = \frac{V_C(t)}{80} = \frac{64e^{-250t}}{80}$$

$$\Rightarrow i(t)|_{t=4\text{msec}} = 0.8e^{-1} = 294.303\text{mA}$$

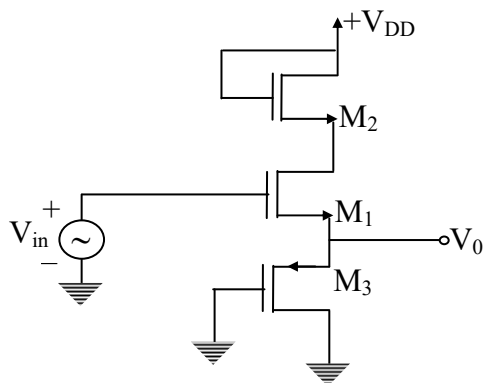
38. In the following circuit, the MOSFETs used are of enhancement mode and operating in saturation region. If all the MOSFETs are identical and by neglecting the channel length modulation, the low

frequency small signal gain $\left(\frac{V_0}{V_{in}}\right)$ is




38. Ans: 0.5 [Range: 0.49 to 0.51]

Sol:

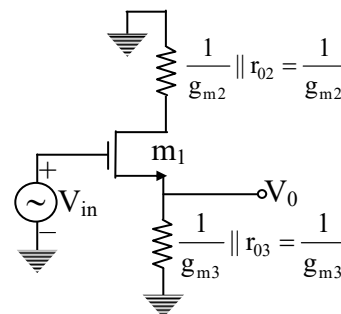

$$\begin{aligned} \frac{V_0}{V_{in}} &= \frac{i_{d1}(1/g_{m3})}{V_{gs1} + i_{d1}(1/g_{m3})} \\ &= \frac{i_{d1}(1/g_m)}{i_{d1}(1/g_m) + i_{d1}(1/g_m)} = \frac{1}{2} \\ &= 0.5 \end{aligned}$$

(OR)

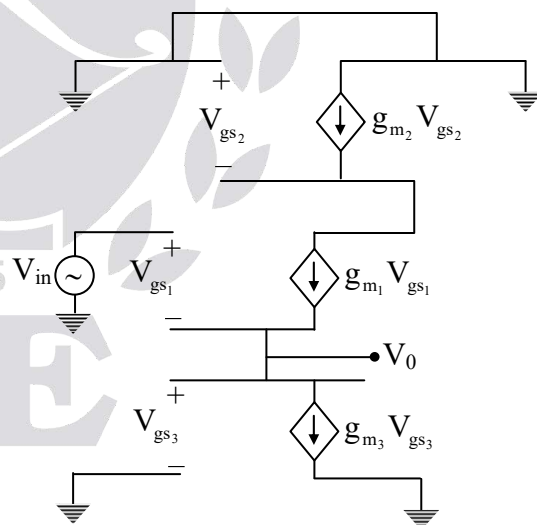

From the above diagram

$$g_{m1} V_{gs1} = g_{m3} V_{gs3}$$

$$\Rightarrow V_{gs1} = V_{gs3} (\because g_{m1} = g_{m2} = g_{m3} = g_m) \quad (1)$$

$$\text{By KVL, } V_{gs1} = V_{in} - V_0 \quad (2)$$

$$V_0 = V_{gs3} \quad (3)$$



Apply Equation (2) and (3) in equation (1)

$$V_{in} - V_0 = V_0$$

$$\Rightarrow V_{in} = 2V_0$$

$$\Rightarrow \frac{V_0}{V_{in}} = \frac{1}{2} = 0.5$$

39. Photons of wavelength 900 nm are incident on a photodiode at the rate of $50 \times 10^{10} \text{ s}^{-1}$ and an average, electrons are collected at the terminals of the diode at the rate of $11 \times 10^{10} \text{ s}^{-1}$. The responsivity of the given photodiode at 900 nm wavelength is

$$\left[\begin{array}{l} \text{Take } h = 6.6 \times 10^{-34} \\ e = 1.6 \times 10^{-19} \\ c = 3 \times 10^8 \end{array} \right]$$

39. Ans: 0.16 [Range: 0.155 to 0.165]

Sol: We know


$$\eta = \frac{\text{Electron current rate}}{\text{Photon current rate}}$$

$$= \frac{11 \times 10^{10}}{50 \times 10^{10}} = 0.22$$

Responsivity

$$R = \frac{\eta e \lambda}{hc} = \frac{0.22 \times 1.6 \times 10^{-19} \times 900 \times 10^{-9}}{6.6 \times 10^{-34} \times 3 \times 10^8} = 0.16$$

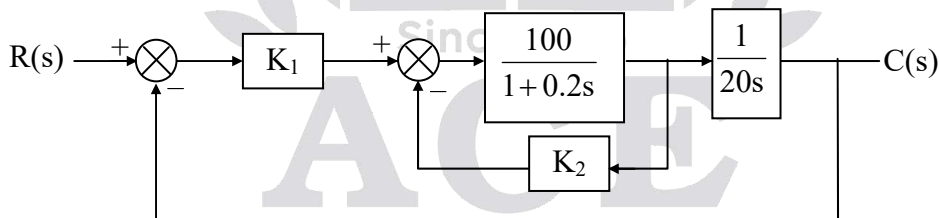40. The system shown below has second order response with a damping ratio of 0.5 and a settling time with $\pm 2\%$ tolerance is 0.5 sec. Then the value of K_1 is _____



40. Ans: 10.24 [Range: 10 to 11]

$$\text{Sol: } \frac{C(s)}{R(s)} = \frac{100K_1 / (20s(1+0.2s))}{1 + \frac{100K_2}{(1+0.2s)} + \frac{100K_1}{20s(1+0.2s)}} = \frac{100K_1}{20s(1+0.2s) + 100K_2(20s) + 100K_1}$$

$$\frac{C(s)}{R(s)} = \frac{100K_1}{20s + 4s^2 + 2000K_2s + 100K_1} = \frac{100K_1}{4s^2 + s(2000K_2 + 20) + 100K_1}$$



$$\underline{\text{CE}} \quad 4s^2 + s(2000K_1 + 20) + 100K_1 = 0$$

$$\underline{\text{CE}} \quad s^2 + s(500K_1 + 5) + 25K_1 = 0$$


Given Data: $\xi = 0.5$, $t_s = 0.5$ sec

$$\pm 2\% \quad t_s = \frac{4}{\xi \omega_n} \Rightarrow 0.5 = \frac{4}{0.5 \times \omega_n}$$

$$\Rightarrow \omega_n = 16 \text{ rad/sec}$$

$$\omega_n^2 = 25K_1 \Rightarrow K_1 = \frac{256}{25} = 10.24$$

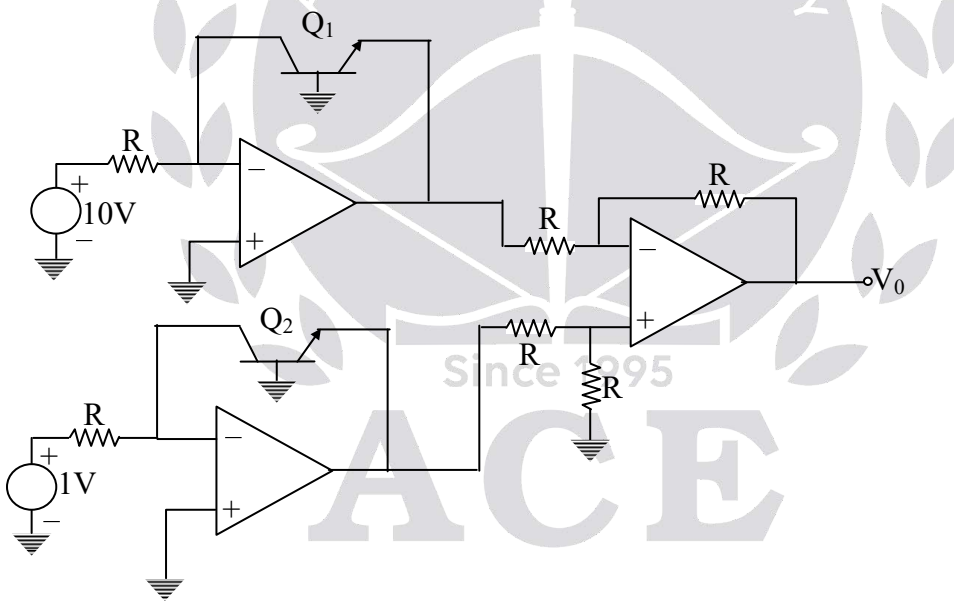41. The transistors shown obey a non linear relation $I_C = I_S e^{\frac{V_{be}}{V_T}}$ where V_T is the thermal voltage equal to 25mV and I_S is the reverse saturation current. If β is large, then the value of output voltage V_0 (in milli volt) is _____



41. **Ans: 57.56 [Range: 57 to 58]**

Sol: Here $V_{e2} = -V_{BE2}$, $V_{e1} = -V_{BE1}$

$$V_0 = V_{e2} - V_{e1} = V_{be1} - V_{be2} = V_T \ln \left[\frac{I_{C1}}{I_{C2}} \right]$$

$$= V_T \ln \left[\frac{10/R}{1/R} \right] = 25m \ln[10]$$

$$V_0 = 57.56 \text{ mV}$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



HYDERABAD | DELHI | VIJAYAWADA | TIRUPATI | PUNE | BHUBANESWAR | BENGALURU | LUCKNOW | CHENNAI | VIZAG | KOLKATA | AHMEDABAD

ADMISSIONS ARE OPEN FOR ESE | GATE | PSUs - 2021 & 2022 @ DELHI

Streams: CE | ME | EC | EE | CS | IT | IN | PI

WEEKEND BATCHES START FROM



11th JAN 2020



8th FEB 2020

Special Discounts for Weekend Batches @ DELHI

Colleges	Individual Discounts	Group Discounts (Minimum 10 Students)	College/Branch Topper Rank 1 & 2
IIT	40% OFF on Tuition Fee	45% OFF on Tuition Fee	50% OFF on Tuition Fee
NIT/DTU/NSUT IIIT/IGDTUW	30% OFF on Tuition Fee	35% OFF on Tuition Fee	40% OFF on Tuition Fee
JMI/USICT YMCA/DCRUST UIET (MDU & KUK)	20% OFF on Tuition Fee	25% OFF on Tuition Fee	30% OFF on Tuition Fee
Other Govt. Engg. Colleges	15% OFF on Tuition Fee	20% OFF on Tuition Fee	25% OFF on Tuition Fee
IPU/AKTU MDU/KUK Affiliated Colleges	10% OFF on Tuition Fee	15% OFF on Tuition Fee	20% OFF on Tuition Fee



ARMED FORCES
CHILDREN

40% OFF
on Tuition Fee

DIFFERENTLY ABLED

50% OFF
on Tuition Fee

Single Parent
(Father Deceased)

50% OFF
on Tuition Fee

Also, Special Discounts
for Previously Qualified
ESE (Prelims/Mains)
/ GATE Students

for more details visit our website:


www.aceenggacademy.com

* Terms & Conditions Apply

Call Us Today for Career Counselling : **7838971777** | Email: delhi@aceenggacademy.com



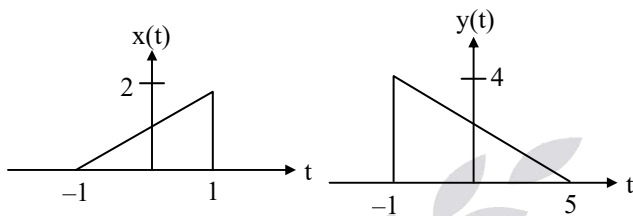42. Consider the signals $x(t)$ & $y(t)$ as shown below. Then $y(t)$ expression in terms of $x(t)$ as $y(t) = Ax\left(\frac{t}{B} + C\right)$. Then the value of $A + B + C$ is _____



42. Ans: -0.333 [Range: -0.30 to -0.35]

Sol: $y(t)$ is amplitude scaled by 2 it is also folded, expanded & shifted version of $x(t)$
 $y(t)$ can be expressed as $y(t) = Ax(\alpha t + \beta)$
 $t = -1$ of $x(t)$ corresponds to $t = 5$ of $y(t)$
 $t = 1$ of $x(t)$ corresponds to $t = -1$ of $y(t)$

$$\left. \begin{array}{l} 5\alpha + \beta = -1 \\ -\alpha + \beta = 1 \end{array} \right\} \alpha = -\frac{1}{3} \text{ \& } \beta = \frac{2}{3}$$

$$\therefore y(t) = 2x\left(\frac{-t}{3} + \frac{2}{3}\right)$$

$$\text{But, given } y(t) = Ax\left(\frac{t}{B} + C\right)$$


$$\text{Then } A = 2$$

$$B = -3$$

$$C = \frac{2}{3}$$


$$A + B + C = \frac{-1}{3} = -0.333$$

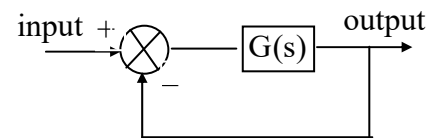43. Consider the feedback control system shown in figure below.



$$\text{where } G(s) = \frac{k}{s(1 + sT_1)(1 + sT_2)(1 + sT_3)},$$

whose Bode plot is given below.

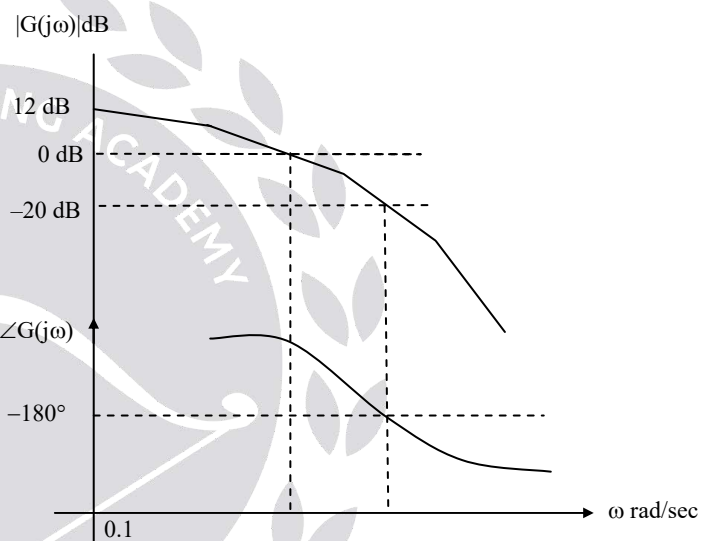

Then the maximum value of 'k' for stability of the system is _____.

43. Ans: 4 [Range: 3.9 to 4]

Sol: For maximum value of k, system should be marginally stable. So, GM = 0 dB.

⇒ Magnitude plot has to shift up by +20 dB

$$20 \log k - 20 \log \omega|_{\omega=0.1} = 12 + 20$$

$$= 32 \text{ dB}$$

$$20 \log k = 12 \text{ dB}$$

$$k = 4$$

New Year Special OFFER



31st DEC 2019 to 15th JAN 2020

40% Discount

GATE – 2020
Online Test Series

Available Now

No. of Tests : 64
+

Free 52 Practice Tests of
GATE – 2019 Online Test Series

50% Discount

ESE – 2020 PRELIMS
Online Test Series

Available Now

No. of Tests : 44
+

Free 30 Practice Tests of
ESE – 2019 Online Test Series

40% Discount

GATE+ESE – 2020
Online Test Series
Combination Pack

All Tests
Will Be Available Till
Respective Exams

☎ 040 – 48539866 / 040 – 40136222

✉ testseries@aceenggacademy.com

UPCOMING BATCHES @ PUNE

(Streams: ME / CE / EC / EE / CS / IT / IN / PI)

LONG TERM PROGRAM

GATE+PSUs 2021

Weekend Batches:
28th December 2019
01st February 2020

Evening Batch
10th February 2020

MPSC

PRELIMS (CE/ME/EE)

Evening Batch
20th January 2020

TWO YEARS PROGRAM

GATE+PSUs 2022

Weekend Batch
01st February 2020

ESE+GATE+PSUs 2022

Weekend Batch
01st February 2020


Branch Office: #302, Venkatest Villa, CTS 1204/9, Upstairs: Janata Sahakari Bank,
Ghole Road, Mahatma Phule Museum, Shivaji Nagar, Pune – 411005.

Call: 020-25535950, 9343499966 | Web: www.aceenggacademy.com



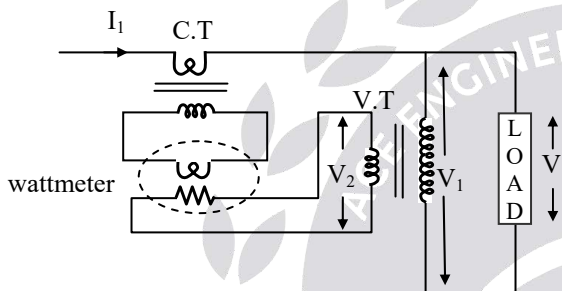
44. An electro dynamic wattmeter with maximum voltage & current ranges of 115 V & 1A respectively it's range extended by C.T & V.T. shown in figure transformer ratio are $\frac{V_1}{V_2} = 2$, & $\frac{I_1}{I_2} = 5$.

If the load voltage is 220 V, load current is 5 A lagging voltage by 25° .
The wattmeter indication in watts is



44. **Ans: 99.7** [Range: 99 to 100]

Sol:

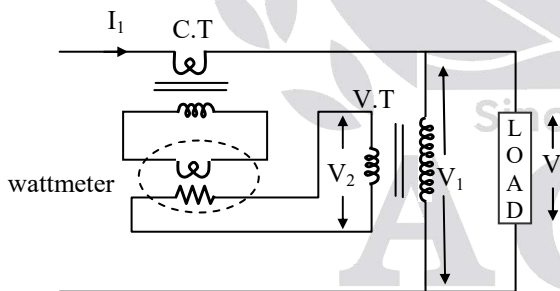

$$I_2 = \frac{I_1}{\left(\frac{I_1}{I_2}\right)} = \frac{5A}{5} = 1A,$$

$$V_2 = \frac{V_1}{\left(\frac{V_1}{V_2}\right)} = \frac{220V}{2} = 110V$$

$$\text{Wattmeter reading} = 110 \text{ V} \times 1A \times \cos 25^\circ = 99.7W$$

45. Consider the differential equation $\frac{dy}{dx} + 2xy = e^{-x^2}$ with initial condition $y(0) = 1$. The value of $y(1)$ is ____.

45. **Ans: 0.7357** [Range 0.73 to 0.74]

Sol: Given $\frac{dy}{dx} + 2xy = e^{-x^2}$ (1)

with $y(0) = 1$ (2)

$$\therefore \text{I. F.} = e^{\int 2x \, dx} = e^{x^2}$$

Now, the general solution of (1) is

$$\Rightarrow y \cdot e^{x^2} = \int e^{x^2} \cdot e^{-x^2} \, dx + c$$

$$\Rightarrow y \cdot e^{x^2} = x + c \quad \text{..... (3)}$$

Using (2), (3) becomes

$$\Rightarrow 1 = 0 + c \Rightarrow c = 1$$

$$y = x e^{-x^2} + e^{-x^2}$$

$$y = (x + 1) e^{-x^2}$$

$$\therefore y(1) = 2 \times e^{-1} = 0.7357$$

46. The surface integral $\iint_S (\vec{F} \cdot \vec{n}) \, dS$ over the surface S of the sphere $x^2 + y^2 + z^2 = 9$, where $F = (x+y)\vec{i} + (x+z)\vec{j} + (y+z)\vec{k}$ and \vec{n} is the unit outward surface normal, yields ____.

46. **Ans: 226.08** [Range: 226 to 227]

Sol: $\vec{F} = (x + y)\vec{i} + (x + z)\vec{j} + (y + z)\vec{k}$



$$\text{div } \vec{F} = 1 + 1 = 2$$

$$\iiint_S \vec{F} \cdot \vec{n} \, dS = \iiint_V \text{div } \vec{F} \, dx \, dy \, dz$$

(By Gauss divergence theorem)

$$= \iiint 2 \, dx \, dy \, dz$$

$$= 2 \times \text{volume of the sphere}$$

$$= 2 \times \frac{4}{3} \pi (3)^3 = 72 \pi = 226.08$$

47. Consider a control system with

$$G(s) = \frac{K(s+40)}{s(s+10)}, H(s) = \frac{1}{(s+20)}$$

The value of 'k' for which the system will oscillate is _____

47. **Ans: 600**

Sol: CE $1 + G(s)H(s) = 0$

CE $1 + \frac{K(s+40)}{s(s+10)} \cdot \frac{1}{(s+20)} = 0$

CE $s(s+10)(s+20) + K(s+40) = 0$

CE $s^3 + 30s^2 + s(K+200) + 40K = 0$

CE $-s^3 + 30s^2 + s(K+200) + 40K = 0$

$$\begin{array}{l|ll} s^3 & 1 & K+200 \\ s^2 & 30 & 40K \\ s^1 & \left(\frac{30(K+200) - 40K}{30} \right) & \\ s^0 & 40K & \end{array}$$

For marginal stable

$$\Rightarrow (30K + 6000 - 40K) = 0$$

$$10K = 6000$$

$$K = 600$$

48. The value of the double integral

$$\int_0^8 \left(\int_{y/2}^{(y/2)+1} \left(\frac{2x-y}{2} \right) dx \right) dy, \quad \text{using the}$$

substitution $u = \left(\frac{2x-y}{2} \right)$ and $v = \frac{y}{2}$ is

_____.

48. **Ans: 4**

Sol: Given $u = \frac{2x-y}{2}$ and $v = \frac{y}{2}$

$$\Rightarrow du = dx, \quad dv = \frac{dy}{2} \quad \text{and} \quad dy = 2 \, dv$$

If $x = \frac{y}{2}$ then $u = 0$

If $x = \frac{y}{2} + 1$ then $u = 1$

If $y = 0$ then $v = 0$

If $y = 8$ then $v = 4$

$$\int_0^8 \left[\int_{\frac{y}{2}}^{\frac{y}{2}+1} \left(\frac{2x-y}{2} \right) dx \right] dy = \int_{v=0}^4 \int_{u=0}^1 2u \, du \, dv = 4$$

49. Given F.T of $x(t)$ is $X(f) = 8\text{Sinc}(2f)\text{Sinc}(4f)$. Then the value of $x(t)$ at $t = 0$ is _____

49. **Ans: 2**

Sol: Using plancheral's theorem




$$\int_{-\infty}^{\infty} x_1(t)x_2(t)dt = \int_{-\infty}^{\infty} X_1(f)X_2(f)df$$

$$\text{Arect}\left(\frac{t}{T}\right) \leftrightarrow AT \text{Sinc}(fT)$$

$$8\text{Sinc}(2f)\text{Sinc}(4f) = [2 \text{Sinc}(2f)][4\text{Sinc}(4f)]$$



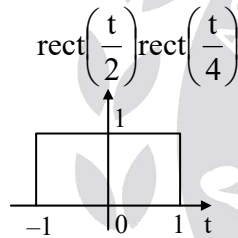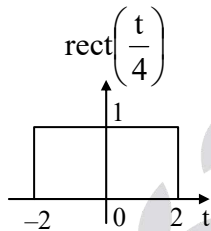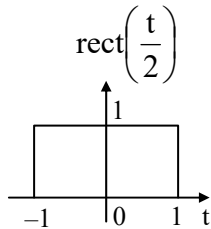
$$\int_{-\infty}^{\infty} (2\text{Sinc}(2f))(4\text{Sinc}(4f))df = \int_{-\infty}^{\infty} \text{rect}\left(\frac{t}{2}\right)\text{rect}\left(\frac{t}{4}\right)dt$$



$$\int_{-\infty}^{\infty} \text{rect}\left(\frac{t}{2}\right)\text{rect}\left(\frac{t}{4}\right)dt = \int_{-1}^1 (1)dt = 2$$

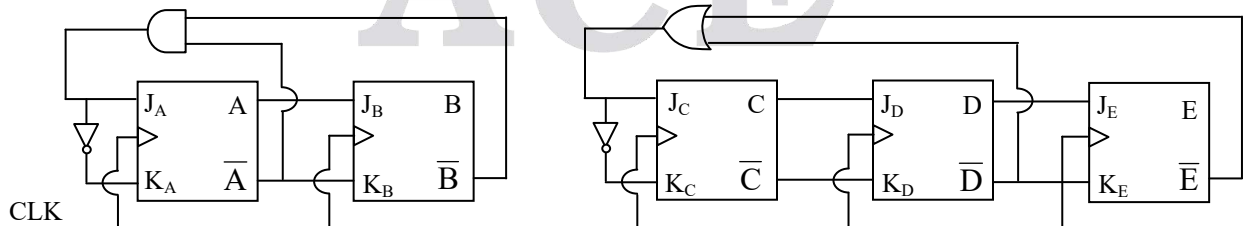50. Two Johnson counters of 2-bit and 3-bit are connected parallelly as shown in the following figure. The initial value of the counter is ABCDE = 00001. The modulus of the counter is _____



50. Ans: 15

Sol: In the given figure

$$J_A = \overline{A} \cdot \overline{B} = \overline{A + B}$$

$$J_B = A$$

$$J_C = \overline{D} + \overline{E} = \overline{DE}$$

$$J_D = C$$

$$J_E = D$$

$$K_A = A + B$$

$$K_B = \overline{A}$$

$$K_C = DE$$

$$K_D = \overline{C}$$

$$K_E = \overline{D}$$




CLK	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D	J _E	K _E	A	B	C	D	E
0											0	0	0	0	1
1	1	0	0	1	1	0	0	1	0	1	1	0	1	0	0
2	0	1	1	0	1	0	1	0	0	1	0	1	1	1	0
3	0	1	0	1	1	0	1	0	1	0	0	0	1	1	1
4	1	0	0	1	0	1	1	0	1	0	1	0	0	1	1
5	0	1	1	0	0	1	0	1	1	0	0	1	0	0	1
6	0	1	0	1	1	0	0	1	0	1	0	0	1	0	0
7	1	0	0	1	1	0	1	0	0	1	1	0	1	1	0
8	0	1	1	0	1	0	1	0	1	0	0	1	1	1	1
9	0	1	0	1	0	1	1	0	1	0	0	0	0	1	1
10	1	0	0	1	0	1	0	1	1	0	1	0	0	0	1
11	0	1	1	0	1	0	0	1	0	1	0	1	1	0	0
12	0	1	0	1	1	0	1	0	0	1	0	0	1	1	0
13	1	0	0	1	1	0	1	0	1	0	1	0	1	1	1
14	0	1	1	0	0	1	1	0	1	0	0	1	0	1	1
15	0	1	0	1	0	1	0	1	1	0	0	0	0	0	1

So, the modulus of the counter is 15

51. Consider an electromagnetic flow meter which is used to measure volumetric flow of a process fluid in a pipe of 60 mm diameter. The velocity profile is symmetrical and can be assumed uniform. The flux density in the fluid is 0.1 Wb/m^2 . The output from the flow meter is given to an amplifier of gain 1000 and impedance between the electrodes is $250 \text{ k}\Omega$. The input impedance of the amplifier is $250 \text{ k}\Omega$. The average velocity (in m/sec) of the liquid when the peak to peak voltage at the amplifier output is 0.6 V .

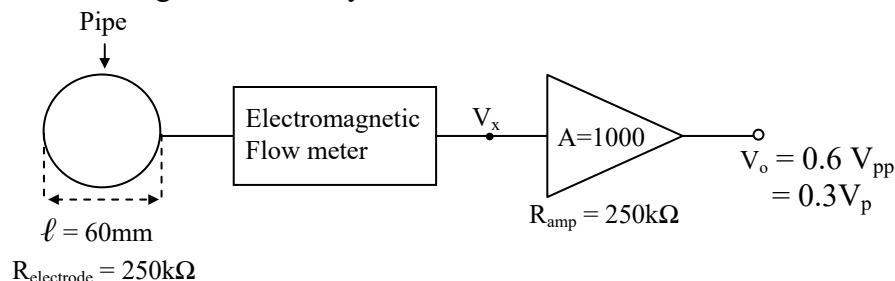51. Ans: 0.1

Sol: Let V_F = average flow velocity of fluid





Voltage generated by electromagnetic flow meter

$$e = B l V_F$$

$$e = 0.1 \times 60 \times 10^{-3} V_F = 6 \times 10^{-3} V_F \quad (V_F = \text{velocity})$$

Voltage at the input of op-amp

$$V_x = \frac{R_{amp}}{R_{amp} + R_{electrode}} \times e = \frac{250k}{250k + 250k} \times 6 \times 10^{-3} V_F = 3mV \times V_F$$

Voltage at output of op-amp

$$V_o = 3mV \times V_F \times A = 0.3$$

$$V_F = \frac{0.3}{3 \times 10^{-3} \times 1000} = 0.1 (\text{m/sec})$$

52. An RTD has $\alpha(20^\circ\text{C}) = 0.004(1/^\circ\text{C})$ RTD has resistance of 106Ω at 20°C . The RTD has a dissipation constant of $25(\text{mW}/^\circ\text{C})$ and is used in a circuit that puts 8mA through the sensor. If the RTD is placed in a bath at 100°C , then RTD indicated temperature in $^\circ\text{C}$ is
(A) 100.00 (B) 99.64 (C) 100.63 (D) 100.36

52. Ans: (D)

Sol: $\alpha(20^\circ\text{C}) = 0.004(1/^\circ\text{C})$

RTD = 106Ω at $T = 20^\circ\text{C}$

$P_D = 25(\text{mW}/^\circ\text{C})$

R_2 is RTD resistance at 100°C

$$R_2 = 106 [1 + 0.004(100 - 20)] = 139.92 \Omega$$

$$P = \text{power dissipation in RTD due to } 8\text{mA current} = (8\text{mA})^2 \times 139.92\Omega \\ = 8.95(\text{mW})$$


$$\text{So rise in temperature} = \frac{P}{P_D} = \frac{8.95(\text{mW})}{25(\text{mW}/^\circ\text{C})}$$

$$\Delta T = 0.36(^\circ\text{C})$$

$$\text{So the RTD indicated temperature} = 100^\circ\text{C} + \Delta T = 100 + 0.36 = 100.36^\circ\text{C}$$

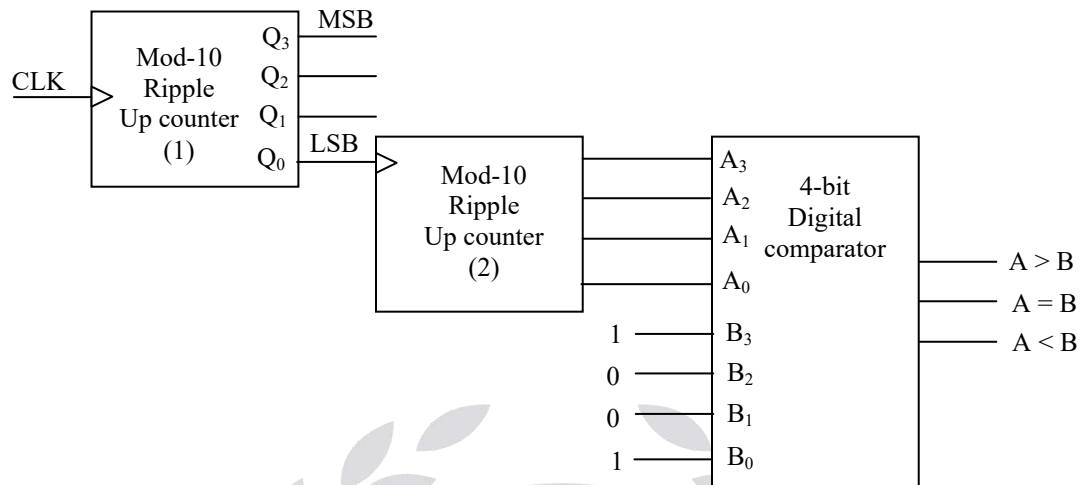53. In the following logic circuit, find the minimum number of clock pulses required to obtain the A = B output HIGH of digital comparator.

Initially both counters are cleared and $A < B$ output is high.



(A) 9 (B) 17 (C) 18 (D) 88

53. Ans: (B)

Sol: Here CLK of up counter (2) is Q_0 of up counter (1).

CLK	Q_3	Q_2	Q_1	Q_0	A_3	A_2	A_1	A_0	B_3	B_2	B_1	B_0	$A = B$
0	0	0	0	0	0	0	0	0	1	0	0	1	0
1	0	0	0	1	0	0	0	1	1	0	0	1	0
2	0	0	1	0	0	0	0	1	1	0	0	1	0
3	0	0	1	1	0	0	1	0	1	0	0	1	0
4	0	1	0	0	0	0	1	0	1	0	0	1	0
5	0	1	0	1	0	0	1	1	1	0	0	1	0
6	0	1	1	0	0	0	1	1	1	0	0	1	0
7	0	1	1	1	0	1	0	0	1	0	0	1	0
8	1	0	0	0	0	1	0	0	1	0	0	1	0
9	1	0	0	1	0	1	0	1	1	0	0	1	0
10	0	0	0	0	0	1	0	1	1	0	0	1	0
11	0	0	0	1	0	1	1	0	1	0	0	1	0
12	0	0	1	0	0	1	1	0	1	0	0	1	0
13	0	0	1	1	0	1	1	1	1	0	0	1	0
14	0	1	0	0	0	1	1	1	1	0	0	1	0
15	0	1	0	1	1	0	0	0	1	0	0	1	0
16	0	1	1	0	1	0	0	0	1	0	0	1	0
17	0	1	1	1	1	0	0	1	1	0	0	1	1
18	1	0	0	0									



AST

Get upto
100%
SCHOLARSHIP
on Tuition Fee

★ **ACE SCHOLARSHIP TEST** ★

A NATIONAL LEVEL SCHOLARSHIP TEST FOR ENGINEERS
GATE | ESE | PSUs

Exam Date : 23rd February 2020

@ 11:00 AM

No. of Questions: **50** (1M:25, 2M:25)

Marks : **75**

Duration : **90 Min.**

Streams : **EC | EE | ME | CE | CSIT | IN | PI**

Mode of Exam

Online



* AI based proctoring examination

* Test can be written from anywhere by using Computer (Desktop or Laptop) and Webcam.

Syllabus for **2nd Year Students - Aptitude Paper**

Engg. Mathematics : 20 Q

Numerical Ability : 20 Q

Verbal Ability : 10 Q

Syllabus for **3rd / 4th Year & Passed-out Students - Technical Paper**

EEE		ECE / IN		CS & IT		CE		ME / PI	
Subject	No. of Questions	Subject	No. of Questions	Subject	No. of Questions	Subject	No. of Questions	Subject	No. of Questions
Networks	5 Q	Networks	6 Q	DS, PL & Algorithm	10 Q	SOM	5 Q	SOM	6 Q
Control System	5 Q	Control System	6 Q	DBMS	5 Q	FM & HM	5 Q	FM & HM	5 Q
Analog Electronics	4 Q	Analog Electronics	5 Q	Computer Networks	5 Q	Geo Technical Engg.	7 Q	TOM	6 Q
Digital Electronics	5 Q	Digital Electronics	5 Q	Operating System	6 Q	Environmental	7 Q	Machine Design	4 Q
Electrical Machines	8 Q	Signal & Systems	5 Q	Computer Organization	4 Q	Transportation	4 Q	Thermal	7 Q
Power System	7 Q	EDC & VLSI	5 Q	Theory of Computation	6 Q	RCC & STEEL	6 Q	Heat Mass Transfer	4 Q
Power Electronics	6 Q	Communications	8 Q	Digital Electronics	4 Q	Surveying	6 Q	Production	8 Q
Engg. Maths	5 Q	Engg. Maths	5 Q	Engg. Maths	5 Q	Engg. Maths	5 Q	Engg. Maths	5 Q
Numerical / Verbal Ability	5 Q	Numerical / Verbal Ability	5 Q	Numerical / Verbal Ability	5 Q	Numerical / Verbal Ability	5 Q	Numerical / Verbal Ability	5 Q

Allocation of Scholarships

100% Fee Waiver*
1st Position
(50 Members)

75% Fee Waiver*
2nd Position
(100 Members)

50% Fee Waiver*
3rd Position
(250 Members)

4th Position (400 Members) **30% Fee Waiver** | **5th Position** (700 Members) **20% Fee Waiver***
6th Position (1000 Members) **10% Fee Waiver***

(The above given positions should achieve Min. 50% of marks in the test).

Applicable for Batches Commencing between

April 2020 - July 2020

Visit our website for online registrations

www.aceenggacademy.com

Fee **₹ 100/-**

* on Tuition Fee

IMPORTANT DATES : Registrations Start from : **8th December 2019**, End Date: **14th February 2020** | Exam Date: **23rd February 2020**



ACE
Engineering Academy
Leading Institute for ESE/GATE/PSUs



48
ALL INDIA
1st RANKS IN GATE




15
ALL INDIA
1st RANKS IN ESE

Contact: **040-23234418/19/20** | Email: **hyderabad@aceenggacademy.com**

HYDERABAD | TIRUPATI | DELHI | PUNE | BHUBANESWAR | BENGALURU | LUCKNOW | CHENNAI | VIJAYAWADA | VIZAG | KOLKATA | AHMEDABAD




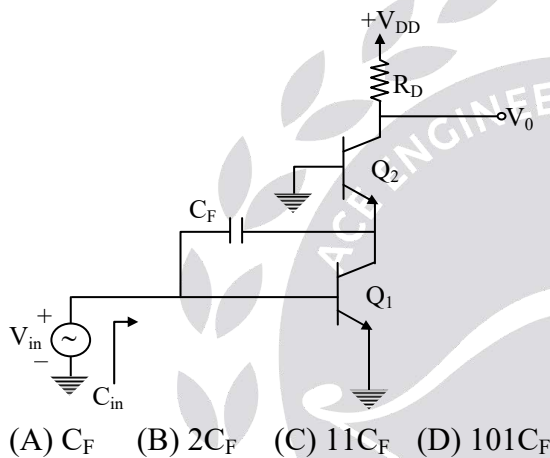54. The transistors Q_1 and Q_2 are similar and neglect early effect. The small signal voltage gain $\left(\frac{V_0}{V_{in}}\right)$ is -100 . Using miller's approximation, find the input capacitance C_{in} (Neglect all other capacitances). Assume the transistors operate with the same bias current.



54. Ans: (B)

Sol: $C_{in} = C_F (1 + A)$

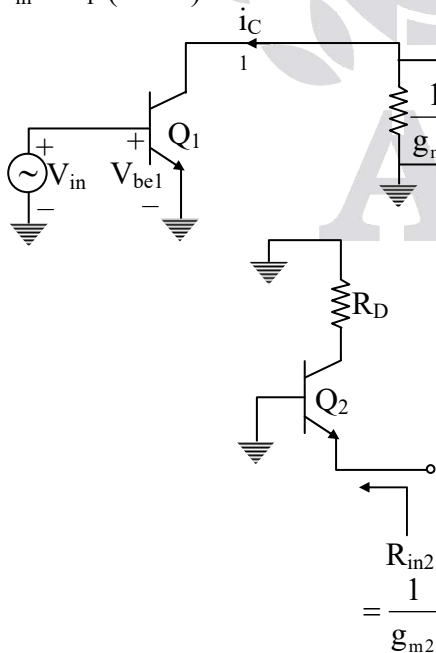


$$\frac{V_{C1}}{V_{in}} = -A = \frac{i_{C1} [1/g_{m2}]}{i_{C1} [1/g_{m1}]} = \frac{-1/g_{m2}}{1/g_{m1}} = -1$$

$$-A = -1$$

$$\therefore A = 1$$

$$C_{in} = C_F (1 + A) = C_F (1 + 1) = 2C_F$$

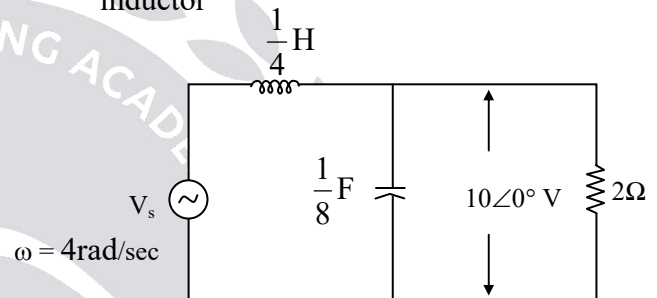
55. For an AC circuit as shown in figure, what is the phase angle of voltage across capacitor lags the voltage across the inductor



- (A) 45° (B) -45°
(C) 135° (D) -135°

55. Ans: (C)

Sol:

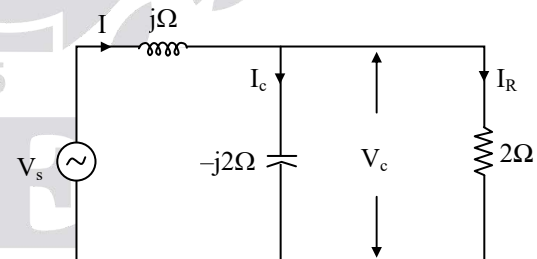

$$I_R = 5A$$

$$I_C = j\omega C V_C = 5 \angle 90^\circ$$

$$I_L = I = I_R + I_C = 5 + j5 = 5\sqrt{2} \angle 45^\circ$$

$$V_L = j\omega L I_L = j5\sqrt{2} \angle 45^\circ = 5\sqrt{2} \angle 135^\circ$$

$$V_C = 10 \angle 0^\circ$$

\Rightarrow Voltage across capacitor lags the voltage across inductor by 135° .



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



HYDERABAD | TIRUPATI | DELHI | PUNE | BHUBANESWAR | BENGALURU | LUCKNOW | CHENNAI | VIJAYAWADA | VIZAG | KOLKATA | AHMEDABAD

DIGITAL CLASSES

for

ESE
GS & Engg. Aptitude

250+

Hours of Classes
with Quizzes

GATE
CS & IT

450+

Hours of Classes
with Quizzes

Launching Soon! for ECE | EEE | MECH | CE | IN



Erudite &
Experienced
Faculty



Free Online
Test Series



Relevant Study Material
by Post



Doubt Clearing
Available



Access the Lectures
from anywhere
and Unlimited Times



Write & Store
Your Notes Online



EMI Option
Available

DEEP
LEARN

Access The Course at
www.deep-learn.in

Call: 040-23234418/19/20 | web: www.aceenggacademy.com



56. Given matrix $[A] = \begin{bmatrix} 4 & 2 & 1 & 3 \\ 6 & 3 & 4 & 7 \\ 2 & 1 & 0 & 1 \end{bmatrix}$, then the

system $AX = O$, where $X = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix}$ has

- (A) no solution
- (B) a unique solution
- (C) only one independent solution
- (D) two linearly independent solutions

56. Ans: (D)

Sol: Given $A = \begin{bmatrix} 4 & 2 & 1 & 3 \\ 6 & 3 & 4 & 7 \\ 2 & 1 & 0 & 1 \end{bmatrix}$

$$R_2 \rightarrow 4R_2 - 6R_1 ;$$

$$R_3 \rightarrow 2R_3 - R_1$$

$$\sim \begin{bmatrix} 4 & 2 & 1 & 3 \\ 0 & 0 & 10 & 10 \\ 0 & 0 & -1 & -1 \end{bmatrix}$$

$$R_3 \rightarrow (10)R_3 + R_2$$

$$\sim \begin{bmatrix} 4 & 2 & 1 & 3 \\ 0 & 0 & 10 & 10 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\therefore \rho(A) = 2$$

\therefore Number of linearly independent solutions

$$= \text{Number of variables} - \text{Rank of } A$$

$$= 4 - 2 = 2$$

57. A temperature transmitter has a calibrated range of -80 to 150 $^{\circ}\text{F}$ & its output signal range is 4 to 20mA . Assuming the perfect calibration (zero error) then the correct table is

(A)

Measured temperature $^{\circ}\text{F}$	% Span	Output Signal (mA)
120	86.96	17.91
-45	15.22	6.435

(B)

Measured temperature $^{\circ}\text{F}$	% Span	Output signal (mA)
120	57.14	13.14
-45	-178.57	-24.57

(C)

Measured temperature $^{\circ}\text{F}$	% Span	Output signal (mA)
120	86.96	17.91
-45	54.35	6.435

(D)

Measured temperature $^{\circ}\text{F}$	% Span	Output signal (mA)
120	15.22	17.91
-45	86.96	6.435

57. Ans: (A)

Sol:

Temp ($^{\circ}\text{F}$)	-80	150
Current (mA)	4	20

T = measured temperature, I = output current signal, S = span percent



$$\frac{T+80}{150+80} = \frac{I-4}{20-4}$$

$$I = \left(\frac{T+80}{230} \right) \times 16 + 4$$

$$T = 120^\circ \text{F} \rightarrow I = \left(\frac{120+80}{230} \right) \times 16 + 4 = 17.91 \text{mA}$$

$$T = -45^\circ \text{F} \rightarrow I = \left(\frac{-45+80}{230} \right) \times 16 + 4 = 6.735 \text{mA}$$

$$\text{Percent of span } S = \frac{T - T_{\min}}{T_{\max} - T_{\min}} \times 100$$

$$T = 120^\circ \text{F} \rightarrow S = \frac{120+80}{150+80} \times 100 = 86.96\%$$


$$T = -45^\circ \text{F} \rightarrow S = \frac{-45+80}{150+80} \times 100 = 15.22\%$$

So the correct option is (a).


58. The open loop transfer function of a system is $G(s)H(s) = \frac{K(s-2)}{(s+1)^2}$

The Nyquist plot for this system is


(A)

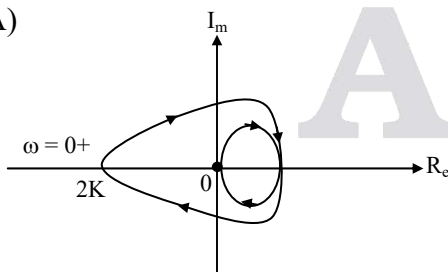


(B)

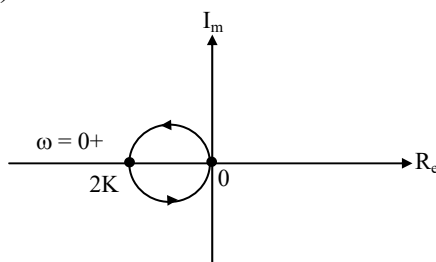

(C)

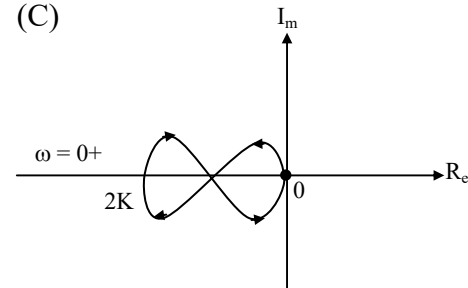

(D)

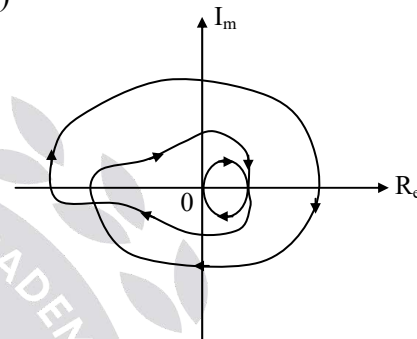

58. Ans: (A)


Sol: $G(j\omega)H(j\omega) = \frac{K(j\omega - 2)}{(j\omega + 1)^2}$

$$M = \frac{K\sqrt{\omega^2 + 4}}{(\omega^2 + 1)} \angle \phi$$


$$= -2 \tan^{-1}(\omega) + \left(180^\circ - \tan^{-1}\left(\frac{\omega}{2}\right) \right)$$

$$\angle \phi = 180^\circ - \tan^{-1}\left(\frac{\omega}{2}\right) - 2 \tan^{-1}(\omega)$$
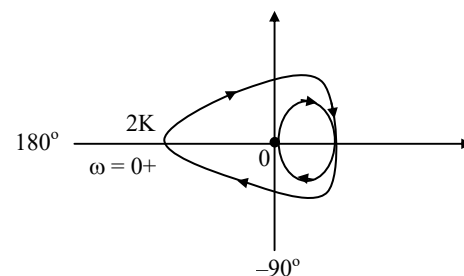
$$\left. \begin{array}{l} \omega = 0 ; 2K \angle 180^\circ \\ \omega = \infty ; 0 \angle -90^\circ \end{array} \right\} \text{Direction is clockwise}$$



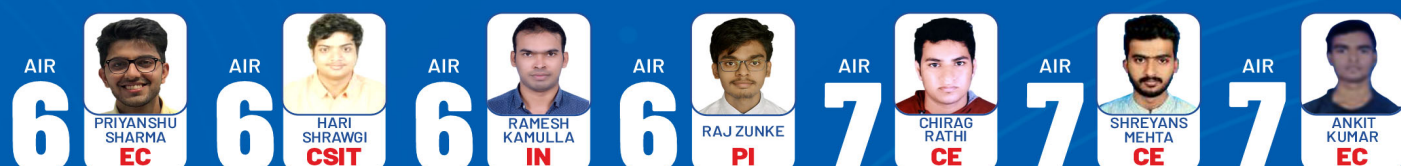Hearty Congratulations to our **GATE-2019 Top Rankers**



and many more...

CE	TOP 10	TOP 100	ME	TOP 10	TOP 100	EE	TOP 10	TOP 100	EC	TOP 10	TOP 100	CS	TOP 10	TOP 100	IN	TOP 10	TOP 100	PI	TOP 10	TOP 100
CE	5	44	ME	6	60	EE	7	71	EC	9	74	CS	5	28	IN	10	74	PI	10	49



59. Let $x(n) = \{3, 4, \underset{\uparrow}{5}, 6\}$. The step interpolated signal $h(n) = x(0.5n-1)$ is _____

(A) $\{3, 0, \underset{\uparrow}{4}, 0, 5, 0, 6, 0\}$

(B) $\{3, 3, \underset{\uparrow}{4}, 4, 5, 5, 6, 6\}$

(C) $\{3, 3, 4, 4, \underset{\uparrow}{5}, 5, 6, 6\}$

(D) $\{3, 4, 5, \underset{\uparrow}{6}, 3, 4, 5, 6\}$

59. Ans: (B)

Sol: $x(n-1) = \{3, \underset{\uparrow}{4}, 5, 6\} = y(n)$

$$h(n) = y\left(\frac{n}{2}\right) = \{3, 3, \underset{\uparrow}{4}, 4, 5, 5, 6, 6\}$$

if we apply step interpolation

60. A 700nm beam with a power of 0.2mW and 5cm diameter strikes a detector with a 0.2cm diameter. The number of photons strike the detector per second is

(A) 0.1128×10^{13}

(B) 0.704×10^{15}

(C) 70.63×10^{13}

(D) 43.962×10^{16}

60. Ans: (A)

Sol: $\lambda = 700 \text{ nm}$

$D = 5 \text{ cm}$

$d = 0.2 \text{ cm}$

$P = 0.2 \text{ mW}$

$$A_1 = \frac{\pi}{4} D^2 = \frac{\pi}{4} \times (5 \times 10^{-2})^2 \\ = 1.96 \times 10^{-3} (\text{m}^2)$$

$$A_2 = \frac{\pi}{4} d^2 = \frac{\pi}{4} \times (0.2 \times 10^{-2})^2 \\ = 3.14 \times 10^{-6} (\text{m}^2)$$

Intensity in the beam

$$I = \frac{P}{A_1} = \frac{0.2 \times 10^{-3}}{\frac{\pi}{4} \times (5 \times 10^{-2})^2} = 0.102 \left(\frac{\text{W}}{\text{m}^2} \right)$$

Energy of each photon

$$= \frac{hc}{\lambda} = \frac{6.62 \times 10^{-34} \times 3 \times 10^8}{700 \times 10^{-9}} \\ = 2.84 \times 10^{-19} (\text{J})$$

The numbers of photons strike the detector per second

$$N = I \left(\frac{\text{W}}{\text{m}^2} \right) \times A_2 \times \frac{1}{E} \\ = I \left(\frac{\text{J}}{\text{sec m}^2} \right) \times A_2 (\text{m}^2) \times \frac{1}{E (\text{J})} \\ = 0.102 \times 3.14 \times 10^{-6} \times \frac{1}{2.84 \times 10^{-19}} \\ N = 0.1128 \times 10^{13} (\text{photons per second}).$$

61. A current transformer has a bar primary & 200 secondary winding turns. The secondary winding burden is an ammeter of resistance 1.2Ω and reactance 0.5Ω .

The secondary winding has a resistance of 0.2Ω & reactance 0.3Ω . The core requires the equivalent of an mmf of 100 AT for magnetization and 50 A for core losses the ammeter connected in the secondary winding circuit indicates 5A, The ratio error and the number of turns to be reduced in the secondary winding in order that ratio error zero for this condition are respectively

(A) -8.5% , 16

(B) $+9.8\%$, 16

(C) -8.5% , 19

(D) $+9.3\%$, 19



61. Ans: (C)

Sol: Total secondary circuit resistance

$$= 1.2 + 0.2 = 1.4 \Omega$$

Total secondary circuit resistance

$$= 0.5 + 0.3 = 0.8 \Omega$$

Total secondary circuit impedance angle

$$(\delta) = \tan^{-1} \left(\frac{0.8}{1.4} \right) = 29.74^\circ$$

$$\cos \delta = 0.8686, \sin \delta = 0.4955, N_p = 1,$$

$$N_s = 200, n = \frac{N_s}{N_p} = 200$$

$$N_p I_m = 100 \text{ AT} \Rightarrow K_n = 200, n = K_n$$

$$I_m = \frac{100}{1} = 100 \text{ A}, N_p I_e = 50 \text{ AT}$$

$$\Rightarrow I_e = \frac{50}{1} = 50 \text{ A}, I_s = 5 \text{ A}$$

$$R = n + \frac{I_e \cos \delta + I_m \sin \delta}{I_s}$$

$$= 200 + \frac{(50 \times 0.8686) + (100 \times 0.4955)}{5}$$

$$= 218.6$$

% Ratio error (%σ)

$$= \frac{K_n - R}{R} \times 100 = \left(\frac{200 - 218.6}{218.6} \right) \times 100$$

$$= -8.5\%$$

* To make ratio error zero, for this $K_n = R$

$$200 = n + \frac{(50 \times 0.8686) + (100 \times 0.4955)}{5}$$

$$200 = n + 18.6$$

$$n = 181.4,$$

$$N_s = n N_p \Rightarrow N_s = 181.4 \times 1 = 181.4$$

Reduction in secondary winding long

$$\text{turns} = 200 - 181.4 \approx 19$$

62. The annual precipitation data of a city is normally distributed with mean and standard deviation as 1000 mm and 200 mm, respectively. The probability that the annual precipitation will be more than 1200 mm is

$$(A) 0.1587 \quad (B) 0.3174$$

$$(C) 0.3456 \quad (D) 0.2345$$

62. Ans: (A)

Sol: Let X = annual precipitation

We know area under normal curve in the interval $(\mu - \sigma, \mu + \sigma) = 0.6826$

where μ is mean and σ is standard deviation

$$\Rightarrow P(800 < X < 1200) = 0.6826$$

Required probability = $P(X > 1200)$

$$= \frac{1 - 0.6826}{2}$$

$$= 0.1587$$

63. In the following 2-bit synchronous up/down counter using T-flip flops


if $m = 1$

\Rightarrow It should act as an 'up counter'

if $m = 0$

\Rightarrow it should act as a "down counter"

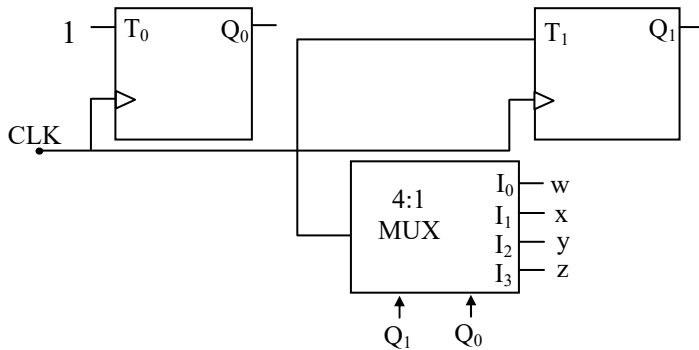w, x, y, z are functions of m , which of the following is correct.



(A) $w = y = m$,

$x = z = \bar{m}$

(C) $w = y = 0$

$x = z = m$

(B) $w = y = \bar{m}$

$x = z = m$

(D) $w = y = m$

$x = z = 1$

63. Ans: (B)

Sol:

P.S	Input		N.S	FF Inputs	
	Q_1	Q_0	m	Q_1	Q_0
	T_1	T_0			
0	0	0	1	1	1
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	1	0
1	1	0	1	0	1
1	1	1	0	0	1

$\Rightarrow T_0 = 1$

$T_1 = Q_0 \odot m$

i.e if $Q_0 = 0 \Rightarrow T_1 = \bar{m}$

if $Q_0 = 1 \Rightarrow T_1 = m$.

Then $I_0 = I_2 = \bar{m}$ i.e $w = y = \bar{m}$

$I_1 = I_3 = m$ i.e $x = z = m$

64. We wish to sample a signal of 1 sec duration, band-limited to 50Hz & compute the DFT of the sampled signal with spectral spacing Δf . The number of zeros needed to be Padded to reduce the spacing to $0.5\Delta f$, using the minimum sampling rate to avoid aliasing if we use radix-2 FFT are

(A) 100

(B) 156

(C) 28

(D) 256

64. Ans: (B)

Sol: Given signal duration = 1 sec

$f_m = 50 \text{ Hz}$ & $f_s = 2f_m = 100 \text{ Hz}$

and $N = (f_s) (\text{signal duration}) = 100 \times 1$

$= 100$

and $\Delta f = \frac{f_s}{N} = 1 \text{ Hz}$

To reduce spectral spacing to

$\frac{\Delta f}{2} = 0.5 \text{ Hz}$, we require 200 samples.

So, $N = 256$ (for FFT)

Available number of samples = 100

\therefore Number of Padding zeros = $256 - 100$

$= 156$

65. Negative feedback is employed in a control system then which one of the following statement (s) is/are true.

1. Gain increases

2. Bandwidth increases



3. Sensitivity of the output with respect to parameter changes in the forward path decreases.

4. Time constant of the system decreases

(A) 1, 2, 3, 4


(B) Only 2, 3, 4

(C) Only 3, 4

(D) Only 2, 4

65. **Ans: (B)**

Sol:

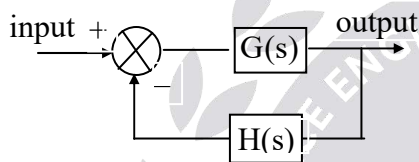

◆ $CLTF = \frac{G(s)}{1 + G(s)H(s)}$

Negative feedback reduces gain of system

◆ $S_G^M = \frac{1}{1 + G(s)H(s)}$ is less than unity

i.e less sensitive to the forward path parameter variations.

◆ Bandwidth increases hence rise time decreases, speed increases, time constant decreases.

Hearty Congratulations to our **ESE-2019 Top Rankers**

AIR 1  KARTIKEYA SINGH EE	AIR 1  RAJAT SONI E&T	AIR 1  HARSHAL BHOSALE ME	AIR 1  ABUZAR GAFFARI CE	
AIR 2  SHAMBHAVI T EE	AIR 2  ANKUSH MANGLA E&T	AIR 2  SAHIL GOYAL ME	AIR 3  ABHISHEK ANAND EE	AIR 3  ROHIT KUMAR E&T
AIR 3  KUMAR CHANDAN ME	AIR 3  AMARJEET CE	AIR 4  ANKIT TAYAL EE	AIR 4  AMIR KHAN E&T	AIR 4  SAURAV ME
AIR 4  AMAN GULIA CE	AIR 5  KUMAR MAYANK EE	AIR 5  AYUSH CHANDRA CE	AIR 6  RITESH LALWANI EE	AIR 6  PUSHPAK ME
AIR 6  KABIL BHARGAVA CE	AIR 7  KARTIKEY SINGH EE	AIR 7  RAHUL JAIN E&T	AIR 7  MANISH RAJPUT ME	AIR 8  KULDEEP KUMAR E&T
AIR 8  HEMANT KUMAR SINGH ME	AIR 8  YOGESH KUMAR CE	AIR 9  DEEPITA ROY EE	AIR 9  SHUBHAM KARNANI E&T	AIR 9  DWEEP SABAPARA ME
AIR 9  ANKIT KUMAR CE	AIR 10  ANKITA SHARMA EE	AIR 10  GAURAV SRIVASTAVA E&T	AIR 10  SUMIT BHAMBOO ME	and many more...

Total Selections in **Top 10: 33** | **EE : 9** | **E&T : 8** | **ME : 9** | **CE : 7**