



ACE
Engineering Academy
Leading Institute for ESE/GATE/PSUs

HYDERABAD | DELHI | PUNE | BANGALORE | LUCKNOW | CHENNAI | VISAKHAPATNAM | VIJAYAWADA | TIRUPATHI | KOLKATA | AHMEDABAD

ESE-2020

(MAINS)

QUESTIONS WITH DETAILED SOLUTIONS

ELECTRONICS & TELECOMMUNICATION ENGINEERING

PAPER-I

ACE Engineering Academy has taken utmost care in preparing the ESE-2020 MAINS Examination solutions. Discrepancies, if any, may please be brought to our notice. ACE Engineering Academy do not owe any responsibility for any damage or loss to any person on account of error or omission in these solutions. ACE Engineering Academy is always in the fore front of serving the students, irrespective of the examination type (GATE/ESE/PSUs/PSC/GENCO/TRANSCO etc.,).

All Queries related to ESE - 2020 MAINS Solutions are to be sent to the following email address hyderabad@aceenggacademy.com

Contact Us : 040-23234418,19,20

www.aceenggacademy.com




ELECTRONICS & TELECOMMUNICATION ENGINEERING
ESE MAINS_2020_PAPER – I
Questions with Detailed Solutions

SUBJECT WISE WEIGHTAGE

S.No	NAME OF THE SUBJECT	Marks
01	Basic Electrical Engineering	40
02	Basic Electronics Engineering	60
03	Materials Science	84
04	Electronic Measurements & Instrumentation	60
05	Network Theory	128
06	Analog Electronics	56
07	Digital Electronics	52

SECTION - A

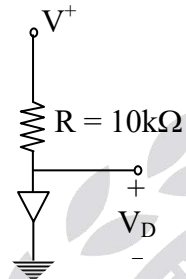
01.(a)(i) Consider the circuit shown below. The power supply V^+ has a dc value of 10V on which is superimposed a 60 Hz sinusoid of 1V peak amplitude, i.e. has a power supply ripple. Calculate both the dc voltage of the diode and the amplitude of the sine-wave signal appearing across it, assuming a 0.7 V drop across it at 1mA current.



(6 M)

Sol:

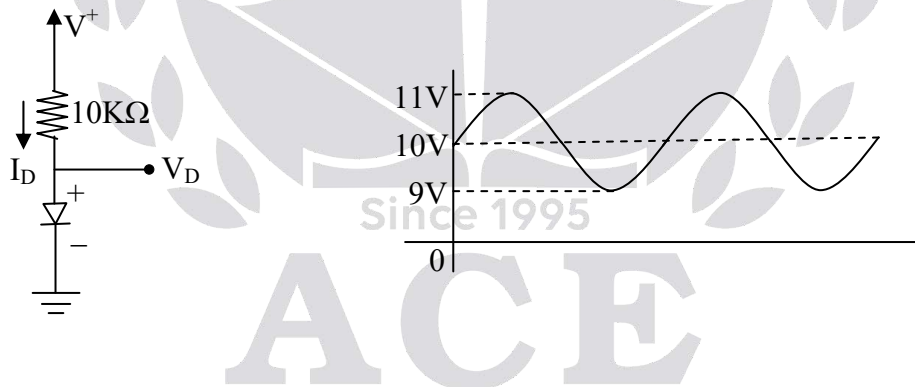(i) Given power supply $V^+ = 10 + V_m \sin \omega t = 10 + 1 \sin 2\pi(60)$



Diode obeys a relation $I_D = I_S e^{\frac{V_D}{V_t}} [\eta = 1]$

$$V_D = V_t \ln \left[\frac{I_D}{I_S} \right]$$

(or)

$$V_{D1} - V_{D2} = V_t \ln \left[\frac{I_{D1}}{I_{D2}} \right]$$

Given $V_D = 0.7V$ when $I_D = 1mA$

$$V_{D1} - 0.7 = 26mV \ln \left[\frac{I_{D1}}{1m} \right]$$

Let as consider $V^+ = 10V, 11V, 9V$

Case1 $V^+ = 10V \rightarrow I_{D1} \approx \frac{10 - 0.7}{10K} = 0.93 \text{ mA}$


$$V_{D1} = 0.7 + 26mV \ln \left[\frac{0.93m}{1m} \right] = 0.698V$$

Case2 $V^+ = 11V \rightarrow I_{D1} \approx \frac{11 - 0.7}{10K} = 1.03m$


$$V_{D1} = 0.7 + 26mV \ln \left[\frac{1.03m}{1m} \right] = 0.70076V$$

Case3: $V^+ = 9V \rightarrow I_{D1} \approx \frac{9 - 0.7}{10K} = 0.83m$
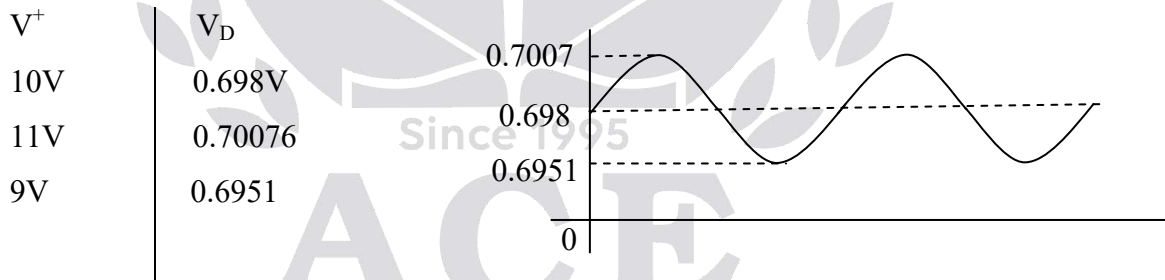
$$V_{D1} = 0.7 + 26mV \ln \left[\frac{0.83m}{1m} \right] = 0.6951V$$




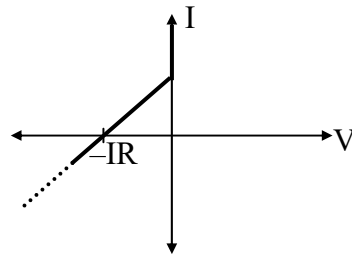01.(a)(ii) For the V-I characteristics as shown below, draw the circuit model using an ideal diode.



(6 M)

Sol:

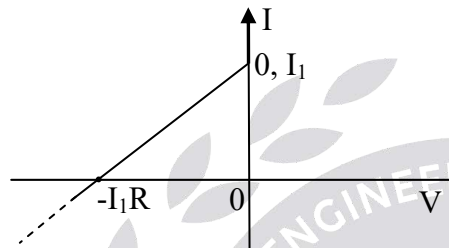

Equation of line $(0, I_1) \quad (-I_1 R, 0)$


$$y - y_1 = \frac{y_2 - y_1}{x_2 - x_1} (x - x_1)$$

$$I - 0 = \frac{I_1}{0 - (-I_1 R)} (V + I_1 R)$$


$$I = \frac{1}{R} (V + I_1 R)$$

(or)


$$V = IR - I_1 R$$

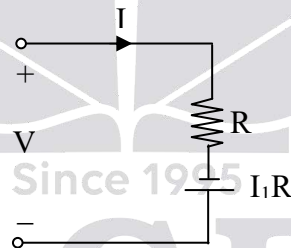

(a) For $I > I_1 \rightarrow V = 0$

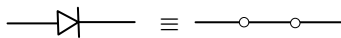

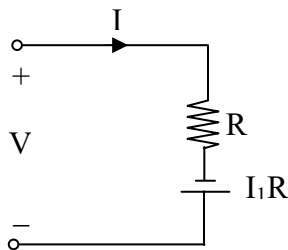(b) For $V < 0 \rightarrow V = IR - I_1 R$





ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

x

DEEP
LEARN




ONLINE COURSES

for **ESE | GATE | PSUs** curated by India's best minds. Access courses through Mobile App only from anywhere.

EXCITING ANNOUNCEMENT!!


We have launched **3 months subscription for GATE 2021**,
Streams: ECE | EEE | ME | CE | CS | IN | PI* **on Deep-Learn**.
Online recorded classes, Fee: Rs. 16,000/- only (without Material).

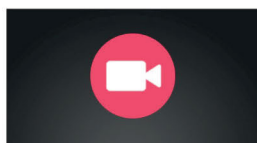

RECORDED VIDEO LECTURES for **GATE + PSUs - 2021/2022**,
ESE + GATE + PSUs - 2021/2022, **ESE : General Studies, SSC-JE**
Streams: ECE | EEE | ME | CE | CS | IN | PI*

SALIENT FEATURES:

- ▶ Dynamic & Experienced Faculty.
- ▶ Subscription options – 3 months, 6 months, 12 months, 18 months & 24 months.
- ▶ Covers Exam Preparation Strategy and Live Doubt clearing sessions.
- ▶ Facilitates Enhanced learning by incorporating 2d & 3d animations.
- ▶ Free Online Test Series (Total 118 tests, subject wise, sectional wise, and full length mock tests).
- ▶ Compose online study notes and save it for future reference.
- ▶ Comprises of weekly self assessment tests.
- ▶ Free Interview Guidance & Post GATE Guidance for subscribers.
- ▶ ASK AN EXPERT feature for doubt clarifications via emails/video (services to be availed within 12 hrs.)
- ▶ Procure Full set of Study Material (Optional)*
- ▶ EMI option available.

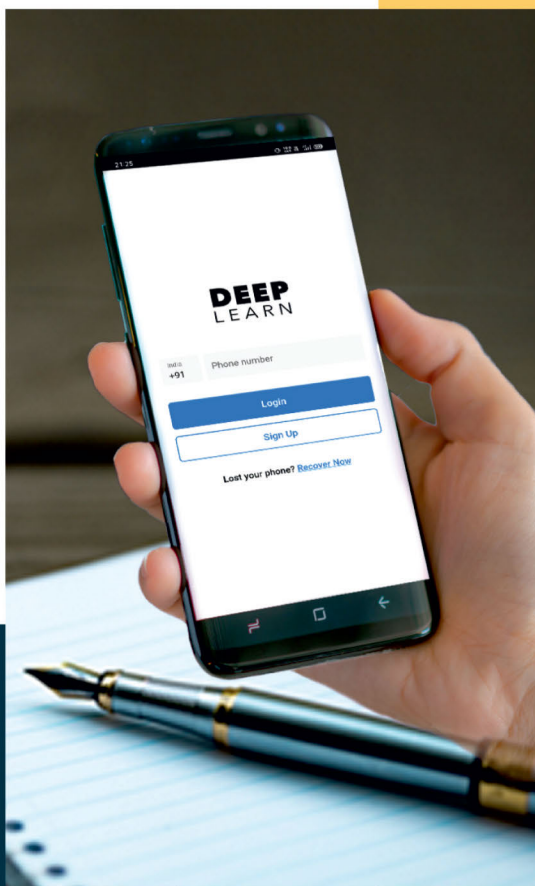

www.deep-learn.in

www.aceenggacademy.com

Help: support@frostinteractive.com


Email: hyderabad@aceenggacademy.com

Call: 040-23234418/19/20

Scan QR Code to
Download DEEP-LEARN
Android Platform App





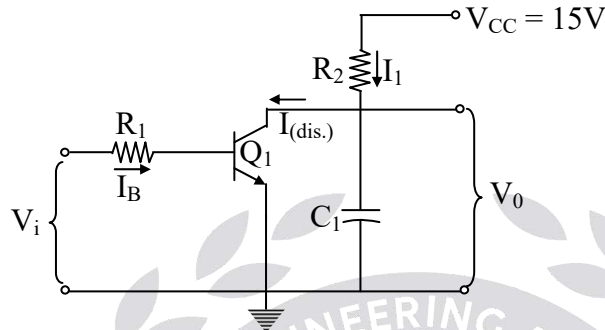01. (b) The circuit shown below is to be used as ramp generator to produce a 1V ramp output when the input is 3V, 0.1ms pulse with a 1ms interval between pulses. The supply voltage is 15V and a load resistance of 100k Ω is connected at the output terminals. Assume Q_1 has $h_{FE(min)} = 50$. Determine values of R_1 , R_2 and C_1 .



(12 M)

Sol:

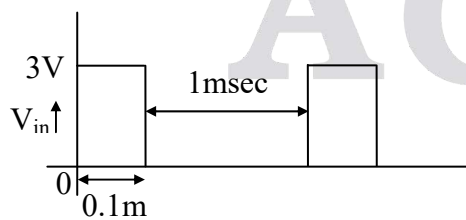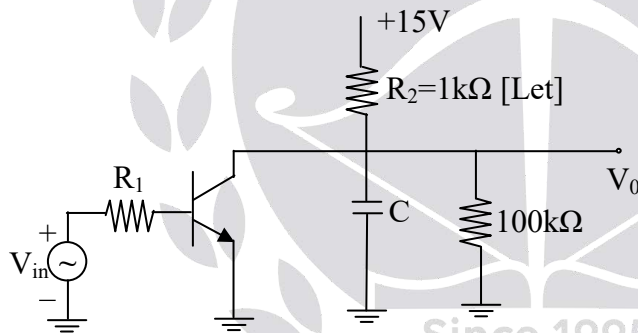


Operation (1) If $V_{in} = 3V$, the transistor is ON.

Capacitor discharges through the transistor

$$V_0 = V_C = V_{CE(sat)} \approx 0V$$

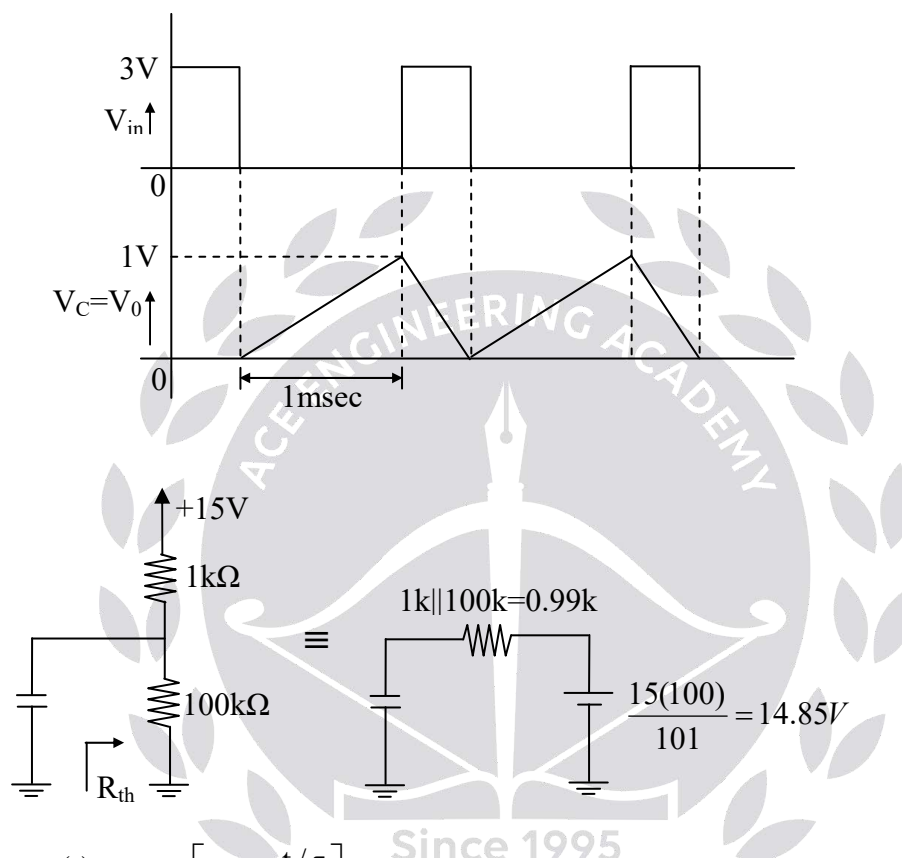2. If $V_{in} = 0V$, the transistor is off. capacitor charges. The final value of capacitor is almost 15V.

The wave form looks almost linear when it charges to 1V in 1msec duration (through the path is exponential)



$$V_C(t) = 14.85 \left[1 - e^{-t/\tau} \right]$$

when $t = 1 \text{ msec} \rightarrow V_c(t) = 1V$

$$\therefore 1 = 14.85 \left[1 - e^{-\frac{1 \text{m}}{\tau}} \right] \rightarrow \tau = 14.34 \text{ msec}$$

$$\therefore \tau = 14.34 \text{ msec} = R_{th} C$$

$$14.34 \text{m} = 0.99 [C]$$

for sat condition

$$|I_B| > \left| \frac{I_C}{\beta} \right|$$


$$I_{C \max} = \frac{(15-1)/1k}{200}$$

$$I_B = \frac{3-0.7}{R_B}$$

$$I_B > I_{C \max} / \beta$$

$$\frac{3-0.7}{R_B} > \frac{14m}{200}$$

$$R_B < 32.857k\Omega$$

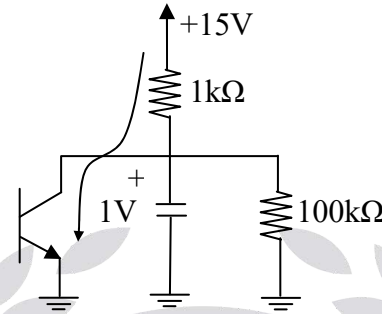

01. (c) A 40 μF capacitance is charged to store 0.2J of energy. An uncharged, 60 μF capacitance is then connected in parallel with the first one through perfectly conducting leads. What is the final energy of the system? (12 M)

Sol: A 40μF charged to 0.2 J

$$W_{C_1} = \frac{1}{2} C_1 V_1^2 \Rightarrow 0.2 = \frac{1}{2} 40 \mu V_1^2$$


$$0.4 = 40 \times 10^{-6} (V_1^2)$$

$$10^4 = V_1^2 \Rightarrow V_1 = 100 \text{ volts}$$

It is connected in parallel with 60μF uncharged capacitor

Capacitor combination voltage V_C
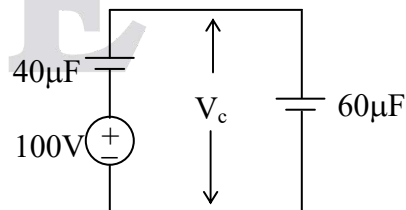
$$V_C = \frac{V_1 C_1 + V_2 C_2}{C_1 + C_2} = \frac{100 \times 40 + 60 \times 0}{(40 + 60)} = 40V$$



$$\text{Total energy} = W_{C_T} = \frac{1}{2} C_T V_C^2$$

$$W_{C_T} = \frac{1}{2} (40 + 60) \times 10^{-6} \times (40)^2 = 0.08J$$

01. (d) Identify magnitude of the Burgers vector for a material having cubic crystal structure, if the density, atomic weight and lattice constant are 7870 kg/m^3 , 55.85 g/mol and 2.86 \AA , respectively. (12 M)

Sol: Given data:

Cubic crystal structure

Density = 7870 kg/m^3

Atomic weight = $A = 55.85 \text{ g/mol}$

Lattice constant = 2.86 \AA

Theoretical density = $\frac{n \times AW}{AN \times V_{vc}}$

$$7870 = \frac{n \times 55.85}{6.023 \times 10^{23} \times (2.86 \times 10^{-10})^3}$$

$$n \approx 2$$

From the above, the crystal structure of metal in body centered cubic (BCC) structure


This slip direction in BCC structure is $[111]$

$$\text{Burgers vector} = \frac{a}{2} [111]$$

$$= \frac{a}{2} [1^2 + 1^2 + 1^2]^{1/2}$$


$$= \frac{a}{2} \times \sqrt{3} = \frac{2.86 \times \sqrt{3}}{2} = 3.502 \text{ \AA}$$

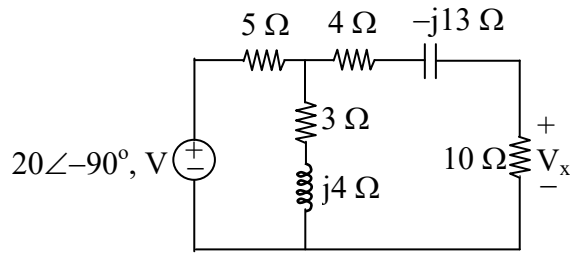01. (e) Calculate V_x in the circuit shown in the figure using the method of source transformation.



(12 M)

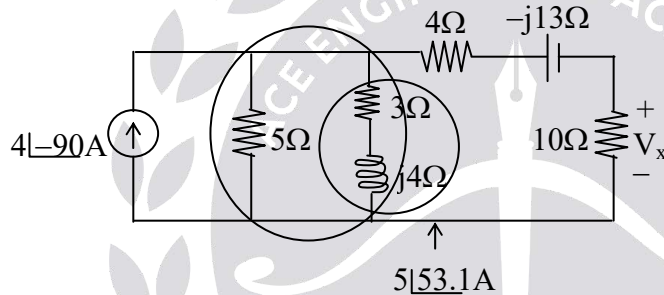
Sol: By STT (source transformation technique)



$$\frac{5(3 + j4)}{(8 + j4)} = \frac{5(5 \angle 53.14)}{4\sqrt{5} \angle 26.56} = 2.79 \angle 26.5$$

$$= 2.79 \angle 26.57 = (2.5 + j1.25)$$

By STT

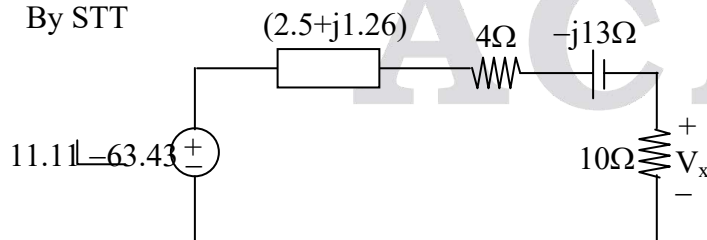


By VDR

$$V_x = \frac{(11.11 \angle -63.43)(10)}{(2.5 + j1.25) + (4 - j13) + 10}$$



$$V_x = 5.484 \angle -27.97 \text{ volts}$$

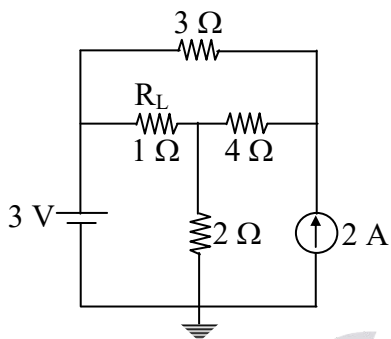02. (a) Find the current through the load resistance ' R_L ' using Thevenin's theorem and hence calculate the voltage across the current source for the circuit shown in figure. (20 M)



Sol: Current in R_L by using Thevenin equation

For V_{oc}

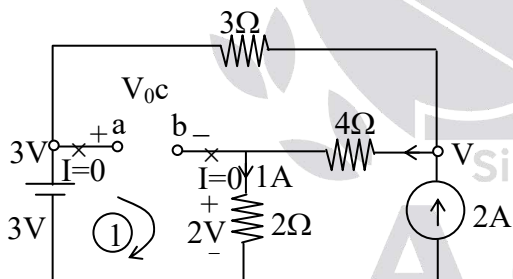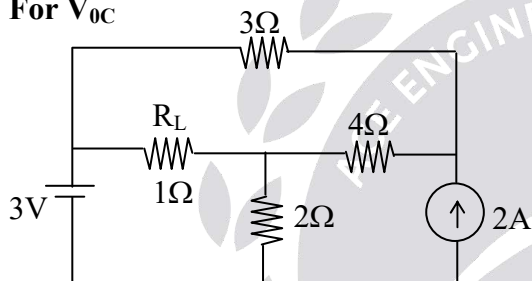

By KCL at V

$$\frac{V-3}{3} + \frac{V}{2+4} = 2 \Rightarrow 2V - 6 + V = 12$$


$$3V = 18 \Rightarrow V = 6 \text{ volts}$$

By KVL for V_{oc}

$$-3 + V_{oc} + 2 = 0$$

$$V_{oc} = V_{th} = 1V$$

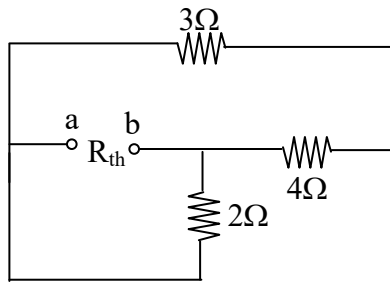
For R_{th} ($V \rightarrow S.C$, $I \rightarrow 0 - C$)



$$R_{th} = (3 + 4) // 2$$

$$R_{th} = \frac{14}{9} \Omega$$


Thevenin's equivalent circuit across R_L

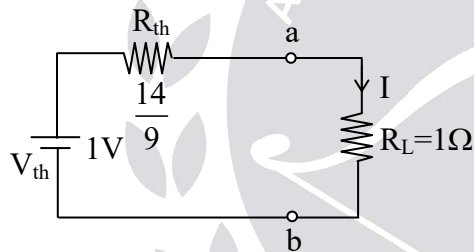

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{1}{\frac{14}{9} + 1} = \frac{9}{23} = 0.39 \text{ A}$$

$$I = 0.4 \text{ A}$$

The voltage across current source

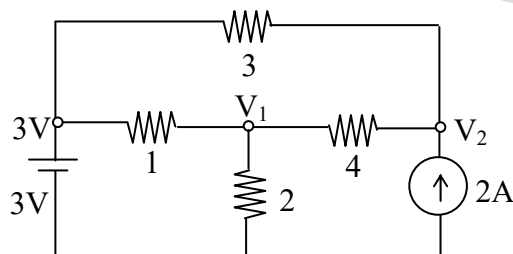

By KCL at V_1

$$\frac{V_1 - 3}{1} + \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 0$$

$$4V_1 - 12 + 2V_1 + V_1 - V_2 = 0$$

$$7V_1 - V_2 = 12 \text{ ----- (1)}$$

By KCL at V_2

$$\frac{V_2 - V_1}{4} + \frac{V_2 - 3}{3} = 2$$

$$3V_2 - 3V_1 + 4V_2 - 12 = 24$$

$$7V_2 - 3V_1 = 36$$

$$3V_1 = 7V_2 - 36 \Rightarrow V_1 = \left(\frac{7V_2 - 36}{3} \right)$$

From (1)

$$7V_1 - V_2 = 12$$

$$7 \left[\frac{7V_2 - 36}{3} \right] - V_2 = 12$$

$$\frac{49}{3}V_2 - 7 \times 12 - V_2 = 12$$

$$\frac{46}{3}V_2 = 8 \times 12 \Rightarrow V_2 = \frac{8 \times 12 \times 3}{46}$$

$$V_2 = 6.26 \text{ Volts}$$

02. (b) An abrupt Si p-n junction ($A = 10^{-4} \text{ cm}^2$) has the following properties at 300 K:

p-side	n-side
$N_a = 10^{17} \text{ cm}^{-3}$	$N_d = 10^{15} \text{ cm}^{-3}$
$\tau_n = 0.1 \mu\text{s}$	$\tau_n = 10 \mu\text{s}$
$\mu_p = 200 \text{ cm}^2/\text{v-s}$	$\mu_n = 300 \text{ cm}^2/\text{v-s}$
$\mu_n = 700 \text{ cm}^2/\text{v-s}$	$\mu_p = 450 \text{ cm}^2/\text{v-s}$

Taken $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$

The junction is forward biased by 0.5V. Find

(i) forward current

(ii) current at a reverse bias of -0.5V.

(20 M)

Sol:
$$I = qA \left[\frac{D_p}{L_p} P_n + \frac{D_n}{L_n} n_p \right] \left[e^{\frac{qV}{KT}} - 1 \right]$$

$$I = I_o \left[e^{\frac{qV}{KT}} - 1 \right]$$

$$P_n = \frac{n_i^2}{n_n} = \frac{(1.5 \times 10^{10})^2}{10^{15}} = 2.25 \times 10^5 \text{ cm}^{-3}$$

$$n_p = \frac{n_i^2}{P_p} = \frac{(1.5 \times 10^{10})^2}{10^{17}} = 2.25 \times 10^3 \text{ cm}^{-3}$$

For minority carriers

$$D_p = \frac{KT}{q} \mu_p = 0.0259 \times 450 = 11.66 \frac{\text{cm}^2}{\text{s}} \text{ on the n side}$$

$$D_n = \frac{KT}{q} \mu_n = 0.0259 \times 700 = 18.13 \frac{\text{cm}^2}{\text{s}} \text{ on the P side}$$

$$L_p = \sqrt{D_p \tau_p} = \sqrt{11.66 \times 10 \times 10^{-4}} = 1.08 \times 10^{-2} \text{ cm}$$

$$L_n = \sqrt{D_n \tau_n} = \sqrt{18.13 \times 0.1 \times 10^{-6}} = 1.35 \times 10^{-3} \text{ cm}$$

$$I_o = qA \left[\frac{D_p}{L_p} P_n + \frac{D_n}{L_n} n_p \right]$$

$$= 1.6 \times 10^{-19} \times 0.0001 \left[\frac{11.66}{0.0108} \times 2.25 \times 10^5 + \frac{18.13}{0.00135} \times 2.25 \times 10^3 \right]$$

$$I_o = 4.37 \times 10^{-15} \text{ A}$$

i) Forward current at a forward bias of O.S.V

$$I = I_o \left[e^{\frac{0.5}{0.0259}} - 1 \right] \approx 1.058 \times 10^{-6} \text{ A}$$

ii) Reverse current at a reverse bias of -O.S.V

$$I = I_o \left[e^{\frac{-0.5}{0.0259}} - 1 \right] \approx -I_o$$

$$= -4.37 \times 10^{-15} \text{ A}$$

EXCLUSIVE

ONLINE LIVE CLASSES

ENGLISH

ESE | GATE | PSUs – 2022

COURSE DETAILS

- **For ESE+GATE+PSUs Students**
 1. Online Live Classes – Technical Subjects Only.
 2. Recorded Classes - General Studies Subjects (on ACE Deep Learn Platform)
- Recorded version of the online live class will be made available through out the course (with 3 times view).
- Doubt clearing sessions and tests to be conducted regularly.
- 3 to 4 hours of live lectures per day in week days (Timing 5 pm to 9 pm) On Sundays 5-6 Hours Live Online Lectures (6 days a week).
- Access the lectures from any where.

BATCH DATE

**7th NOVEMBER
2020**

DISCOUNTS

- ▲ **Rs. 5,000 OFF for ACE Old Students**
- ▲ **Pay Full fee & Get 5% Additional Discount.**
- ▲ **20% off for IIT / NIT, Students.**
- ▲ **15% off for IIIT / Govt. College students.**

FEE

ESE + GATE + PSUs : Rs. 70,000/-
GATE + PSUs : Rs. 55,000/-
(Fee can be paid in two installments)

02. (c) An InGaAs pin photodiode has the following parameters at a wavelength of 1300 nm:

$$I_D = 4 \text{ nA}; \eta = 0.90; R_L = 1 \text{ k}\Omega; P_{in} = 300 \text{ nW}$$

Where P_{in} is incident optical power. The receiver bandwidth is 20 MHz.

Assume surface leakage current is negligible.

Determine

- (i) mean-square shot noise current,
- (ii) mean-square dark current and
- (iii) mean-square thermal noise current.

Which noise is more severe and why?

(20 M)

Sol: Primary photocurrent (I_p)

$$I_p = \frac{\eta q}{hf} P_{in} = \frac{\eta q \lambda}{hc} P_{in}$$

$$I_p = \frac{(0.9) \times (1.6 \times 10^{-19} \text{ C}) \times (1.3 \times 10^{-6} \text{ m})}{(6.625 \times 10^{-34} \text{ J-s}) \times (3 \times 10^8 \text{ m/s})} \times 3 \times 10^{-7} \text{ W}$$

$$I_p = 0.282 \text{ }\mu\text{A}$$

i) Mean square shot noise current (i_{shot}^2):

$$\begin{aligned} i_{\text{shot}}^2 &= 2qI_pB_e \\ &= 2 \times (1.6 \times 10^{-19} \text{ C}) (0.282 \times 10^{-6} \text{ A}) (20 \times 10^6 \text{ Hz}) \\ &= 1.8 \times 10^{-18} \text{ A}^2 \end{aligned}$$

$$\text{or } [i_{\text{shot}}^2]^{1/2} = 1.34 \text{ nA}$$

ii) Mean-square dark current (i_{DB}^2):

$$\begin{aligned} i_{\text{DB}}^2 &= 2qI_D B_e \\ &= 2 \times (1.6 \times 10^{-19} \text{ C}) (4 \times 10^{-9} \text{ A}) (20 \times 10^6 \text{ Hz}) \\ &= 2.56 \times 10^{-20} \text{ A}^2 \end{aligned}$$

$$\text{or } [i_{\text{DB}}^2]^{1/2} = 0.16 \text{ nA}$$

iii) Mean square thermal noise current (i_T^2):

$$i_T^2 = \frac{4K_B T}{R_L} B_e$$

$$= \frac{4(1.38 \times 10^{-23} \text{ J/K})(293 \text{ K})}{1 \text{ K}\Omega} B_e = 323 \times 10^{-8} \text{ A}^2$$

$$\text{or } [i_T^2]^{1/2} = 18 \text{ nA}$$

Thus for this receiver the rms thermal noise current is about 14 times greater than the rms shot noise current and about 100 times greater than the rms dark current

03. (a) The entry point and exit point of X-rays on a power pattern taken from a cubic crystal material could not be distinguished. Assuming one of the points to be the exit point, the following S values were obtained:

S values: 311.95 mm, 319.10 mm and 335.05 mm.

The camera radius is 57.3 mm and Molybdenum K_α radiation of wavelength 0.7 \AA was used.

Determine the structure and the lattice parameter of the material.

(20 M)

Sol: Given Data:

X-Ray distraction method

S values

$$S_1 = 311.95 \text{ mm}$$

$$S_2 = 319.10 \text{ mm}$$

$$S_3 = 335.05 \text{ mm}$$

The camera radius = 57.3 mm

Wave length $\lambda = 0.7 \text{ \AA}$

From the Brag's law,

The Brag's angle of each characteristic line on the film follows the ratio, $\frac{S_i}{S_n} = \frac{\theta_i}{\theta_n}$

S_i = distance from the exit to the line of interest = 57.3 mm

S_n = distance from the exit to the entrance ($\theta_n = 90^\circ$)

$$S_n = \frac{2\pi R}{4} = \frac{2\pi \times 57.3}{4} = 89.961$$

$$\theta_1 = \frac{89.961}{311.95} \times 90 = 25.95$$

$$\theta_2 = \frac{89.961}{319.10} \times 90 = 25.37$$

$$\theta_3 = \frac{89.961}{335.05} \times 90 = 24.165$$

$$Q^2 = h^2 + k^2 + l^2$$

$$\lambda = \frac{2a \sin \theta}{\sqrt{h^2 + k^2 + l^2}}$$

$$\lambda^2 = \frac{4a^2 \sin^2 \theta}{Q^2}$$

Example of Trial calculations on assumption of FCC

Q_i	$\sin \theta_i$	$\frac{4 \sin^2 \theta}{\lambda^2} (l)$	Q^2	$h^2 + k^2 + l^2$	hkl	a
25.95	0.437	1.5589	1.142	$\approx 3(1.142)$	111	1.48
25.37	0.428	1.495	1.09	$3(1.09)$	111	1.48
4.16	0.409	1.365	1	$3(1.00)$	111	1.48

$$a = \frac{\lambda \sqrt{h^2 + k^2 + l^2}}{2 \sin \theta} = 1.48 \text{ \AA}$$

Lattice parameter is 1.48 \AA

Structure is FCC

03. (b) (i) Obtain the exact equivalent circuit (per phase) of three-phase induction motor.

(ii) A 6-pole, 3-phase, 50 Hz induction motor takes 50 kW power at 940 rpm. The stator copper loss is 1.4kW, stator core loss is 1.6 kW, and rotor mechanical losses are 1kW.

Find the motor efficiency.

(20 M)


Sol: (i) Equivalent circuit Analysis:

Equivalent circuit

A 3-phase wound rotor induction is very similar in construction to a 3-phase transformer. Thus, the motor has 3 identical primary windings and 3 identical secondary windings-one set for each phase. On account of the perfect symmetry, we can consider a single primary winding and single secondary winding in analysing the behaviour of the motor.

When the motor is at standstill, it acts exactly like a conventional transformer, and so its equivalent circuit is the same as that of a transformer.

Equivalent Circuit of Stator:

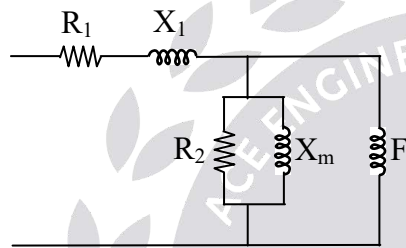


R_1 : Resistance of the stator winding/ph

X_1 : Leakage reactance of the stator/ph

R_n : Iron loss component

X_m : Magnetizing component E_c induced emf stator winding N_w : Effective turns stator

Equivalent circuit of rotor

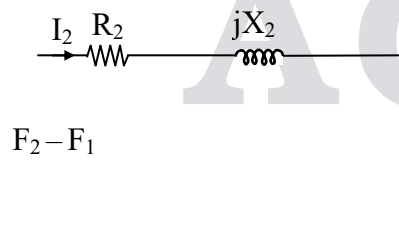

R_2 : Rotor resistance/ph


X_2 : Leakage reactance of the rotor/ph

F_2 : EMF induced in the rotor/ph

I_2 : Rotor current/ph

$F_2 = 8F_{20}$; $X_2 = 5X_{20}$

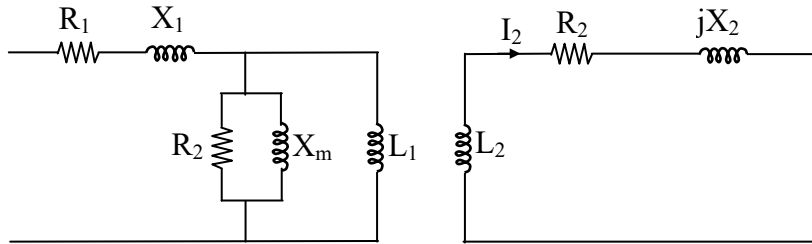Exact equivalent circuit of the induction motor




The secondary side loop is excited by a voltage SF_2 . Which is also at a frequency sf_1 . This is the reason why the rotor

$$I_2 = \frac{SF_{22}}{\sqrt{R_2^2 + (SX_{22})^2}}$$

This expression can be modified as follows (dividing numerator and denominator by S)
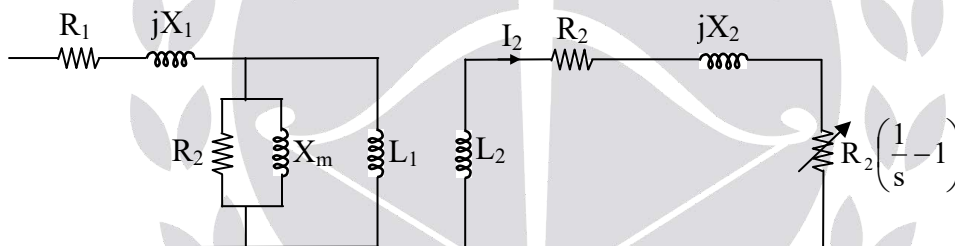
$$\frac{V_1 - V_2}{V_1} \times 100 = 22.86\%$$



Now the resistance $\frac{R_2}{s}$ can be written as $R_2, R_2\left(\frac{1}{s} - 1\right)$. It consists of two points

- (i) The first part R_2 is the rotor resistance itself and represents the rotor copper loss
- (ii) The second part is $R_2\left(\frac{1}{s} - 1\right)$.

$R_2\left(\frac{1}{s} - 1\right)$ is known as the load resistance R_L and is the electrical equivalent at the mechanical load placed on the motor shaft. In other words. The mechanical load on an induction motor can be represented by a non-inductive resistance of the value.

$$R_2\left(\frac{1}{s} - 1\right)$$

Equivalent circuit of the induction motor referred to stator side

As in the case of transformer, in this case also, the secondary values may be transferred to the primary values may be transferred to the primary and vice versa. As before, it should be remembered that when shifting impedance on resistance from secondary to primary, it should be divided by K^2 whereas current should be multiplied by K . The equivalent circuit at an induction motor all values have been referred to stator side is shown in the following figure.

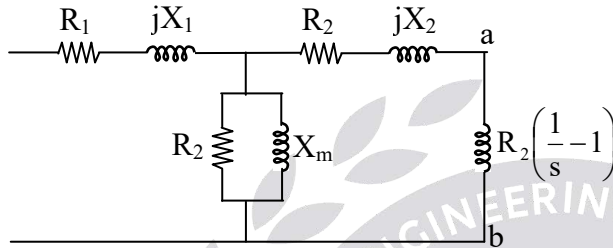


Fig: Equivalent circuit of induction motor referred to stator side with load impedance

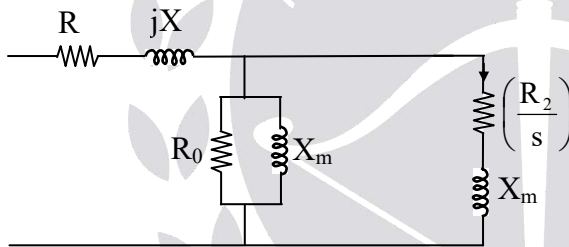


Fig: Equivalent circuit of induction motor referred to stator side with load impedance

This is then the per-phase equivalent circuit of the induction machine, also called as exact equivalent circuit, note that the voltage coming across the magnetizing branch is the applied stator voltage, reduced by the stator impedance drop. Generally the stator impedance drop is any a small fraction of the applied voltage.

From the equivalent circuit, one can see that the dissipation in R represents the stator loss, and dissipation in R_0 , represents the iron loss. Therefore the power absorption indicated by the inner part at the circuit must represent all other means at power consumption the actual mechanical output, friction and windage loss components and the rotor copper loss components. Since the dissipation in R'_2 is rotor copper loss. The power dissipation in $R'_2 (1 - s)/s$ is the sum total of the

remaining in standard terminology, dissipation in $I_2^2 \frac{R'_2}{s}$ is called the air gap power

(ii) Given data:

$$P = 6; f = 50 \text{ Hz, I/P} = 50 \text{ kW}$$

$$N_r = 940 \text{ rpm}$$

$$\text{Stator Copper loss} = 1.4 \text{ kW}$$

$$\text{Stator Iron loss} = 1.6 \text{ kW}$$

$$\text{rotor mechanical loss} = 1 \text{ kW}$$

$$\eta = ?$$

$$N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$S = \frac{N_s - N_r}{N_s} = \frac{1000 - 940}{1000} = 0.06$$

$$\Rightarrow \text{Stator O/P} = \text{Rotor I/P} = \text{Motor I/P} - \text{stator losses}$$

$$= 50 \text{ kW} - (1.4 + 1.6) \text{ kW}$$

$$= 47 \text{ kW}$$

$$\Rightarrow \text{Rotor copper loss} = 5 \times \text{Rotor I/P}$$

$$= 0.006 \times 47 \text{ kW}$$

$$= 2.82 \text{ kW}$$

$$\Rightarrow \text{Gross Rotor O/P} = \text{Rotor I/P} - \text{Rotor loss}$$

$$= 47 \text{ kW} - 2.82 \text{ kW}$$

$$= 44.18 \text{ kW}$$

$$\Rightarrow \text{Net Rotor O/P} = 44.18 \text{ kW} - \text{Rotor mechanical loss}$$

$$= 44.18 \text{ kW} - 1 \text{ kW}$$

$$= 43.18 \text{ kW}$$

$$\therefore \text{Efficiency, } \eta = \frac{\text{O/P}}{\text{I/P}} = \frac{43.18}{50} \times 100 = 86.36\%$$

03. (c) An industrial consumer is operating a 50 kW induction motor at a lagging p.f. of 0.8. The source voltage is 230V rms. In order to obtain lower electrical rates, the customer wishes to raise the p.f. to 0.95 lagging. Specify a suitable solution. (20 M)

Sol: $P_{I/P} = 50 \text{ kW}$

$$\cos \phi_1 = 0.8 \text{ lag} \Rightarrow \tan \phi_1 = 0.75$$

$$V_s = 230 \text{ V}$$

$$\cos \phi_2 = 0.9 \text{ lag} \Rightarrow \tan \phi_2 = 0.48$$

In order to improve the power factor capacitor bank must be connected across the machine.

The VAR supplied by the capacitor bank is


$$\begin{aligned} &= P[\tan \phi_1 - \tan \phi_2] \\ &= 50 \times 10^3 [0.75 - 0.48] \\ &= 13.5 \text{ KVAR} \end{aligned}$$

$$\text{Reactive power, } Q = 13.7 \text{ kVAR} = \frac{V^2}{X_c}$$

$$X_c = \frac{V^2}{Q} = \frac{230 \times 230}{137 \times 10^3} = 3.86 \Omega$$

The capacitor of reactance 3.86Ω is to be connected to increase the p.f from 0.8 to 0.95.

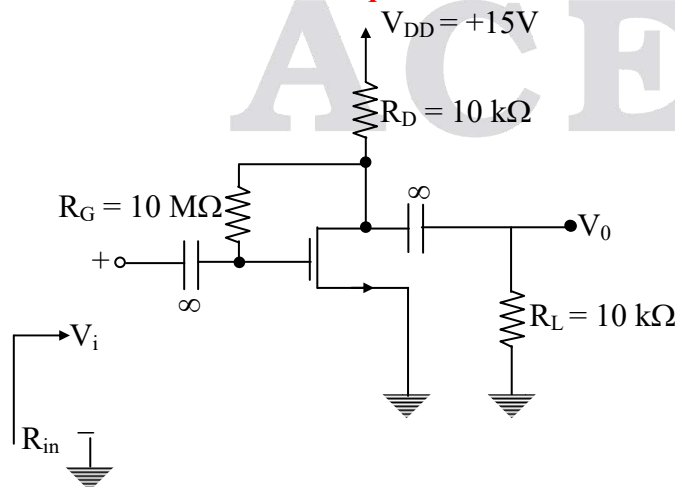- 04. (a)** Figure below shows a discrete MOSFET amplifier utilizing a drain-to-gate resistance R_G . The input signal V_i is coupled to the gate via a large capacitor, and the output signal at the drain is coupled to load resistance R_L via another large capacitor. Analyze this amplifier circuit to determine its small signal voltage gain, its input resistance, and the largest allowable input signal. Assume $V_t = 1.5 \text{ V}$, $K'_n \text{ (W/L)}$ (process transconductance parameter) $= 0.25 \text{ mA/V}^2$, and $V_A = 50 \text{ V}$, where V_A is the intercept on the V_{DS} axis of the $i_D - V_{DS}$ characteristics when extrapolated. Assume that coupling capacitors are sufficiently large so as to act as short circuit at the frequencies of interest.



The effect of channel length modulation on the dc operating point can be neglected (20 M)

Sol:

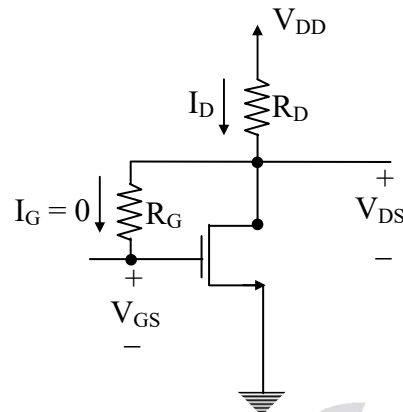


Fig (a): circuit for determining the DC operating point

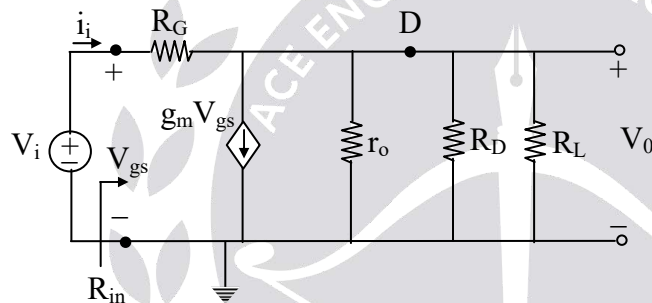


Fig (b)

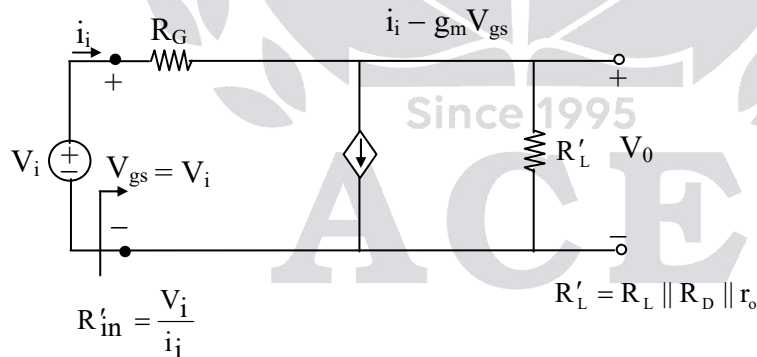


Fig (c) simplified Amplifier Small-signal equivalent circuit

$$V_{GS} = V_{DS} = V_{DD} - I_D R_D$$

with $V_{DS} = V_{GS}$, the NMOS transistor will be operating in saturation. Thus

$$I_D = \frac{1}{2} K_n [V_{GS} - V_T]^2$$

$$I_D = \frac{1}{2} \times 0.25 \times 10^{-3} (V_{DD} - I_D R_D - V_T)^2$$

$$8I_D = [15 - 10 I_D - 1.5]^2$$

$$8I_D = (13.5 - 10 I_D)^2$$

$$\Rightarrow I_D = 1.06 \text{ mA}$$

$$\text{which corresponds to: } V_{GS} = V_{DS} = 15 - 1.06 \text{ mA} \times 10 \text{ k} \\ = 4.4 \text{ V}$$

$$\text{and } V_{OV} = V_{GS} - V_T = 4.4 - 1.5 = 2.9 \text{ V}$$

$$g_m = K_n [V_{GS} - V_T] = K_n \frac{W}{L} \cdot V_{ov} = 0.25 \times 2.9 = 0.725 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{50}{1.06} = 47 \text{ K}\Omega$$

$$R_L^1 = R_L \parallel R_D \parallel r_o = 10 \parallel 10 \parallel 47 = 4.52 \text{ K}$$

$$V_o = (i_i = g_m V_{gs}) R_L^1 \dots \dots \dots (1)$$

$$i_i = \frac{V_{gs} - V_o}{R_G} \dots \dots \dots (2)$$

Substituting equation (2) in (1)

$$A_v = \frac{V_o}{V_i} = \frac{V_o}{V_{gs}} = -g_m R_L^1 \left[\frac{1 - \frac{1}{g_m R_G}}{1 + \frac{R_L^1}{R_G}} \right]$$

$$\text{since } R_G \text{ is very large } g_m R_G \gg 1 \text{ \& } \frac{R_L^1}{R_G} \ll 1$$

Voltage gain (A_v): $A_v \approx g_m R_L$

$$A_v = -0.725 \text{ mA/V} \times 4.52 \text{ k} = -3.3$$

$$\text{Input resistance (} R_{in} \text{): } R_{in} = \frac{R_G}{1 - A_v} = \frac{R_G}{1 + g_m R_L^1} = \frac{10 \text{ M}\Omega}{1 + 3.3} = 2.33 \text{ M}\Omega$$

Largest allowable input signal (\hat{V}_i):

The largest allowable i/p signal (\hat{V}_i) is considered by the need to keep the transistor in saturation at all times, that is

$$V_{DS} \geq V_{GS} - V_t$$

Enforcing this condition with equality at the point V_{GS} is maximum and V_{DS} is minimum, we write

$$V_{DS_{min}} = V_{GS_{max}} - V_t$$

$$V_{DS} - |A_v| \hat{V}_i = V_{GS} + \hat{V}_i - V_t$$

since $V_{DS} = V_{GS}$, we obtain

$$\hat{V}_i = \frac{V_t}{|A_v| + 1}$$

$$\hat{V}_i = \frac{1.5}{3.3 + 1} = 0.35V$$

04.(b)(i) Define nanomaterials and classify nanomaterials on the basis of number of dimensions. What are the different approaches for the preparation of nanomaterials? Discuss any one method of preparation of nanomaterials from each approach. (10 M)


(ii) Explain how dislocation density increases on cold working. (10 M)

Sol:

(i) * At least one dimension of material is in nano-scale that is varying from 1 nm - 100 nm.

Ex: (1). $\left. \begin{array}{l} \text{DNA \& virus} = 40\text{nm} \\ \text{Transistor} = 30\text{nm} \end{array} \right\} \text{Nano material}$

(2).

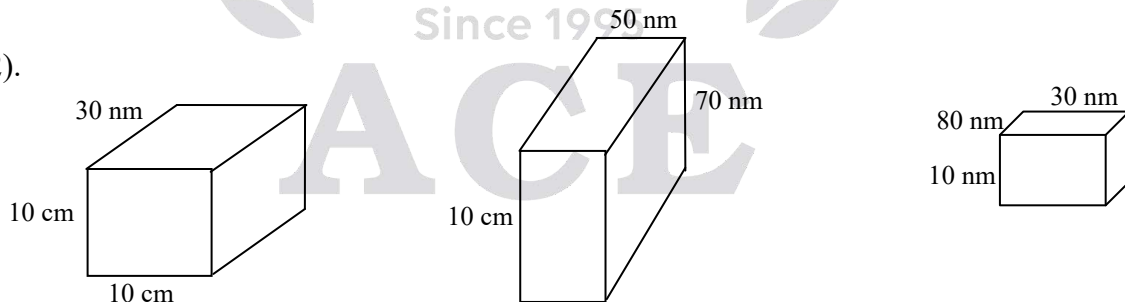


Types of Nano Materials:

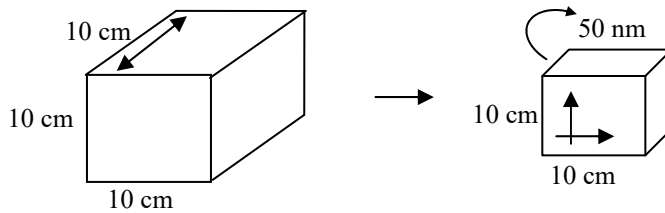1. Quantum Well: (One dimensional nanomaterial) (Two dimensional bulk material)

Reduction of size of bulk material upto the nano range in only one dimension and other two dimensions are in normal range (or) bulk form and hence this material is known as one dimensional nanomaterial.

- * In Quantum well electron flow takes place in two dimension & in nano direction electron flow is restricted.




* Graphene:

Graphene is a carbon made nanomaterial and graphene is a single layer of graphite.

- * In graphene every carbon atom is covalently bonded with three carbon atoms and forms "two single covalent bonds & double covalent bonds". It is also called SP^2 hybridization. To break the double covalent bond requires more energy and hence it is the hardest, strongest, thinnest nanomaterial.

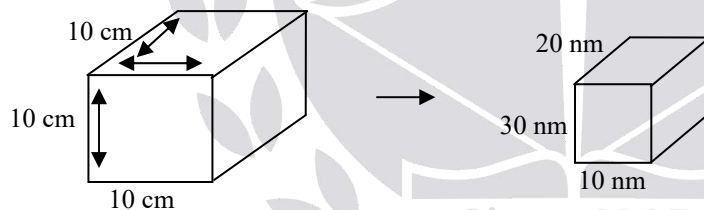2. Quantum Dot: (Three dimensional nanomaterial) (Zero dimensional material)



Ex: 1. Fullerence

2. Dendrimers

3. Quantum dot

- * Reduction of size of bulk material upto the nanorange in all directions.
- * Electron flow is completely restricted in all directions.


* Fullerenes:

Fullerenes are produced by folding single layer of graphite (or) graphene into spherical form.

- * In Fullerenes both hexagon & pentagons present in the shape of soccer ball. In C_{60} fullerence, 12 pentagons & 20 Hexagons are present.




Applications:

1. Drug delivery
2. Gene therapy

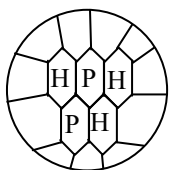


Quantum Dot:

- * It is a smallest size zero dimensional material and the size of quantum dot is less than ($< 10 \text{ nm}$)
- * In quantum dot, the surface atoms are having high energy levels with low wave length and inner core atoms are having low energy and high wave length.
- * By changing wavelength of the atom conduction of electron takes place and hence, these materials are used in electronic industry as semi conductors.
- * The structure of graphene is honey comb structure.
- * The graphene is the highest electrical conductivity material with -ve temperature coefficient of resistivity.

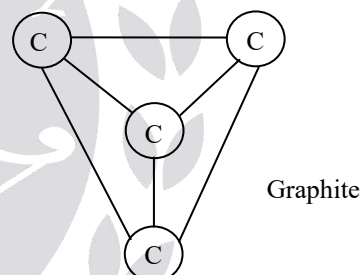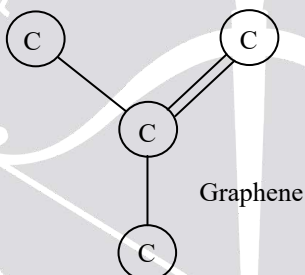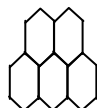

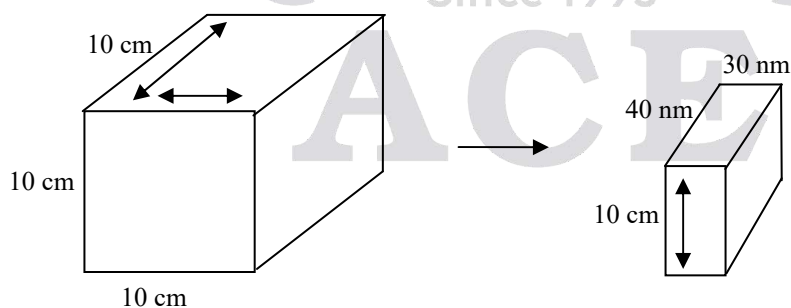3. Quantum Wire: (Two dimensional nanomaterial) (One dimensional material)



- * Reduction of size of bulk material upto nano range in two dimensions and in third dimension the size is in normal range.
- * In Quantum wire electron flow takes place in only one direction


Ex: Carbon Nano Tube, Nano wire, Nano rod, Whiskers.

a) Carbon NanoTube:

- * Carbon Nano Tubes are produced by folding single layer of graphite (or) graphene into a cylindrical form and capped with hemispherical fullerene on both sides of material.
- * The electrical conductivity of Nano material also depends on shape.
- * The electrical conductivity of single wall nanotube different from the multi wall carbon nanotube.

1. Top-Down Approach Method:

Principle: Cutting/Slicing of material

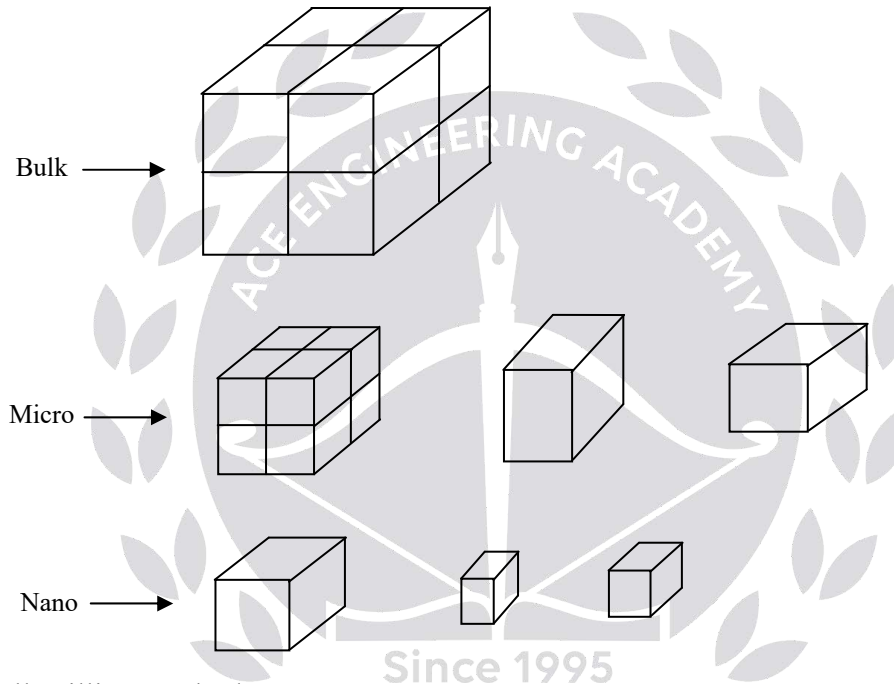

Ex: Ball Milling Method

Advantages:


1. Easy to produce
2. No skilled & low cost

Disadvantages:

1. No uniform size
2. Impurities
3. Crystalline defects generated


Methods:

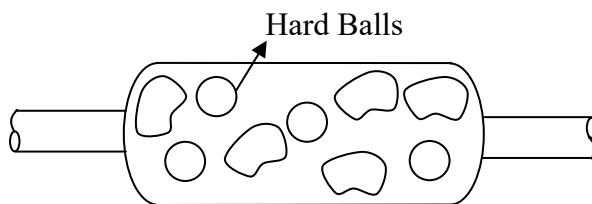1. Ball Milling
2. Lithography method → Photo lithography
→ Electron lithography
3. Laser Ablation method
4. Plasma Arcing




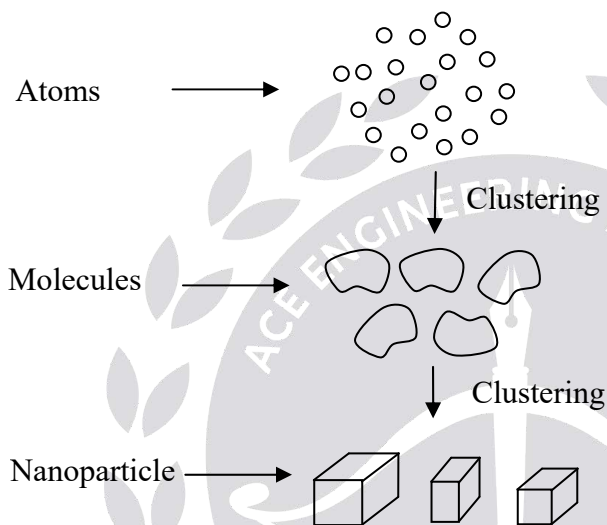2. Bottom up approach Method:

Principle: Clustering of atoms and molecules



Ex: Chemical vapour deposition method:

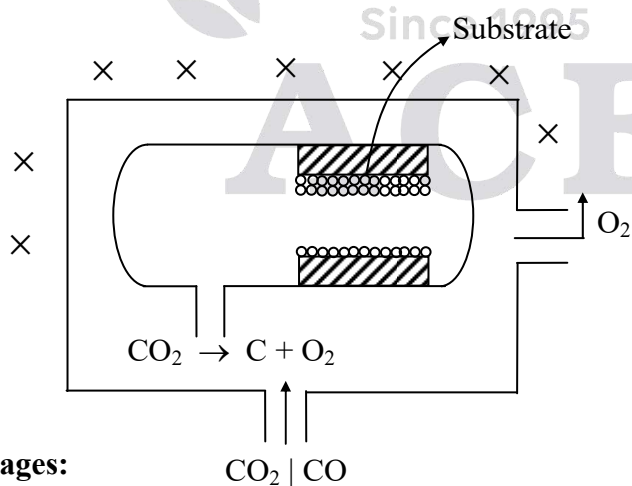

Advantages:

1. Uniform size
2. Purity
3. No defects

Disadvantages:

1. More cost
2. Skilled


Methods:

1. Chemical vapour deposition method
2. Physical vapour deposition method
3. Sol gel Technique
4. Molecular self assembly method

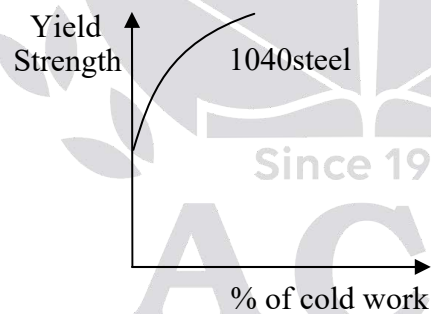- (ii) Cold working is one of the strengthening mechanisms of applying mechanical force and deformed permanently below re-crystallization temperature.

$$\text{Dislocation Density} = \frac{\text{Total dislocation length}}{\text{Volume}}$$

In cold working process, number of point defects, line defects are increased by applying stresses on the material. So dislocation density increased in cold working and there dislocations arrest the dislocation motion so strength and hardness of material increased.



- 04.(c)(i) The Burgers vector of a mixed dislocation line is $\frac{1}{2} [1 \ 1 \ 0]$. The dislocation line lies along the $[1 \ 1 \ 2]$ direction. Find the slip plane on which this dislocation lies. (10 M)
- (ii) Explain, why end centered tetragonal geometry does not exist. (10 M)

Sol: (i) The Burger's vector of a mixed dislocation line is $\frac{1}{2}[1\ 1\ 0]$

Crystallographic direction = $[1\ 1\ 2]$

Consider the slip plane tube to be: $(h\ k\ l)$

From Wies zone law:

$$\vec{b} \rightarrow h + k = 0 \text{ [on } [110] \text{]} \rightarrow (1)$$

$$\vec{t} \rightarrow h + k + 2l = 0 \text{ [on } [112] \text{]} \rightarrow (2)$$

from equation (1)

$$h = -k$$


$$-k + k + 2l = 0$$

$$l = 0$$

$$\text{Slip plane} = (1\ T\ 0)$$

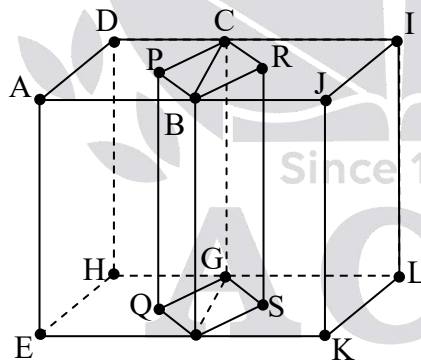(ii) To prove that a Base Centered Tetragonal lattice does not exist:

ABCDEFGH and BJCFKLG are two Base centered tetragonal unit cells joined together (see figure below).



In addition to the corner lattice points, top and bottom bases of the two unit cells have lattice points at their center (P, Q, R and S). Consider the unit cell formed by joining the points B, P, C, R in the top and Q, G, S, F in the bottom face. The side BP, PC, CR and RB are all equal and form the sides of a square. Similarly the sides QG, GS, SF & FQ form the sides of a square. The side surfaces of this cell are identical rectangle.

Hence it is a simple tetragonal lattice.

Hence a base centered tetragonal does not exist.

ONLINE + OFFLINE CLASSES

ENGLISH

ESE | GATE | PSUs – 2022

**Morning / Evening / Weekend Batches
for College Going Students**

📍 DELHI 📍 HYDERABAD 📍 PUNE
📍 VIJAYAWADA 📍 VIZAG 📍 TIRUPATI

COURSE DETAILS

- Classes will be planned & conducted as per Government Regulations - partially online and offline (classroom coaching).
- Payment options Available - Partial Payment/ Full Payment.
- After the payment of II Installment - Get access to complete study material and Online Test Series.
- Recorded version of the online live class will be made available through out the course (with 3 times view).
- Doubt clearing sessions and tests to be conducted regularly.

BATCH DATE


**7th NOVEMBER
2020**



Scan QR Code for more info.


SECTION - B

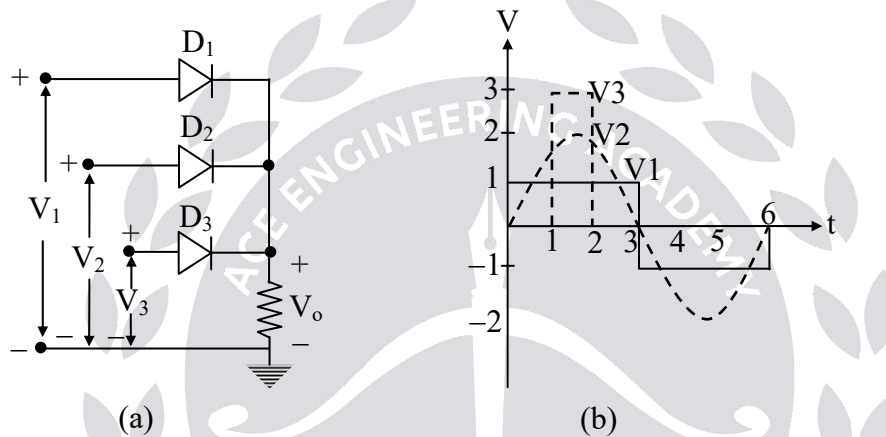- 05.(a)(i) Sketch the circuit of a one-shot using a 555 timer to provide one time period of $20 \mu\text{s}$. If $R_A = 7.5 \text{ k}\Omega$, what value of C is needed? Also sketch the input and output waveforms, when triggered by a 10 kHz clock for $R_A = 5.1 \text{ k}\Omega$ and $C = 5 \text{ nF}$. (6 M)**
- (ii) The logic OR gate can be used to fabricate composite waveforms. Sketch the output V_o of the gate of figure (a) shown below if the three signals as shown below in (b) are impressed on the input terminals. Assume the diodes are ideal. (6 M)**




Sol:


(i)

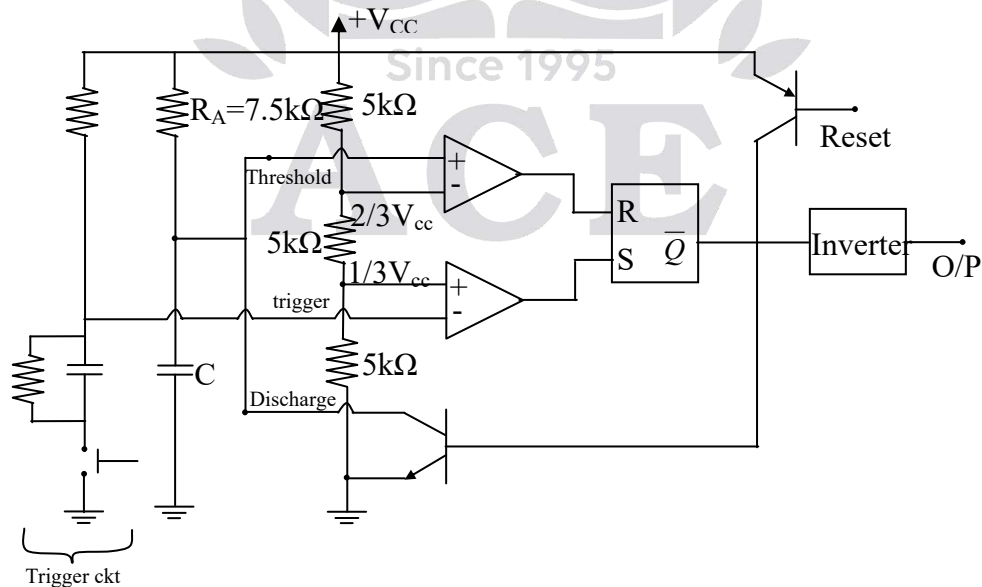

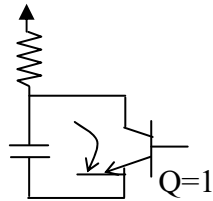Let us assume, capacitor charges from V_{CC} towards $2/3 V_{CC}$



		R	S	\bar{Q}	O/P	
Before trigger	$V_C > 2/3 V_{CC}$	1	0	1	0	Transistor ON Capacitor discharge
	$V_C = 0$	0	0	0	0	(Previous state)
Let us give trigger for a short duration						
After	$V_C = 0$	0	1	0	1	Transistor OFF Capacitor discharge
	$V_C > 1/3 V_{CC}$	0	0	0	0	(Previous state)
	$V_C > 2/3 V_{CC}$	1	0	1	0	Transistor ON Capacitor discharge
$V_C = 0$		0	0	1	0	

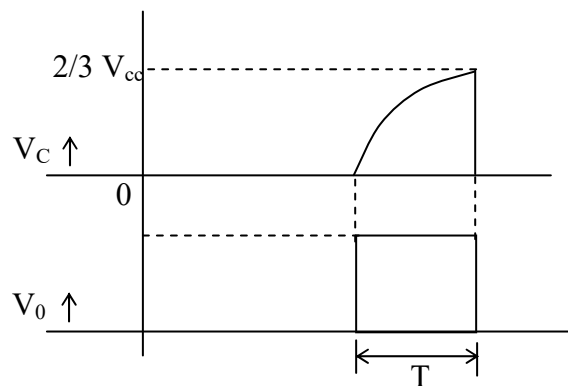

$$V_c(t) = V_{CC} [1 - e^{-t/RC}]$$

$$\text{At } t = T \quad V_c(t) = 2/3 V_{CC}$$



$$2/3 V_{CC} = V_{CC} [1 - e^{-T/RC}]$$

$$T = 1.1RC = 20\mu\text{Sec}$$

$$1.1 \times 7.5k \times C = 20\mu$$

$$C = 2.42 \times 10F$$


$$= 2.42 \text{ nF}$$

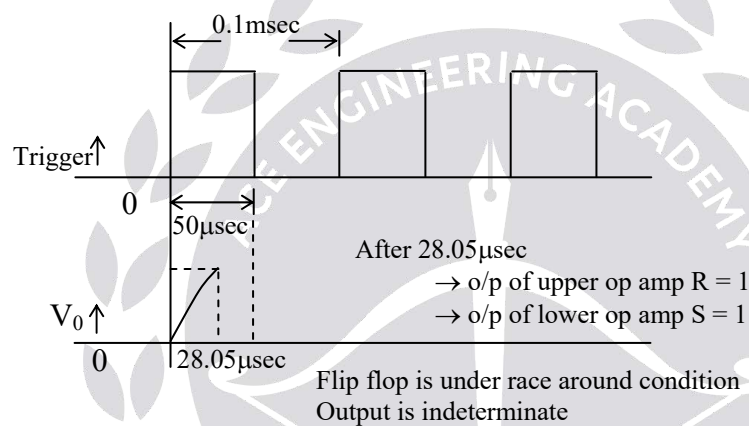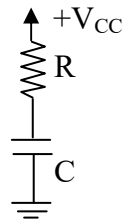



$$R_A = 5.1K$$

$$C = 5nF$$

$$T = 1.1RC = 28.05\mu \text{ Sec}$$

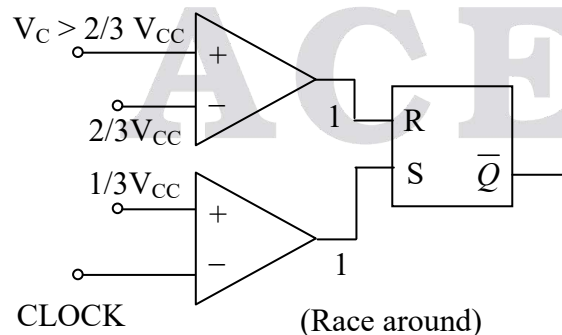


(ii)

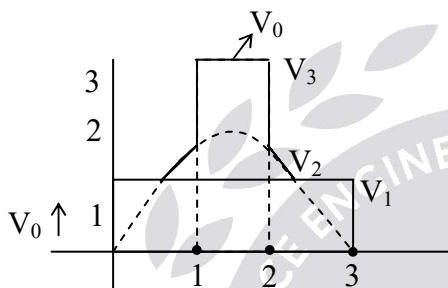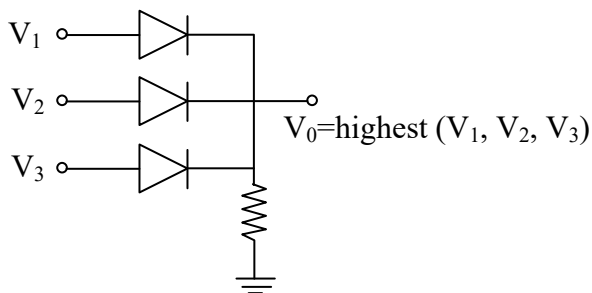


05. (b) A dc voltage of 100 v is suddenly applied in the network shown in the figure. Find the transient currents in both the loops and obtain the transient voltage across the capacitor.

(12 M)

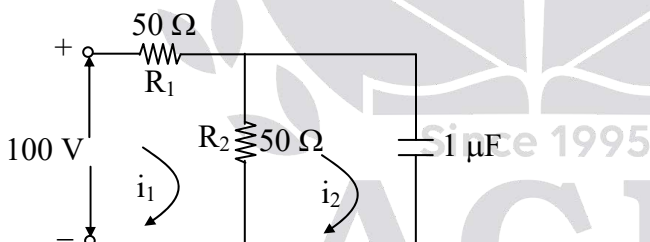


Sol:

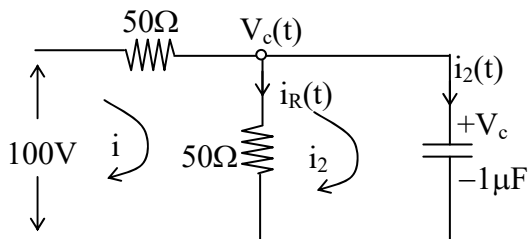

For first order R – C network the voltage across capacitor $V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-t/RC}$

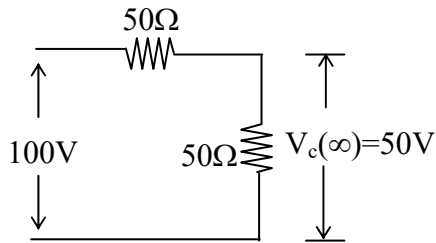$V_c(0) = 0$ $V_c(\infty) = ?$ At $t = \infty$, open circuit



Time constant $\tau = R_{eq} C = (50 // 50) \cdot 1\mu F$

$= 25\mu\text{Sec}$

$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-t/RC}$

$= 50 + (0 - 50)e^{-t/25\mu}$

$V_c(t) = 50(1 - e^{-t/25\mu}) \text{ Volts } t \geq 0$

For $i_2(t) = \frac{cdV_c(t)}{dt}$

$= 1\mu F \left[50 \left(0 - e^{-t/25\mu} \left(\frac{-1}{25\mu} \right) \right) \right]$

$i_2(t) = 2e^{-t/25\mu} \text{ amps } t \geq 0$

$i_R(t) = \frac{V_c}{R} = (i_1 - i_2)$

$\frac{50(1 - e^{-t/25\mu})}{50} = (i_1 - i_2)$

$i_1 = 1 - e^{-t/25\mu} + 2e^{-t/25\mu}$

$i_1(t) = (1 + e^{-t/25\mu}) \text{ amps } t \geq 0$

Voltage across capacitor

$V_c(t) = 50(1 - e^{-4 \times 10^4 t}) \text{ volts}$

Transient loop currents

$i_1(t) = (1 + e^{-4 \times 10^4 t}) \text{ amps } t \geq 0$

$i_2(t) = (2e^{-4 \times 10^4 t}) \text{ amps } t \geq 0$

05. (c) Predict and draw the crystal structure of MgO and compute its theoretical density.

(Give Ionic radius of Mg^{++} ion, $r_{\text{Mg}^{++}} = 0.72 \text{ \AA}$ and ionic radius of O^{--} ion, $r_{\text{O}^{--}} = 1.40 \text{ \AA}$; atomic masses of 'Mg' and 'O' are 24.31 g/mol and 16.00 g/mol, respectively, Avogadro's Number = 6.023×10^{23} g/mol) (12 M)

Sol: Given data:

$$r_{\text{Mg}^{++}} = 0.72 \text{ \AA}$$

$$r_{\text{O}^{--}} = 1.40 \text{ \AA}$$

Atomic masses of ions

$$A_{\text{Mg}} = 24.31 \text{ g/mol}$$

$$A_{\text{O}} = 16 \text{ g/mol}$$

$$\text{Avogadro's number (AN)} = 6.023 \times 10^{23} \text{ g/mol}$$

$$\text{Theoretical Density} = \frac{n_{\text{Mg}} \times A_{\text{Mg}} + n_{\text{O}} \times A_{\text{O}}}{V_{\text{uc}} \times \text{AN}}$$

MgO is a rocksalt structure with effective number of cations and anions = 4

$$n_{\text{Mg}} = 4, n_{\text{O}} = 4$$

Relationship between lattice parameters and ionic radius

$$2(r_{\text{Mg}} + r_{\text{O}}) = a$$

$$a = 2(0.72 + 1.4) = 4.24 \text{ \AA} = 4.25 \times 10^{-10} \text{ m}$$

$$\text{Volume of unit cell} = V_{\text{uc}} = a^3 = 76.22 \times 10^{-30} \text{ m}^3$$

$$\begin{aligned} \text{Theoretical Density} &= \frac{4 \times 24.31 + 4 \times 16}{76.22 \times 10^{-30} \times 6.023 \times 10^{23}} \\ &= 0.3512 \times 10^7 \text{ g/m}^3 \\ &= 0.3512 \times 10^4 \text{ kg/m}^3 \\ &= 3512 \text{ kg/m}^3 \end{aligned}$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

Online Test Series

GATE 2021

ESE 2021

SSC JE

MPSC

KPTCL

UPPSC

TSPSC

KPWD

THE BIG FESTIVAL OFFER

Flat 20% off

From 20th to 26th October

Call: 040-48539866, 4013 6222

Email: testseries@aceenggacademy.com

www.aceenggacademy.com

05. (d) A digital ramp A/D converter has the following values:

Clock frequency, $f_c = 1\text{MHz}$

Threshold voltage, $V_T = 100\ \mu\text{V}$

D/A- $V_{\text{ref.}}$ = 10.24 V and number of input bits = 10

Determine:

(i) Digital/equivalent representation for $V_{\text{in}} = 4.872\text{ V}$

(ii) Resolution of the A/D converters and

(iii) Conversion time required by this digital ramp A/D converter. (12 M)

Sol: A digital ramp ADC has the following values

Clock frequency = 1MHz

Threshold voltage = 100 μV .

DAC_{ref} = 10.24 V, number of input bits = 10.

(i) Digital equivalent representation for $V_{\text{in}} = 4.872\text{ V}$

$$\text{Stepsize} = \frac{V_R}{2^N} = \frac{10.24}{2^{10}} = 0.01\text{ V} = 10\text{mV}$$

Given threshold value $V_T = 100\ \mu\text{V} = 0.1\text{ mV} = 0.0001\text{ V}$

i.e., DAC output ' V_d ' has to reach $4.872\text{V} + 0.1\text{ mV}$ before the comparator switch to 0.


$$\text{Digital output} = \frac{4.872\text{V} + 0.0001\text{V}}{10\text{mV}} = \frac{4.8721\text{V}}{10\text{mV}} = 487.21 = 488$$

i.e., Digital output = $488_{10} = 1\text{E } 8_{16} = 0111101000$.

(ii) ADC resolution = $10\text{mV} + V_T = 10.1\text{ mV}$

(iii) Conversion time = $488 \times 1T = 488 \times 1\mu\text{s} = 488\mu\text{s}$

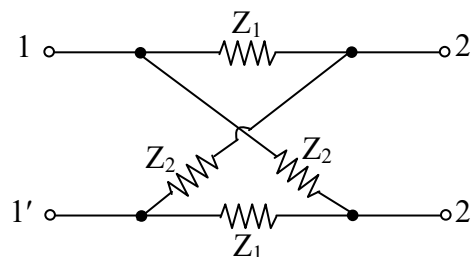05. (e) For the lattice two port network of the figure shown, find the image impedance and the image transfer constant. (12 M)



Sol: The given network is symmetrical and reciprocal network.

The z – parameter of the lattice network can be determined directly

$$z_{11} = z_{22} = \frac{z_1 + z_2}{2} \Omega$$

$$z_{12} = z_{21} = \frac{z_2 - z_1}{2} \Omega$$

The two part lattice network image impedances interms of ABCD parameters.

$$z_{i1} = \sqrt{\frac{AB}{CD}}, z_{i2} = \sqrt{\frac{BD}{AC}}$$

And the image transfer constant

$$\theta = \tan^{-1} \left[\sqrt{\frac{BC}{AD}} \right]$$

The ABCD parameters interms of z – parameter

$$A = \frac{z_{11}}{z_{21}} = D \text{ is } \rightarrow \text{Symmetry}$$

$$B = \frac{\Delta z}{z_{21}}, C = \frac{1}{z_{21}}$$

$$A = \left(\frac{z_2 + z_1}{z_2 - z_1} \right) = D \text{ and } C = \frac{2}{(z_2 - z_1)} \text{ mho}$$

$$B = \frac{\left(\frac{z_2 + z_1}{2} \right)^2 - \left(\frac{z_2 - z_1}{2} \right)^2}{\left(\frac{z_2 - z_1}{2} \right)} = \frac{2z_1 z_2}{(z_2 - z_1)} \Omega$$

Image impedance

$$z_{i1} = \sqrt{\frac{AB}{CD}}$$

$$z_{i1} = \sqrt{\frac{2z_1 z_2 (z_2 - z_1)}{2}} = \sqrt{z_1 z_2} = z_{i2}$$

$$z_{i1} = z_{i2} = \sqrt{z_1 z_2} \Omega$$

$$\text{Image transfer constant } \theta = \tan^{-1} \sqrt{\frac{BC}{AD}}$$

$$\theta = \tan^{-1} \sqrt{\frac{2z_1z_2}{(z_2 - z_1)(z_2 - z_1)} \cdot \frac{2}{\left(\frac{z_2 + z_1}{z_2 - z_1}\right)^2}}$$

$$\theta = \tan^{-1} \left[\frac{2\sqrt{z_1z_2}}{(z_2 + z_1)} \right]$$

06. (a) A first-order thermometer was dipped in a temperature-controlled water bath maintained at 100°C and the following time-temperature readings were obtained:

Time (s)	0	4	8	12	16	20
Temperature (°C)	15	50	70	85	90	95

Estimate the time constant of the thermometer. Determine the steady state error when the thermometer is required to measure the temperature of a liquid which is being heated at a constant rate of 0.1°C/s. (20 M)

Sol: A time constant is equal to time taken to reach 0.632 of the difference between old & new value.

So temperature corresponding to the time constant is

$$T = 0.632 (100 - 15) + 15^\circ\text{C} = 53.72^\circ\text{C} + 15^\circ\text{C} = 68.72^\circ\text{C}$$

From given chart time corresponding to temperature 68.72°C ($\approx 70^\circ\text{C}$) is 8 sec.

So time constant $\tau = 8$ sec

The steady state error (e_{ss}) when the thermometer is required to measure the temperature of a liquid which is being heated at a constant rate 0.1°C/sec is

$$e_{ss} = A\tau$$

Here $A = 0.1^\circ\text{C/sec}$

$$\tau = 8 \text{ sec}$$

$$e_{ss} = 0.1 \times 8 = 0.8^\circ\text{C}$$

- 06. (b) A quartz Piezoelectric Transducer (PZT) has the following specifications: Area = 1cm²; Thickness = 2mm; Young's modulus = 9×10¹⁰ Pa; Charge sensitivity = 2 pC/N; Relative permittivity = 5 and Resistivity = 10¹² Ω-cm. A 10pF capacitor and a 100 MΩ resistor are connected in parallel across the electrodes of the PZT. If a force $F = 0.02 \sin (10^3 t)$ N is applied, determine**
- (i) the peak-to-peak voltage generated across the electrodes and**
- (ii) the maximum change in crystal thickness. (20 M)**

Sol:(i). The rms value of voltage under open circuit is

$$e_o = \frac{F}{A} \times \frac{dt}{\epsilon_o \epsilon_r}$$

The maximum value of voltage

$$e_{o\max} = \sqrt{2} \frac{dt}{\epsilon_o \epsilon_r} \times \frac{F}{A} = \frac{dt}{\epsilon_o \epsilon_r} \times \frac{F_{\max}}{A} \quad (F_{\max} = \sqrt{2} F)$$

Peak to peak value of voltage under open circuit:

$$\begin{aligned} e_{o(pp)} &= 2e_{o\max} = 2 \times \frac{dt}{\epsilon_o \epsilon_r} \times \frac{F_{\max}}{A} \\ &= \frac{2 \times 2 \times 10^{-12} \times 2 \times 10^{-3}}{8.85 \times 10^{-12} \times 5} \times \frac{0.02}{10^{-4}} = 0.0036 \times 10 \\ &= 36 \text{ mV} \end{aligned}$$

The leakage resistance of crystal

$$R_p = \frac{\rho t}{A} = \frac{10^{12} \times 10^{-2} \times 2 \times 10^{-3}}{10^{-4}} = 2 \times 10^{11} \Omega$$

Load resistance $R_L = 100 \text{ M}\Omega$

Conclusion is $R_p \gg R_L$ so that we can neglect R_p

$$\begin{aligned} C_p &= \frac{\epsilon_o \epsilon_r A}{t} \\ &= \frac{8.85 \times 10^{-12} \times 5 \times 10^{-4}}{2 \times 10^{-3}} \\ &= 22.125 \times 10^{-13} \end{aligned}$$

$$C_p = 2.21 \times 10^{-12} \text{ F}$$

The peak to peak output voltage under load conditions is

$$C_p = \frac{2dF_{\max}t}{\epsilon_o\epsilon_rA} \left[\frac{\omega C_p R_L}{\sqrt{1 + \omega^2 (C_p + C_L)^2 R_L^2}} \right]$$

$$e_{OPP} = \frac{2 \times 2 \times 10^{-12} \times 0.02 \times 2 \times 10^{-3}}{8.85 \times 10^{-12} \times 5 \times 10^{-4}} \times \left[\frac{1000 \times 2.21 \times 10^{-12} \times 100 \times 10^6}{\sqrt{1 + [1000 \times (2.21 + 10) \times 10^{-12} \times 100 \times 10^6]^2}} \right]$$

$$= 36.15 \times 10^{-3} \times 0.634 \times 2.21 \times 10^{-1}$$

$$= 50.65 \times 10^{-4}$$

$$e_{OPP} = 5.065 \text{ mV}$$

(ii) The maximum value of change in thickness is

$$\Delta t = \frac{F_{\max}t}{YA} = \frac{0.02 \times 2 \times 10^{-3}}{9 \times 10^{10} \times 10^{-4}} = 0.0044 \times 10^{-9}$$

$$(\Delta t)_{pp} = 4.4 \times 10^{-12} \text{ m}$$



06.(c)(i) Generate the logic function given in the table below using IC74151 8-to-1 MUX.

(10M)

Inputs			Output
C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


(ii) Show the states of the five-bit register shown below using waveforms, for the specified data input and clock signal. Assume the registers to be initially cleared (all 0s). How long will it take to shift an 8-bit number into a shift register if the clock is set to 10 MHz?

(10 M)

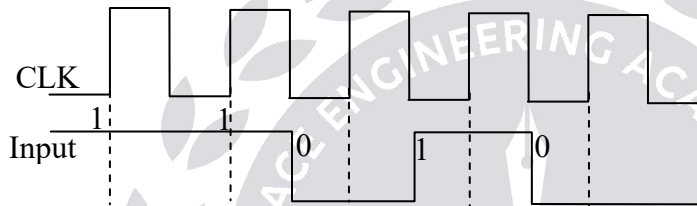
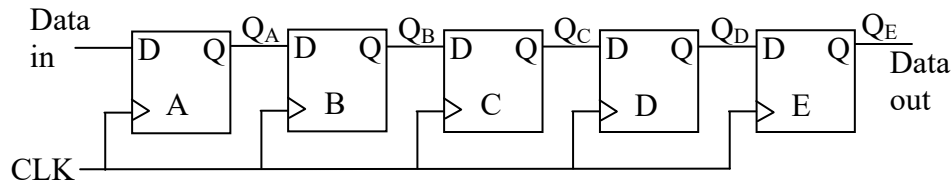


Sol:

(i)

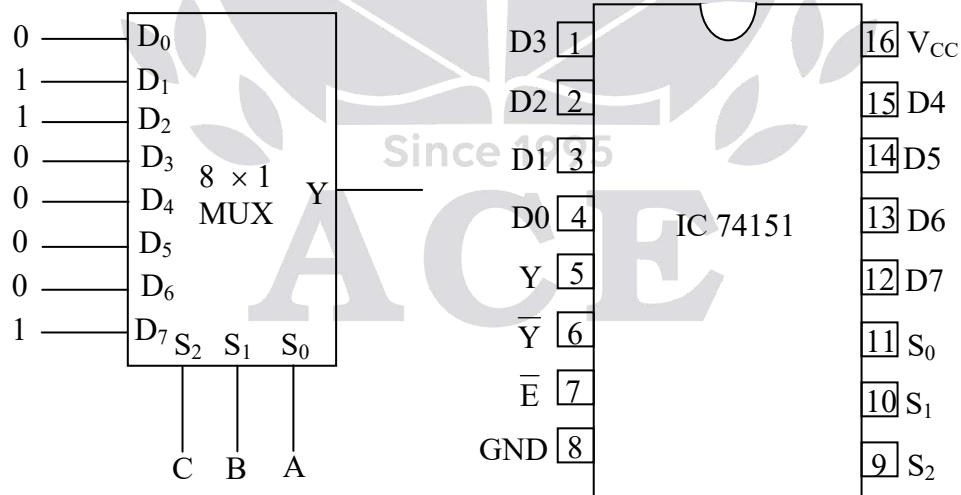

(ii)

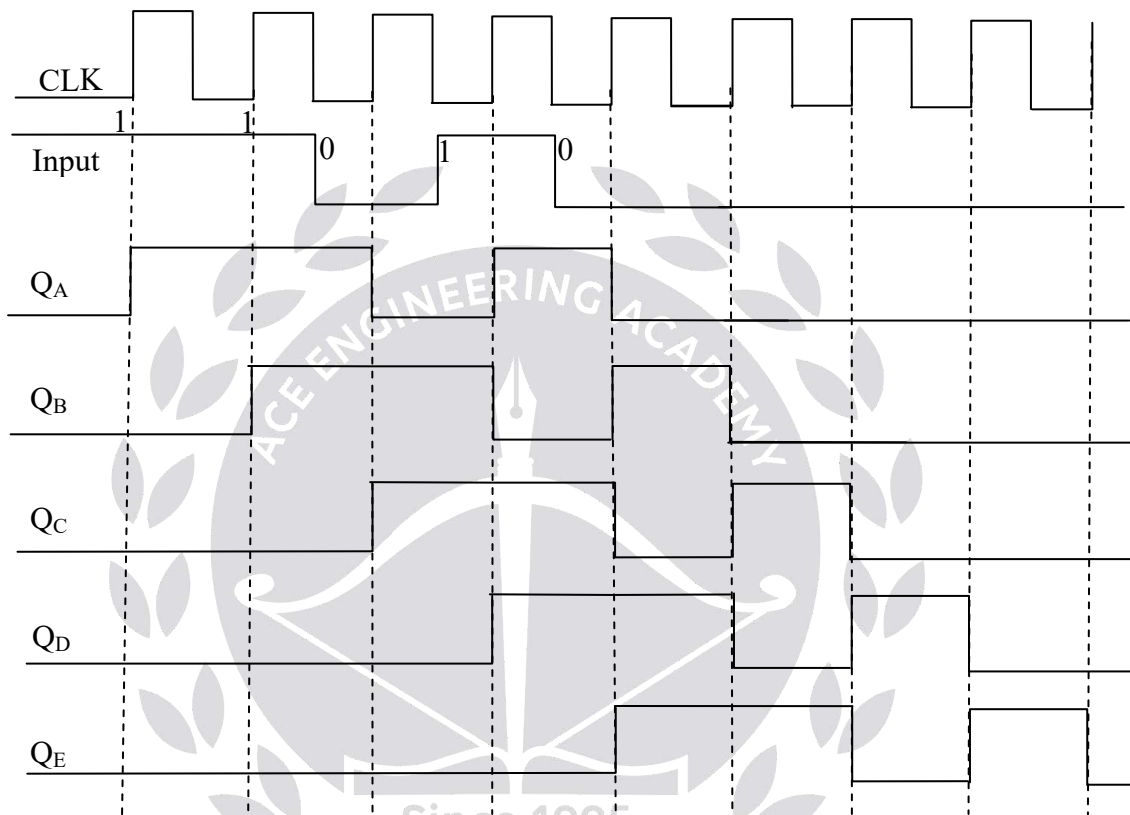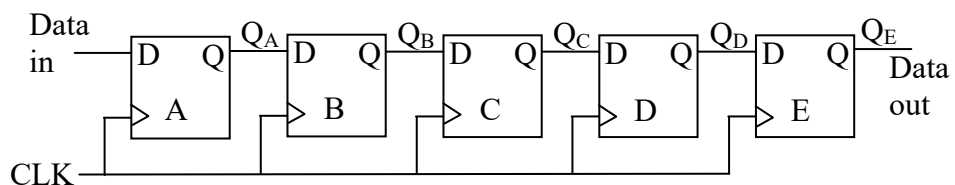


$$f = 10 \text{ MHz}$$

$$T = \frac{1}{10 \text{ MHz}} = 0.1 \mu\text{s}$$


The number of clock cycles to read 8-bit data $8T$ and the time is $= 8 \times 0.1 \mu\text{s} = 0.8 \mu\text{s}$.

07. (a) Find $V_o(t)$ in the circuit shown in the figure. Assume $V_o(0) = 5V$.


(20 M)

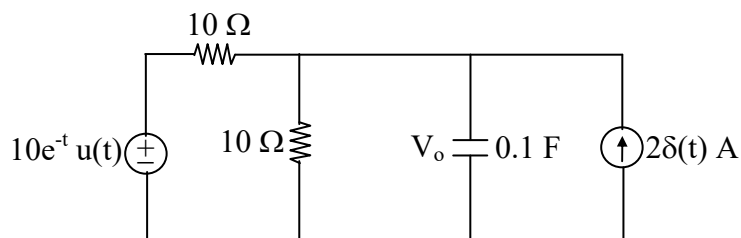

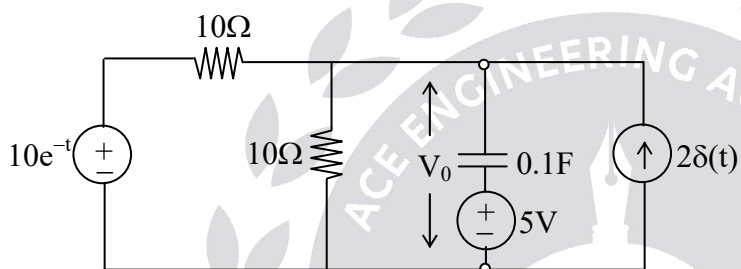Sol: For $t > 0$, $10e^{-t}u(t) = 10e^{-t}$



t – domain

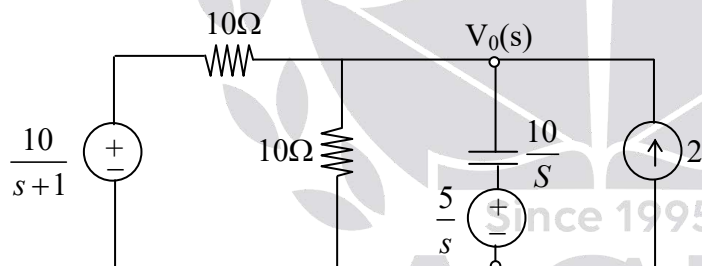

S – domain

By KCL at $V_o(s)$

$$\frac{V_o(s) - \frac{10}{s+1}}{10} + \frac{V_o(s)}{10} + \frac{V_o(s) - \frac{5}{s}}{\frac{10}{s}} = 2$$

$$V_o(s) \left[\frac{1}{10} + \frac{1}{10} + \frac{s}{10} \right] = \frac{1}{s+1} + \frac{1}{2} + 2$$

$$V_o(s) \left[\frac{s+2}{10} \right] = \frac{1}{s+1} + \frac{5}{2}$$

$$V_0(s) \left[\frac{s+2}{10} \right] = \frac{2+5(s+1)}{(s+1)^2}$$

$$V_0(s) \left[\frac{s+2}{10} \right] = \frac{5s+7}{2(s+1)}$$

$$V_0(s) = \frac{25s+35}{(s+1)(s+2)} = \frac{25s+25+10}{(s+1)(s+2)}$$

$$V_0(s) = \frac{25}{(s+2)} + \frac{10}{(s+1)(s+2)}$$

$$V_0(s) = \frac{25}{s+2} + \frac{10}{s+1} - \frac{10}{s+2} = \frac{15}{s+2} + \frac{10}{s+1}$$

By I.L.T

$$V_0(t) = (15e^{-2t} + 10e^{-t}) \text{ Volts } t \geq 0$$

07.(b)(i) In a cathode-ray tube, the electron beam is displaced vertically by a magnetic field of flux density $2 \times 10^{-4} \text{ Wb/m}^2$. The length of the magnetic field along the tube axis is same as that of electrostatic deflection plates. The final anode voltage is 1kV. Determine the voltage which should be applied to the y-deflection plates 10mm apart to return the spot back to the centre of the screen. Take

Mass of electron = $9.107 \times 10^{-31} \text{ kg}$ and

Charge on electron = $1.6 \times 10^{-19} \text{ C}$. (10 M)

(ii) A moving coil milli-ammeter having a resistance of 20Ω gives full scale deflection when a current of 10 mA is passed through it. Describe how this instrument can be used for measurement of current up to 1 A and voltage up to 5V. (10 M)

Sol:

(i) The magnetostatic deflection,

$$D = \frac{lBL}{\sqrt{V_a}} \sqrt{\frac{q}{2m}} \quad \text{----- (1)}$$

The electrostatic deflection,

$$D = \frac{LV_d}{2dV_a} \quad \text{----- (2)}$$

For returning the beam back to the centre, the electrostatic deflection & the magnetostatic deflection must be equal from (1) & (2)

$$\frac{IBL}{\sqrt{V_a}} \sqrt{\frac{q}{2m}} = \frac{LV_d}{2dV_a}$$

$$V_d = dB \times \sqrt{\frac{2V_a q}{m}}$$

Here $d = 10 \text{ mm}$

$$B = 2 \times 10^{-4} \text{ Wb/m}^2$$

$$V_a = 1 \text{ kV}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$m = 9.107 \times 10^{-31} \text{ kg}$$

$$V_d = 10 \times 10^{-3} \times 2 \times 10^{-4} \times \sqrt{\frac{2 \times 1000 \times 1.6 \times 10^{-19}}{9.107 \times 10^{-31}}}$$

$$= 2 \times 10^{-6} \sqrt{351.4 \times 10^{12}}$$

$$V_d = 37.49 \text{ V}$$


(ii)



$$I_m = 10 \text{ mA}; R_m = 20 \Omega$$


$$V_m = I_m R_m = 200 \text{ mV}$$

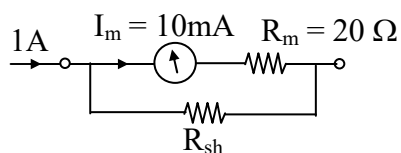(1) By using this basic instrument, we can measure current 1 A by connecting shunt resistance



$$R_{sh} = \frac{R_m}{\left(\frac{I}{I_m} - 1\right)} = \frac{20}{\left(\frac{1}{10\text{mA}} - 1\right)} = \frac{20}{99} = 0.2\Omega$$

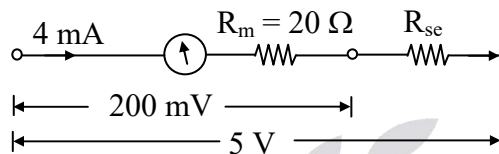(2) We can measure voltage 5V, by connecting a series resistance.



$$R_{se} = R_m \left(\frac{V}{V_m} - 1 \right) = 20 \left(\frac{5}{200\text{mV}} - 1 \right) = 480\Omega$$


07.(c)(i) Draw the oriented graph of a network with fundamental cutset matrix as shown below:

(10 M)

Twigs				Links		
1	2	3	4	5	6	7
1	0	0	0	-1	0	0
0	1	0	0	1	0	1
0	0	1	0	0	1	1
0	0	0	1	0	1	0

(ii) For the network shown in the figure, draw the oriented graph, obtain the cutset matrix and find the number of links.

(10 M)

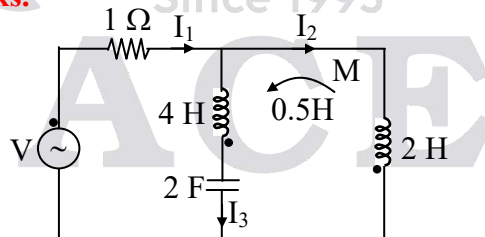

Sol:

(i) The fundamental cutset matrix



$$[C] = \begin{matrix} & \begin{matrix} \text{Twigs} & & & & \text{Links} & & & \end{matrix} \\ \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 & 0 \end{bmatrix} & \end{matrix}_{(n-1) \times b}$$

$$[C] = [V_t]_t [C]_l]_{(n-1) \times b}$$


$(n - 1) = 4 \Rightarrow n = 5 = \text{number of nodes in the graph}$

The tree for the given cut set

The oriented graphs

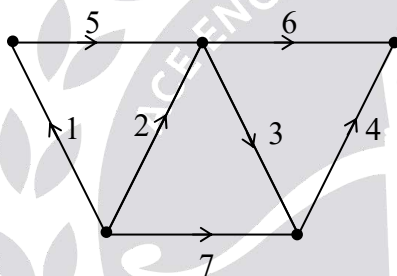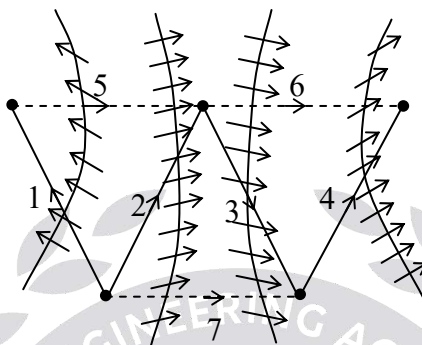

(ii)

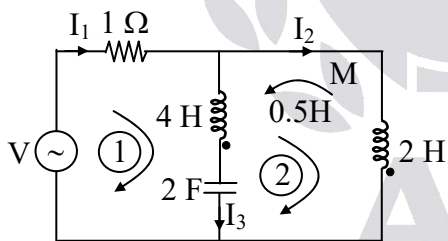


By KVL for (1)


$$V = I_1 + 4 \frac{dI_3}{dt} + 0.5 \frac{dI_2}{dt} + \frac{1}{2} \int I_3 dt \quad \text{---- (1)}$$

$$2 \frac{dI_2}{dt} + 0.5 \frac{dI_3}{dt} = \frac{1}{2} \int I_3 dt + 4 \frac{dI_3}{dt} + 0.5 \frac{dI_2}{dt} \quad \text{---- (2)}$$

The circuit can be drawn without dots

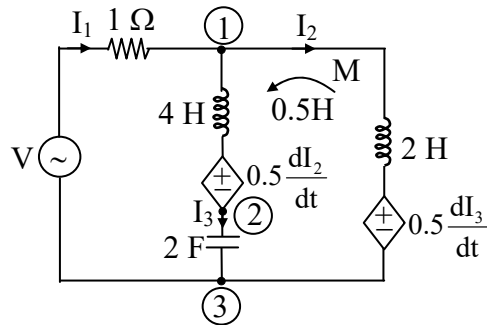


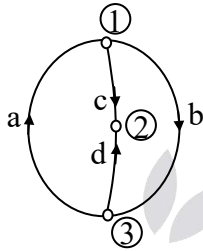The oriented graph, of the given coupled circuit



Cut-set matrix (Q):

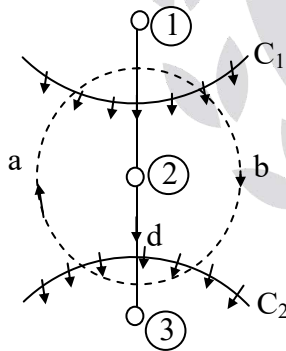For cut-set matrix select any one of the tree form the obtained oriented graph



Number of twigs = $N - 1 = 2$

Number of links = 2

Cut-set matrix (Q):

Cut-set	Links		Twigs	
	a	b	c	d
$[Q] =$	-1	+1	+1	0
		-1	+1	0

(n-1) × b
2 × 4

$$[Q] = [[C_l] [V_t]]_{2 \times 4}$$

ACE POSTAL COACHING

POSTAL COACHING

ESE / GATE / PSUs









PSCs

ACE Engineering Academy, the leading institute for GATE, ESE and PSUs offers postal coaching (Distance learning programme) for engineering students.



Scan QR Code for more info.

ACE PUBLICATIONS

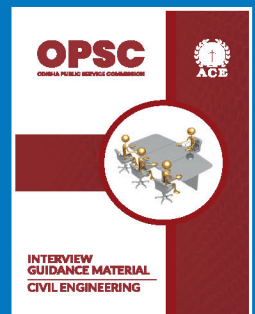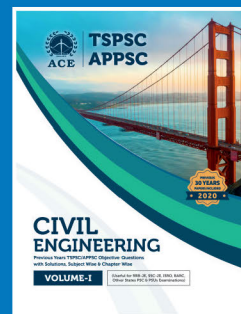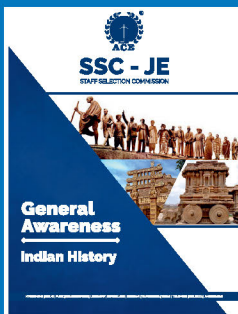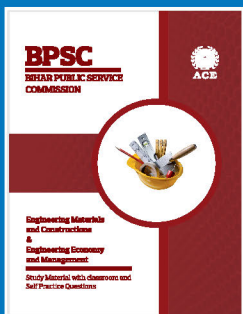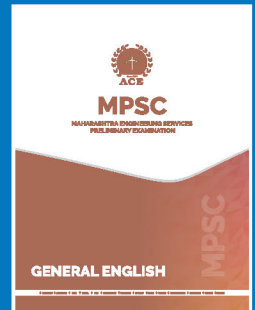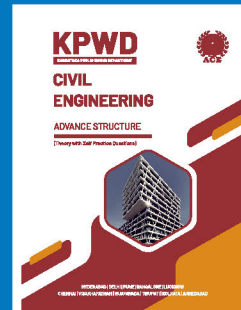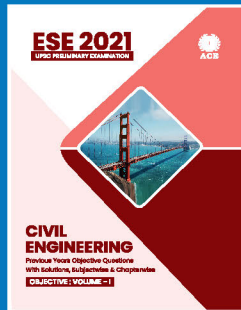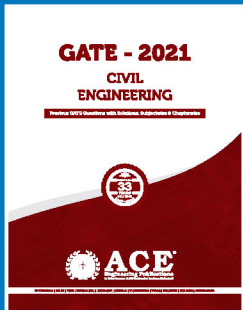

www.aceengineeringpublications.com

amazon

Flipkart

Limited Period Offer **UPTO 25% DISCOUNT***

*on MRP Prices


Call: 040-40044403, 040-23234420 | Email: acepostalcoaching@gmail.com | www.aceenggacademy.com

08.(a)(i) For the network in the figure shown below, determine

- I. r_e
- II. Z_i
- III. Z_o
- IV. A_v


Repeat parts II, III and IV with $r_o = 20k\Omega$ and compare results.

(10 M)

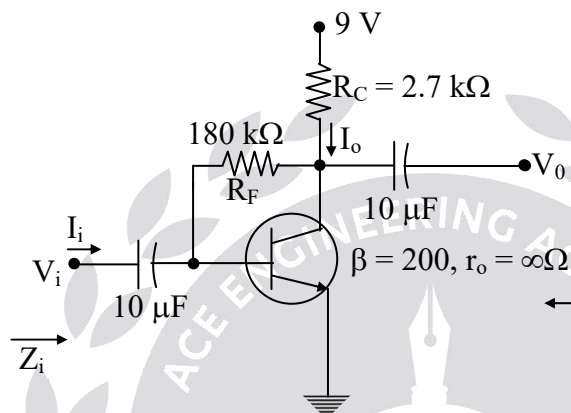


(ii) Draw the equivalent circuit (hybrid- π high frequency model) of the CB amplifier shown below. Find an expression for the high-frequency voltage-gain ratio. Also describe the high-frequency behaviour of this amplifier.

(10 M)

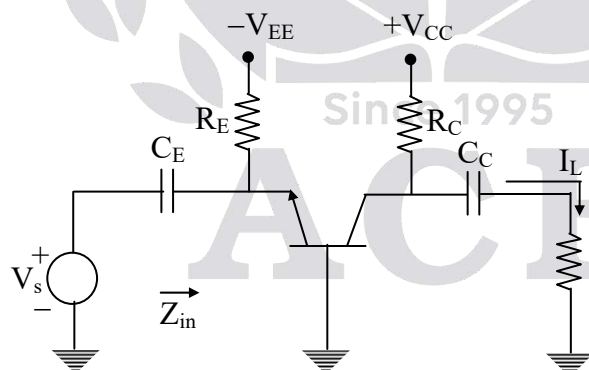

Sol:

(i) DC Analysis

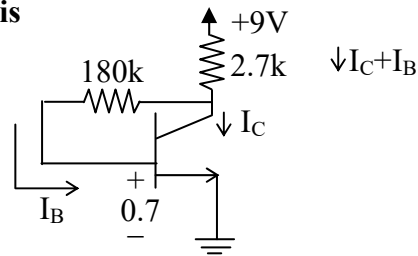

KVL

$$9 = (I_C + I_B)2.7k + I_B(180k) + 0.7$$

$$I_C = \frac{9 - 0.7}{2.7K + \frac{182.7k}{\beta}} = \frac{9 - 0.7}{2.7k + \frac{182.7k}{200}}$$

$$= 2.29694 \text{ mA}$$

$$1. r_e = \frac{\alpha}{g_m}$$

$$\text{where } g_m = \frac{I_C}{V_t}$$

$$= \frac{2.2969\text{m}}{26\text{m}}$$

$$= 0.08834 \text{ (A/V)}$$

$$= \left(\frac{\beta}{\beta + 1} \right) \frac{1}{g_m}$$



$$= \frac{[200/201]}{0.08834}$$

$$= 11.263\Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{200}{0.08834}$$

$$= 2.2638k$$

AC Analysis

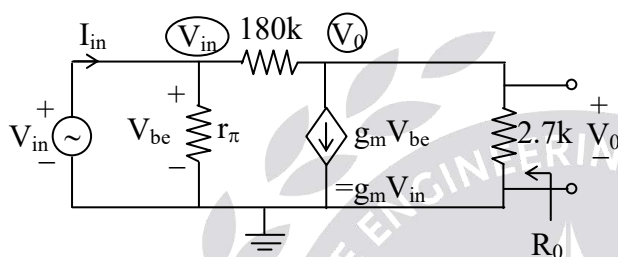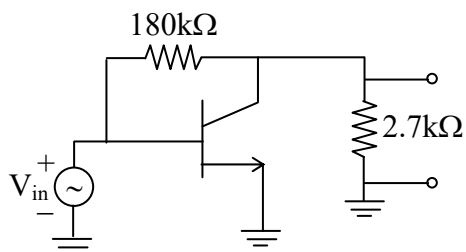

$$\text{KCL} \quad \frac{V_0 - V_{in}}{180K} + g_m V_{in} + \frac{V_0}{2.7K} = 0$$

$$V_0 \left[\frac{1}{180K} + \frac{1}{2.7K} \right] = V_{in} \left[\frac{1}{180K} - g_m \right]$$

$$2. \quad A_v = \frac{V_0}{V_{in}} = \left[\frac{\frac{1}{180K} - g_m}{\frac{1}{180K} + \frac{1}{2.7K}} \right]$$

$$= -234.988$$

$$= -235 \text{ (V/V)}$$

$$3. \quad R_i = \frac{V_{in}}{I_{in}}$$

$$I_{in} = \frac{V_{in}}{r_{\pi}} + \frac{V_{in} - V_0}{180k}$$

$$I_{in} = V_{in} \left[\frac{1}{r_{\pi}} + \frac{1}{180K} - \frac{A_v}{180K} \right]$$

$$\frac{V_{in}}{I_{in}} = \frac{1}{\frac{1}{r_{\pi}} + \frac{1}{180k} + \frac{235}{180k}}$$

$$= \frac{1}{\frac{1}{2.2638K} + \frac{1}{180K} + \frac{235}{180K}}$$

$$= 0.57k\Omega = 570\Omega$$

(or)

$$R_{in} = r_{\pi} \left[\frac{180K}{10A_v} \right] = 2.2638k \parallel \frac{180k}{236}$$


$$= 0.57k\Omega$$

Output resistance

$$R_o \Big|_{V_{in}=0} = R_o \Big|_{V_{be}=0} = R_o \Big|_{g_m v_{be}=0}$$

$$= 2.7k\Omega$$

With $r_o = 20k\Omega$

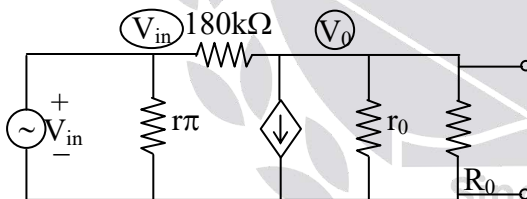

$$2. A_v = \frac{V_o}{V_m} = \frac{\frac{1}{180k} - g_m}{\frac{1}{180k} + \frac{1}{2.7k} + \frac{1}{20k}}$$

$$= (2.347k)[-0.08833]$$


$$= -207.33$$

$$3. R_{in} = r_{\pi} \parallel \frac{180K}{1 + A_v} = 2.2638K \parallel \frac{180K}{1 + 207.3}$$


$$= 2.2638k \parallel 0.864k$$

$$= 625.33\Omega$$


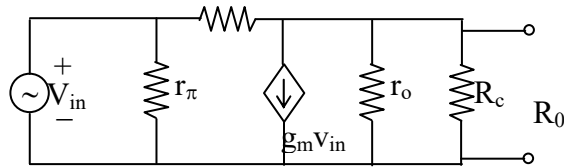
$$3. R_0 = r_o \parallel R_C = 20k \parallel 2.7k = 2.37k\Omega$$



(ii) AC equivalent

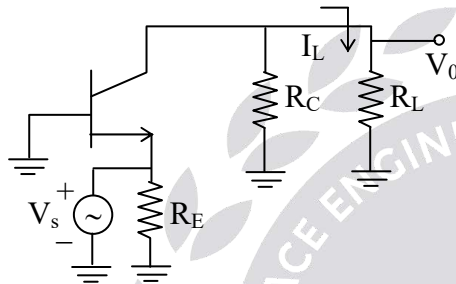


HF model of BJT

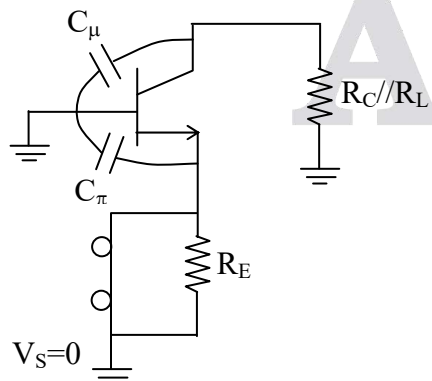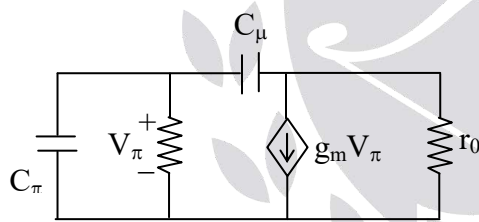

$$\text{Input pole } (\omega_{p1}) = \frac{1}{T_2} = \frac{1}{C\pi[R_{eq}]}$$

$$= \frac{1}{(\pi(0))} = \infty$$
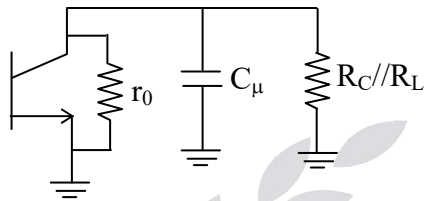
$$\text{Out put pole } (\omega_{p2}) = \frac{1}{T_2} = \frac{1}{C\mu[RC \parallel R_L]r_o}$$




$$\text{Bandwidth } (\omega_{3db}) = \frac{1}{\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}}$$

$$= \frac{1}{\frac{1}{\omega_{p1}}}$$

$$\omega_{3db} = \omega_{p1}$$

Neglect early effect $r_o = \infty$

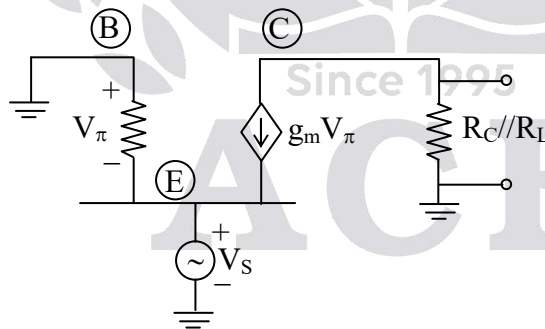

KVL


$$V_{\pi} + V_s = 0 \rightarrow V_s = -V_{\pi}$$

$$V_0 = -g_m V_{\pi} [R_C \parallel R_L]$$

$$= -g_m (-V_s) [R_C \parallel R_L]$$

$$\frac{V_0}{V_s} = g_m [R_C \parallel R_L]$$

Frequency response

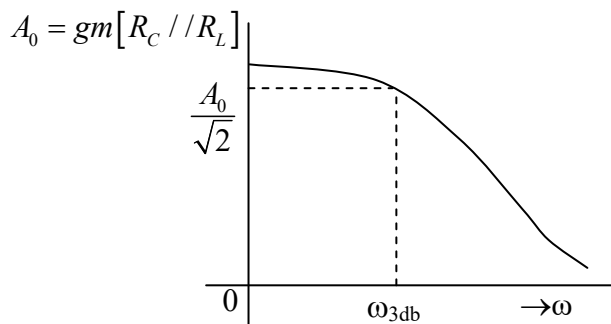

08. (b) Find (z) and (g) of a two-port network if $[T] = \begin{bmatrix} 10 & 1.5\Omega \\ 2s & 4 \end{bmatrix}$ (20 M)

Sol: Two - port network ABCD parameters

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = [T] = \begin{bmatrix} 10 & 1.5\Omega \\ 2s & 4 \end{bmatrix} \text{ (given)}$$

For ABCD parameters

$$\left. \begin{aligned} V_1 &= 10V_2 - 1.5I_2 \\ I_1 &= 2V_2 - 4I_2 \end{aligned} \right\} \dots\dots\dots (1)$$

For Z – parameters $V_1 = z_{11}I_1 + z_{12}I_2$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

From (1)

$$I_1 = 2V_2 - 4I_2$$

$$V_2 = \frac{(I_1 + 4I_2)}{2} = 0.5I_1 + 2I_2$$

$$V_1 = 10(0.5I_1 + 2I_2) - 1.5I_2$$

$$V_1 = 5I_1 + 18.5I_2$$

$$V_2 = 0.5I_1 + 2I_2$$

Z – parameter matrix

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} 5 & 18.5 \\ 0.5 & 2 \end{bmatrix}$$

In g – parameters

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

From (1)

$$I_1 = 2V_2 - 4I_2$$

$$I_1 = 2 \left[\frac{\overbrace{V_2}^{V_1 + 1.5I_2}}{10} \right] - 4I_2$$

$$I_1 = 0.2V_1 - 3.7I_2$$


$$V_2 = 0.1V_1 + 0.15I_2$$

g – parameters

$$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} = \begin{bmatrix} 0.2 & -3.7 \\ 0.1 & 0.15 \end{bmatrix}$$

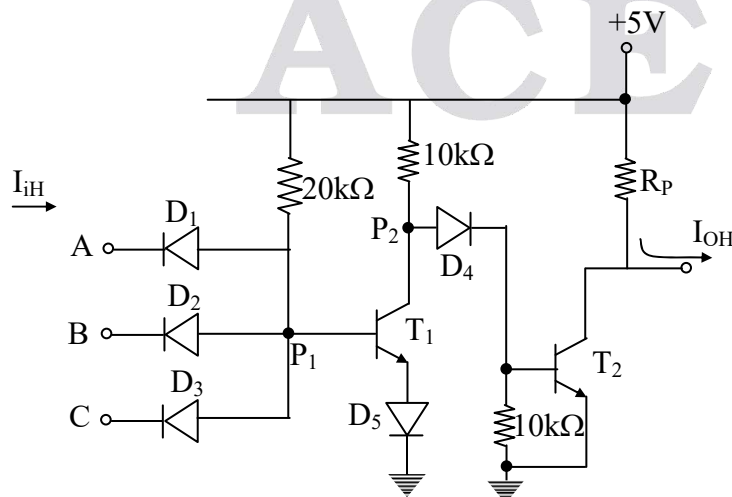
08. (c) For the circuit shown below, identify the logic function performed by it. Also determine the high level fan-out, if R_P (pull-up resistor) = 10 k Ω . Compute the maximum value of R_P for a fan-out of 5. Assume that input diode has a leakage current of 100 μ A.

Given: $V_T = 0.7$ V, V_D (forward voltage drop) = 0.8 V, $V_{BE(\text{cut-in})} = 0.5$ V, $V_{CE(\text{sat})} = 0.2$ V. Transistor leakage current is negligible. (20 M)



Sol:

(i)

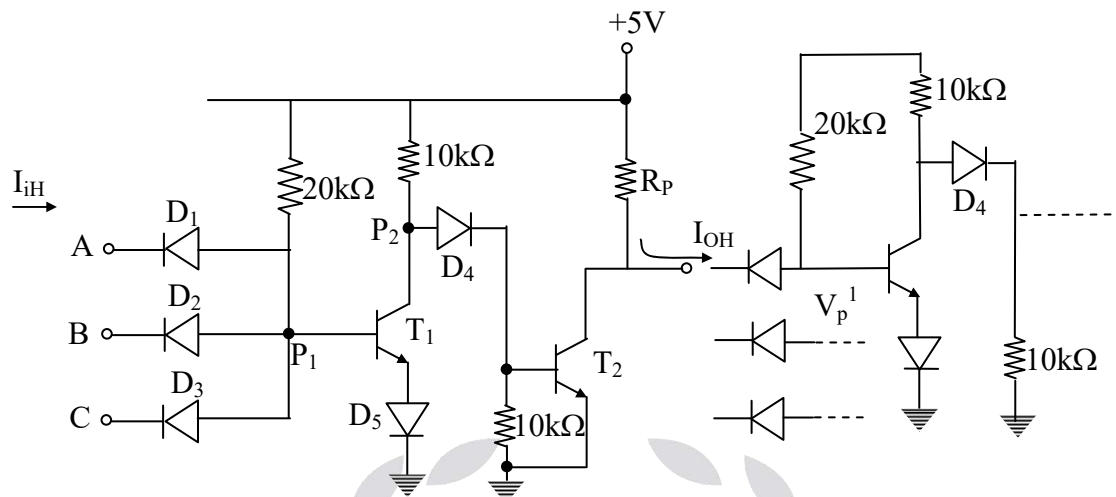

Given $R_p = 10k\Omega$

$$\text{Fan out} = \frac{I_{OH}}{I_{IH}}$$

Let $A = B = C = 1 \Rightarrow V_o = 1$ and $V_p' = 0.7 + 0.8 = 1.5V$

$$\text{Thus, } I_{OH} = \frac{V_{CC} - V'_{P1}}{R_p} = \frac{5 - 1.5}{10k} = 3.5 \times 10^{-4} = 350 \mu A$$

and $I_{IH} = 100 \mu A$

$$\text{So Fanout} = I_{OH} = \frac{I_{OH}}{I_{IH}} = \frac{350}{100} = 3.5$$

i.e., Fanout = 3

(ii) Find R_p if Fanout is 5

$$\text{Fanout} = \frac{I_{OH}}{I_{IH}} \Rightarrow 5 = \frac{I_{OH}}{100 \times 10^{-6}} \Rightarrow I_{OH} = 500 \times 10^{-6}$$

$$\frac{5 - (0.8 + 0.5)}{R_p} = 500$$

$$R_p = \frac{5-1.3}{500 \times 10^{-6}} = 7.4 \text{ k}\Omega$$

$$R_p = 7.4k\Omega$$

(iii) It is an AND gate

If any one input is 0 \rightarrow then $V_o = 0$

If all inputs are 1 \rightarrow then $V_o = 1$

GATEway to Government JOBS...



COURSE DETAILS

- Experienced and erudite faculty from ACE Hyd.
- Focussed and relevant
- Structured online practice tests (FREE)
- Scheduled live doubt clearing sessions (FREE)
- Access lectures from anywhere.
- Recorded version of the online live class will be made available throughout the course (with 3 times view).
- 5 to 6 Hours live online lectures per day (5-7 Days a week)

KPSC / KPWD

Starts from **22nd OCT. 2020**

SSC JE (GS)

Starts from **14th OCT. 2020**

APPSC / TSPSC

Starts from **22nd OCT. 2020**

MPSC

OPSC

BPSC