




X **DEEP**
LEARN

GATE | PSUs

COMPUTER SCIENCE & INFORMATION TECHNOLOGY

Digital Logic

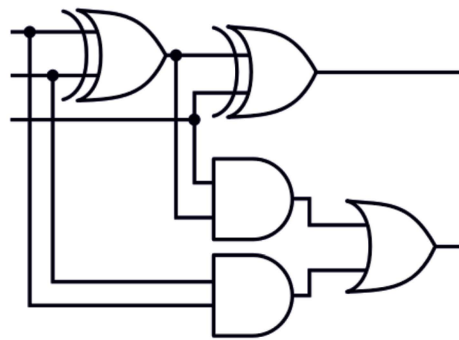(Text Book : Theory with worked out Examples
and Practice Questions)



Hyderabad | Delhi | Pune | Bhubaneswar | Lucknow | Bengaluru | Chennai
Vijayawada | Vizag | Tirupati | Ahmedabad | Kolkata

1. Number Systems

01. Ans: (d)

Sol: $135_x + 144_x = 323_x$

$$(1 \times x^2 + 3 \times x^1 + 5 \times x^0) + (1 \times x^2 + 4 \times x^1 + 4 \times x^0) = 3x^2 + 2x^1 + 3x^0$$

$$\Rightarrow x^2 + 3x + 5 + x^2 + 4x + 4 = 3x^2 + 2x + 3$$

$$x^2 - 5x - 6 = 0$$

$$(x-6)(x+1) = 0 \quad (\text{Base cannot be negative})$$

Hence $x = 6$.

(OR)

As per the given number x must be greater than 5. Let us consider $x = 6$

$$(135)_6 = (59)_{10}$$

$$(144)_6 = (64)_{10}$$

$$(323)_6 = (123)_{10}$$

$$(59)_{10} + (64)_{10} = (123)_{10}$$

So that $x = 6$

02. Ans: (a)

Sol: 8-bit representation of

$$+127_{10} = 01111111_{(2)}$$

1's complement representation of

$$-127 = 10000000.$$

2's complement representation of

$$-127 = 10000001.$$

No. of 1's in 2's complement of

$$-127 = m = 2$$

No. of 1's in 1's complement of

$$-127 = n = 1$$

$$\therefore m : n = 2 : 1$$

03. Ans: (c)

Sol: In 2's complement representation the sign bit can be extended towards left any number of times without changing the value. In given number the sign bit is ' X_3 ', hence it can be extended left any number of times.

04. Ans: (c)

Sol: Binary representation of $+(539)_{10}$:

2	539	
2	269	-1
2	134	-1
2	67	-0
2	33	-1
2	16	-1
2	8	-0
2	4	-0
2	2	-0
1		-0

$$(+539)_{10} = (1000011011)_2$$

$$= (00100\ 0011011)_2$$

$$2\text{'s complement} \rightarrow 110111100101$$

$$\text{Hexadecimal equivalent} \rightarrow (DE5)_H$$

05. Ans: 5

Sol: Symbols used in this equation are 0, 1, 2, 3.

Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0)(x+3x^0+x^{-1})$$

$$3x^2 + x + 2 = (2x) \left(x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0 \Rightarrow x(x-5) = 0$$

$$x = 0 \text{ (or) } x = 5$$

x must be $x > 3$, So $x = 5$

06. Ans: 3 possible solutions

Sol: $123_5 = x8_y$

$$1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0 = x.y^1 + 8 \times y^0$$

$$25 + 10 + 3 = xy + 8$$

$$\therefore xy = 30$$

Possible solutions:

i. $x = 1, y = 30$

ii. $x = 2, y = 15$

iii. $x = 3, y = 10$

3 possible solutions

07. Ans: 1

Sol: The range (or) distinct values

For 2's complement $\Rightarrow -(2^{n-1})$ to $+(2^{n-1}-1)$

For sign magnitude

$$\Rightarrow -(2^{n-1}-1) \text{ to } +(2^{n-1}-1)$$

Let $n = 2 \Rightarrow$ in 2's complement

$$-(2^{2-1}) \text{ to } +(2^{2-1}-1)$$

$$-2 \text{ to } +1 \Rightarrow -2, -1, 0, +1 \Rightarrow x = 4$$

$n = 2$ in sign magnitude $\Rightarrow -1 \text{ to } +1 \Rightarrow y = 3$

$$x - y = 1$$

08. Ans: (c)

09. Ans: (b)

10. Ans: (b) & (d)

Sol: [B 9 F. A E]₁₆

$$= [1011 \ 1001 \ 1111. \ 1010 \ 1110]_2$$

$$= [5637. \ 534]_8$$

2. Logic Gates & Boolean Algebra

01. Ans: (b)

Sol: Truth table of XOR

A	B	o/p
0	0	0
0	1	1
1	0	1
1	1	0

Stage 1:

Given one i/p = 1 Always.

1	X	o/p	
1	0	1	$= \bar{X}$
1	1	0	$= \bar{X}$

For First XOR gate o/p = $\bar{X}$

Stage 2:

$\bar{X}$	X	o/p
0	1	1
1	0	1

For second XOR gate o/p = 1.

Similarly for third XOR gate o/p = $\bar{X}$ & for fourth o/p = 1

For Even number of XOR gates o/p = 1

For 20 XOR gates cascaded o/p = 1.

02. Ans: 1

Sol: $f = [\overline{D} + \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{A}\overline{C}\overline{D} + \overline{A}\overline{C}\overline{D}]$

Let $x = \overline{D} + \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{A}\overline{C}\overline{D} + \overline{A}\overline{C}\overline{D}$ [then $f = \overline{x}$]

Simplify $x \Rightarrow$

$x = \overline{D} + \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{C}\overline{D}[\underbrace{A + \overline{A}}_1]$

$x = \overline{D} + \overline{C}\overline{D} + \overline{A}\overline{B} + \overline{A}\overline{C}$

$x = [\overline{D} + (\overline{D})\overline{C}] + \overline{A}\overline{B} + \overline{A}\overline{C} [\because p + \overline{p}q = p + q]$

$x = \overline{D} + \overline{C} + \overline{A}\overline{B}$

$x = \overline{D} + [\overline{C} + (\overline{C})\overline{A}] + \overline{A}\overline{B}$

$x = \overline{D} + \overline{C} + \overline{A} + \overline{A}\overline{B}$

$x = \overline{D} + \overline{C} + [\overline{A} + (\overline{A})\overline{B}]$

$x = \overline{D} + \overline{C} + \overline{A} + \overline{B}$

$x = \overline{A} + \overline{B} + \overline{C} + \overline{D}$

$f = \overline{x} = \overline{\overline{A} + \overline{B} + \overline{C} + \overline{D}} = \overline{\overline{A}}.\overline{\overline{B}}.\overline{\overline{C}}.\overline{\overline{D}} = A.B.C.D$

Number of minterms are "one" Ans: 1.

03. Ans: (c)

Sol: $f = f_1 f_2 + f_3$

04. Ans: (c)

Sol: Let $x_1 = x_2 = x_3 = x_4$

For all cases options a, b, d not satisfy.

05. Ans: (d)

06. Ans: (b)

07. Ans: (b)

08. Ans: (c)

09. Ans: (a) & (d)

Sol: $(x + y)(x + \overline{y}) + \overline{x} + x\overline{y}$

using Distributive Law

$F = (x + y.\overline{y}) + (\overline{x} + \overline{y}) = x + xy = x$

10. Ans: (b) & (c)

Sol: Let $B \odot B$ [Here no. of XOR=1 $\Rightarrow$ odd]

$\overline{B}\overline{B} + B.B = \overline{B} + B = 1$


Let $B \odot B \odot B$ [Here no. of XOR=2 $\Rightarrow$ even]

$= 1 \odot B = \overline{1}.B + 1.B = B =$ remain same as given variable

3. K-Maps

01. Ans: (b)


Sol:

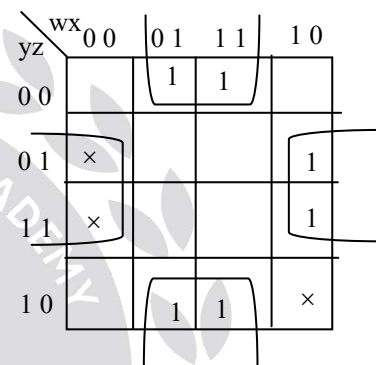

$f = \overline{x}z + x\overline{z}$

02. Ans: (b)


Sol:

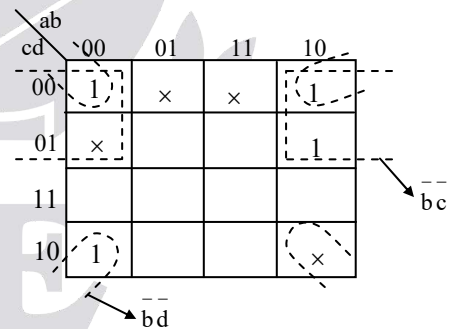

$f = \overline{b}\overline{d} + \overline{b}\overline{c}$

03.

Sol:

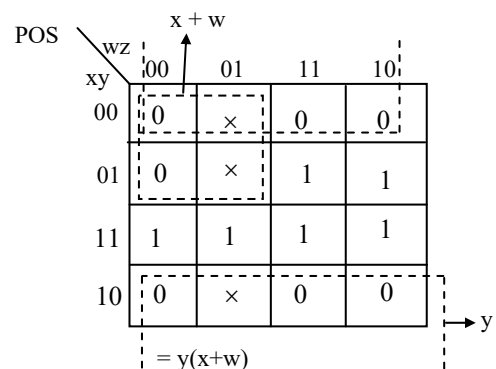

DEEP
LEARN

SOP

xy \ wz	00	01	11	10
00	0	x	0	0
01	0	x	1	1
11	1	1	1	1
10	0	x	0	0

= xy + yw

SOP: $xy + yw$

POS: $y(x + w)$

04. Ans: (a)

Sol: For n-variable Boolean expression,

Maximum number of minterms = 2^n

Maximum number of implicants = 2^n

Maximum number of

Essential prime implicants = $\frac{2^n}{2}$
= 2^{n-1}

05. Ans: (c)

Sol:

AB \ C	00	01	11	10
0	1	1	0	0
1	0	1	1	0

$$F(A, B, C) = \overline{A}\overline{C} + BC$$

06. Ans: 3

Sol: $\overline{w}\overline{z} + \overline{w}xy + \overline{x}yz$

yz \ wx	00	01	11	10
00	1			1
01	1	1		1
11				
10				1

07. Ans: (c) 08. Ans: (a) 09. Ans: (a)

10. Ans: (b) & (d)

Sol: Given $f = \Pi M [1, 3, 4, 6, 9, 11, 12, 14] + d [2, 7, 8, 13]$

AB \ CD	00	01	11	10
00		0	0	X
01	0		X	0
11	0	X		0
10	X	0	0	

$\downarrow$

$[B + \overline{D}]$

$f_{pos} = [B + \overline{D}][\overline{B} + D]$ hence option (d) is correct

$$f_{sop} = \frac{B \cdot \overline{B}}{0} + BD + \overline{B} \overline{D} + \frac{\overline{D} \cdot D}{0} = BD + \overline{B} \overline{D}$$

So option (c) is wrong

$f_{sop} = B \cdot D + \overline{B} \overline{D}$
 $f_{pos} [B + \overline{D}][\overline{B} + D]$ Both cases variables A, C are absent so Independent of "2" variables

Hence option (b) is correct

4. Combinational Circuits

01. Ans: (d)

Sol: Let the output of first MUX is "F₁"

$$F_1 = AI_0 + \overline{A}I_1$$

Where A is selection line, I₀, I₁ = MUX Inputs

$$F_1 = \overline{S}_1 \cdot W + S_1 \cdot \overline{W} = S_1 \oplus W$$

Output of second MUX is

$$F = \overline{A} \cdot I_0 + A \cdot I_1$$

$$F = \overline{S}_2 \cdot F_1 + S_2 \cdot \overline{F}_1$$

$$F = S_2 \oplus F_1$$


$$\text{But } F_1 = S_1 \oplus W$$

$$F = S_2 \oplus S_1 \oplus W$$

$$\text{i.e., } F = W \oplus S_1 \oplus S_2$$

02. Ans: 19.2

Sol: F.A using H.A

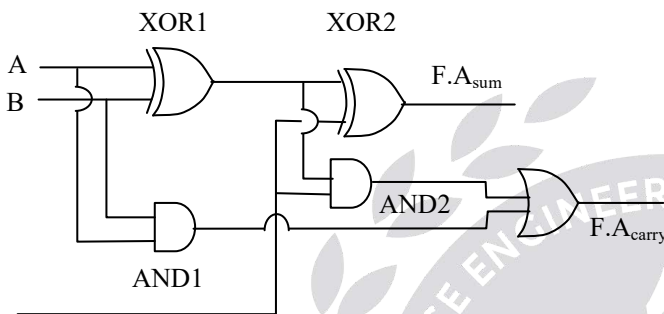

$$t_{\text{AND}} = 1.2\mu\text{s} ; t_{\text{OR}} = 1.2\mu\text{s}$$

$$\text{XOR} = 2 \times 1.2 = 2.4 \mu\text{sec}$$

$$\begin{aligned} \text{Time for addition} &= \text{XOR1} + \text{XOR2} = 2.4 + 2.4 \\ &= 4.8\mu\text{sec} \end{aligned}$$

$$\begin{aligned} \text{Time for carry} &= \text{XOR1} + \text{AND2} + \text{OR} \\ &= 2.4 + 1.2 + 1.2 = 4.8\mu\text{sec} \end{aligned}$$

for n-bit total time required

$$= (n-1) t_c + \text{Max}[t_c, t_s]$$

$\Rightarrow$ for 4 bit

$$(4-1) \times 4.8 + \text{Max}[4.8, 4.8]$$

$$3 \times 4.8 + 4.8 = 19.2\mu\text{sec}$$

03. Ans: 6

Sol: $T = 0 \rightarrow \text{NOR} \rightarrow \text{MUX 1} \rightarrow \text{MUX 2}$

$$2\text{ns} \quad 1.5\text{ns} \quad 1.5\text{ns}$$

$$\text{Delay} = 2\text{ns} + 1.5\text{ns} + 1.5\text{ns} = 5\text{ns}$$

$T = 1 \rightarrow \text{NOT} \rightarrow \text{MUX 1} \rightarrow \text{NOR} \rightarrow \text{MUX 2}$

$$1\text{ns} \quad 1.5\text{ns} \quad 2\text{ns} \quad 1.5\text{ns}$$

$$\text{Delay} = 1\text{ns} + 1.5\text{ns} + 2\text{ns} + 1.5\text{ns} = 6\text{ns}$$

Hence, the maximum delay of the circuit is 6ns

04. Ans: 195

Sol: Given $t_{\text{carry}} = 12\text{ns}$

$$t_{\text{sum}} = 15\text{ns}$$

$$n = 16 \text{ bit}$$

$$\text{Time required} = (16-1) \times 12 + \text{max}(15, 12)$$

$$15 \times 12 + 15 = 195\text{nsec.}$$

05. Ans: (b), (c) & (d)

Sol: For “n” bit number addition we require

= “n” F.A (or) 1 H.A, (n-1) F.A (or)

(2n-1) H.A, (n-1) OR Gates

06. Ans: (a) & (c)

Sol: Output $= Y = \sum m(0, 1, 2, 6) + \bar{C}$

BC A				
	00	01	11	10
0	1	1		1
1				1

$$Y = \bar{A} \bar{B} + B \bar{C} + \bar{C}$$

$$= \bar{A} \bar{B} + \bar{C}[B + 1] = \bar{C} + \bar{A} \bar{B} \rightarrow \text{Option (c)}$$

$$\begin{aligned} \Rightarrow Y &= \bar{C} + \bar{A} \bar{B} = (\bar{C} + \bar{A})(\bar{C} + \bar{B}) = (\bar{A} + \bar{C})(\bar{B} + \bar{C}) \\ &\rightarrow \text{Option (d)} \end{aligned}$$

5. Sequential Circuits

01. Ans: 4

Sol: In the given first loop of states, zero has repeated 3 times. So, minimum 4 number of Flip-flops are needed.

02. Ans: (b)
Sol:

CLK	Serial in= $B \oplus C \oplus D$	A B C D
0		1 0 1 0
1	1 $\longrightarrow$	1 1 0 1
2	0 $\longrightarrow$	0 1 1 0
3	0 $\longrightarrow$	0 0 1 1
4	0 $\longrightarrow$	0 0 0 1
5	1 $\longrightarrow$	1 0 0 0
6	0 $\longrightarrow$	0 1 0 0
7	1 $\longrightarrow$	1 0 1 0

03. Ans: (b)
Sol:

J	K	Q_n	$\bar{Q}_n$	$T = (J + Q_n) (K + \bar{Q}_n)$	Q_{n+1}
0	0	0	1	$0.1 = 0$	0 } Q_n
0	0	1	0	$1.0 = 0$	
0	1	0	1	$0.1 = 0$	0 } 0
0	1	1	0	$1.1 = 1$	
1	0	0	1	$1.1 = 1$	1 } 1
1	0	1	0	$1.0 = 0$	
1	1	0	1	$1.1 = 1$	1 } $\bar{Q}_n$
1	1	1	0	$1.1 = 1$	

J	KQ_n	00	01	11	10
0				1	
1		1		1	1

$$T = J \bar{Q}_n + KQ_n = (J + Q_n) (K + \bar{Q}_n)$$

04. Ans: (c)
05. Ans: (d)
06. Ans: 3
07. Ans: (c)
Sol: From circuit we can write

$$D = X \oplus Q$$

$$\text{but for D FF } \Rightarrow Q_{n+1} = D$$

$$Q_{n+1} = D = X \oplus Q$$

$$Q_{n+1} = \bar{X}Q + X\bar{Q}$$

[This is same as T FF output]

$$\text{T FF output } Q_{n+1} = \bar{T}Q + TQ$$

Therefore given circuit act as T Flip-Flop

08. Ans: (d)

$$\text{Sol: } D_A = Q_B \odot Q_C ; D_B = Q_A ; D_C = Q_B$$

$$\text{Given initially } Q_A = Q_B = Q_C = 0$$

CLOCK	D_A	D_B	D_C	Q_A	Q_B	Q_C
0	-	-	-	0	0	0
1	1	0	0	1	0	0
2	1	1	0	1	1	0
3	0	1	1	0	1	1
4	1	0	1	1	0	1
5	0	1	0	0	1	0
6	0	0	1	0	0	1

 The output observed at Q_A is 0110100-----

09. Ans: (b) & (c)

$$\text{Sol: Total states in 'n' bit Johnson counter} = 2^n$$

$$\text{number of used states} = 2 \times n$$

$$\text{Here } n = 4 \text{ bits}$$

$$\text{So, total number of states} = 2^4 = 16$$

$$\text{number of used states} = 2 \times 4 = 8$$

$$\text{unused states} = \text{Total states} - \text{used states}$$

$$\text{Unused states} = 16 - 8$$

$$= 8$$


DEEP
 LEARN

Regular Doubt clearing Sessions | Free Online Test Series Programme

Affordable Fee | Available 3M | 6M | 12M | 18M and 24 Months Subscription Packages