



ACE
Engineering Academy
Leading Institute for ESE/GATE/PSUs

HYDERABAD | DELHI | PUNE | BANGALORE | LUCKNOW | CHENNAI | VISAKHAPATNAM | VIJAYAWADA | TIRUPATHI | KOLKATA | AHMEDABAD

ESE-2021 (MAINS)

QUESTIONS WITH DETAILED SOLUTIONS

ELECTRONICS & TELECOMMUNICATION ENGINEERING

PAPER-I

ACE Engineering Academy has taken utmost care in preparing the ESE-2021 MAINS Examination solutions. Discrepancies, if any, may please be brought to our notice. ACE Engineering Academy do not owe any responsibility for any damage or loss to any person on account of error or omission in these solutions. ACE Engineering Academy is always in the fore front of serving the students, irrespective of the examination type (GATE/ESE/PSUs/PSC/GENCO/TRANSCO etc.,).

All Queries related to ESE - 2021 MAINS Solutions are to be sent to the following email address hyderabad@aceenggacademy.com

Contact Us : 040-23234418,19,20

www.aceenggacademy.com



ELECTRONICS & TELECOMMUNICATION ENGINEERING
ESE MAINS 2021 PAPER – I
Questions with Detailed Solutions

SUBJECT WISE WEIGHTAGE

S.No	NAME OF THE SUBJECT	Marks
01	BASIC ELECTRICAL ENGINEERING	32
02	BASIC ELECTRONICS ENGINEERING	94
03	MATERIALS SCIENCE	54
04	ELECTRONIC MEASUREMENTS & INSTRUMENTATION	72
05	NETWORK THEORY	126
06	ANALOG ELECTRONICS	62
07	DIGITAL ELECTRONICS	40


SECTION - A

01. (a) An N-type silicon bar of conductivity $\sigma = 1/\Omega\text{-cm}$ has a battery applied across it as shown in the figure below. Assume a hypothetical situation in which the battery is able to sweep some electrons into a region of length 0.03 cm in the middle of the bar, thereby locally increasing the electron density in the region by 1% of the thermal equilibrium density. Make the rough calculation of the order of magnitude of the electric field which will develop there due to this increase in majority carrier density.

Assume, mobility of electron $\mu_n = 1350 \text{ cm}^2/\text{V-s}$,

Permittivity of Si $\epsilon_{Si} = 10^{-12} \text{ F/cm}$.

(12 M)

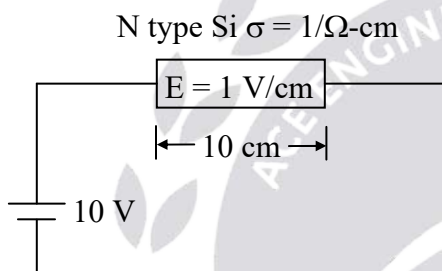

Sol: The electric field can be given as

$$E_x = -V_T \frac{1}{n(x)} \frac{dn(x)}{dx}$$

$$n(x) = n_0 + 1\% n_0 x \quad 0 \leq x \leq 0.03 \text{ cm}$$

$$n(x) = n_0 + 0.01 n_0 x \quad 0 \leq x \leq 0.03 \text{ cm}$$

$$\text{Given } \sigma = 1 (\Omega\text{-cm})^{-1}$$

$$\Rightarrow P = 1 \Omega\text{-cm}$$

$$P = \frac{1}{n_0 q \mu_n} \Rightarrow n_0 = \frac{1}{pq \mu_n}$$

$$n_0 = \frac{1}{1 \times 1.6 \times 10^{-19} \times 1350} = 4.63 \times 10^{15} / \text{cm}^3$$

$$\frac{dn(x)}{dx} = \frac{d}{dx} (n_0 + 0.01 n_0 x) = 0.01 n_0$$

$$E_x = -V_T \left(\frac{1}{n_0 + 0.01 n_0 x} \right) 0.01 n_0 = -V_T \left(\frac{0.01}{1 + 0.01x} \right)$$

At $x = 0.03$

$$E_x = -0.026 \times \frac{0.01}{1 + (0.01)(0.03)} = 2.6 \times 10^{-4} \text{ V/cm} = 0.26 \text{ mV/cm}$$



We Have Evolved!

DEEP
LEARN

is now



ACE
ONLINE

Our Courses are Available on


► IOS (Mobile/Tab), ► Android (Mobile/Tab), ► Windows (Laptop/Desktop)

Scan QR Cocde to download the APP



01. (b) The work function ϕ_m of platinum is 5eV and the electron affinity for silicon is $\chi_{Si} = 4.05\text{eV}$. Determine the barrier height ϕ_{Bn} (barrier height for transfer of electron from metal to semiconductor) and ϕ_{Bp} (barrier height for transfer) of holes from metal to semiconductor). Also calculate the built-in voltage V_{bi} for metal-semiconductor contact of platinum with N-type silicon having doping concentration $N_D = 2.8 \times 10^{14}/\text{cm}^3$. Assume that effective density of states in the conduction band edge is $N_C = 2.8 \times 10^{19}/\text{cm}^3$, $KT = 0.025 \text{ eV}$ at room temperature, $E_G = 1.1\text{eV}$. (12 M)

Sol:

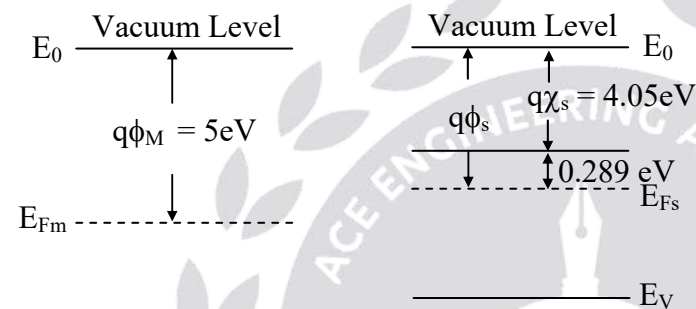

$$q\phi_s = q\chi_s + (E_C - E_{Fs})$$

$$E_C - E_{fs} = KT \ln\left(\frac{N_C}{N_D}\right) = 0.025 \ln\left(\frac{2.8 \times 10^{19}}{2.8 \times 10^{14}}\right)$$

$$= 0.287 \text{ eV}$$

$$q\phi_s = 4.05 \text{ eV} + 0.289 \text{ eV} = 4.339 \text{ eV}$$

$$\phi_{Bn} = \phi_m - \phi_s = 5 - 4.339 = 0.661 \text{ V}$$

(or)

$$q\phi_{Bn} = 0.661 \text{ eV}$$

$$\phi_{Bp} = -\phi_{Bn} = -0.661 \text{ V}$$

(or)


$$q\phi_{Bp} = -0.661 \text{ eV}$$

Built in potential

$$V_{bi} = V_T \ln\left(\frac{N_D N_C}{n_i^2}\right)$$


$$= 0.025 \times \ln\left(\frac{2.8 \times 10^{14} \times 2.8 \times 10^{19}}{(1.5 \times 10^{10})^2}\right) = 0.78 \text{ V}$$

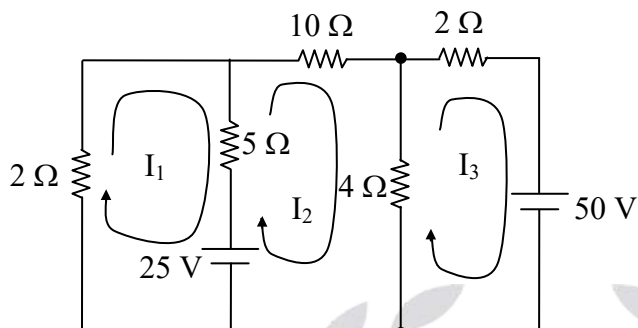01. (c) Write the mesh current matrix equation for the network of figures shown by inspection, and solve for the currents.



(12 M)

Sol:

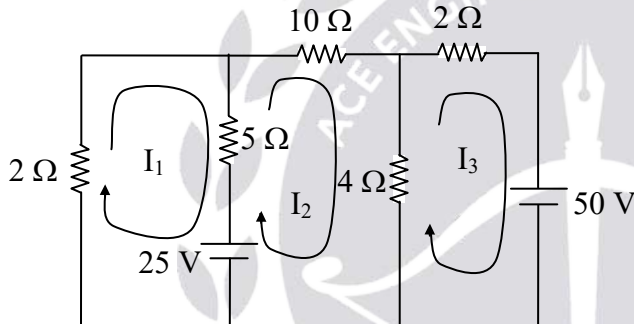

By KVL for (1)

$$2I_1 + (I_1 - I_2) 5 + 25 = 0$$

$$7I_1 - 5I_2 + 25 = 0 \dots\dots(1)$$

By KVL for (2)

$$10I_2 + (I_2 - I_3) 4 - 25 + (I_2 - I_1) 5 = 0$$

$$-5I_1 + 19I_2 - 4I_3 = 25 \dots\dots(2)$$

By KVL for (3)

$$2I_3 + 50 + (I_3 - I_2) 4 = 0$$

$$-4I_2 + 6I_3 - 50 = 0 \dots\dots(3)$$

From (1)(2) & (3)

$$\begin{bmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -25 \\ 25 \\ -50 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} -25 & -5 & 0 \\ 25 & 19 & -4 \\ -50 & -4 & 6 \end{vmatrix}}{\begin{vmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{vmatrix}} = \frac{-25(114-16)+5(150-200)}{7(114-16)+5(-30)}$$

$$= \frac{-2450-250}{686-150} = \frac{-2700}{536}$$

$$I_1 = -5.037 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 7 & -25 & 0 \\ -5 & 25 & -4 \\ 0 & -50 & 6 \end{vmatrix}}{536}$$

$$= \frac{7(150-200)+25(-30)}{536}$$

$$= \frac{-350-750}{536} = \frac{-1100}{536}$$

$$= -2.05 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 7 & -5 & -25 \\ -5 & 19 & 25 \\ 0 & -4 & -50 \end{vmatrix}}{536}$$

$$= \frac{7(-950+100)+5(250)-25(20)}{536}$$





$$= \frac{-850 \times 7 + 1250 - 500}{536} = \frac{-5200}{536} = -9.7 \text{ A}$$

$$I_1 = -5.037 \text{ A}$$

$$I_2 = -2.05 \text{ A}$$

$$I_3 = -9.7 \text{ A}$$

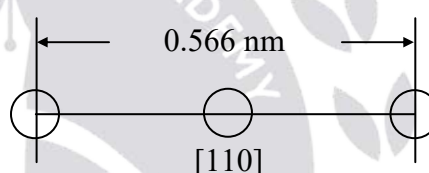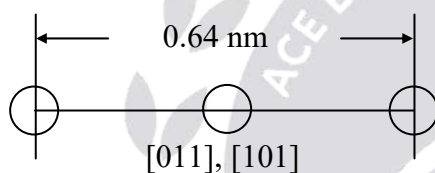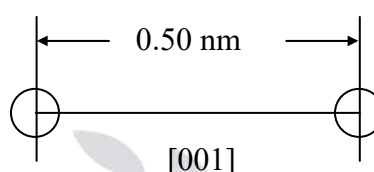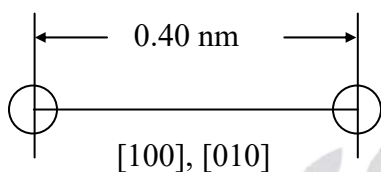
01. (d) The atomic packing schemes for some hypothetical material for several different crystallographic directions are shown. For each direction the circles represents only those atoms contained within a unit cell, where circles are reduced from their actual diameter/size.



Identify the unit cell and the crystal system it belongs to.


(12 M)

Sol:

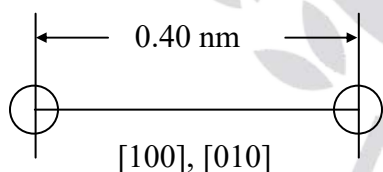


The given direction represent a side of a unit cell
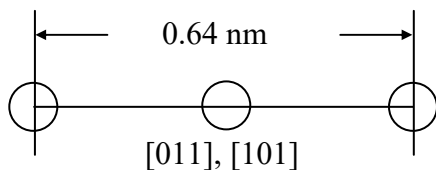
$$a_y = a_x = 0.40 \text{ nm} \quad (\text{X, Y - direction})$$




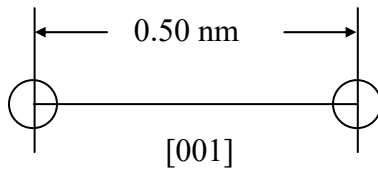The given direction represent a Face diagonal $\sqrt{2}a = 0.64 \text{ nm}$



The given direction also represent a side of unit cell in 2-direction

$$a_z = 0.50 \text{ nm}$$

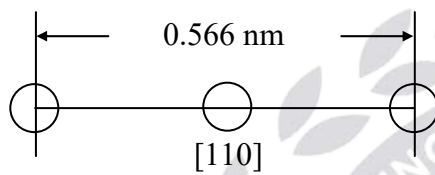


The given direction is a x-y-Face diagonal

$$\sqrt{2}a_{xy} = 0.566 \text{ nm}$$

$$a_x = a_y \neq a_z$$
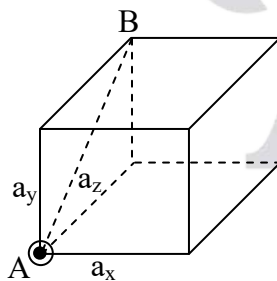
$$\begin{aligned} \text{X-Y Face diagonal} &= \sqrt{2}a_x \\ &= \sqrt{2} \times 0.4 \\ &= 0.5656 \end{aligned}$$



Y-Z Face diagonal

$$(AB) = \sqrt{a_z^2 + a_y^2} = \sqrt{0.5^2 + 0.4^2} = 0.64 \text{ nm}$$

Conclusion: From the above, the crystal system is Face centered tetragonal structure and unit cell is Tetragonal.

01. (e) What are the different types of batteries? How is the right battery selected for an application? (12 M)

Sol: CLASSIFICATION OF CELLS:

Cells are divided into two main types. The primary cell and the secondary cell.

Primary Cells: The Primary cell once it has exhausted its activity is of no further use, i.e., once discharged cannot be recharged.

Ex: Copper zinc cell

Classification of primary cells: Primary cells may be either wet or dry type

(a) **Wet cell:** In wet cell, the electrolyte is in completely liquid form. In this cell, the positive plate is copper and the negative plate is zinc and electrolyte is dilute sulphuric acid. The voltage level is 1.5V.

(b) **Dry cell:** In dry cell, as absorbent material is saturated with the electrolyte and is then placed in contact with the plates.

(i) In dry cell, zinc case is acting as negative plate and carbon rod as the positive plate. The electrolyte is the Ammonium chloride (NH_4Cl). It delivers an emf of 1.5V when it is in good condition.

(ii) Dry cells deteriorate even when not in use owing to the evaporation of the electrolyte and decomposition of zinc electrode.

(iii) **Polarization:** Polarization is due to an accumulation of hydrogen on positive plate, which results in increased internal resistance and lower battery voltage and capacity. The use of depolarizing agent manganese dioxide. (MnO_2) tends to prevent this.

(iv) **Local action:** Local action refers to counter voltage set up in a plate because of chemical impurities. It is prevented in the dry cell by amalgamating with zinc and mercury.

Secondary cells:

The secondary cell can be recharged by sending current through it in the reverse direction.

The secondary cells are also called as storage cells

Ex: lead-acid cell.



FREE Interview Guidance Program for **ESE-2021 MAINS** Qualified Students

Details:

- Orientation Sessions on how to fill **DAF**
- Free Interview Guidance Classes for Technical Subjects, Personality Development & Interview Tips
- Free Mock Interviews
- Relevant Study Materials


Mode:
Online/Offline



For Updates follow our website:
www.aceenggacademy.com


- (a) The advantages of storage cell over primary cell are
- (i) it can be recharged
 - (ii) it can be built to provide heavier current capabilities
 - (iii) it is more economical in the long run
- (b) A hydrometer is used to determine the specific gravity of lead-acid cells.
- (c) The number of plates in a lead acid is an odd integer. The reason for this is that the negative group has one more plate than positive group.
- (d) The lead acid cell depends on its action on the presence of two plates cover with PbO_2 and Pb respectively in a solution of dilute H_2SO_4 of specific gravity 1.21 or near about.
- (e) When a lead acid cell is fully charged, the positive plate is dark chocolate brown in colour and negative plate is in slate gray colour. During discharging both anode and cathode become PbSO_4 which is whitish in colour.

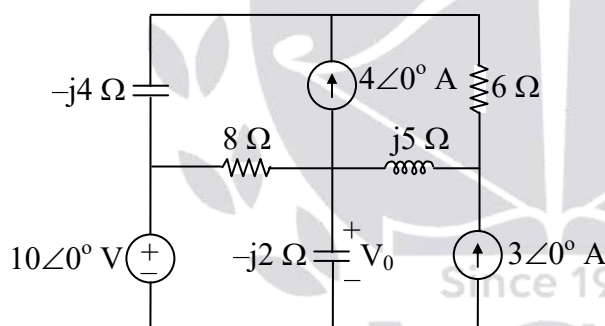02. (a) Solve for V_0 in the circuit shown in the figure.



(20 M)

Sol:

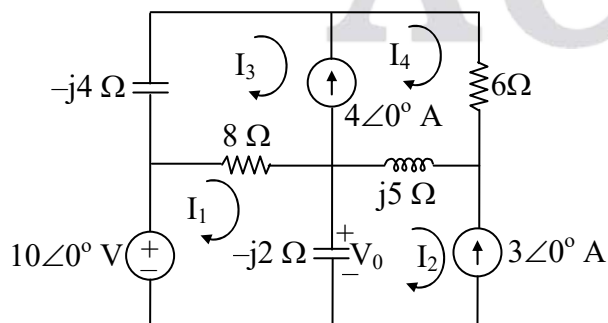

$$-10 + (8-j2) I_1 - (-j2) I_2 - 8I_3 = 0$$

$$(or) (8-j2) I_1 + j2 I_2 - 8I_3 = 10 \quad (1)$$

$$I_2 = -3 \text{ _____ (2)}$$

$$(8-j4)I_3 - 8I_1 + (6+j5)I_4 - j5I_2 = 0 \text{ _____ (3)}$$

$$I_4 = I_3 + 4 \text{ _____ (4)}$$

Combine (1) and (2)

$$(8-j2)I_1 - 8I_3 = 10 + j6 \text{ _____ (5)}$$

Combine (2) and (4)

$$-8I_1 + (14+j)I_3 = (-24-j35) \text{ _____ (6)}$$

Matrix form

$$\begin{bmatrix} (8-j2) & -8 \\ -8 & (14+j) \end{bmatrix} \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10+j6 \\ -24-j35 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} (8-j2) & -8 \\ -8 & (14+j) \end{vmatrix} = (50-j20)$$

$$\Delta_1 = \begin{vmatrix} (10+j6) & -8 \\ (-24-j35) & (14+j) \end{vmatrix} = (-58-j186)$$

$$\text{So, } I_1 = \frac{\Delta_1}{\Delta} = \frac{(-58-j186)}{50-j20} = 3.618 \angle 274.5^\circ \text{ A}$$

Then finally V_0 is

$$V_0 = -j2(I_1 - I_2) = -j2 [3.618 \angle 274.5^\circ + 3] = -7.2134 - j6.568$$

$$V_0 = 9.756 \angle 222.32^\circ \text{ V}$$

02. (b) An MOS capacitor having the gate oxide thickness, $t_{ox} = 0.1 \mu\text{m}$ and substrate boron doping density $N_A = 10^{15}/\text{cm}^3$ is biased in the depletion mode with a gate voltage, V_G . If the surface potential is 0.2V for this bias condition, determine the following:

(5×4 = 20 M)

(i) Peak electric in silicon substrate

(ii) electric field in the oxide

(iii) The gate voltage V_G


(iv) Thermal equilibrium hole concentration, P_P and the hole concentration, P_s at the silicon surface.

Note: That $\epsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}$, $\epsilon_s = 12$ for silicon and $\epsilon_{ox} = 4$ for SiO_2 .

Sol: $t_{ox} = 0.1 \mu m$

$$N_A = 10^{15} / cm^3$$

$$\psi_s = 0.2V$$

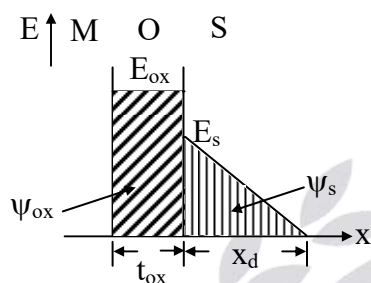

(i) $\psi_s = \frac{1}{2} x_d E_s$

$$E_s = \frac{2\psi_s}{x_d} - \text{Peak electric field at the surface}$$

$$|Q_d| = qN_A x_d$$

$$\text{Depletion width } (x_d) = \frac{|Q_d|}{qN_A} = \frac{\sqrt{2qN_A \epsilon_s \psi_s}}{qN_A} = \sqrt{\frac{2\epsilon_s \psi_s}{qN_A}}$$

$$x_d = \sqrt{\frac{2 \times 12 \times 8.854 \times 10^{-14} \times 0.2}{1.6 \times 10^{-19} \times 10^{15}}}$$

$$x_d = 5.15 \times 10^{-5} \text{ cm}$$

$$E_s = \frac{2\psi_s}{x_d} = \frac{2 \times 0.2}{5.15 \times 10^{-5}} = 7.8 \text{ kV/cm}$$

- (ii) To Calculate the peak electric field in oxide, apply boundary conditions.

$$D_{n1} = D_{n2}$$

$$\epsilon_1 E_{n1} = \epsilon_2 E_{n2}$$

$$\epsilon_{ox} E_{ox} = \epsilon_s E_s$$

$$\Rightarrow E_{ox} = \left(\frac{\epsilon_s}{\epsilon_{ox}} \right) E_s = \left(\frac{12}{4} \right) 7.8 \text{ kV/cm} = 23.4 \text{ kV/cm}$$

- (iii) $V_G = \psi_{ox} + \psi_s$

$$\psi_{ox} = t_{ox} E_{ox} = 0.1 \times 10^{-4} \text{ cm} \times 23.4 \text{ kV/cm}$$

$$\psi_{ox} = 0.234 \text{ V}$$

$$V_G = 0.234 + 0.2$$

$$V_G = 0.434 \text{ V}$$

- (iv) The equilibrium hole concentration

$$p_p = N_A = 10^{15} / \text{cm}^3$$

Surface holes concentration

$$p_s = n_i e^{\frac{(E_i - E_{FS})}{KT}}$$

$q\psi_s$ is the extent of band bending at the surface

$$\Rightarrow p_s = n_i e^{\frac{q\psi_s}{KT}} = 1.5 \times 10^{10} \times e^{\frac{0.2}{0.026}}$$

$$p_s = 3.3 \times 10^{13} / \text{cm}^3$$

- 02. (c) (i) A silicon P-N junction photodiode has a uniform area of cross-section of $A = 0.04 \text{ cm}^2$. In the p-region, $N_A = P_p = 1.5 \times 10^{15} / \text{cm}^3$ and in the N-region, $N_D = n_n = 1.5 \times 10^{13} / \text{cm}^3$. The intrinsic carrier density in silicon is $n_i = 1.5 \times 10^{10} / \text{cm}^3$. The diffusion constant for electrons and holes are $D_n = 35 \text{ cm}^2/\text{s}$ and $D_p = 12.5 \text{ cm}^2/\text{s}$. Holes lifetime in the N-region is $\tau_p = 100 \text{ } \mu\text{sec}$ and electron lifetime in the p-region is $\tau_n = 35 \text{ } \mu\text{sec}$ and electron lifetime in the P-region is $\tau_n = 35 \text{ } \mu\text{sec}$. Assuming that light of a suitable mixture of wavelength falls on the diode producing an idealized generation of EHP, $G_L = 10^{16} \text{ pairs/sec/cm}^2$ uniformly at all points within the volume of diode, and the diode is kept short circuited, calculate the light induced current through the photodiode. (15 M)**
- (ii) In the photodiode of Q2(c)(i), if instead of short circuiting, the diode is kept open circuited, calculate the open circuit photo voltage, V_{oc} across the diode. Assume $V_T = 0.026 \text{ V}$ at room temperature. (5 M)**

Sol:

(i) $A = 0.04 \text{ cm}^2$
 $N_A = 1.5 \times 10^{15} / \text{cm}^3$
 $N_D = 1.5 \times 10^{13} / \text{cm}^3$
 $n_i = 1.5 \times 10^{10} / \text{cm}^3$
 $D_n = 35 \text{ cm}^2 / \text{sec}, D_p = 12.5 \text{ cm}^2 / \text{sec}$
 $\tau_n = 35 \text{ } \mu\text{sec}, \tau_p = 100 \text{ } \mu\text{sec}$
 $L_n = \sqrt{D_n \tau_n} = \sqrt{35 \times 35 \times 10^{-6}} = 35 \times 10^{-3} \text{ cm}$
 $L_p = \sqrt{D_p \tau_p} = \sqrt{12.5 \times 100 \times 10^{-6}} = 3.5 \times 10^{-2} \text{ cm}$
 $I_L = AqG' (W + L_n + L_p)$
 $W = \sqrt{\frac{2\epsilon V_0}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)}$
 $V_0 = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$

$$= 0.026 \times \ln \left(\frac{1.5 \times 10^{15} \times 1.5 \times 10^{13}}{(1.5 \times 10^{10})^2} \right)$$

$$V_0 = 0.48 \text{ V}$$

$$W = \sqrt{\frac{2 \times 12 \times 8.854 \times 10^{-14} \times 0.48}{1.6 \times 10^{-19}}} \left(\frac{1}{1.5 \times 10^{15}} + \frac{1}{1.5 \times 10^{13}} \right) = 6.5 \times 10^{-4} \text{ cm}$$

$$I_L = Aq G' (W + L_n + L_p)$$

$$= 0.04 \times 1.6 \times 10^{-19} \times 10^{16} (6.5 \times 10^{-4} + 35 \times 10^{-3} + 3.5 \times 10^{-2})$$

$$I_L = 4.521 \text{ } \mu\text{A}$$

(ii) Open-Circuit voltage

$$V_{OC} = V_T \ln \left(1 + \frac{I_L}{I_0} \right)$$

$$I_0 = Aq \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_p N_A} \right] n_i^2$$

$$I_0 = 0.04 \times 1.6 \times 10^{-19} \left(\frac{12.5}{3.5 \times 10^{-2} \times 1.5 \times 10^{13}} + \frac{35}{35 \times 10^{-3} \times 1.5 \times 10^{15}} \right) (1.5 \times 10^{10})^2$$

$$I_0 = 3.5 \times 10^{-11} \text{ A}$$

$$V_{oc} = 0.026 \ln \left(1 + \frac{2.5 \times 10^{-6}}{3.5 \times 10^{-11}} \right)$$

$$= 0.3 \text{ V}$$

03. (a) (i) Explain, how Burgers vector is invariant for the type of dislocation. (10 M)

(ii) Out of (100) and (110) crystallographic planes, which plane will have more surface energy for copper single crystal? (10 M)

Given: Bond energy per bond for copper = 65.4 kJ/mol

Lattice parameter for copper = 3.61 \AA

Avogadro's number = $6.023 \times 10^{23} \text{ g/mol}$


Sol:

(i) Burger's vector is a direction and magnitude of dislocation motion.

In edge dislocation, burger's vector is parallel to the applied force but it is perpendicular to the dislocation line.

In screw dislocation, burger's vector is perpendicular to the applied force but it is parallel to the dislocation vector.

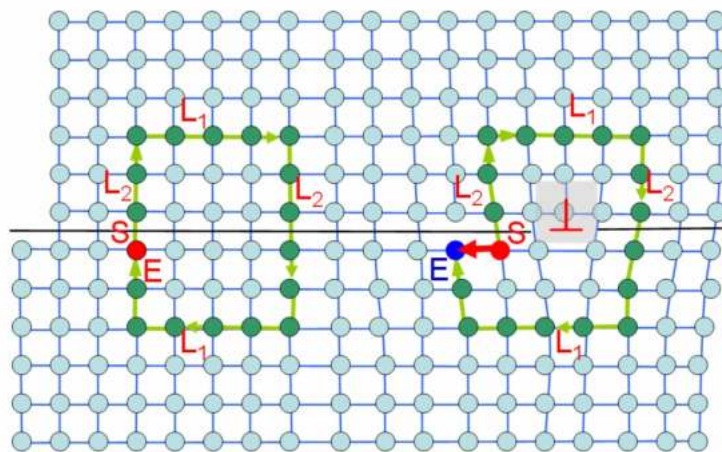The burger's vector is not necessary to be straight. When it is curved some parts can be a screw dislocation and some parts an edge dislocation. For a given vector that points in one direction along the dislocation, the burger's vector is invariant.



CLASSROOM COACHING



@ HYDERABAD

CE | ME | EC | EE | CS | PI | IN

ESE | GATE | PSUs - 2023

- **College Goers Batch:**

26th Nov-2021

@ ABIDS

@ KUKATPALLY

@ KOTHAPET



- **Regular Batches:**

20th Jan-2022

26th Feb-2022

13th Mar-2022

27th Mar-2022

11th Apr-2022

25th Apr-2022

08th May-2022

22nd May-2022

11th Jun-2022

- **Spark Batches:**

8th May-2022

22nd May-2022

11th Jun-2022

- **Summer Short-Term Batches:**

8th May-2022

22nd May-2022

11th Jun-2022

DISCOUNTS


10% OFF | **EARLY BIRD OFFER**

valid till
30th Nov. 2021

50% OFF | **ACE OLD STUDENTS**


(ii) Copper is FCC structure metal:

(100) Plane:-

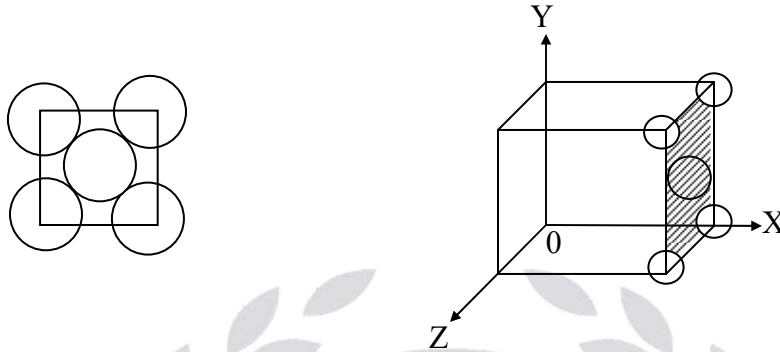

$$\text{Planar density} = \frac{2}{a^2}$$

(110) Plane:-

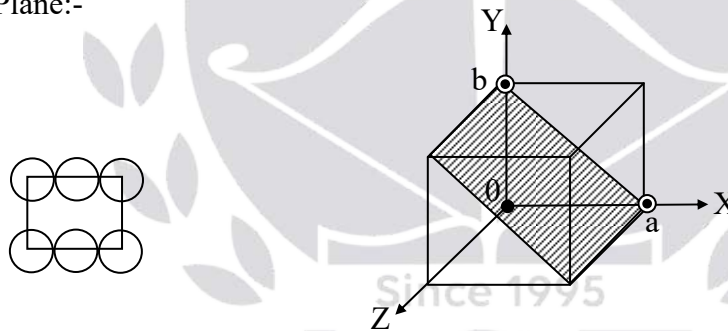


$$\text{Planar density} = \frac{2}{\sqrt{2}a^2} = \frac{\sqrt{2}}{a^2}$$

Planar density of (100) > Planar density of (110)

$$\text{Planar density} \propto \frac{1}{\text{Surface energy}}$$

So surface energy in (110) plane is greater than (100).

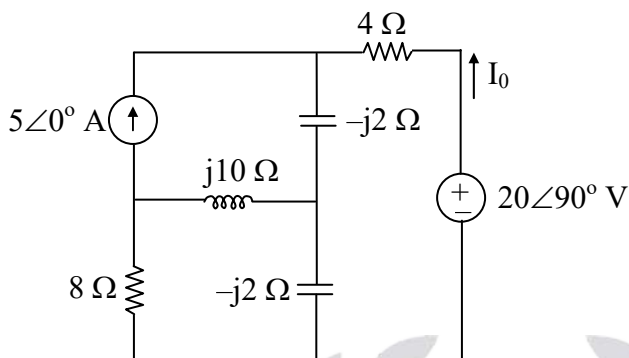
03. (b) Use the superposition theorem to find I_0 in the circuit shown in the figure.



(20 M)

Sol: Let $I_0 = I'_0 + I''_0$

Statement I: Due to voltage source only

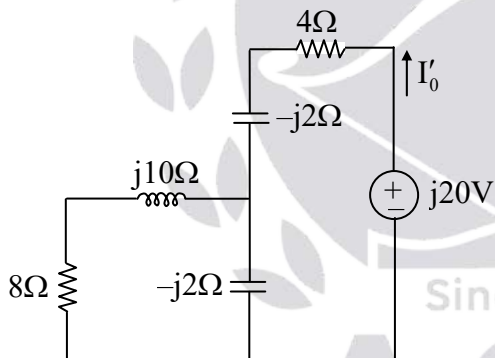


$$Z = \frac{-j2(8 + j10)}{-j2 + 8 + j10} = (0.25 - j2.25)$$

$$\text{So, } I'_0 = \frac{j20}{4 - j2 + 2} = \frac{j20}{(4.25 - j4.25)}$$

$$I'_0 = (-2.353 + j2.353)$$

Statement II: Due to current source only

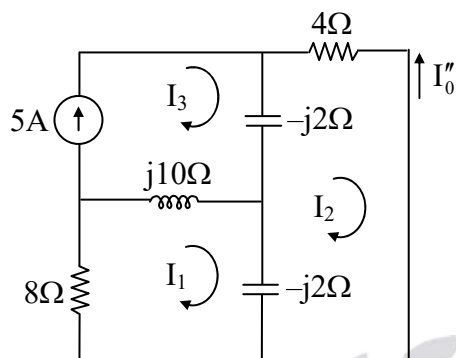

Mesh-1

$$(8+j8) I_1 - j10 I_3 + j2I_2 = 0 \quad (1)$$

Mesh-2

$$(4-j4) I_2 + j2 I_1 + j2I_3 = 0 \quad (2)$$

Mesh-3

$$I_3 = 5 \quad (3)$$

Substituting (2) & (3) we get

$$(4-j4) I_2 + j2 I_1 + j10 = 0$$

$$I_1 = (2+j2) I_2 - 5 \quad (4)$$

Sub (3) and (4) in (2)

$$(8+j8)[(2+j2)I_2 - 5] - j50 + j2 I_2 = 0$$

$$I_2 = \frac{(90-j40)}{34} = (2.647 - j1.176)$$

$$I_0'' = -[I_2] = (-2.647 + j1.176)$$

By Superposition Theorem

$$I_0 = I_0' + I_0'' = (-5 + j3.529)$$

$$= 6.12 \angle 144.78^\circ$$

03. (c) A separately excited DC generator is characterized by the magnetization curve of the figure shown below.


(i) If the prime mover is driving the generator at 800 rev/min, what is the no-load terminal voltage, V_a ?

(ii) If a $1\text{-}\Omega$ load is connected to the generator, what is the generated voltage ?

Generator ratings : 100 V, 100 A, 1000 rev/min

Circuit parameters : $R_a = 0.14\ \Omega$, $V_f = 100\text{ V}$, $R_f = 100\ \Omega$

(20 M)

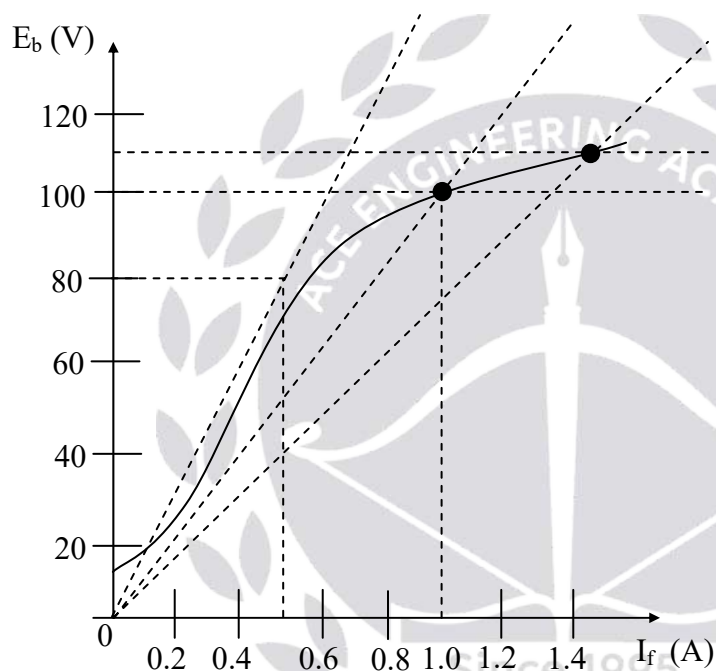

Sol:

(i) At no load, $I_a = 0$

$$E \propto N$$


$$\Rightarrow \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\Rightarrow E_2 = \frac{E_1}{N_1} \times N_2$$

$$= \frac{800}{1000} \times 100 = 80\text{ V}$$

$$\begin{aligned}
 \text{(ii)} \quad E_{g_2} &= V + I_a (R_a + R_{\text{ext}}) \\
 &= 100 + 100 (0.14 + 1) \\
 &= 100 + 114 \\
 &= 214 \text{ Volt}
 \end{aligned}$$

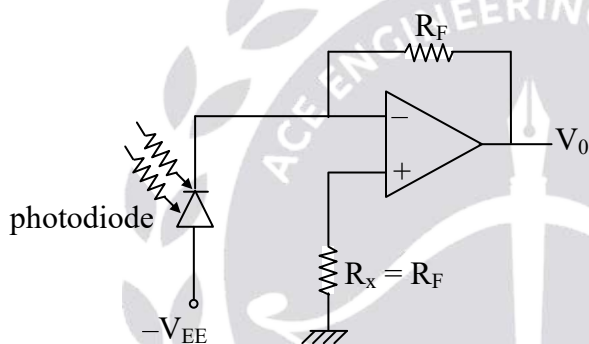04. (a) (i) Design a photo detector circuit of the form as shown in the figure below to give an output voltage of $V_0 = -200 \text{ mV}$ at an incident power density of $D_P = 500 \text{ nW/cm}^2$. The current responsivity of the photodiode is $D_i = 1 \text{ A/W}$, and the active area is $a = 400 \text{ mm}^2$.



(10 M)

(ii) The measured values of a diode at a junction temperature of 25°C are given by

$$V_D = \begin{cases} 0.5\text{V} & \text{at } I_D = 5\mu\text{A} \\ 0.6\text{V} & \text{at } I_D = 100\mu\text{A} \end{cases}$$

Determine the (I) Emission coefficient η , and (II) the leakage current I_s . Assume $V_T = 25.8\text{mV}$.

(10 M)

Sol:

(i) (1) photo diode need to be always in reverse bias So, $-V_{EE}$ must to be selected to make it reverse bias.

(2) Sine responsivity (or) sensitivity

$$R = \frac{I_P}{P_0} = 1\text{A} / \text{W}$$

Where $I_p \rightarrow$ photo diode output current

$P_o \rightarrow$ incident optical power

where optical power,

$$P_o = I_x A,$$

where $I_x \rightarrow$ power /unit area received by light W/cm^2 .

$$\text{Given } I_x = 500nW/cm^2$$

Also, where $A \rightarrow$ Area (Achieve Area), Given $A = 400mm^2$

Hence, diode current, $I_p = R \times P_o$


$$= 1A/w \times 500nw/cm^2 \times 400mm^2.$$

$$\therefore I_p = 1 \times 500 \times 10^{-9} W/cm^2 \times 4cm^2$$

$$= [1 \times 500 \times 10^{-9} \times 4] \text{ Amp}$$


$$= 2\mu A$$

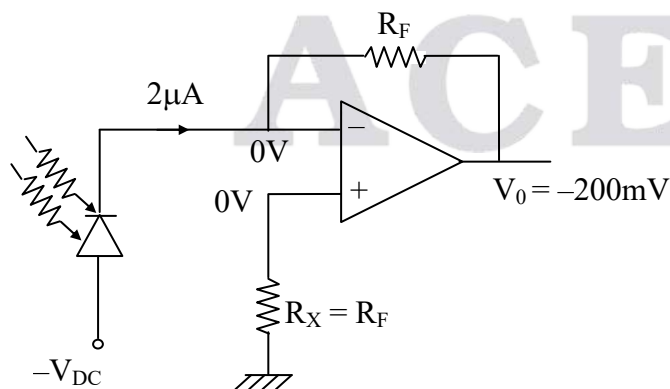(3) Now from the circuit, by virtual short, $I_{R_f} = 2\mu A = \frac{0 - (-200m)}{R_f}$



$$\text{Hence, } R_f = \frac{200mA}{2\mu A} = 100k\Omega$$

Hence the design is →

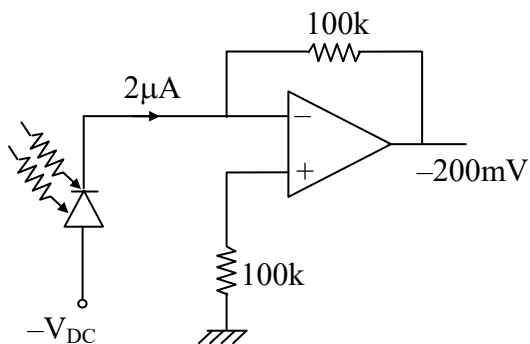

(ii) $I = I_s (e^{V/\eta V_T} - 1) \approx I_s e^{V/\eta V_T}$

$$V_{D1} = 0.5V \rightarrow I_{D1} = 5\mu A$$

$$V_{D2} = 0.6V \rightarrow I_{D2} = 100\mu A$$

$$I_D = I_s e^{V_D/\eta V_T}$$

$$\Rightarrow V_D = \eta V_T \ln \left(\frac{I_D}{I_s} \right)$$

$$V_{D2} - V_{D1} = \eta V_T \ln \left(\frac{I_{D2}}{I_{D1}} \right)$$

$$0.6 - 0.5 = \eta \times 0.0258 \times \ln \left(\frac{100\mu A}{5\mu A} \right)$$

$$\eta = 1.294$$

$$\rightarrow I_{D1} = I_s e^{V_{D1}/\eta V_T}$$

$$\Rightarrow I_s = \frac{5 \times 10^{-6}}{e^{0.5/1.294 \times 0.0258}}$$

$$I_s = 1.56 \times 10^{-12} \text{ A}$$

UPCOMING BATCHES - CLASSROOM COACHING
@ OUR CENTRES
ESE | GATE | PSUs - 2023 / 2024

@ Delhi

☎ 7838971777 (Call/WhatsApp)

• **Weekend Batches:**

19th Dec-2021, 22nd Jan-2022,

• **Regular Batches:**

21st Feb-2022, 27th Mar-2022, 16th Apr-2022,

8th & 22th May-2022, 11th Jun-2022

• **Summer Short Term Batches:**

8th & 22nd May-2022



@ Pune

☎ 9343499966

• **Evening Batches:** 13th Dec-2021, 10th Jan-2022

• **Weekend Batch:** 8th Jan-2022

• **MPSC (Prelims) Batch:** 26th Dec-2021

@ Vijayawada

☎ 9341699966

• **Weekend Batch:** 18th Dec-2021

@ Vizag

☎ 8374808999

• **Weekend Batches:**

18th Dec-2021, 20th Jan-2022, 26th Feb-2022

DISCOUNTS

10% OFF | **EARLY BIRD OFFER**


valid till
30th Nov. 2021

50% OFF | **ACE OLD STUDENTS**

04. (b) (i) (I) Design the basic current source shown in the figure below to give an output current, $I_0 = 5 \mu\text{A}$.

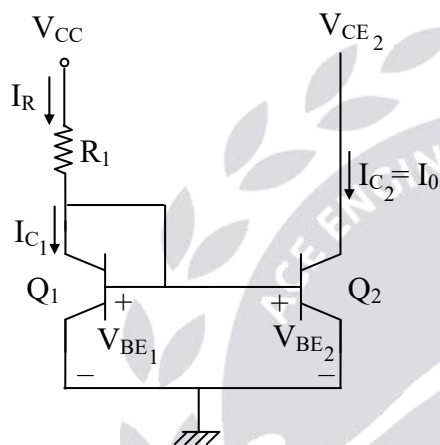(II) For Q4(b)(i)(I) calculate the output resistance R_0 , Thevenin's equivalent voltage V_{TH} , and the collector current ratio if $V_{CE_2} = 20\text{V}$.

The BJT parameters are $\beta_F = 100$, $V_{CC} = 30\text{V}$, $V_{BE_1} = V_{BE_2} = 0.7\text{V}$, and the early voltage $V_A = 150\text{V}$.



(5×2 = 10 M)

(ii) Using the phasor approach, determine the current $i(t)$ in a circuit described by the integro-differential equation $4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$. (10 M)

Sol:

(i) (I) Now from the given data,

$\beta_{F_1} = \beta_{F_2} \Rightarrow$ we could consider as identical transistors

Then the design would be \rightarrow

$$I_{B_1} = I_{B_2} \Rightarrow I_B = 2I_{B_1} = 2I_{B_2}$$

$$I_{C_1} = I_{C_2} \Rightarrow I_{C_1} = I_{C_2} = I_0 = 5\mu\text{A}$$

$$\text{Also, } I_{\text{ref}} = I_{C_1} + I_B = 5\mu + 2I_{B_2}$$

$$\therefore I_{\text{ref}} = 5\mu + \frac{2}{\beta_F} I_{C_2} = 5\mu + \frac{2}{100} \times 5\mu$$


$$\therefore I_{\text{ref}} = 5\mu \left[1 + \frac{2}{100} \right] = 5.1\mu\text{A}$$

Now from circuit

$$R_1 = \frac{30 - 0.7}{I_{\text{ref}}} = \frac{30 - 0.7}{5.1\mu}$$

$$R_1 = 5.7\text{M}\Omega$$

Hence the design is \rightarrow

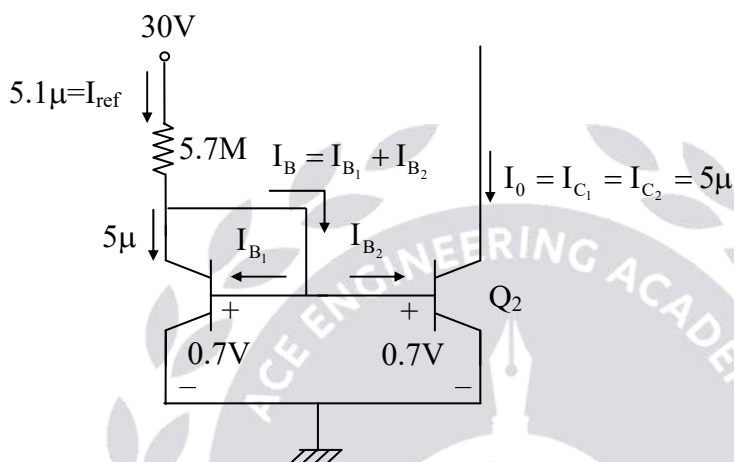

(II) Since $I_{C_1} = I_{C_{01}} \exp\left(\frac{V_{BE_1}}{V_T}\right) \left(1 + \frac{V_{CE_1}}{V_A}\right)$

In forward active due to early effect

Also, since $I_{C_2} = I_{C_{02}} \exp\left(\frac{V_{BE_2}}{V_T}\right) \left(1 + \frac{V_{CE_2}}{V_A}\right)$

So, $\frac{I_{C_1}}{I_{C_2}}$ for $V_{BE_1} = V_{BE_2}$

$$I_{0_1} = I_{0_2}$$

and $V_{CE_2} = 20\text{V}$, with V_A for both transistors = 150V

Then from circuit,

$$V_{CC} = I_{\text{ref}} (R_1) + V_{CE_1}$$

$$30 = 5.1\mu (5.7\text{M}) + V_{CE_2}$$

$$\Rightarrow V_{CE_1} = 30 - 29.07 = 0.93\text{V}$$

$$\therefore \frac{I_{C_1}}{I_{C_2}} = \frac{1 + \frac{V_{CE_1}}{V_A}}{1 + \frac{V_{CE_2}}{V_A}} = \frac{1 + \frac{0.93}{150}}{1 + \frac{20}{150}} = \frac{1.0062}{1.133} = 0.88$$

$$\therefore \frac{I_{C_1}}{I_{C_2}} = 0.88 \quad (\text{or}) \quad \frac{I_{C_2}}{I_{C_1}} = 1.128$$

$$\text{Also output resistance, } R_o = (r_o)_{Q_2} = \frac{V_A}{I_{C_2}} = \frac{150 \text{ V}}{5 \mu\text{A}} = 30 \text{ M}\Omega.$$

(ii) Considering the given function is clearly KVL


$$iR + \frac{1}{C} \int i dt + L \frac{di}{dt} = V_s$$

$$\text{But } R = 4\Omega$$

$$C = \frac{1}{8}$$

$$L = 3\text{H}$$

$$\omega = 2 \text{ (given)}$$

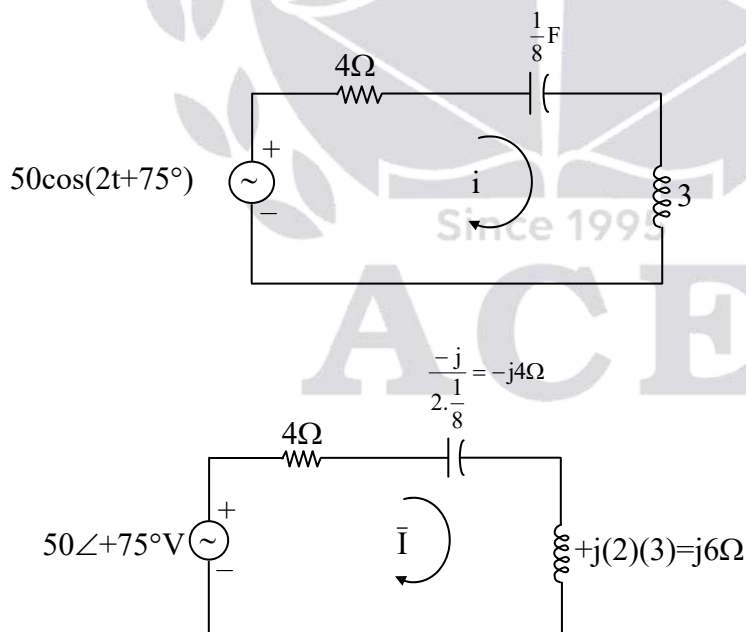

$$- [50\angle 75^\circ] + \bar{I}4 - j4\bar{I} + 6\bar{I} = 0$$

$$\bar{I}[4 + j2] = 50\angle 75^\circ$$

$$\bar{I} = \frac{50 \angle 75^\circ}{(4 + j2)} = \frac{50 \angle 75^\circ}{4.472 \angle 26.56^\circ}$$

$$\bar{I} = 11.18 \angle 48.78 = 11.18 \cos(2t + 48.44) \text{ A}$$

04. (c) (i) Draw a schematic cross-sectional view of a MOSFET transistor. How is the insulating layer fabricated in it and what are the parameters that control the thickness of this layer? **(10 M)**

(ii) Classify magnetic materials; and calculate the saturation magnetization and the saturation flux density for nickel. **(10 M)**

Given : Density of nickel = 8.90 g/cm^3

Atomic weight of nickel = 58.71 g/mol


Net magnetic moment per atom for nickel = 0.60 Bohr magneton

Bohr magneton = $9.27 \times 10^{-27} \text{ A-m}^2$

Avogadro's number = $6.023 \times 10^{23} \text{ g/mol}$

Sol:

(i)

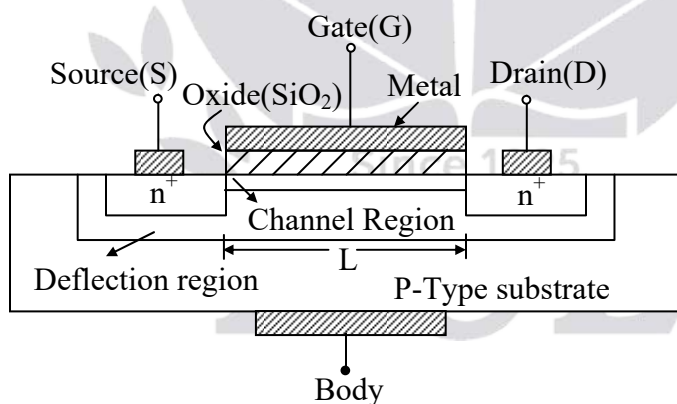

Cross sectional view of MOSFET



→ In MOSFET, the insulating layer we use is known as SiO_2 layer. The insulating silicon dioxide layer is formed through a process of self-limiting oxidation, which is described by the Deal-grove model. A conductive gate material is subsequently deposited over the gate oxide to form the transistor.

Thermal Oxidation:

It is the process of growing a thin layer of oxide on the surface of a wafer. This process is usually performed at a temperature between 900°C & 1100°C. It uses either dry oxidation or wet oxidation.

For dry oxidation

For wet oxidation

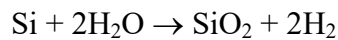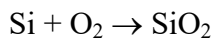

The most commonly used mathematical model to estimate oxide thickness is Deal-grove model

$$t = \frac{Ax + y^2x^2}{B}$$

Parameter that Control the thickness of SiO_2

→ Pressure

→ temperature

→ Diffusion time

(ii) Classification of magnetic material

(a) Dia magnetic material

(b) Para magnetic material

(c) Ferro magnetic material

(d) Antiferro magnetic material

(e) Ferri magnetic material

Given data $\rho_{\text{Ni}} = 8.9 \text{ g/cm}^3$

$AW = 58.71 \text{ g/mol}$

Net magnetic moment per atom = 0.6 Bohr magneton

Bohr magneton = $9.27 \times 10^{-27} \text{ A-m}^2$

Avagadro's number = $6.023 \times 10^{23} \text{ g/mol}$

No. of atoms per unit volume in Ni = $N = \frac{\rho \times AN}{AW}$

$$N = \frac{8.9 \times 10^6 \times 6.023 \times 10^{23}}{58.71} = 0.9130 \times 10^{29} \text{ atoms/m}^3$$

Saturation magnetization = $\mu_s = N \times D_m$


$$\begin{aligned}
 &= \left(\frac{\rho \times AN}{AW} \right) \times 0.6 \times 9.27 \times 10^{-27} \\
 &= \frac{8.9 \times 10^6 \times 6.023 \times 10^{23}}{58.71} \times 0.6 \times 9.27 \times 10^{-27} \\
 &= 5.078 \times 10^2 \text{ A/m}
 \end{aligned}$$

Saturation flux density = $B_s = \mu_0 \mu_s$

$$\begin{aligned}
 &= 4\pi \times 10^{-7} \times 5.078 \times 10^2 \\
 &= 63.77 \times 10^{-5} \text{ Wb/m}^2
 \end{aligned}$$

SECTION - B

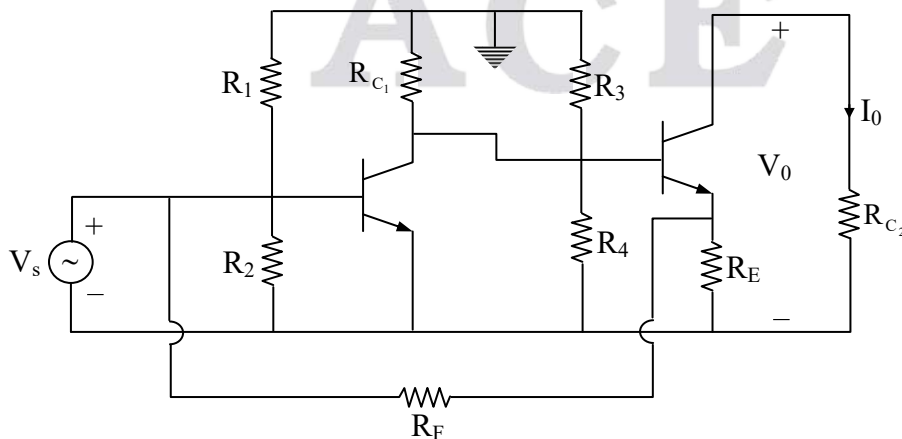05. (a) The open loop gain of the amplifier shown in the figure below has break frequency at $f_{p1} = 100\text{kHz}$, $f_{p2} = 1 \text{ MHz}$ and $f_{p3} = 10 \text{ MHz}$. The low frequency gain is $A_o = 200 \text{ A/A}$ and the emitter resistance $R_E = 500 \Omega$. Determine the value of compensating capacitor C_F and resistance R_F to give (i) low frequency closed loop gain of $A_f = 20 \text{ A/A}$ and cancel the pole $f_{p1} = 100 \text{ kHz}$, and (ii) to add pole of $f_p = 10 \text{ MHz}$ and cancel the pole $f_{p1} = 100 \text{ kHz}$.




(12 M)


Sol: Given the open loop amplifier 3 break frequencies

$$\begin{aligned}
 A &= \frac{A_0}{\left(1 + \frac{S}{\omega_1}\right) \left(1 + \frac{S}{\omega_2}\right) \left(1 + \frac{S}{\omega_3}\right)} \\
 &= \frac{200}{\left(1 + j \frac{\omega}{\omega_1}\right) \left(1 + j \frac{\omega}{\omega_2}\right) \left(1 + j \frac{\omega}{\omega_3}\right)} \\
 &= \frac{200}{\left(1 + j \frac{f}{100k}\right) \left(1 + j \frac{f}{1M}\right) \left(1 + j \frac{f}{10M}\right)}
 \end{aligned}$$

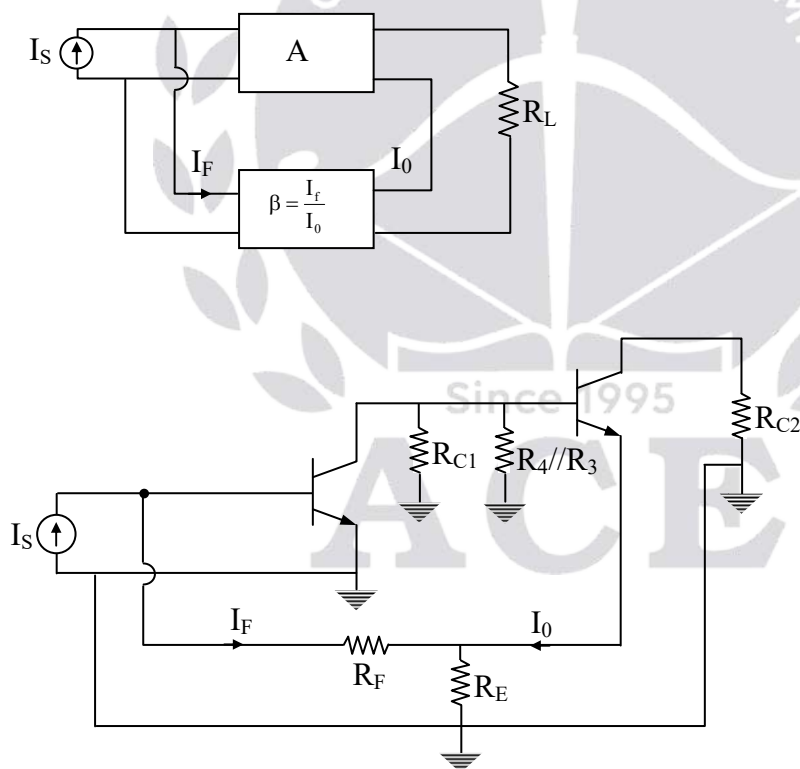Feedback is shunt series (or) current shunt feedback



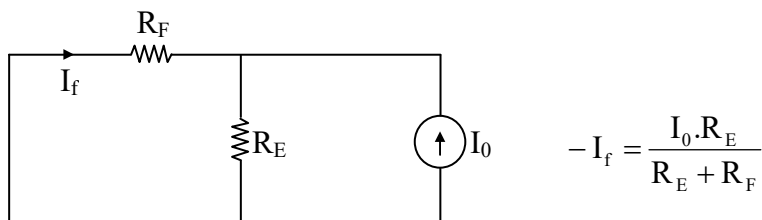The closed loop gain $\frac{I_o}{I_s} = \frac{A}{1 + A\beta} = \frac{1}{\beta}$




$$\beta = \frac{I_f}{I_0} = \frac{-R_E}{R_E + R_F}$$

$$\text{closed loop gain} = \frac{1}{\beta} = \frac{R_E + R_F}{R_E} = 20 \left(\frac{A}{A} \right)$$

But $R_E = 500\Omega$ (given)

$$\therefore 1 + \frac{R_F}{500} = 20 \rightarrow R_F = 9.5k\Omega$$

Let us design a compensation network

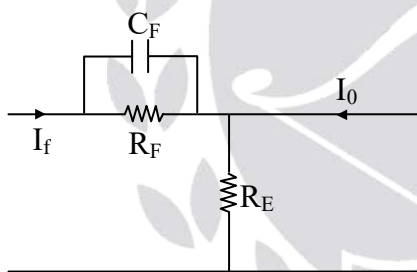

$$\beta = \left| \frac{I_f}{I_0} \right| = \frac{R_E}{R_E + \left(R_F // \frac{1}{SC_F} \right)} = \frac{R_E}{R_E + \frac{R_F}{1 + SC_F R_F}}$$

$$= \frac{R_E (1 + SC_F R_F)}{R_F + R_E (1 + SC_F R_F)}$$

$$= \frac{R_E (1 + SC_F R_F)}{(R_E + R_F) \left(1 + \frac{SC_F R_F R_E}{R_F + R_E} \right)}$$

$$A\beta = \frac{A_0 \left(\frac{R_E}{R_E + R_F} \right) (1 + SC_F R_F)}{\left(1 + j \frac{f}{100k} \right) \left(1 + j \frac{f}{1M} \right) \left(1 + j \frac{f}{10M} \right) (1 + SC_F (R_F // R_E))}$$

In order to cancel a pole at 100kHz

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi C_F R_F} = 100k$$

$$R_F = 9.5k\Omega \rightarrow$$


$$C_F = \frac{1}{2\pi R_F (100k)}$$

$$\therefore C_F = 1.675 \times 10^{-10} F = 0.1675nF$$

$$\left[\text{For } (1 + SCR_F) = \left(1 + j \frac{f}{100k} \right) = \left(1 + \frac{S}{\omega_1} \right) \right]$$


$$f = \frac{1}{2\pi C_F (R_F // R_E)} = \frac{1}{2\pi (0.1675nF)(500 // 9.5k)} = 2MHz$$

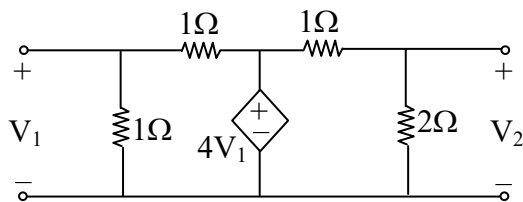05. (b) Determine the Z-parameters for the two-port network shown and check for its symmetry and reciprocity.



(12 M)

Sol:

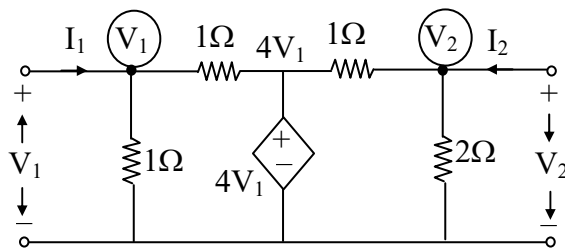

By KCL at V_1

$$I_1 = \frac{V_1}{1} + \frac{V_1 - 4V_1}{1}$$

$$I_1 = -2V_1 \quad \text{----- (1)}$$

By KCL at V_2

$$I_2 = \frac{V_2}{2} + \frac{V_2 - 4V_1}{1}$$

$$I_2 = \frac{3}{2}V_2 - 4V_1$$

$$I_2 = -4V_1 + \frac{3}{2}V_2 \quad \text{----- (2)}$$

From (1) & (2) get Y-Parameters

$$I_1 = -2V_1 + (0)V_2$$

$$I_2 = -4V_1 + \frac{3}{2}V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -2 & 0 \\ -4 & \frac{3}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[Z] = [Y]^{-1} = \frac{1}{-3 - (0)} \begin{bmatrix} \frac{3}{2} & 0 \\ 4 & -2 \end{bmatrix}$$

$$[Z] = \begin{bmatrix} -\frac{1}{2} & 0 \\ \frac{4}{3} & \frac{2}{3} \end{bmatrix}$$

$Z_{11} \neq Z_{22} \Rightarrow$ Network is not symmetry

$Z_{12} \neq Z_{21} \Rightarrow$ Network is not Reciprocal

05. (c) What is superconductivity? How are the superconducting materials classified? Give the applications of high temperature superconductors, in brief. (12 M)


Sol: Super conductivity:- It is a state of material below a critical transition temperature it's resistivity is zero.

In 1911, Kammerling Onnes discovered that the resistivity of pure mercury decreases with temperature and abruptly becomes zero at a sharp critical temperature of 4.2K. At the $T < T_C$ material shows zero resistivity and becomes a superconductor, at $T \geq T_C$ it is a Normal Conductor (NC).

- About 21 elements are found to exhibit Superconductivity property. Generally the valency of the element varies between 2 and 8.
- Alkali metals like sodium, noble metals like Cu, Au, Ag etc and ferro, antiferro magnetic materials do not become superconductors.
- Type-II superconductors are usually alloys and transition metals
- Addition of non-magnetic impurities have no (or) very little effect on superconductivity.
- Addition of magnetic impurities decreases the critical temperature
- Currents once setup in superconductor rings continue to flow for very long time and are called *persistent currents*.
- Magnetic fields are capable of destroying superconductivity: It is called critical field

$$H_c = H_c(0) \left[1 - \frac{T^2}{T_c^2} \right] \text{ Thus } H_c$$

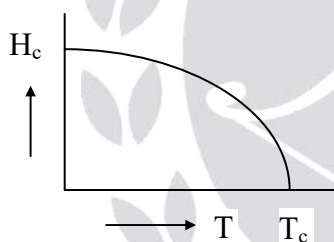depends on the T of the super conductor below T_c .



Types of super conductor:-

- (i) **Type - I (soft) superconductors** have only one critical field B_C and can exist in two states only. (NC or SC).
 - There are Type - II (hard) superconductors (usually alloys) which have two critical field values (B_{C1} & B_{C2}) and can exist in 3 states (NC, Mixed and SC).
 - Between B_{C1} and B_{C2} , they exist in Mixed state, and do not show complete Meissner effect here they are superconducting but start allowing magnetic flux lines to pass through i.e. don't exhibit perfect diamagnetism.
 - For Type – I SCs, magnetization M abruptly becomes zero at B_C whereas for Type – II SCs it gradually decreases to zero between B_{C1} and B_{C2} that is in mixed state.
 - When a specimen becomes a superconductor, its thermal conductivity decreases
 \Rightarrow the superconductivity is not due to ordinary conduction electrons.

Exclusive Online Live Classes for ESE | GATE | PSUs - 2023

Batches for English

Morning & Evening (Last Batch)

13th November, 2021

Regular Batches

BATCH DATES

18th December, 2021

20th January 2022

26th February 2022

13th March 2022

27th March 2022

11th April 2022

25th April 2022

08th May 2022

22nd May 2022

11th June 2022

Batches for Hindi + English (Hinglish)

College Goers Batch (Evening Batch)

13th November, 2021

18th December, 2021

COURSE DETAILS

- For ESE+GATE+PSUs Students
 - >> Online Live Classes - Technical Subjects Only
 - >> Recorded Classes - General Studies Subjects & ESE Addl. Subjects. on ACE Online (Deep Learn)
- Recorded version of the online live class will be made available through out the course (with 3 times view)
- Doubt clearing sessions and tests to be conducted regularly
- Free study material (hard copy)
- Morning Batch: 6 am - 8 am
- Evening Batch: 8 pm - 10 pm
- Regular Batches: 4 - 6 Hours on Weekdays, 6 - 7 Hours on Sundays and Public Holidays
- Access the lectures from any where

FEATURES



Experienced Faculty



Daily Doubt Clearance



Replica of Classroom



Structured Course



Backup Classes

DISCOUNTS

25% OFF

for ACE
old students

20% OFF

for IIT/NIT
students

15% OFF

for IIT/Govt. College
students



Scan QR Code to Enroll


- When a specimen becomes a superconductor, its entropy decreases \Rightarrow superconducting state is less disorderly state.
- When a specimen becomes a superconductor, its electronic specific heat changes abruptly and decreases exponentially in superconducting state \Rightarrow There must be some energy gap in superconductors.

This energy gap in super conductors is about.

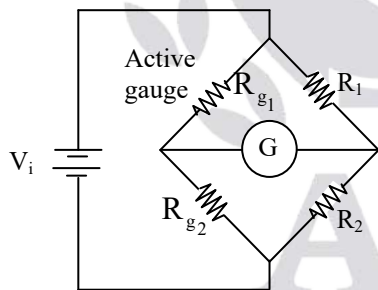
05. (d) How is the temperature compensation achieved in the measurement of strain?

The unstrained resistance of each of the four elements of the unbounded strain gauge is 120Ω . The strain gauge has a gauge factor of 3 and is subjected to a strain of 10^{-4} . If the detector is a high impedance voltmeter, calculate the reading of this voltmeter for a battery voltage of 10 V. Assume the bridge arms A and D are under tension whereas arms B and C are under compression. (12 M)

Sol: In order to cancel the temperature effects on the strain gauge it is important to use a dummy gauge in the neighbourhood of the active gauge. Both the active and dummy gauges are identical in all aspects. They have same temperature coefficient of resistance & temperature coefficient of expansion.



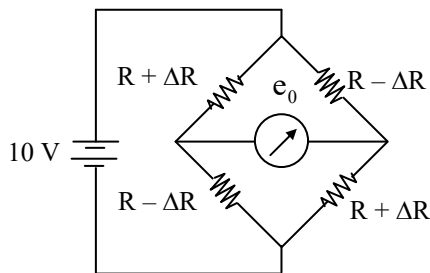Due to temperature changes, if any change in R_{g1} is exactly compensated by the some change made in R_{g2} . In above figure temperature compensation is shown.



$$\frac{\Delta R}{R} = G_f \varepsilon$$

$$G_f = 3, R = 120 \Omega$$

$$\varepsilon = 10^{-4}$$

$$e_i = 10V$$

$$\Delta R = 3 \times 10^{-4} \times 120 = 360 \times 10^{-4} = 0.036 \Omega$$

$$R + \Delta R = 120.036 \Omega$$

$$R - \Delta R = 119.964 \Omega$$


$$e_0 = e_i \times \left(\frac{R - \Delta R}{(R - \Delta R) + (R + \Delta R)} - \frac{R + \Delta R}{(R - \Delta R) + (R + \Delta R)} \right)$$

$$e_0 = 10 \times \left(\frac{119.964}{119.964 + 120.036} - \frac{120.036}{119.964 + 120.036} \right)$$

$$e_0 = 10 \times (0.49985 - 0.50015)$$

$$e_0 = -3mV$$

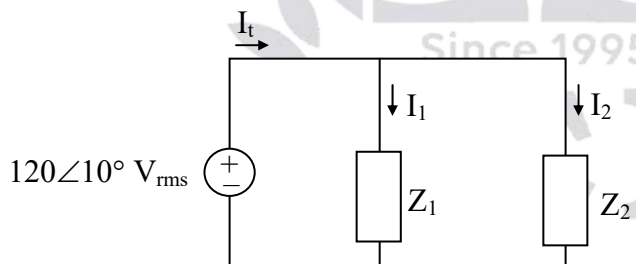05. (e) In the circuit shown in figure $Z_1 = 60 \angle -30^\circ \Omega$ and $Z_2 = 40 \angle 45^\circ \Omega$. Calculate the total (i) apparent power, (ii) real power, (iii) reactive power, and (iv) P.f.



(12 M)

Sol: Current through Z_1 is

$$I_1 = \frac{V}{Z_1} = \frac{120 \angle 10^\circ}{60 \angle -30^\circ} = 2 \angle 40^\circ A \quad (\text{RMS})$$

Current through Z_2 is

$$I_2 = \frac{V}{Z_2} = \frac{120 \angle 10^\circ}{40 \angle 45^\circ} = 3 \angle -35^\circ A \quad (\text{RMS})$$

Complex power absorbed by the impedance are

$$S_1 = \frac{V_{\text{RMS}}^2}{Z_1^*} = \frac{(120)^2}{60 \angle 30^\circ} = 240 \angle -30^\circ$$

$$= (207.85 - j120) \text{ VA's}$$

$$S_2 = \frac{V_{\text{RMS}}^2}{Z_2^*} = \frac{(120)^2}{40 \angle -45^\circ} = 360 \angle 45^\circ$$

$$= (254.6 + j254.6) \text{ VA}$$

Total complex power is

$$S_T = S_1 + S_2 = (462.4 + j134.6) \text{ VA}$$

(i) Total apparent power is

$$|S_T| = \sqrt{(462.4)^2 + (134.6)^2} = 481.6 \text{ VA}$$

(ii) Total real power is

$$P_T = \text{Re}[S_T] = 462.4 \text{ W}$$

$$(\text{or}) P_T = P_1 + P_2$$

(iii) Total reactive power is


$$Q_T = \text{Im}[S_T] = 134.6 \text{ VAR}$$

$$(\text{or}) Q_T = Q_1 + Q_2$$

$$(\text{iv}) \text{ P.F} = \frac{P_T}{|S_T|} = \frac{462.4}{481.6} = 0.96 (\text{lagging})$$

06. (a) (i) In a CRT, the anode to cathode voltage is 2 kV. The parallel deflector plates are 1.5cm long and spaced 5 mm apart. The screen is 50 cm from the centre of the deflecting plates. Find the beam speed and deflection sensitivity of the tube. Mass of electron = 9.109×10^{-31} kg, Charge on electron = 1.602×10^{-19} C. (10 M)

(ii) The coil of a moving iron voltmeter has a resistance of 500 Ω and an inductance of 1.0 H. The series resistor is 2 k Ω . When 250 V dc is applied, the voltmeter reads 250 V. Find the reading when an ac voltage of 250 V, 50 Hz is applied. What is the per cent error? What capacitance must be connected in parallel with the series resistor to remove this error? (10 M)



QUICK REVISION COURSE

PRE-RECORDED CLASSES



COMPUTER SCIENCE

- Detailed Analysis of relevant questions of each topic
- Duration of course 120 days.
- **20% Discount for ACE old students**



Scan to
Download App



UTTAR PRADESH PUBLIC SERVICE COMMISSION

Assistant Engineer-2021

**Online
Test
Series**

CE | ME | EE

Starts from: **1st Dec-2021**

No. of Tests: **16**

Subject Wise: **12**

Mock Tests: **4**

**All tests will be available till
UPPSC AE Examination**

Sol:

(i) $V_a = 2\text{kV}$

$L = 1.5\text{cm}$

$s = 5\text{mm}$

$D = 50\text{cm}$

$m = 9.109 \times 10^{-31} \text{ kg}$

$e = 1.602 \times 10^{-19} \text{ C}$

We know $V_x = \text{Beam Speed}$

$$\Rightarrow V_x = \sqrt{\frac{2eV_a}{m}} = \sqrt{\frac{2 \times 1.602 \times 10^{-19} \text{ C} \times 2\text{kV}}{9.109 \times 10^{-31} \text{ kg}}} = 26.52 \times 10^6 \text{ m/sec}$$

$S_V = \text{Deflection Sensitivity}$

$$\Rightarrow S_V = \frac{LD}{2sV_a} = \frac{1.5\text{cm} \times 50\text{cm}}{2 \times 5\text{mm} \times 2\text{kV}} = 3.75 \times 10^{-4} \text{ m/V} = 0.375 \text{ mm/V}$$

(ii) $R_m = 500\Omega$; $L_m = 0.1\text{H}$; $R_{se} = 2000 \Omega$

$V_{DC} = 250\text{V}$

$V_{AC} = 250\text{V}$, $f = 50\text{Hz}$

$\% \epsilon = ?$ $C = ?$

$$I_{FSD} = \frac{V_{DC}}{R_{total}} = \frac{250}{2500} = 0.1\text{A}$$

$$V_{AC_{reading}} = 0.1 \left[\sqrt{(2500)^2 + (2 \times \pi \times 50 \times 0.1)^2} \right]$$

$$= 250.019 \text{ volts}$$

$$I_{AC} = \frac{250}{Z} = \frac{250}{2500.19} = 0.099 \text{ A}$$

$$\% \epsilon = \frac{0.0999 - 0.1}{0.1} \times 100 = -0.1\%$$

$$C = 0.41 \frac{L_m}{R_{se}^2} = 0.41 \times \frac{0.1}{(2000)^2} = 1.025 \times 10^{-8} \text{ F}$$

06. (b) (i) An ac bridge has the following constants:

arm AB, $R = 1 \text{ k}\Omega$ in parallel with $C = 0.159 \mu\text{F}$;


arm BC, $R = 1 \text{ k}\Omega$; arm CD, $R = 500 \Omega$; arm DA, $C = 0.636 \mu\text{F}$ in series with an unknown resistor. Find the frequency for which the bridge is in balance and determine the value of resistance in arm DA to produce this balance. (10 M)

(ii) A dynamometer type wattmeter connected normally to read power in a single phase circuit indicates the value P_1 . A second reading P_2 is obtained when a capacitor of reactance equal to the pressure coil resistance is connected in series with pressure coil. Show that the phase angle of the load can be obtained from the expression:

$$\tan \phi = 1 - \frac{2P_2}{P_1} \quad (10 \text{ M})$$

Sol:

(i)

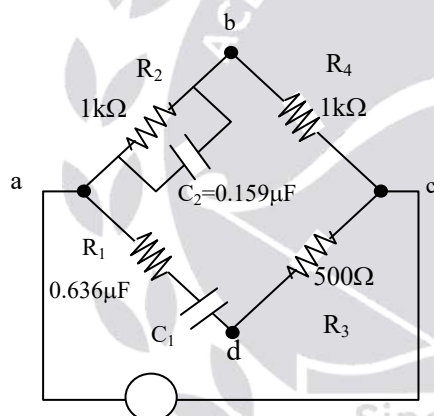

$$Z_1 Z_4 = Z_2 Z_3$$

$$\frac{R_1}{R_2} + \frac{C_2}{C_1} = \frac{R_3}{R_4}$$

$$\frac{R_1}{1000} + \frac{0.159 \times 10^{-6}}{0.636 \times 10^{-6}} = \frac{500}{1000}$$

$$R_1 = 250 \Omega$$

$$f = \frac{1}{2\pi R_1 R_2 C_1 C_2}$$

$$= \frac{1}{2 \times \pi \times 250 \times 100 \times 0.159 \times 10^{-6} \times 0.636 \times 10^{-6}}$$

$$= 62.9 \text{ MHz}$$

- (ii) In a dynamometer type wattmeter, the pressure coil connected across the supply is highly resistive.

Now given, a capacitor of reactance equal to the pressure coil resistance is connected in series with the pressure coil.

$$Z = R_p + j(X_L - X_C) \approx R_p - j X_C$$

$$\text{Angle } \beta = \tan^{-1} \left(\frac{-X_C}{R_p} \right)$$

$$\text{Given, } R_p = X_{C2}$$

$$\Rightarrow \beta = -45^\circ$$

$$\text{Wattmeter reading } (P_1) = \frac{VI}{R_p} \cos \phi (dM/d\theta)$$

$$\text{Wattmeter reading } (P_2) \text{ due to angle } \beta \text{ is } = \frac{VI}{R_p} \cos \beta \cos(\phi - \beta) (dM/d\theta)$$

$$\frac{P_1}{P_2} = \frac{\frac{VI}{R_p} \cos \phi (dM/d\theta)}{\frac{VI}{R_p} \cos \beta \cos(\phi - \beta) (dM/d\theta)} = \frac{\cos \phi}{\cos \beta \cos(\phi - \beta)}$$

$$\frac{P_1}{P_2} = \frac{\cos \phi}{\cos(-45^\circ) \cos(\phi + 45^\circ)}$$

$$\frac{P_2}{P_1} = \frac{\cos(\phi + 45^\circ)}{\sqrt{2} \cos \phi}$$

$$\frac{P_2}{P_1} = \frac{\cos(\phi + 45^\circ)}{\sqrt{2} \cos \phi}$$

$$\frac{P_2}{P_1} = \frac{\cos \phi \cos 45^\circ - \sin \phi \sin 45^\circ}{\sqrt{2} \cos \phi}$$

$$\frac{P_2}{P_1} = \frac{1}{2} - \frac{1}{2} \tan \phi$$

$$\therefore \tan \phi = \left(1 - \frac{2P_2}{P_1} \right)$$



ACE ONLINE

Pre-Recorded Classes

For **ESE | GATE | PSUs | SSC-JE** curated by India's best minds. Access courses through **Mobile / Tablet / Laptop / Desktop** from anywhere.

We have subscriptions options of **1 Month, 3 Months, 6 Months, 12 months, 18 months and 24 months.**

CE | ME | EC | EE | CS | IN | PI

OUR COURSES

- GATE + PSUs (650+ Hours) (English)
- GATE + PSUs (650+ Hours) (Hinglish)
- ESE: General Studies (250+ Hours)
- ESE + GATE + PSUs (1000+ Hours)
- SSC-JE : Technical (CE) (400+ Hours)
- SSC-JE : GS (200+ Hours)
- APPSC / TSPSC-AEE: Tech. (CE) (500+ Hours)
- APPSC / TSPSC-AEE/AE: GS (350+ Hours)
- GENCO / TRANSCO / DISCOMs: EE (550+)
- APPSC-AE (Technical Paper-II) (100+ Hours)
- Quick Revision Course: CSE (250+ Hours)

SALIENT FEATURES



Experienced
Faculty



Free Online
Test Series



Live Doubt
clearance



Learning with
2d & 3d animations



Preparation
Strategy



Self Assessment
Tests



ASK AN
EXPERT



Free Interview
Guidance




Full set of
Study Material



EMI option
Available

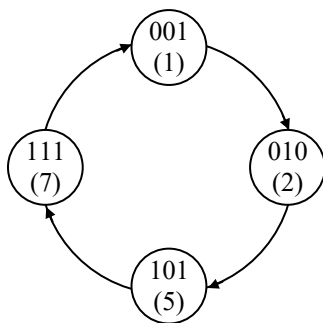06. (c) Design a counter with the irregular binary count sequence shown in the state diagram of the following figure. use J-K flip-flops.



(20 M)

Sol: From the state diagram,

$Q_C Q_B Q_A$	$Q_C^+ Q_B^+ Q_A^+$	$J_C K_C$	$J_B K_B$	$J_A K_A$
0 0 1	0 1 0	0 ×	1 ×	× 1
0 1 0	1 0 1	1 ×	× 1	1 ×
1 0 1	1 1 1	× 0	1 ×	× 0
1 1 1	0 0 1	× 1	× 1	× 0

From the above table,

$J_B = 1$; $K_B = 1$; $J_A = 1$; states 0, 3, 4, 6 are unused states consider them as don't cares.

K-map for J_C :-

$$J_C(Q_C, Q_B, Q_A) = \sum m(2) + d(0, 3, 4, 6, 5, 7)$$

$Q_C \backslash Q_B Q_A$	00	01	10	11
0	×	0	×	1
1	×	×	×	×

$$\therefore J_C = Q_B$$

K-map for K_C :-

$$K_C(Q_C, Q_B, Q_A) = \sum m(7) + d(0, 3, 4, 6, 1, 2)$$

$Q_C \backslash Q_B Q_A$	00	01	10	11
0	×	×	×	×
1	×	0	1	×


$$\therefore K_C = Q_B$$

K-map for K_A :-

$$K_A(Q_C, Q_B, Q_A) = \Sigma m(1) + d(0, 3, 4, 6, 2)$$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	×	1	×	×
1	×	0	0	×


$$\therefore K_A = \overline{Q_C}$$

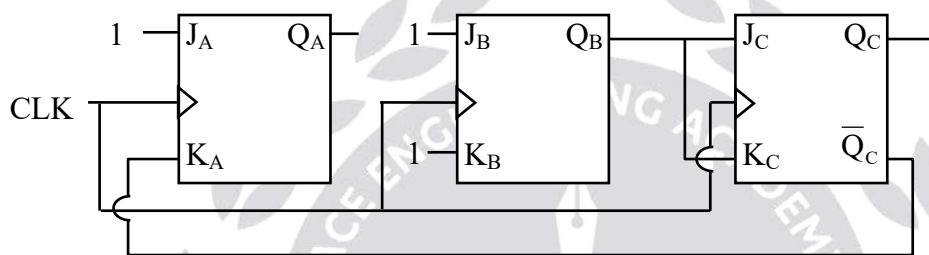


Lock-Out Condition:

P.S.	Inputs						N.S.
$Q_C Q_B Q_A$	J_C	K_C	J_B	K_B	J_A	K_A	$Q_C^+ Q_B^+ Q_A^+$
0 0 0	0	0	1	1	1	1	0 1 1
0 1 1	1	1	1	1	1	1	1 0 0
1 0 0	0	0	1	1	1	0	1 1 1
1 1 0	1	1	1	1	1	0	0 0 1

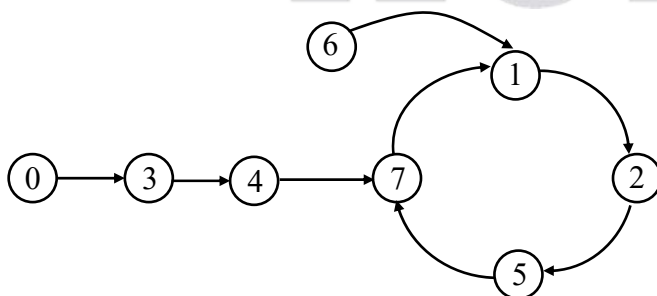Even if the counter starts with 000, there is no problem, the state diagram as follows



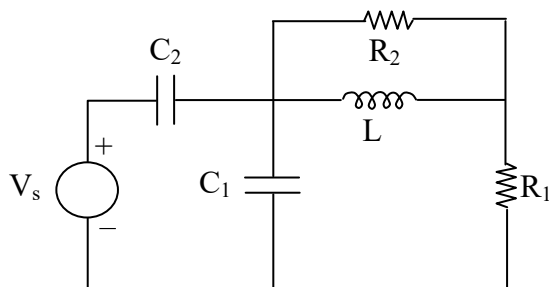07. (a) (i) For the circuit shown, obtain the state equations for $R_1 = R_2 = R$.




(12 M)

(ii) A two-element series circuit is connected across an ac source given by $e(t) = 200\sqrt{2} \sin(314t + 20^\circ)$. The current in the circuit is found to be $i(t) = 10\sqrt{2} \cos(314t - 25^\circ)$. Determine the parameters of the circuit. (8 M)

Sol:

(i)

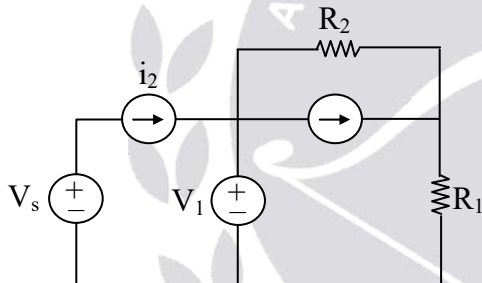


→ Here all voltage loop is formed by voltage source, C_1 and C_2

→ Let V_1 and i_L are the state variables

→ The capacitor C_2 excess element and its voltage $V_2 = [V_s - V_1]$

→ The order of complexity of network = 2

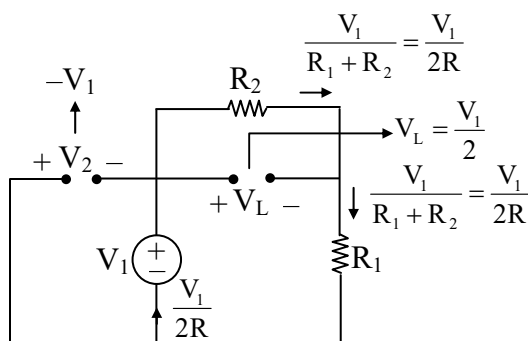

Online Test Series

GATE – 2022

Online Test Series

No. of Tests : **65**

+

Free 52 Practice Tests of
GATE – 2021 Online Test Series

Total Tests : 117

ESE – 2022 Prelims

Online Test Series

No. of Tests : **44**

+

Free 30 Practice Tests of
ESE – 2021 Online Test Series

Total Tests : 74

GATE + ESE – 2022

Online Test Series
Combination Pack

All tests will be available

till GATE – 2022

& ESE – 2022 (Prelims)

examinations respectively.




TEST SERIES HIGHLIGHTS




Detailed Solutions are Available | Video Solutions are Available for Difficult Questions.
All India rank will be given for each test | Comparison with all India toppers of ACE student

TEST WISE STATISTICS:



QUESTION WISE STATISTICS:

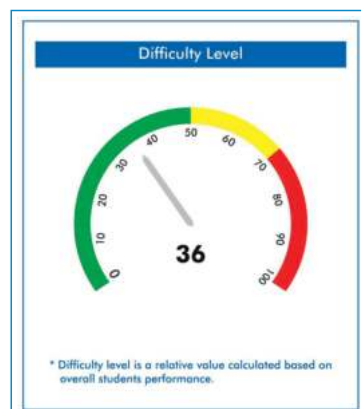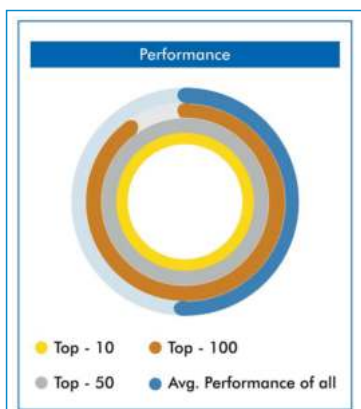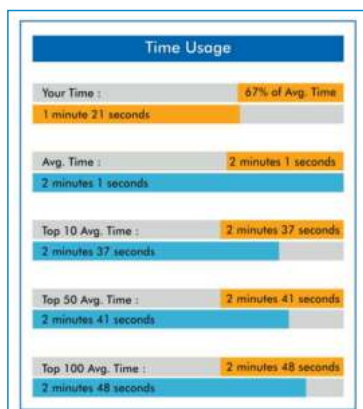

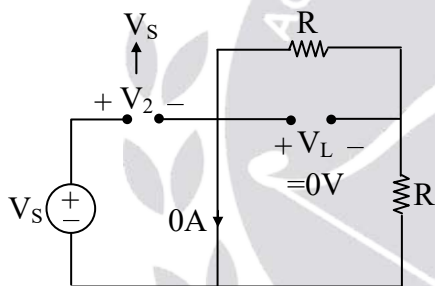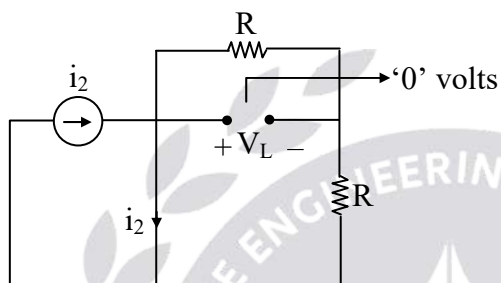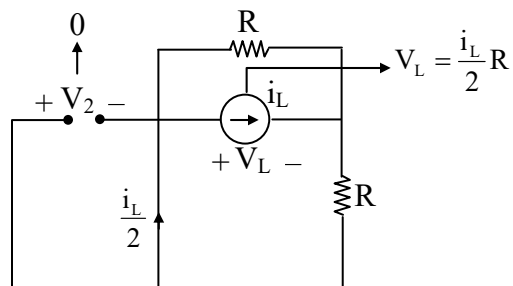

→ Voltage across inductor 'L' is sum of all four voltages

$$L \frac{di_L}{dt} = \frac{V_1}{2} - \frac{R}{2} i_L + 0 + 0$$

→ Also current through 'Ci' is sum of all four currents

$$C_1 \frac{dV_1}{dt} = -\frac{V_1}{2R} - \frac{i_L}{2} + i_2 + 0$$

$$\text{but } i_2 = C_2 \frac{dV_2}{dt} = C_2 \frac{d}{dt} [V_s - V_1]$$

$$i_2 = C_2 \frac{dV_s}{dt} - C_2 \frac{dV_1}{dt}$$

Finally

$$\frac{di_L}{dt} = \frac{V_1}{2L} - \frac{R}{2L} i_L$$

$$\frac{di_L}{dt} = -\frac{R}{2L}i_L + \frac{V_1}{2L} \text{---(A)}$$

$$\frac{dV_1}{dt} = -\frac{i_L}{2C_1} - \frac{V_1}{2RC_1} + \frac{i_2}{C_1} \text{---(B)}$$

$$i_2 = C_2 \frac{dV_s}{dt} - C_2 \frac{dV_1}{dt} \text{---(C)}$$

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dV_1}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R}{2L} & \frac{1}{2L} \\ -\frac{1}{2C_1} & -\frac{1}{2RC_1} \end{bmatrix} \begin{bmatrix} i_L \\ V_1 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{C_1} \end{bmatrix} i_2 \text{---(D)}$$


$$\text{and } i_2 = [C_2 - C_2] \begin{bmatrix} \frac{dV_s}{dt} \\ \frac{dV_1}{dt} \end{bmatrix} \text{---(E)}$$

Substitute (E) in (D)

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dV_1}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R}{2L} & \frac{1}{2L} \\ -\frac{1}{2C_1} & -\frac{1}{2RC_1} \end{bmatrix} \begin{bmatrix} i_L \\ V_1 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{C_1} \end{bmatrix} [C_2 - C_2] \begin{bmatrix} \frac{dV_s}{dt} \\ \frac{dV_1}{dt} \end{bmatrix}$$

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dV_1}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R}{2L} & \frac{1}{2L} \\ -\frac{1}{2C_1} & -\frac{1}{2RC_1} \end{bmatrix} \begin{bmatrix} i_L \\ V_1 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{C_2}{C_1} - \frac{C_2}{C_1} \end{bmatrix} \begin{bmatrix} \frac{dV_s}{dt} \\ \frac{dV_1}{dt} \end{bmatrix}$$

(ii) A two element series circuit

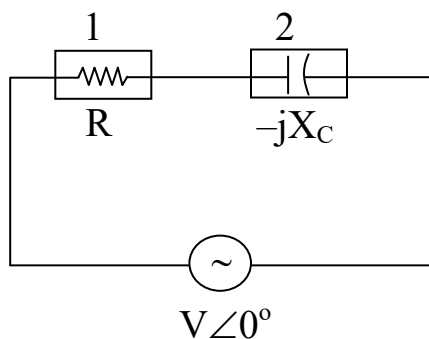

ESE-2022 (Prelims)

OFFLINE TEST SERIES

No. of Tests : **24**

20

Grand Tests

04

Mock Tests

Streams:

EC | EE | CE | ME

Starts from: **27th Nov-2021**

HYDERABAD | DELHI | PUNE

HIGHLIGHTS:

1. Meticulously designed tests series, which maximizes your potentials.
2. All India rank will be given for each test.
3. Detailed solutions will be provided for each test.

Call: 040-48539866, 40136222 | E-mail: testseries@aceenggacademy.com

UPPCL

UTTAR PRADESH POWER
CORPORATION LIMITED

Assistant Engineer (Trainee)

**Online
Test Series**
(EE | CSIT)

Starts from:
1st DEC
2021

No. of Tests: **15**
Subject wise Tests: **13**
Full Length
Mock Tests: **02**

All tests will be available till UPPCL-AE Examination.

Call: 040-48539866, 40136222 | E-mail: testseries@aceenggacademy.com

$$V(t) = 200\sqrt{2} \sin(314t + 20^\circ) \text{V}$$

$$i(t) = 10\sqrt{2} \cos(314t - 25^\circ) \text{A}$$

$$= 10\sqrt{2} \sin(314t - 25^\circ + 90^\circ) \text{A}$$

$$i(t) = 10\sqrt{2} \sin(314t + 65^\circ) \text{A}$$

$$V_t = \frac{200\sqrt{2}}{\sqrt{2}} \angle 20^\circ \text{Volts} \quad i(t) = \frac{10\sqrt{2}}{\sqrt{2}} \angle 65^\circ \text{Amps}$$

$$V = 200 \angle 20^\circ \text{ Volts} \quad I = 10 \angle 65^\circ \text{ Amps}$$

$$Z = \frac{V}{I} = \frac{200 \angle 20^\circ}{10 \angle 65^\circ} = 20 \angle -45^\circ \Omega$$

$$Z = \frac{20}{\sqrt{2}} - j \frac{20}{\sqrt{2}} = (10\sqrt{2} - j10\sqrt{2})$$

$$Z = (14.14 - j14.14) \Omega$$

$$R = 14.14 \Omega$$

$$X_C = \frac{1}{\omega C} = 14.14$$

$$C = \frac{1}{\omega(14.14)} = \frac{1}{(314)(14.14)} = 225.2 \mu\text{F}$$

$$R = 14.14 \Omega, C = 225.2 \mu\text{F}$$

07. (b) (i) A chromel-constantan thermocouple has its cold junction at 0°C. The characteristics of the thermocouple is:

Temp. °C	0	10	20	30	40	50
emf mV	0	0.593	1.191	1.8	2.415	3.02

Find the temperature of the hot junction if the thermoelectric emf is 2.95 mV. (10 M)

(ii) A thermometer, initially at 70°C, is suddenly dipped in a liquid at 300°C. After 3 seconds, the thermometer indicates 200°C. After what time is the thermometer expected to give a reliable reading, say well within 1% of the actual value? (10 M)

Sol:

(i)

Temp - T(°C)	EMF - E (mV)
0	0
10	0.593
20	1.191
30	1.8
40	2.415
50	3.02

To fit the straight line

$$\frac{T - 0}{50 - 0} = \frac{E - 0}{3.02}$$

$$T = \frac{50}{3.02} \times 2.95 \text{ mV}$$

$$T = 48.84^\circ\text{C}$$

(ii) $\theta_0 = 70^\circ\text{C}$

$$\theta_f = 300^\circ\text{C}$$

$$\theta(t) = \theta_f + (\theta_0 - \theta_f)e^{-t/\tau}$$

$$\theta(t) = 300 + (70 - 300)e^{-t/\tau}$$

At $t = 3\text{sec}$ $\theta = 200^\circ\text{C}$

$$200 = 300 + (70 - 300)e^{-3/\tau}$$

$$-100 = -230e^{-3/\tau}$$


$$0.435 = e^{-3/\tau}$$

$$\ln(0.435) = \frac{-3}{\tau}$$

$$\tau = 3.604 \text{ sec}$$


Since a reliable reading can be obtained at 5τ , the required time is $= 5 \times 3.604 \approx 18 \text{ sec}$

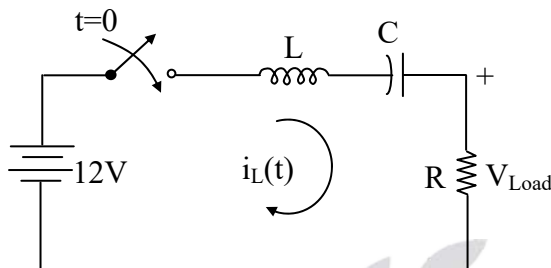07. (c) Find the load voltage as a function of time for the circuit shown in the figure. Assume no energy is stored in the capacitor and inductor before the switch closes. Circuit parameters: $R = 10 \Omega$, $C = 10 \mu\text{F}$, $L = 5 \text{ mH}$.




(20 M)

Sol:

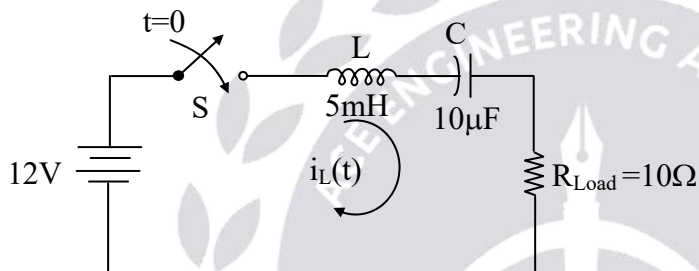

For $t > 0$, 'S' is closed

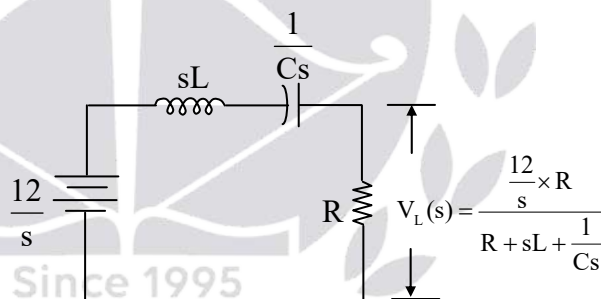

$$V_L(s) = \frac{12RC}{Cs^2 + RCs + 1} = \frac{12 R/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$V_L(s) = \frac{12 \times \frac{10}{5\text{m}}}{s^2 + \frac{10}{5\text{m}}s + \frac{1}{10 \times 10^{-6} \times 5 \times 10^{-3}}} = \frac{24000}{s^2 + 2000s + 20 \times 10^6}$$

$$V_L(s) = \frac{24000}{\sqrt{19} \times 10^3} \left[\frac{\sqrt{19} \times 10^3}{(s + 1000)^2 + 19 \times 10^6} \right]$$

$$V_L(s) = \frac{24}{\sqrt{19}} \left[\frac{\sqrt{19} \times 10^3}{(s + 1000)^2 + \sqrt{19} \times (10^3)^2} \right]$$



POSTAL COACHING

ESE | GATE | PSUs

PSCs

ACE Engineering Academy, the leading institute for GATE, ESE, PSUs and SSC-JE offers postal coaching (Distance learning programme) for engineering students.

ACE PUBLICATIONS




By I.L.T

$$V_L(t) = \frac{24}{\sqrt{19}} e^{-1000t} \sin(\sqrt{19} \times 10^3 t)$$


$$V_L(t) = 5.505 e^{-1000t} \sin 4358.89 t \text{ Volts} \quad t > 0$$

- 08. (a) (i) Design a sawtooth waveform generator shown in the figure below, so that $f_0 = 4 \text{ kHz}$, threshold voltage $V_{TH} = 5 \text{ V}$ and the circuit has a duty cycle of 0.25. Assume $V_{sat} = |-V_{sat}| = 14 \text{ V}$, and $R_1 = 10 \text{ k}\Omega$, $C = 0.01 \mu\text{F}$.**

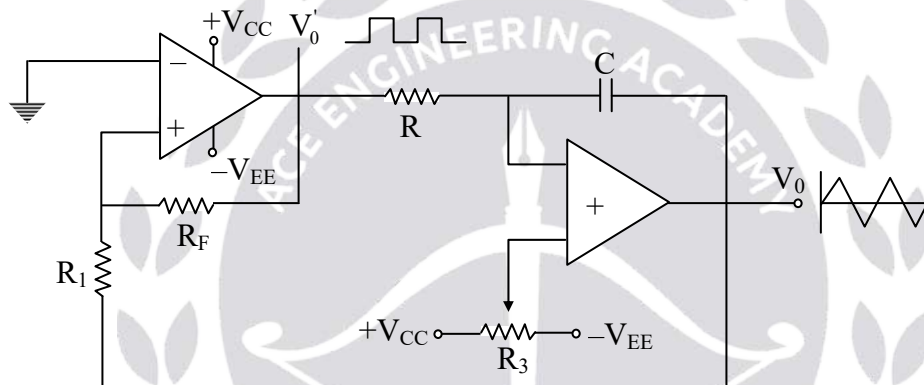

(10 M)

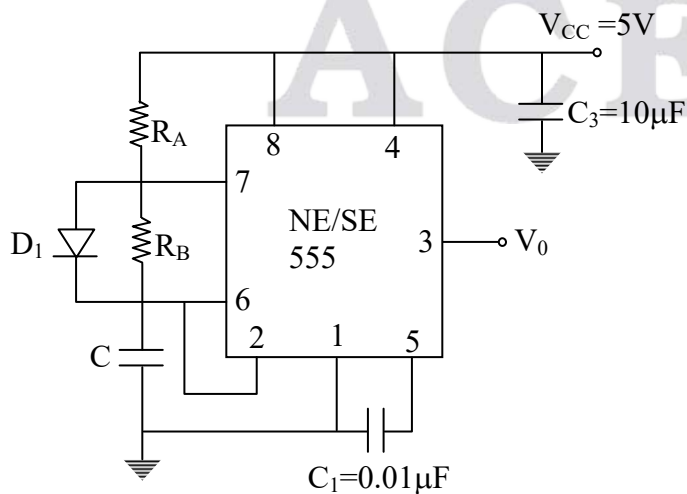- (ii) Design a square wave generator as shown in the figure below, so that duty cycle is 50% and $f_0 = 2.5 \text{ kHz}$. Assume $V_{CC} = 12$ and $C = 0.1 \mu\text{F}$.**



(10 M)

Sol:

- (i) Step-1: Consider the formula for f_0 in a saw tooth waveform generator,

$$f_0 = \frac{R_f}{4RCR_1} \dots\dots(1)$$

$$\Rightarrow R = \frac{R_f}{4f_0CR_1} \dots\dots(2)$$

Step-2: In the Schmitt trigger,

$$\text{Consider } V_{UT} = -V_{LT} = \frac{R_1 V_{sat}}{R_1 + R_f} \dots\dots(3)$$

[\because Duty cycle of saw tooth wave is 0.25 means duty cycle of square wave is 0.5,

$$\text{i.e., } T_1 = \frac{T}{2} = \frac{T}{2}]$$

$$\Rightarrow R_1 + R_f = R_1 \frac{V_{sat}}{V_{Th}} = 10k\Omega \left(\frac{14V}{5V} \right) = 28k\Omega \dots\dots(4)$$

$$\Rightarrow R_f = 28k\Omega - 10k\Omega = 18k\Omega \dots\dots(5)$$


Step-3: Equation(5) in equation(2)

$$R = \frac{18k\Omega}{4.4kHz \times 0.01\mu F \times 10k\Omega} \dots\dots(6)$$

$$= \frac{18k\Omega}{1.6}$$

$$\therefore R = 11.25k\Omega$$

(ii)

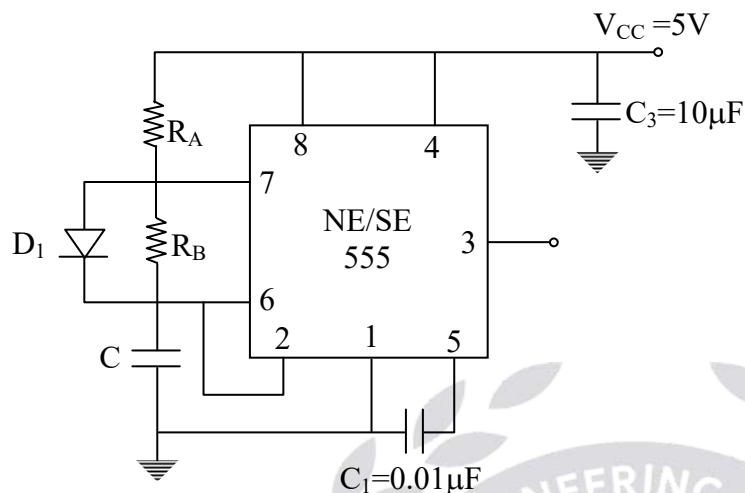

Step (1): During charging period of capacitor

$$T_{\text{charging}} = 0.693 R_A C \quad (1)$$

During discharging period of capacitor,

$$T_{\text{Discharging}} = 0.693 R_B C \quad (2)$$

$$\text{Step (2) Duty cycle, } D = \frac{T_{\text{charging}}}{T_{\text{charging}} + T_{\text{Discharging}}} \quad (3)$$

$$\Rightarrow 0.5 = \frac{0.693 R_A C}{0.693 R_A C + 0.693 R_B C}$$

$$\Rightarrow 0.5 = \frac{R_A}{R_A + R_B}$$

$$\Rightarrow R_A = R_B \quad (4)$$

$$\text{Step (3) counter } f_0 = \frac{1.45}{(R_A + R_B)C} \quad (5)$$

$$\Rightarrow R_A + R_B = \frac{1.45}{2.5\text{kHz} \times 0.1\mu\text{F}}$$

$$\Rightarrow 2R_A = \frac{1.45}{0.25 \times 10^{-3}}$$

$$= 5.8\text{k}\Omega$$

$$\therefore R_A = 2.9\text{k}\Omega \quad (6)$$



We Have Evolved!

DEEP
LEARN

is now



ACE
ONLINE

Our Courses are Available on

► IOS (Mobile/Tab), ► Android (Mobile/Tab), ► Windows (Laptop/Desktop)

Scan QR Cocde to download the APP



Step (4): From equation (4)


$$R_B = R_A = 2.9\text{k}\Omega \quad (7)$$

Step (5): Designed values.

$$R_A = 2.9\text{k}\Omega$$


$$R_B = 2.9\text{k}\Omega$$

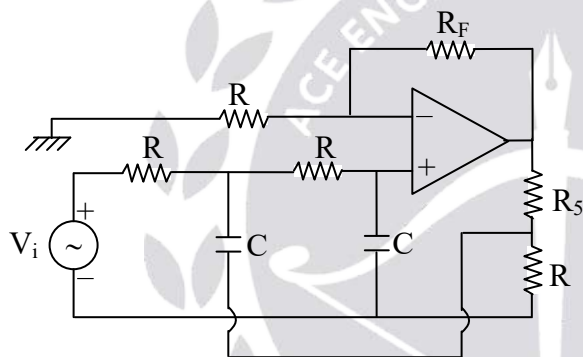- 08. (b) (i) For a second order low pass filter as shown in the figure below, to give a high cutoff frequency of $f_H = f_o = 1 \text{ kHz}$, a pass band gain $K = 4$, $Q = 0.707$ and $C = 0.01 \mu\text{F}$. Calculate resistance R , R_F and R_5 .**



(10 M)

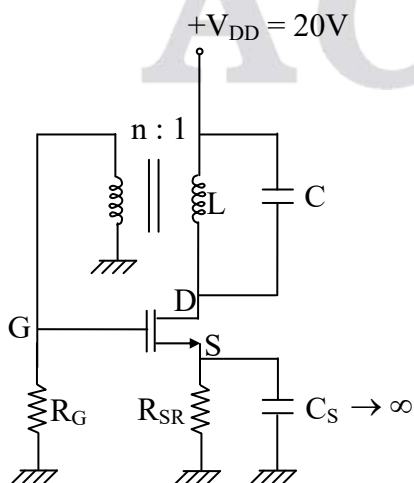- (ii) An LC tuned MOS oscillator is shown in the figure below. Find the value of oscillation frequency and n for $L = 112.6 \mu\text{H}$ and $C = 0.01 \mu\text{F}$. The parameters of the MOSFET are $g_m = 5 \text{ mA/V}$, $r_d = 25 \text{ k}\Omega$ and $R_G = 10 \text{ k}\Omega$.**



(10 M)

Sol:

- (i) For LPF 2nd order, as $Q = 0.707 \Rightarrow$ it is butterworth 2nd order LPF

$$\frac{V_0}{V_i} = \frac{k\omega_c^2}{s^2 + \frac{1}{Q}s\omega_c + \omega_c^2}$$

where $\omega_c = \frac{1}{RC}$

$$\Rightarrow f_c = \frac{1}{2\pi RC} = 1\text{kHz}$$

Given $C = 0.01\mu$

$$\therefore 1k \times 2\pi \times 0.01\mu = \frac{1}{R}$$

$$\therefore R = 16k\Omega$$

Also, $k = 4 = \left[1 + \frac{R_f}{R}\right]$

$$\therefore 3 = \frac{R_f}{R} \Rightarrow R_f = 48k\Omega$$

- (ii) Step (i) consider the general formula for frequency of oscillations in LC tuned oscillator,

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad (1)$$

$$= \frac{1}{2\pi\sqrt{112.6\mu\text{H} \times 0.01\mu\text{F}}}$$

$$= \frac{1}{2\pi \times 1.06 \times 10^{-6}} \text{Hz}$$

$$\therefore f_0 = 0.15\text{MHz or } = 150\text{KHz} \quad (2)$$

Step (2): Consider the general formula for gain $|A_V| = g_m R_L \quad (1)$

where $R_L = r_d // \frac{R_G}{n^2} \quad (2)$

Note: at f_0 , $|g_m R_L| = |A_V| = 1 \quad (3)$

$$\Rightarrow R_L = \frac{1}{g_m} = \frac{1}{5\text{mA/V}} = 200\Omega \quad (4)$$

Step (3): equation (4) in equation (3)

$$R_L = 200\Omega = 25k\Omega // \frac{10k\Omega}{n^2} \text{ _____ (5)}$$

$$\Rightarrow \frac{25k\Omega \left(\frac{10k}{n^2} \right)}{25k\Omega \frac{10k}{n^2}} = 200\Omega$$

$$\Rightarrow \frac{\frac{25k\Omega \times 10k\Omega}{n^2}}{\frac{25k\Omega \times n^2 + 10k\Omega}{n^2}} = 200\Omega \text{ _____ (6)}$$

$$\Rightarrow 250 \times 10^6 \Omega = 5 \times 10^6 n^2 + 2 \times 10^6 = 10^6 (5n^2 + 2) \text{ _____ (7)}$$


$$\Rightarrow 5n^2 = 248$$

$$\Rightarrow n^2 = 49.6 \text{ _____ (8)}$$

$$\therefore n = 7.04 \text{ _____ (9)}$$

08. (c) Draw a 16×8 -bit ROM array, showing all the inputs and outputs. List the types of read-only memories and explain the differences. (20 M)

Sol:

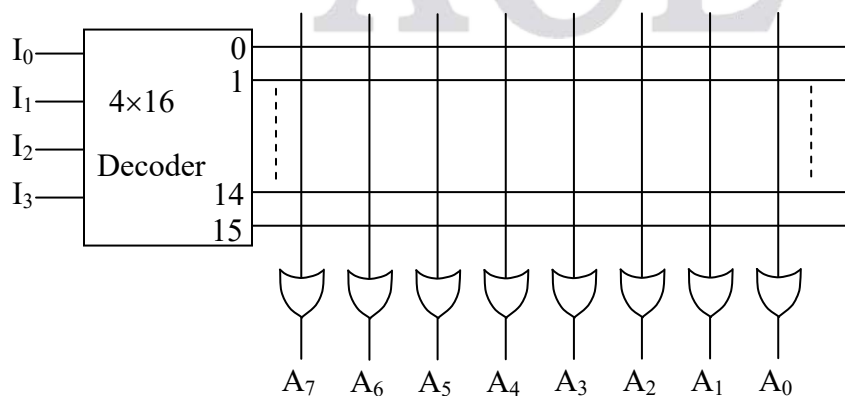

TYPES OF ROMs

Two types of semiconductor technologies are used for the manufacturing of ROM ICs. These are bipolar technology and MOS technology which use bipolar devices and MOS devices respectively. The process of entering information into a ROM is referred to as programming the ROM. Bipolar ROMs and MOS ROMs use different mechanisms of programming. Depending upon the programming process employed, the ROMs are categorized as follows:

Mask programmable read-only memory (MROM)

In this type of read-only memory, the user specifies the data to be stored to the manufacturer of the memory. The data pattern specified by the user are programmed as a part of the fabrication process.

Once programmed, the data pattern can never be changed. This type of read-only memory is referred to as ROM. ROMs are highly suited for very high volume usage due to their low cost.

Programmable read-only memory (PROM)

This type of memory comes from the manufacturer without any data stored in it, i.e. empty. The data pattern is programmed electrically by the user using a special circuit known as PROM programmer. It can be programmed only once during its life time. Once programmed, the data cannot be altered. This type of memory is known as PROM. These are highly suited for high volume usage due to their low cost of production.

Erasable Programmable read-only memory (EPROM)

In this type of memory, data can be written any number of times, i.e. they are reprogrammable. Before it is reprogrammed, the contents already stored are erased by exposing the chip to ultraviolet radiation for about 30 minutes. This type of memory is referred to as EPROM. EPROMs are possible only in MOS technology. Programming is done using a PROM programmer.

Electrically erasable and programmable read-only memory (EEPROM or E²ROM)

This is another type of reprogrammable memory in which erasing is done electrically rather than exposing the chip to the ultraviolet radiation. It is referred to as EEPROM or electrically alterable ROM (EAROM).

Hearty Congratulations to our

ESE - 2020 TOP RANKERS



CHARUDATTA S ME



SHASHANK GAUR EE



PRAKASH JHA E&T



GAURAV KUMAR CE



K S SHARADRAO ME



ABHISHEK SINGH EE



PARTH BATRA E&T



PRASHANT SINGH CE



SURAJ KUMAR S ME



VIKASH SHANKAR EE



RAHUL NAREDI E&T



KULDEEP JANGRA CE



SHUBHAM B ME



ANUPAM S EE



SHUBHAM E&T



ANISH BAGGA CE



KAMLESH PARWAR ME



MANOJ KUMAR E&T



PAVITRA GOYAL CE



MD ZUHAIB ME



VISHWA SIMHAA EE



SAURAV KUMAR S E&T



PRATEEK S ME



DINESH KUMAR S EE



RAGHAV PURWAR E&T



V SAIKRISHNA REDDY ME



GAGAN GHUNAWAT EE



RAM KRISHNA E&T



GANESH KUMAR A ME



AKSHAY KUMAR T EE



CHHAVI JAIN E&T



ARPIT JAIN CE



HEMABH TRIVEDI ME



RAJAT DIXIT EE



L KUMARI JAISWAL E&T



AMIT SHARMA CE

and many more...

TOTAL 36 RANKS IN TOP 10

ME 10

EE 09

E&T 10

CE 07