




GATE | PSUs

ELECTRICAL ENGINEERING

Digital Electronics

 Text Book: Theory with worked out Examples
and Practice Questions



Chapter 1 Number Systems

(Solutions for Text Book Practice Questions)

01. Ans: (d)

Sol: $135_x + 144_x = 323_x$

$$(1 \times x^2 + 3 \times x^1 + 5 \times x^0) + (1 \times x^2 + 4 \times x^1 + 4 \times x^0) = 3x^2 + 2x^1 + 3x^0$$

$$\Rightarrow x^2 + 3x + 5 + x^2 + 4x + 4 = 3x^2 + 2x + 3$$

$$x^2 - 5x - 6 = 0$$

$$(x-6)(x+1) = 0 \quad (\text{Base cannot be negative})$$

Hence $x = 6$.

(OR)

As per the given number x must be greater than 5. Let consider $x = 6$

$$(135)_6 = (59)_{10}$$

$$(144)_6 = (64)_{10}$$

$$(323)_6 = (123)_{10}$$

$$(59)_{10} + (64)_{10} = (123)_{10}$$

So that $x = 6$

02. Ans: (a)

Sol: 8-bit representation of

$$+127_{10} = 01111111_{(2)}$$

1's complement representation of

$$-127 = 10000000.$$

2's complement representation of

$$-127 = 10000001.$$

No. of 1's in 2's complement of

$$-127 = m = 2$$

No. of 1's in 1's complement of

$$-127 = n = 1$$

$$\therefore m:n = 2:1$$

03. Ans: (c)

Sol: In 2's complement representation the sign bit can be extended towards left any number of times without changing the value. In given number the sign bit is 'X₃', hence it can be extended left any number of times.

04. Ans: (c)

Sol: Binary representation of $+(539)_{10}$:

2	539	
2	269 -1	
2	134 -1	
2	67 -0	
2	33 -1	
2	16 -1	
2	8 -0	
2	4 -0	
2	2 -0	
	1 -0	

$$(+539)_{10} = (10000\ 11\ 0\ 11)_2 = (00100\ 0011011)_2$$

$$\text{2's complement} \rightarrow 110111100101$$

$$\text{Hexadecimal equivalent} \rightarrow (DE5)_H$$

05. Ans: 5

Sol: Symbols used in this equation are 0,1,2,3
Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0)(x+3x^0+x^{-1})$$

$$3x^2 + x + 2 = (2x) \left(x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$x(x-5) = 0$$

$$x = 0(\text{or}) x = 5$$

$$x \text{ must be } x > 3, \text{ So } x = 5$$

06. Ans: 3
Sol: $123_5 = x8_y$

$$1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0 = x \cdot y^1 + 8 \times y^0$$

$$25 + 10 + 3 = xy + 8$$

$$\therefore xy = 30$$

Possible solutions:

i. $x = 1, y = 30$

ii. $x = 2, y = 15$

iii. $x = 3, y = 10$

 $\therefore$ 3 possible solutions exists.

07. Ans: 1
Sol: The range (or) distinct values

For 2's complement $\Rightarrow -(2^{n-1})$ to $+(2^{n-1}-1)$

For sign magnitude

$$\Rightarrow -(2^{n-1}-1) \text{ to } +(2^{n-1}-1)$$

 Let $n = 2 \Rightarrow$ in 2's complement

$$-(2^{2-1}) \text{ to } +(2^{2-1}-1)$$

$$-2 \text{ to } +1 \Rightarrow -2, -1, 0, +1 \Rightarrow X = 4$$

$$n = 2 \text{ in sign magnitude} \Rightarrow -1 \text{ to } +1 \Rightarrow Y = 3$$

$$X - Y = 1$$

08. Ans: (a, b & c)
Sol: (a) When we have 10 base then we have (0 - 9) number.

when we have 16 base then we have (0 - 15) number.

when we have 8 base then we have (0 - 7) number.

 So, this is correct statement as the longest digit decimal value is $(k - 1)$ in base k system

(b) This is also true because as an example $10 \rightarrow$ We borrow k as a significant digit

$$(86)_{10}$$

$$-(79)_{10}$$

$$(06)_{10}$$

(c) This statement is also true and have easy conversion as well as it has highest number of bits.

(d) Direct conversion is possible between binary & octal number system

$$\text{ex: } 100111 \\ \quad \quad \quad \underbrace{\quad\quad\quad}_{(47)_8}$$

Chapter 2 Logic Gates & Boolean Algebra

01. Ans: (c)

Sol: Given 2's complement numbers of sign bits are x & y. z is the sign bit obtained by adding above two numbers. $\therefore$ Overflow is indicated by $= \bar{x}\bar{y}z + x y \bar{z}$

Examples

1. A = +7 0111
B = +7 0111
14 1110 $\Rightarrow \bar{x}\bar{y}z$
2. A = +7 0111
B = +5 0101
12 1100 $\Rightarrow \bar{x}\bar{y}z$
3. A = -7 1001
B = -7 1001
-14 10010 $\Rightarrow x y \bar{z}$
4. A = -7 1001
B = -5 1011
-12 10100 $\Rightarrow x y \bar{z}$

02. Ans: (b)

Sol: Truth table of XOR

A	B	o/p
0	0	0
0	1	1
1	0	1
1	1	0

Stage 1:

Given one i/p = 1 Always.

1	X	o/p	
1	0	1	$= \bar{X}$
1	1	0	$= X$

For First XOR gate o/p = $\bar{X}$

Stage 2:

$\bar{X}$	X	o/p
0	1	1
1	0	1

For second XOR gate o/p = 1.


Similarly for third XOR gate o/p = $\bar{X}$ & for fourth o/p = 1

For Even number of XOR gates o/p = 1

For 20 XOR gates cascaded o/p = 1.

03. Ans: (b)


Sol:

 

Number of min terms = 20

04. Ans: (c)

Sol:

 



$$x = f_1 f_2$$

$$f_4 = f_1 \cdot f_2 + f_3$$

$$f_2 = \sum m(6, 8)$$

05. Ans: (d)

 

 

06. Ans: (c)

Sol: $\overline{x_1} \oplus \overline{x_3} = \overline{x_1} x_3 + x_1 \overline{x_3} = y$

$\overline{x_2} \oplus \overline{x_4} = \overline{x_2} x_4 + x_2 \overline{x_4} = z$

$(\overline{x_1} \oplus \overline{x_3}) \oplus (\overline{x_2} \oplus \overline{x_4})$

$= y \oplus z = 0, \text{ when } y = z$

$\therefore$ option (c) is true

For all cases option A, B, D not satisfy.

07. Ans: (b)

Sol: $M(a,b,c) = ab + bc + ca$

$\overline{M(a,b,c)} = \overline{bc} + \overline{ab} + \overline{ac}$

$M(a, \overline{b}, \overline{c}) = ab + b\overline{c} + \overline{c}a$

$M(\overline{M(a,b,c)}, M(a,b,\overline{c}), c)$

$= (\overline{bc} + \overline{ab} + \overline{ac})(ab + b\overline{c} + \overline{c}a)$
 $+ (ab + b\overline{c} + \overline{c}a)c + (\overline{bc} + \overline{ab} + \overline{ac})c$

$= (\overline{bc} + \overline{ab} + \overline{ac})(ab + b\overline{c} + \overline{c}a)$

$+ (\overline{bc} + \overline{ab} + \overline{ac})(c) + abc$

$= a\overline{b}\overline{c} + \overline{a}b\overline{c} + abc + \overline{a}\overline{b}c$

$= \overline{c}[a\overline{b} + \overline{a}b] + c[ab + \overline{a}\overline{b}]$


$= \sum m(1, 2, 4, 7)$

$\therefore M(x, y, z) = a \oplus b \oplus c$

Where $x = \overline{M(a,b,c)}$, $y = M(a,b,\overline{c})$, $z = c$

08. Ans: 40

Sol:

 

$\therefore Z$ is 1 for 40 nsec

09. Ans: (c)

Sol: Logic gates $\overline{X} + Y = \overline{X\overline{Y}} = \overline{X}Y_1$


Where $Y_1 = \overline{Y}$

It is a NAND gate and thus the gate is 'Universal gate'.

10. Ans: (a & d)

Sol: (a) is correct because stair case operation is performed with ex-OR gate.

 (d) 4 number of 2 input NOR gates are sufficient to implement 2-input Ex-NOR gate.




A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Chapter 3

K - Maps


01. Ans: (b)

Sol:

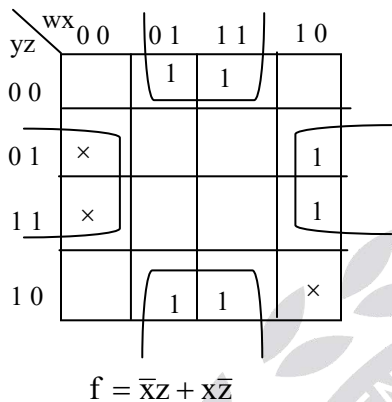



02. Ans: (b)

Sol:

 

03.

Sol:

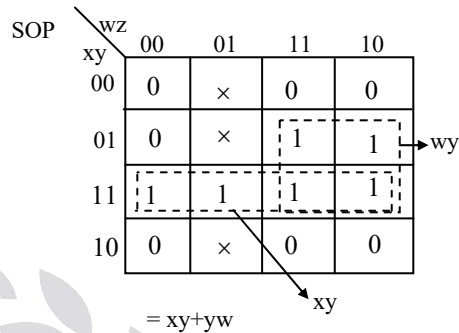 

SOP: $x y + y w$

POS: $y(x + w)$

04. Ans: (a)

Sol: For n-variable Boolean expression,


Maximum number of minterms = 2^n

Maximum number of implicants = 2^n

Maximum number of prime implicants = $\frac{2^n}{2}$
 $= 2^{n-1}$

05. Ans: (c)

Sol:

 

06. Ans: 1

Sol: After minimization = $(\bar{A} + \bar{B} + \bar{C} + \bar{D})$

$= ABCD$

$\therefore$ only one minterm.

07. Ans: 3
Sol: $\bar{w}\bar{z} + \bar{w}xy + \bar{x}y\bar{z}$

		yz			
wx		00	01	11	10
	00	1			1
	01	1	1		1
	11				
	10				1


∴ Total number of prime implicants of the function 'f' is 3.

08. Ans: (a, b & c)
Sol: (d) is incorrect because resultant term will have 1 literal after grouping 8 number of cells.

Ex:

		cd			
ab		00	01	11	10
	00			1	1
	01			1	1
	11			1	1
	10			1	1

$f = c$ Only 1 literals

 

Chapter 4 Combinational Circuits

01. Ans: (d)

Sol: Let the output of first MUX is “F₁”

$$F_1 = AI_0 + AI_1$$

Where A is selection line, I₀, I₁ = MUX Inputs

$$F_1 = \bar{S}_1 \cdot W + S_1 \cdot \bar{W} = S_1 \oplus W$$

Output of second MUX is

$$F = \bar{A} \cdot I_0 + A \cdot I_1$$

$$F = \bar{S}_2 \cdot F_1 + S_2 \cdot \bar{F}_1$$

$$F = S_2 \oplus F_1$$


$$\text{But } F_1 = S_1 \oplus W$$

$$F = S_2 \oplus S_1 \oplus W$$

$$\text{i.e., } F = W \oplus S_1 \oplus S_2$$


02. Ans: 50

Sol:

 


Initially all the output values are ‘0’, at $t = 0$, the inputs to the 4-bit adder are changed to $X_3X_2X_1X_0 = 1100$, $Y_3Y_2Y_1Y_0 = 0100$


 
----- indicates critical path delay to get the output



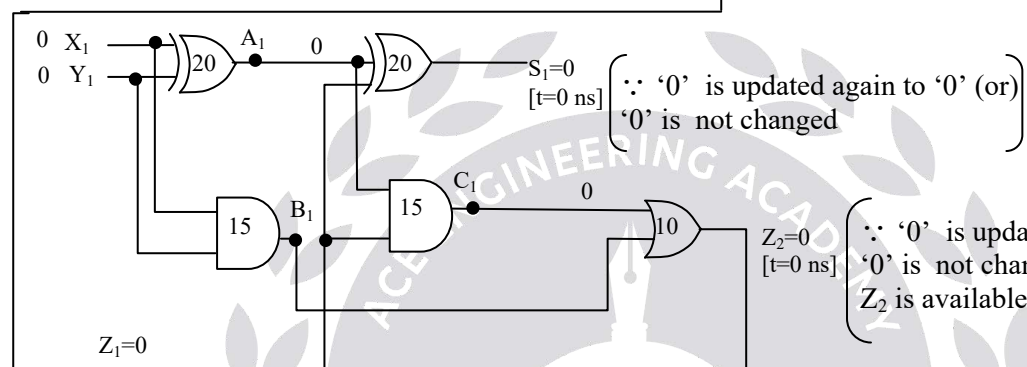$\therefore$ '0' is updated again to '0' (or)
'0' is not changed, i.e.
 Z_1 is available @ $t=0$ ns



  $\therefore$ '0' is updated again to '0' (or)
'0' is not changed, i.e.
 Z_2 is available @ $t=0$ ns



Total time taken = $\Delta t_1 + \Delta t_2 = 50$ ns

i.e. critical time (or) maximum time is taken for Z_4 to get final output as '1'

03. Ans: (a)

Sol: The given circuit is binary parallel adder/subtractor circuit. It performs $A+B$, $A-B$ but not $A + 1$ operations.

K	C ₀	Operation
0	0	$A+B$ (addition)
0	1	$A+B+1$ (addition with carry)
1	0	$A+\bar{B}$ (1's complement addition)
1	1	$A+\bar{B}+1$ (2's complement subtraction)

04. Ans: (d)

Sol: It is expansion of 2:4 decoders to 1:8 demultiplexer A_1, A_0 must be connected to S_1, S_0 i.e., $R = S_0, S = S_1$

Q must be connected to S_2 i.e., $Q = S_2$

P is serial input must be connected to D_{in}

05. Ans: 6

Sol: $T = 0 \rightarrow \text{NOR} \rightarrow \text{MUX 1} \rightarrow \text{MUX 2}$

2ns 1.5ns 1.5ns

Delay = $2\text{ns} + 1.5\text{ns} + 1.5\text{ns} = 5\text{ns}$

$T = 1 \rightarrow \text{NOT} \rightarrow \text{MUX 1} \rightarrow \text{NOR} \rightarrow \text{MUX 2}$

1ns 1.5ns 2ns 1.5ns

Delay = $1\text{ns} + 1.5\text{ns} + 2\text{ns} + 1.5\text{ns} = 6\text{ns}$

Hence, the maximum delay of the circuit is 6ns.

06. Ans: -1

Sol: When all bits in 'B' register is '1', then only it gives highest delay.


$\therefore$ '-1' in 8 bit notation of 2's complement is 1111 1111.

07. Ans: (b & c)


Sol: (a) It is incorrect because for getting $\bar{B}$ is $(A+B) = \bar{A}\bar{B}$

we need one more 2×1 MUX

(b) It is correct

 

 (c) It is correct we need minimum 2 number of 2×1 muxes for implementing 2 input exnor gate



(d) It is incorrect because one 16×1 MUX is sufficient for all 4 variable function.


Chapter 5 Sequential Circuits

01. Ans: (c)

Sol: Given Clk, X_1 , X_2

Output of First D-FF is Q_1

Output of Second D-FF is Q_2

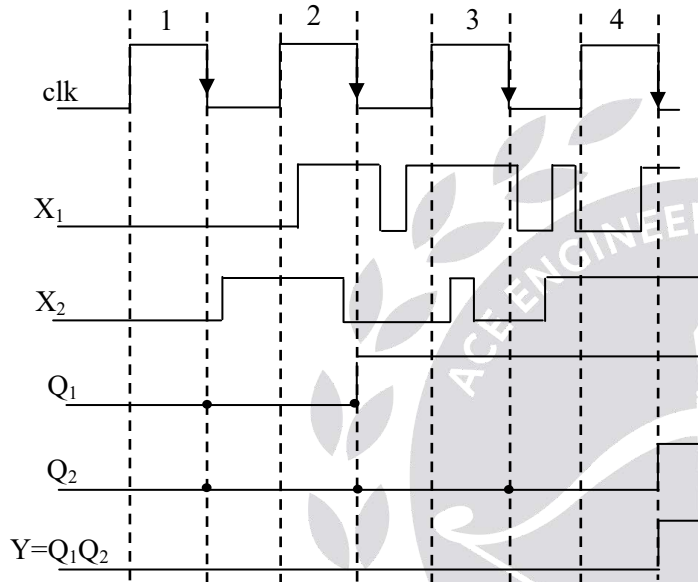

02. Ans: 4

Sol: In the given first loop of states, zero has repeated 3 times. So, minimum 4 number of Flip-flops are needed.

03. Ans: 7

Sol: The counter is cleared when $Q_D Q_C Q_B Q_A = 0110$

Clk	Q_D	Q_C	Q_B	Q_A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	0	0	0

As the clear input is given to be synchronous so it waits upto the next clock pulse to clear the counter & hence the counter get's cleared during the 7th clock pulse.

$\therefore$ mod of counter = 7


04. Ans: (b)

Sol: The given circuit is a mod 4 ripple down counter. Q_1 is coming to 1 after the delay of $2\Delta t$.

CLK	Q_1	Q_0
	0	0
1	1	1
2	1	0
3	0	1
4	0	0

05. Ans: (c)

Sol: Assume $n = 2$

 

Outputs of counter is connected to inputs of decoder

Counter outputs		Decoder inputs		Decoder outputs			
Q_1	Q_0	a	b	d_3	d_2	d_1	d_0
0	0	0	0	0	0	0	1
0	1	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0

The overall circuit acts as 4-bit ring counter $n = 2$

$\therefore k = 2^2 = 4$, k-bit ring counter

06. Ans: (b)

Sol:

CLK	Serial in= $B \oplus C \oplus D$	A B C D
0		1 0 1 0
1	1 $\longrightarrow$	1 1 0 1
2	0 $\longrightarrow$	0 1 1 0
3	0 $\longrightarrow$	0 0 1 1
4	0 $\longrightarrow$	0 0 0 1
5	1 $\longrightarrow$	1 0 0 0
6	0 $\longrightarrow$	0 1 0 0
7	1 $\longrightarrow$	1 0 1 0

$\therefore$ After 7 clock pulses content of shift register become 1010 again.

07. Ans: (b)

Sol:

J	K	Q	$\bar{Q}_n$	$T = (J + Q_n)(K + \bar{Q}_n)$	Q_{n+1}
0	0	0	1	$0.1 = 0$	0
0	0	1	0	$1.0 = 0$	1
0	1	0	1	$0.1 = 0$	0
0	1	1	0	$1.1 = 1$	0
1	0	0	1	$1.1 = 1$	1
1	0	1	0	$1.0 = 0$	1
1	1	0	1	$1.1 = 1$	1
1	1	1	0	$1.1 = 1$	0

J	$\bar{K}Q_n$	00	01	11	10
0				1	
1		1		1	1


$$T = J \bar{Q}_n + KQ_n = (J + Q_n)(K + \bar{Q}_n)$$

08. Ans: 1.5

Sol:

Clk	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Y = Q ₃ + Q ₅
0	0	1	0	1	0	0
1	0	0	1	0	1	1
2	1	0	0	1	0	0
3	0	1	0	0	1	1
4	1	0	1	0	0	1
5	0	1	0	1	0	0

 The waveform at OR gate output, Y is [A = +5V]



Average power

$$P = \frac{V_{Ao}^2}{R} = \frac{1}{R} \left[\lim_{T_1 \rightarrow \infty} \frac{1}{T_1} \int_0^{T_1} y^2(t) dt \right] = \frac{1}{RT_1} \left[\int_T^{2T} A^2 dt + \int_{3T}^{5T} A^2 dt \right]$$

$$= \frac{A^2}{RT_1} [(2T - T) + (5T - 3T)] = \frac{A^2 \cdot 3T}{R(5T)} = \frac{5^2 \cdot 3}{10 \times 5} = 1.5 \text{ mW}$$

09. Ans: (b & d)

Sol: (a) It is incorrect statement ripple counter is slower than synchronous counter is apply with 1 clock.

(b) It is correct statement because mod counters means it counts the number of clock pulses arriving at its clock input, which is basically we do in electronic time clocks.

(c) It is incorrect, because with the help of positive edge triggered JK-flip-flop we design binary down counter.

(d) It is correct statement because D-flipflop is easy to design and easy to get the next possible state output.



Chapter 6 A/D & D/A Converters


01. Ans: (b)

Sol:

CLK	Counter			Decoder				V ₀
	Q ₂	Q ₁	Q ₀	D ₃	D ₂	D ₁	D ₀	
1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	1
3	0	1	0	0	0	1	0	2
4	0	1	1	0	0	1	1	3
5	1	0	0	1	0	0	0	8
6	1	0	1	1	0	0	1	9
7	1	1	0	1	0	1	0	10
8	1	1	1	1	0	1	1	11

02. Ans: (b)

Sol:

 

$$R_{\text{equ}} = (((((2R \parallel 2R) + R) \parallel 2R) + R) \parallel 2R) + R \parallel 2R$$

$$R_{\text{equ}} = R = 10\text{k}\Omega.$$

$$I = \frac{V_R}{R} = \frac{10\text{V}}{10\text{k}} = 1\text{mA}.$$

$$\begin{aligned} \text{Current division at } \frac{I}{16} \\ = \frac{1 \times 10^{-3}}{16} = 62.5 \mu\text{A} \end{aligned}$$

03. Ans: (c)

Sol: Net current at inverting terminal,

$$I_i = \frac{I}{4} + \frac{I}{16} = \frac{5I}{16}$$

$$\begin{aligned} V_0 &= -I_i R = -\frac{5I}{16} \times 10\text{k}\Omega \\ &= \frac{-5 \times 1 \times 10^{-3} \times 10 \times 10^3}{16} = -3.125\text{V} \end{aligned}$$

04. Ans: (d)

Sol: Given that $V_{\text{DAC}} = \sum_{n=0}^3 2^{n-1} b_n$ Volts

$$V_{\text{DAC}} = 2^{-1} b_0 + 2^0 b_1 + 2^1 b_2 + 2^2 b_3$$

$$\Rightarrow V_{\text{DAC}} = 0.5b_0 + b_1 + 2b_2 + 4b_3$$

Initially counter is in 0000 state

Up counter o/p				V _{DAC} (V)	o/p of comparator
b ₃	b ₂	b ₁	b ₀		
0	0	0	0	0	1
0	0	0	1	0.5	1
0	0	1	0	1	1
0	0	1	1	1.5	1
0	1	0	0	2	1
0	1	0	1	2.5	1
0	1	1	0	3	1
0	1	1	1	3.5	1
1	0	0	0	4	1
1	0	0	1	4.5	1
1	0	1	0	5	1
1	0	1	1	5.5	1
1	1	0	0	6	1
1	1	0	1	6.5	0

When $V_{\text{DAC}} = 6.5$ V, the o/p of comparator is '0'. At this instant, the clock pulses to the counter are stopped and the counter remains in 1101 state.

$\therefore$ The stable reading of the LED display is 13.

05. Ans: (b)

Sol: The magnitude of error between V_{DAC} & V_{in} at steady state is $|V_{DAC} - V_{in}| = |6.5 - 6.2|$
 $= 0.3 \text{ V}$

06. Ans: (a)

Sol: In Dual slope

$$ADC \Rightarrow V_{in} T_1 = V_R \cdot T_2$$

$$\Rightarrow V_{in} = \frac{V_R T_2}{T_1}$$

$$= \frac{100 \text{ mV} \times 370.2 \text{ ms}}{300 \text{ ms}}$$

DVM indicates = 123.4

07. Ans: (d)

Sol: Ex: $f_{in} = 1 \text{ kHz} \rightarrow f_s = 2 \text{ kHz}$

$$f_{in} = 25 \text{ kHz} \leftarrow f_s = 50 \text{ kHz}$$

$$1. \text{ Max conversion time} = 2^{N+1} T = 2^{11} \cdot 1 \mu\text{s} = 2048 \mu\text{s}$$

$$2. \text{ Sampling period} = T_s \geq \text{maximum conversion time}$$

$$T_s \geq 2048 \mu\text{s}$$

$$3. \text{ Sampling rate } f_s = \frac{1}{T_s} \leq \frac{1}{2048 \times 10^{-6}}$$

$$f_s \leq 488 \quad f_s \leq 500 \text{ Hz}$$

$$4. f_{in} = \frac{f_s}{2} = 250 \text{ Hz}$$

08. Ans: (d)

Sol: In an ADC along with S-H circuit (sample and hold) circuit, to avoid error at output, voltage across capacitor should not drop by more than $\pm \Delta/2$, where Δ is step size.

$$\text{Here, } \Delta = \frac{10 - 0}{(2^{10} - 1)} = 9.775 \times 10^{-3} \text{ V}$$

$$\text{Hence } \frac{\Delta}{2} = 4.8875 \times 10^{-3} \text{ V}$$

So conversion time (maximum) should be such that the drop across capacitor voltage must reach maximum value $\Delta/2$.

Hence, time taken for this

$$t = \frac{\Delta/2}{\text{droprate}} = \frac{4.8875 \times 10^{-3}}{10^{-4} \text{ V/msec}}$$

$$t \cong 49 \text{ msec}$$

09. Ans: (b & d)

Sol: (a) It is incorrect, minimum number of comparator required in 'n' bit flash ADC is $2^n - 1$.

(b) It is correct (no register/counter required in flash ADC, only comparator required).

(c) It is incorrect,

$$\text{Conversion time of SAR} = n T_{\text{clk}}$$

Conversion time of Dual Slope ADC

$$= (2^{n+1}) T_{\text{clk}}$$

SAR faster than Dual slope ADC.

(d) It is correct, because it compares DAC output with analog voltage & does the same till both are equal in magnitude. At this moment counter will stop. Maximum conversion time is equal to $(2^{n+1}) T_{\text{clk}}$ of n-bit ADC. The conversion time depends on analog input voltage as well as on size of ADC.