



**GATE | PSUs**

# **INSTRUMENTATION ENGINEERING**

**Electrical Circuits and Machines**

(Text Book: Theory with worked out Examples and  
Practice Questions)



# Chapter 1 Basic Concepts


(Solutions for Text Book Practice Questions)

01. Ans: (c)

Sol: We know that;

$$i(t) = \frac{dq(t)}{dt}$$

$$dq(t) = i(t) \cdot dt$$

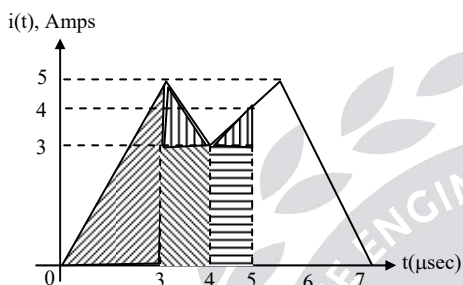

$$q = \int_0^{5 \mu\text{sec}} i(t) dt = \text{Area under } i(t) \text{ upto } 5 \mu\text{sec}$$


$$q = q_1 + q_2 + q_3$$

$$= \left(\frac{1}{2} \times 3 \times 5\right) + \left(\frac{1}{2} \times 1 \times 2 + (1 \times 3)\right) + \left(\frac{1}{2} \times 1 \times 1 + (1 \times 3)\right)$$

$$q = 15 \mu\text{C}$$

02. Ans: (a)

Sol:

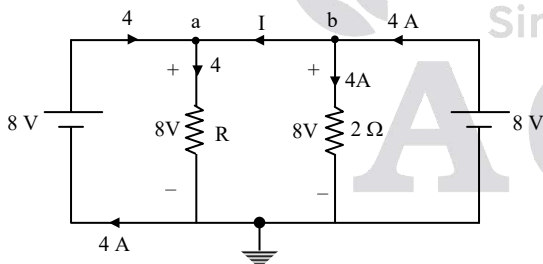

Applying KCL at node 'b'

$$I + 4 = 4$$

$$\Rightarrow I = 0\text{A}$$

And  $\frac{8}{R} = 4$

$$\Rightarrow R = 2\Omega$$

03. Ans: (a)

Sol: The energy stored by the inductor ( $1\Omega$ ,  $2\text{H}$ ) upto first 6 sec:

$$E_{\text{stored upto 6 sec}} = \int_0^6 P_L dt = \int_0^6 v_L(t) i_L(t) dt$$

$$= \int \left( L \frac{di(t)}{dt} \cdot i(t) \right) dt$$

$$= \int_0^2 \left( 2 \left[ \frac{d}{dt} (3t) \right] \times 3t \right) dt + \int_2^4 \left( 2 \left[ \frac{d}{dt} (6) \right] \times 6 \right) dt$$

$$+ \int_4^6 \left( 2 \left[ \frac{d}{dt} (-3t + 18) \right] \times (-3t + 18) \right) dt$$

$$= \int_0^2 18t dt + \int_2^4 0 dt + \int_4^6 (-6[-3t + 18]) dt$$

$$= 36 + 0 - 36 = 0 \text{ J}$$

(or)

$$E_{\text{stored upto 6 sec}} = E_L |_{t=6 \text{ sec}}$$

$$= \frac{1}{2} L (i(t) |_{t=6})^2$$

$$= \frac{1}{2} \times 2 \times 0^2 = 0 \text{ J}$$

04. Ans: (d)

Sol: The energy absorbed by the inductor ( $1\Omega$ ,  $2\text{H}$ ) upto first 6sec:

$$E_{\text{absorbed}} = E_{\text{dissipated}} + E_{\text{stored}}$$

Energy is dissipated in the resistor

$$E_{\text{dissipated}} = \int P_R dt = \int (i(t))^2 R dt$$

$$= \int_0^2 (3t)^2 \times 1 dt + \int_2^4 (6)^2 \times 1 dt + \int_4^6 (-3t + 18)^2 \times 1 dt$$

$$= \int_0^2 9t^2 dt + \int_2^4 36 dt + \int_4^6 (9t^2 + 324 - 108t) dt$$

$= 24 + 72 + 24$

$= 120J$

$\therefore E_{\text{dissipated}} = 120 J$


And  $E_{\text{stored upto 6 sec}} = 0J$

$\therefore E_{\text{absorbed}} = E_{\text{dissipated}} + E_{\text{stored}}$

$\Rightarrow E_{\text{absorbed}} = 120J + 0J = 120J$

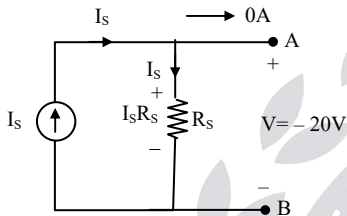**05. Ans: (a)**

**Sol:** Point  $(-20, 0) \Rightarrow V = -20V$  and  $I = 0A$




By KVL  $\Rightarrow I_s R_s - V = 0$

$\Rightarrow I_s R_s + 20 = 0$

$\Rightarrow I_s R_s = -20V \dots\dots\dots (1)$

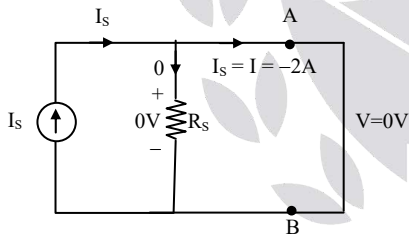Point:  $(0, -2) \Rightarrow V = 0V$  and  $I = -2A$




$I_s = I$

$\Rightarrow I_s = -2A$

Substituting  $I_s$  in eq. (1)

$R_s = 10\Omega$

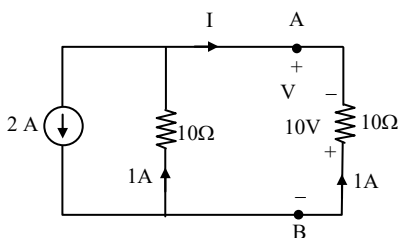


From the diagram;

$I = -1A$  and  $V = -10V$

**06. Ans: (a)**


**Sol:**

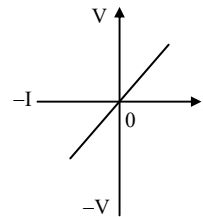

- \* linear
- \* Passive
- \* bilateral

**07. Ans: (b)**


**Sol:**

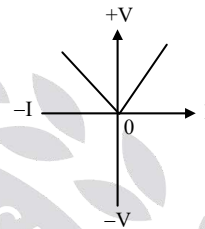

- \* Non linear
- \* Active
- \* Unilateral

**08. Ans: (e)**


**Sol:**

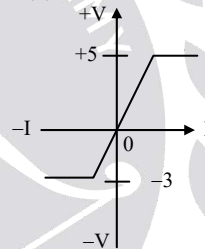

- \* Non linear
- \* Passive
- \* Unilateral

**09. Ans: (c)**


**Sol:**

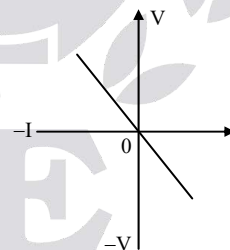

- \* Linear
- \* Active
- \* Bilateral

**10.**

**Sol:**

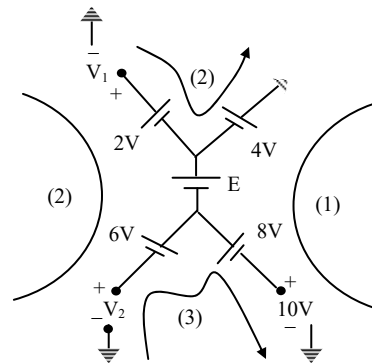

(1) By KVL  $\Rightarrow + 10 + 8 + E + 4 = 0$

$E = -22V$

(2) By KVL  $\Rightarrow + V_1 - 2 + 4 = 0$


$V_1 = -2V$

(3) By KVL  $\Rightarrow + V_2 + 6 - 8 - 10 = 0$

$V_2 = 12V$

**11. Ans: (d)**


**Sol:**

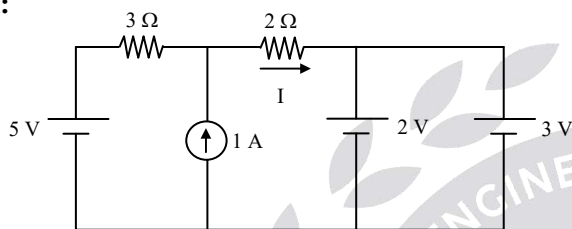

Here the 2V voltage source and 3V voltage source are in parallel which violates the KVL. Hence such circuit does not exist. (But practical voltage sources will have some internal resistance so that when two unequal voltage sources are connected in parallel current can flow and such a circuit may exist).

**12. Ans: (d)**

**Sol:**

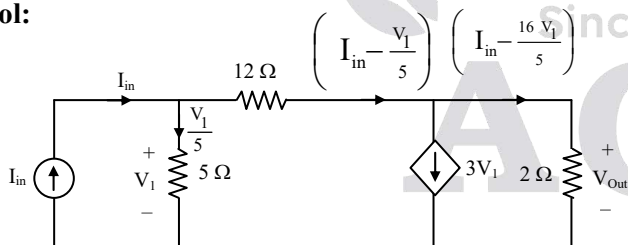

Applying KVL,

$$-V_1 + 12 \left( I_{in} - \frac{V_1}{5} \right) + 2 \left( I_{in} - \frac{16V_1}{5} \right) = 0$$

$$-V_1 + 12I_{in} - \frac{12V_1}{5} + 2I_{in} - \frac{32V_1}{5} = 0$$

$$14I_{in} = \frac{49}{5} V_1$$

$$\Rightarrow V_1 = \frac{70}{49} I_{in} \dots\dots (1)$$

$$\therefore V_{out} = 2 \left( I_{in} - \frac{16V_1}{5} \right) \dots\dots (2)$$

Substitute equation (1) in equation (2)

$$V_{out} = 2 \left( I_{in} - \frac{16}{5} \times \frac{70}{49} I_{in} \right)$$


$$= 2 \left( \frac{-25}{7} \right) I_{in}$$

$$= \frac{-50}{7} I_{in}$$

$$\therefore V_{out} = -7.143 I_{in}$$

**13. Ans: (c)**

**Sol:**

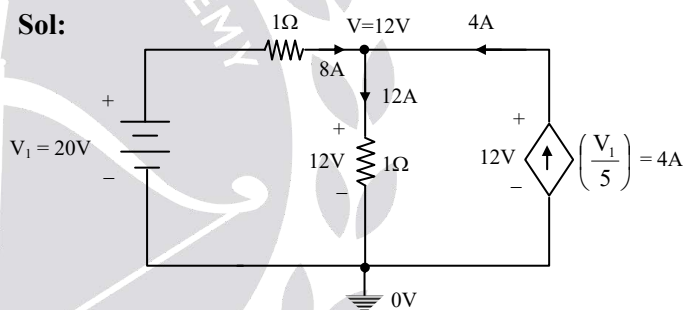

By nodal  $\Rightarrow$

$$V - 20 + V - 4 = 0$$


$$V = 12 \text{ volts}$$


Power delivered by the dependent source is

$$P_{del} = (12 \times 4) = 48 \text{ watts}$$

**14. Ans: (d)**

**Sol:**

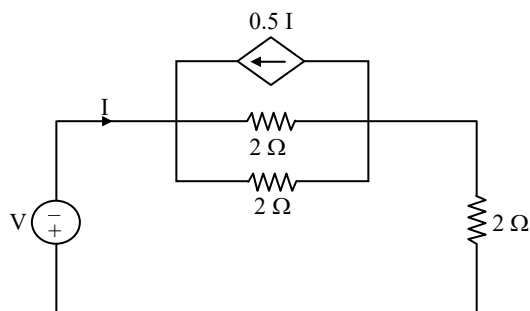


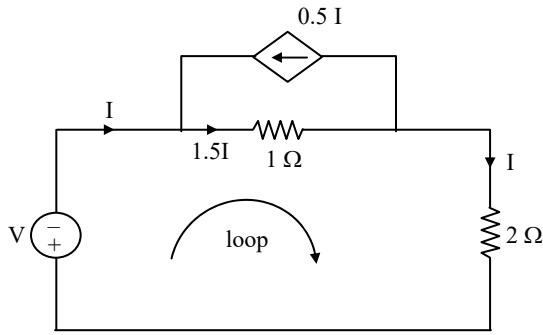

Applying KVL,  
 $\Rightarrow V + 1.5I + 2I = 0$   
 $\Rightarrow V = -3.5 I$

15. Ans: (c)

Sol:

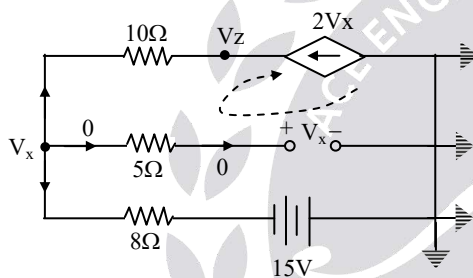

By using Nodal Analysis


$$\frac{V_x + 15}{8} - 2V_x = 0 \Rightarrow V_x = 1 \text{ V}$$

By using nodal Analysis at  $V_z$  node

$$\frac{V_z + 15}{18} - 2 = 0 \Rightarrow V_z = +21 \text{ V}$$

16.

Sol:

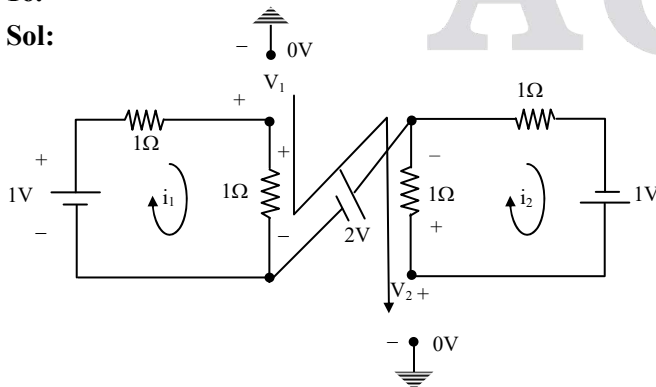

By KVL  $\Rightarrow 1 - i_1 - i_1 = 0$   
 $i_1 = 0.5 \text{ A}$

By KVL  $\Rightarrow -i_2 - i_2 + 1 = 0$

$$i_2 = 0.5 \text{ A}$$

By KVL  $\Rightarrow V_1 - 0.5 + 2 + 0.5 - V_2 = 0$


$$V_2 = V_1 + 2 \text{ V}$$

17.

Sol: As the bridge is balanced; voltage across (G) is "0V".

By KCL at node "A"  $\Rightarrow -I_s + 5\text{mA} + 5\text{mA} = 0$


$$I_s = 10\text{mA}$$

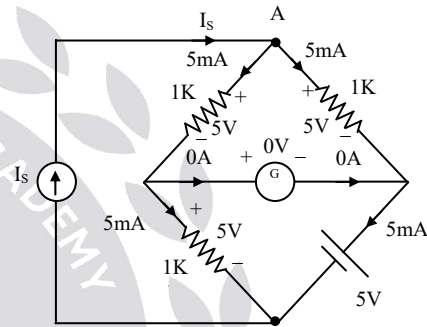

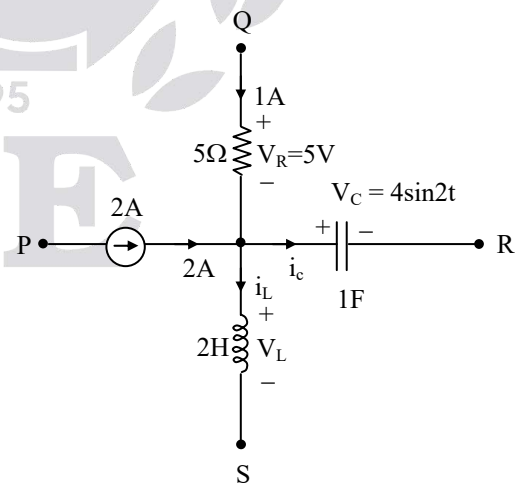18.

Sol: Given data:

$$V_R = 5 \text{ V and } V_C = 4\sin 2t \text{ then } V_L = ?$$



$$i_c = \frac{CdV_c}{dt} = \frac{d}{dt}(4\sin 2t) = 8\cos 2t$$

By KCL;  $-1 - 2 + i_L + i_c = 0$

$$i_L = 3 - 8\cos 2t$$

We know that;


$$V_L = L \frac{di_L}{dt} = 2 \frac{d}{dt} (3 - 8\cos 2t)$$

$$= 2(-8)(-2)\sin 2t$$

$$V_L = 32\sin 2t \text{ volt}$$

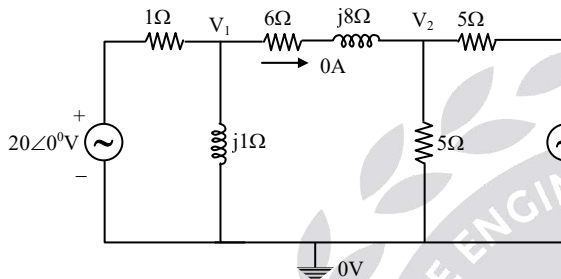19.

**Sol:**  $V = ?$  If power dissipated in  $6\Omega$  resistor is zero.



$P_{6\Omega} = 0 \text{ W (Given)}$

$\Rightarrow i_{6\Omega}^2 \cdot 6 = 0$

$\Rightarrow i_{6\Omega} = 0 (V_{6\Omega} = 0)$

$\frac{V_1 - V_2}{6 + j8} = 0; V_1 = V_2$

By Nodal  $\Rightarrow$

$\frac{V_1 - 20\angle 0^\circ}{1} + \frac{V_1}{j1} + 0 = 0$

$V_1 = 10\sqrt{2} \angle 45^\circ = V_2$

By Nodal  $\Rightarrow$


$0 + \frac{V_2}{5} + \frac{V_2 - V}{5} = 0$

$V = 2V_2 = 2(10\sqrt{2} \angle 45^\circ)$

$\therefore V = 20\sqrt{2} \angle 45^\circ$

20. **Ans: (d)**

**Sol:**

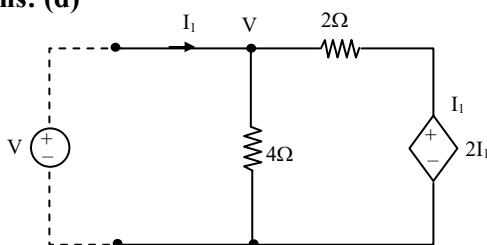

**Note:** Since no independent source in the network, the network is said to be unenergised, so called a DEAD network".

The behavior of this network is a load resistor behavior.

By Nodal  $\Rightarrow$


$-I_1 + \frac{V}{4} + \frac{V - 2I_1}{2} = 0$

$3V = 8I_1$

$R_{eq} = \frac{V}{I_1} = \frac{8}{3} \Omega$

21. **Ans: (a)**

**Sol:**

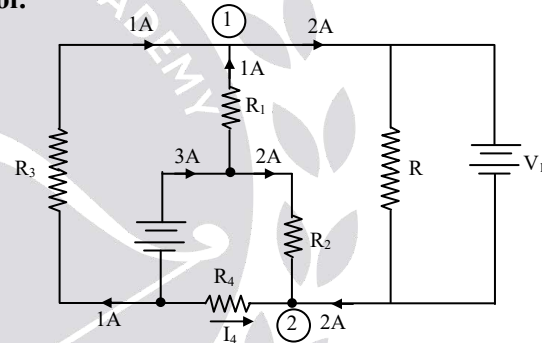

Apply KCL at Node - 1,

$I = I_{R1} + I_{R3} = 1 + 1 = 2A$

Apply KCL at Node-2,

$I_4 = -I_2 - I = -2 - 2 = -4A$

22.

**Sol:**

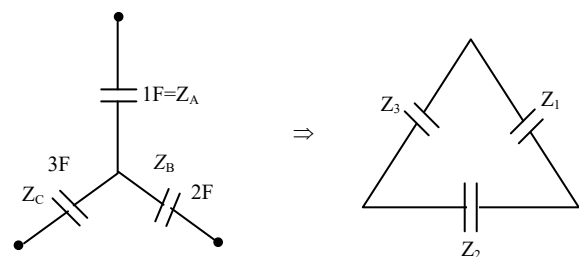


Fig.1

$$Z_1 = Z_A + Z_B + \left( \frac{Z_A Z_B}{Z_C} \right)$$

$$= \frac{1}{s} + \frac{1}{2s} + \left( \frac{\left( \frac{1}{s} \right) \left( \frac{1}{2s} \right)}{\left( \frac{1}{3s} \right)} \right)$$

$$Z_1 = \frac{1}{s \left( \frac{1}{3} \right)} ; \quad C = \frac{1}{3} \text{ F}$$


$$Z_2 = Z_B + Z_C + \frac{Z_B Z_C}{Z_A} = \frac{1}{2s} + \frac{1}{3s} + \left( \frac{\left( \frac{1}{2s} \right) \left( \frac{1}{3s} \right)}{\left( \frac{1}{s} \right)} \right)$$

$$Z_2 = \frac{1}{s(1)} ; \quad C = 1 \text{ F}$$

$$Z_3 = Z_A + Z_C + \frac{Z_A Z_C}{Z_B}$$


$$= \frac{1}{s} + \frac{1}{3s} + \left( \frac{\left( \frac{1}{s} \right) \left( \frac{1}{3s} \right)}{\left( \frac{1}{2s} \right)} \right)$$
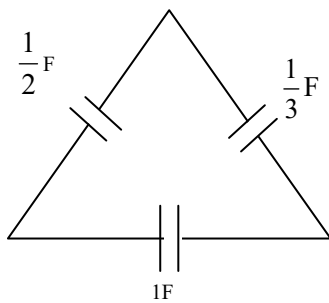
$$Z_3 = \frac{1}{s \left( \frac{1}{2} \right)} ; \quad C = \frac{1}{2} \text{ F}$$




23.

Sol:  $Z_{ab} = ?$

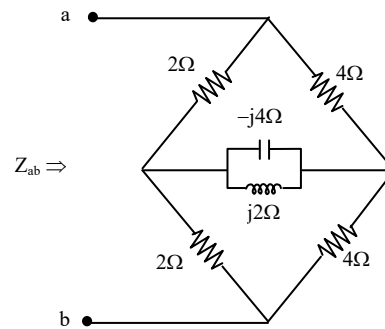

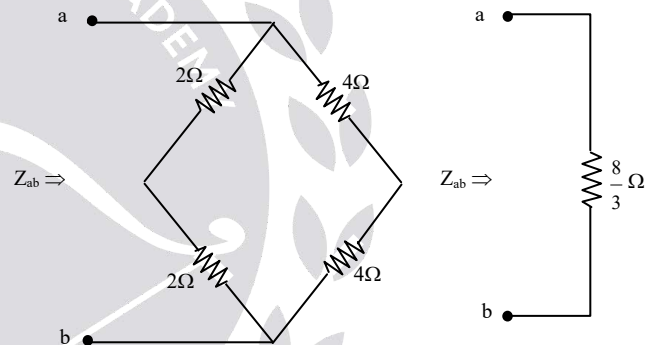
Since  $2 \times 4 = 4 \times 2$ ; the given bridge is balanced one, therefore the current through the middle branch is zero. The bridge acts as below:




$$Z_{ab} = \frac{4 \times 8}{4 + 8} = \frac{8}{3} \Omega$$

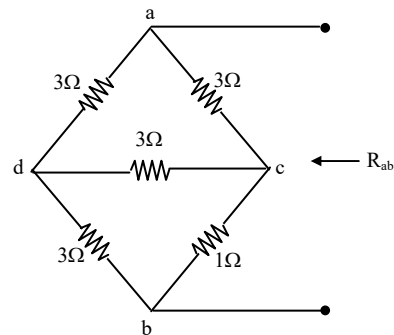24.

Sol: Redraw the circuit diagram as shown below:




Using  $\Delta$  to star transformation:

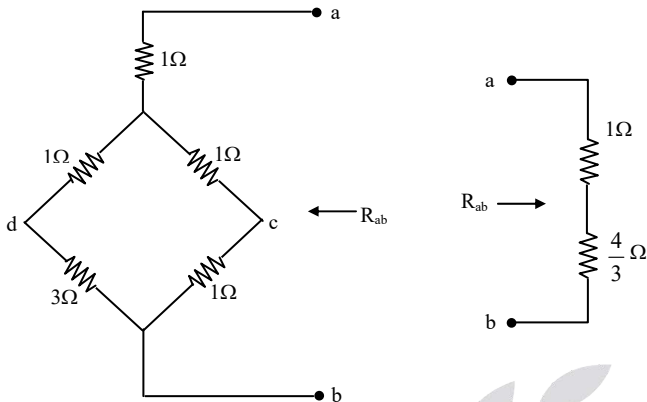

$$\therefore R_{ab} = 1 + \frac{4}{3} = \frac{7}{3} \Omega$$

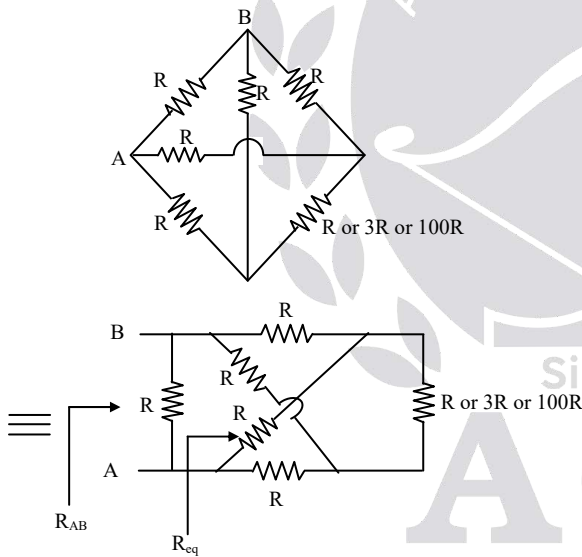
25.

**Sol:** On redrawing the circuit diagram



As bridge is balanced,  $R_{eq} = R$
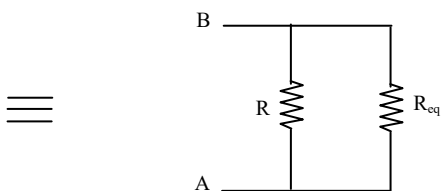
$$\text{So } R_{AB} = R \parallel R_{eq} = R \parallel R = R/2$$



26. **Ans: (b)**

**Sol:** The equivalent capacitance across a, b is calculated by simplifying the bridge circuit as shown in Fig. 1 [ $\because C = 0.1\mu\text{F}$ ]



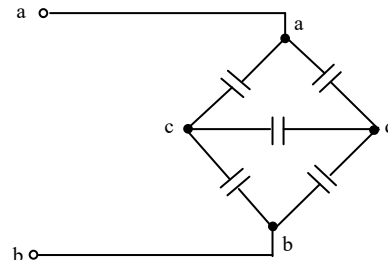


Fig. 1

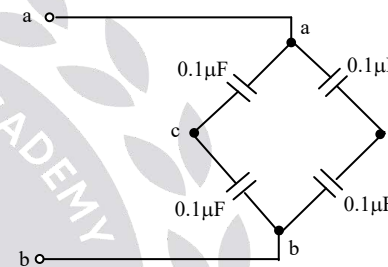
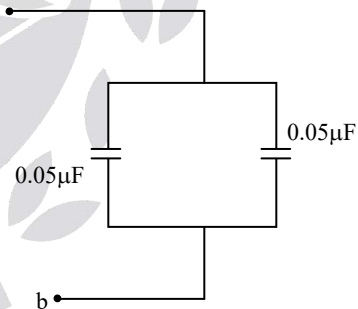
$$= \frac{0.1 \times 0.1}{0.2} = 0.05 \mu\text{F}$$




$$C_{ab} = 0.1 \mu\text{F}$$

**Note:** The bridge is balanced and the answer is easy to get.

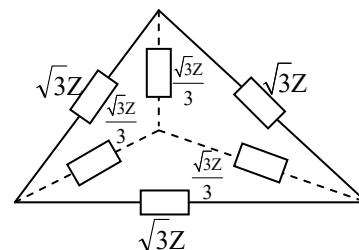27. **Ans: (a)**

**Sol:** Consider a  $\Delta$  connected network






Then each branch of the equivalent Y-connected impedance is  $\frac{\sqrt{3}Z}{3} = \frac{Z}{\sqrt{3}}$

**28. Ans: (a)**

**Sol:** Network is redrawn as

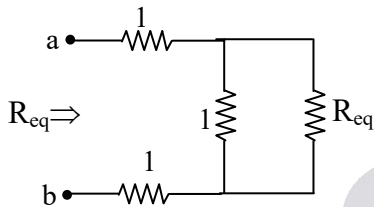

$$R_{eq} = 1 + 1 + \frac{R_{eq}}{1 + R_{eq}}$$

$$= 2 + \frac{R_{eq}}{1 + R_{eq}} = \frac{2 + 2R_{eq} + R_{eq}}{1 + R_{eq}}$$

$$R_{eq} + R_{eq}^2 = 2 + 3R_{eq}$$

$$R_{eq}^2 - 2R_{eq} - 2 = 0$$


$$R_{eq} = (1 + \sqrt{3}) \Omega$$

**29. Ans: (c)**

**Sol:** Applying KCL

$$I_{0.25\Omega} = 2i + i = 3i$$

$$I_{0.125\Omega} = (1 - 3i) A$$

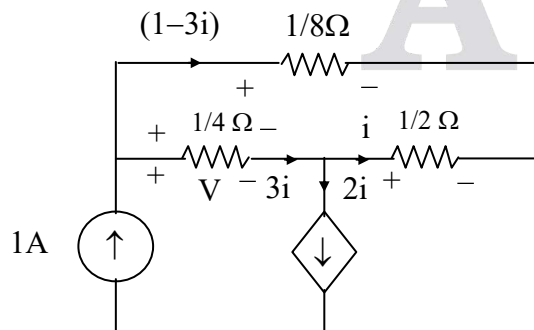

Applying KVL in upper loop.

$$-\frac{(1-3i)}{8} + \frac{i}{2} + \frac{3i}{4} = 0$$


$$\frac{5i}{4} = \frac{1-3i}{8} \Rightarrow 10i = 1-3i$$

$$\therefore i = \frac{1}{13} A$$

$$V = \frac{3i}{4} = \frac{3}{4} \times \frac{1}{13} = \frac{3}{52} V$$

**30. Ans: (a)**

**Sol:**

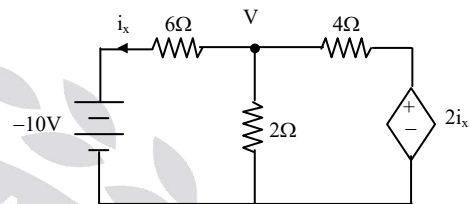

Applying KCL at Node V

$$\frac{V}{2} + \frac{V-2i_x}{4} + i_x = 0 \dots\dots\dots (1)$$

$$i_x = \frac{V+10}{6} \Rightarrow V = 6i_x - 10$$

Put in equation (1), we get

$$3i_x - 5 + i_x - 2.5 + i_x = 0$$

$$5i_x = 7.5$$

$$i_x = 1.5A$$


$$V = -1V$$

$$I_{\text{dependent source}} = \frac{V-2i_x}{4} = \frac{-1-3}{4} = -1A$$

$$\therefore \text{Power absorbed} = (I_{\text{dependent source}}) (2i_x) = (-1)(3) = -3W$$

**31. Ans: (d)**

**Sol:**  $V_0 = ?$

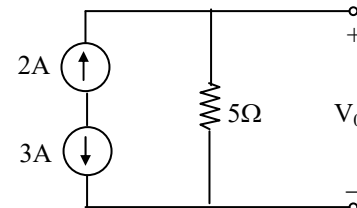


$$\text{By KCL} \Rightarrow \begin{aligned} +2 + 3 &= 0 \\ +5 &\neq 0 \end{aligned}$$

Since the violation of KCL in the circuit ; physical connection is not possible and the circuit does not exist.

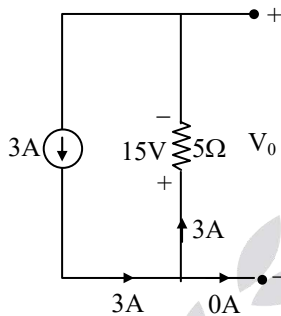**32. Ans: (b)**

**Sol:** Redraw the given circuit as shown below:



By KVL  $\Rightarrow$

$$-15 - V_0 = 0$$

$$V_0 = -15V$$

**33. Ans: (d)**

**Sol:** Redraw the circuit diagram as shown below:


Across any element two different voltages at a time is impossible and hence the circuit does not exist.

Another method:

By KVL  $\Rightarrow$

$$5 + 10 = 0$$


$$15 \neq 0$$

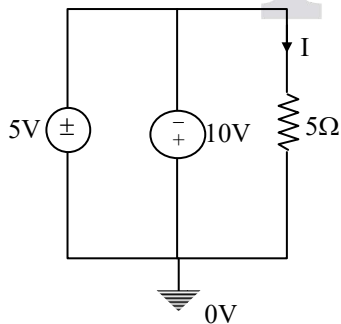

Since the violation of KVL in the circuit, the physical connection is not possible.

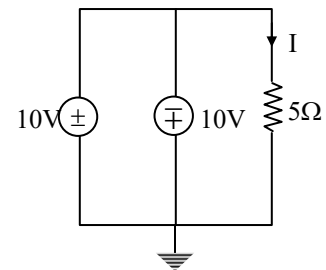**34. Ans: (d)**

**Sol:** Redraw the given circuit as shown below:



By KVL  $\Rightarrow$

$$-10 - 10 = 0$$

$$-20 \neq 0$$

Since the violation of KVL in the circuit, the physical connection is not possible.

**35. Ans: (b)**

**Sol:** Redraw the given circuit as shown below:

By KVL  $\Rightarrow$


$$10 - 10 = 0$$

$$0 = 0$$

KVL is satisfied

$$I_{5\Omega} = \frac{10}{5} = 2A$$

$$I_{5\Omega} = 2A$$

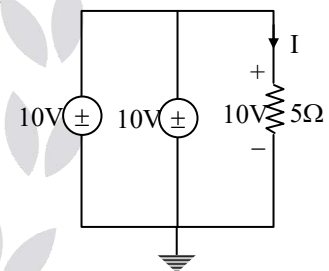

**36. Ans: (d)**

**Sol:**

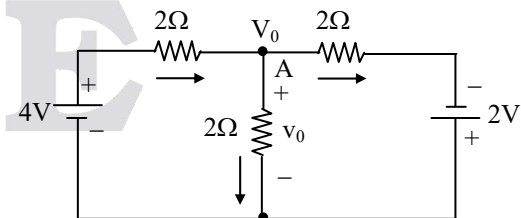


Fig. 1

The diode is forward biased. Assuming that the diode is ideal, the Network is redrawn with node A marked as in Fig. 1.

Apply KCL at node A

$$\frac{4 - v_0}{2} = \frac{v_0}{2} + \frac{v_0 + 2}{2}$$

$$\frac{3v_0}{2} = 1$$




$$v_0 = \frac{2}{3}V$$

(Here polarity is different what we assume so

$$V_0 = -\frac{2}{3}V$$


37.

**Sol:** The actual circuit is

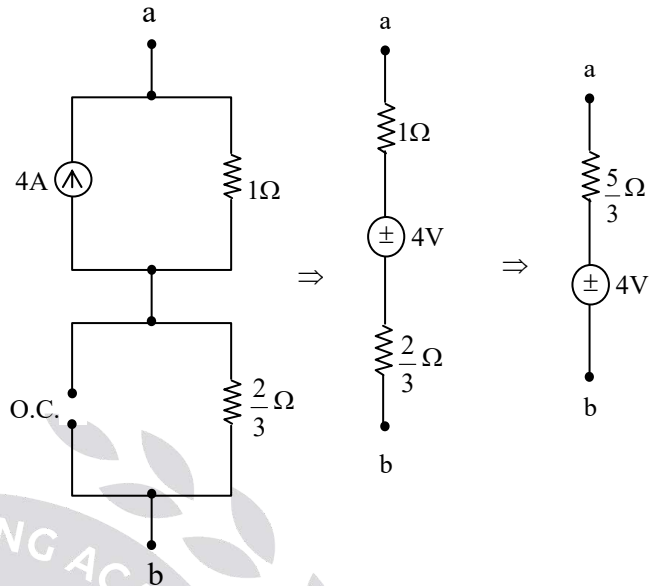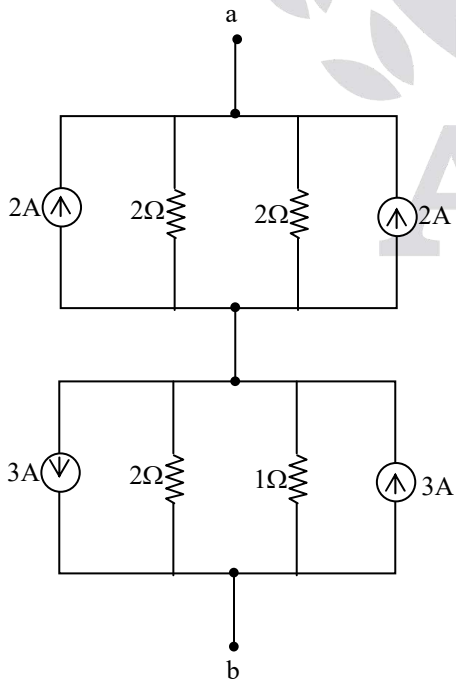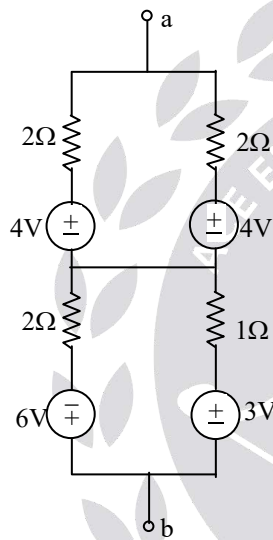

38. Ans: (b)

**Sol:**

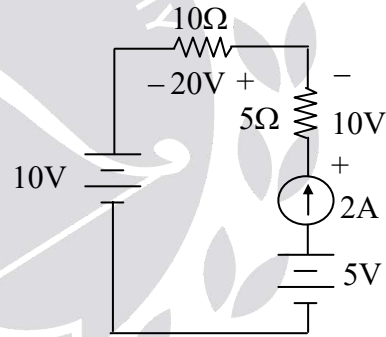

Voltage across 2A = 10 + 20 + 10 - 5


$$= 35V$$

∴ Power supplied = VI

$$= 35 \times 2 = 70W$$

39. Ans: (d)

**Sol:**

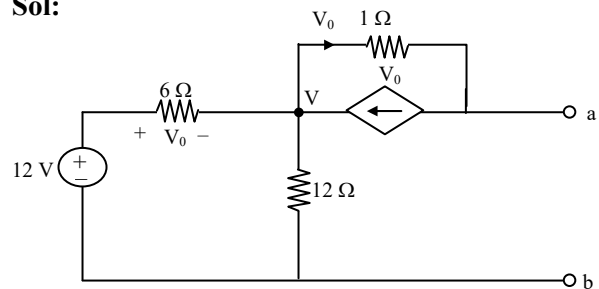

Applying KCL at node V

$$\frac{V-12}{6} + \frac{V}{12} - V_0 + V_0 = 0$$

$$\Rightarrow \frac{V}{6} + \frac{V}{12} = 2 \Rightarrow V = 8V$$

$$\therefore V_0 = 4V$$

Applying KVL in outer loop

$$\Rightarrow -V + 1(V_0) + V_{ab} = 0$$

$$\Rightarrow V_{ab} = V - V_0 = 8 - 4 = 4V$$

40.

Sol: By KVL

$$\Rightarrow V_i - 6 - 10 = 0$$


$$V_i = 16V$$

$$P_{4\Omega} = (8 * 2) = 16 \text{ watts} - \text{absorbed}$$

$$P_{2A} = (24 * 2) = 48 \text{ watts delivered}$$

$$P_{3\Omega} = (6 * 2) = 12 \text{ watts} - \text{absorbed}$$
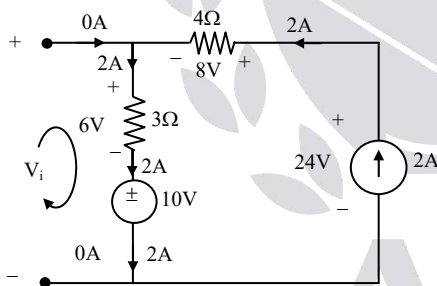
$$P_{10V} = (10 * 2) = 20 \text{ watts} - \text{absorbed}$$



$$48 = 16 + 12 + 20$$

$$48 = 48 \text{ W}$$

Since;  $P_{del} = P_{abs} = 48 \text{ watts}$ . Tellegen's Theorem is satisfied.


41.

Sol: By KVL in first mesh

$$\Rightarrow V_x - 6 + 6 - 12 = 0$$

$$V_x = 12V$$
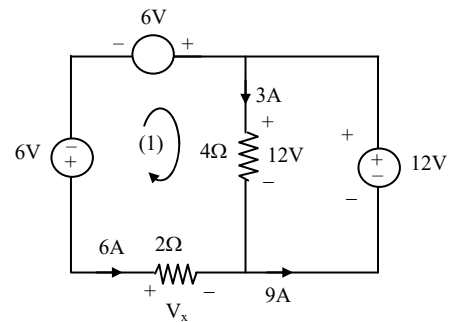
$$P_{12V} = (12 \times 9) = 108 \text{ watts delivered}$$



$$P_{4\Omega} = (12 \times 3) = 36 \text{ watts} - \text{absorbed}$$

$$P_{6V} = (6 \times 6) = 36 \text{ watts} - \text{absorbed}$$


$$P_{6V} = (6 \times 6) = 36 \text{ watts} - \text{delivered}$$

$$P_{2\Omega} = (12 \times 6) = 72 \text{ watts} - \text{absorbed}$$

Since  $P_{del} = P_{abs}$ ; Tellegen's theorem is satisfied.

42.

Sol:

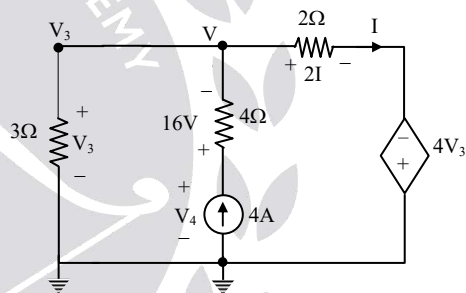

By Nodal  $\Rightarrow$

$$\frac{V}{3} - 4 + \frac{V + 4V_3}{20} = 0$$

$$\frac{5V}{6} = 4 - 2V_3 \dots\dots\dots (1)$$

By KVL  $\Rightarrow$

$$V_3 - 2I + 4V_3 = 0$$

$$5V_3 - 2I = 0 \dots\dots\dots (2)$$

By KVL  $\Rightarrow$

$$V = V_3 \dots\dots\dots (3)$$

Substitute (3) in (1), we get

$$V_3 = \frac{24}{17} ; V_4 = V + 16 = \frac{24}{16} + 16 = \frac{296}{17} \text{ V}$$

$$V_3 = \frac{24}{17} \text{ Volt and } I = \frac{60}{17} \text{ A}$$

$P_{3\Omega} = 0.663\text{W}$  absorbed

$P_{4\Omega} = 64\text{W}$  absorbed

$P_{4A} = 69.64\text{W}$  delivered

$P_{2\Omega} = 24.91\text{W}$  absorbed

$P_{4V3} = 19.92\text{W}$  delivered

Since  $P_{\text{del}} = P_{\text{abs}} = 89.57\text{W}$  ; Tellegen's Theorem is satisfied.


**43. Ans: (a, d)**

**Sol:** → For practical voltage source  $V_S$  is connected in series with its internal resistance  $R_S$  as low as possible. For ideal V.S  $\Rightarrow R_S = 0 \Omega$

→ For practical current  $I_S$  its internal resistance  $R_S$  connected in parallel as maximum as possible. For ideal C.S  $\Rightarrow R_S = \infty \Omega$

Any element connected with an ideal current source is not effect.

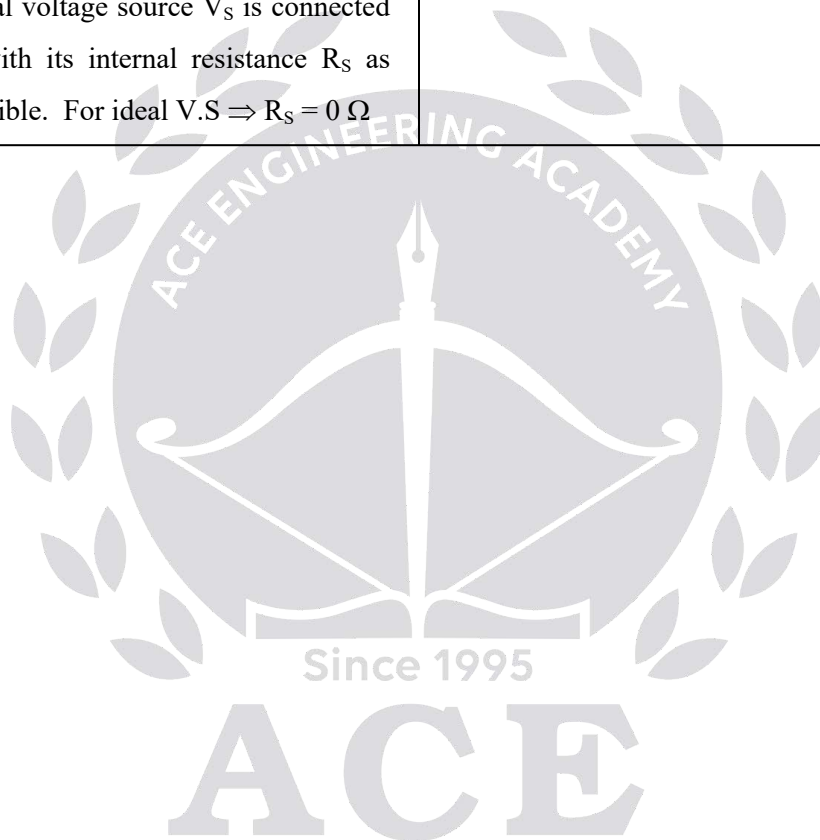
Any element connected in parallel with an ideal voltage source is not effect.



# Chapter 2 Circuit Theorems


01.

Sol: The current "I" = ?

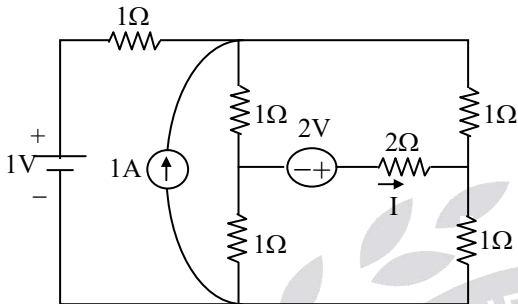


By superposition theorem, treating one independent source at a time.

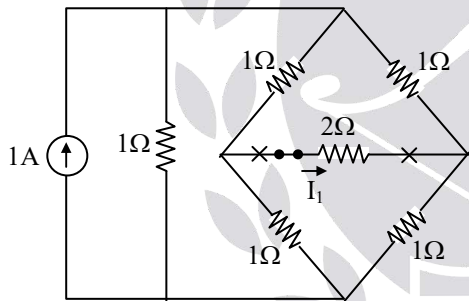(a) When 1A current source is acting alone.



Since the bridge is balanced;  $I_1 = 0A$

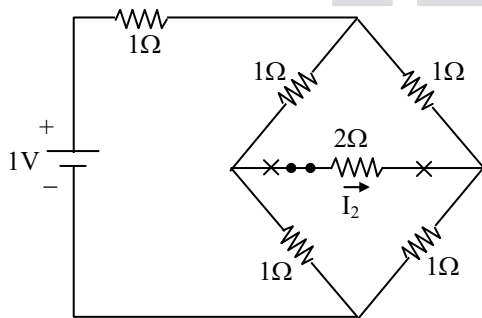(b) When 1V voltage source is acting alone




$I_2 = 0A$

Since the bridge is balanced.

(c) When 2V voltage source is acting alone and apply Reciprocity theorem, interchange source 2 volt and 1 Ω positions.

Excitation = same  
Response

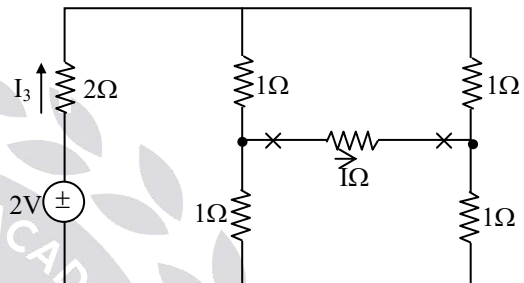

$$I_3 = \frac{2}{3} = 0.66A$$


By superposition theorem;  $I = I_1 + I_2 + I_3$

$$I = 0 + 0 + 0.66A$$

$$I = 0.66A$$

02.


Sol:

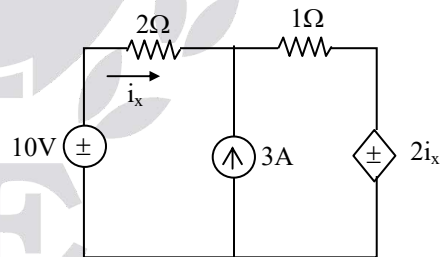

$i_x = ?$

By super position theorem; treating only one independent source at a time

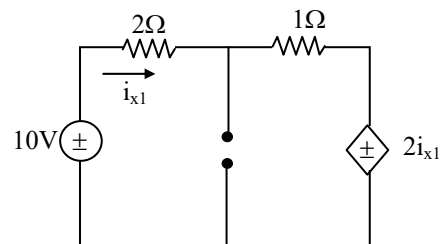(a) When 10V voltage source is acting alone




By KVL  $\Rightarrow$

$$10 - 2i_{x1} - i_{x1} - 2i_{x1} = 0$$

$$i_{x1} = 2A$$

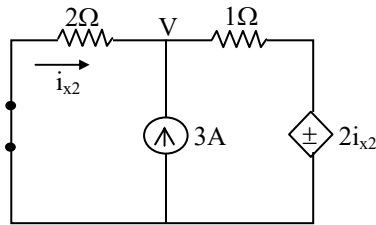(b) When 3A current source is acting alone



By Nodal  $\Rightarrow$

$$\frac{V}{2} - 3 + \frac{(V - 2i_{x2})}{1} = 0$$

$$3V - 4i_{x2} = 6 \dots\dots\dots (1)$$

And

$$i_{x2} = \frac{0 - V}{2} \Rightarrow V = -2i_{x2} \dots\dots(2)$$

Put (2) in (1), we get

$$i_{x2} = -\frac{3}{5} A$$


By SPT ;

$$i_x = i_{x1} + i_{x2} = 2 - \frac{3}{5} = \frac{7}{5}$$

$$\therefore i_x = 1.4A$$

**03.**

**Sol:**

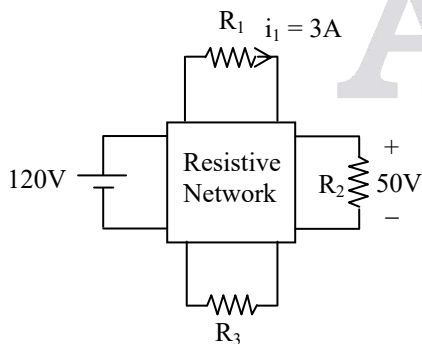

$$P_{R_3} = 60 W$$

$$\text{For } 120 V \rightarrow i_1 = 3 A$$

$$\text{For } 105 V \rightarrow i_1 = \frac{105}{120} \times 3 = 2.625A$$

$$\text{For } 120 V \rightarrow V_2 = 50 V$$

$$\text{For } 105 V \rightarrow V_2 = \frac{105}{120} \times 50 = 43.75 V$$

$$V_2 = 120 V \Rightarrow I^2 R_3 = 60 W \Rightarrow I = \sqrt{\frac{60}{R_3}}$$

$$\text{For } V_S = 105 V$$

$$P_3 = \left( \frac{105}{120} \sqrt{\frac{60}{R_3}} \right)^2 \times R_3 = 45.9 W$$

**04. Ans: (b)**

**Sol:** It is a liner network

$\therefore V_x$  can be assumed as function of  $i_{s1}$  and  $i_{s2}$

$$V_x = A i_{s1} + B i_{s2}$$

$$80 = 8A + 12 B \rightarrow (1)$$

$$0 = -8A + 4B \rightarrow (2)$$

From equation 1 & 2


$$A = 2.5, B = 5$$

$$\text{Now, } V_x = (2.5)(20) + (5)(20)$$


$$V_x = 150V$$

**05. Ans: (c)**

**Sol:**

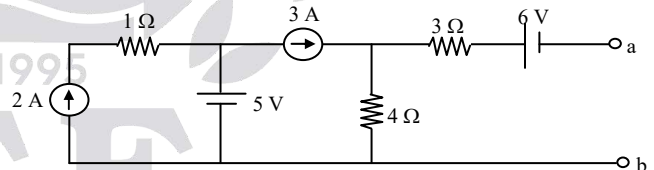

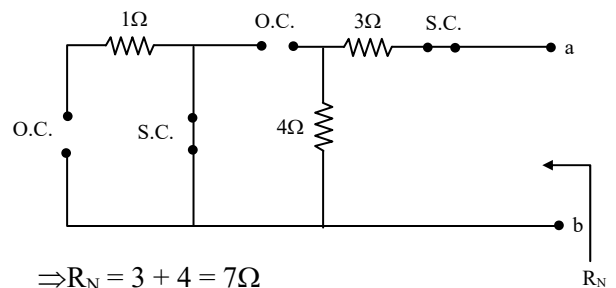
For finding Norton's equivalent resistance independent voltage sources to be short circuited and independent current sources to be open circuited, then the above circuit becomes




$$\Rightarrow R_N = 3 + 4 = 7\Omega$$

06. Ans: (b)

Sol:

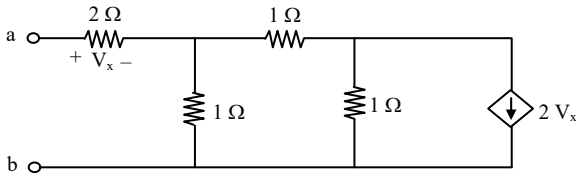

Excite with a voltage source 'V'

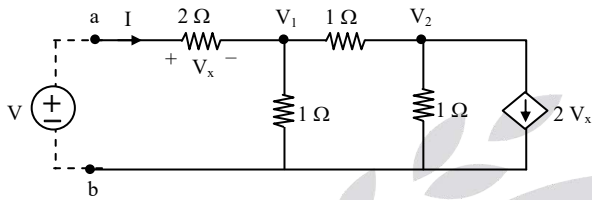

Apply KCL at node  $V_1$

$$-I + \frac{V_1}{1} + \frac{V_1 - V_2}{1} = 0$$

$$\Rightarrow 2V_1 - V_2 - I = 0 \dots\dots(1)$$

Apply KCL at node  $V_2$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{1} + 2V_x = 0$$

$$2V_2 - V_1 + 4I = 0 \dots\dots(2)$$

But from the circuit,

$$V_x = 2I \dots\dots(3)$$

Substitute (3) in (2)

$$\Rightarrow 2V_2 - V_1 + 4I = 0$$

$$4V_2 - 2V_1 + 8I = 0$$

From (1),

$$2V_1 = V_2 + I$$

$$\therefore 4V_2 - (V_2 + I) + 8I = 0$$

$$\Rightarrow 3V_2 + 7I = 0$$

$$\Rightarrow V_2 = -\frac{7I}{3}$$

Substitute ( $V_2$ ) in (1)

$$2V_1 - \left(-\frac{7I}{3}\right) - I = 0$$

$$2V_1 + \frac{7}{3}I - I = 0 \Rightarrow 2V_1 = \frac{-4I}{3}$$

$$\Rightarrow V_1 = \frac{-2I}{3}$$

$$\therefore V = V_x + V_1 = 2I + \left(-\frac{2I}{3}\right)$$

$$= \frac{4I}{3}$$


$$\Rightarrow V = \frac{4I}{3}$$

$$\Rightarrow \frac{V}{I} = \frac{4}{3} \Omega$$

$$\Rightarrow R_{eq} = \frac{4}{3} \Omega$$


07.

Sol:

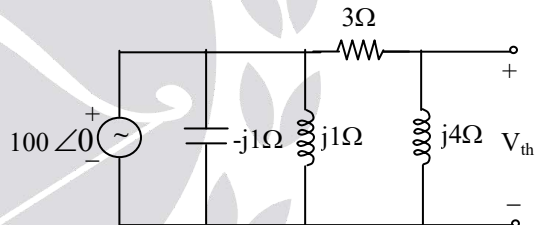

Here  $j1\Omega$  and  $-j1\Omega$  combination will act as open circuit.

The circuit becomes

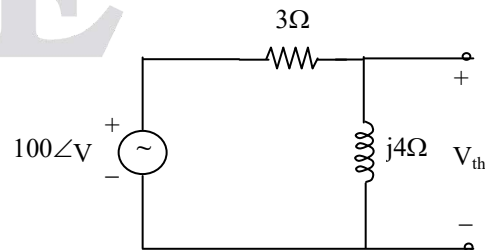


$$\Rightarrow V_{th} = \frac{100\angle 0^\circ \times j4}{3 + j4}$$

$$= 80\angle 36.86^\circ \text{ V}$$



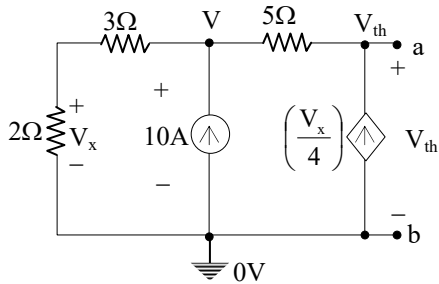08.

**Sol:** Thevenin's and Norton's equivalents across a, b.



By Nodal  $\Rightarrow$

$$\frac{V}{5} - 10 + \frac{V}{5} - \frac{V_{th}}{5} = 0 \quad \dots\dots\dots (1)$$

$$\frac{V_{th}}{5} - \frac{V}{5} - \frac{V_x}{4} = 0 \quad \dots\dots\dots (2)$$

$$V_x = \left(\frac{2V}{5}\right) \quad \dots\dots\dots (3)$$


$$\frac{2V}{5} = \left(10 + \frac{V_{th}}{5}\right) \quad \dots\dots\dots (4)$$

$$\frac{V_{th}}{5} = \left(\frac{V}{10} + \frac{V}{5}\right)$$

VDR:  $V_x = V \times \frac{2}{2+3}$

Solve eq (1) and (2) & (3)

$$V_{th} = 150V, V = 100V$$

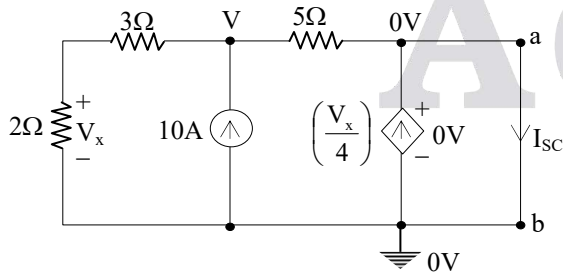

$$\frac{V}{5} - 10 + \frac{V}{5} = 0$$

$$\frac{2V}{5} = 10$$

$$V = 25V$$


$$V_x = \frac{2V}{5} = \frac{2 \times 25}{5}$$

$$V_x = 10V, \frac{0 - V}{5} - \frac{V_x}{4} + I_{sc} = 0$$

$$I_{sc} = \left(\frac{10}{4} + 5\right) = \frac{15}{2} A$$


$$I_{sc} = \frac{15}{2} A$$
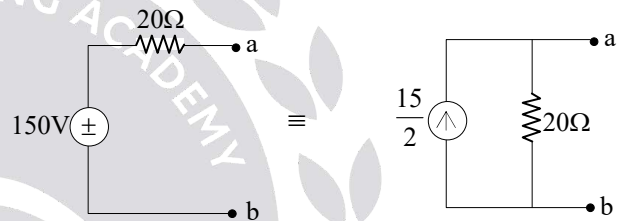
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{150}{\frac{15}{2}} = 20\Omega$$



09.

**Sol:**

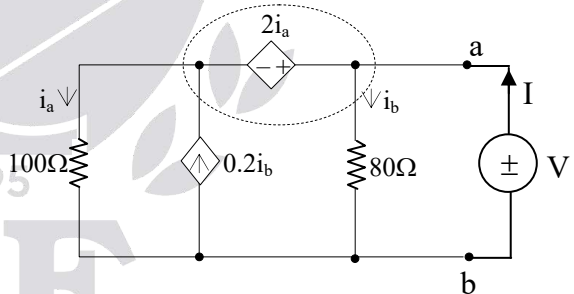

Super nodal equation

$$\Rightarrow i_a - 0.2i_b + i_b - I = 0$$


$$I = i_a + 0.8i_b$$

$$V = 80i_b ; i_b = \frac{V}{80}$$

- Inside the supernode, always the KVL is written.

By KVL  $\Rightarrow$

$$100i_a + 2i_a - 80i_b = 0$$

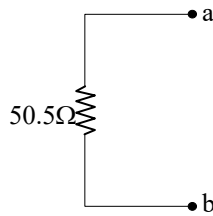

$$I = \frac{V}{102} + \frac{0.8 \times V}{80}$$


$$\frac{V}{I} = R_L = \frac{1}{\frac{1}{102} + \frac{1}{100}}$$

$$= 50.5\Omega.$$

$$R_L = 50.5\Omega$$

10.

Sol:  $V_{th}$ :

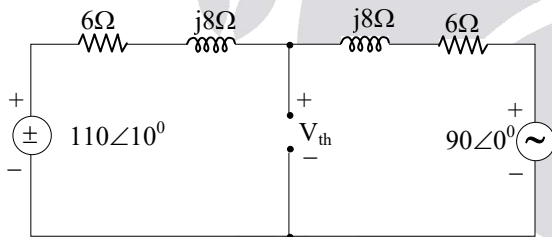


By Nodal  $\Rightarrow$


$$\frac{V_{th}}{(6 + j8)} - \frac{110\angle 0^\circ}{(6 + j8)} + \frac{V_{th}}{(6 + j8)} - \frac{90\angle 0^\circ}{(6 + j8)} = 0$$

$$2V_{th} = 200\angle 0^\circ \Rightarrow V_{th} = 100\angle 0^\circ.$$

$R_{th}$ :

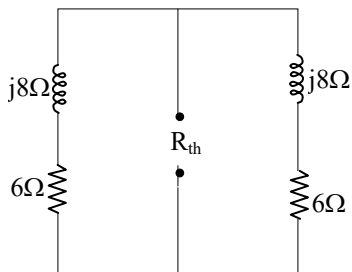
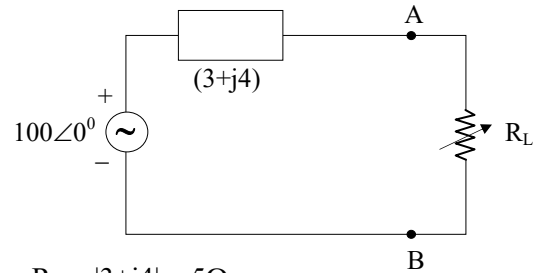
$$R_{th} = (6 + j8) \parallel (6 + j8) \equiv (3 + j4)\Omega$$



$$R_L = |3 + j4| = 5\Omega$$

$$I = \frac{100\angle 0^\circ}{(8 + j4)}$$


$$P = |I|^2 \times R_L$$

$$P_{max} = 125 \times 5 = 625 \text{ W}$$

$$\therefore P_{max} = 625 \text{ watts}$$

11.

Sol:

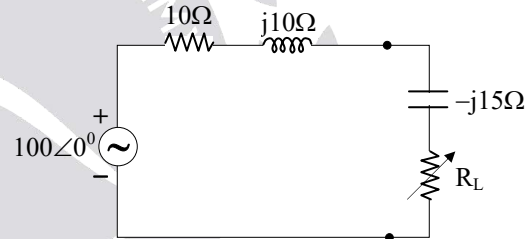

The maximum power delivered to "RL" is

$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$$

Here  $R_s = 10\Omega$ ;  $X_s = 10\Omega$  &  $X_L = -15\Omega$

$$R_L = \sqrt{10^2 + (10 - 15)^2}$$


$$R_L = 5\sqrt{5}\Omega.$$

$$I = \frac{100\angle 0^\circ}{(10 + j10 - j15 + 5\sqrt{5})}$$

$$P_{max} = |I|^2 \cdot 5\sqrt{5} = 236 \text{ W}$$

12.

Sol:

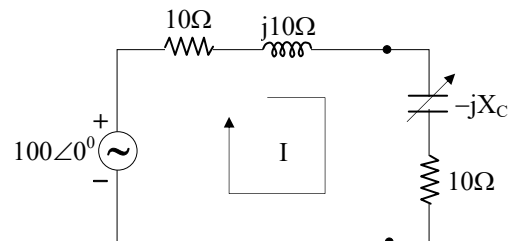

The maximum power delivered to  $10\Omega$  load resistor is:

$$Z_L = 10 - jX_C = 10 + j(-X_C)$$

$$X_L = -X_C$$

So for MPT;  $(X_S + X_L) = 0$

$$10 - X_C = 0;$$

$$X_C = 10$$


$$I = \frac{100\angle 0^\circ}{(10 + j10 - j10 + 10)} = 5\angle 0^\circ$$

$$P_{\max} = |I|^2 R_L = 5^2(10) = 250W$$

$$P_{\max} = 250 \text{ Watts}$$


**13. Ans: (b)**

**Sol:**

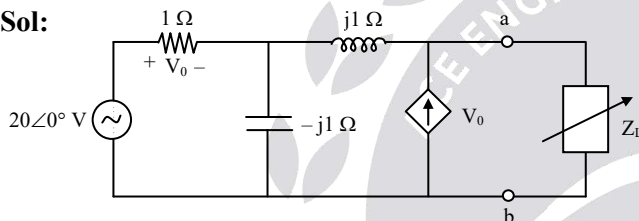

For maximum power delivered to  $Z_L$ ,

$$Z_L = Z_{th}^*$$

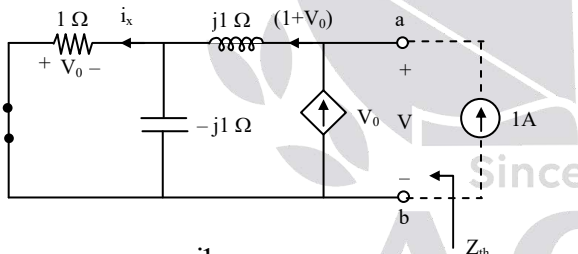

$$i_x = (1 + V_0) \times \frac{-j1}{1 - j1} = (1 + V_0) (0.5 - j0.5)$$

But

$$V_0 = -i_x$$

$$= -(1 + V_0) (0.5 - j0.5)$$

$$(-1 - j) V_0 = 1 + V_0$$

$$\Rightarrow V_0 (-1 - j - 1) = 1$$

$$V_0 = \frac{1}{-2 - j} = -0.4 + j0.2$$

Applying KVL

$$+ V_0 - j1(1 + V_0) + V = 0$$

$$\Rightarrow V = -V_0 + j1(1 + V_0)$$

$$= 0.4 - j0.2 + j1(0.6 + j0.2)$$


$$V = (0.2 + j0.4)V$$

$$\therefore Z_{th} = \frac{V}{I} = \frac{V}{1} = (0.2 + j0.4)\Omega$$

$$\therefore Z_L = Z_{th}^* = (0.2 - j0.4)\Omega$$

**14.**


**Sol:**

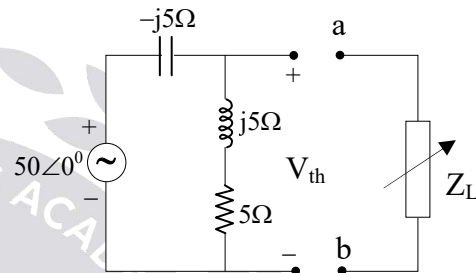

The maximum true power delivered to “ $Z_L$ ” is :

$$V_{th} = \left( \frac{50\angle 0^\circ}{-j5 + j5 + 5} \right) (j5 + 5) = 50\sqrt{2} \angle 45^\circ$$
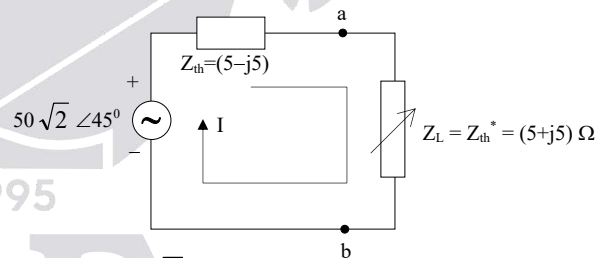
$$Z_{th} = (-j5) \parallel (5 + j5) = (5 - j5)\Omega$$




$$I = \frac{50\sqrt{2}\angle 45^\circ}{(5 - j5 + 5 + j5)} = 5\sqrt{2}\angle 45^\circ$$

$$P = |I|^2 5 = |5\sqrt{2}|^2 \cdot 5 = 250 \text{ Watts}$$

$$\therefore P_{\max} = 250 \text{ watts}$$


**15. Ans: (c)**

**Sol:**

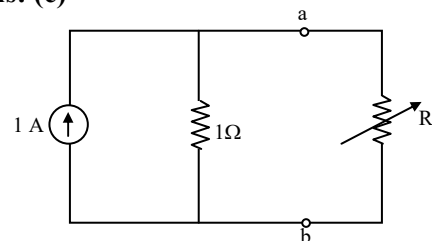


Maximum power will occur when  $R = R_s$

$$\Rightarrow R = 1 \Omega$$

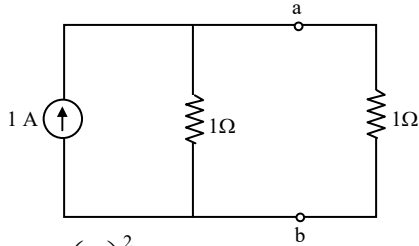

$$\therefore P_{\max} = \left(\frac{1}{2}\right)^2 \times 1 = \frac{1}{4} \text{ W}$$
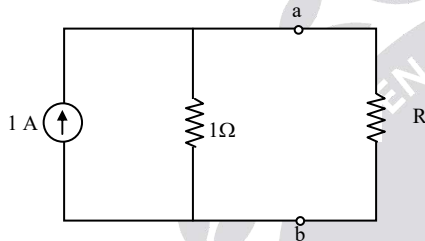
$$25\% \text{ of } P_{\max} = \frac{1}{4} \times \frac{1}{4} = \frac{1}{16} \text{ W}$$



current passing through 'R'

$$I = 1 \times \frac{1}{1+R} = \frac{1}{1+R}$$

$$\therefore P = I^2 R = \left(\frac{1}{1+R}\right)^2 R = \frac{1}{16}$$

$$\Rightarrow (R+1)^2 = 16R$$

$$\Rightarrow R^2 + 2R + 1 = 16R$$

$$\Rightarrow R^2 - 14R + 1 = 0$$

$$R = 13.9282\Omega \text{ or } 0.072\Omega$$

From the given options  $72\text{m}\Omega$  is correct.


**16. The network 'N' shown in figure contains only resistances.**

**$E = 10\text{V}$  and  $0\text{V}$**

**$I = 0\text{A}$  and  $2\text{A}$**

**$V = 3\text{V}$  and  $2\text{V}$  respectively.**

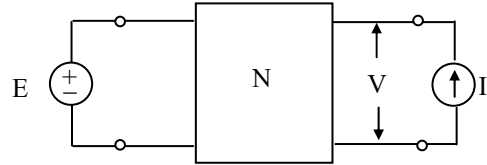**If  $E = 100\text{V}$  and  $I$  is replaced by  $R = 2\Omega$ , then determine  $V$ .**



**Sol:** For,  $E = 10\text{V}$ ,  $I = 0\text{A}$  then  $V = 3\text{V}$

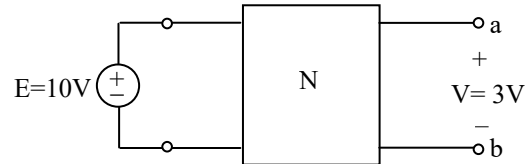


Fig.(b)

$V_{oc} = 3\text{V}$  (with respect to terminals a and b)

For,  $E = 0\text{V}$ ,  $I = 2\text{A}$  then  $V = 2\text{V}$


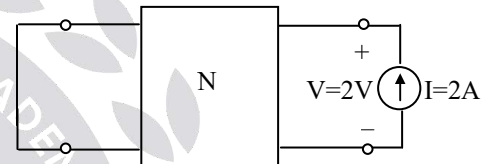



Fig.(c)

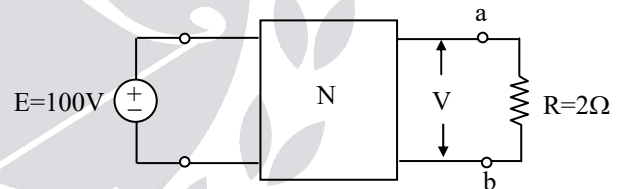Now when  $E = 100\text{V}$ , and  $I$  is replaced by  $R = 2\Omega$  then  $V = ?$



When  $E = 100\text{V}$ ,

From Fig.(b) using homogeneity principle

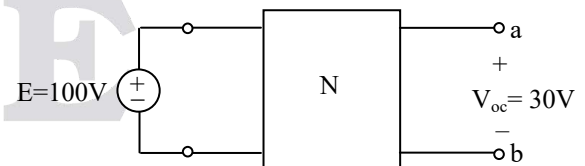

For finding Thevenin's resistance across ab independent voltage sources to be short circuited & independent current sources to be open circuited.


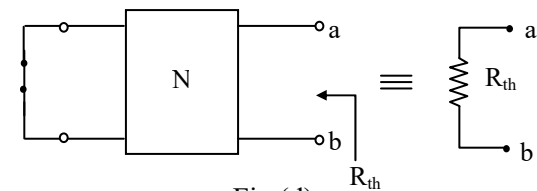




Fig.(d)

Fig.(c) is the energized version of Fig. (d)

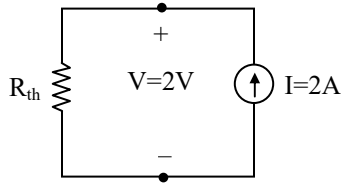

$$\Rightarrow R_{th} = \frac{2}{2} = 1\Omega$$

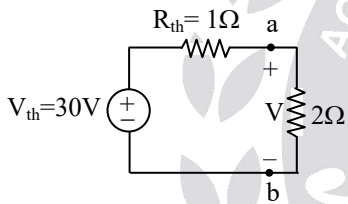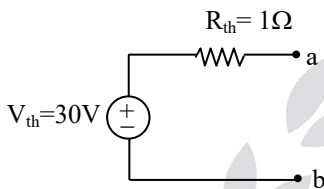∴ With respect to terminals a and b the Thevenin's equivalent becomes.



$$V = 30 \times \frac{2}{2+1} = 20V$$

$$\therefore V = 20V$$

17.

**Sol:** Superposition theorem cannot be applied to fig (b)

Since there is only voltage source given:


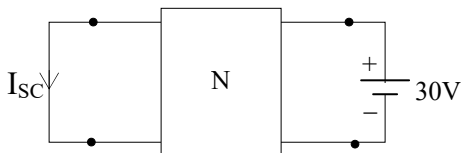


Fig (c)

By homogeneity and Reciprocity principles to fig (a);

$$I_{sc} = 6A$$

For  $R_{th}$ :

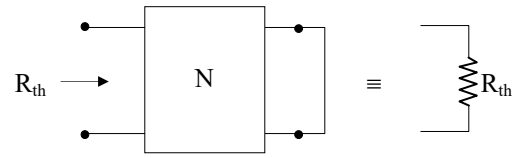

Statement: Fig (a) is the energized version of figure (d)

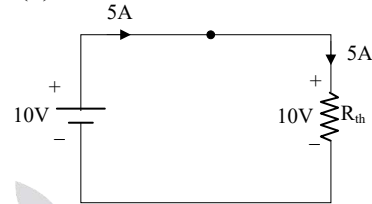


Fig (a)

$$10 = R_{th} \cdot 5 \quad \text{by ohm's law}$$

$$R_{th} = 2\Omega.$$

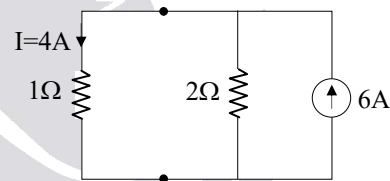


Fig (b)

$$I = \frac{6 \times 2}{(2+1)} = 4A$$


$$I = 4A$$

18. **Ans: (b)**

$$\text{Sol: } \begin{bmatrix} 10 \\ 4 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} 4 \\ 0 \end{bmatrix}$$

$$10 = Z_{11} (4) + Z_{12} (0)$$

$$4 = Z_{21} (4) + Z_{22} (0)$$

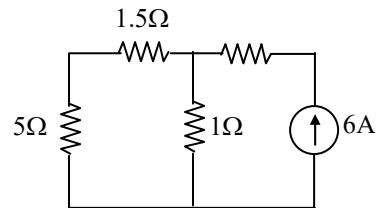

$$Z_{11} = \frac{10}{4} = 2.5$$

$$Z_{21} = \frac{4}{4} = 1$$

$$I_{5\Omega} = \frac{6 \times 1}{6.5 + 1} = \frac{6}{7.5} = 0.8 \text{ A}$$

19. Ans: (b)

Sol:

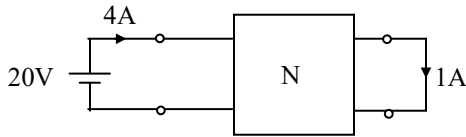


Fig.(a)

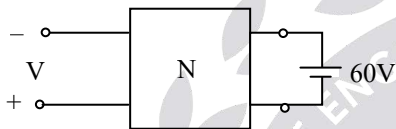


Fig.(b)

Using reciprocity theorem, for Fig.(a)

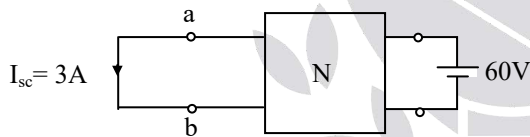


Fig.(c)

Norton's resistance between a and b is


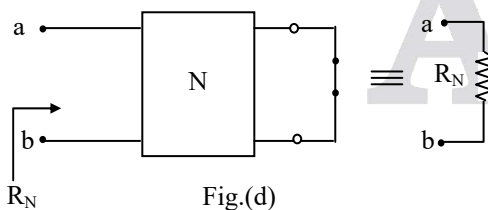



Fig.(d)

Fig.(a) is the energized version of Fig.(d)


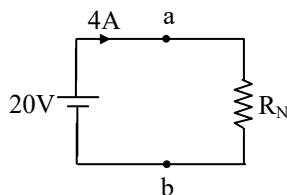


$$\Rightarrow R_N = \frac{20}{4} = 5\Omega$$

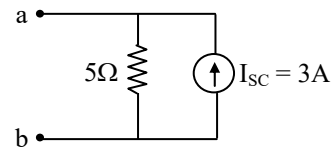With respect to terminals a and b the Norton's equivalent of Fig.(b) is





∴ From Fig.(b)

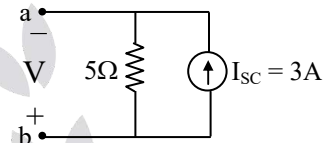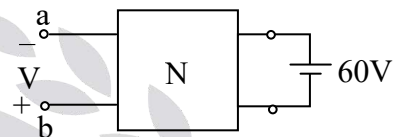

$$\Rightarrow V = -15\text{V}$$

20.


Sol:

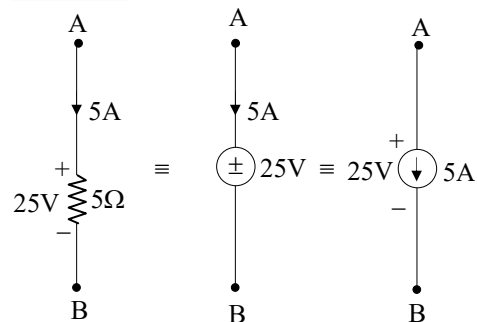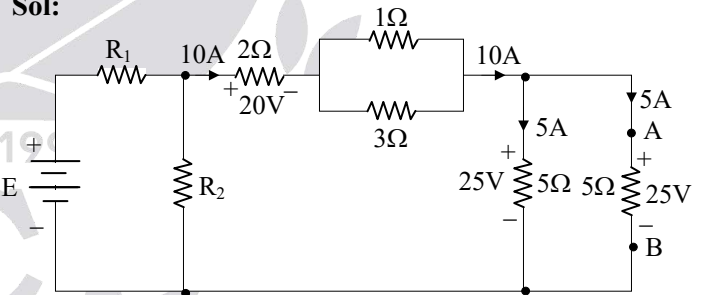

$$P_{AB} = P_{5\Omega} = P_{25V} = P_{5A} = 5 \times 25 = 125 \text{ watts (ABSORBED)}$$

21.


Sol:

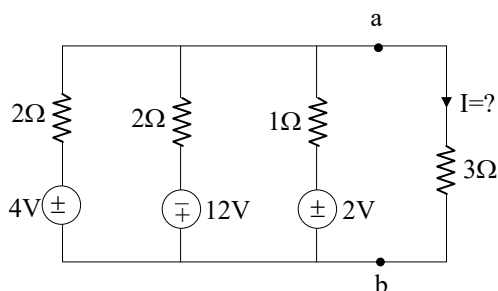

By Mill Man's theorem;

$$V' = \frac{V_1 G_1 + V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3}$$
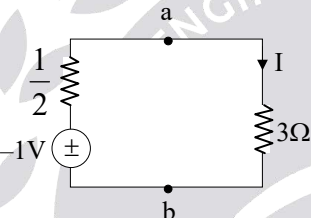
$$\equiv \frac{\frac{4}{2} - \frac{12}{2} + \frac{2}{1}}{\left(\frac{1}{2} + \frac{1}{2} + 1\right)} = \frac{4 - 12 + 4}{2 * 2} \equiv -1V$$



∴ V' = -1V


$$\frac{1}{R^1} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2} + \frac{1}{2} + 1 = 2$$

∴ R<sup>1</sup> = 1/2 Ω

$$I = \frac{-1}{\left(\frac{1}{2} + 3\right)} \Rightarrow I = \frac{-2}{7} A$$

22. Ans: (d)

Sol:

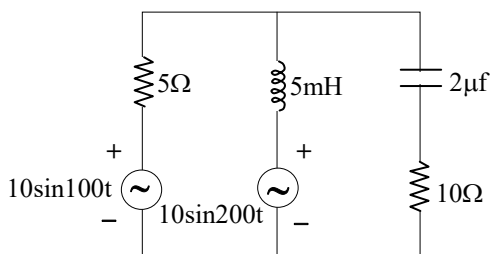

Since the two different frequencies are operating on the network simultaneously; always the super position theorem is used to evaluate the

responses since the reactive elements are frequency sensitive


i.e.,  $Z_L = j\omega L$  and  $Z_C = \frac{1}{j\omega c}$

23.

Sol: In the above case if both the source are 100rad/sec, each then Millman's theorem is more conveniently used.


24.

Sol:

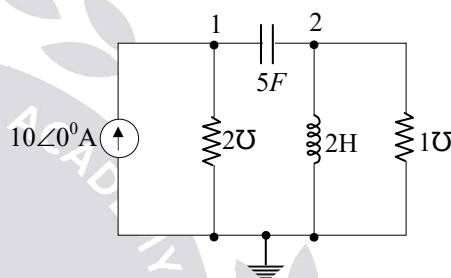

25.

Sol:

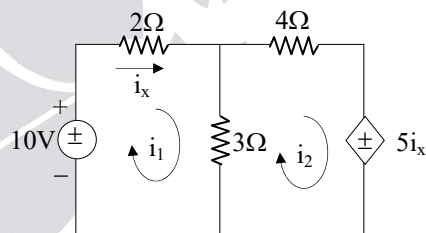

Nodal equations

i = GV

i<sub>x</sub> = i<sub>1</sub>


10 = 2i<sub>1</sub> + 3(i<sub>1</sub> - i<sub>2</sub>) ..... (1)

0 = 4i<sub>2</sub> + 2i<sub>x</sub> + 3(i<sub>2</sub> - i<sub>1</sub>) ..... (2)

V<sub>x</sub> = V<sub>1</sub>

10 = 2V<sub>1</sub> - 3(V<sub>1</sub> - V<sub>2</sub>) ..... (3)

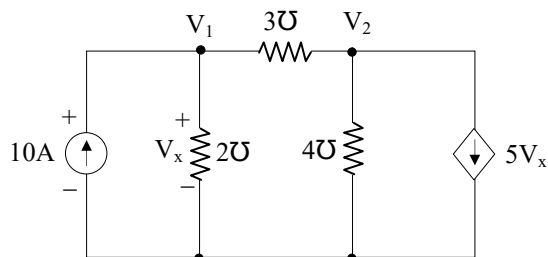0 = 4V<sub>2</sub> + 2V<sub>x</sub> + 3(V<sub>2</sub> - V<sub>1</sub>) ..... (4)




26. (b, c)

**Sol:** Tellegen's Theorem is applicable to any nonlinear Network.

27. **Ans: (c, d)**

**Sol:**

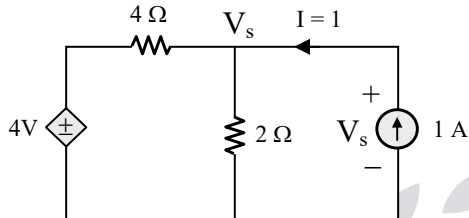

$$I = 1 \Rightarrow 4I = 4(1) = 4 \text{ V}$$

$$R_{th} = \frac{V_s}{I}$$


$$\frac{V_s - 4}{4} + \frac{V_s}{2} - 1 = 0$$

$$\frac{3V_s}{4} - 2 = 0 \Rightarrow V_s = \frac{8}{3} \text{ V}$$

$$R_{th} = \frac{V_s}{I} = \frac{8}{3} \Omega$$

$\therefore$  There is no independent source,  $V_{th} = 0$

$\therefore$  (c, d) are correct.

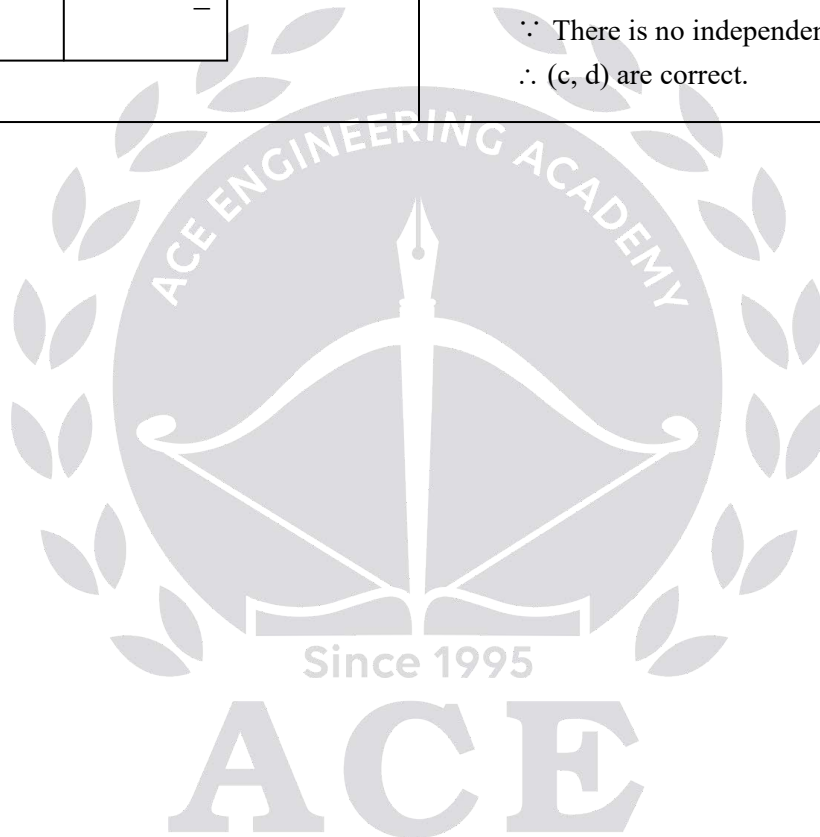




# Chapter 3 Transient Circuit Analysis

01.

Sol:

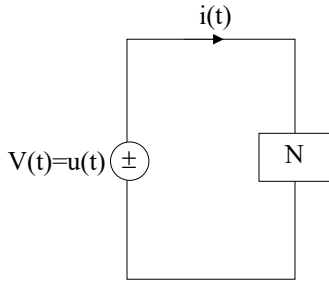

$i(t) = e^{-3t}A$  for  $t > 0$  (given)

Determine the elements & their connection

$\frac{\text{Response Laplace transform}}{\text{Excitation Laplace transform}} = \text{System}$

transfer function

$$\text{i.e., } \frac{I(s)}{V(s)} = H(s) = \frac{1}{(s+3)} = \frac{1}{\frac{1}{s}}$$

$$= \frac{s}{(s+3)} = y(s) = \frac{1}{Z(s)}$$

$$\therefore Z(s) = \left( \frac{s+3}{s} \right)$$


$$= 1 + \frac{1}{s\left(\frac{1}{3}\right)} = R + \frac{1}{SC}$$

$\therefore R = 1\Omega$  and  $C = \frac{1}{3}F$  are in series

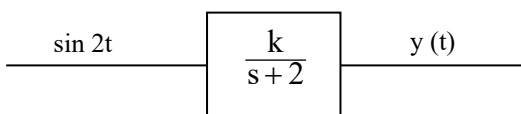02. Ans: (c)

Sol: The impulse response of first order system is  $Ke^{-2t}$ .

$$\text{So T/F} = L(I.R) = \frac{K}{s+2}$$



$$G(s) = \frac{K}{s+2}$$

$$|G(j\omega)| = \frac{K}{\sqrt{\omega^2 + 2^2}} = \frac{K}{2\sqrt{2}}$$


$$\angle G(j\omega) = -\tan^{-1} \frac{\omega}{2} = -\tan^{-1} 1 = -\frac{\pi}{4}$$

So steady state response will be

$$y(t) = \frac{K}{2\sqrt{2}} \sin\left(2t - \frac{\pi}{4}\right)$$

03.

Sol:

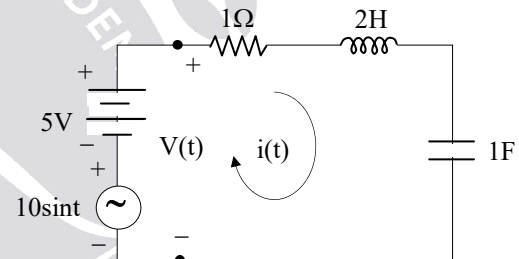

By KVL  $\Rightarrow v(t) = (5 + 10\sin t)$  volt

Evaluating the system transfer function  $H(s)$ .

$\frac{\text{Desired response L.T}}{\text{Excitation response L.T}} = \text{System transfer function}$

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \frac{1}{Z(s)} = \frac{1}{\left( R + SL + \frac{1}{SC} \right)}$$

$$H(s) = \frac{S}{(2s^2 + s + 1)}$$

$$H(j\omega) = \frac{1}{\left( 1 + \frac{1}{j\omega} + 2j\omega \right)}$$

II. Evaluating at corresponding  $\omega_s$  of the input

$$H(j\omega)|_{\omega=0} = 0$$

$$H(j\omega)|_{\omega=1} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

III.  $\frac{I(s)}{V(s)} = H(s)$

$I(s) = H(s)V(s)$

$i(t) = 0 \times 5 + \frac{1}{\sqrt{2}} \times 10 \sin(t - 45^\circ)$

$i(t) = 7.07 \sin(t - 45^\circ) \text{ A}$

OBS: DC is blocked by capacitor in steady state.

04.

Sol:  $\frac{V(s)}{I(s)} = H(s) = Z(s) = \frac{1}{Y(s)} = \frac{1}{\left(\frac{1}{R} + \frac{1}{sL} + sC\right)}$

$H(s) = \frac{1}{\left(1 + \frac{1}{s} + s\right)}$

$H(j\omega) \Big|_{\omega=1} = \frac{1}{\left(1 + \frac{1}{j} + j\right)} = 1$


$V(s) = I(s) H(s) = \sin t$

$v(t) = \sin t \text{ volts}$

05.


Sol:  $\tau = \frac{L_{eq}}{R_{eq}}$

$R_{eq} :$

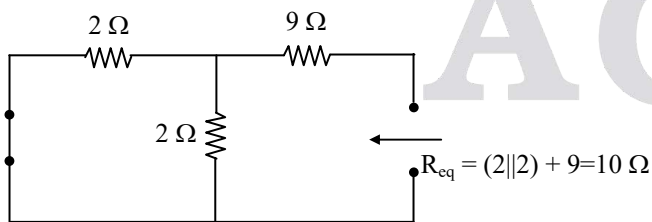

$R_{eq} = (2 \parallel 2) + 9 = 10 \Omega$

$L_{eq} :$

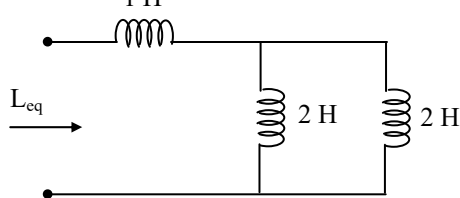


$L_{eq} = (2 \parallel 2) + 1 = 2 \text{ H}$

$\therefore \tau = \frac{L_{eq}}{R_{eq}} = \frac{2}{10} = 0.2 \text{ sec}$

06.


Sol:  $\tau = R_{eq} C_{eq}$

$R_{eq} :$

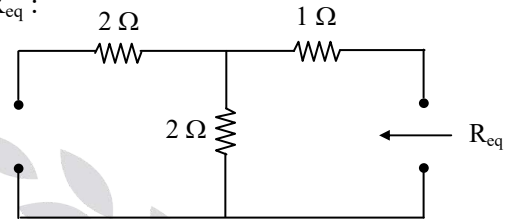

$R_{eq} = 3 \Omega$

$C_{eq} :$

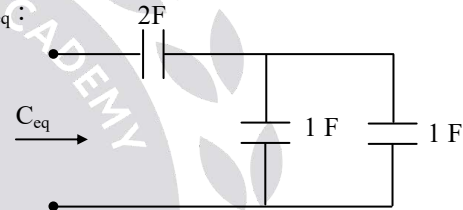


$C_{eq} = 1 \text{ F}$

$\therefore \tau = 3 \times 1 = 3 \text{ sec}$

07.

Sol:  $\tau = R_{eq} C$

$R_{eq} :$

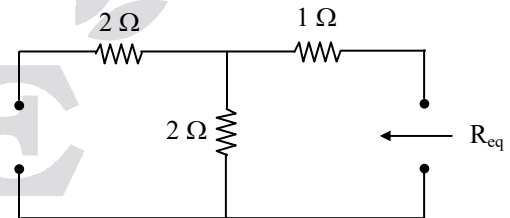


$R_{eq} = 3 \Omega$

$\therefore \tau = 3 \times 1 = 3 \text{ sec}$

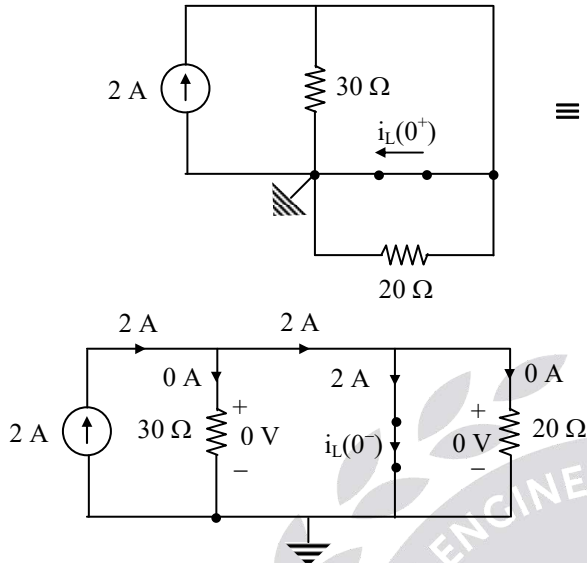08.

Sol: Let us assume that switch is closed at  $t = -\infty$ , now we are at  $t = 0^-$  instant, still the switch is closed i.e., an infinite amount of time, the independent dc source is connected to the network and hence it is said to be in steady state.

In steady state, the inductor acts as short circuit and nature of the circuit is resistive.



At  $t = 0^-$  : Steady state: A resistive circuit


**Note:** The number of initial conditions to be evaluated at just before the switching action is equal to the number of memory elements present in the network.

(i)  $t = 0^-$


$$i_L(0^-) = 2 = i_L(0^+)$$

$$E_L(0^-) = \frac{1}{2} L i_L^2(0^-)$$
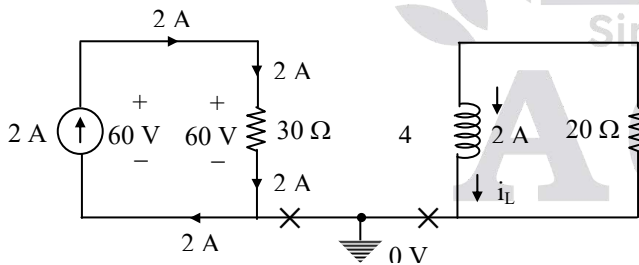
$$= \frac{1}{2} \times 4 \times 2^2 = 8\text{J} = E_L(0^+)$$



For  $t \geq 0$

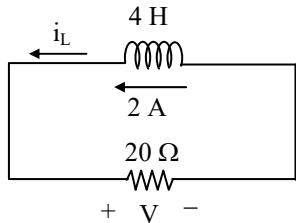


For  $t \geq 0$  : Source free circuit

$$I_0 = 2\text{ A}; \tau = \frac{L}{R} = \frac{4}{20} = \frac{1}{5}\text{ sec}$$


$$i_L = 2 e^{-5t} \text{ for } 0 \leq t \leq \infty$$
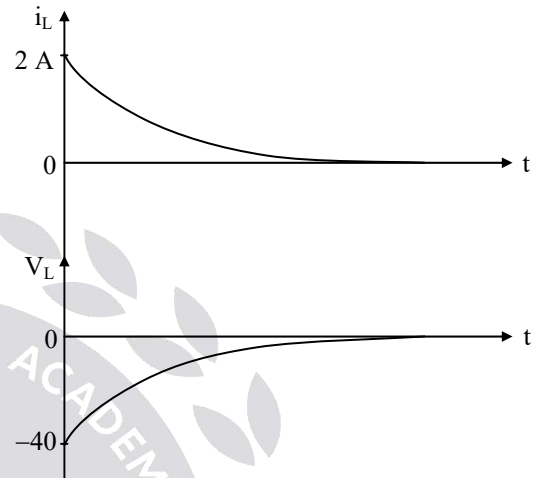
$$V_L = L \frac{di_L}{dt} = -40 e^{-5t} \text{ V for } 0 \leq t \leq \infty$$




$$t = 5\tau = 5 \times \frac{1}{5} = 1\text{ sec for steady state}$$

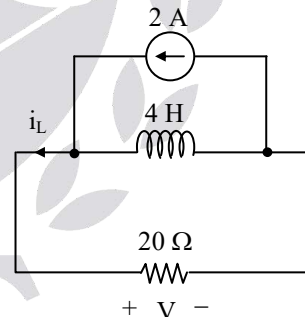practically i.e., with in 1 sec the total 8 J stored in the inductor will be delivered to the resistor.



For  $t \geq 0$

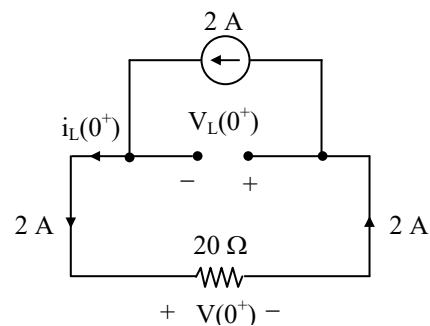

At  $t = 0^+$  : Resistive circuit :  
Network is in transient state

By KCL:

$$-2 + i_L(0^+) = 0$$

$$i_L(0^+) = 2 \text{ A}$$

$$V(0^+) = R i_L(0^+) \text{ |By Ohm's law}$$

$$V(0^+) = 20 (2) = 40 \text{ V}$$

By KVL:

$$V_L(0^+) + V(0^+) = 0$$

$$V_L(0^+) = -V(0^+) = -40 \text{ V} = V_L(t) \Big|_{t=0^+}$$

**Observations:**

$$t = 0^-$$

$$i_L(0^-) = 2 \text{ A}$$

$$i_{20\Omega}(0^-) = 0 \text{ A}$$

$$V_{20\Omega}(0^-) = 0 \text{ V}$$

$$V_L(0^-) = 0 \text{ V}$$

$$t = 0^+$$

$$i_L(0^+) = 2 \text{ A}$$

$$i_{20\Omega}(0^+) = 2 \text{ A}$$


$$V_{20\Omega}(0^+) = 40 \text{ V}$$

$$V_L(0^+) = -40 \text{ V}$$

**Conclusion:**

To keep the same energy as  $t = 0^-$  and to protect the KCL and KVL in the circuit (i.e., to ensure the stability of the network), the inductor voltage, the resistor current and its voltage can change instantaneously i.e., within zero time at  $t = 0^+$ .

(2)

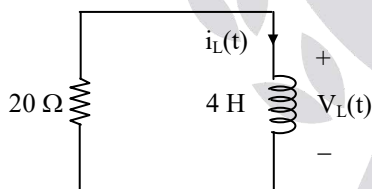

For  $t \geq 0$

$$i_L(t) = 2 e^{-5t} \text{ A for } 0 \leq t \leq \infty$$

$$V_L(t) = -40 e^{-5t} \text{ V for } 0 \leq t \leq \infty$$

**Conclusion:**

For all the source free circuits,  $V_L(t) = -ve$  for  $t \geq 0$ , since the inductor while acting as a temporary source (upto  $5\tau$ ), it discharges from positive terminal i.e., the current will flow from negative to positive terminals. (This is the must condition required for delivery, by Tellegen's theorem)

$$(3) V_L(0^+) = -40 \text{ V}$$

$$V_L(t) \Big|_{t=0^+} = -40 \text{ V}$$

$$L \frac{d i_L(t)}{dt} \Big|_{t=0^+} = -40$$

$$\frac{d i_L(t)}{dt} \Big|_{t=0^+} = -\frac{40}{L} = -\frac{40}{4} = -10 \text{ A/sec}$$

**Check :**


$$i_L(t) = 2 e^{-5t} \text{ A for } 0 \leq t \leq \infty$$

$$\frac{d i_L(t)}{dt} = -10 e^{-5t} \text{ A/sec for } 0 \leq t \leq \infty$$

$$\frac{d i_L(t)}{dt} \Big|_{t=0^+} = -10 \text{ A/sec}$$

**09.**

**Sol:**

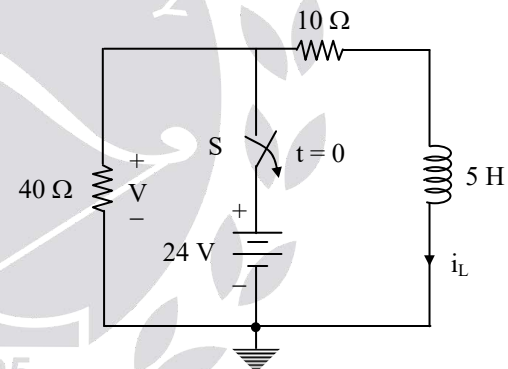


$$i_L(0^+) = 2.4 \text{ A}$$

$$V(0^+) = -96 \text{ V}$$

$$i_L(t) = 2.4 e^{-10t} \text{ A for } 0 \leq t \leq \infty$$

**10.**

**Sol:**

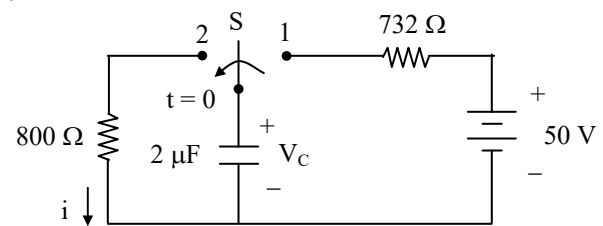

$$V_C(0^+) = 50 \text{ V ; } i(0^+) = 62.5 \text{ mA}$$

$$V_C(t) = 50 e^{-\frac{t}{1.6 \times 10^{-3}}} \text{ V for } t \geq 0$$

$$i_C = C \frac{dV_C}{dt} \quad \left| \begin{array}{l} \text{By Ohm's law} \end{array} \right.$$


$$= 2 \times 10^{-6} 50 e^{-\frac{t}{1.6 \times 10^{-3}}} \times \frac{-1}{1.6 \times 10^{-3}}$$

$$= \frac{100 \times 10^{-6}}{1.6 \times 10^{-3}}$$

$$= \frac{1}{16}$$

11.

Sol: Case (i):  $t < 0$

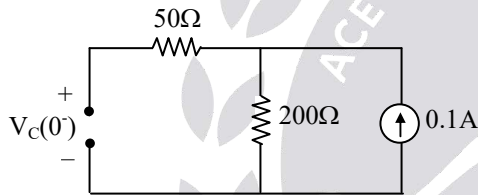


$$V_C(0^-) = 20\text{V} \text{ \& } i(0^-) = 0.1\text{A}$$

∴ Capacitor never allows sudden changes in voltages

$$V_C(0^-) = V_C(0) = V_C(0^+) = 20\text{V}$$

Case (ii):  $t > 0$

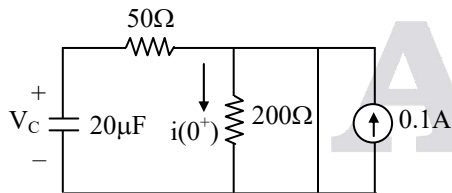

To find the time constant  $\tau = R_{eq}C$

After switch closed

$$R_{eq} = 50\Omega \quad C = 20\mu\text{F}$$

$$i(0^+) = 0\text{A}$$

$$\tau = 50 \times 20\mu$$


$$\tau = 1\text{msec}$$

$$V_C(t) = V_0 e^{-t/\tau} = 20 e^{-t/1\text{m}}$$

$$V_C(t) = 20 e^{-t/1\text{m}} \text{V}; \quad 0 \leq t < \infty$$

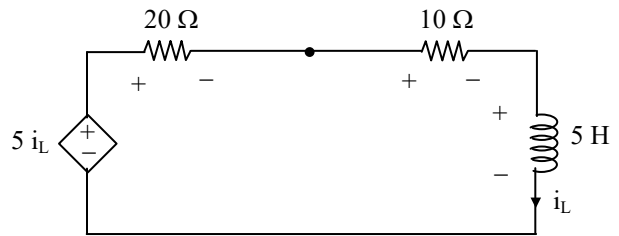12.

Sol: After performing source transformation;



By KVL;

$$5 i_L - 30 i_L - 5 \frac{di_L}{dt} = 0$$

$$\frac{di_L}{dt} + 5 i_L = 0$$

$$(D + 5) i_L = 0$$

$$i_L(t) = K e^{-5t} \text{ A for } 0 \leq t < \infty$$

$$\tau = \frac{1}{5} \text{ sec}$$

13.

$$\text{Sol: } i_{L_1}(0) = 10 \text{ A} ; i_{L_2}(0) = 2 \text{ A}$$

$$i_{L_1}(t) = I_0 e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R} = \frac{1}{1} = 1 \text{ sec}$$

$$i_{L_1}(t) = 10 e^{-t} \text{ A}$$


$$\text{Similarly, } i_{L_2}(t) = I_0 e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R} = 2 \text{ sec}$$

$$i_{L_2}(t) = 20 e^{-\frac{t}{2}} \text{ A}$$

14.

Sol:

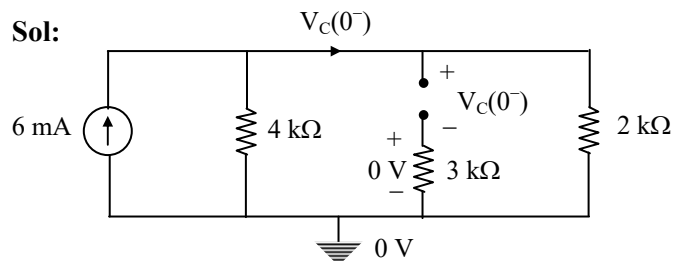


At  $t = 0^-$ : Steady state: A resistive circuit

By Nodal:

$$-6 \text{ mA} + \frac{V_C(0^-)}{4 \text{ K}} + \frac{V_C(0^-)}{2 \text{ K}} = 0$$


$$V_C(0^-) = 8 \text{ V} = V_C(0^+)$$

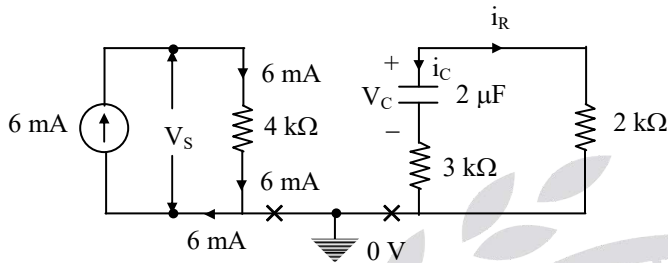

For  $t \geq 0$ : A source free circuit

$$V_s = 6 \text{ m} \times 4 \text{ K} = 24 \text{ V}$$
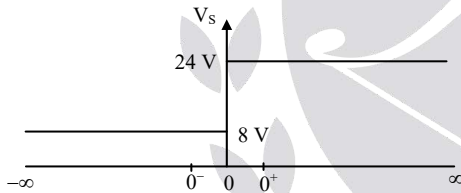
$$\tau = R_{eq} C = (5 \text{ K}) 2 \mu = 10 \text{ m sec}$$



$$V_C = 8 e^{-\frac{t}{10 \text{ m}}} = 8 e^{-100t} \text{ V for } 0 \leq t \leq \infty$$

$$i_C = C \frac{dV_C}{dt} \Big|_{\text{By Ohm's law}} = -1.6 e^{-100t} \text{ mA for } 0 \leq t \leq \infty$$

By KCL:

$$i_C + i_R = 0$$

$$i_R = -i_C = 1.6 e^{-100t} \text{ mA for } 0 \leq t \leq \infty$$

**Observation:**

In all the source free circuit,  $i_C(t) = -ve$  for  $t \geq 0$  because the capacitor while acting as a temporary source it discharges from the +ve terminal i.e., current will flow from -ve to +ve terminals.

15.

Sol: By KCL:

$$i(t) = i_R(t) + i_L(t)$$

$$= \frac{V_R(t)}{R} + \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$

$$= \frac{V_s(t)}{10} + i_L(0) + \frac{1}{L} \int_0^t V_s(t) dt$$


$$i(t) = 4t + 5 + 4t^2$$

$$i(t) |_{t=2 \text{ sec}} = 8 + 16 + 5 = 29 \text{ A} = 29000 \text{ mA}$$

16. Ans: (c)

17.

Sol:

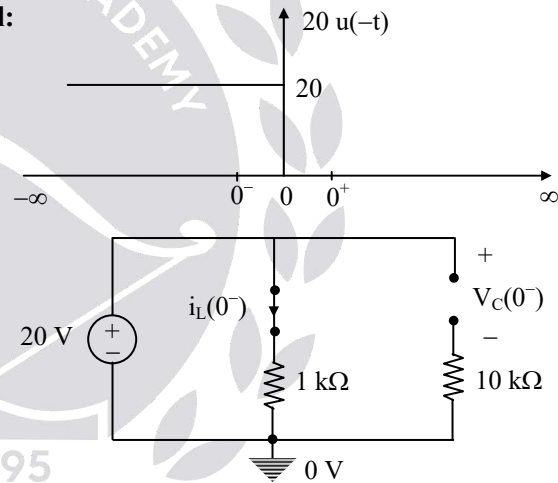


At  $t = 0^-$ : steady state: A resistive circuit.

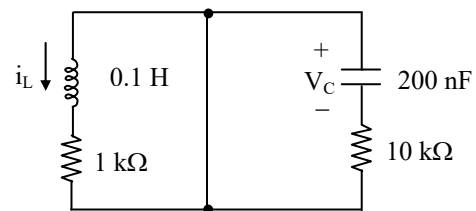(i)  $t = 0^-$

$$V_C(0^-) = 20 \text{ V} = V_C(0^+)$$

$$i_L(0^-) = \frac{20}{1 \text{ K}} = 20 \text{ mA} = i_L(0^+)$$



For  $t \geq 0$ : A source free RL & RC circuit

$$\tau = \frac{0.1}{1K} = 100 \mu\text{sec}$$

$$\tau_C = 200 \times 10^{-9} \times 10 \times 10^3 = 2 \text{ m sec}$$

$$\frac{\tau_C}{\tau_L} = 20 ; \tau_C = 20 \tau_L$$

**Observation:**

$\tau_L < \tau_C$  ; therefore the inductive part of the circuit will achieve steady state quickly i.e., 20 times faster.

$$V_C = 20 e^{-\frac{t}{\tau_C}} \text{ V for } 0 \leq t \leq \infty$$


$$i_L = 20 e^{-\frac{t}{\tau_L}} \text{ mA for } 0 \leq t \leq \infty$$

$$V_L = L \frac{di_L}{dt} \quad \text{By Ohm's law}$$

$$i_C = C \frac{dV_C}{dt} \quad \text{By Ohm's law}$$

**18. Ans: (c)**

**Sol:**

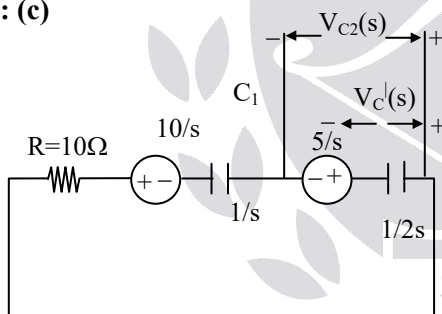

$$V_c^1(s) = \frac{5/s \cdot (1/2s)}{R + 1/s + 1/2s}$$

$$= \frac{5}{2Rs^2 + 2 + 1} = \frac{5}{s(2Rs + 3)}$$

$$V_{c_2}(\infty) - V_c^1(s) - \frac{5}{s} = 0$$

$$V_c(\infty) = V_c^1(s) + \frac{5}{s}$$

$$V_c(\infty) = \lim_{s \rightarrow 0} s \left[ \frac{5}{s(2Rs + 3)} + \frac{5}{s} \right] = \frac{5}{3} + 5 = \frac{20}{3}$$

**19. Ans: (d)**

**Sol:** at  $t = 0$


$$L \frac{di(0)}{dt} = V_L(0)$$

$$V_L = 2 \times 3 = 6$$

$$V_L = 6V$$

$$E_2 + 6 - 8R = 0$$

$$E_2 = 8R - 6$$

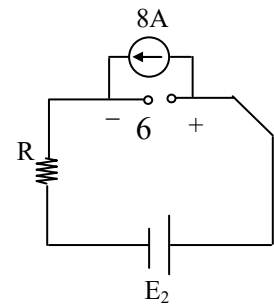


$$E_2 - 4R = 0$$

$$E_2 = 4R$$

$$8R - 6 = 4R$$



$$4R = 6$$

$$R = 1.5\Omega$$

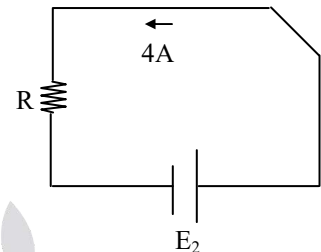

**20. Ans: (d)**

**Sol:** at  $t < 0$

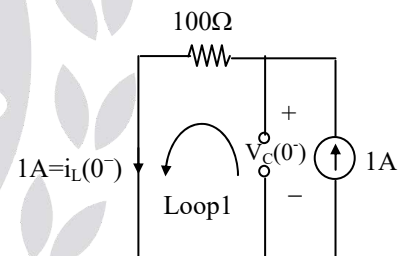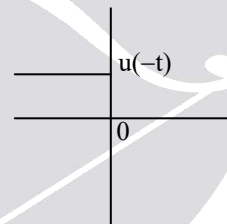

Apply KVL in loop1  $\Rightarrow V_C(0^-) - 100 = 0$


$$\Rightarrow V_C(0^-) = 100V$$

At  $t = 0^+$

$$V_L(0^+) = 0$$

$$L \frac{di(0^+)}{dt} = 0$$


$$\frac{di(0^+)}{dt} = 0$$

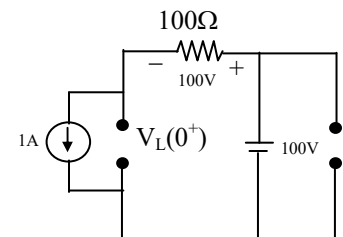

**21.**

**Sol:** Case -1 at  $t = 0^+$


By redrawing the circuit

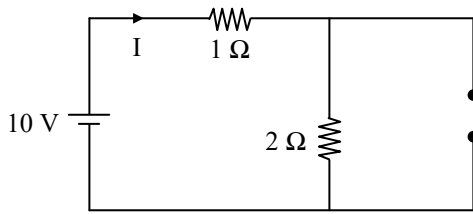

Current through the battery at  $t = 0^+$  is

$$\frac{10}{3} \text{ Amp}$$


Case -2 at  $t = \infty$

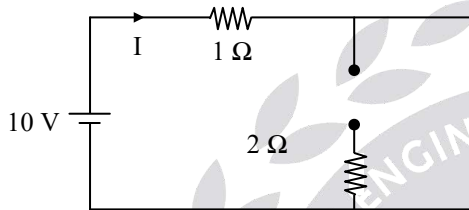

Current through the battery at  $t = \infty$  is 10 A

22.

Sol:

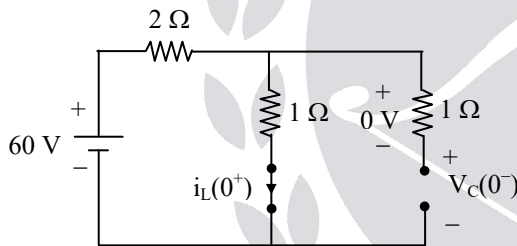


At  $t = 0^-$  : Steady state: A resistive circuit

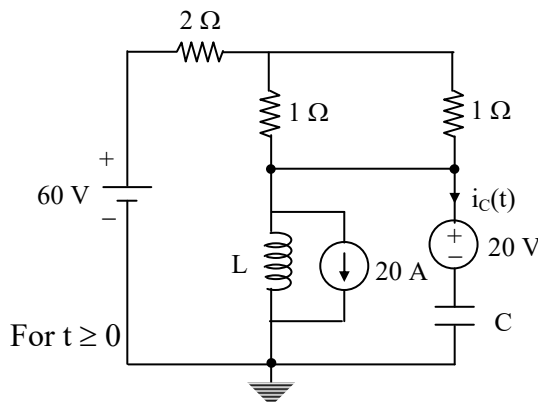
(i)  $t = 0^-$  :

$$i_L(0^-) = \frac{60}{3} = 20 \text{ A} = i_L(0^+)$$

$$V_{1\Omega} = 20 \text{ V} = V_C(0^-) = V_C(0^+)$$



For  $t \geq 0$

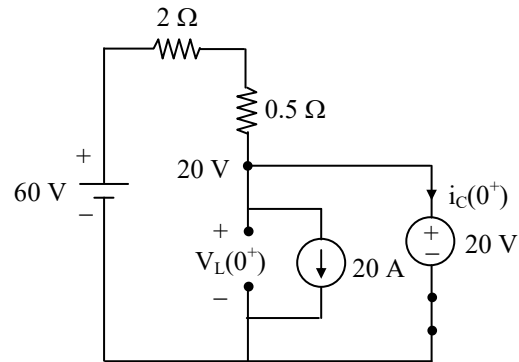

At  $t = 0^+$  : A resistive circuit :  
Network is in transient state

$$V_L(0^+) = 20 \text{ V}$$

Nodal :

$$\frac{20 - 60}{2.5} + 20 + i_C(0^+) = 0$$

$$i_C(0^+) = -4 \text{ A}$$

23.


Sol: Repeat the above problem procedure :

$$\left. \frac{di_L(t)}{dt} \right|_{t=0^+} = \frac{V_L(0^+)}{L} = 0 \text{ A/sec}$$

$$\left. \frac{dV_C(t)}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = -10^6 \text{ V/sec}$$

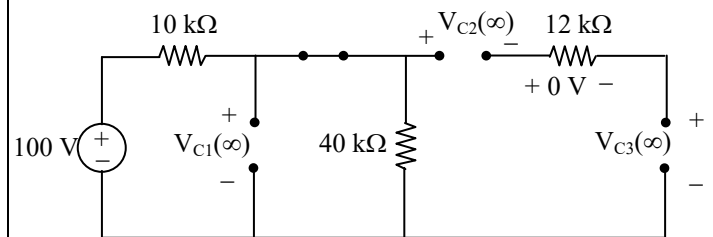24.


Sol: **Observation:** So, the steady state will occur either at  $t = 0^-$  or at  $t = \infty$ , that depends where we started i.e., connected the source to the network.



At  $t = \infty$  : Steady state: A Resistive circuit


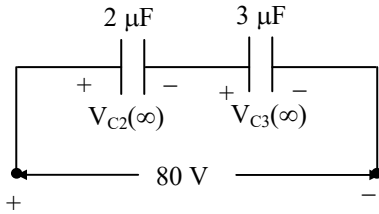
$$V_{C_1}(\infty) = \frac{100}{50K} \times 40K = 80 \text{ V}$$




$$V_{C_2}(\infty) = \frac{80 \times 3\mu\text{F}}{(2+3)\mu\text{F}} = 48 \text{ V}$$

$$V_{C_3}(\infty) = \frac{80 \times 2\mu\text{F}}{5\mu\text{F}} = 32 \text{ V}$$

25.


Sol:

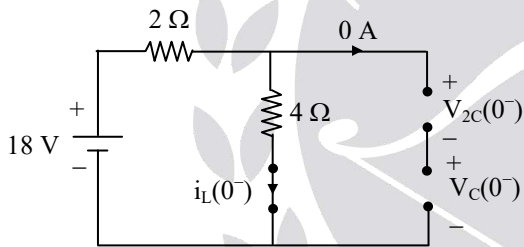

At  $t = 0^-$  : Circuit is in Steady state: Resistive circuit

$$i_L(0^-) = 3 \text{ A} = i_L(0^+)$$

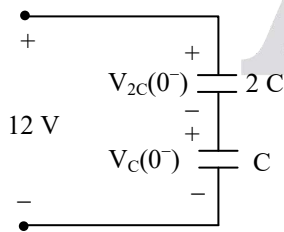
$$V_{4\Omega} = 4 \times 3 = 12 \text{ V}$$



$$V_{2C}(0^-) = \frac{12 \times C}{2C + C}$$


$$= 4 \text{ V} = V_{2C}(0^+)$$

$$V_C(0^-) = 8 \text{ V} = V_C(0^+)$$

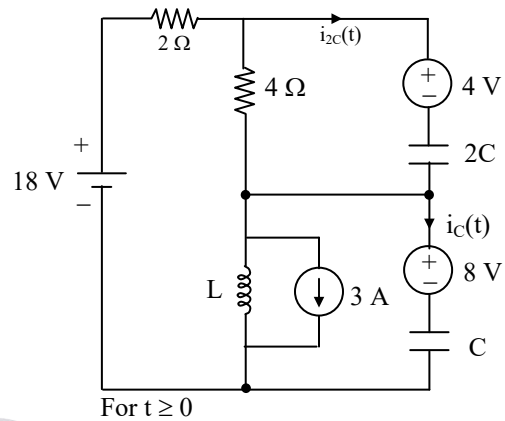

For  $t \geq 0$

and redrawing the circuit

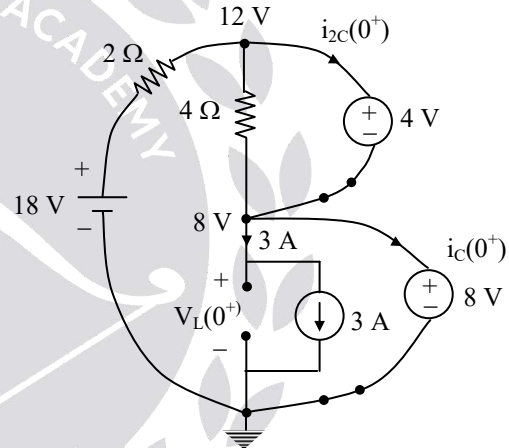

By Nodal;

$$\frac{12 - 18}{2} + \frac{12 - 8}{4} + i_{2C}(0^+) = 0$$

$$\frac{-6}{2} + \frac{4}{4} + i_{2C}(0^+) = 0$$

$$i_{2C}(0^+) = 2 \text{ A} = i_{2C}(0^-)$$

$$\frac{8 - 12}{4} - i_{2C}(0^+) + 3 + i_C(0^+) = 0$$

$$i_C(0^+) = 0 \text{ A} = i_C(0^-)$$

26.

Sol:  $t = 0^-$        $t = 0^+$        $t = 0^+$

$$i_L(0^-) = 5 \text{ A} \quad i_L(0^+) = 5 \text{ A}$$

$$\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L} = 40$$

$$i_R(0^-) = -5 \text{ A} \qquad i_R(0^+) = -1 \text{ A}$$

$$\frac{di_R(0^+)}{dt} = -40 \text{ A/sec}$$

$$i_C(0^-) = 0 \text{ A} \qquad i_C(0^+) = 4 \text{ A}$$

$$\frac{di_C(0^+)}{dt} = -40 \text{ A/sec}$$

$$V_L(0^-) = 0 \text{ V}$$

$$V_L(0^+) = 120 \text{ V}$$

$$\frac{dV_L(0^+)}{dt} = 1098 \text{ V/sec}$$

$$V_R(0^-) = -150 \text{ V}$$

$$V_R(0^+) = -30 \text{ V}$$

$$\frac{dV_R(0^+)}{dt} = -1200 \text{ V/sec}$$

$$V_C(0^-) = 150 \text{ V}$$

$$V_L(0^+) = 150 \text{ V}$$

$$\frac{dV_C(0^+)}{dt} = 108 \text{ V/sec}$$

(i).  $t = 0^-$

$$\text{By KCL} \Rightarrow i_L(t) + i_R(t) = 0$$

$$t = 0^- \Rightarrow i_L(0^-) + i_R(0^-) = 0$$

$$i_R(0^-) = -5 \text{ A}$$

$$V_R(t) = R i_R(t) \text{ |By Ohm's law}$$

$$V_R(0^-) = R i_R(0^-) = 30(-5) = -150 \text{ V}$$

$$\text{By KVL} \Rightarrow V_L(t) - V_R(t) - V_C(t) = 0$$

$$V_C(0^-) = V_L(0^-) - V_R(0^-) = 150 \text{ V}$$

(ii). At  $t = 0^+$

$$\text{By KCL at 1}^{\text{st}} \text{ node} \Rightarrow$$

$$-4 + i_L(t) + i_R(t) = 0$$

$$-4 + i_L(0^+) + i_R(0^+) = 0$$

$$i_R(0^+) = -i_L(0^+) + 4$$

$$i_R(0^+) = -5 + 4 = -1 \text{ A}$$

$$V_R(t) = R i_R(t) \text{ |By Ohm's law}$$

$$V_R(0^+) = R i_R(0^+)$$

$$V_R(0^+) = -30 \text{ V}$$

$$\text{By KVL} \Rightarrow V_L(t) - V_R(t) - V_C(t) = 0$$

$$V_L(0^+) = V_R(0^+) + V_C(0^+)$$

$$= 150 - 30 = 120 \text{ V}$$

$$\text{By KCL at 2}^{\text{nd}} \text{ node};$$

$$-5 + i_C(t) - i_R(t) = 0$$

$$i_C(0^+) = 4 \text{ A}$$

(iii).  $t = 0^+$

$$\text{By KCL at 1}^{\text{st}} \text{ node} \Rightarrow$$

$$-4 + i_L(t) + i_R(t) = 0$$

$$0 + \frac{di_L(t)}{dt} + \frac{d}{dt} i_R(t) = 0$$

$$V_R(t) = R i_R(t) \text{ |By Ohm's law}$$

$$\frac{d}{dt} V_R(t) = R \frac{d}{dt} i_R(t)$$

$$\text{By KVL} \Rightarrow$$

$$V_L(t) - V_R(t) - V_C(t) = 0$$

$$\frac{dV_L(t)}{dt} - \frac{dV_R(t)}{dt} - \frac{dV_C(t)}{dt} = 0$$

$$\text{By KCL at node 2:}$$


$$-5 + i_C(t) - i_R(t) = 0$$

$$0 + \frac{d}{dt} i_C(t) - \frac{d}{dt} i_R(t) = 0$$

$$\frac{d}{dt} i_C(0^+) = -(-40) = 40 \text{ A/sec}$$

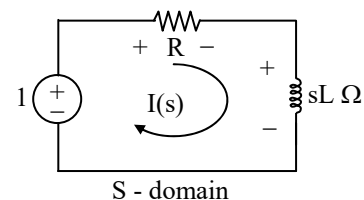27.

**Sol:** Transform the network into Laplace domain



$$V(s) = Z(s) I(s)$$

$$\text{By KVL in S-domain} \Rightarrow$$

$$1 - R I(s) - s L I(s) = 0$$


$$I(s) = \frac{1}{L} \frac{1}{\left(s + \frac{R}{L}\right)}$$

$$i(t) = \frac{1}{L} e^{-\frac{R}{L}t} \text{ A for } t \geq 0$$

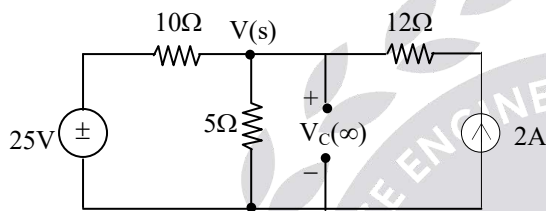28.

**Sol:** By Time domain approach;

$$V_C(0^-) = 5 \times 2 = 10 \text{ V} = V_C(0^+)$$



At  $t = \infty$ : Steady state: A resistive circuit

$$\text{Nodal} \Rightarrow \frac{V_C(\infty) - 25}{10} + \frac{V_C(\infty)}{5} - 2 = 0$$

$$V_C(\infty) = 15 \text{ V}$$

$$\tau = R_{eq} C = (5 \parallel 10) \cdot 1 = (10/3) \text{ sec}$$


$$V_C = 15 + (10 - 15) e^{-\frac{t}{(10/3)}}$$

$$V_C = 15 - 5 e^{-3t/10} \text{ V for } t \geq 0$$

$$i_C = C \frac{dV_C}{dt} = 1.5 e^{-3t/10} \text{ A for } t \geq 0$$

29.

**Sol:**

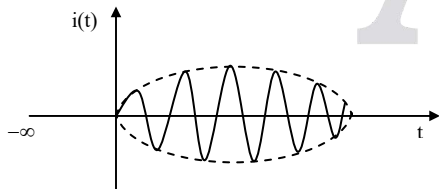

That is the response is oscillatory in nature

30.



**Sol:**  $i(0^-) = 0 \text{ A} = i(0^+)$

$$i(\infty) = \frac{V}{R} \text{ A}$$

$$\tau = \frac{L}{R} \text{ sec}$$

$$i(t) = \frac{V}{R} + \left(0 - \frac{V}{R}\right) e^{-t/\tau} = \frac{V}{R} (1 - e^{-t/\tau})$$
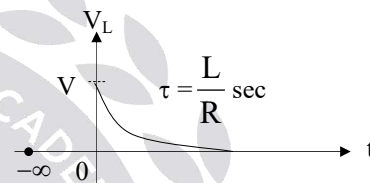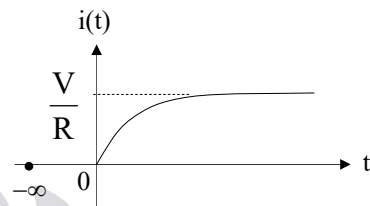
$$V_L = \frac{L di(t)}{dt} = V e^{-Rt/L} \text{ for } t \geq 0$$



Exponentially Increasing Response

31.

**Sol:**  $V_C(0^-) = 0 = V_C(0^+)$



$$V_C(\infty) = V$$

$$\tau = RC$$

$$V_C = V + (0 - V) e^{-t/\tau} = V(1 - e^{-t/RC}) \text{ for } t \geq 0$$

$$i_C = C \frac{dV_C}{dt} = \frac{V}{R} e^{-t/RC} \text{ for } t \geq 0$$

$$= i(t)$$

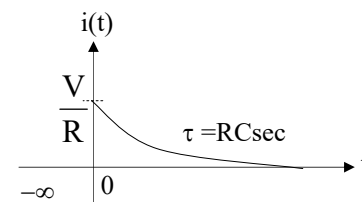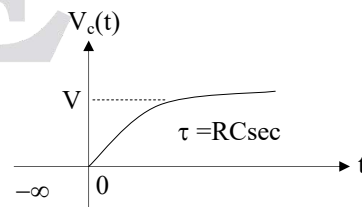


Exponentially Decreasing Response

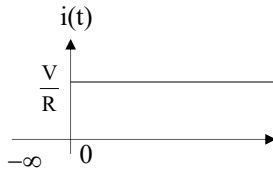32.

**Sol:** It's an RL circuit with  $L = 0 \Rightarrow \tau = 0$  sec

$$i(t) = \frac{V}{R}, \forall t \geq 0 \text{ So, } 5\tau = 0 \text{ sec}$$



i.e., the response is constant

33.

**Sol:**  $i_1 = \frac{100u(t) - V_L}{10}$

$$i_1 = \left( 10u(t) - \frac{1}{100} \frac{di_L}{dt} \right) \text{A}$$

Nodal  $\Rightarrow$

$$-i_1 + i_L + \frac{V_L - 20i_1}{20} = 0$$

$$-2i_1 + i_L + \frac{1}{200} \frac{di_L}{dt} = 0$$

Substitute  $i_1$ ;

$$\frac{di_L}{dt} + 40i_L = 800u(t)$$

$$sI_L(s) - i_L(0^+) + 40I_L(s) = \frac{800}{s}$$

$$i_L(0^-) = 0 \text{A} = i_L(0^+)$$

$$I_L(s) = \frac{800}{s(s+40)} = \frac{20}{s} - \frac{20}{s+40}$$

$$I_L(t) = 20u(t) - 20e^{-40t} u(t)$$


$$I_L(t) = 20(1 - e^{-40t}) u(t)$$

$$i_1 = 10u(t) - \frac{1}{100} d \frac{i_L}{dt}$$


$$i_1 = (10 - 8e^{-40t}) u(t)$$

34.

**Sol:** By Laplace transform approach:

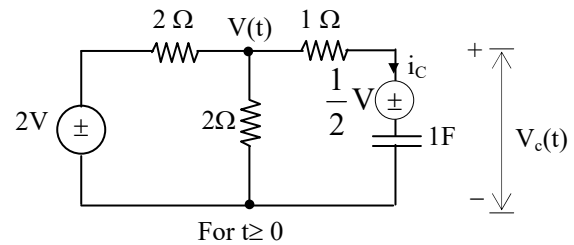

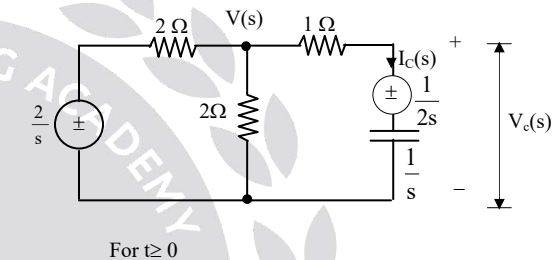Transform the above network into the Laplace domain



Nodal  $\Rightarrow$

$$\frac{V(s) - \frac{2}{s}}{2} + \frac{V(s)}{2} + \frac{V(s) - \frac{1}{2s}}{1 + \frac{1}{s}} = 0$$

$$I_c(s) = \left( \frac{V(s) - \frac{1}{2s}}{1 + \frac{1}{s}} \right)$$



$$\Rightarrow i_c(t) = \frac{1}{4} e^{-\frac{t}{2}} \text{ A for } t \geq 0$$

By KVL  $\Rightarrow$

$$V_c(s) - \frac{1}{2s} - \frac{1}{s} I_c(s) = 0$$

$$V_c(s) = \frac{1}{2s} + \frac{1}{s} I_c(s)$$
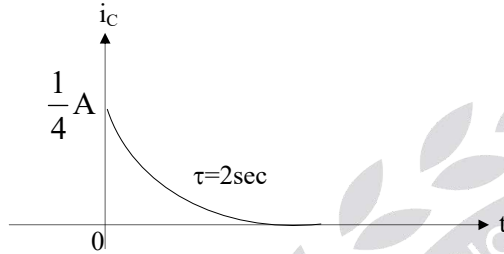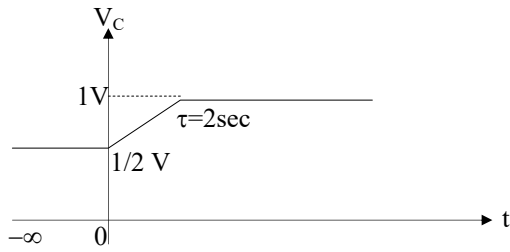
$$v_c(t) = 1 - \frac{1}{2} e^{-\frac{t}{2}} \text{ V for } t \geq 0$$




35.

**Sol:** By Time domain approach ;

$$V_C(0) = 6 \text{ V (given)}$$

$$V_C(\infty) = 10 \text{ V}$$

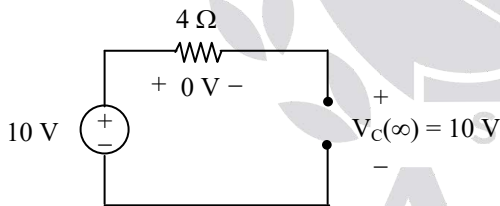

At  $t = \infty$  : Steady state : Resistive circuit

$$\tau = RC = 8 \text{ sec}$$

$$V_C = 10 + (6 - 10) e^{-t/8}$$

$$V_C = 10 - 4 e^{-t/8}$$


$$V_C(0) = 6 \text{ V}$$

$$i_C = C \frac{dV_C}{dt} = e^{-t/8} = i(t)$$

$$E_{4\Omega} = \int_0^{\infty} (e^{-t/8})^2 \cdot 4 \, dt = 16 \text{ J}$$

36.

**Sol:**

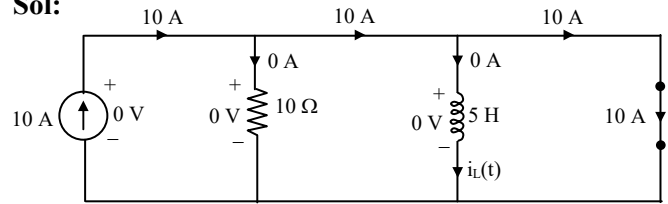


At  $t = 0^-$  : Network is not in steady state i.e., unenergised

$t = 0^-$  :

$$i_L(0^-) = 0 \text{ A} = i_L(0^+)$$
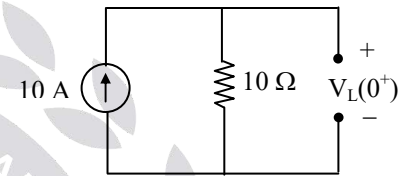
$$V_L(0^+) = 10 \times 10 = 100 \text{ V}$$



At  $t = 0^+$  : Network is in transient state : A resistive circuit

$$i_L(\infty) = 10 \text{ A (since inductor becomes short)}$$

$$\tau = \frac{L}{R} = \frac{5}{10} = 0.5 \text{ sec}$$

$$i_L(t) = 10 + (0 - 10) e^{-t/\tau}$$


$$= 10 (1 - e^{-t/0.5}) \text{ A for } 0 \leq t \leq \infty$$

$$V_L(t) = L \frac{d}{dt} i_L(t) = 100 e^{-2t} \text{ V for } 0 \leq t \leq \infty$$

$$E_L \Big|_{t=5\tau \text{ or } t=\infty} = \frac{1}{2} Li^2 = \frac{1}{2} \times 5 \times 10^2 = 250 \text{ J}$$

37. **Ans: (b)**

**Sol:**

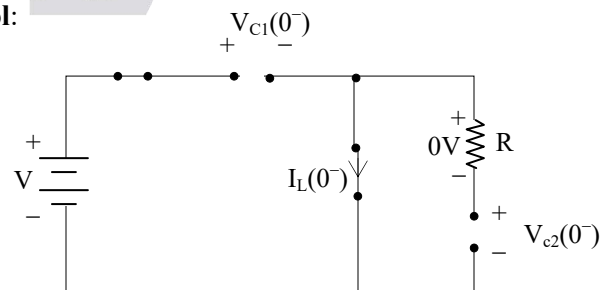

At  $t = 0^-$  : Steady state: A resistive circuit


By KVL  $\Rightarrow$

$$V - V_{C1}(0^-) = 0$$


$$V_{C1}(0^-) = V = V_{C1}(0^+)$$

$$V_{C2}(0^-) = 0V = V_{C2}(0^+)$$

$$i_L(0^-) = 0A = i_L(0^+)$$

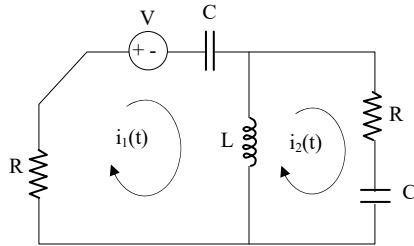

For  $t \geq 0$  Fig (a)

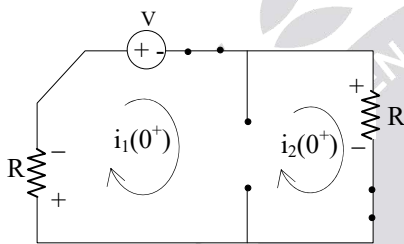

At  $t = 0^+$ : A resistive circuit: Network is in transient state.

$$i_1(0^+) = i_2(0^+)$$

By KVL  $\Rightarrow$

$$-Ri_1(0^+) - V - Ri_1(0^+) = 0$$

$$i_1(0^+) = \frac{-V}{2R} = i_2(0^+)$$

OBS:  $i_L(t) = i_1(t) \sim i_2(t)$

At  $t = 0^+ \Rightarrow$

$$i_L(0^+) = i_1(0^+) \sim i_2(0^+)$$


$$= 0A \Rightarrow \text{Inductor: open circuit}$$

38.

**Sol:** Evaluation of  $i_L(t)$  and  $e_1(t)$  for  $t \geq 0$  by Laplace transform approach.


$$i_L(0^+) = 6A; i_L(\infty) = 4A$$

$$e_1(0^+) = 8V; e_1(\infty) = 8V$$

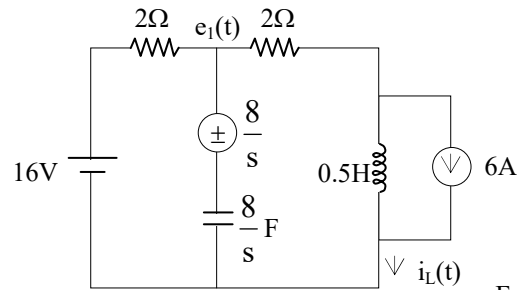


For  $t \geq 0$

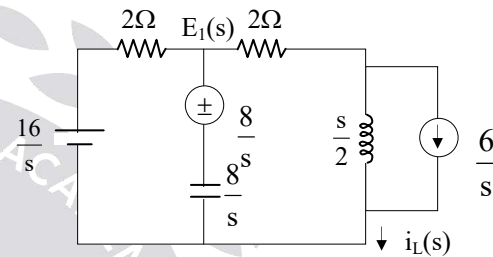Transform the above network into Laplace domain.



S-domain:

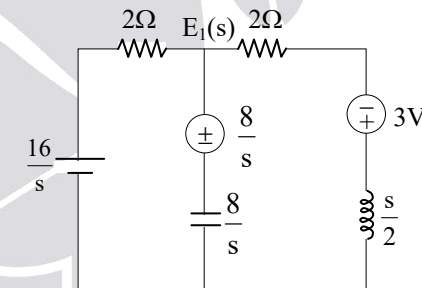


Nodal in S-domain

$$\frac{E_1(s) - 16/s}{2} + \frac{E_1(s) - \frac{8}{s}}{\frac{8}{s}} + \frac{E_1(s) + 3}{2 + \frac{s}{2}} = 0$$

$$E_1(s) = \frac{8}{s} \left( \frac{s^2 + 6s + 32}{s^2 + 8s + 32} \right)$$

$$E_1(s) = \frac{8}{s} \left( 1 - \frac{2s}{(s+4)^2 + 4^2} \right)$$

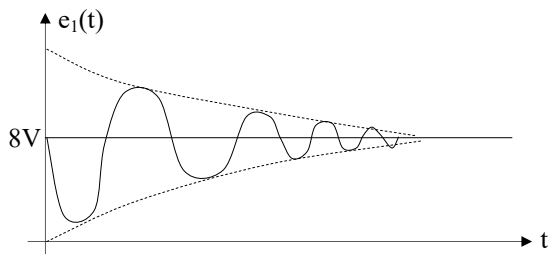
$$e_1(t) = 8 - 4e^{-4t} \sin 4t \text{ V for } t \geq 0$$



$$I_L(s) = \frac{E_1(s) + 3}{2 + \frac{s}{2}}$$

$$i_L(t) = 4 + 2e^{-4t} \cos 4t \text{ A}$$

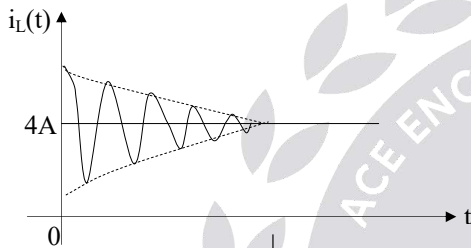for  $t \geq 0$   $\omega_n = 4 \text{ rad/sec}$



**OBS:**  $\tau = \frac{1}{4} \text{ sec} = \frac{1}{\xi \omega_n} \left| \omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{2} \times \frac{1}{8}}} = 4 \right.$

$$\frac{1}{4} \times \omega_n = \frac{1}{\xi}$$

$$\xi = \frac{4}{\omega_n} = \frac{4}{4} = 1$$

$\xi = 1$  (A critically damped system)

**39.**

**Sol:**  $\omega t|_t = t_0 = \tan^{-1} \left( \frac{\omega L}{R} \right)$

$$\omega t_0 = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$2\pi(50)t_0 = \tan^{-1} \left( \frac{2\pi(50)(0.01)}{5} \right)$$

$$t_0 = 32.14 \times \frac{\pi}{180^\circ}$$

$$t_0 = 1.78 \text{ msec.}$$

So, by switching exactly at 1.78msec from the instant voltage becomes zero, the current is free from Transient.

**40.**

**Sol:**  $\omega t_0 + \phi = \tan^{-1}(\omega CR) + \frac{\pi}{2}$


$$2t_0 + \frac{\pi}{4} = \tan^{-1}(\omega CR) + \frac{\pi}{2}$$

$$2t_0 + \frac{\pi}{4} = \tan^{-1} \left( 2 \left( \frac{1}{2} \right) (1) \right) + \frac{\pi}{2} = \frac{\pi}{4} + \frac{\pi}{2}$$


$$2t_0 = \frac{\pi}{2} \Rightarrow t_0 = 0.785 \text{ sec}$$

**41. Ans: (b, c, d)**

**Sol:**

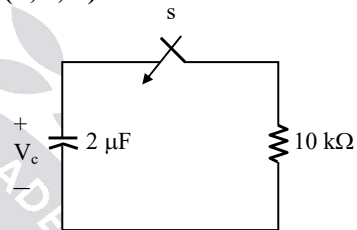

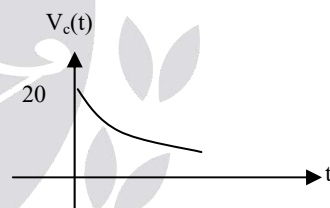(b)  $V_c(t) = V_c(0)e^{-t/\tau}$   
 $V_c = 20e^{-t/\tau} = 20e^{-t/(1/50)}$   
 $= 20e^{-50t} \text{ V}$



(c)  $i_c(t) = C \frac{dV_c(t)}{dt}$   
 $= 2 \times 10^{-6} \times 20 e^{-50t} \times (-50)$   
 $i_c(t) = -2e^{-50t} \text{ mA}$

(d)  $\tau = RC = (10k)(2\mu)$   
 $= 20 \text{ ms}$   
 $= \frac{20}{1000} = 1/50 \text{ sec}$

**42. Ans: (a, c)**

**Sol:** At  $t = 0^+$ ;  $i_1(0) = 2 \text{ A} \neq i_2(0) = 1 \text{ A}$

So,  $2 \text{ A} \neq 1 \text{ A}$

The given network violates KCL at  $t = 0^+$

Constant current applied to inductor the voltage across inductor is impulse.

# Chapter

# 4

# AC Circuit Analysis

01.

$$\text{Sol: } I_{\text{avg}} = I_{\text{dc}} = \frac{1}{T} \int_0^T i(t) dt$$

$$= 3 + 0 + 0 = 3A$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$= \sqrt{3^2 + \left(\frac{4\sqrt{2}}{\sqrt{2}}\right)^2 + \left(\frac{5\sqrt{2}}{\sqrt{2}}\right)^2 + 0 + 0 + 0}$$

$$= 5\sqrt{2}A$$

02.

$$\text{Sol: } V_{\text{dc}} = V_{\text{avg}} = \frac{1}{T} \int_0^T V(t) dt = 2V$$

Here the frequencies are same, by doing simplification

$$v(t) = 2 - 3\sqrt{2} \left( \cos 10t \times \frac{1}{\sqrt{2}} - \sin 10t \times \frac{1}{\sqrt{2}} \right) + 3\cos 10t$$

$$= 2 + 3\sin 10t V$$

$$\text{So } V_{\text{rms}} = \sqrt{(2)^2 + \left(\frac{3}{\sqrt{2}}\right)^2} = \sqrt{8.5} V$$

03.

$$\text{Sol: } X_{\text{avg}} = X_{\text{dc}} = \frac{1}{T} \int_0^T x(t) dt = 0$$



$$X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt} = \frac{A}{\sqrt{3}}$$

04. Ans: (a)

Sol: For a symmetrical wave (i.e., area of positive half cycle = area of negative half cycle.) The RMS value of full cycle is same as the RMS value of half cycle.

05.

Sol: Complex power,  $S = VI^*$

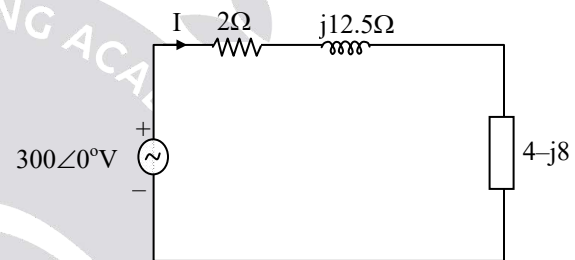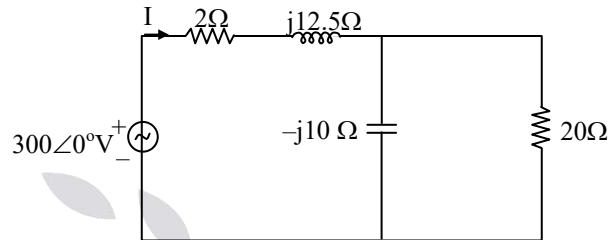

$$\Rightarrow I = \frac{300\angle 0^\circ}{2 + j12.5 + 4 - j8}$$

$$\Rightarrow I = 40\angle -36.86^\circ$$

∴ Complex power,  $S = VI^*$

$$= 300\angle 0^\circ \times 40\angle 36.86^\circ$$

$$= 9600 + j7200$$

∴ Reactive power delivered by the source

$$Q = 72000 \text{ VAR}$$

$$= 7.2 \text{ KVAR}$$

06.

$$\text{Sol: } Z = j1 + (1-j1) \parallel (1+j2) = 1.4 + j0.8$$

$$I = \frac{E_1}{Z} \Big|_{\text{By ohm's law}} = \frac{10\angle 20}{1.4 + j0.8}$$

$$= 6.2017\angle -9.744^\circ \text{ A}$$

$$I_1 = \frac{I(1+j2)}{1-j1+1+j2}$$

$$= 6.2017\angle 27.125^\circ \text{ A}$$



$$I_2 = \frac{I(1 - j1)}{1 - j1 + 1 + j2}$$

$$= 3.922 \angle -81.31^\circ \text{ A}$$


$$E_2 = (1 - j1)I_1 = 8.7705 \angle -17.875^\circ \text{ V}$$

$$E_0 = 0.5I_2 = 1.961 \angle -81.31^\circ \text{ V}$$

07.

**Sol:** Since two different frequencies are operating on the network simultaneously always the super position theorem is used to evaluate the response.


By SPT: (i)

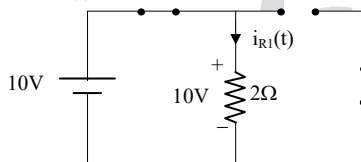

Network is in steady state, therefore the network

is resistive.  $I_{R1}(t) = \frac{10}{2} = 5 \text{ A}$


(ii)

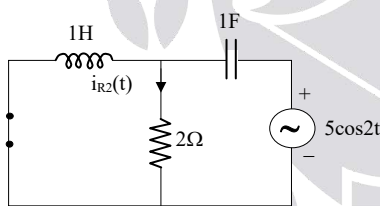

Network is in steady state

As impedances of L and C are present because of  $\omega = 2$ . They are physically present.

$$Z_L = j\omega L; Z_C = \frac{1}{j\omega C} \Big|_{\omega=2}$$

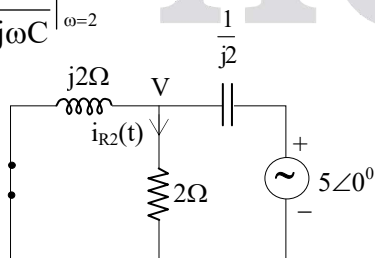

Network is in phasor domain

Nodal  $\Rightarrow$

$$\frac{V}{j2} + \frac{V}{2} + \frac{V - 5\angle 0^\circ}{-j0.5} = 0$$

$$V = 6.32 \angle 18.44^\circ$$

$$I_{R2} = \frac{V}{2} = 3.16 \angle 18.44^\circ = 3.16 e^{j18.14^\circ}$$

$$i_{R2}(t) = R.P.[I_{R2}e^{j2t}] \text{ A}$$

$$= 3.16 \cos(2t + 18.44^\circ)$$

By super position theorem,

$$i_R(t) = i_{R1}(t) + i_{R2}(t)$$

$$= 5 + 3.16 \cos(2t + 18.44^\circ) \text{ A}$$

08. **Ans: (c)**

$$\text{Sol: } \frac{1}{s^2 + 1} - I(s) \left( 2 + 2s + \frac{1}{s} \right) = 0$$

$$I(s) \left( \frac{2s + 2s^2 + 1}{s} \right) = \frac{1}{s^2 + 1}$$

$$I(s) + 2s^2 I(s) + 2s I(s) = \frac{s}{s^2 + 1}$$

$$i(t) + \frac{2d^2 i}{dt^2} + 2 \frac{di}{dt} = \cos t$$

$$2 \frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + i(t) = \cos t$$

09.

$$\text{Sol: } V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V = V_R = I.R$$

$$100 = I.20; I = 5 \text{ A}$$

$$\text{Power factor} = \cos \phi = \frac{V_R}{V} = \frac{V_R}{V_R} = 1$$

So, unity power factor.

10.


**Sol:** By KCL in phasor - domain

$$\Rightarrow -I_1 - I_2 - I_3 = 0$$

$$I_3 = -(I_1 + I_2)$$

$$i_1(t) = \cos(\omega t + 90^\circ)$$

$$I_1 = 1 \angle 90^\circ = j1$$

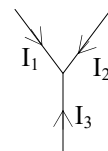

$$I_2 = 1 \angle 0^\circ = (1 + j0)$$

$$I_3 = \sqrt{2} \angle \pi + 45^\circ = \sqrt{2} e^{j(\pi+45^\circ)}$$

$$i_3(t) = \text{Real part}[I_3 \cdot e^{j\omega t}] \text{mA}$$

$$= -\sqrt{2} \cos(\omega t + 45^\circ + \pi) \text{mA}$$

$$i_3(t) = -\sqrt{2} \cos(\omega t + 45^\circ) \text{mA}$$

11.

**Sol:**  $I = \frac{V}{R} + \frac{V}{Z_L} + \frac{V}{Z_C} = 8 - j12 + j18$

$$I = 8 + 6j$$

$$|I| = \sqrt{100} = 10 \text{A}$$

12.

**Sol:** By KCL  $\Rightarrow$

$$-I + I_L + I_C = 0$$

$$I = I_L + I_C$$


$$I_L = \frac{V}{Z_L} = \frac{V}{j\omega L} = \frac{3 \angle 0^\circ}{j(3) \cdot \left(\frac{1}{3}\right)}$$

$$I_L = \frac{3 \angle 0^\circ}{j} = \frac{3 \angle 0^\circ}{\angle 90^\circ} = 3 \angle -90^\circ$$

$$I = 3 \angle -90^\circ + 4 \angle 90^\circ = -j3 + j4 = j1 = 1 \angle 90^\circ$$

13. **Ans: (d)**

**Sol:**

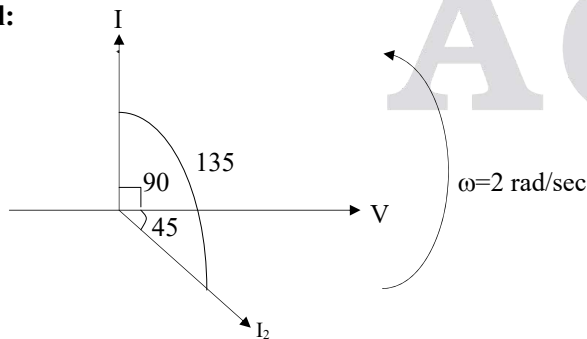

$$I_1 = I_C = \frac{V}{Z_C} = \frac{V}{X_C} \angle 90^\circ$$

$$I_2 = \frac{V}{2 + j\omega L} = \frac{V}{2 + j2} = \frac{V}{2\sqrt{2}} \angle 45^\circ$$

Therefore, the phasor  $I_1$  leads  $I_2$  by an angle of  $135^\circ$ .

14.

**Sol:**  $I_2 = \sqrt{I_R^2 + I_C^2} \Rightarrow 10 = \sqrt{I_R^2 + 8^2}$

$$I_R = 6 \text{A}$$

$$I_1 = I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$10 = \sqrt{6^2 + (I_L - I_C)^2}$$

$$I_L - I_C = \pm 8 \text{A}$$

$$I_L - 8 = \pm 8$$


$$I_L - 8 = -8 \text{ (Not acceptable)}$$

$$\text{Since } I_L = \frac{V}{Z_L} \neq 0.$$

$$I_L - 8 = 8$$

$$I_L = 16 \text{A}$$

$$I_L > I_C$$

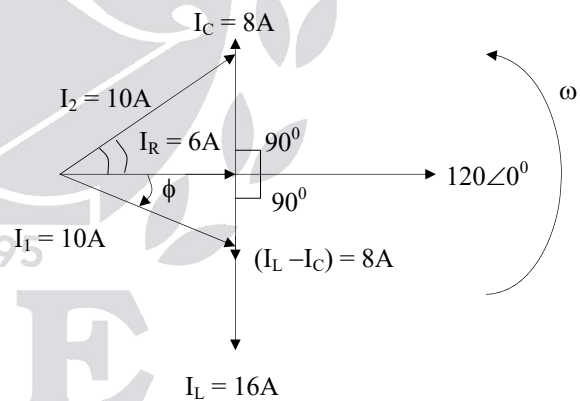

$$I_2 \text{ leads } 120 \angle 0^\circ \text{ by } \tan^{-1} \left( \frac{8}{6} \right)$$


$$I_1 \text{ lags } 120 \angle 0^\circ \text{ by } \tan^{-1} \left( \frac{8}{6} \right)$$

$$\text{Power factor } \cos \phi = \frac{I_R}{I} = \frac{I_R}{I}$$

$$= \frac{6}{10} = 0.6 \text{ (lag)}$$

15.

Sol:

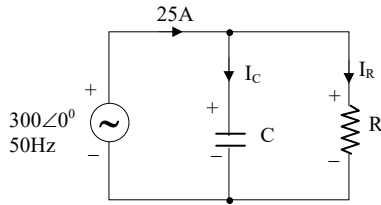

Network is in steady state.

$$|I_C| = \frac{|V|}{|Z_C|} = \frac{300\angle 0^\circ}{|1/j\omega C|} = v\omega C$$


$$= 300 \times 2\pi \times 50 \times 159.23 \times 10^{-6}$$

$$I_C = 15A$$

$$I = \sqrt{I_R^2 + I_C^2}$$

$$25 = \sqrt{I_R^2 + 15^2}$$

$$I_R = 20A$$

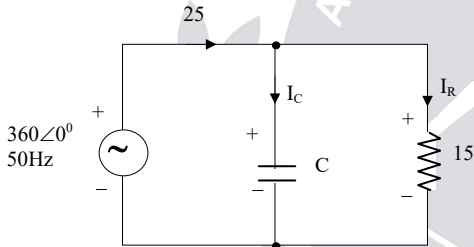

$$V_R = RI_R \text{ | By ohm's law}$$

$$300 = R \cdot 20$$

$$R = 15\Omega$$

Network is in steady state

$$I_R = \frac{360}{15} = 24A$$

$$\text{So the required } I_C = \sqrt{25^2 - 24^2}$$

$$v\omega C = 7$$

$$360 \times 2\pi \times f \times 159.23 \times 10^{-6} = 7$$

$$f = 19.4Hz$$

$$\text{OBS: } I_C = \frac{V}{Z_C}$$

$$Z_C = \frac{1}{j\omega C} \Omega$$

As  $f \downarrow \Rightarrow Z_C \uparrow \Rightarrow I_C \downarrow$

16.

$$\text{Sol: } P_{5\Omega} = 10 \text{ Watts (Given)}$$

$$= P_{avg} = I_{rms}^2 R$$

$$10 = I_{rms}^2 \cdot 5$$

$$I_{rms} = \sqrt{2} \text{ A}$$

Power delivered = Power observed

(By Tellegen's Theorem)

$$P_T = I_{rms}^2 (5 + 10)$$

$$V_{rms} I_{rms} \cos\phi = (\sqrt{2})^2 (15)$$

$$\frac{50}{\sqrt{2}} \times \sqrt{2} \cos\phi = 2 \times 15$$

$$\cos\phi = 0.6 \text{ (lag)}$$

17. Ans: (d)

Sol:

$$V_L = 14V$$

$$V$$

$$V_R = 3V$$

$$V_C = 10V$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= \sqrt{(3)^2 + (14 - 10)^2}$$

$$V = 5V$$

18.

$$\text{Sol: } Y = Y_1 + Y_c = \frac{1}{Z_L} + \frac{1}{Z_C}$$

$$= \frac{1}{30\angle 40^\circ} + \frac{1}{\left(\frac{1}{j\omega C}\right)}$$

$$= j\omega C + \frac{1}{30} \angle -40^\circ$$

$$= j\omega C + \frac{1}{30} (\cos 40^\circ - j\sin 40^\circ)$$

Unit power factor  $\Rightarrow$  j-term = 0

$$\omega C = \frac{\sin 40^\circ}{30}$$

$$C = \frac{\sin 40^\circ}{2\pi \times 50 \times 30} = 68.1 \mu\text{F}$$

$$C = 68.1 \mu\text{F}$$

**19. Ans: (b)**

**Sol:** To increase power factor shunt capacitor is to be placed.

VAR supplied by capacitor

$$= P (\tan \phi_1 - \tan \phi_2)$$

$$= 2 \times 10^3 [\tan(\cos^{-1} 0.65) - \tan(\cos^{-1} 0.95)]$$

$$= 1680 \text{ VAR}$$

$$\text{VAR supplied} = \frac{V^2}{X_C} = V^2 \omega C = 1680$$

$$\therefore C = \frac{1680}{(115)^2 \times 2\pi \times 60} = 337 \mu\text{F}$$

**20.**

$$\text{Sol: } Z = \frac{V}{I} = \frac{160 \angle 10^\circ - 90^\circ}{5 \angle -20^\circ - 90^\circ} = 32 \angle 30^\circ$$

$$\phi = 30^\circ \text{ (Inductive)}$$

$$V_{\text{rms}} = \frac{160}{\sqrt{2}} \text{ V, } I_{\text{rms}} = \frac{5}{\sqrt{2}}$$

$$\text{Real power (P)} = \frac{160}{\sqrt{2}} \times \frac{5}{\sqrt{2}} \times \cos 30^\circ$$

$$= 200\sqrt{3} \text{ W}$$

$$\text{Reactive power (Q)} = \frac{160}{\sqrt{2}} \times \frac{5}{\sqrt{2}} \times \frac{1}{2}$$

$$= 200 \text{ VAR}$$

$$\text{Complex power} = P + jQ = 200(\sqrt{3} + j1) \text{ VA}$$

**21.**

$$\text{Sol: } V = 4 \angle 10^\circ \text{ and } I = 2 \angle -20^\circ$$

**Note:** When directly phasors are given the magnitudes are taken as rms values since they are measured using rms meters.

$$V_{\text{rms}} = 4 \text{ V and } I_{\text{rms}} = 2 \text{ A}$$

$$Z = \frac{V}{I} = 2 \angle 30^\circ; \phi = 30^\circ \text{ (Inductive)}$$

$$P = 10\sqrt{3} \text{ W, } Q = 10 \text{ VAR}$$

$$S = 10(\sqrt{3} + j1) \text{ VA}$$

**22. Ans: (a)**

$$\text{Sol: } S = VI^*$$

$$= (10 \angle 15^\circ) (2 \angle 45^\circ)$$

$$= 10 + j17.32$$

$$S = P + jQ$$

$$P = 10 \text{ W } Q = 17.32 \text{ VAR}$$

**23. Ans: (c)**

$$\text{Sol: } P_R = (I_{\text{rms}})^2 \times R$$

$$I_{\text{rms}} = \frac{10}{\sqrt{2}}$$

$$P_R = \left(\frac{10}{\sqrt{2}}\right)^2 \times 100$$

**24.**

$$\text{Sol: } P_{\text{avg}} = \frac{V_{\text{rms}}^2}{R} = \frac{\left(\frac{240}{\sqrt{2}}\right)^2}{60} = 480 \text{ Watts}$$

$$V = 240 \angle 0^\circ$$

$$I_R = \frac{V}{R} = \frac{240}{60} = 4 \text{ A}$$

$$I_L = \frac{V}{Z_L} = \frac{V}{X_L} = \frac{240}{40} = 6 \text{ A}$$

$$I_C = \frac{V}{Z_C} = \frac{V}{X_C} = \frac{240}{80} = 3 \text{ A}$$


$I_L > I_C$  : Inductive nature of the circuit.

$$I = \sqrt{I_R^2 + (I_L - I_C)^2} = \sqrt{4^2 + 3^2} = 5A$$

$$\text{Power factor} = \frac{I_R}{I} = \frac{4}{5} = 0.8 \text{ (lagging)}$$

**25. Ans: (a)**

**Sol:**

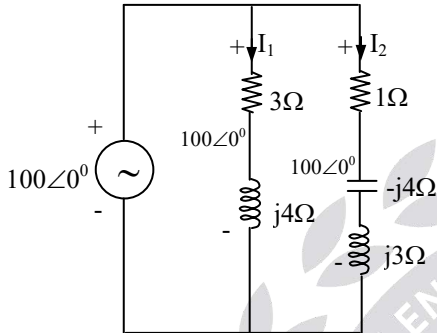

NW is in Steady state.

$$V = 100\angle 0^\circ \Rightarrow V_{\text{rms}} = 100V$$

$$I_1 = \frac{100\angle 0^\circ}{(3 + j4)\Omega} \Rightarrow |I_1| = 20 = I_{1\text{rms}}$$

$$I_2 = \frac{100\angle 0^\circ}{(1 - j1)\Omega} \Rightarrow |I_2| = \frac{100}{\sqrt{2}} A = I_{2\text{rms}}$$

$$\begin{aligned} P &= P_1 + P_2 \\ &= (I_{1\text{rms}})^2 \cdot 3 + (I_{2\text{rms}})^2 \cdot 1 \\ &= 20^2 \cdot 3 + \left(\frac{100}{\sqrt{2}}\right)^2 \cdot 1 \end{aligned}$$



$$P = 6200 \text{ W}$$

$$\begin{aligned} Q &= Q_1 + Q_2 \\ &= (I_{1\text{rms}})^2 \cdot 4 + (I_{2\text{rms}})^2 \cdot (1) \\ &= 3400 \text{ VAR} \end{aligned}$$

$$\text{So, } S = P + jQ = (6200 + j3400) \text{ VA}$$

**26.**

**Sol:**

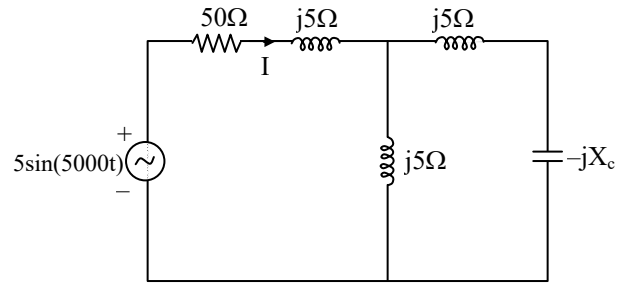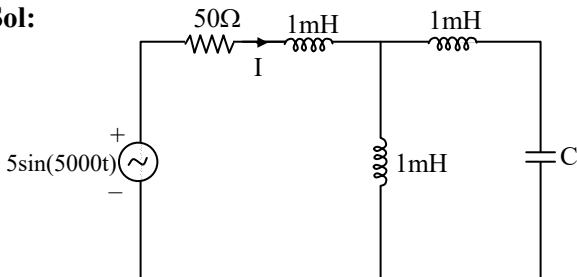

when  $I = 0$ ,

$\Rightarrow$  impedance seen by the source should be infinite

$$\Rightarrow Z = \infty$$

$$\begin{aligned} \therefore Z &= (50 + j5) + (j5) \parallel j(5 - X_c) \\ &= 50 + j5 + \frac{j5 \times j(5 - X_c)}{j5 + j(5 - X_c)} = \infty \end{aligned}$$

$$\Rightarrow j(10 - X_c) = 0$$

$$\Rightarrow X_c = 10 \Rightarrow \frac{1}{\omega C} = 10$$

$$\Rightarrow C = \frac{1}{5000 \times 10} = 20 \mu\text{F}$$

**27. Ans: (c)**

$$\begin{aligned} \text{Sol: } I_{\text{rms}} &= \sqrt{3^2 + \left(\frac{4}{\sqrt{2}}\right)^2 + \left(\frac{4}{\sqrt{2}}\right)^2} \\ &= \sqrt{25} = 5 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Power dissipation} &= I_{\text{rms}}^2 R \\ &= 5^2 \times 10 \\ &= 250 \text{ W} \end{aligned}$$

**28.**

$$\text{Sol: } X_C = X_L$$

$\Rightarrow \omega = \omega_0$ , the circuit is at resonance

$$V_C = QV_S \angle -90^\circ$$

$$Q = \frac{\omega_0 L}{R} = \frac{X_L}{R} = 2$$

$$= \frac{1}{\omega_0 c R} = \frac{X_C}{R} = 2$$

$$\Rightarrow V_C = 200 \angle -90^\circ$$

$$= -j200V$$

29.

**Sol:** Series RLC circuit


$$f = f_L, \text{ PF} = \cos \phi = 0.707(\text{lead})$$

$$f = f_H, \text{ PF} = \cos \phi = 0.707(\text{lag})$$

$$f = f_0, \text{ PF} = \cos \phi = 1$$

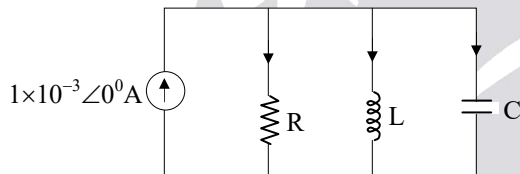30. **Ans:** (a)

**Sol:** Network is in steady state (since no switch is given)



Let  $I = 1\text{mA}$

$\omega = \omega_0$  (Given)

$$\Rightarrow I_R = I$$

$$I_L = QI \angle -90^\circ = -jQI$$

$$I_C = QI \angle 90^\circ = jQI$$

$$I_L + I_C = 0$$

$$|I_R + I_L| = |I - jQI|$$


$$= I\sqrt{1 + Q^2} > I$$

$$|I_R + I_C| = |I + jQI|$$

$$= I\sqrt{1 + Q^2} > I$$

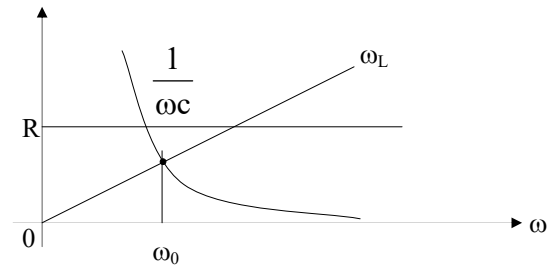31. **Ans:** (c)

**Sol:** Since; "I" leads voltage, therefore capacitive effect and hence the operating frequency ( $f < f_0$ )



32.

$$\text{Sol: } Y = \frac{1}{R_L + j\omega L} + \frac{1}{R_C - \frac{j}{\omega C}}$$


$$= \frac{R_L - j\omega L}{R_L^2 + (\omega L)^2} + \frac{R_C + j/\omega C}{R_C^2 + (1/\omega C)^2}$$

$j$  - term  $\Rightarrow 0$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}} \text{ rad/sec}$$

33.

**Sol:**

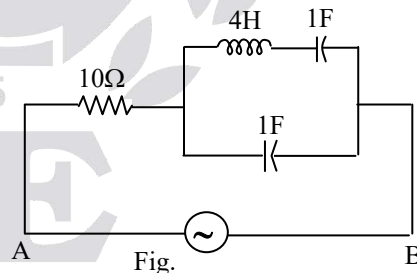

The given circuit is shown in Fig.

$$Z_{AB} = 10 + Z_1$$

$$\text{where, } Z_1 = \left( \frac{-j}{\omega} \right) \parallel \left( j4\omega - \frac{j}{\omega} \right)$$

$$= \frac{\left( \frac{-j}{\omega} \right) \left( j4\omega - \frac{j}{\omega} \right)}{\frac{-j}{\omega} + j4\omega - \frac{j}{\omega}}$$

$$= \frac{4 - \frac{1}{\omega^2}}{j4\omega - \frac{j2}{\omega}}$$

For circuit to be resonant i.e.,  $\omega^2 = \frac{1}{4}$

$$\omega = \frac{1}{2} = 0.5 \text{ rad/sec}$$

$$\therefore \omega_{\text{resonance}} = 0.5 \text{ rad/sec}$$

34.

**Sol:** (i)  $\frac{L}{C} = R^2 \Rightarrow$  circuit will resonate for all the

frequencies, out of infinite number of frequencies we are selecting one frequency.

$$\text{i.e., } \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{2} \text{ rad/sec}$$

then  $Z = R = 2\Omega$ .

$$I = \frac{V}{Z} = \frac{10\angle 0^\circ}{2} = 5\angle 0^\circ$$

$$i(t) = 5\cos\left(\frac{t}{2}\right) \text{ A}$$

$$Z_L = j\omega_0 L = j2\Omega; Z_C = \frac{1}{j\omega_0 C} = -j2\Omega.$$

$$I_L = \frac{I(2 - j2)}{2 + j2 + 2 - j2} = \frac{I}{\sqrt{2}} \angle -45^\circ$$

$$i_L = \frac{5}{\sqrt{2}} \cos\left(\frac{t}{2} - 45^\circ\right) \text{ A}$$

$$i_c = \frac{I(2 + j2)}{2 + j2 + 2 - j2} = \frac{I}{\sqrt{2}} \angle 45^\circ$$

$$i_c = \frac{5}{\sqrt{2}} \cos\left(\frac{t}{2} + 45^\circ\right) \text{ A}$$

$$P_{\text{avg}} = I_{L(\text{rms})}^2 \cdot R + I_{C(\text{rms})}^2 \cdot R$$

$$= \left(\frac{5/\sqrt{2}}{\sqrt{2}}\right)^2 \cdot 2 + \left(\frac{5/\sqrt{2}}{\sqrt{2}}\right)^2 \cdot 2$$

$$= 25 \text{ watts}$$

(ii)  $\frac{L}{C} \neq R^2$  circuit will resonate at only one frequency.

$$\text{i.e., at } \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{4} \text{ rad/sec}$$

$$\text{Then } Y = \frac{2R}{R^2 + \frac{L}{C}} \text{ mho}$$

$$Y = \frac{2(2)}{2^2 + \frac{4}{4}} = \frac{4}{5} \text{ mho}$$

$$Z = \frac{5}{4} \Omega$$

$$I = \frac{V}{Z} = \frac{10\angle 0^\circ}{5/4} = 8\angle 0^\circ$$

$$i(t) = 8\cos\left(\frac{t}{4}\right) \text{ A}$$

$$Z_L = j\omega_0 L = j1\Omega$$

$$Z_C = \frac{1}{j\omega_0 C} = -j1\Omega$$

$$I_L = \frac{I(2 - j1)}{2 + j1 + 2 - j1} = \frac{\sqrt{5}}{4} I \angle \tan^{-1}\left(\frac{1}{2}\right)$$

$$i_L = \frac{8\sqrt{5}}{4} \cos\left(\frac{t}{4} - \tan^{-1}\left(\frac{1}{2}\right)\right)$$

$$I_c = \frac{I(2 + j1)}{2 + j1 + 2 - j1} = \frac{\sqrt{5}}{4} I \angle \tan^{-1}\left(\frac{1}{2}\right)$$

$$i_c = \frac{8\sqrt{5}}{4} \cos\left(\frac{t}{4} + \tan^{-1}\left(\frac{1}{2}\right)\right)$$

$$P_{\text{avg}} = I_{L(\text{rms})}^2 \cdot R + I_{C(\text{rms})}^2 \cdot R$$

$$= \left(\frac{2\sqrt{5}}{\sqrt{2}}\right)^2 \cdot 2 + \left(\frac{2\sqrt{5}}{\sqrt{2}}\right)^2 \cdot 2$$

$$= 40 \text{ watts}$$

35.

**Sol: (i)**  $Z_{ab} = 2 + (Z_L \parallel Z_C \parallel 2)$

$$= 2 + jX_L \parallel -jX_C \parallel 2$$

$$= \frac{2 + 2X_L X_C (X_L X_C - j2(X_L - X_C))}{(X_L X_C)^2 + 4(X_L - X_C)^2}$$

j-term = 0

$$\Rightarrow -2(X_L - X_C) = 0$$

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4.4}} = \frac{1}{4} \text{ rad/sec}$$

At resonance entire current flows through  $2\Omega$  only.

(ii)  $Z_{ab}|_{\omega=\omega_0} = 2 + 2 = 4\Omega$   
 $X_L = X_C$

(iii)  $V_i(t) = V_m \sin\left(\frac{t}{4}\right) V$

$$Z = 4\Omega$$

$$i(t) = \frac{V_i(t)}{Z} = \frac{V_m}{4} \sin\left(\frac{t}{4}\right) = i_R$$

$$V = 2i_R = \frac{V_m}{2} \sin\left(\frac{t}{4}\right) V = V_C = V_L$$

$$i_C = C \frac{dV_C}{dt} = \frac{V_m}{2} \cos\left(\frac{t}{4}\right)$$

$$i_C = \frac{V_m}{2} \sin\left(\frac{t}{4} + 90^\circ\right) A$$

$$i_L = \frac{1}{L} \int V_L dt = -\frac{V_m}{2} \cos\left(\frac{t}{4}\right)$$


$$i_L = \frac{V_m}{2} \sin\left(\frac{t}{4} - 90^\circ\right) A$$

OBS: Here  $i_L + i_C = 0$

$\Rightarrow$  LC Combination is like an open circuit.

36. Ans: (d)

Sol:

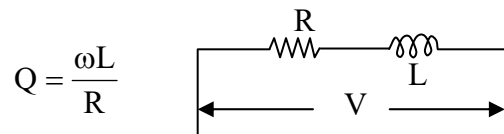

$$Q = \frac{\omega L}{R}$$

$$Q = \frac{2\omega L}{R} = 2 \times \text{original} \rightarrow Q - \text{doubled}$$

$$S = V.I = V \cdot \frac{V}{R + j\omega L} \times \frac{R - j\omega L}{R - j\omega L}$$

$$S = \frac{V^2}{R^2 + (\omega L)^2} - \frac{V^2 \cdot j\omega L}{R^2 + (\omega L)^2}$$

$$S = P + jQ$$

$$\text{Active power (P)} = \frac{V^2}{R^2 + (\omega L)^2}$$

$$P = \frac{V^2}{R^2(1 + Q^2)}$$

$$P \approx \frac{V^2}{R^2 Q^2}$$

As Q is doubled, P decreases by four times.


37.

Sol:  $Z_C = \frac{1}{j\omega C}$

$$\omega = 0; Z_C = \infty \Rightarrow C : \text{open circuit} \Rightarrow i_2 = 0$$

$$\omega = \infty; Z_C = 0 \Rightarrow C : \text{Short Circuit} \Rightarrow i_2 = \frac{E_m}{R_2} \angle 0^\circ$$

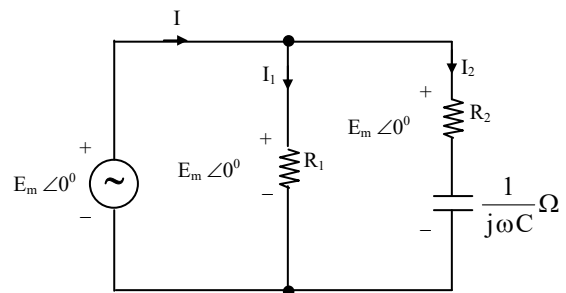Transform the given network into phasor domain.





Network is in phasor domain.

By KCL in P-d  $\Rightarrow I = I_1 + I_2$

$$I_1 = \frac{E_m \angle 0^\circ}{R_1}$$



$$I_2 = \frac{E_m \angle 0^\circ}{R_2 + \frac{1}{j\omega C}} = \frac{E_m \angle 0^\circ}{R_2 - \frac{j}{\omega C}}$$

$$I_2 = \frac{E_m \angle \tan^{-1}\left(\frac{1}{\omega CR_2}\right)}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

$$\omega = \infty \Rightarrow I_2 = \frac{E_m \angle 0^\circ}{R_2}$$

$$\omega = 0 \Rightarrow I_2 = 0 \text{ A}$$

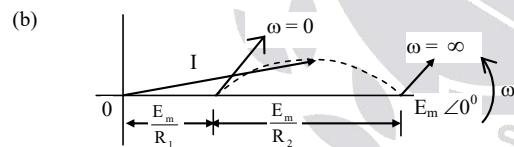
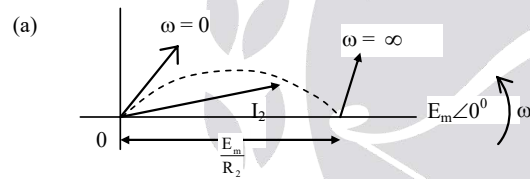
$\omega : (0 \text{ and } \infty)$  j the current phasor  $I_2$  will always lead the voltage  $E_m \angle 0^\circ$ .



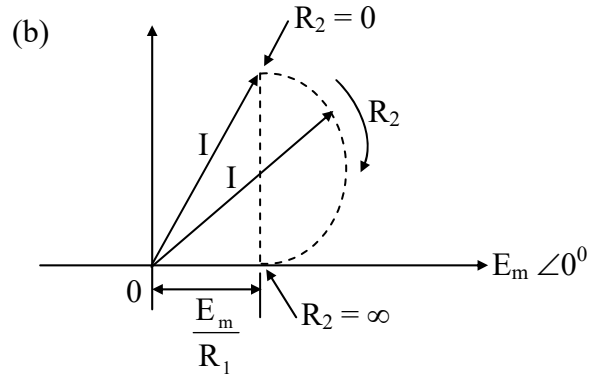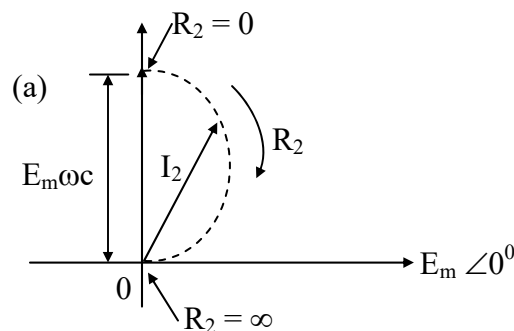38.

**Sol:**  $R_2 = 0 \Rightarrow I_2 = \frac{E_m \angle 0^\circ}{0 + \frac{1}{j\omega C}} = E_m \omega C \angle 90^\circ$

$$R_2 = \infty \Rightarrow I_2 = 0 \text{ A}$$





39.


**Sol:**  $I = I_1 + I_2; I_1 = \frac{E_m \angle 0^\circ}{R_1}$

$$I_2 = \frac{E_m \angle 0^\circ}{R_2 + j\omega L} = \frac{E_m}{\sqrt{R_2^2 + (\omega L)^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R_2}\right)$$

(i) If " $\omega$ " Varied

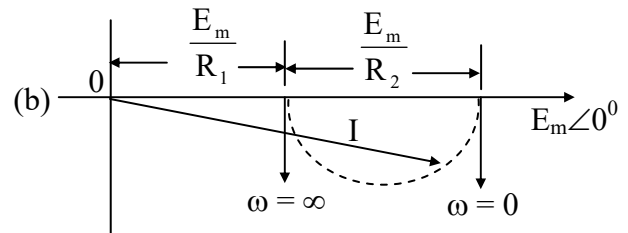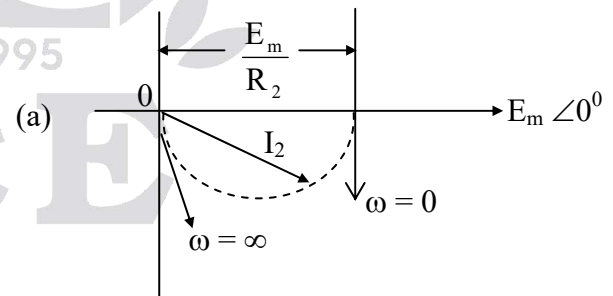

ii. If “R<sub>2</sub>” is varied

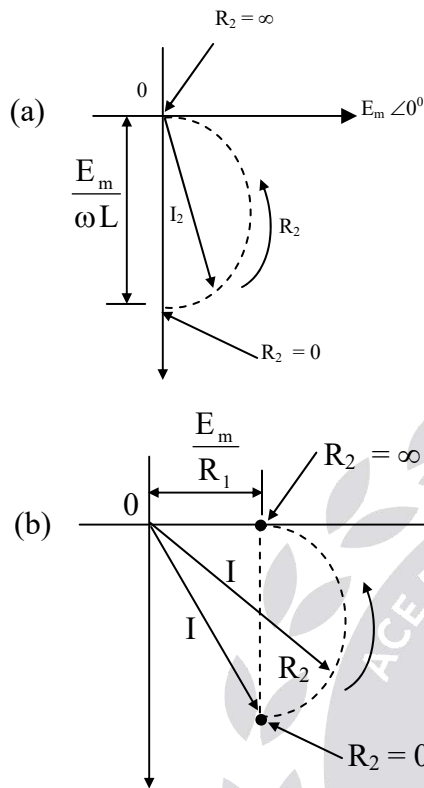

$$Y_T = \frac{1}{10 + j\omega(5m)} + j\omega(2\mu)$$

$$= \frac{10 - j\omega(5m)}{100 + \omega^2(25\mu)} + j\omega(2\mu)$$

$$= \frac{j\omega(5m)}{100 + \omega^2(25\mu)} + j\omega(2\mu)$$

$$2500 = 100 + \omega^2(25\mu)$$

$$2400 = \omega^2(25)\mu$$

$$24 \times 4 M = \omega^2$$

$$\omega = 9.8 \text{ rad/sec}$$

$$(Q) \text{ pf of coil} = \frac{R}{Z} = \frac{10}{\sqrt{10^2 + (5m \times 2000)^2}}$$

$$= \frac{1}{\sqrt{2}} = 0.707 \text{ lag}$$

$$(R) \text{ Q-factor} = \frac{\omega L}{R} = \frac{(2000)(5m)}{10} = 1$$

$\therefore$  (b, c) are correct

40. Ans: (a)

Sol: The given circuit is a bridge.

$I_R = 0$  is the bridge is balanced. i.e.,  $Z_1 Z_4 = R_2 R_3$

Where  $Z_1 = R_1 + j\omega L_1$ ,

$$Z_4 = R_4 - \frac{j}{\omega C_4}$$

As  $R_2 R_3$  is real, imaginary part of  $Z_1 Z_4 = 0$


$$\omega L_1 R_4 - \frac{R_1}{\omega C_4} = 0 \quad \text{or} \quad \frac{\omega L_1}{R_1} = \frac{1}{\omega C_4 R_4}$$

$$\text{or } Q_1 = Q_4$$

Where Q is the Quality factor.

41. Ans: (b, c)

Sol:

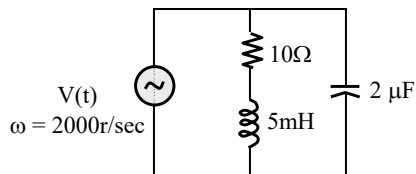

42. Ans: (a, d)

Sol:  $R = 30 \Omega$ ,  $X_L = 60 \Omega$ ,  $X_C = 20 \Omega$

$$V(t) = 100\sin 10\omega t$$

$$(a) \phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$= \tan^{-1} \left( \frac{40}{30} \right) = 53.13^\circ \text{ lag}$$

$$(b) \text{ p.f} = \cos 53.13^\circ = 0.6 \text{ lag}$$

$$(c) \text{ current is lagging by } 53.13^\circ$$

$$(d) \text{ p.f} = \cos 53.13^\circ = 0.6 \text{ lag}$$

$\therefore$  a, d are correct

# Chapter 5 Magnetic Circuits

01.

Sol:  $X_C = 12$  (Given)

$X_{eq} = 12$  (must for series resonance)

So the dot in the second coil at point "Q"

$$L_{eq} = L_1 + L_2 - 2M$$

$$L_{eq} = L_1 + L_2 - 2K\sqrt{L_1L_2}$$

$$\omega L_{eq} = \omega L_1 + \omega L_2 - 2K\sqrt{L_1L_2}\omega$$

$$12 = 8 + 8 - 2K\sqrt{8 \cdot 8}$$

$$\Rightarrow K = 0.25$$

02.

Sol:  $X_C = 14$  (Given)

$X_{Leq} = 14$  (must for series resonance)

So the dot in the 2<sup>nd</sup> coil at "P"

$$L_{eq} = L_1 + L_2 + 2M$$

$$L_{eq} = L_1 + L_2 + K\sqrt{L_1L_2}$$

$$\omega L_{eq} = \omega L_1 + \omega L_2 + 2K\sqrt{\omega L_1L_2}$$


$$14 = 2 + 8 + 2K\sqrt{2(8)}$$

$$\Rightarrow K = 0.5$$

03.

Sol:  $L_{ab} = 4H + 2 - 2 + 6H + 2 - 2 + 8H - 2 - 2$

$$L_{ab} = 14H$$

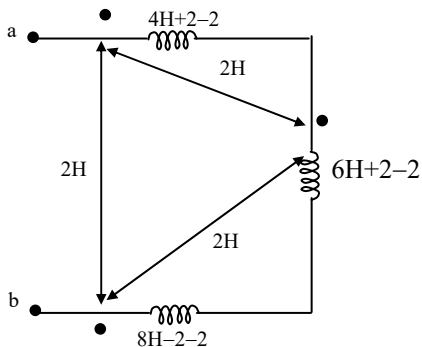


04. Ans: (c)

Sol: Impedance seen by the source

$$\begin{aligned} Z_s &= \frac{Z_L}{16} + (4 - j2) \\ &= \frac{10\angle 30^\circ}{16} + (4 - j2) \\ &= 4.54 - j1.69 \end{aligned}$$

05.

Sol:

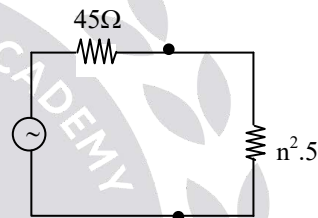

$$Z_{in} = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_L$$


$$R'_{in} = n^2 \cdot 5$$

For maximum power transfer;  $R_L = R_s$

$$n^2 \cdot 5 = 45 \Rightarrow n = 3$$

06. Ans: (b)

Sol:

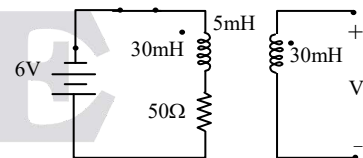

Apply KVL at input loop

$$-6 - 30 \times 10^{-3} \frac{di_1}{dt} + 5 \times 10^{-3} \frac{di_2}{dt} - 50i_1 = 0 \dots (1)$$

Take Laplace transform

$$-\frac{6}{s} + [-30 \times 10^{-3}(s) - 50]I_1(s) + 5 \times 10^{-3} s I_2(s) = 0 \dots (2)$$

Apply KVL at output loop

$$V_2(s) - 30 \times 10^{-3} \frac{di_2}{dt} + 5 \times 10^{-3} \frac{di_1}{dt} = 0$$

Take Laplace transform

$$V_2(s) - 30 \times 10^{-3} s I_2(s) + 5 \times 10^{-3} s I_1(s) = 0$$

Substitute  $I_2(s) = 0$  in above equation

$$V_2 + 5 \times 10^{-3} s I_1(s) = 0 \dots\dots\dots (3)$$

From equation (2)

$$-\frac{6}{s} + (-30 \times 10^{-3}(s) + 50) I_1(s) = 0$$

$$I_1(s) = \frac{-6}{s(30 \times 10^{-3}(s) + 50)} \dots\dots\dots (4)$$

Substitute eqn (4) in eqn (3)

$$V_2(s) = \frac{-5 \times 10^{-3}(s)(-6)}{s(30 \times 10^{-3}(s) + 50)}$$

Apply Initial value theorem

$$\lim_{s \rightarrow \infty} s \frac{-5 \times 10^{-3}(s)(-6)}{s(30 \times 10^{-3}(s) + 50)}$$

$$v_2(t) = \frac{-5 \times 10^{-3} \times (-6)}{30 \times 10^{-3}} = +1$$

**07.**

**Sol:**  $R_{in}' = \frac{8}{2^2} = 2\Omega$

$$R_{in} = 3 + R_{in}' = 3 + 2 = 5\Omega$$

$$I_1 = \frac{10 \angle 20^\circ}{5} = 2 \angle 20^\circ$$

$$\frac{I_1}{I_2} = n = 2 \Rightarrow I_2 = 1 \angle 20^\circ \text{A}$$

**08.**

**Sol:** By the definition of KVL in phasor domain

$$V_s - V_0 - V_2 = 0$$

$$V_0 = V_s - V_2 = V_s \left( 1 - \frac{V_2}{V_s} \right)$$

$$V = ZI$$

By KVL

$$V_s = j\omega L_1 I_1 + j\omega M (0)$$

$$V_2 = j\omega L_2 (0) + j\omega M I_1$$

$$V_0 = V_s \left( 1 - \frac{M}{L_1} \right)$$

Since 1995

# ACE

# Chapter 6 Two Port Networks

01.

**Sol:** The defining equations for open circuit impedance parameters are:

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$[Z] = \begin{bmatrix} \frac{10}{s} & \frac{4s+10}{s} \\ \frac{s}{10} & \frac{s}{3s+10} \end{bmatrix} \Omega$$

02. **Ans: (b)**

**Sol:** The matrix given is  $\begin{bmatrix} 0 & -\frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

since  $y_{11} \neq y_{22}$



$\Rightarrow$  Asymmetrical, and

$y_{12} \neq y_{21}$

$\Rightarrow$  Non reciprocal network

03.

**Sol:** Convert Y to  $\Delta$  :

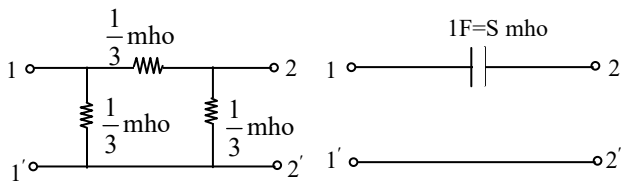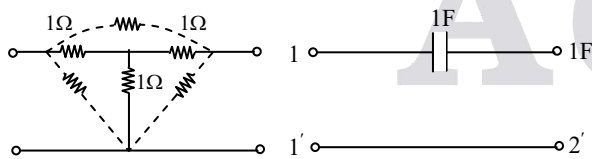

**Fig: A**


**Fig: B**

$$Y_A = \begin{bmatrix} \frac{2}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{bmatrix} \quad Y_B = \begin{bmatrix} S & -S \\ -S & S \end{bmatrix}$$

$$Y = \begin{bmatrix} S + \frac{2}{3} & -S - \frac{1}{3} \\ -S - \frac{1}{3} & S + \frac{2}{3} \end{bmatrix} \text{ mho}$$

04.

**Sol:**

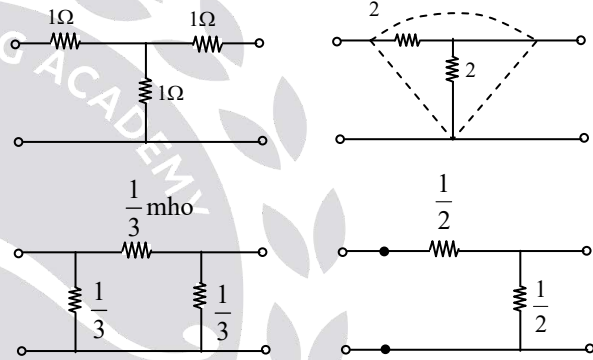


$$Y_A = \begin{bmatrix} \frac{2}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{bmatrix} \quad Y_B = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & 1 \end{bmatrix}$$


$$Y = \begin{bmatrix} \frac{7}{6} & -\frac{5}{6} \\ -\frac{5}{6} & \frac{5}{3} \end{bmatrix}$$

05.

**Sol:** Convert Y to  $\Delta$  :

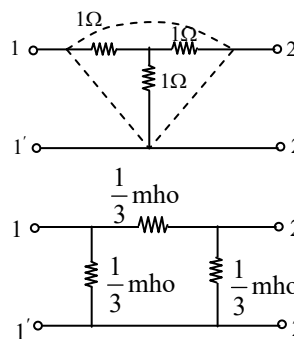

Convert Y to  $\Delta$  :

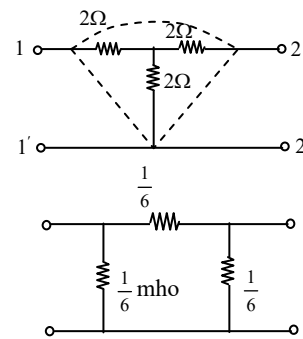

$$Y_A = \begin{bmatrix} \frac{2}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{bmatrix} \text{ mho} \quad Y_B = \begin{bmatrix} \frac{2}{6} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{2}{6} \end{bmatrix} \text{ mho}$$

$$Y = \begin{bmatrix} \frac{6}{6} & -\frac{3}{6} \\ -\frac{3}{6} & \frac{6}{6} \end{bmatrix} = \begin{bmatrix} 1 & -\frac{1}{2} \\ -\frac{1}{2} & 1 \end{bmatrix}$$

06.

**Sol:**  $T_1 = T_2 = \begin{bmatrix} 1 + \frac{1}{-j1} & 1 \\ \frac{1}{-j1} & 1 \end{bmatrix}$

$$= \begin{bmatrix} 1 + j & 1 \\ j & 1 \end{bmatrix}$$

$T_3 \Rightarrow Z_1 = 1\Omega; Z_2 = \infty$

$$T_3 = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix}$$

$T = (T_1)(T_2)(T_3)$

$$T = \begin{bmatrix} j3 & 2 + j4 \\ -1 + j2 & j3 \end{bmatrix}$$

07.

**Sol:**  $T_1 : Z = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}$

$$T_1 = \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$$

$T_2 : Z_1 = 0; Z_2 = 2\Omega$

$$T_2 = \begin{bmatrix} 1 & 0 \\ \frac{1}{2} & 1 \end{bmatrix}$$

$T = [T_1][T_2]$

$$T = \begin{bmatrix} 3.5 & 3 \\ 2 & 2 \end{bmatrix}$$

08. **Ans: (a)**

**Sol:** For  $I_2 = 0$  (O/P open), the Network is shown in Fig.1

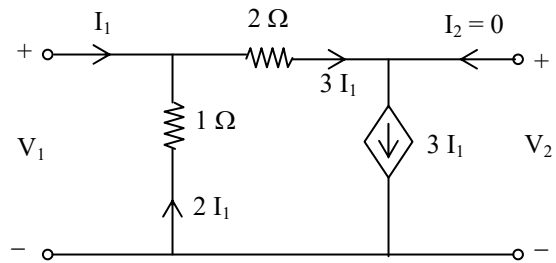


Fig. 1

$$V_1 = -2 I_1 \dots\dots\dots (1)$$

$$Z_{11} = \frac{V_1}{I_1} = -2$$

$$V_2 = -6 I_1 + V_1 \dots\dots\dots (2)$$

From (1) and (2)

$$V_2 = -6 I_1 - 2 I_1$$

$$\text{or } V_2 = -8 I_1$$

$$Z_{21} = \frac{V_2}{I_1} = -8$$

For  $I_1 = 0$  (I/P open), the network is shown in Fig.2

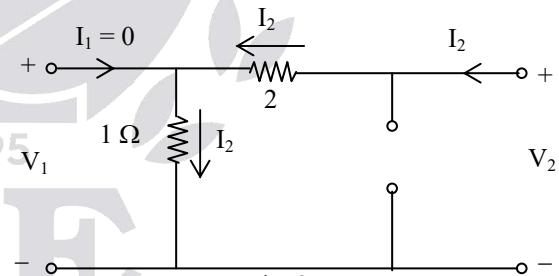


Fig. 2

Note: that the dependent current source with current  $3 I_1$  is open circuited.

$$V_1 = 1 I_2, \quad Z_{12} = \frac{V_1}{I_2} = 1$$

$$V_2 = 3 I_2, \quad Z_{22} = \frac{V_2}{I_2} = 3$$

$$[Z] = \begin{bmatrix} -2 & 1 \\ -8 & 3 \end{bmatrix}$$

09.

**Sol:** By Nodal

$$-I_1 + V_1 - 3V_2 + V_1 + 2V_1 - V_2 = 0$$

$$-I_2 + V_2 + V_2 - 2V_1 = 0$$

$$Y = \begin{bmatrix} 4 & -4 \\ -3 & 2 \end{bmatrix} \bar{V}$$

$$[Z] = Y^{-1}$$

We can also obtain [g], [h], [T] and  $[T]^{-1}$  by re-writing the equations.

10.

**Sol:** The defining equations for open-circuit impedance parameters are:

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

In this case, the individual Z-parameter matrices get added.

$$(Z) = (Z_a) + (Z_b)$$

$$[Z] = \begin{bmatrix} 10 & 2 \\ 2 & 7 \end{bmatrix} \Omega$$

11.

**Sol:** For this case the individual y-parameter matrices get added to give the y-parameter matrix of the overall network.

$$Y = Y_a + Y_b$$


The individual y-parameters also get added

$$Y_{11} = Y_{11a} + Y_{11b} \text{ etc}$$

$$[Y] = \begin{bmatrix} 1.4 & -0.4 \\ -0.4 & 1.4 \end{bmatrix} \text{mho}$$

12. **Ans:** (c)

**Sol:**  $Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$

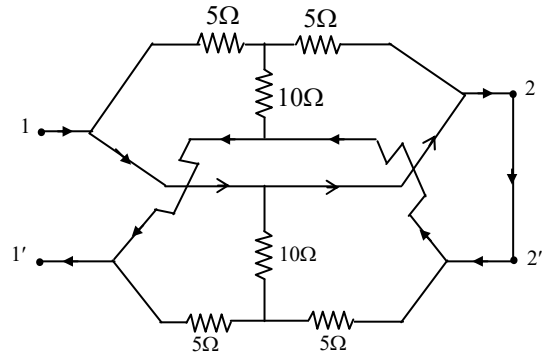

$$Y_{11} = \frac{I_1}{0} = \infty$$

13.

**Sol:** (i).  $[T_a] = \begin{bmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 \\ \frac{1}{Z_2} & 1 \end{bmatrix}$

(ii).  $[T_a] = \begin{bmatrix} 1 & Z_1 \\ \frac{1}{Z_2} & 1 + \frac{Z_1}{Z_2} \end{bmatrix}$

$[T_a]$  and  $[T_b]$  are obtained by defining equations for transmission parameters.

14.

**Sol:** In this case, the individual T-matrices get multiplied

$$(T) = (T_1) \times (T_{N1})$$

$$(T) = (T_1)(T_{N1}) = \begin{pmatrix} 1+s/4 & s/2 \\ 1/2 & 1 \end{pmatrix} \begin{pmatrix} 8 & 4 \\ 2 & 5 \end{pmatrix} = \begin{pmatrix} 3s+8 & 3.5s+4 \\ 6 & 7 \end{pmatrix}$$

15.

**Sol:**  $Z_{in} = R_{in} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2} = \frac{V_2 - 2I_2}{V_2 - 3I_2}$ ,

$$V_2 = 10(-I_2)$$

$$Z_{in} = R_{in} = \frac{12}{13} \Omega$$

16.

Sol:  $\left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_{11}$

$\Rightarrow V_1 = (4 \parallel 4) I_1 |_{I_2=0}$

$\Rightarrow Z_{11} = 2\Omega$

$V_2 = (4 \parallel 4) I_2 |_{I_1=0}$

$\Rightarrow Z_{22} = 2\Omega$

By KVL  $\Rightarrow$

$\frac{3I_1}{2} - V_2 - \frac{I_1}{2} = 0$

$V_2 = I_1$

$\Rightarrow Z_{21} = 1\Omega = Z_{12}$

$Z = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \Omega$

$Y = Z^{-1} = \begin{bmatrix} \frac{2}{3} & \frac{-1}{3} \\ \frac{-1}{3} & \frac{2}{3} \end{bmatrix} \text{S}$

Now [T] parameters;

$V_1 = 2I_1 + I_2 \dots\dots\dots (1)$

$V_2 = I_1 + 2I_2 \dots\dots\dots (2)$

$\Rightarrow I_1 = V_2 - 2I_2 \dots\dots\dots (3)$

Substituting (3) in (1):

$V_1 = 2(V_2 - 2I_2) + I_2 = 2V_2 - 3I_2 \dots\dots\dots (4)$

$T = \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$

$T^{-1} = T^{-1} = \begin{bmatrix} 2 & -3 \\ -1 & 2 \end{bmatrix}$


Now h parameters

$2I_2 = -I_1 + V_2$

$I_2 = \frac{-I_1 + V_2}{2} \dots\dots\dots (5)$

Substitute (5) in (1)

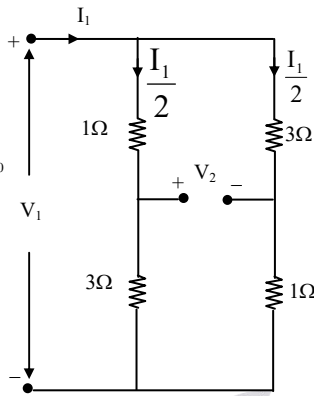$V_1 = 2I_1 \frac{-I_1 + V_2}{2} + \frac{V_2}{2}$



$V_1 = \frac{3}{2} I_1 + \frac{1}{2} V_2 \dots\dots\dots (6)$


$h = \begin{bmatrix} \frac{3}{2} & \frac{1}{2} \\ \frac{-1}{2} & \frac{1}{2} \end{bmatrix}$

$g = [h]^{-1} = \begin{bmatrix} \frac{1}{2} & -1 \\ \frac{1}{2} & \frac{3}{2} \end{bmatrix}$


17. Ans: (a)

Sol:  $Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$

Just use reciprocity of fig (a)

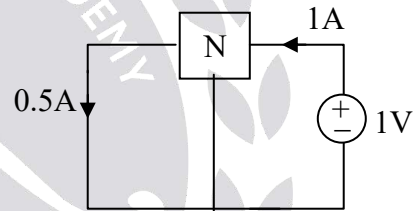

Now use Homogeneity

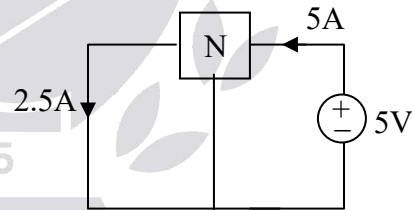

So,  $Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{5}{5} = 1 \text{ mho}$

This has nothing to do with fig (b) since fig (b) also valid for some specific resistance of 2 Ω at port-1, but  $Y_{22}, V_1 = 0$ . So S.C port-1

18.

Sol:  $\frac{V_2}{V_1} = \frac{N_2}{N_1} = n = \frac{-I_1}{I_2}$

$\frac{V_2}{V_1} = n$



$$\Rightarrow V_1 = \frac{1}{n} V_2 - (0)I_2$$

$$\Rightarrow T = \begin{bmatrix} \frac{1}{n} & 0 \\ 0 & n \end{bmatrix}$$

$$T^{-1} = T^{-1} = \begin{bmatrix} n & 0 \\ 0 & \frac{1}{n} \end{bmatrix}$$

$$T^{-1} = T^{-1} = \begin{bmatrix} n & 0 \\ 0 & \frac{1}{n} \end{bmatrix}$$

Now h-parameters

$$V_1 = (0)I_1 + \frac{1}{n} V_2$$

$$I_2 = \frac{-I_1}{n} + (0)V_2$$

$$g = \begin{bmatrix} 0 & \frac{1}{n} \\ \frac{-1}{n} & 0 \end{bmatrix}$$

$$h = \begin{bmatrix} 0 & -n \\ n & 0 \end{bmatrix}$$

**Note:** In an ideal transformer, it is impossible to express  $V_1$  and  $V_2$  in terms of  $I_1$  and  $I_2$ , hence the 'Z' parameters do not exist. Similarly, the y-parameters.

**19. Ans: (c)**

**Sol:**  $Z_{22} = \left. \frac{V_2}{I_2^1} \right|_{V_1=0}$


$$\frac{V_1}{V_2} = \frac{1}{n} = \frac{I_2}{I_1}$$

$$V_1 = \frac{1}{n} V_2$$

$$\frac{V_2 - V_1}{R} = I_1$$

$$I_2^1 = I_2 + I_1$$
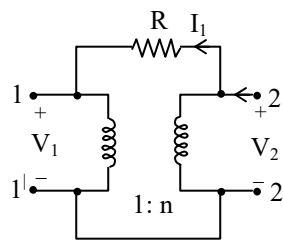
$$\frac{1}{n} = \frac{I_2}{I_1} = \frac{I_2^1 - I_1}{I_1} = \frac{I_2^1}{I_1} - 1$$



$$\frac{I_2^1}{I_1} = \frac{1}{n} + 1 = \frac{1+n}{n}$$

$$I_2^1 = \left( \frac{1+n}{n} \right) I_1$$


$$I_2^1 = \left( \frac{1+n}{n} \right) \left( \frac{V_2 - V_1}{R} \right)$$

$$I_2^1 = \left( \frac{1+n}{n} \right) \left( \frac{V_2 - \frac{1}{n} V_2}{R} \right)$$

$$\frac{I_2^1}{V_2} = \left( \frac{1+n}{n} \right) \left( \frac{n-1}{nR} \right)$$

$$\frac{V_2}{I_2^1} = \frac{n^2 R}{n^2 - 1}$$

**20. Sol:**

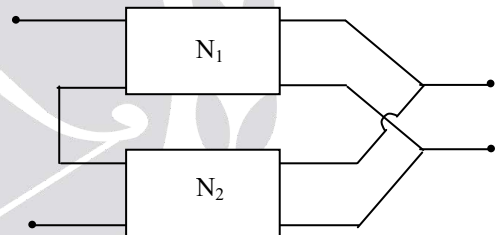

For series parallel connection individual h-parameters can be added.

$\therefore$  For network 1,  $h_1 = g_1^{-1}$

$$= \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}^{-1} = \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix}$$

For network 2,  $h_2 = g_2^{-1}$

$$= \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix}^{-1} = \begin{bmatrix} 1 & -1 \\ 0 & 1 \end{bmatrix}$$

$$\therefore h = \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix}$$


$\therefore$  overall g-parameters,

$$g = h^{-1} = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix}^{-1} = \frac{1}{3} \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}$$

$$g = \begin{bmatrix} 2/3 & 1/3 \\ 1/3 & 2/3 \end{bmatrix}$$

21. Ans: (a, b)

Sol:

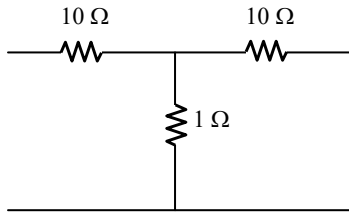

$$[Z] = \begin{bmatrix} 11 & 1 \\ 1 & 11 \end{bmatrix}$$

$$Z_{22} = 11, Z_{12} = 1$$

$$[y] = [Z]^{-1} = \frac{1}{121-1} \begin{bmatrix} 11 & -1 \\ -1 & 11 \end{bmatrix}$$


$$= \begin{bmatrix} \frac{11}{120} & \frac{-1}{120} \\ \frac{-1}{120} & \frac{11}{120} \end{bmatrix}$$

$$Y_{11} = \frac{11}{120} \text{ } \Omega, Y_{12} = \frac{-1}{120} \text{ } \Omega$$

22. Ans: (a, c)

$$\text{Sol: } V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

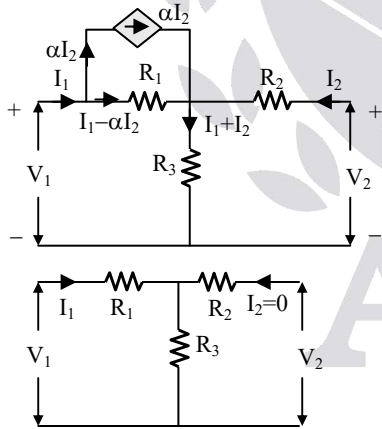


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$V_2 = V_1 \frac{R_3}{R_1 + R_3}$$

$$\Rightarrow A = \frac{V_1}{V_2} = \frac{R_1 + R_3}{R_3}$$

$$\Rightarrow C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{\frac{V_1}{R_1 + R_3}}{V_1 \frac{R_3}{R_1 + R_3}} = \frac{1}{R_3}$$

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

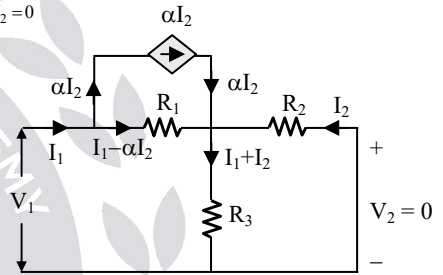

$$V_1 = (I_1 - \alpha I_2)R_1 - I_2 R_2 \quad \dots\dots\dots (1)$$

$$V_1 = (I_1 - \alpha I_2)R_1 + (I_1 + I_2)R_3 \quad \dots\dots (2)$$

$$I_2 R_2 + (I_1 + I_2)R_3 = 0 \quad \dots\dots\dots (3)$$

From eq. (3)

$$I_2 R_2 + I_1 R_3 + I_2 R_3 = 0$$

$$D = \frac{I_1}{-I_2} = \frac{R_2 + R_3}{R_3}$$

$$B = \frac{V_1}{-I_2} = \left[ \frac{(R_2 + R_3)(R_1 + R_3)}{R_3} - R_3 + \alpha R_1 \right]$$

01. Ans: (c)

Sol:  $n > \frac{b}{2} + 1$

Note: Mesh analysis simple when the nodes are more than the meshes.

02. Ans: (c)

Sol: Loops =  $b - (n-1) \Rightarrow$  loops = 5  
 $n = 7 \quad \therefore b = 11$


03. Ans: (a)

04.

Sol: Nodal equations required = f-cut sets  
 $= (n-1) = (10-1) = 9$   
 Mesh equations required = f-loops  
 $= b - n + 1 = 17 - 10 + 1 = 8$   
 So, the number of equations required  
 $= \text{Minimum (Nodal, mesh)} = \text{Min}(9,8) = 8$

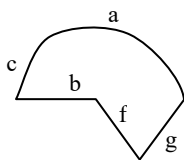05. Ans: (c)

Sol: Not a tree (Because trees are not in closed path)



06. Ans: (a)

07.

Sol: For a complete graph ;

$$b = n_{C_2} \Rightarrow \frac{n(n-1)}{2} = 66$$

$$n = 12$$

$$\text{f-cut sets} = (n-1) = 11$$

$$\text{f-loops} = (b-n+1) = 55$$

$$\begin{aligned} \text{f-loop} = \text{f-cutset matrices} &= n^{(n-2)} \\ &= 12^{12-2} = 12^{10} \end{aligned}$$

08. Ans: (a)

Sol: Let  $N=1$


Nodes=1, Branches = 0 ; f-loops = 0

Let  $N=2$



Nodes = 2; Branches = 1; f-loop = 0


Let  $N=3$

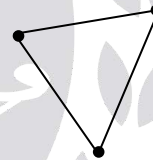

Nodes = 3; Branches = 3; f-loop = 1


$\Rightarrow$  Links = 1

Let  $N=4$

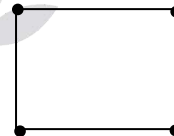


Nodes=4; Branches = 4; f-loops=Links=1

Still  $N = 4$

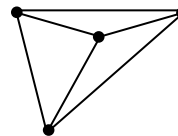

Branches = 6; f-loops = Links = 3

Let  $N = 5$

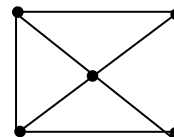


Nodes = 5; Branches = 8; f-loops = Links = 4  
etc

Therefore, the graph of this network can have at least “N” branches with one or more closed paths to exist.

09. Ans: (b)

Sol:

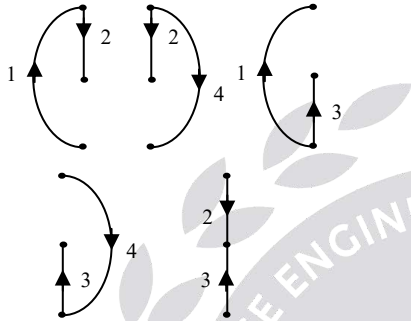

10. Ans: (d)


Sol:

(a) 1,2,3,4 →

(b) 2,3,4,6 →

(c) 1,4,5,6 →

(d) 1,3,4,5 →

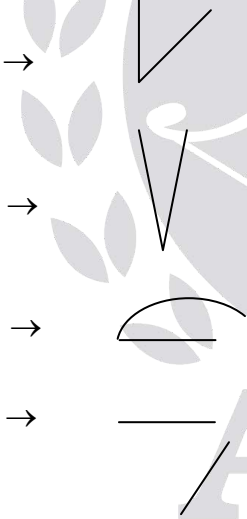


11. Ans: (b)

Sol:  $m = b - n + 1 = 8 - 5 + 1 = 4$

12. Ans: (d)


13. Ans: (d)

Sol: The valid cut-set is (1,3,4,6)

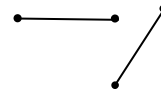


14. Ans: (b)

Sol:

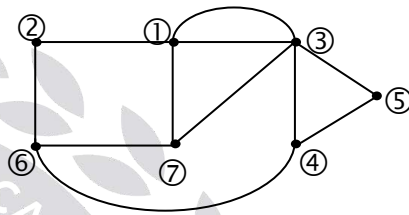

15. Ans: (d)

Sol:

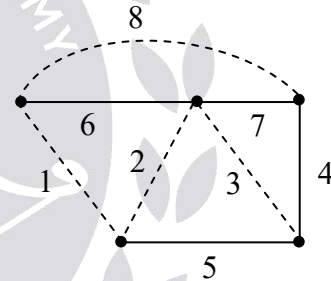

Fundamental loop should consist only one link, therefore option (d) is correct.

01.

Sol:

$$\left. \begin{aligned} \omega=0 &\Rightarrow V_0 = V_i \\ \omega=\infty &\Rightarrow V_0 = 0 \end{aligned} \right\} \Rightarrow \text{Low pass filter}$$

02.

$$\text{Sol: } \omega=0 \Rightarrow V_0 = \frac{V_i R_2}{R_1 + R_2}$$

“V<sub>0</sub>” is attenuated  $\Rightarrow V_0 = 0$

$$\omega=\infty \Rightarrow V_0 = V_i$$

It represents a high pass filter characteristics.

03.

$$\text{Sol: } H(s) = \frac{V_i(s)}{I(s)} = \frac{s^2 LC + sRC + 1}{sC}$$

$$\text{Put } s = j\omega \Rightarrow H(j\omega) = \frac{\omega^2 LC + j\omega RC + 1}{j\omega C}$$

$$\omega=0 \Rightarrow H(s)=0$$

$$\omega=\infty \Rightarrow H(s)=0$$

It represents band pass filter characteristics.

04.

$$\text{Sol: } \omega=0 \Rightarrow V_0 = 0$$

$$\omega=\infty \Rightarrow V_0 = 0$$

It represents Band pass filter characteristics.

05.

$$\text{Sol: } \omega=0 \Rightarrow V_0 = 0$$

$$\omega=\infty \Rightarrow V_0 = V_i$$

It represents High Pass filter characteristics.

06.

$$\text{Sol: } H(s) = \frac{1}{s^2 + s + 1}$$

$$\omega=0 : s=0 \Rightarrow H(s) = 1$$

$$\omega=\infty : s=\infty \Rightarrow H(s) = 0$$

It represents a Low pass filter characteristics.

07.

$$\text{Sol: } H(s) = \frac{s^2}{s^2 + s + 1}$$

$$\omega=0 : s=0 \Rightarrow H(s) = 0$$

$$\omega=\infty : s=\infty \Rightarrow H(s) = 1$$

It represents a High pass filter characteristics.

08.

$$\text{Sol: } \omega=0; V_0 = V_i$$

$$\omega=\infty; V_0 = 0$$

It represents a low pass filter characteristics.

09.

$$\text{Sol: } \omega=0 \Rightarrow V_0 = V_{in}$$

$$\omega=\infty \Rightarrow V_0 = V_{in}$$

It represents a Band stop filter or notch filter.

10.

$$\text{Sol: } H(s) = \frac{s}{s^2 + s + 1}$$

$$\omega=0 : s=0 \Rightarrow H(s) = 0$$

$$\omega=\infty : s=\infty \Rightarrow H(s) = 0$$

It represents a Band pass filter characteristics.

11.

$$\text{Sol: } H(s) = \frac{s^2 + 1}{s^2 + s + 1}$$

$$\omega=0 \Rightarrow s=0 \Rightarrow H(s) = 1$$

$$\omega=\infty \Rightarrow s=\infty \Rightarrow H(s) = 1$$

It represents a Band stop filter

12.

**Sol:**  $H(s) = \frac{1-s}{1+s}$


$\omega = 0 \Rightarrow S = 0 \Rightarrow H(s) = 1$

$\omega = \infty \Rightarrow S = \infty \Rightarrow H(s) = -1 = 1 \angle 180^\circ$

It represents an All pass filter

13. **Ans: (c)**

**Sol.**

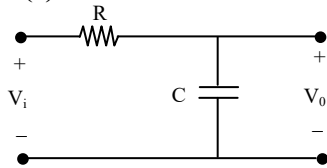


$\omega = 0 \Rightarrow V_0 = V_i$

$\omega = \infty \Rightarrow V_0 = 0$

$$V_0(s) = \left( \frac{V_i(s)}{R + \frac{1}{sC}} \right) \left( \frac{1}{sC} \right)$$

$$\frac{V_0(s)}{V_i(s)} = H(s) = \frac{1}{sCcR + 1}$$
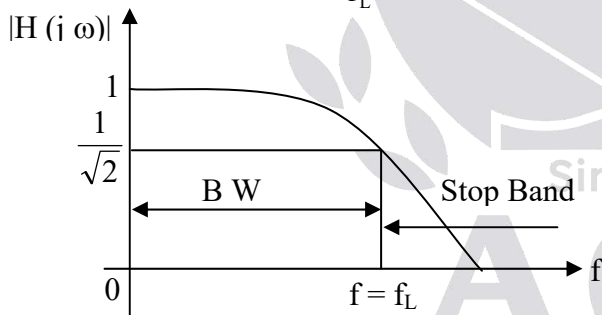
$$H(j\omega) = \frac{1}{1 + j\omega c R} = \frac{1}{1 + j \frac{f}{f_L}}$$



Where  $f_L = \frac{1}{2\pi RC}$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}}$$


$$\angle H(j\omega) = -\tan^{-1}\left(\frac{f}{f_L}\right)$$

$f = 0 \Rightarrow \phi = 0^\circ = \phi_{\min}$

$f = f_L \Rightarrow \phi = -45^\circ = \phi_{\max}$

14. **Ans: (b)**

**Sol:**

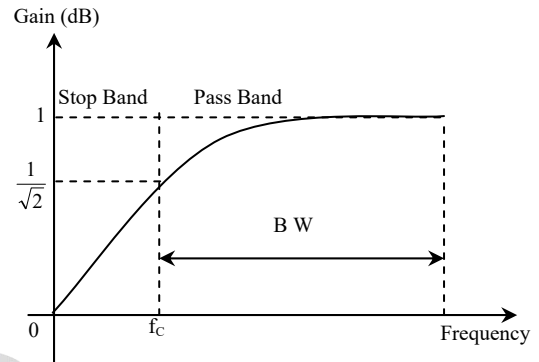

First order high pass filter =  $\frac{s}{1+sT}$

Phase shift =  $90 - \tan^{-1}\omega T$

Max. phase shift is at corner frequency

$$\omega = \frac{1}{T}$$

Max. phase shift =  $90 - \tan^{-1}\omega T$

$$= 90 - \tan^{-1}\left(\frac{1}{T} \times T\right)$$

$$= 90 - 45$$

$$= 45^\circ$$

15. **Ans: (d)**

16. **Ans: (a)**

**Sol:** Half power of series RC circuit is at  $t = T$   
(Time constant)

$T = RC$

Frequency =  $\frac{1}{RC}$

17. **Ans: (c)**

**Sol:** Magnitude of voltage gain 0.707 is at half power frequency

$$\omega = \frac{1}{RC}$$

# Chapter 9 Single Phase Transformer

01. Ans: (b)

Sol:  $\uparrow B_{\max} \propto \frac{V}{f \downarrow}$

Here  $V \rightarrow$  constant,  $f \rightarrow$  decreased to half  
 $\Rightarrow B_{\max}$  increased to double, which will drive the core in to deep saturation and also  $I_{\mu}$  is very high to create double the rated flux.

02. Ans: (d)

Sol: As  $\frac{V}{f}$  ratio is not equal

- (i)  $W_h \propto \frac{V_1^{1.6}}{f^{0.6}}$ ; as frequency increases, the hysteresis loss will decrease.  
 (ii)  $W_e \propto V_1^2$  (Independent on frequency)  
 $\therefore$  Eddy current loss will be constant.

03. Ans: (a)

Sol: Lenz's Law:

The direction of statically induced emf is such that the current due to this emf will flow through a closed circuit in such a direction that it will in turn produce some flux according to **Electro Magnetic Theory** and this flux must opposes the changes in main field flux which is the cause for production of emf as well as current.

04. Ans: (a)

Sol: Specific weight =  $\frac{\text{weight of transformer}}{\text{kVA rating}}$

If flux density is high, then required cross sectional area of core will be less.

$$\left( \because B \propto \frac{1}{A} \right)$$

Therefore transformer weight will be decreased, the transformer should have less specific weight.

05. Ans: (d)

Sol: In ideal transformer, resistance of windings and magnetic leakage flux are zero.

06. Ans: (d)

Sol: As leakage flux is more, coefficient of coupling of transformer will decrease and also the inductive reactance drop will be increased.

07. Ans: (a)

Sol:  $V =$  constant and  $f > f_{\text{rated}}$

$$\Rightarrow \frac{V}{f} \text{ Ratio is not constant}$$

$$\therefore W_h \propto \frac{V_1^{1.6}}{f^{0.6} \uparrow} \Rightarrow W_h \downarrow \text{ \& } W_e = \text{Const}$$

But " $W_h$ " is due to core loss component of current  $I_w$

$$\Rightarrow \text{As } f \uparrow, W_h \downarrow \Rightarrow I_w \downarrow.$$

$$\text{Similarly } \downarrow I_{\mu} \propto \downarrow B_{\max} \propto \frac{V}{f \uparrow}$$

$$\Rightarrow f \uparrow \Rightarrow B_{\max} \downarrow \Rightarrow I_{\mu} \downarrow$$

**08. Ans: (c)**

**Sol:** Copper loss  $\propto I^2$  i.e depends on load current called variable losses.

Iron loss ( $W_h + W_e$ )  $\propto V^2$  (applied voltage), called constant losses.

**09. Ans: (a)**

**Sol:**  $W_i = 100$  W at 40 Hz.

$$= 72 \text{ W at } 30 \text{ Hz.}$$

At 40 Hz,  $W_i = Af + Bf^2$ .

$$100 = A \times 40 + B \times 40^2 \dots\dots (1)$$

At 30 Hz,  $72 = A \times 30 + B \times 30^2 \dots\dots (2)$

By solving above two equations,

$$B = 1/100 \text{ and } A = 2.1$$

Hysteresis loss,  $W_h = A \times f$

$$= 2.1 \times 50 \Rightarrow 105 \text{ W.}$$

Eddy current loss  $W_e = B \times f^2$

$$= \frac{50 \times 50}{100}$$

$$= 25 \text{ W.}$$

**10. Ans: (c)**

**Sol:** • For a given kVA rating of transformer, more the design frequency, lesser the cross sectional area of the core and lesser will be the size and weight of transformer.

For a given kVA rating and designed frequency of transformer, superior the magnetic material used for transformer core, higher will be the flux density and lesser will be the size and weight of the transformer.

Copper loss is directly proportional to square of the current and resistance.

**11. Ans: (a)**

**Sol: Distribution transformer:** Cu-losses take place based on load cycle of Consumer and Iron losses takes place throughout 24 hrs. Iron losses are kept minimum while designing

**Power transformer:** Cu-losses and Iron losses takes place steadily throughout 24 hrs. Copper losses are kept minimum while designing.

Both assertion and reason are correct, reason is correct explanation to assertion.

**12. Ans: (a)**

**Sol:** At 230 V, 50 Hz  $\Rightarrow W_I = 1050$  W

At 138 V, 30 Hz  $\Rightarrow W_I = 500$  W

$$V_{11} = 230 \text{ V}$$

$$\frac{V_{11}}{f_1} = \frac{230}{50} = 4.6$$

$$f_1 = 50 \text{ Hz}$$

$$\frac{V_{12}}{f_2} = \frac{138}{30} = 4.6$$

$$V_{12} = 138 \text{ v}$$

$$f_2 = 30 \text{ Hz}$$

$$\frac{V_1}{f} = \text{constant}$$

$$\text{at } \frac{V_1}{f} = \text{constant}$$

$$W_I = Af + Bf^2$$

$$\text{at } 50 \text{ Hz } \Rightarrow 1050 = A(50) + B(50)^2 \text{ -----(i)}$$

$$\text{at } 30 \text{ Hz } \Rightarrow 500 = A(30) + B(30)^2 \text{ -----(ii)}$$

by solving equation (1) & (2), we get

$$A = 10.1667$$

$$B = 0.2167$$

Then at 230V, 50 Hz

$$W_h = Af = 10.1667 \times 50 = 508.33 \text{ W}$$

$$W_e = Bf^2 = 0.2167 \times (50)^2 = 541.75 \text{ W}$$



13. Ans: (b)

**Sol:** Open circuit test is convenient to conduct on LV side by opening H.V winding due to the following reasons:

1. If the test is conducted on LV side, LV source sufficient to conduct the test to maintain rated flux.
2. If the test is conducted on LV side, low range meters are sufficient to conduct the test.
3. As magnitude of no-load current is more on LV side, this high no-load current can be accurately measured on LV side when compared to HV side.

**Short circuit Test:** As rated current is less on HV side, it is convenient to conduct this test on HV side by short circuiting LV terminals. By doing so low range of meters can be used for conducting this test.

14. Ans: (b)

**Sol:**  $P = V I_w$

$$\therefore \text{Loss component } I_w = \frac{5 \times 10^3}{220} = 22.7 \text{ A}$$

15. Ans: (a)

16. Ans: (a)


**Sol:** It is equivalent circuit of the Transformer under S.C condition when referred to primary side.

17. Ans: (b)

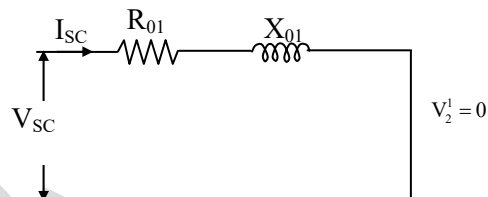18. Ans: (d)

**Sol:** S.C test is conducted at reduced voltage ( $V_{SC}$ ) and at rated frequency.

If  $V_{SC}$  constant and 'f' ( $f > f_{rated}$ ) is increased, the consequences are



Equivalent circuit under S.C test

(i)  $R_{01} = \text{constant}$

(ii)  $\uparrow X_{01} \propto f \uparrow$

(iii)  $z_{01} = \sqrt{x_{01}^2 + R_{01}^2} \Rightarrow z_{01} \uparrow$

(iv)  $\downarrow I_{SC} = \frac{V_{SC} = \text{constant}}{z_{01} \uparrow}$

(v)  $\downarrow \cos \phi_{SC} = \frac{R_{01} = \text{constant}}{z_{01} \uparrow}$

19. Ans: (c)

**Sol:** The Condition for maximum efficiency  
 $= 2W_i$

$\therefore$  At maximum efficiency

$$W_{\text{total}} = (150 + 150) \text{ W} = 300 \text{ W}$$

20. Ans: (b)

**Sol:** kVA at  $\eta_{\text{max}} = F.L \text{ kVA} \times \sqrt{\frac{\text{Iron loss}}{F.L \text{ cu loss}}}$

$$= F.L \text{ kVA} \times \sqrt{\frac{P_c}{P_{sc}}}$$

21. Ans: (d)

**Sol:** As lamination size is thin, resistance offered by the each laminated part of core is

increased, hence the magnitude of eddy current will decrease and therefore corresponding loss will be decreased.

**22. Ans: (c)**

**Sol:** Core losses = 150 W (Constant)

Copper loss at full load = 220 W

∴ Copper loss at half full load

$$= \left(\frac{1}{2}\right)^2 220W = 55 W$$

∴ Total losses at half full load

$$= 150 + 55 \\ = 205 W$$

Efficiency at half full load

$$= \frac{\frac{1}{2} \times 10^3 \times 1}{\frac{1}{2} \times 10 \times 10^3 + 205} \times 100 \\ = 96.06\%$$

**23. Ans: (c)**

$$\text{Sol: } \% \eta = \frac{(x)(VI) \cos \phi}{x(VI) \cos \phi + W_c + W_{cu}} \times 100 \\ x = 1 (\because \text{full load})$$

VI = 200 kVA;  $\cos \phi = 0.9$  lag;  $W_c = 1.8$  kW

$$W_{cu} = \left(\frac{1.1}{100}\right) \times 200 \times 10^3 = 2200 \text{ watts}$$

$$\% \eta = \frac{(1)(200 \times 10^3)(0.9)}{(200 \times 10^3 \times 0.9) + (1.8 \times 10^3) + 2200} \times 100 \\ = 97.82\%$$

**24. Ans: (a)**

**Sol:** % Reg = (%R)  $\cos \phi_2 \pm$  (%X)  $\sin \phi_2$

For lagging power for

$$\% V.R = (2)(0.8) + (4)(0.6) = 4\%$$

For leading power factor

$$\% V.R = (2)(0.8) - (4)(0.6) = -0.8\%$$

**25. Ans: (a)**

**Sol:** Given %R = 1%, %X = 5% and  $\cos \phi = 0.8$

$$\% \text{ Reg} = (\%R) \cos \phi + (\%X) \sin \phi \quad (\because \text{lag pf}) \\ = (1)(0.8) + (5)(0.6) \\ = 3.8\%$$

**26. Ans: (a)**

**Sol:** If resistance drop is completely compensated by reactance drop, zero voltage regulation takes place. It is possible at leading power factor loads.

If reactance drop is more as compared to resistance drop at leading power factor loads, negative voltage regulation will occur.

**27. Ans: (c)**


**Sol:** 3, 4, 5 condition's are necessary conditions 1 & 2 are desirable conditions for parallel operations.

**28. Ans: (d)**

**Sol:** If impedance decreases, current will increase and therefore sharing of load will increase.

**29. Ans: (d)**

**Sol:**

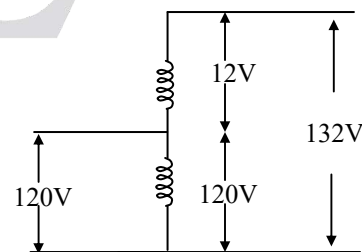

For series additive polarity of winding, voltage = 132 V.

For series subtractive polarity of winding, voltage = 108 V.

**30. Ans: (c)****Sol:** 240/120 V, 12 kVA

$$\eta = 96.2\%$$

$$\eta = \frac{12000 \times 1}{12000 \times 1 + \text{losses}} = 0.962$$


$$\Rightarrow 12000 + \text{losses} = 12474$$

$$\text{Losses} = 474 \text{ W}$$

When connected across 360V,

$$\text{The rating becomes} = \frac{12}{1-k} = \frac{12}{1-\frac{2}{3}} = 36 \text{ kVA}$$

$$\begin{aligned} \therefore \text{Efficiency} &= \frac{36000 \times 0.85}{36000 \times 0.85 + \text{losses}} \\ &= \frac{30,600}{30,600 + 474} = 98.5\% \end{aligned}$$

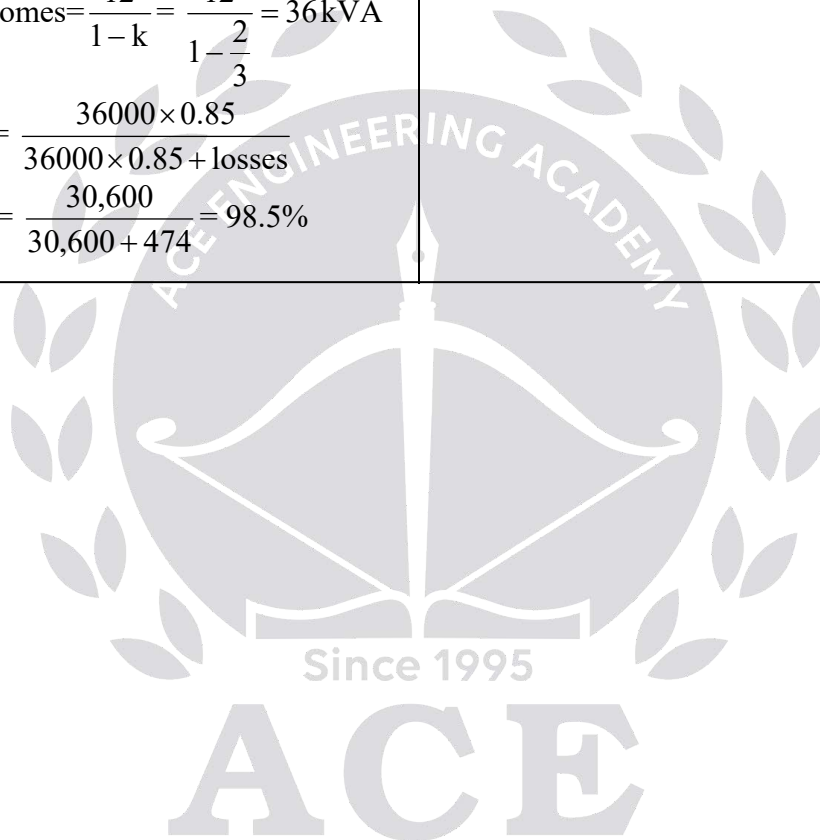**31. Ans: (c)****Sol:** In auto transformer, power is not only transferred by induction process but also by conduction process.

# Chapter 10 Three Phase Induction Motors

**01. Ans: (d)**

**Sol:** For motoring, the stator poles and rotor poles must be equal. In the above case, the stator windings are wound for 4 poles, whereas the rotor windings are wound for 6 poles. As the stator poles and rotor poles are unequal the torque developed is zero and speed is zero.

**02. Ans: (c)**

**Sol:** An induction motor stator is replaced by a 6-pole stator, then the rotor poles will also be 6 poles, because in squirrel cage rotor, the rotor poles are induced pole. Then, the synchronous speed with 6 poles for 50 Hz supply is 1000 rpm. Therefore, the rotor speed will be less than 1000 rpm.

**03. Ans: (c)**

**Sol:** With the increase in the air gap, the reluctance of the magnetic circuit will be increased; because of this the motor draws more magnetizing current. Hence the power factor decreases.

**04. Ans: (b)**

**Sol:** 1. It helps in reduction of magnetic hum, thus keeping the motor quiet,  
2. It also helps to avoid "Cogging", i.e. locking tendency of the rotor. The tendency of rotor teeth remaining under

the stator teeth due to the direct magnetic attraction between the two,

3. Increase in effective ratio of transformation between stator & rotor,
4. Increased rotor resistance due to comparatively lengthier rotor conductor bars, to improve the starting torque & starting power factor
5. Increased slip for a given torque.

**05. Ans: (a, d)**

**Sol:** Synchronous speed of stator field,

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

Synchronous speed of Rotor field,

$$(N_r)_s = \frac{120 \times 30}{4} = 900 \text{ rpm}$$

But rotor speed,  $N_r = N_s \pm (N_r)_s$

$$= 1500 \pm 900$$

$$= 2400 \text{ rpm and } 600 \text{ rpm}$$

**06. Ans: (b)**

**Sol:** The frequency of generated emf by the alternator is given as

$$f = \frac{PN_{pm}}{120} = \frac{4 \times 1500}{120} = 50 \text{ Hz}$$

The synchronous speed of Induction motor

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\begin{aligned} \% \text{ Slip} &= \frac{N_s - N_r}{N_s} \times 100 \\ &= \frac{1000 - 960}{1000} \times 100 = 4\% \end{aligned}$$

**07. Ans: (a)**

**Sol:** Given data:  $P = 4$ ,  $N_r = 1440$  rpm and  $f = 50$  Hz

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$\text{Slip} = \frac{N_s - N_r}{N_s} = \frac{1500 - 1440}{1500} = \frac{6}{150}$$

The frequency in the rotor of induction motor is slip frequency (sf).

$$\therefore \text{Frequency of emf is, } \frac{6}{150} \times 50 = 2 \text{ Hz.}$$

**08. Ans: (c)**

**Sol:** If the rotor is assumed to run at synchronous speed  $N_s$  in the direction of rotating magnetic fields, then there would be no flux cutting action, no emf in the rotor conductors, no currents in the rotor bars and therefore no developed torque. Thus, the rotor of 3-phase induction motor can never attain synchronous speed.

**09. Ans: (d)**

**Sol:** For 50 Hz, supply the possible synchronous speeds with different poles.

2 poles  $\rightarrow$  3000 rpm

4 poles  $\rightarrow$  1500 rpm

6 poles  $\rightarrow$  1000 rpm

8 poles  $\rightarrow$  750 rpm

10 poles  $\rightarrow$  600 rpm

12 poles  $\rightarrow$  500 rpm

20 poles  $\rightarrow$  300 rpm

We know that, the rotor of an induction motor always tries to rotate with speed closer to synchronous speed, therefore the synchronous speed closer to 285 rpm for 50 Hz supply is 300 rpm and poles are 20 poles.

So its 20 poles induction motor.


**10. Ans: (c)**

**Sol:** If any two leads from slip rings are interchanged in a 3-phase induction motor, the motor will run in a direction opposite to previous one

The direction of rotation in a 3-phase motor depends upon the sequence in which the magnetic poles are created by the respective phase lines. This in turn creates a rotating magnetic field. By interchanging any two phases (lines) the sequence of pole formation is being changed i.e., the direction of the rotating magnetic field is reversed. Hence the direction of rotation of the motor also changes accordingly.

**11. Ans: (a)**

**Sol:**

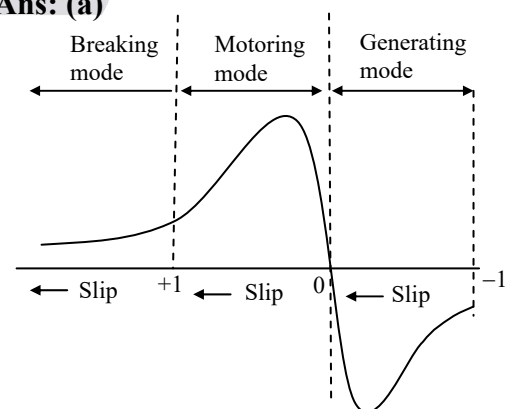

Torque-slip characteristics of a 3-phase Induction machine

**12. Ans: (c, d)**

$$\begin{aligned} \text{Sol: Rotor speed} &= \frac{120 \times f}{P} \\ &= \frac{120 \times 50}{4} \\ &= 1500 \text{ rpm} \end{aligned}$$

Possible relative speeds between stator and rotor are  $N_s + N_r$  and  $N_s - N_r$ .

Synchronous speed

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$s = \frac{N_s + N_r}{N_s} = \frac{1000 + 1500}{1000} = 2.5$$

$$\begin{aligned} \text{Slip frequency, } sf &= 2.5 \times 50 \\ &= 125 \text{ Hz} \end{aligned}$$

$$s = \frac{N_s - N_r}{N_s} = \frac{1000 - 1500}{1000} = -0.5$$

$$\text{Slip frequency} = 25 \text{ Hz}$$

**13. Ans: (b)**

$$\text{Sol: } \frac{T_{st}}{T_{FL}} = \frac{2s_m}{1 + s_m^2}$$

$$\text{Where } s_m = \frac{N_s - N_r}{N_s}$$

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$N_r = 1200 \text{ rpm}$$

$$\therefore s_m = \frac{1500 - 1200}{1500} = 0.2 = 20\%$$

$$\text{Now, } \frac{T_{st}}{T_{FL}} = \frac{2(0.2)}{1 + (0.2)^2} = 0.384$$

**14. Ans: (c)**

$$\text{Sol: Efficiency } (\eta) = \frac{\text{output shaft power}}{\text{input power}}$$

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$N_r = 975 \text{ rpm (Given)}$$

$$\therefore s = \frac{N_s - N_r}{N_s} = \frac{1000 - 975}{1000} = 0.025$$

$$\begin{aligned} \text{Air gap power} &= \text{Stator input} - \text{Stator losses} \\ &= 40 - 1 = 39 \text{ kW} \end{aligned}$$

Gross mechanical power output

$$\begin{aligned} &= (1 - s) \times \text{Air gap power} \\ &= (1 - 0.025) \times 39 = 38.025 \text{ kW} \end{aligned}$$

Shaft power output

$$\begin{aligned} &= \text{Gross mechanical power output} \\ &\quad - \text{Mechanical losses} \end{aligned}$$

$$= 38.025 - 2 = 36.025 \text{ kW}$$

$$\begin{aligned} \therefore \% \eta &= \frac{36.025}{40} \times 100 \\ &= 90.0625\% \end{aligned}$$

**15. Ans: (c)**

$$\text{Sol: Slip } s = 5\% = 0.05$$

Rotor output/gross mechanical power developed  $P_{ro} = 20 \text{ kW}$ .

$$\begin{aligned} \text{Rotor copper loss} &= \frac{s}{1-s} \times P_{ro} \\ &= \frac{0.05}{1-0.05} \times 20 \text{ k} \\ &= 1052 \text{ W} \end{aligned}$$

**16. Ans: (c)**

**Sol:** Increase in air gap, increase reluctance and hence draws more magnetizing current and power factor decreases.

**17. Ans: (b)**
**Sol:**  $\tau_{em} = 500 \text{ Nm}$ ,  $V_2 = 0.5 V_1$ 

$$\tau_{em} \propto V^2$$

$$\Rightarrow \frac{\tau_{em1}}{\tau_{em2}} = \left( \frac{V_1}{V_2} \right)^2$$

$$\Rightarrow \tau_{em2} = (0.5)^2 \times 500 = 125 \text{ Nm}$$

**18. Ans: (a)**
**Sol:** Given rotor resistance per phase

$$R_2 = 0.21 \Omega$$

Stand still rotor reactance per phase

$$X_{20} = 7 \Omega$$

We have slip at maximum torque given by

$$s_{T_{max}} = \frac{R_2}{X_{20}} = \frac{0.21}{7} = 0.03$$

The synchronous speed of the motor is

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$


Rotor speed at maximum torque is given by

$$\begin{aligned} N_{rT_{max}} &= N_s(1 - s) \\ &= 1500(1 - 0.03) = 1455 \text{ rpm} \end{aligned}$$

**19. Ans: (d)**

**Sol:** Power factor of an induction motor on no-load is very low because of the high value of magnetizing current. With load the power factor increases because the power component of the current is increased and a stage comes after which as load further increase the over all power factor starts slowly decreasing. Low power factor operation is one of the

disadvantages of an induction motor. An induction motor draws a heavy amount of magnetizing current due to presence of air gap between the stator and rotor (unlike a transformer). The reduced the magnetizing current in an induction motor, the air gap is kept as small as possible. It is therefore usual to find the air gap of induction motor smaller than any other type of electrical machine.

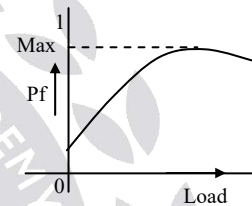
**20. Ans: (b)**

**Sol:** The rotor bars of squirrel cage induction motor are short circuited at both ends by end-rings of the same material, hence we unable to connect external resistance into rotor, so Rotor resistance control not applicable to cage induction motor.

**21. Ans: (a)**

**Sol:** Rotor current's in an induction motor is due to relative speed between stator RMF and physical rotor.

If  $N_r = N_s$  i.e. if rotor rotating with ' $N_s$ ' speed in the same direction of stator RMF ( $N_s$  speed), then the relative speed between them is zero.

$\Rightarrow$  EMF induced in the rotor winding is zero.

$\Rightarrow$  current's in rotor winding is zero.

Hence torque production is zero

⇒ at  $N = N_s$  ; rotor won't rotate, hence called "Asynchronous machine".

**22. Ans: (d)**

**Sol:** The main function of a starter in a 3- $\phi$  induction motor is to limit high starting current to reasonable values.

**23. Ans: (a)**

**24. Ans: (a)**

**25. Ans: (c)**

**Sol:** This method is used in the case of motors, which are built to run normally with a delta connected stator winding. It consists of a two-way switch, which connects the motor in star for starting and then in delta for normal running. When star connected, the applied voltage over each phase is reduced by factor  $\frac{1}{\sqrt{3}}$  and hence the torque developed becomes 1/3 of that which would have been developed if motor were directly connected in delta. The line current is reduced to 1/3. Hence during starting period when motor is star connected, it takes 1/3rd as much starting current and develops 1/3 rd as much torque as would have been developed it directly connected in delta.

**26. Ans: (c)**

**Sol:**  $I_{ac} = 400A; k = 0.7$

$$I_{st, supply} = k^2 I_{sc} = 0.7^2 \times 400 = 196A$$

**27. Ans: (a)**

**Sol:**  $\frac{\text{Starting line current with stator winding in star}}{\text{Starting line current with stator winding in delta}} = \frac{1}{3}$

Starting line current with stator winding in delta (DOL) =  $3 \times$  Starting line current with stator winding in star

$$= 3 \times 50 \\ = 150A$$

**28. Ans: (a)**

**Sol:**  $T_{st} = \frac{1}{4} T_{fl}$

$$I_{sc} = 4I_{fl}$$

we have for auto transformer starting

$$\frac{T_{st}}{T_{fl}} = k^2 \left( \frac{I_{sc}}{I_{fl}} \right)^2 s_{fl}$$

$$\frac{1}{4} = k^2 \times 4^2 \times 0.03$$

$$K = 72.2\%$$

**29. Ans: (c)**

**Sol:** Magnitude of starting torque depends upon value of capacitor used at the time of starting. Practically permanent split capacitor start consist high value of capacitor and shaded pole type produces low starting torque.

**30. Ans: (d)**



**31. Ans: (d)**

**Sol:** Harmonic field effects on the performance of induction motor are of the following kinds:

1. Asynchronous crawling
2. Locking and synchronous crawling
3. Magnetic noise and vibration

These harmonics fields are due to

- (i) Winding
- (ii) Slotting
- (iii) Saturation and
- (iv) Irregularities in the air gap field

**32. Ans: (b)**

**Sol:** Magnetic locking tendency of rotor is nothing but cogging.

