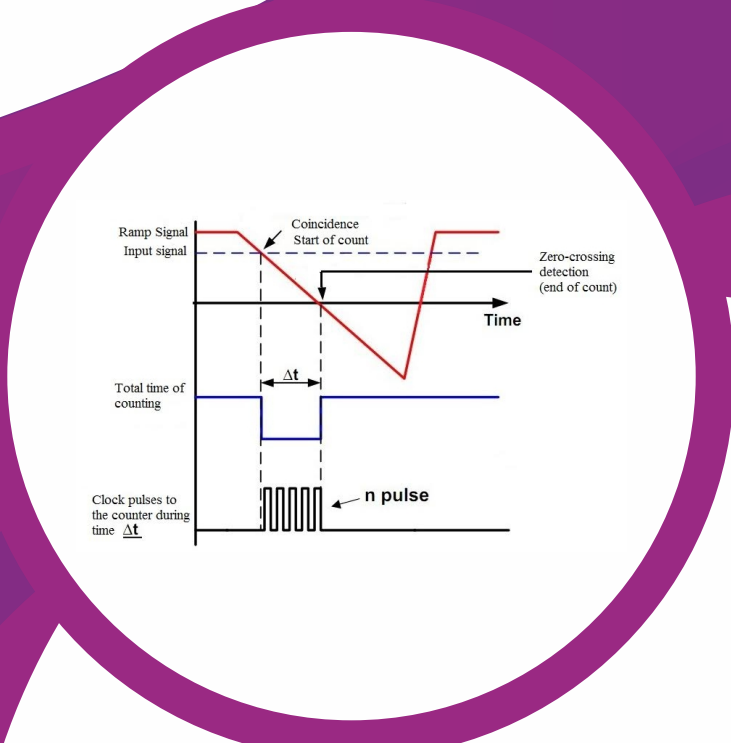


# INSTRUMENTATION ENGINEERING

## Measurements

(Text Book: Theory with worked out Examples and Practice Questions)



# Chapter 1 Error Analysis

(Solutions for Text Book Practice Questions)

01. Ans: (b)

$$\begin{aligned} \text{Sol: } \% \text{ LE} &= \frac{\text{FSV}}{\text{true value}} \times \% \text{GAE} \\ &= \frac{200 \text{ V}}{100 \text{ V}} \times \pm 2\% \\ &= \pm 4\% \end{aligned}$$

02. Ans: (d)

Sol: Variables are measured with accuracy  
 $x = \pm 0.5\%$  of reading 80 (limiting error)  
 $Y = \pm 1\%$  of full scale value 100  
 (Guaranteed error)  
 $Z = \pm 1.5\%$  reading 50 (limiting error)  
 The limiting error for Y is obtained as  
 Guaranteed  
 Error =  $100 \times (\pm 1/100)$   
 $= \pm 1$   
 Then % L.E in Y meter  
 $20 \times \frac{x}{100} = \pm 1$   
 $x = 5\%$   
 Given  $w = xy/z$ , Add all %L.E s  
 Therefore  $= \pm (0.5\% + 5\% + 1.5\%)$   
 $= \pm 7\%$


03. Ans: (d)

Sol:  $W_T = W_1 + W_2$   
 $= 100 - 50$   
 $= 50 \text{ W}$   
 $\frac{\partial W_T}{\partial W_1} = \frac{\partial W_T}{\partial W_2} = 1$   
 Error in meter 1  $= \pm \frac{1}{100} \times 100$   
 $= \pm 1 \text{ W}$   
 Error in meter 2  $= \pm \frac{0.5}{100} \times 100$   
 $= \pm 0.5 \text{ W}$   
 $W_T = W_1 + W_2$   
 $= 50 \pm 1.5 \text{ W}$   
 $W_T = 50 \pm 3\%$

04. Ans: (a)

Sol: For 10V total input resistance  
 $R_v = \frac{V_{\text{fsd}}}{I_{\text{m fsd}}} = 10/100\mu\text{A} = 10^5\Omega$   
 Sensitivity  $= R_v/V_{\text{fsd}} = 10^5/10$   
 $= 10\text{k}\Omega/\text{V}$   
 For 100V  $R_v = 100/100\mu\text{A}$   
 $= 10^6\Omega$   
 Sensitivity  $= R_v/V_{\text{fsd}} = 10^6/100$   
 $= 10 \text{ k}\Omega/\text{V}$   
 (or)  
 Sensitivity  $= \frac{1}{I_{\text{fsd}}} = \frac{1}{100 \times 10^{-6}}$   
 $= 10 \text{ k}\Omega/\text{V}$

05.

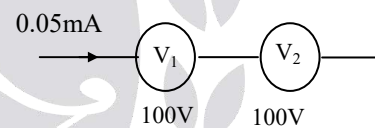Sol:   
 $V_1:$   $S_{\text{dc}_1} = 10 \text{ k}\Omega/\text{V}$   
 $I_{\text{fsd}} = \frac{1}{S_{\text{dc}_1}} = 0.1 \text{ mA}$   
 $V_2:$   $S_{\text{dc}_2} = 20 \text{ k}\Omega/\text{V}$   
 $I_{\text{fsd}} = \frac{1}{S_{\text{dc}_2}} = 0.05 \text{ mA}$

The maximum allowable current in this combination is 0.05mA, since both are connected in series.  
 Maximum D.C voltage can be measured as  
 $= 0.05 \text{ mA} (10 \text{ k}\Omega/\text{V} \times 100 + 20 \text{ k}\Omega/\text{V} \times 100)$   
 $= 3000 \times 0.05 = 150 \text{ V}$

06.

Sol: Internal impedance of 1<sup>st</sup> voltmeter  
 $= \frac{100\text{V}}{5 \text{ mA}} = 20 \text{ k}\Omega$   
 Internal impedance of 2<sup>nd</sup> voltmeter  
 $= 100 \times 250 \Omega/\text{V}$   
 $= 25 \text{ k}\Omega$

Internal impedance of 3<sup>rd</sup> voltmeters,  
= 5 kΩ

Total impedance across 120 V  
= 20 + 25 + 5  
= 50 kΩ

Sensitivity =  $\frac{50\text{k}\Omega}{120\text{V}}$   
= 416.6 Ω/V


⇒ Reading of 1<sup>st</sup> voltmeter  
=  $\frac{20\text{k}\Omega}{416.6\Omega/\text{V}}$

= 48 V  
Reading of 2<sup>nd</sup> voltmeter  
=  $\frac{25\text{k}\Omega}{416.6\Omega/\text{V}}$

= 60 V  
Reading of 3<sup>rd</sup> voltmeter  
=  $\frac{5\text{k}\Omega}{416.6\Omega/\text{V}}$   
= 12 V

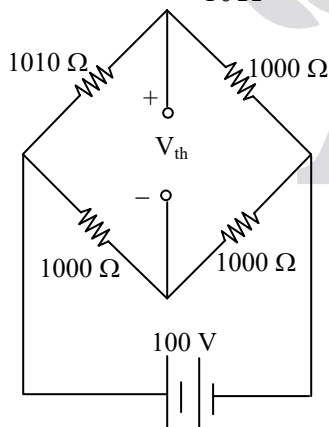**07. Ans: (b)**

**Sol:** Bridge sensitivity =  $\frac{\text{Change in output}}{\text{Change in input}}$   
=  $\frac{V_{th}}{10\Omega}$



$$V_{th} = \frac{1010 \times 100}{2000} - \frac{1000 \times 100}{2000}$$

$$= 0.25\text{V}$$

$$S_B = \frac{0.25\text{V}}{10\Omega}$$

$$= 25\text{ mV}/\Omega$$

**08. Ans: (b)**

**Sol:** Resolution =  $\frac{200}{100} \times \frac{1}{10}$   
= 0.2 V

**09. Ans: (a & b)**

**Sol:** RSE = LE =  $\frac{\text{Error}}{\text{True Value}} \times 100$


The Error which is expressed with respect to true value is called

- Relative static error
- % Limiting error

# Chapter **2** Basics of Electrical Instruments

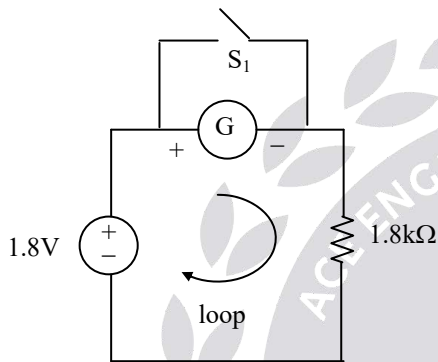01. Ans: (d)

Sol: The pointer swings to 1 mA and returns, settles at 0.9 mA i.e, pointer has oscillations. Hence, the meter is under-damped. Now the current in the meter is 0.9 mA.



Applying KVL to circuit,

$$1.8 \text{ V} - 0.9 \text{ mA} \times R_m - 0.9 \text{ mA} \times 1.8 \text{ k}\Omega = 0$$

$$1.8 \text{ V} - 0.9 \times 10^{-3} R_m - 1.62 = 0$$

$$R_m = \frac{0.18}{0.9 \times 10^{-3}} = 200 \Omega$$

02. Ans: 32.4° and 21.1°

Sol:  $I_1 = 5 \text{ A}$ ,  $\theta_1 = 90^\circ$ ;  $I_2 = 3 \text{ A}$ ,  $\theta_2 = ?$

$\theta \propto I^2$  (as given in Question)

(i) Spring controlled

$$\theta \propto I^2$$

$$\frac{\theta_2}{\theta_1} = \left( \frac{I_2}{I_1} \right)^2$$

$$\Rightarrow \frac{\theta_2}{90} = \left( \frac{3}{5} \right)^2$$

$$\theta_2 = 32.4^\circ$$

(ii) Gravity controlled

$$\sin \theta \propto I^2$$

$$\frac{\sin \theta_2}{\sin \theta_1} = \left( \frac{I_2}{I_1} \right)^2$$

$$\frac{\sin \theta_2}{\sin 90} = \left( \frac{3}{5} \right)^2$$

$$\Rightarrow \frac{\sin \theta_2}{1} = 0.36$$

$$\theta_2 = \sin^{-1}(0.36) = 21.1^\circ$$

# Chapter 3 Electromechanical Indicating Instruments


01. Ans: (c)

Sol:  $S = \frac{1}{1000} \Omega/\text{volt}$

$$S = \frac{1}{I_{\text{fsd}}} \Omega/V$$

$$I_{\text{fsd}} = \frac{1}{S} = \frac{1}{1000} = 1 \text{ mA}$$

100 V → 1 mA  
 50 V → ?  
 = 0.5 mA

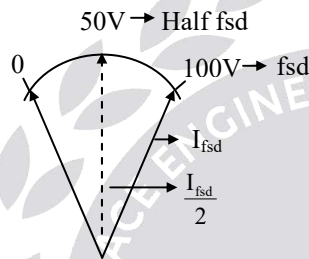

02. Ans: (a)

Sol:


	1°C↑	10°C	T <sub>c</sub>	θ
Spring stiffness(K <sub>c</sub> )	0.04%↓	0.4%↓	0.4%↓	0.4%↑
			T <sub>d</sub>	θ
Strength of magnet (B)	0.02%↓	0.2%↓	0.2%↓	0.2%↓

Net deflection (θ<sub>net</sub>) = 0.4%↑ - 0.2%↓  
 = 0.2% ↑

Increases by 0.2%

03. Ans: (a)

Sol:

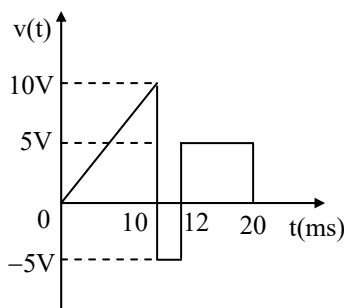

PMMC meter reads Average value

$$V_{\text{avg}} = \frac{\left(\frac{1}{2} \times 10 \times 10\text{ms}\right) + (-5\text{V} \times 2\text{ms}) + (5\text{V} \times 8\text{ms})}{20\text{ms}}$$

$$= \frac{50 - 10 + 40}{20} = 4\text{V}$$

(or)

$$\text{Avg. value} = \frac{1}{20} \left[ \int_0^{10} (1)t \, dt - \int_{10}^{12} 5 \, dt + \int_{12}^{20} 5 \, dt \right]$$

$$= \frac{1}{20} \left[ \left[ \frac{t^2}{2} \right]_0^{10} - 5[t]_{10}^{12} + 5[t]_{12}^{20} \right]$$

$$= 4\text{V}$$

04. Ans: 3.6 MΩ

Sol:  $V_m = (0 - 200) \text{ V}$  ;  $S = 2000 \Omega/V$

$$V = (0 - 2000) \text{ V}$$

$$R_m = s \times V_m$$

$$= 2000 \Omega/V \times 200 \text{ V}$$

$$= 400000 \Omega$$

$$R_{\text{sc}} = R_m \left( \frac{V}{V_m} - 1 \right)$$

$$= 400000 \left( \frac{2000}{200} - 1 \right)$$

$$= 3.6 \text{ M}\Omega$$

05. Ans: (c)

Sol:  $T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$

$$K_c \theta = \frac{I^2}{2} \frac{dL}{d\theta}$$

$$25 \times 10^{-6} \times \theta = \frac{25}{2} \times \left( 3 - \frac{\theta}{2} \right) \times 10^{-6}$$



$$2\theta = 3 - \frac{\theta}{2}$$

$$\frac{5}{2}\theta = 3$$

$$\theta = 1.2 \text{ rad}$$

**06. Ans: 2511.5 Ω**

**Sol:**

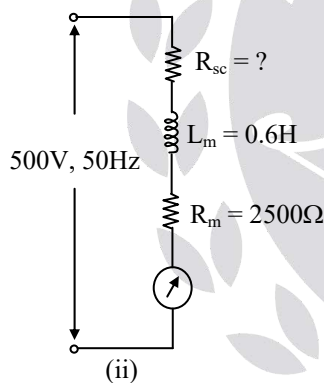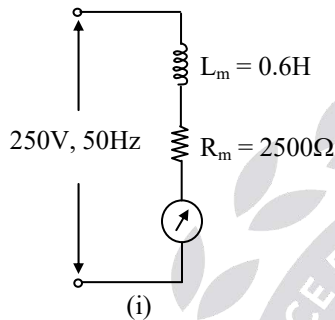

Current is same in case (i) & (ii)

In case (i),

$$I_m = \frac{250 \text{ V}}{\sqrt{R_m^2 + (\omega L_m)^2}}$$

$$= \frac{250 \text{ V}}{\sqrt{(2500)^2 + (2\pi \times 50 \times 0.6)^2}}$$

$$= 0.0997 \text{ A}$$

In case (ii),

$$I_m = \frac{250 \text{ V}}{\sqrt{(R_m + R_{sc})^2 + (\omega L_m)^2}}$$

$$0.0997 \text{ A} = \frac{500 \text{ V}}{\sqrt{(2500 + R_{sc})^2 + (2\pi \times 50 \times 0.6)^2}}$$

$$\sqrt{(2500 + R_{sc})^2 + 35.53 \times 10^3} = \frac{500}{0.0997}$$

$$\sqrt{(2500 + R_{sc})^2 + 35.53 \times 10^3} = 5.015 \times 10^3$$

$$R_{sc} = 2511.5 \Omega$$

**07. Ans: 0.1025 μF**


**Sol:**  $C = \frac{0.41 L_m}{R_{sc}^2}$

$$C = \frac{0.41 \times 1}{(2 \text{ k}\Omega)^2}$$

$$= 0.1025 \mu\text{F}$$

**08. Ans: (c)**

**Sol: MC - connection**

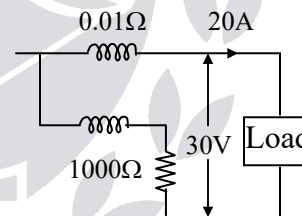


Error due to current coil

$$= \frac{20^2 \times 0.01}{(30 \times 20)} \times 100$$

$$= 0.667\%$$

**LC - connection**

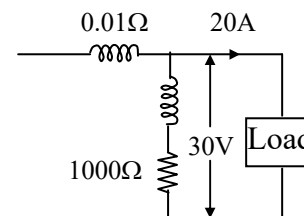

Error due to potential coil

$$= \frac{(30^2 / 1000)}{(30 \times 20)} \times 100$$

$$= 0.15\%$$

As per given options, 0.15% high

**09. Ans: (c)**

**Sol:**  $R_{\text{load}} = \frac{V}{I} = \frac{200}{20} = 10 \Omega$

For same error  $R_L = \sqrt{R_C \times R_V}$

$$\therefore 100 = 10 \times 10^3 \times R_C$$

$$\Rightarrow R_C = 0.01 \Omega$$

**10. Ans: (d)**

**Sol:**  $R_p = 1000 \Omega, L_p = 0.5 \text{ H}, f = 50 \text{ Hz},$

$$\cos \phi = 0.7,$$

$$X_{Lp} = 2 \times \pi \times f \times L, \tan \phi = 1$$

$$= 2 \times \pi \times 50 \times 0.5$$

$$= 157 \Omega$$

$$\tan \beta = \frac{X_{Lp}}{R_p}$$

$$\% \text{ Error} = \pm (\tan \phi \tan \beta) \times 100$$

$$= \pm \left( 1 \times \frac{157}{1000} \right) \times 100$$

$$= 15.7\% \approx 16\%$$

**11. Ans: (a, b & c)**

**Sol:** Sensitivities related to galvanometer is/are:

- Current sensitivity
- Voltage sensitivity
- Megohm sensitivity

**12. Ans: (a, b & c)**

**Sol:** In moving iron ammeter, the errors associated with dc current measurement is,

- Temperature error
- Hysteresis error
- Stray magnetic field error

**13. Ans: (a & c)**

**Sol:** In electrodynamic type instruments,

- Fixed coil is air core
- Moving coil is air core

**14. Ans: (a, b & d)**


**Sol:** The hysteresis error in moving iron type instruments can be minimized by,

- Using small iron piece,
- Using iron parts at low flux density,
- Using iron alloy with narrow hysteresis loop.

# Chapter 4 Measurement of Power

01. Ans: (b)

Sol:

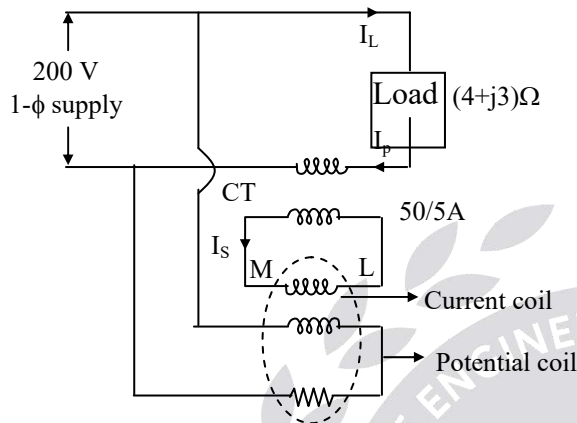

Potential coil voltage = 200 V

C.T. primary current ( $I_p$ )

$$I_p = I_L = \frac{200 \text{ V}}{\sqrt{4^2 + 3^2} \tan^{-1}\left(\frac{3}{4}\right)}$$

$$I_p = I_L = \frac{200 \text{ V}}{5 \angle 36.86^\circ}$$

$$I_p = 40 \angle -36.86^\circ$$

$$\frac{I_p}{I_s} = \frac{50}{5}$$

$$\frac{40}{I_s} = \frac{50}{5}$$

$$I_s = \frac{5}{50} \times 40 = 4 \text{ A}$$

C.T secondary ( $I_s$ ) =  $4 \angle -36.86^\circ$


Wattmeter current coil =  $I_c$

$$= 4 \angle -36.86^\circ$$

Wattmeter reading

$$= 200 \text{ V} \times 4 \times \cos(36.86)$$

$$= 640.08 \text{ W}$$

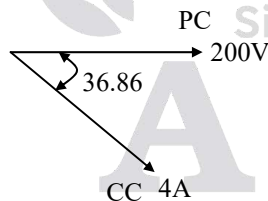


02. Ans: (c)

$$\text{Sol: } W = \frac{E_1}{\sqrt{2}} \times \frac{I_1}{\sqrt{2}} \cos \phi_1 + \frac{E_3}{\sqrt{2}} \times \frac{I_3}{\sqrt{2}} \cos \phi_3$$

$$W = \frac{1}{2} [E_1 I_1 \cos \phi_1 + E_3 I_3 \cos \phi_3]$$

03. Ans: (c)

Sol:

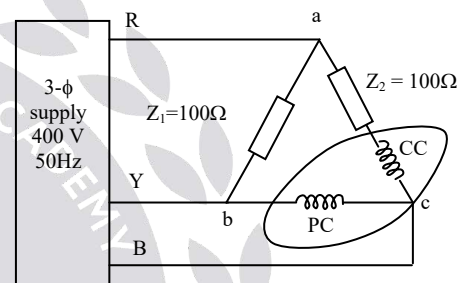

Based on R-Y-B

Assume abc phase sequence

$$V_{ab} = 400 \angle 0^\circ ;$$

$$V_{bc} = 400 \angle -120^\circ$$

$$V_{ca} = 400 \angle -240^\circ \text{ or } 400 \angle 120^\circ$$

$$\text{Current coil current } (I_c) = \frac{V_{ca}}{Z_2}$$


$$= \frac{400 \angle 120^\circ}{100 \Omega}$$

$$= 4 \angle 120^\circ$$

Potential coil voltage ( $V_{bc}$ ) =  $400 \angle -120^\circ$

$$W = 400 \times 4 \times \cos(240)$$


$$= -800 \text{ W}$$

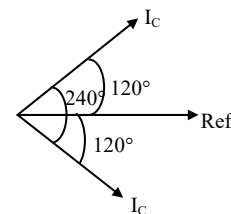



**04. Ans: -596.46 W**

**Sol:**

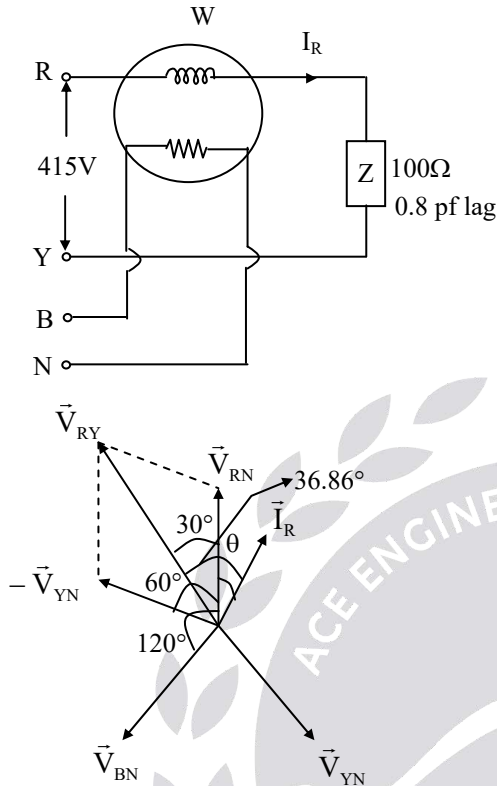

Current coil is connected in 'R<sub>phase</sub>', it reads ' $\vec{I}_R$ ' current.

Potential coil reads phase voltage i.e.,  $\vec{V}_{BN}$

$$W = \vec{V}_{BN} \times \vec{I}_R \times \cos(\vec{V}_{BN} \cdot \vec{I}_R)$$

$$V_L = 415 \text{ V}, V_{BN} = \frac{415}{\sqrt{3}} \text{ V}$$

$$I_R = \frac{V_{RY}}{Z} = \frac{415}{100} = 4.15 \text{ A}$$

$$\cos \phi = 0.8$$

$$\Rightarrow \phi = 36.86 \text{ between } \vec{V}_{RY} \text{ \& } \vec{I}_R$$

$$\theta = 36.86^\circ - 30^\circ = 6.86^\circ$$

Now angle between  $\vec{V}_{BN}$  and  $\vec{I}_R$

$$= 120 + 6.86 = 126.86^\circ$$

$$W = \frac{415}{\sqrt{3}} \times 4.15 \times \cos(126.86)$$

$$= -596.467 \text{ W}$$

**05. Ans: (d)**

**Sol:**  $V_L = 400 \text{ V}, I_L = 10 \text{ A}$

$$\cos \phi = 0.866 \text{ lag}, \phi = 30^\circ$$

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$

$$W_1 = 400 \times 10 \times \cos(30 - 30) = 4000 \text{ W}$$

$$W_2 = 400 \times 10 \times \cos(30 + 30) = 2000 \text{ W}$$

**06. Ans: (b)**

$$\text{Sol: } \phi = \tan^{-1} \left[ \frac{\sqrt{3}(W_1 - W_2)}{(W_1 + W_2)} \right]$$

$$\text{Power factor} = \cos \phi$$

$$= 0.917 \text{ lag (since load is inductive)}$$

**07. Ans: W = 519.61 VAR**

**Sol:**

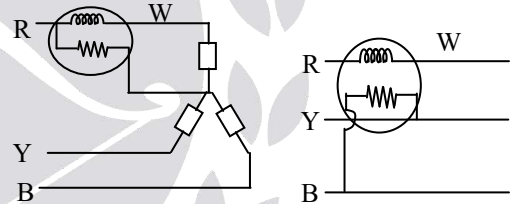


Fig. (a)

Fig. (b)

$$W = 400 \text{ watt}; W = V_{ph} I_{ph} \cos \phi$$

$$V_{ph} I_{ph} = 400/0.8$$

This type of connection gives reactive power

$$W = \sqrt{3} V_p I_p \sin \phi$$


$$= \sqrt{3} \times \frac{400}{0.8} \times 0.6$$

$$= 519.6 \text{ VAR}$$

**08. Ans: (a & d)**

**Sol:** The errors in power measurement because of eddy currents in wattmeters are such that measured power in comparison to true power is,

- Higher for lagging power factor
- Higher for leading power factor

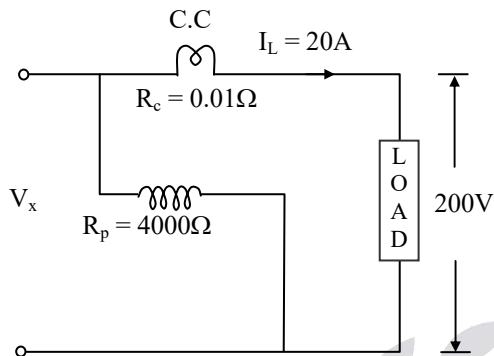**09. Ans: (a & d)**
**Sol: Case (i):**


$$I_L = 20 \text{ A, P.F} = 0.8 \text{ (lag)}$$


$$P_{\text{true}} = VI \cos\phi = 200 \times 20 \times 0.8$$

$$P_{\text{true}} = 3200 \text{ W}$$

$$\begin{aligned} \text{Error due to C.C} &= R_c = (20)^2 \times 0.01 \\ &= 4 \text{ W} \end{aligned}$$

Measured error due to C.C on load side

$$= \frac{4}{3200} \times 100 = 0.125\%$$

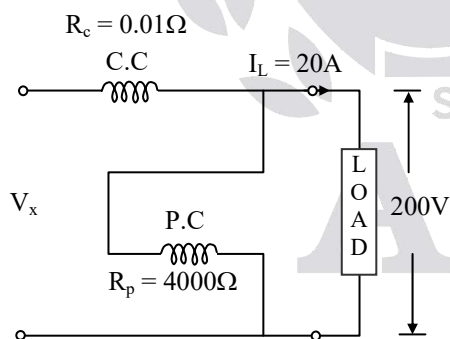**Case (ii):**


$$\text{Error due to P.C} = \frac{V^2}{R_p} = \frac{(200)^2}{4000} = 10 \text{ W}$$

Measured error due to C.C on source side or P.C on load side

$$= \frac{10}{3200} \times 100$$

$$= 0.3125\%$$

So both options a &amp; d are correct.

**10. Ans: (a & c)**
**Sol:**  $W = 1200 \text{ W}$  &  $W_2 = 600 \text{ W}$  (given)

Note:  $W_1 = 2W_2$

for  $W_1 = 2W_2$  or  $W_2 = 2W_1 \rightarrow \cos\phi = 0.866$

So option (c) is correct.

total measured power =  $W_1 + W_2$

$$= 1200 + 600$$

$$= 1800 \text{ W}$$

So option (a) is also correct.

# Chapter 5 Measurement of Energy

**01. Ans: (a)**

**Sol:** Energy consumed in 1 minute

$$= \frac{240 \times 10 \times 0.8}{1000} \times \frac{1}{60} = 0.032 \text{ kWh}$$

Speed of meter disc

= Meter constant in rev/kWhr  $\times$  Energy consumed in kWh/minute

$$= 400 \times 0.032$$

$$= 12.8 \text{ rpm (revolutions per minute)}$$

**02. Ans: (a)**

**Sol:** Energy consumed (True value)

$$= \frac{230 \times 5 \times 1}{1000} \times \frac{3}{60} = 0.0575 \text{ kWhr}$$

Energy recorded (Measured value)

$$= \frac{\text{No. of rev (N)}}{\text{meter constant (k)}} \\ = \frac{90 \text{ rev}}{1800 \text{ rev/kWh}} = 0.05 \text{ kWhr}$$

$$\% \text{Error} = \frac{0.05 - 0.0575}{0.0575} \times 100$$

$$= -13.04\% = 13.04\% \text{ (slow)}$$

**03. Ans: (c)**

**Sol:**  $V = 220 \text{ V}$ ,  $\Delta = 85^\circ$ ,  $I = 5 \text{ A}$

$$\text{Error} = VI [\sin(\Delta - \phi) - \cos \phi]$$

$$(1) \cos \phi = \text{UPF}, \phi = 0^\circ$$

$$\text{Error} = 220 \times 5 [\sin(85 - 0) - \cos 0]$$

$$= -4.185 \text{ W}$$

$$\approx -4.12 \text{ W}$$

$$(2) \cos \phi = 0.5 \text{ lag}, \phi = 60^\circ$$

$$\text{Error} = 220 \times 5 [\sin(85 - 60) - \cos 60]$$

$$= -85.12 \text{ W}$$

**04. Ans: (c)**

**Sol:** Meter constant = 14.4 A-sec/rev

$$= 14.4 \times 250 \text{ W-sec/rev}$$

$$= \frac{14.4 \times 250}{1000} \text{ kW-sec/rev}$$

$$= \frac{14.4 \times 250}{1000 \times 3600} \text{ kWhr/rev}$$

$$\text{Meter constant} = \frac{1}{1000} \text{ kWhr/rev}$$

Meter constant in terms of rev/kWhr = 1000

**05. Ans: (a & b)**

**Sol:** In energy meters,

$$\text{Speed of disc} \propto \frac{T_B Z}{k_3 \phi_m^2 R}$$

$$N \propto Z$$

$$N \propto \frac{1}{\phi_m^2}$$

So both options a & b are correct.

**06. Ans: (a & d)**

**Sol:**  $K = 0.4 \text{ (rev/kwhr)}$

$$\text{Recorded energy} = \frac{40}{0.4} = 100 \text{ (kwhr)}$$

So option (a) is correct

Measured energy

$$= 20 \times 10^3 \times 400 \times 0.8 \times \frac{60}{3600} \times 10^{-3}$$

$$= 106.67 \text{ (kwhr)}$$

$$\text{Error} = -6.67 \text{ (kwhr)}$$

% error measured as % of measured value

$$= \frac{-6.67}{100} \times 100 = -6.67\%$$

$$\text{Power factor} = \frac{P}{S} = \frac{288000 \times 10^3}{400000 \times 10^3}$$

$$\text{Power factor} = 0.72$$


**07. Ans: (a & c)**

**Sol:** Average monthly load factor

$$= \frac{\text{total kwhr through month}}{\text{peak load in kw} \times 720}$$

$$= \frac{288000 \times 10^3}{1600 \times 10^3 \times 720}$$

$$= \frac{1}{4} = 0.25$$

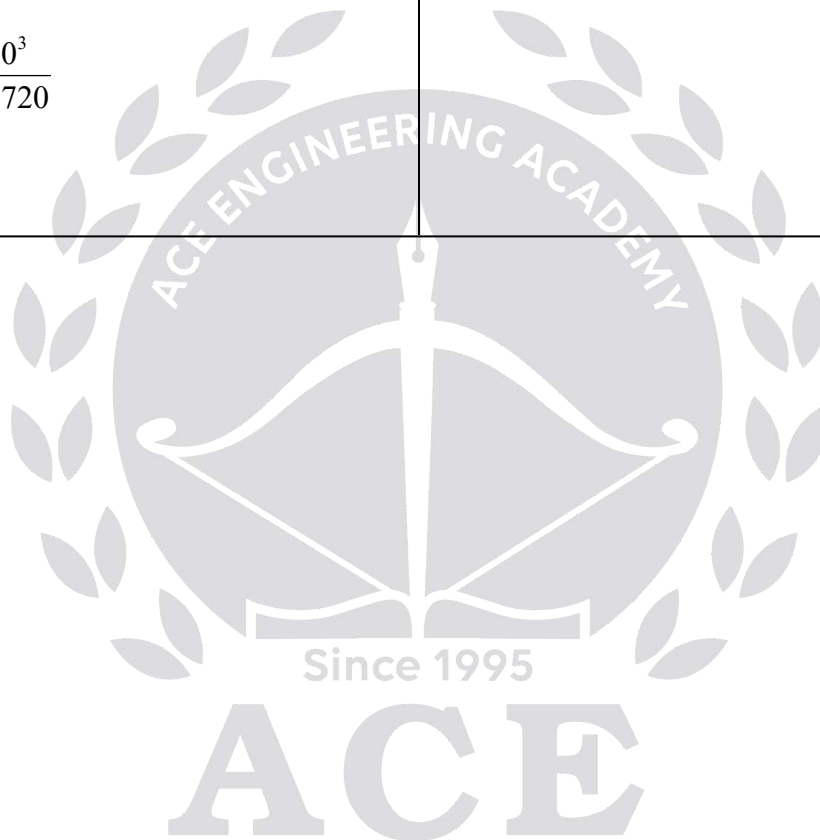

# Chapter 6 Bridge Measurement of R, L & C

01. Ans: (a)

Sol: The deflection of galvanometer is directly proportional to current passing through circuit, hence inversely proportional to the total resistance of the circuit.

Let S = standard resistance

R = Unknown resistance

G = Galvanometer resistance

$\theta_1$  = Deflection with S

$\theta_2$  = Deflection with R

$$\therefore \frac{\theta_1}{\theta_2} = \frac{R + G}{S + G}$$

$$\Rightarrow R = (S + G) \frac{\theta_1}{\theta_2} - G$$


$$= (0.5 \times 10^6 + 10 \times 10^3) \left( \frac{41}{51} \right) - 10 \times 10^3$$

$$= 0.4 \times 10^6 \Omega$$

$$= 0.4 \text{ M}\Omega$$

02. Ans: (d)

Sol:

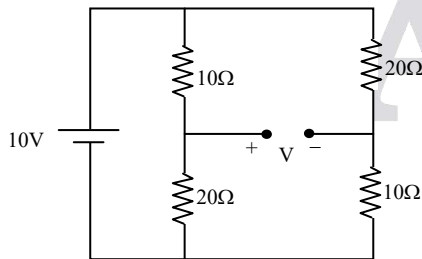

$$V = V_+ - V_-$$

$$= 10 \times \frac{20}{30} - 10 \times \frac{10}{30}$$

$$= 6.66 - 3.33$$

$$= 3.33 \text{ V}$$

03. Ans: (c)

Sol: The voltage across  $R_2$  is

$$= E \frac{R_2}{R_1 + R_2} = \frac{E}{2}$$

The voltage across  $R_1$  is

$$= E \frac{R_1}{R_1 + R_2} = \frac{E}{2}$$

$$\text{Now, } \frac{E}{2} = IR_3 + V$$

$$I = \frac{E - 2V}{2R_3} \Rightarrow I = \frac{E - 2V}{2R}$$

$$\text{and } \frac{E}{2} = IR_4$$

$$\frac{E}{2} = \left( \frac{E - 2V}{2R} \right) (R + \Delta R)$$

$$ER = (E - 2V)(R + \Delta R)$$

$$R + \Delta R = \frac{ER}{(E - 2V)}$$

$$\Delta R = \frac{ER}{(E - 2V)} - R$$

$$= \frac{ER - ER + 2VR}{(E - 2V)}$$

$$\Delta R = \frac{2VR}{(E - 2V)}$$

04. Ans: (c)

$$\text{Sol: } R = \frac{0.4343 T}{C \log_{10} \left( \frac{E}{V} \right)}$$

$$= \frac{0.4343 \times 60}{600 \times 10^{-2} \times \log_{10} \left( \frac{250}{92} \right)}$$

$$= \frac{26.058}{260.49 \times 10^{-12}}$$

$$R = 100.03 \times 10^9 \Omega$$

**05. Ans: 0.118 μF, 4.26kΩ**

**Sol:** Given:  $R_3 = 1000 \Omega$

$$C_1 = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$= \frac{2.3 \times 4\pi \times 10^{-7} \times 314 \times 10^{-4}}{0.3 \times 10^{-2}}$$

$$C_1 = 30.25 \mu\text{F}$$

$$\delta = 9^\circ \text{ for } 50 \text{ Hz}$$

$$\tan \delta = \omega C_1 r_1$$

$$= \omega L_4 R_4$$

$$\Rightarrow r_1 = 16.67 \Omega$$

$$\text{Variable resistor } (R_4) = R_3 \left( \frac{C_1}{C_2} \right)$$

$$R_4 = 4.26 \text{ k}\Omega$$

$$C_4 = 0.118 \mu\text{F}$$

**06. Ans: (a)**


**Sol:** It is Maxwell Inductance Capacitance bridge

$$R_x R_4 = R_2 R_3$$

$$R_x = \frac{R_2 R_3}{R_4}$$

$$R_x = \frac{750 \times 2000}{4000}$$

$$R_x = 375 \Omega$$

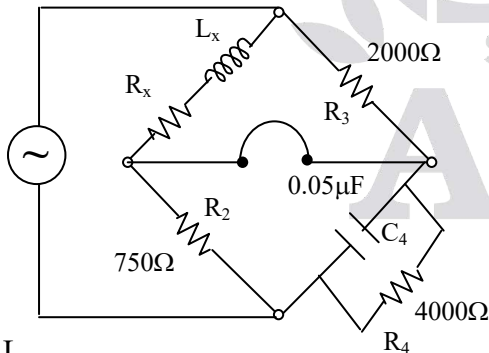

$$\frac{L_x}{C_4} = R_2 R_3$$

$$L_x = C_4 R_2 R_3$$

$$L_x = 0.05 \times 10^{-6} \times 750 \times 2000$$

$$L_x = 75 \text{ mH}$$

**07. Ans: (a & d)**

**Sol:** At balance

$$\left( R_1 + \frac{1}{j\omega C_1} \right) R_4 = R_2 \left( \frac{R_3}{1 + j\omega C_3 R_3} \right)$$

$$R_4 (j\omega C_1 R_1 + 1) R_4 = \frac{j\omega C_1 R_2 R_3}{1 + j\omega C_3 R_3}$$

$$R_4 (j\omega C_1 R_1 - \omega^2 C_1 R_1 C_3 R_3 + 1 + j\omega C_3 R_3)$$

$$= j\omega C_1 R_1 C_3 R_3$$

$$j\omega (R_1 C_1 R_4 + C_3 R_3 R_4 - C_1 R_2 R_3)$$

$$= \omega^2 C_1 R_1 C_3 R_3 R_4 - R_4 \dots \dots \dots (i)$$

Equate imaginary term to zero

$$R_1 C_1 R_4 + C_3 R_3 R_4 = C_1 R_2 R_3$$

$$\frac{R_1}{R_3} + \frac{C_3}{C_1} = \frac{R_2}{R_4}$$

So option (a) is correct

So equate real terms to zero in equation (i)

$$\omega = \frac{1}{\sqrt{R_1 R_3 C_1 C_3}}$$

So both options a & d are correct.

**08. Ans: (a, c & d)**

**Sol:**

- Direct deflection method is commonly used for cable resistance measurement
- Kelvin double bridge eliminates error due to contact and lead wire resistance
- Earth electrode resistance must be of low value due to safety reasons.

**09. Ans: (a, b, c & d)**

**Sol:** The value of earthing electrode resistance depends upon:

- Specific resistance of soil
- Depth of electrode
- Shape of electrode
- Electrode material

# Chapter 7 Potentiometers & Instrument Transformers

01. Ans: (d)

Sol: Under null balanced condition the current flow in through unknown source is zero. Therefore the power consumed in the circuit is ideally zero.

02. Ans: (d)

Sol: Potentiometer is used for measurement of low resistance, current and calibration of ammeter.

03. Ans: (a)

Sol: Since the instrument is a standardized with an emf of 1.018 V with sliding contact at 101.8 cm, it is obvious that a length 101.8 cm represents a voltage of 1.018.

$$\begin{aligned} \text{Resistance of 101.8 cm length of wire} \\ &= (101.8/200) \times 400 \\ &= 203.6 \Omega \end{aligned}$$

∴ Working current

$$\begin{aligned} I_m &= 1.018/203.6 \\ &= 0.005 \text{ A} = 5 \text{ mA} \end{aligned}$$

Total resistance of the battery circuit

$$\begin{aligned} &= \text{resistance of rheostat} \\ &\quad + \text{resistance of slide wire} \end{aligned}$$

∴ Resistance of rheostat

$R_h =$  total resistance

$$\begin{aligned} &\quad - \text{resistance of slide wire} \\ &= \frac{3}{5 \times 10^{-3}} - 400 \\ &= 600 - 400 \\ &= 200 \Omega \end{aligned}$$

04. Ans: (b)

Sol: Voltage drop per unit length

$$= \frac{1.45 \text{ V}}{50 \text{ cm}} = 0.029 \text{ V/cm}$$

Voltage drop across 75 cm length

$$= 0.029 \times 75 = 2.175 \text{ V}$$

Current through resistor (I)

$$\begin{aligned} &= \frac{2.175 \text{ V}}{0.1 \Omega} \\ &= 21.75 \text{ A} \quad (\text{or}) \end{aligned}$$

75 cm  $\rightarrow$  0.1  $\Omega$

50 cm  $\rightarrow$  ?

Slide wire resistance with standard cell


$$\begin{aligned} &= \frac{50}{70} \times 0.1 \\ &= 0.067 \Omega \end{aligned}$$

Then  $0.067 \times I_w = 1.45 \text{ V}$

$$I_w = \frac{1.45}{0.067} = 21.75 \text{ A}$$

05. Ans: (a)

Sol:

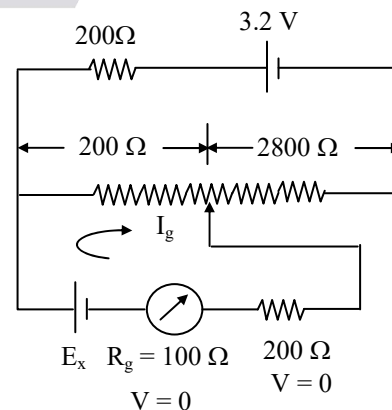

Under balanced,  $I_g = 0$


$$E_x = 3.2 \text{ V} \times \frac{200}{(200 + 200 + 2800)}$$

$$= 0.2 \text{ V}$$

$$E_x = 200 \text{ mV}$$

**06. Ans: (a)**

**Sol:**

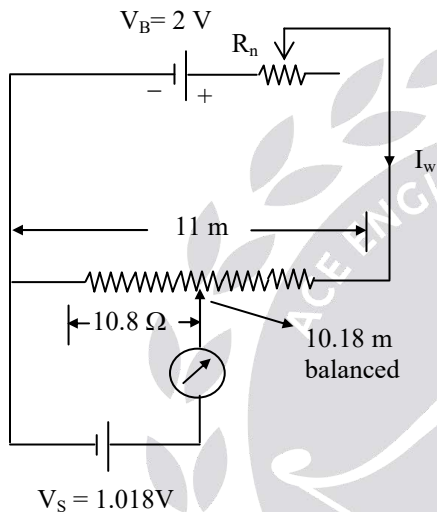

Resistance  $1 \Omega/\text{cm}$

For 11 m  $\rightarrow 11 \Omega$

For 10m + 18cm  $\rightarrow 10.8\Omega$

$$I_w \times 10.8\Omega = 1.018 \text{ V}$$

$$I_w = \frac{V_B}{R_n + 11}$$

$$\Rightarrow 0.1 = \frac{2}{R_n + 11\Omega}$$

$$R_n = \frac{2}{0.1} - 11$$

$$= 9 \Omega$$

**07. Ans:  $R_1 = 19 \text{ M}\Omega$  &  $R_2 = 1 \text{ M}\Omega$**

**Sol:** By using voltage division rule we can write

$$V_2 = \frac{R_2}{R_1 + R_2} V_x$$

$$V_x = 100 \text{ V (given)}$$

$$R_1 + R_2 = 20 \text{ M}\Omega \text{ (given)}$$


$$V_2 = 5 \text{ V (given)}$$

$$5 = \frac{R_2}{20 \text{ M}\Omega} \times 100$$

$$R_2 = 1 \text{ M}\Omega \text{ \& } R_1 = 19 \text{ M}\Omega$$

**08. Ans: (a & c)**

**Sol:**

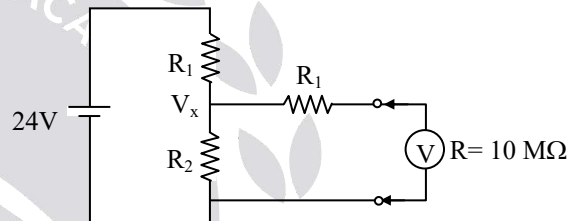

**Case (i):** True value of voltage measured without considering the voltmeter internal resistance

$$V_x = \frac{250}{250 + 250} \times 24 = 12 \text{ V}$$

So option (a) is correct

**Case (ii):**

Now we consider voltmeter internal resistance (r)

$$\frac{24 - V_x}{250} = \frac{V_x}{250} + \frac{V_x}{10}$$

$$24 - V_x = V_x + 25 V_x$$

$$27 V_x = 24$$

$$V_x = \frac{24}{27} = \frac{8}{9} = 0.89 \text{ V}$$

So option (b) is incorrect.



**Case (iii):** Considering additional resistance

$R_1$  then  $V_x$  must be 90% of accuracy

$$V_x = 0.9 \times 12 \text{ V} = 10.8 \text{ V}$$

$$\frac{24 - 10.8}{250} = \frac{10.8}{250} + \frac{10.8}{10 + R_1}$$

$$13.2 = 10.8 + \left( \frac{10.8 \times 250}{10 + R_1} \right)$$

$$R_1 = 1115 \text{ M}\Omega$$

So option (c) is true.

So we can say that option a & c are correct.

**09. Ans: (a & c)**

**Sol:** Unknown resistance =  $\frac{0.2(\Omega)}{1.75(\text{V})} \times 0.525 (\text{V})$

$$R_x = 0.06 (\Omega)$$

Power lost in unknown resistance

$$= I^2 R_x$$

$$= \left( \frac{1.75}{0.2} \right)^2 \times 0.06$$

$$= 4.6 \text{ W}$$

**10. Ans: (a, c & d)**

**Sol:** The following statements related to instrumentation transformers are:

- CTs and PTs are used for measurement of current and voltage measurement of high power circuits.
- Circular cores are used for CTs to eliminate joints and hence to decrease the reluctance of flux path.
- Standard burden rating for CTs are 2.5, 5, 7.5, 15 etc.

**11. Ans: (a, c & d)**

<b>Sol: Parameter</b>	<b>Power transformer</b>	<b>Potential transformer</b>
• Efficiency	Low	High
• Core size	High	Low
• Core type	Rectangular	Rectangular

**12. Ans: (a, b, c & d)**

**Sol:**

- A CT (current transformer) is equivalent to series transformer
- A PT (Potential transformer) is equivalent to parallel transformer.
- The marked ratio on instrumentation transformer (CT or PT) is nominal ratio.
- Errors in current and potential transformers are due to no-load current.

# Chapter 8 Cathode Ray Oscilloscope

**01. Ans: (b)**

$$\begin{aligned} \text{Sol: Time period of one cycle} &= \frac{8.8}{2} \times 0.5 \\ &= 2.2 \text{ msec} \end{aligned}$$

$$\begin{aligned} \text{Therefore frequency} &= \frac{1}{T} = \frac{1}{2.2 \times 10^{-3}} \\ &= 454.5 \text{ Hz} \end{aligned}$$

$$\begin{aligned} \text{The peak to peak Voltage} &= 4.6 \times 100 \\ &= 460 \text{ mV} \end{aligned}$$

$$\text{Therefore the peak voltage } V_m = 230 \text{ mV}$$

$$\text{R.M.S voltage} = \frac{230}{\sqrt{2}} = 162.6 \text{ mV}$$

**02. Ans: (c)**

**Sol:** In channel 1

The peak to peak voltage is 5V and peak to peak divisions of upper trace voltage = 2

Therefore for one division voltage is 2.5V

In channel 2, the no. of divisions for unknown voltage = 3

Divisions = 3, voltage/division = 2.5

$$\therefore \text{ voltage} = 2.5 \times 3 = 7.5 \text{ V}$$

Similarly frequency of upper trace is 1kHz

So the time period T

$$\text{(for four divisions)} = \frac{1}{f}$$

$$T = \frac{1}{10^3} = 1 \text{ msec}$$

i.e., for four divisions time

period = 1m sec

In channel 2, for eight divisions of unknown waveform time period = 2m sec.

**03. Ans: (c)**

**Sol:** No. of cycles of signal displayed

$$\begin{aligned} &= f_{\text{signal}} \times T_{\text{sweep}} \\ &= 200\text{Hz} \times \left(10 \text{ cm} \times \frac{0.5\text{ms}}{\text{cm}}\right) = 1 \end{aligned}$$

i.e., one cycle of sine wave will be displayed.

$$\text{We know } V_{\text{rms}} = \frac{V_{\text{p-p}}}{2\sqrt{2}}$$

$$V_{\text{rms}} = \frac{N_v \times \text{Volt/div}}{2\sqrt{2}}$$

$$\Rightarrow N_v = \frac{2\sqrt{2} \times V_{\text{rms}}}{\text{Volt/div}}$$


$$\Rightarrow N_v = \frac{2\sqrt{2} \times 300\text{mV}}{100\text{mv/cm}}$$

$$\Rightarrow N_v = 8.485\text{cm}$$

i.e., 8.485cm required to display peak to peak of signal. But screen has only 8cm (vertical) As such, peak points will be clipped.

**04. Ans: (b)**

**Sol:**

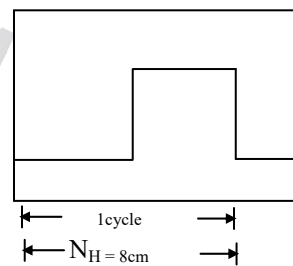

→ Given data: Y input signal is a symmetrical square wave

$$f_{\text{signal}} = 25\text{kHz}, V_{\text{pp}} = 10\text{V}$$

→ Screen has 10 Horizontal divisions & 8 vertical divisions

which displays 1.25 cycles of Y-input signal.

$$\rightarrow V_{pp} = N_V \times \frac{\text{VOLT}}{\text{div}}$$


$$\Rightarrow \frac{\text{VOLT}}{\text{div}} = \frac{V_{pp}}{N_V} = \frac{10V}{5\text{cm}} = 2 \text{ volt/ c.m}$$

$$\rightarrow T_{\text{signal}} = N_H \text{ per cycle} \times \frac{\text{TIME}}{\text{div}}$$

$$\Rightarrow \frac{\text{TIME}}{\text{div}} = \frac{T_{\text{signal}}}{N_H \text{ per cycle}} = \frac{1}{25\text{kHz} \times 8\text{cm}} = 5 \frac{\mu\text{s}}{\text{cm}}$$

**05. Ans: (a)**


**Sol:** Frequency ratio is 2

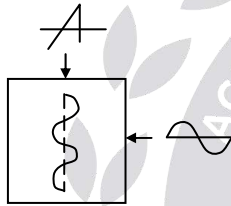

∴ Two cycles of sine wave displayed on vertical time base.

**06. Ans: (a)**

**Sol:**

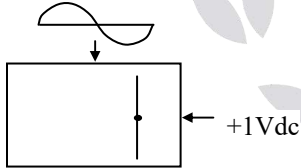

Vertical straight line

**07. Ans: (a)**


**Sol:** Since the coupling mode is set to DC the capacitance effect at the input side is zero. Therefore the waveform displayed on the screen is both DC and AC components.

**08. Ans: (a)**

**Sol:** In order to display correctly, a delay line of 150 ns has to be inserted in to the Y-channel between output of vertical amplifier and Y-input of CRT.


**09. Ans: (d)**

**Sol:**

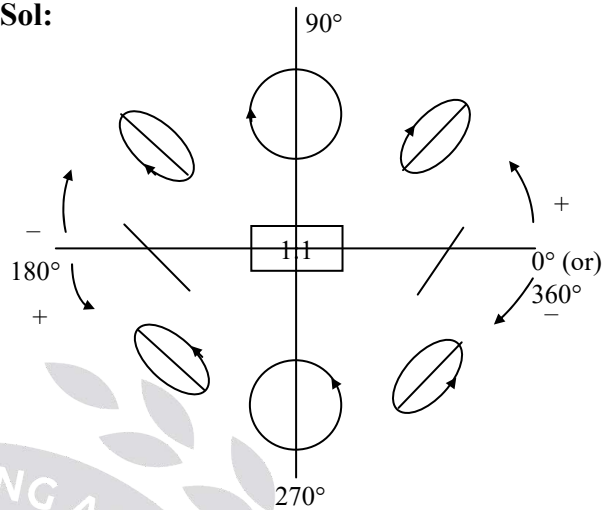

**10. Ans: (b)**

**Sol:**

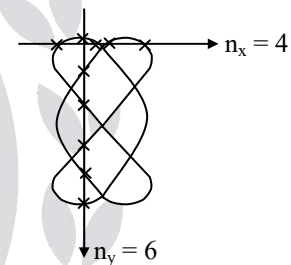



$$f_y = \frac{n_x}{n_y} f_x$$

$$= \frac{4}{6} \times 600\text{Hz}$$

$$= 400 \text{ Hz}$$

**11. Ans: (d)**

**Sol:**

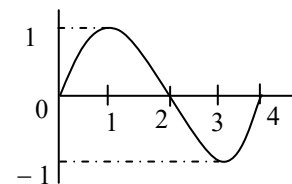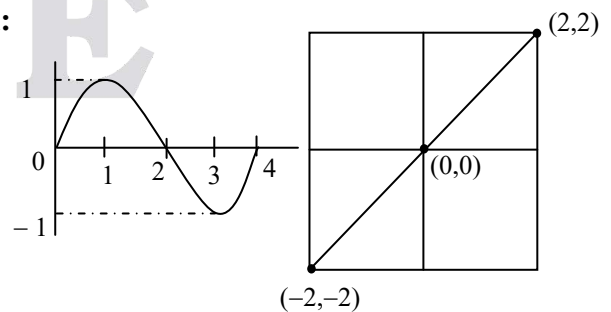


Let  $K_y = K_x = 2 \text{ Volt/div}$

t	$V_y$	$V_x$	$d_y = k_y V_y$	$d_x = k_x V_x$	points
0	0	0	0	0	(0,0)
1	1	1	2	2	(2,2)
2	0	0	0	0	(0,0)
3	-1	-1	-2	-2	(-2,-2)
4	0	0	0	0	(0,0)

By using these points draw the line which is a diagonal line inclined at  $45^\circ$  w.r.t the x-axis.

**12. Ans: (a, b & c)**

**Sol:**

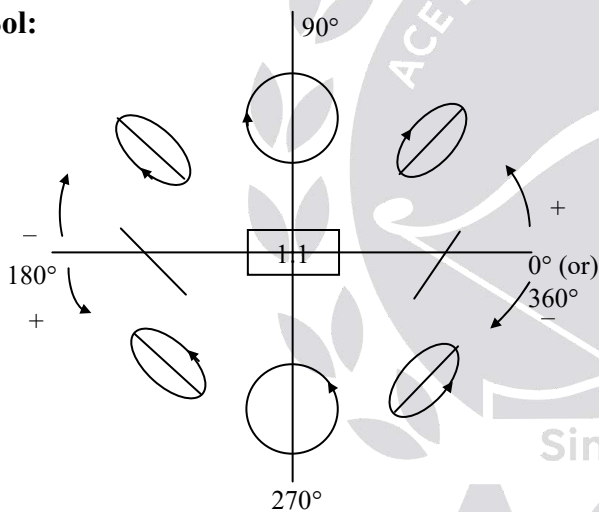

- If the major axis of the ellipse lies in the first and third quadrants the phase angle is either between  $0^\circ$  to  $90^\circ$  or between  $270^\circ$  to  $360^\circ$ .
- when the major axis of ellipse lies in the second and fourth quadrants, the phase angle is either between  $90^\circ$  to  $180^\circ$  or between  $180^\circ$  to  $270^\circ$ .
- an aquadag is used in a CRO to collect secondary emission electrons.

**13. Ans: (c & d)**

**Sol:**  $f_v = f_h \times \frac{\text{Horizontal cut}}{\text{Vertical cut}}$

$$f_v = f_h \times \frac{4}{2}$$

$$\frac{f_v}{f_h} = \frac{2}{1} \quad (\text{or}) \quad \frac{f_h}{f_v} = \frac{1}{2}$$

# Chapter 9 Digital Voltmeters

**01. Ans: (a)**

**Sol:** The type of A/D converter normally used in a  $3\frac{1}{2}$  digit multimeter is Dual-slope integrating type since it offers highest Accuracy, Highest Noise rejection and Highest Stability than other A/D converters.

**02. Ans: (d)**

**Sol:** DVM measures the average value of the input signal which is 1 V.  
 $\therefore$  DVM indicates as 1.000 V

**03. Ans: (c)**

**Sol:**  $0.2\%$  of reading + 10 counts  $\rightarrow$  (1)  
 $= 0.2 \times \frac{100}{100} + 10(\text{sensitivity} \times \text{range})$   
 $= 0.2 \times \frac{100}{100} + 10\left(\frac{1}{2 \times 10^4} \times 200\right)$   
 $= 0.2 + 0.1 = \pm 0.3 \text{ V}$   
 $\% \text{error} = \pm \frac{0.3}{100} \times 100 = 0.3\%$

**04. Ans: (d)**

**Sol:** When  $\frac{1}{2}$  digit is present voltage range becomes double. Therefore 1V can read upto 1.9999 V.

**05. Ans: (d)**

**Sol:** Resolution =  $\frac{\text{full - scale reading}}{\text{maximum count}}$

$$= \frac{9.999\text{V}}{9999} = 1\text{mV}$$

**06. Ans: (b)**

**Sol:** Sensitivity = resolution  $\times$  lowest voltage range  
 $= \frac{1}{10^4} \times 100 \text{ mV}$   
 $= 0.01 \text{ mV}$

**07. Ans: (c)**

**Sol:** The DVM has  $3\frac{1}{2}$  digit display  
 Therefore, the count range is from 0 to 1999 i.e., 2000 counts. The scale resolution is 0.001. And, the resolutions in each selected voltage Ranges of 2V, 20V & 200V are 1mV, 10mV & 100mV.

**08. Ans: (a)**

**Sol:** Resolution =  $\frac{\text{max. voltage}}{\text{max. count}} = \frac{3.999}{3999} = 1\text{mV}$

**09. Ans: (b)**

**Sol:** A and R are true, but R is not correct explanation for A.

**10. Ans: (c)**

**Sol:** When  $\frac{1}{2}$  digit switched ON, then DVM will be able to read more than the selected range.

**11. Ans: (a, b & d)**

**Sol:** The below statements correct one(s) are

- Electronic voltmeter is more accurate than digital voltmeter.
- Electronic voltmeter employs op - amp.
- In ramp type DVM, voltage to time conversion takes place.

# Chapter 10

# Q-meter

**01. Ans: (a)**

**Sol:**  $C_1 = 300\text{pF}$        $C_2 = 200\text{ pF}$   
 $Q = 1/(\omega C_1 R) = 120 = 1/(C_2 + C_x)R$   
 $C_1 = C_2 + C_x$   
 $\therefore C_x = 100\text{ pF}$

**02. Ans: (b)**

**Sol:**  $\% \text{error} = -\frac{r}{r+R} \times 100 = -\frac{0.02}{0.02+10} \times 100$   
 $= -0.2\%$

**03. Ans: (c)**

**Sol:** Q-meter consists of R, L, C connected in series.

$\therefore$  Q-meter works on the principle of series resonance.

**04. Ans: (b)**

**Sol:** Given data:  $C_d = 820\text{ pF}$ ,  
 $\omega = 10^6\text{ rad/sec}$  &  $C = 9.18\text{ nF}$

We know,  $L = \frac{1}{\omega^2 [C + C_d]}$   
 $= \frac{1}{(10^6)^2 [9.18\text{ nF} + 820\text{ pF}]}$   
 $= 100\mu\text{H}$

The inductance of coil tested with a Q-meter is  $100\mu\text{H}$ .

**05. Ans: (b)**

**Sol:** A series RLC circuit exhibits voltage magnification property at resonance. i.e., the voltage across the capacitor will be equal to Q-times of applied voltage.

Given that V = applied voltage and

$V_0 =$  Voltage across capacitor

There fore,  $Q = \frac{V_{c\text{max}}}{V_{in}}$

$\Rightarrow Q = \frac{V_0}{V}$

**06. Ans: (b)**

**Sol:**  $f_1 = 500\text{ kHz}$ ;     $f_2 = 250\text{ kHz}$

$C_1 = 36\text{ pF}$ ;     $C_2 = 160\text{ pF}$

$n = \frac{250\text{ kHz}}{500\text{ kHz}} \Rightarrow n = 0.5$

$C_d = \frac{36\text{ pF} - (0.5)^2 160\text{ pF}}{(0.5)^2 - 1}$   
 $= 5.33\text{ pF}$

**07. Ans: (c)**

**Sol:**  $Q = \frac{\text{capacitor voltmeter reading}}{\text{Input voltage}}$

$= \frac{10}{500 \times 10^{-3}} = 20$

**08. Ans: i  $\rightarrow$  (c), ii  $\rightarrow$  (a)**

**Sol:** (i)  $C_d = \frac{C_1 - n^2 C_2}{n^2 - 1}$   
 $= \frac{360 - 288}{3} = 24\text{ pF}$

(ii)  $L = \frac{1}{\omega_1^2 [C_1 + C_d]}$   
 $= \frac{1}{[2\pi \times 500 \times 10^3]^2 [24 + 360] \times 10^{-6}} = 264\mu\text{H}$

**09. Ans: (b)**

**Sol:**  $Q_{\text{true}} = Q_{\text{meas}} \left( 1 + \frac{r}{R_{\text{coil}}} \right)$

$$Q_{\text{actual}} = Q_{\text{observed}} \left[ 1 + \frac{R}{R_s} \right]$$

**10. Ans: (c)**

**Sol:**  $1 + \frac{C_d}{C} = \frac{Q_{\text{true}}}{Q_{\text{measured}}}$

$$\Rightarrow \frac{C_d}{C} = \frac{245}{244.5} - 1$$
$$= 2.044 \times 10^{-3}$$

$$\Rightarrow \frac{C}{C_d} = 489$$





# Chapter 11 Analog Electronic Voltmeter

**01. Ans: (a)**

**Sol:** The full wave Rectifier type electronic AC voltmeter has a scale calibrated to read r.m.s value for square wave inputs. As such, the scale calibration factor used for deriving rms volt scale from DC volt scale is 1.

Reading =  $1 \times V_{dc}$  Where  $V_{dc}$  is Average voltage of output of full wave Rectifier for given input.

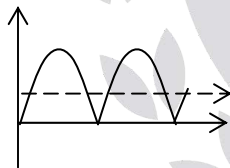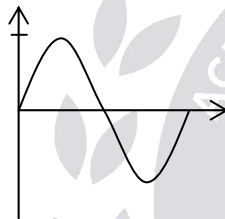This voltmeter is used to measure a sinusoidal voltage



DC voltmeter measures  $V_{dc}$  of output of FWR



$$V_{dc} = \frac{2V}{\pi}$$

Therefore, reading =  $1 \times V_{dc} = \frac{2}{\pi} V$

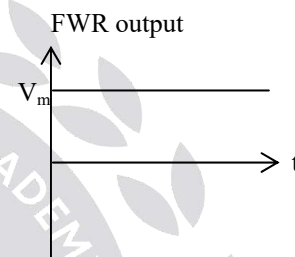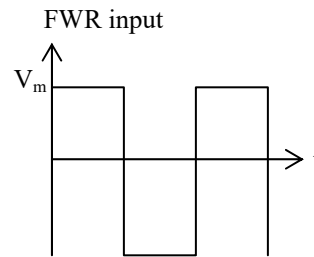**02. Ans: (b)**

**Sol:** The scale of a full wave rectifier type voltmeter is calibrated to read r.m.s for ideal sine wave i.e, reading =  $1.11V_{dc}$  where  $V_{dc}$  is average voltage of output of FWR for given input.

This voltmeter is used for square wave input



DC voltmeter measures  $V_{dc}$  of output of FWR

$$V_{dc} = V_m$$

$$\begin{aligned} \text{reading} &= 1.11V_{dc} \\ &= 1.11V_m \end{aligned}$$

i.e., indicated rms is  $1.11V_m$  where true rms of square wave is  $V_m$ .

Therefore, the multiplying factor of the meter for correction is

$$\frac{1}{1.11} \left( \because 1.11V_m \times \frac{1}{1.11} \Rightarrow V_m \right)$$

**03. Ans: (b)**

**Sol:** Given data: Voltmeter sensitivity is  $20k\Omega/V$   
Reading of 4.5V on its 5V full scale  
Reading of 6V on its 10V full scale \*Say, voltage source is  $V_s$  and its internal resistance is  $R_s$ .

**5V range:**

$$R_v = 20 \frac{k\Omega}{V} \times 5 = 100k\Omega$$



$$\text{Reading} = V_s \times \frac{100\text{k}\Omega}{R_s + 100\text{k}\Omega}$$

$$4.5\text{V} = V_s \times \frac{100\text{k}\Omega}{R_s + 100\text{k}\Omega}$$

$$\therefore V_s = \frac{4.5\text{V}}{100\text{k}\Omega} (R_s + 100\text{k}\Omega) \rightarrow (1)$$

**10V Range:**

$$R_v = 20 \frac{\text{K}\Omega}{\text{V}} \times 10\text{V}$$

$$= 200\text{k}\Omega$$

$$\text{Reading} = V_s \times \frac{200\text{k}\Omega}{R_s + 200\text{k}\Omega} = 89.9\text{k}\Omega$$

$$6\text{V} = V_s \times \frac{200\text{k}\Omega}{R_s + 200\text{k}\Omega}$$

$$\therefore V_s = \frac{6\text{V}}{200\text{k}\Omega} (R_s + 200\text{k}\Omega) \rightarrow (2)$$

Solving equation (1) & (2)

$$\begin{aligned} \frac{6\text{V}}{200\text{k}\Omega} (R_s + 200\text{k}\Omega) &= \frac{4.5\text{V}}{100\text{k}\Omega} (R_s + 100\text{k}\Omega) \\ R_s + 200\text{k}\Omega &= 1.5(R_s + 100\text{k}\Omega) \\ 0.5R_s &= 50\text{k}\Omega \\ R_s &= 100\text{k}\Omega \end{aligned}$$

Putting the value of  $R_s$  in equation (1)

$$\begin{aligned} V_s &= \frac{4.5\text{V}}{100\text{k}\Omega} (100\text{k}\Omega + 100\text{k}\Omega) \\ &= 4.5\text{V} \times 2 \\ &= 9\text{V} \end{aligned}$$

Therefore, the voltage source is 9V and its internal resistance is 100k $\Omega$

**04. Ans: (c)**

**Sol:** Given data: Full wave Bridge Rectifier AC voltmeter's AC volt range is 0-100V. The PMMC ammeter used in the design has full scale current rating of 1mA and internal resistance of 100 $\Omega$  & diodes are ideal

$$R_s = 0.9 \times \frac{V_{\text{rmsFSD}}}{I_{\text{dcFSD}}} - 2R_d - R_m$$

$$= 0.9 \times \frac{100\text{V}}{1\text{mA}} - 100\Omega$$

$$= 90\text{k}\Omega - 100\Omega$$

$$= 89.9\text{k}\Omega$$

**05. Ans: (b)**

**Sol:** Given data: PMMC ammeter full scale current range is 100 $\mu\text{A}$ , and internal resistance is 100 $\Omega$ .

Required current range is 1A

$$R_{\text{sh}} = \frac{100\Omega}{\frac{1\text{A}}{100\mu\text{A}} - 1}$$

$$\Rightarrow R_{\text{sh}} = 10\text{m}\Omega$$

$\therefore$  10m $\Omega$  in parallel with the meter

**06. Ans: (c)**

**Sol:** PMMC ammeter will read average value of current.

$$I_{\text{dc}} = 0.636 I_m$$

( $\because$  full wave rectified sinusoidal)

$$= 0.636 \times \frac{1\text{V}}{10\text{k}\Omega}$$

$$= 0.0636\text{mA}$$

$$= 63.6\mu\text{A}$$