



**ACE**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs



# ESE – 2025

## MAINS EXAMINATION

### QUESTIONS WITH DETAILED SOLUTIONS

## ELECTRICAL ENGINEERING

(Paper-2)

**ACE Engineering Academy** has taken utmost care in preparing the **ESE-2025** Examination solutions. Discrepancies, if any, may please be brought to our notice. ACE Engineering Academy do not owe any responsibility for any damage or loss to any person on account of error or omission in these solutions. ACE Engineering Academy is always in the fore front of serving the students, irrespective of the examination type (**GATE/ESE/IRMS/SSC/RRB/PSUs/PSC/GENCO/TRANSCO etc.,**).

All Queries related to **ESE-2025** Solutions are to be sent to the following email address **help@ace.online**

☎ +91- 779999 6602

[www.ace.online](http://www.ace.online) | [www.aceenggacademy.com](http://www.aceenggacademy.com)



## **ELECTRICAL ENGINEERING**

### **ESE MAINS 2025\_PAPER – II**

#### **Questions with Detailed Solutions**

#### **SUBJECT WISE WEIGHTAGE**

<b>S.No</b>	<b>NAME OF THE SUBJECT</b>	<b>Marks</b>
01	Analog and Digital Electronics	72
02	Systems and signal processing	72
03	Control systems	84
04	Electrical Machines	84
05	Power Systems	84
06	Power Electronics	84
<b>Total Marks</b>		<b>480</b>

# ONLINE



## PROGRAMMES OFFERED



### Self-Paced Learning Program

Immerse yourself in a personalized and enriching learning experience, with high-quality video content delivered by India's most esteemed and highly accomplished faculty members.

Enjoy the freedom of unlimited access, allowing you to study at your convenience from any location. Take advantage of complimentary live doubt clearing sessions and an extensive online test series to elevate your exam readiness.



LIVE

### Exclusive Online Live Classes

Engage in our exclusive live classes, offering an interactive learning experience from any location nationwide. Benefit from real-time guidance and the opportunity to resolve doubts directly with our esteemed faculty. Additionally, access recorded videos of the live sessions for convenient review before exams or to catch up on missed classes at your own pace.

0%  
No-Cost  
EMI  
Available

## ESE | GATE | PSUs | SSC | RRB & 30+ Other Exams

Streams: **CE | ME | EE | EC | CS | IN | DA**



Experienced  
Faculty



Ask an  
Expert



Live Doubt  
Clearance




Learn with  
2D & 3D  
Animations



Free Online  
Test Series



Full Set of  
Study Material

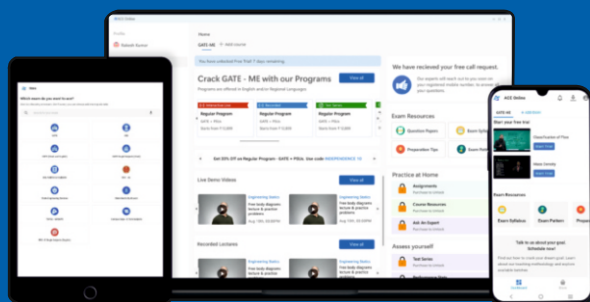

Scan QR  
& start your  
**7-DAY  
Free Trial!**



Download on the  
App Store

Get it on  
Google play

Download on the  
Windows Store

## SECTION – A

1[a] Give the circuit diagram of a negative peak clamper circuit using op-amp, and


(i) Considering  $V_{ref} = +2\text{ V}$ , sketch the output waveform for an input signal  $v_i = 2\sin(1000t)$ .

(ii) Provide conditions to achieve precision clamping and explain how will you protect op-amp against excessive discharge currents.

(iii) State how will you modify your circuit to achieve positive peak clamping

[12M]


**Solution**

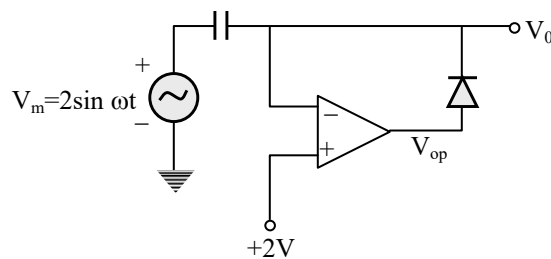

Let  $V_{op}$  is pos for diode ON

Step 1:

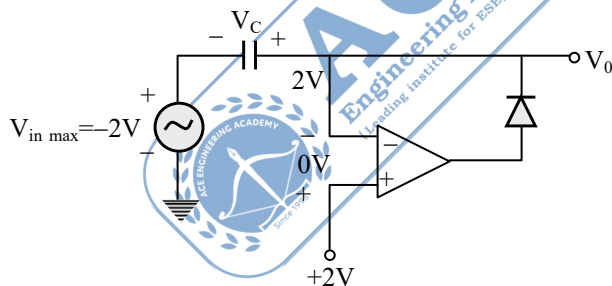
$V_{in} < 2\text{ V} \rightarrow V_{op}$  positive and capacitor charges





$$V_{Cmax} = 2 - (-2) = +4\text{ V}$$

Step 2:

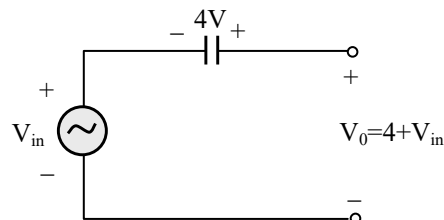After capacitor is fully charged the diode is  $R_B$





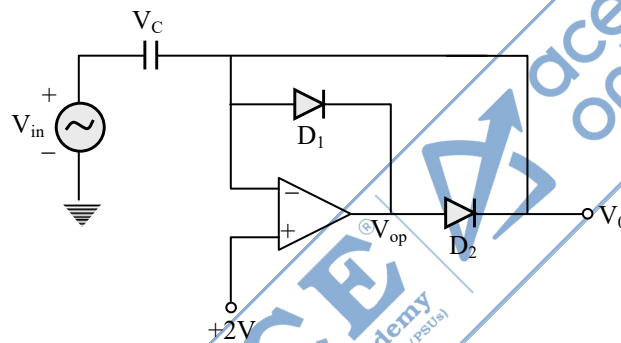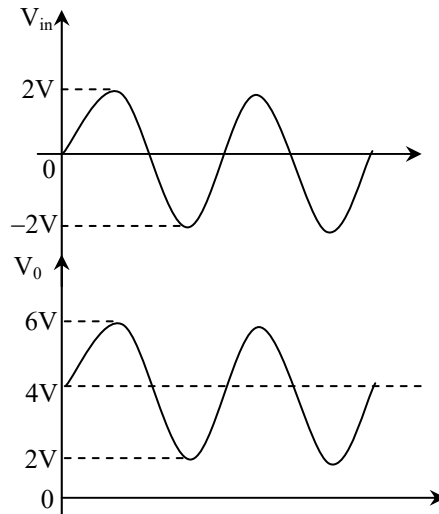

In order to avoid  $V_{op}$  to reach saturation when  $D_2$  is OFF,  $D_1$  will be ON avoiding saturation at output.

**1[b] A 7.5 kW, 440 V, 3-phase, star-connected, 50 Hz, 4-pole squirrel cage induction motor develops full load torque at a slip of 3% when operated at rated voltage and frequency. The leakage reactance of stator and rotor windings are five times the respective stator and rotor resistances. The ratio of stator to rotor winding is 3 : 5. Determine the percentage increase in stator reactance to limit starting current to 2.5 times the full load current. Assuming  $R_1$  and  $R_2$  are equal and of requisite amount, and motor has negligible magnetizing reactance and core losses. [12M]**

**Solution:**

$V_L = 440 \text{ V}$ ; Y-connected

$$V_{L/ph} = \frac{440}{\sqrt{3}} = 254.03 \text{ V}$$

Let  $R_1 = R_2 = R$ ,  $X_1 = 5 R$

$$X_{20} = 5R$$

$$a = \frac{3}{5} = 0.6; R'_2 = R_2 a^2$$

$$= R \times 0.6^2$$

$$= 0.36 R$$

$$X'_2 = 0.6^2 \times 5R = 1.8R$$

$$s_{fl} = 0.03$$

Assuming the mechanical losses are neglected

$$P_{im} = 7.5 \text{ kW}$$

$$P_{ag} = \frac{P_{im}}{1-s} = \frac{7.5 \times 10^3}{1-0.03}$$

$$= 7.731 \text{ kW}$$

$$P_{ag} = 3 \frac{V_1^2}{\left[ \left( R + \frac{R'_2}{s} \right)^2 + [X_1 + X'_2]^2 \right]} \times \frac{R'_2}{s}$$

$$= \frac{3 \times 254.03^2}{\left[ \left( R + \frac{0.36R}{0.03} \right)^2 + [5R + 1.8R]^2 \right]} \times \frac{0.36R}{0.03}$$

$$= 7.731 \times 10^3$$

Solving for R

$$R = 1.4 \Omega$$

$$I_{fl} = \frac{V_1}{\sqrt{\left( R_1 + \frac{R'_2}{s} \right)^2 + (X_1 + X'_2)^2}}$$

$$= \frac{254.03}{\sqrt{\left( 1.4 + \frac{0.36 \times 1.4}{0.03} \right)^2 + [5R + 1.8R]^2}}$$

$$= \frac{254.03}{\sqrt{\left( 1.4 + \frac{0.36 \times 1.4}{0.03} \right)^2 + (6.8 \times 1.4)^2}} = 12.36$$

Similarly

$$I_{st} = \frac{254.03}{\sqrt{\left( 14 + \frac{0.36 \times 1.4}{1} \right)^2 + (6 \times 1.4)^2}} = 26.16 \text{ A}$$

$$\frac{I_{st}}{I_{fl}} = \frac{26.16}{12.36} \leq 2.116$$

Percentage increase should be zero.

**1[c] In a short circuit test on a 3-pole, 110 kV circuit breaker, power factor of the fault was 0.4, the recovery voltage was 0.95 times full line value. The breaking current was symmetrical. The frequency of oscillation of restriking voltage was 15,000 cycles/sec. Estimate the average rate of rise of restriking voltage. The neutral is grounded and fault involves earth. [12M]**

**Solution:**

$$V_L = 110 \text{ kV}$$

$$V_{ph(rms)} = \frac{110}{\sqrt{3}} \text{ kV}$$

$$V_m = \sqrt{2} \times \frac{110}{\sqrt{3}} \text{ kV} = 89.814 \text{ kV}$$

$$\cos\phi = 0.4 \Rightarrow \sin\phi = 0.917$$

$$K_1 = 0.95; K_2 = 1$$

$$f = 15000 \text{ cycles/sec} = 15000 \text{ Hz} = \frac{1}{2\pi\sqrt{LC}}$$

$$\begin{aligned} RRRV_{avg} &= \frac{2 \cdot ARV}{\pi\sqrt{LC}} \times \frac{2}{2} \\ &= \frac{4 \times K_1 \cdot K_2 \cdot V_m \sin\phi}{2\pi\sqrt{LC}} \\ &= 4 \times 0.95 \times (1) \times 89.814 \times 0.917 \times 10^3 \times 15000 \\ &= 4.69 \text{ kV}/\mu\text{sec} \end{aligned}$$

**1[d] The standstill impedances of the inner and outer cages of a double cage 3- $\phi$  induction motor rotor are given as  $Z_{ic} = (0.1 + j0.5) \Omega$  and  $Z_{oc} = (0.05 + j0.1) \Omega$  respectively. Assuming the stator impedance to be negligible, determine the approximate ratio of the torques produced by the output cage ( $T_{oc}$ ) to the torque produced by the inner cage ( $T_{ic}$ ) at a slip of  $s = 0.05$ ? Also determine the net torque developed as a function of  $T_{oc}$  and comment on performance as compared to single cage motor. [12M]**

**Solution:**

Given

$$Z_{ic} = 0.01 + j0.5 \Omega$$

$$R_{ic} = 0.01 \Omega; X_{ic} = 0.5 \Omega$$

$$Z_{oc} = 0.05 + j0.1 \Omega$$

$$R_{oc} = 0.05; X_{oc} = 0.1 \Omega$$

Neglected, stator impedance

$$T_{em} = K' \frac{V_1^2 \times \frac{R'_2}{2}}{\left(\frac{R'_2}{s}\right)^2 + X_{oc}^2}$$

$$\frac{T_{oc}}{T_{ic}} = \frac{\frac{R_{oc}/s}{\left(\frac{R_{oc}}{s}\right)^2 + X_{oc}^2}}{\frac{R_{ic}}{\left(\frac{R_{ic}}{s}\right)^2 + X_{ic}^2}}$$

$$\frac{T_{oc}}{T_{ic}} = \frac{\frac{0.05}{0.05}}{\frac{0.01}{0.05}} = 1.436$$

Net torque

$$\begin{aligned} T_{net} &= T_{ic} + T_{oc} \\ &= T_{ic} + 1.436 T_{ic} \\ &= 2.436 T_{ic} \end{aligned}$$

Because of high resistance of output cage starting torque is high, because of low resistance of inner cage the running performance is good.



**OFFLINE**



**ACE<sup>®</sup>**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs



# **Classroom Coaching** **@ Kothapet & Abids, Hyd**

**GATE | PSUs -2026**

**06<sup>th</sup> Aug 2025**

**21<sup>st</sup> Aug 2025**

**Achievers Batches TARGET - 2027**

**06<sup>th</sup> Aug 2025**

**03<sup>rd</sup> Sep 2025**

**Foundation Batch TARGET - 2028**

**03<sup>rd</sup> Sep 2025**

**SPECIAL CONCESSIONS**

**Available for IITs/NITs/IIITs & Govt. College Students**

**50% Concession for ACE old students**



**Kothapet Address: 2<sup>nd</sup> Floor, BAHETI SPECTRUM, Beside: Kinara Grand,  
Near Victoria Memorial Metro Station, Metro Pillar No: CHPNP-32, 33,  
Margadarshi Colony, Kothapet, Hyderabad, Telangana – 500035.**



**Abids Address: #3<sup>rd</sup> Floor, Suryalok Complex, Rosary Convent School Road,  
Gun Foundry, Basheer Bagh, Hyderabad, Telangana – 500001.**

**1[e] A 10 MVA, 13.8 kV turbo-generator having  $X_d'' = X_2 = 15\%$  and  $X_0 = 5\%$  is about to be connected to power system. The generator has current limiting reactor of  $0.7 \Omega$  in the neutral. Before the generator is connected to the system, its voltage is adjusted to 13.2 kV. When a double line to ground fault develops at terminal 'b' and 'c', find the initial symmetrical rms currents in the ground and in line 'b'.**

**[12M]**

**Solution:**

$$S_{B(3-\phi)} = 10 \text{ MVA}$$

$$V_{BL} = 13.8 \text{ kV}$$

$$X_d'' = X_1 = X_2 = 0.15$$


$$X_0 = 0.05$$

$$X_n = 0.7 \Omega$$

$$V_{PF} = 13.2 \text{ kV}$$

$$X_{npu} = 0.7 \times \frac{10 \times 10^6}{(13.8 \times 10^3)^2}$$

$$= 0.037 \text{ PU}$$

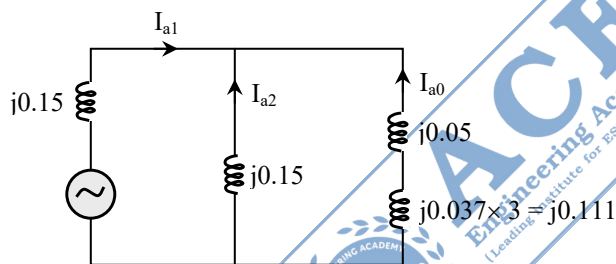

$$I_{a1} = \frac{V_{PF}}{j(X_1 + (X_2 \parallel (X_0 + 3X_n)))}$$

$$V_{PF} = \frac{13.2}{13.8} = 0.957 \text{ PU}$$

$$\therefore I_{a1} = \frac{0.957}{j(0.15 + (0.15 \parallel (0.05 + 0.111)))}$$

$$= \frac{-j0.957}{0.15 + 0.078}$$

$$= -j4.197 \text{ PU}$$

$$\therefore I_{a0} = -I_{a1} \times \frac{j0.15}{j0.15 + j0.05 + j0.111}$$

$$= +j4.197 \times \frac{0.15}{0.311}$$

$$I_{a0} = j2.02 \text{ PU}$$

$$I_{a2} = j2.177$$

$$\therefore I_f = 3 \cdot I_{a0} = 3 \times j2.02 = j6.06 \text{ PU}$$

$$\begin{aligned} I_b &= I_{b0} + I_{b1} + I_{b2} = I_{a0} + K^2 \cdot I_{a1} + K \cdot I_{a2} \\ &= j2.02 + 1 \angle -120^\circ \times 4.197 \angle -90^\circ + 1 \angle 120^\circ \times 2.177 \angle 90^\circ \\ &= -5.52 + j3.03 = 6.29 \angle 151.23 \text{ PU} \end{aligned}$$

**2[a] A 15 km long 3-phase overhead line delivers 5 MW at 11 kV at a power factor of 0.8 lagging. Line loss is 12% of the power delivered. Line inductance is 1.1 mH per km per phase.**

**Calculate:**

**(i) Sending end voltage and voltage regulation**

**[15M]**

**(ii) Power factor of the load to make voltage regulation zero.**

**[5M]**

**Solution:**

$$\ell = 15 \text{ km}$$

$$P_D = 5 \text{ MW}$$


$$V_{RL} = 11 \text{ kV}$$

$$\cos \phi = 0.8$$

$$P_{\text{Loss}} = 0.12 \times 5 \text{ MW}$$

$$= 0.6 \text{ MW}$$

$$L = 1.1 \text{ mH/km}$$

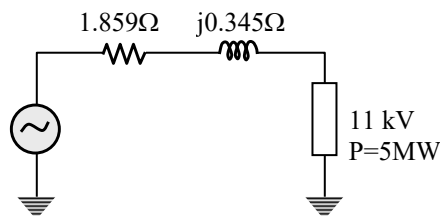

$$P_{3-\phi} = \sqrt{3} \cdot V_{RL} \cdot I_{RL} \cdot \cos \phi$$

$$\therefore I_{RL} = I_{Rph} = \frac{5 \times 10^6}{\sqrt{3} \times 11 \times 10^3 \times 0.8} = 328 \text{ A}$$

$$P_{\text{Loss}(3-\phi)} = 3 \cdot I_R^2 \cdot R$$

$$\frac{0.6 \times 10^6}{3 \times (32P)^2} = R$$

$$\therefore R = 1.859 \Omega$$

$$\therefore Z = R + jX_L$$

$$= 1.859 + j0.345 \Omega$$

$$= 1.89 \angle 10.51^\circ \Omega$$

$$(i) V_{S_{ph}} = V_{R_{ph}} + I_R \cdot Z$$

$$= \frac{11}{\sqrt{3}} \angle 0^\circ \text{ kV} + 328 \angle -36.86^\circ \times (1.89 \angle 10.51^\circ)$$

$$= 6906.36 - j275.15$$

$$= 6.911 \angle -2.28^\circ \text{ kV}$$

$$\therefore V_{SL} = \sqrt{3} \times 6.911$$

$$= 11.97 \text{ kV}$$

$$\% V_{\text{reg}} = \frac{I_R \cdot Z \cos(\theta - \phi_R)}{V_R} \times 100$$

$$= \frac{328 \times 1.89 \cos(10.51^\circ - 36.86^\circ)}{\left(\frac{11}{\sqrt{3}}\right) \times 10^3} \times 100$$

$$= 8.74\%$$

(ii) To have zero voltage regulation

$$\theta + \phi_R = 90^\circ$$

$$\phi_R = 90 - \theta = 90 - 10.51$$

$$= 79.49^\circ$$

$$\therefore \cos \phi = 0.182$$

**2[b] A 2200/220 V, single phase transformer has maximum possible voltage regulation of 6% and it occurs at a power factor of 0.3 lag. Find the load voltage at full load at a power factor of 0.8 lead. [20M]**

**Solution:**

$$\text{Given a 1-}\phi, \frac{2200\text{V}}{220\text{V}}$$



Maximum voltage Regulation = 6% = %Z

At a pf of  $\cos\phi = 0.3$

$$\cos\phi = \frac{\%R}{\%Z} = 0.3$$

$$\Rightarrow \%R = 1.8\%$$


$$\begin{aligned}\%X &= \sqrt{\%Z^2 - \%R^2} \\ &= \sqrt{6^2 - 1.8^2}\end{aligned}$$

$$\%X = 5.72\%$$

%Regulation at 0.8 pf lead

$$\begin{aligned}\% \text{ Regulation} &= (\%R) \cos\phi - (\%X) \sin\phi \\ &= 1.8 \times 0.8 - 5.72 \times 0.6 \\ &= -1.99\%\end{aligned}$$

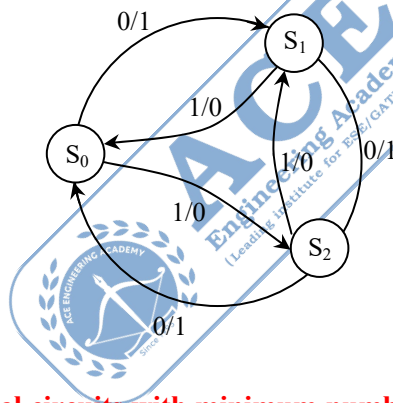2[c] (i) For the state diagram shown below, design the circuit using D-flip flops. Assume  $S_0 : 00$ ,  $S_1 : 10$  and  $S_2 : 01$ .




Realize the signal circuits with minimum number of NAND gates (More than two input NAND gates are allowed). [10M]

**Solution:**

$S_0 : 00$

$S_1 : 10$

$S_2 : 01$

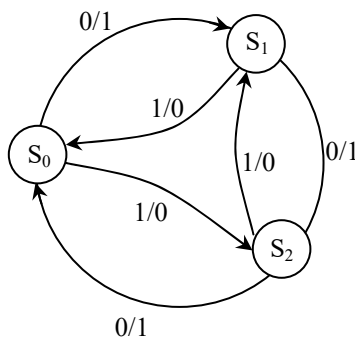

PS	PI	NS	O/P
S <sub>0</sub>	0	S <sub>1</sub>	1
S <sub>0</sub>	1	S <sub>2</sub>	0
S <sub>1</sub>	0	S <sub>2</sub>	1
S <sub>1</sub>	1	S <sub>0</sub>	0
S <sub>2</sub>	0	S <sub>0</sub>	1
S <sub>2</sub>	1	S <sub>1</sub>	0

	PS $\theta_1\theta_2$	PI X	NS $\theta_1\theta_0$	FF i/ps $D_1D_0$	O/P Z
0	00	0	10	10	1
1	00	1	01	01	0
4	10	0	01	01	1
5	10	1	00	00	0
2	01	0	00	00	1
3	01	1	10	10	0

$$D_1 = \sum m(0, 3)$$

$$D_0 = \sum m(1, 4)$$

$$Z = \sum m(0, 2, 4)$$

$\theta_1 \backslash \theta_0 x$	00	01	11	10
0	①		①	
1				

$$D_1 = \bar{\theta}_1 \bar{\theta}_0 \bar{x} + \bar{\theta}_1 \theta_0 x$$

$$= \bar{\theta}_1 (\theta_0 \odot x)$$

$\theta_1 \backslash \theta_0 x$	00	01	11	10
0		①		
1	①			


$$D_0 = \bar{\theta}_1 \bar{\theta}_0 X + \theta_1 \bar{\theta}_0 \bar{X}$$

$$= \bar{\theta}_0 (\theta_1 \oplus \mathbf{x})$$

$\theta_0 \backslash \theta_1$	00	01	11	10
0	1			1
1	1			

$$Z = \bar{\theta}_1 \bar{x} + \bar{\theta}_0 \bar{x}$$
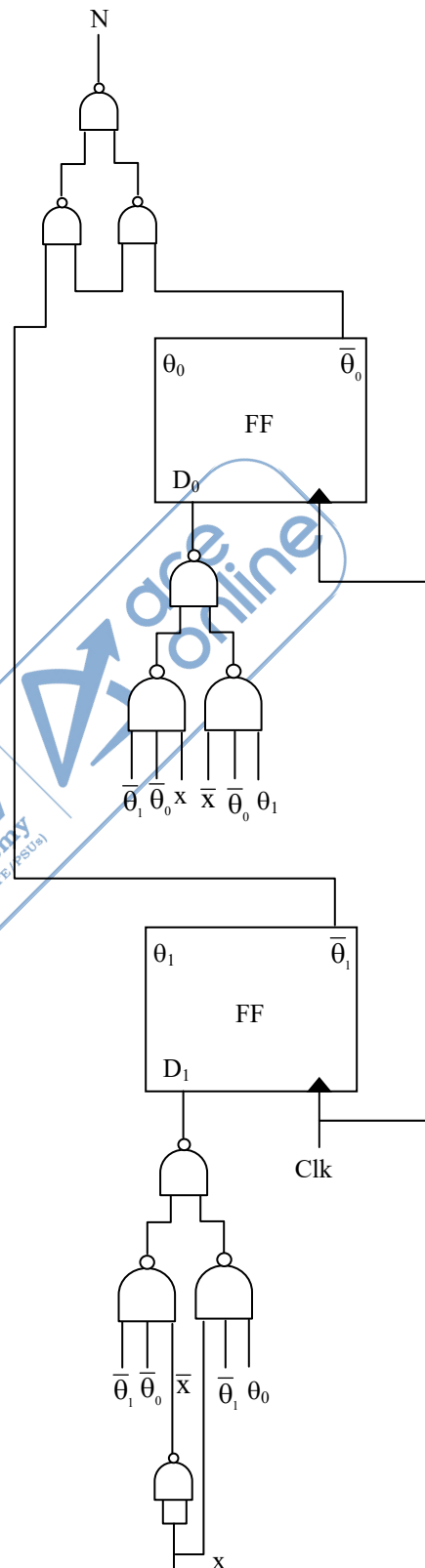
$$= \bar{\mathbf{x}}(\bar{\boldsymbol{\theta}}_1 + \bar{\boldsymbol{\theta}}_0)$$



**ONLINE**



## Upcoming Live Batches

### GATE | PSUs -2026

**06<sup>th</sup> Aug 2025**

**21<sup>st</sup> Aug 2025**

### Achievers Batches TARGET - 2027

**06<sup>th</sup> Aug 2025**

**21<sup>st</sup> Aug 2025**

### Foundation Batch TARGET - 2028

**03<sup>rd</sup> Sep 2025**



**Experienced  
Faculty**



**Ask an  
Expert**



**Live Doubt  
Clearance**



**Online  
Test Series**




**Full Set of  
Study Material**

- Freedom of Unlimited Access
- No-Cost EMI Available
- Backup Recorded Sessions
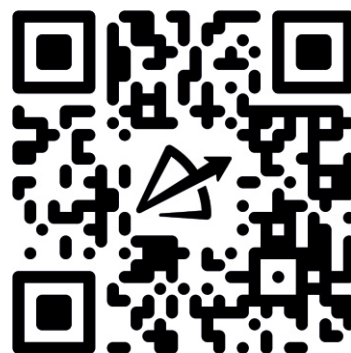
### SPECIAL CONCESSIONS

**Available for: IITs/NITs/IIITs & Govt. College Students**  
**25% Off for ACE old students**



Scan QR Code for more details

**2[c] (ii) An angle modulated signal is given as**

$$X(t) = 20 \cos(12000 t) \text{ for } |t| \leq 1$$

**If the carrier wave frequency  $\omega_c = 10000$  rad/sec, determine**

**(A) Modulation index  $m(t)$ , if  $X(t)$  were a PM (phase modulated) signal with**

$$K_p = 500 \text{ over } |t| \leq 1.$$

**(B) Modulation index  $m(t)$ , if  $X(t)$  were a frequency modulated (FM) signal with**

$$K_f = 500 \text{ over } |t| \leq 1.$$

**[10M]**

**Solution:**

$$X(t) = 20 \cos(1200t), |t| \leq 1 \text{ (or) } -1 \leq t \leq 1$$

$$\omega_c = 10000 \text{ (rad/sec)}$$

**NOTE:**

This might be the message signal

$$A_m \text{ (or) } |m(t)|_{\max} = 20 \text{ (volts)}$$

$$(A) \beta_{PM} = \Delta\phi_{\max} = K_p |m(t)|_{\max}$$

$$= 500 \times 20$$

$$= 10000$$

$$(B) \beta_{FM} = \frac{\Delta f_{\max}}{f_{\max}} = \frac{K_f |m(t)|_{\max}}{f_{\max}}$$

$$= \frac{500 \times 20 \times 2\pi}{1200}$$

$$= \frac{5 \times 20 \times 2\pi}{12} = \frac{200\pi}{12} = 52.35$$

$$f_{\max} = \frac{1200}{2\pi} \text{ (Hz)}$$

**3[a] Give the circuit diagram of a second order highpass Butterworth filter circuit using op-amp. Evaluate the component values, such that the filter has lower cutoff frequency of 5 kHz and a pass band gain  $A_F = 2$ . Also give expression for voltage gain magnitude and sketch its frequency response. [20M]**

**Solution:**

The normalized butterworth polynomial for second order is

$$S_n^2 + 1.414 S_n + 1$$


This is of the form

$$S_n^2 + (3 - A_0) S_n + 1 \text{ of the Salen - key filter drawn below}$$

$$\therefore 3 - A_0 = 1.414$$

$$\rightarrow A_0 = 1.586$$

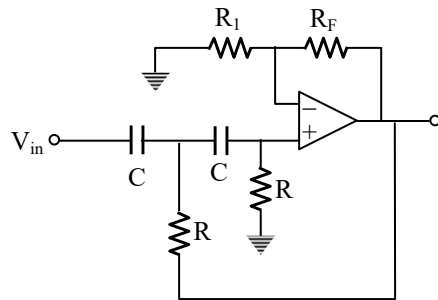Second order high pass Butterworth filter



Given cutoff frequency  $f_c = \frac{1}{2\pi RC} = 5 \text{ kHz}$

Let  $C = 0.1 \mu\text{F} \rightarrow R = \frac{1}{2\pi(5\text{K})(0.1\mu)}$   
 $R = 318.309 \Omega$

Gain for Butterworth filter = 1.586

$\therefore 1.586 = 1 + \frac{R_F}{R_1}$

Let  $R_1 = 10 \text{ k}\Omega \rightarrow R_F = 5.86 \text{ k}\Omega$

**3[b] A 50 Hz alternator is supplying 40% of the power that it is capable of delivering through a transmission line to an infinite bus. A fault occurs that increases the reactances between the generator and the infinite bus to 600% of the value before the fault. When the fault is isolated, the maximum power that can be delivered is 80% of the original maximum value, find critical clearing angle. [20M]**

**Solution:**

$P_s = P_{e1} = 0.4 P_{\max_1}$

So,  $\sin^{-1}\left(\frac{P_s}{P_{\max_1}}\right) = \sin^{-1}(0.4) = 23.57 = 0.4113 \text{ rad}$

$P_{\max_2} = \frac{EV}{X_{2\text{equ}}} = \frac{EV}{6 \times X_{1\text{equ}}}$

$P_{\max_2} = 0.167 \times P_{\max_1}$

$P_{\max_3} = 0.8 P_{\max_1} = 0.8 \times \frac{P_s}{0.4}$

$\therefore \frac{P_s}{P_{\max_2}} = \frac{0.4}{0.8} = 0.5$

$$\therefore S_{\max} = 180 - \sin^{-1} \left( \frac{P_s}{P_{\max_3}} \right) = 180 - \sin^{-1}(0.5)$$

$$= 150$$

$$= 2.618 \text{ rad}$$

$$\therefore \delta_C = \cos^{-1} \left[ \frac{P_s (\delta_{\max} - \delta_0) + P_{\max_3} \cos \delta_{\max} - P_{\max_2} \cos \delta_0}{P_{\max_3} - P_{\max_2}} \right]$$

$$= \cos^{-1} \left[ \frac{0.4P_{\max_1} (2.618 - 0.4113) + 0.8P_{\max_1} \times \cos(150) - 0.167P_{\max_1} \cos(23.57)}{0.8P_{\max_1} - 0.167P_{\max_1}} \right]$$

$$= \cos^{-1} \left[ \frac{0.4 \times 2.2067 + 0.8 \times (-0.866) - 0.167 \times 0.917}{0.8 - 0.167} \right]$$

$$= \cos^{-1} (0.0580)$$

$$= 86.67$$

**3[c] A 240 V D.C. series motor takes 40 A when giving its rated output at 1500 rpm. Its resistance is 0.3Ω.**

**Calculate the value of resistance that must be added to obtain the rated torque**

**(i) during starting and**

**(ii) at 1000 rpm**

**[20M]**

**Solution:**

Given 240 V,


$I_{a1} = 40 \text{ A}$  at rated output

$N_1 = 1500 \text{ rpm}$

$R = 0.3 \Omega$

$E_{b1} = 240 - 40(0.3)$

$= 228 \text{ V}$

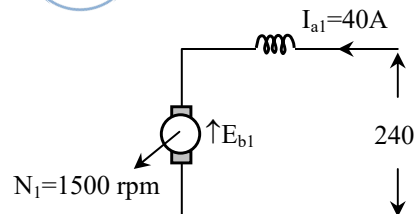

(i) For rated torque  $\Rightarrow I_{a2} = 40 \text{ A}$

$$\text{At starting} \Rightarrow I_a = \frac{V - 0}{R + R_e}$$

**OFFLINE**



# Classroom Coaching

- Engaging in classroom coaching provides a transformative and engaging learning experience that deeply encourages interactive student-faculty relationships within an ideal educational environment.
- By participating in our extensive classroom sessions, students not only acquire knowledge but also develop crucial skills and enhanced confidence levels that are pivotal for their success.
- ACE provides classroom coaching by experienced educators to support increased competition and participation in competitive exams.



→ **Smart Classrooms**

→ **Library/Reading Rooms**

→ **Calm Study Environment**

→ **Near to Metro Station**

→ **Centralized AC Classrooms**

→ **No-Cost EMI available**



H.O. @ Abids # 3<sup>rd</sup> Floor, Suryalok Complex, Rosary Convent School Road, Gun Foundry, Basheer Bagh, Hyderabad, Telangana – 500001.



B.O. @ Kothapet # 2<sup>nd</sup> floor, BAHETI SPECTRUM, Beside: Kinara Grand, Near Victoria Memorial Metro Station, Pillar No: CHPNP-32, 33, Kothapet, Hyderabad, Telangana.



$$\Rightarrow 40 = \frac{240}{0.3 + R_e}$$

$$\Rightarrow R_e = 5.7 \Omega$$

(ii) At rated torque,  $I_{a2} = I_{a1} = 40 \text{ A}$

For  $N_2 = 1000 \text{ rpm} \Rightarrow R_e = ?$

$$E_{b2} = 240 - 40(R + R_e)$$

$$\therefore \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

$$\Rightarrow \frac{1000}{1500} = \frac{240 - 40(0.3 + R_e)}{228} \times 1$$

$$\Rightarrow R_e = 1.9 \Omega$$


**4[a] Figure shows a two bus system. If a power of 125 MW is transferred from plant 1 to load, a power loss of 15.625 MW occurs. Find generation schedule and load demand if cost of received power is ₹24 per MWh. The incremental production costs are**

$$\frac{dF_1}{dP_1} = 0.025 P_1 + 15$$

$$\frac{dF_2}{dP_2} = 0.05 P_2 + 20$$

**Assume penalty factor of 2nd generator = 1.**

**[20M]**

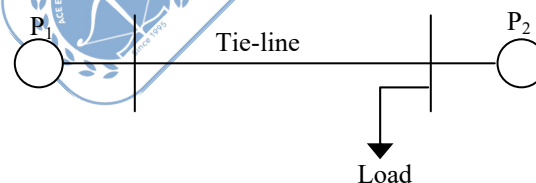

**Solution:**

$$P_1 = 125 \text{ MW}$$

$$P_L = 15.625 \text{ MW}$$

$$P_L = B_{11} \cdot P_G^2$$

$$15.625 = B_{11} \times (125)^2$$

$$\therefore B_{11} = 0.001 \text{ MW}^{-1}$$

Penalty factor of plant-1

$$L_1 = \frac{1}{1 - \frac{\partial P_2}{\partial P_{G_1}}} ; \frac{\partial P_L}{\partial P_{G_1}} = 2.B_{11}.P_{G_1}$$

$$= \frac{1}{1 - 0.25} = 2 \times 0.001 \times 125$$

$$= 1.33 = 0.25$$

$$L_2 I_{C2} = 24$$

$$0.05 P_2 + 20 = 24$$

$$0.05 P_2 = 4$$

$$P_2 = \frac{4}{0.05} = 80 \text{ MW}$$

$$\therefore \text{Total power received} = P_1 + P_2 - P_L$$

$$= 125 + 80 - 15.625$$

$$= 189.375 \text{ MW}$$


**4[b] (i) Give the block diagram of AM Receiver and FM Receiver. Also explain each block. [10M]**

**Solution:**

**AM Receivers:**


- (1) Tuned radio frequency (TRF) Receiver
- (2) Superheterodyne Receiver

**TRF Receiver:**

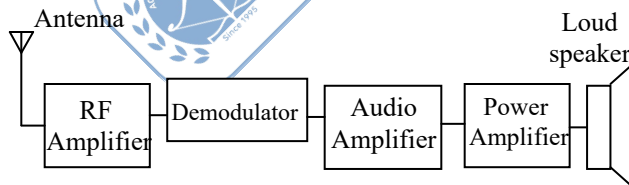


RF amplifier must be a low noise amplifier.

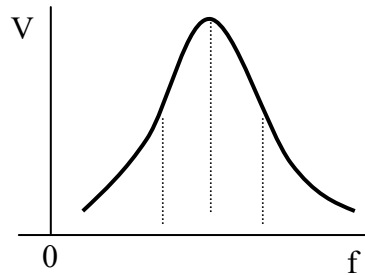RF amplifier itself acts as a BPF. RF amplifier itself consists of a tuned circuit. Thus it is called tuned RF amplifier.



By tuning arrangement we are making the resonant frequency of the tuned circuit equal to the carrier frequency of the required channel.

### Superheterodyne AM Receiver:

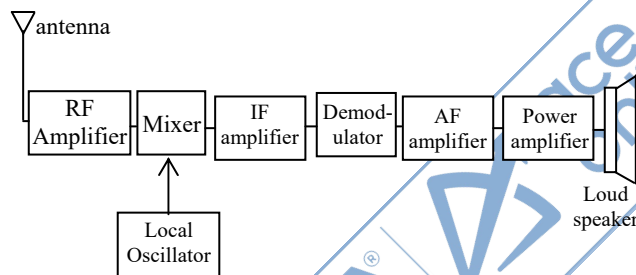


In the superheterodyne receiver the signal voltage is combined with the local oscillator voltage and converted into a signal of lower fixed frequency. The signal at this intermediate frequency contains the same modulation as the original carrier and is now amplified and detected to reproduce the original information. A constant frequency difference is maintained between the local oscillator and the RF circuits.

In mixer, down conversion is done with respect to the tuned circuit. Tuning means changing the local oscillator frequency. Mixer will change the carrier frequency from  $f_s$  to  $f_{IF}$ .

AM range  $\rightarrow$  550 kHz – 1650 kHz

IF  $\rightarrow$  455 kHz

**FM receiver block diagram :**

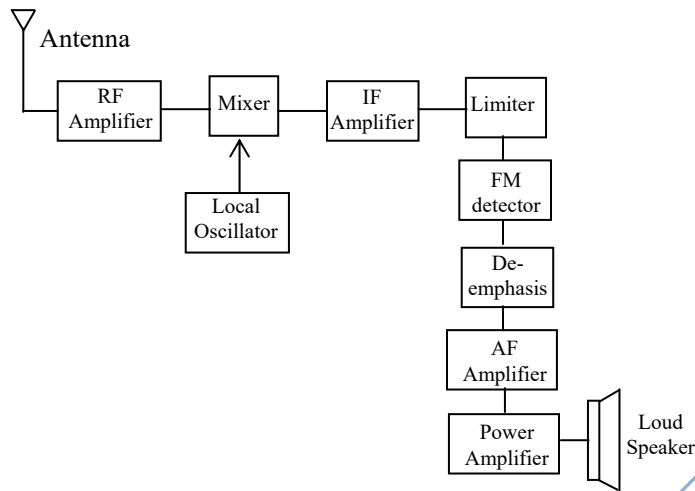


FM range → 88 MHz to 108 MHz

IF → 10.7 MHz

**Image frequency:**

$$f_{si} = f_s + 2 \text{ IF}$$

**Image (Frequency) Rejection Ratio:**

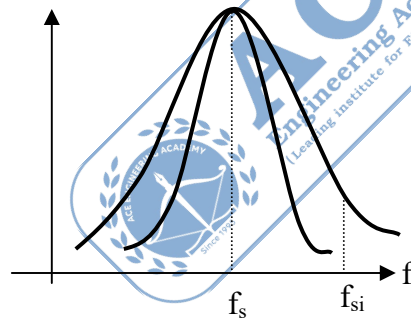

$$\text{IRR} = \frac{\text{Gain at } f_s}{\text{Gain at } f_{si}}$$

By increasing the Intermediate frequency, IRR can be increased. By increasing the bandwidth, the gain at  $f_{si}$  can be decreased so that IRR increases.

$$\text{IRR} \propto \frac{1}{\text{B.W}}$$

A minimum of 10 kHz bandwidth should be maintained at the first tuned circuit that is placed before mixer.

$$IRR = \sqrt{1 + Q^2 \rho^2}$$

$$\text{where } \rho = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}}$$

IRR should be as high as possible. If two tuned circuits are cascaded then the overall

$$IRR = \sqrt{1 + Q_1^2 \rho^2} \cdot \sqrt{1 + Q_2^2 \rho^2}$$

**4[b] (ii) What is the largest value of output voltage from an 8-bit DAC that produces 2.0 V for digital Input of 01110010 ? [10M]**

**Solution:**

For a digital input 01110010,

the output voltage is 2 V

$$V_0 = \Delta(\text{decimal equivalent of digital})$$

$$2V = \Delta(0 \times 2^7 + 1 \times 2^6 + 1 \times 2^5 + 1 \times 2^4 + 0 + 0 + 1 \times 2^1 + 0)$$

$$2V = \Delta(0 + 64 + 32 + 16 + 2)$$


$$2V = \Delta(114)$$

$$\Delta = \frac{2V}{114}$$

Then the full scale voltage is

$$V_0 = \Delta(255)$$
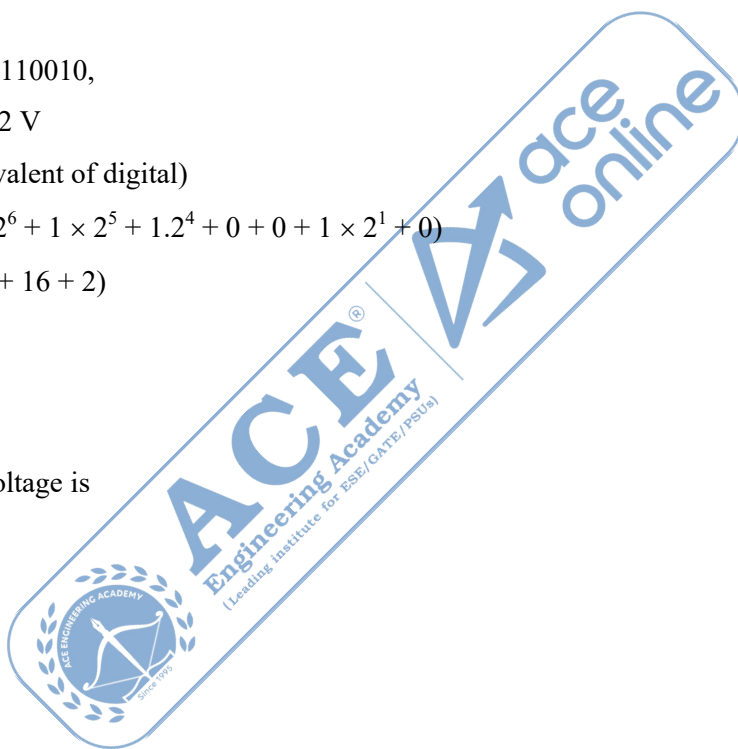
$$V_0 = \frac{2V}{114}(255) = 4.4737 \text{ V}$$



**4[c] A 3-phase, 6-pole, 500 kVA, 6600 V, 50 Hz star-connected synchronous motor having synchronous impedance of  $j 80 \Omega$  per phase operates at unity power factor at rated conditions.**

- (i) Determine the mechanical torque driving capability for this motor at rated conditions, neglecting all mechanical losses.**
- (ii) At this rated torque, what are the required deviations from rated armature current and excitation (in terms of  $E_f \angle \delta$ ) to produce a maximum torque of 1.26 times to the maximum rated torque for a leading power factor operation of motor.**
- (iii) Determine the value of the leading power factor for motor operation as stated in (ii) above.**

**[20M]**

**Solution:**

A 3-phase, 6-pole, 500 kVA, 6600 V, 50 Hz, Y-connected synchronous motor,  $X_s = 80 \Omega$ , operate at UPF at rated conditions.

$$V_L = 6600 \Rightarrow V_{ph} = \frac{6600}{\sqrt{3}} = 3810.5 \text{ V}$$

$$I_L = \frac{\text{kVA}}{\sqrt{3}V_L} = \frac{500 \times 10^3}{\sqrt{3} \times 6600} = 43.74 \text{ A} = I_{aph} \quad (\because \text{Y-connection})$$

At UPF, rated condition

$$P = \text{kVA} \times \text{PF} = 500 \times 1 = 500 \text{ kW}$$

(i) Mechanical torque driving capacity for this motor at rated condition

$$T = \frac{P}{W} = \frac{500 \times 10^3}{2\pi \frac{N}{60}}; \quad N = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$= \frac{500 \times 10^3}{2\pi \times \frac{1000}{60}} = 4774.64 \text{ Nm}$$

$$\therefore T = 4774.64 \text{ Nm} = 4.774 \text{ kNm}$$

(ii) At rated condition, the excitation emf or back emf

$$E = V - I_a Z_s$$

$$= 3810.5 \angle 0^\circ - 43.74 \angle 0^\circ \times 80 \angle 90^\circ$$

$$= 3810.5 \angle 0^\circ - 3500 \angle 90^\circ$$

$$= 3810.5 - j3500$$

$$E = 5173.9 \angle -42.56^\circ$$

The required deviation from rated condition of  $E \angle \delta$  and armature current  $I_a$  to produce maximum torque of 1.26 times maximum rated torque as below

At maximum torque  $\delta = 90^\circ$

$$T_2 = 1.26 T_1$$

$$\frac{P_2}{W} = \frac{1.26 P_1}{W}$$

$$\frac{E_2 V}{X_s W} \sin 90^\circ = \frac{1.26 E_1 V}{X_s W} \sin 90^\circ$$

$$\Rightarrow E_2 = 1.26 E_1 = 1.26 \times 5173.9 = 6519.14 \text{ V}$$

$\therefore$  The deviation of induced emf from rated condition

$$E_1 = 5173.9 \text{ to } E_2 = 6519.14 \text{ V}$$

For leading power factor  $E_2 \cos \delta_2 > V$

$$\therefore 6519.14 \cos \delta_2 > 3810.5$$

$$\therefore \cos \delta_2 > \frac{3810.5}{6519.14}$$

$$\therefore \cos \delta_2 > 0.584$$

$$\delta_2 < 54.23^\circ$$

$$\therefore \text{The deviation from rated condition } \delta_1 = 42.56 \text{ to } \delta_2 < 54.23^\circ$$

At maximum torque, power drop max

$$\therefore P_2 = 1.26 P_1$$

$$V I_{a2} \cos \phi_2 = 1.26 V I_{a1} \cos \phi_1 \quad [\text{PF is UPF}]$$

$$I_{a2} \times 1 = 1.26 \times 43.74 = 55.1 \text{ A}$$

$$\therefore I_{a2} = 55.1 \text{ A}$$

The deviation of current from rated condition

$$I_{a1} = 43.74 \text{ A to } I_{a2} = 55.1 \text{ A}$$

(iii) In part let  $E_2 = 6519.14 \text{ V}$

$$\delta_2 < 54.23^\circ, \text{ Let } \delta_2 = 30^\circ$$

$$\begin{aligned} \text{Then } I_{a2} &= \frac{V \angle 0 - E_2 \angle -\delta_2}{X_s \angle 0} = \frac{3810.5 \angle 0 - 6519.14 \angle -30^\circ}{80 \angle 90^\circ} \\ &= \frac{3810.5 - (6519.14 \cos 30 - j6519.14 \sin 30)}{80 \angle 90} \\ &= \frac{3810.5 - (5645.14 - j3259.57)}{80 \angle 90} \\ &= \frac{-1834.64 + j3259.57}{80 \angle 90} \\ &= \frac{3740.41 \angle -60.62^\circ}{80 \angle 90} \end{aligned}$$

$$I_{a2} = 46.75 \angle 29.38^\circ$$

$$\therefore \text{Power factor} = \cos \phi = \cos 29.38$$

$$= 0.871 \text{ lead}$$



## ACE Interview Guidance Program

### Empowering Job Seekers to Succeed

- Job seekers confront a variety of challenges on their path to securing a job. Our ACE Interview Guidance programme has been carefully designed to provide thorough assistance in overcoming these challenges.
- With a team of seasoned experts at the helm, our focus is on empowering individuals with the intricate skills and extensive knowledge required to fully shine during interviews.
- Whether it's perfecting your presentation strategies or fine-tuning your overall interview skills, we are completely committed to improving your prospects of securing desired positions.
- ACE conducts comprehensive mock interviews with expert panel members, both in person and virtually. These simulations are designed to thoroughly prepare individuals for college admissions or job interviews.

**# ACE YOUR INTERVIEWS WITH OUR EXPERT GUIDANCE!**



Our Social Links



aceonlineprep



aceonlineprep



aceonline



@aceengacademy




aceacademyindia\_official




## SECTION – B

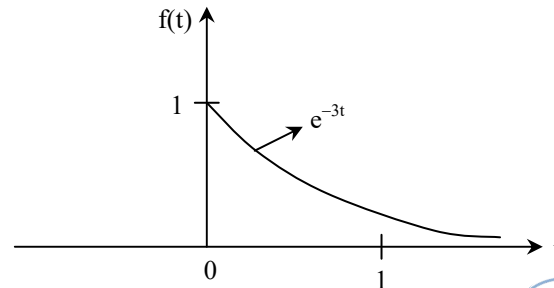**5[a] An exponential function  $f(t) = e^{-3t} u(t)$  as shown in the following figure is delayed by 1 sec. Sketch and describe mathematically the delayed function. Also repeat the same if  $f(t)$  is advanced by 1 second. [12M]**




**Solution:**

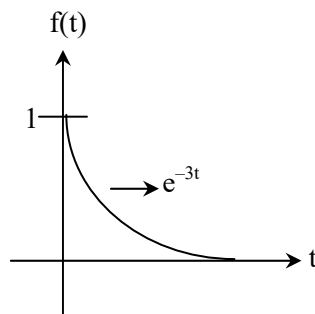


The delayed function delayed by 1 sec is
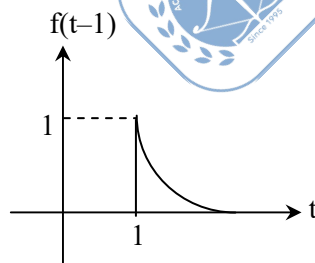
$$\begin{aligned} f(t-1) &= e^{-3(t-1)} & t > 1 \\ &= 0 & t < 1 \end{aligned}$$




The advanced function advanced by 1 sec is
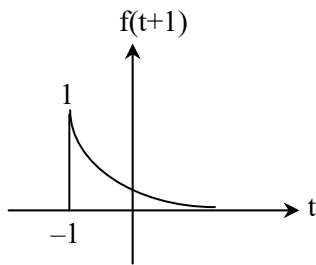
$$\begin{aligned} f(t+1) &= e^{-3(t+1)} & t > -1 \\ &= 0 & t < -1 \end{aligned}$$



5[b] A step-down DC-DC convertor is feeding an RLE load with a freewheeling diode across the load. Assuming a ripple free load current, derive the expression for maximum duty cycle in terms of supply voltage  $V_s$  and back emf of the load  $E$  for which the RMS current through the freewheeling diode has maximum value. [12M]

**Solution:**

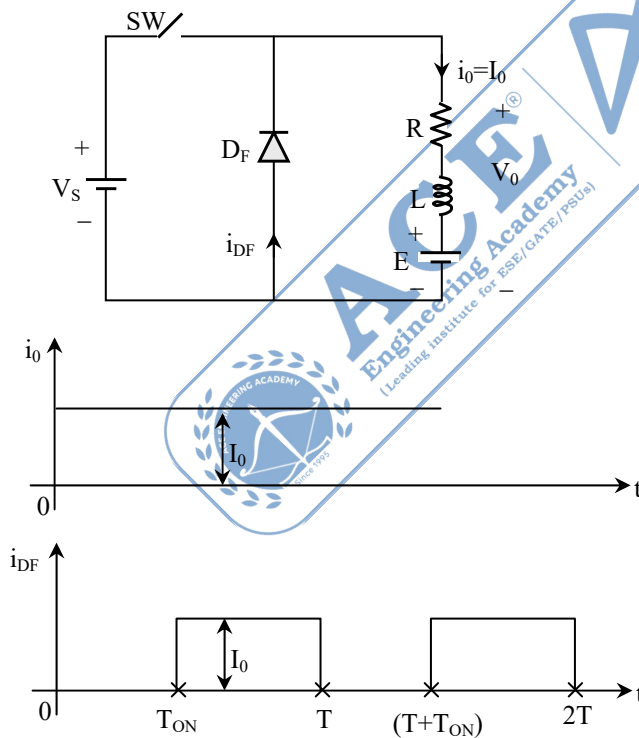

$$i_{DF \text{ RMS}} = \left[ \frac{1}{T} \int_{T_{ON}}^T I_0^2 dt \right]^{\frac{1}{2}}$$

$$= I_0 \left[ \frac{T - T_{ON}}{T} \right]^{\frac{1}{2}}$$

$$i_{DF\text{ RMS}} = \sqrt{1-D} I_0 \dots\dots\dots (1)$$

$$I_0 = \frac{V_0 - E}{R}$$

$$I_0 = \frac{DV_s - E}{R}$$

Put “ $I_0$ ” in equation (1)

$$i_{DF\text{ RMS}} = \sqrt{(1-D)} \left[ \frac{DV_s - E}{R} \right]$$

Using maximum theorem,  $\frac{d}{dD} (i_{DF\text{ RMS}}) = 0$

$$\frac{d}{dD} \left[ \sqrt{(1-D)} \left\{ \frac{DV_s - E}{R} \right\} \right] = 0$$

$$\frac{d}{dD} [\sqrt{(1-D)} \cdot \{DV_s - E\}] = 0$$

$$\sqrt{(1-D)} \cdot V_s + (DV_s - E) \cdot \left[ \frac{-1}{2\sqrt{1-D}} \right] = 0$$

$$\sqrt{(1-D)} \cdot V_s - \frac{(DV_s - E)}{2\sqrt{1-D}} = 0$$


$$\sqrt{(1-D)} \cdot V_s = \frac{(DV_s - E)}{2\sqrt{(1-D)}}$$

$$2(1-D)V_s = DV_s - E$$


$$2 - 2DV_s = DV_s - E$$

$$2 + E = 3DV_s$$


$$\therefore D = \frac{(2 + E)}{3V_s}$$

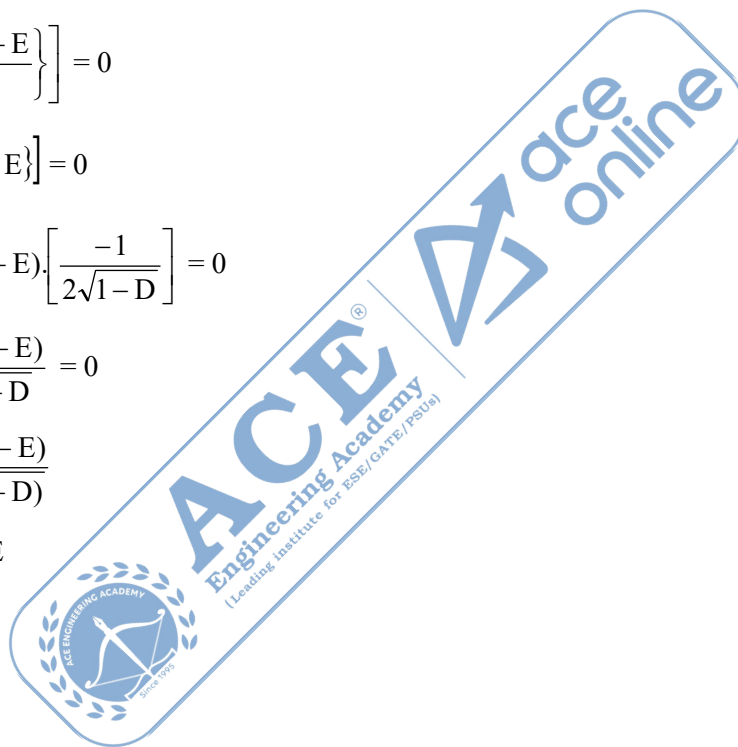

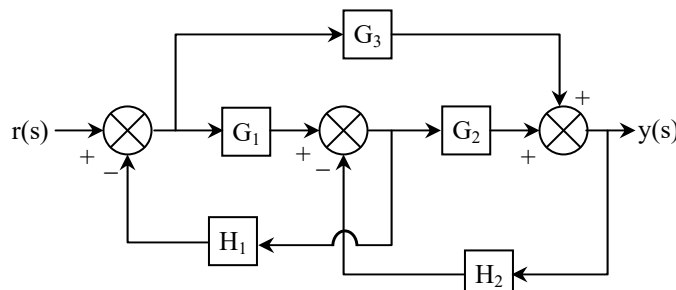
**5[c] The block diagram of a system is as shown below. Find the overall transfer function of the system using block diagram reduction technique. [12M]**




**Solution:**

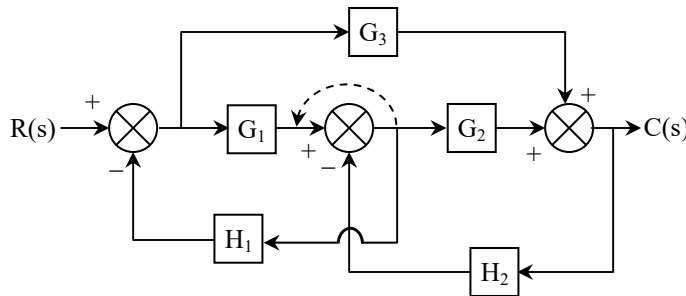

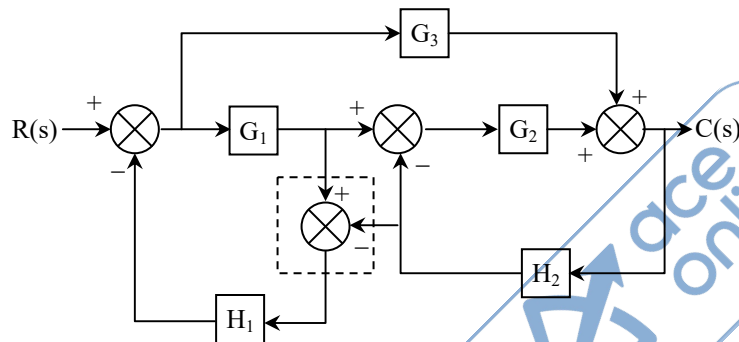
S1: Shift take—off point a head of summing point. The equivalent block diagram as follows.



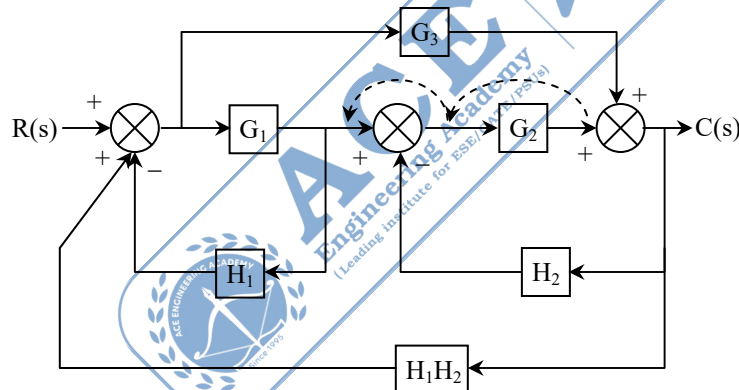
S2: Redraw the above block diagram by eliminating summing point.



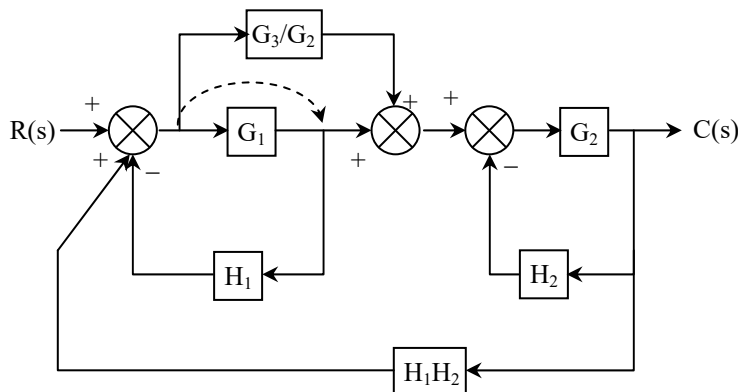
S3: Shift summing point a head of  $G_2$ , the equivalent diagram as follows.



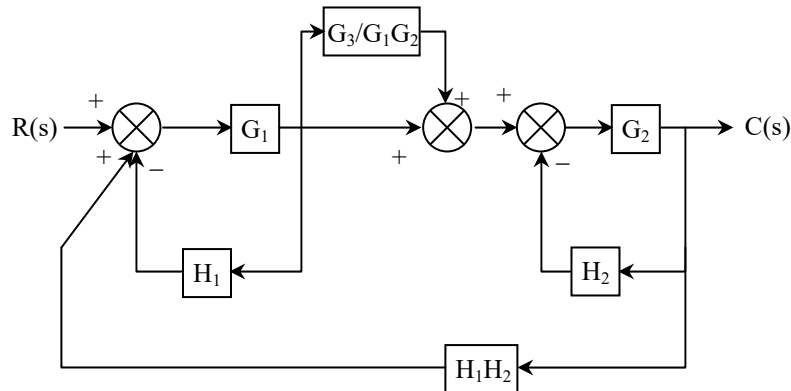
S4: Shift take-off point after  $G_1$ , the equivalent diagram as follows.



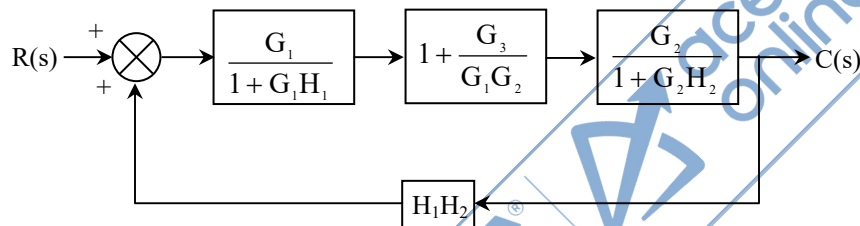
S5: Simplifying feedback & parallel combinations.



S6: Simplifying series combinations.

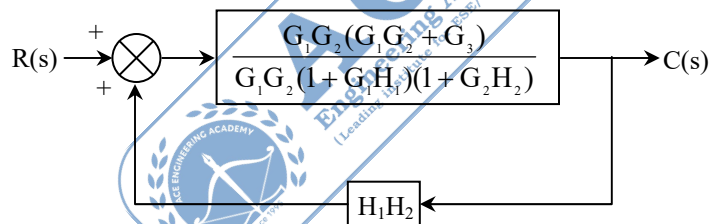

S7: Simplifying feedback,

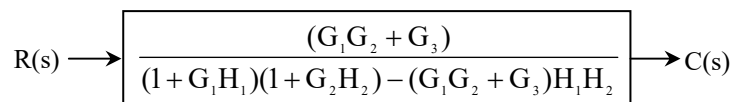

$$\frac{C(s)}{R(s)} = \frac{(G_1G_2 + G_3)}{1 + G_1H_1 + G_2H_2 + G_1H_1G_2H_2 - G_1G_2H_1H_2 - G_3H_1H_2}$$

$$\frac{C(s)}{R(s)} = \frac{(G_1G_2 + G_3)}{1 + G_1H_1 + G_2H_2 - G_3H_1H_2}$$



**ACE**<sup>®</sup>  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs

 **ace**  
online



Scan QR code for more details

# GATE | ESE - 2026

## Online Test Series

### GATE - 2026

EC | EE | CE | ME | CS | IN | PI | DA

No. of Tests: **54**

+

**FREE** 54 Tests of  
GATE - 2025

Total Tests: **108\***

### ESE (Prelims) 2026\*

EC | EE | CE | ME


No. of Tests: **44**

+

**FREE** 30 Tests of  
ESE (Prelims) 2025

Total Tests: **74\***

**Losing Marks To  
Poor Time Management?**  
Solve with **ACE Test Series**

 REAL-TIME MOCK TESTS

 SMART FEEDBACKS

 VIDEO SOLUTIONS

GATE | ESE | PSUs | SSC | State AE | JE exams

**GRAB FLAT**

**20% OFF**

**FREEDOM FESTIVAL**


from **9<sup>th</sup>** to **17<sup>th</sup>** August

5[d] (i) Draw the silicon cross-section view of IGBT and identify the distinguishing feature from MOSFET with reference to the conductivity modulation. Also, state its impact on IGBT operation and performance. [8M]

(ii) Draw 2-transistor and simplified equivalent circuits with proper labels and their significance. [4M]

**Solution:**


(i)

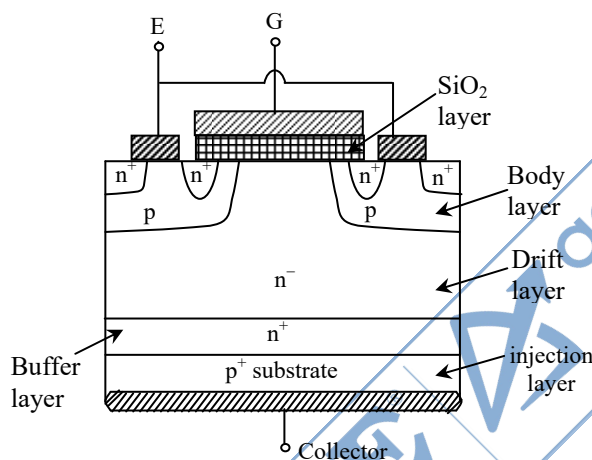

IGBT is constructed in the same manner as a power MOSFET, there is however a major difference in the substrate. The  $n^+$  layer substrate at the drain in a power MOSFET is now substituted in the IGBT by a  $p^+$  layer substrate called collector 'C'.

In IGBT,  $p^+$  substrate is called injection layer because it injects holes into  $n^-$  layer. When gate is made positive with respect to emitter by voltage  $V_G$ , with gate emitter voltage more than the threshold voltage  $V_{GET}$  of IGBT, an  $n$ -channel is framed in the upper part of  $p$  region just beneath the gate. This  $n$ -channel short circuit the  $n^-$  region with  $n^+$  emitter regions. Electrons from  $n^+$  emitter begin to flow to  $n$  drift region through  $n$ -channel. Also  $p^+$  collector region injects holes into  $n^-$  drift region. In short  $n^-$  drift region is flooded with electrons from  $n^+$  region and holes from  $p^+$  collector region, with this, injection carrier density in  $n^-$  drift region increases and conductivity of  $n^-$  region enhances, this will reduce ON state resistance of IGBT is less than power MOSFET.

(ii)

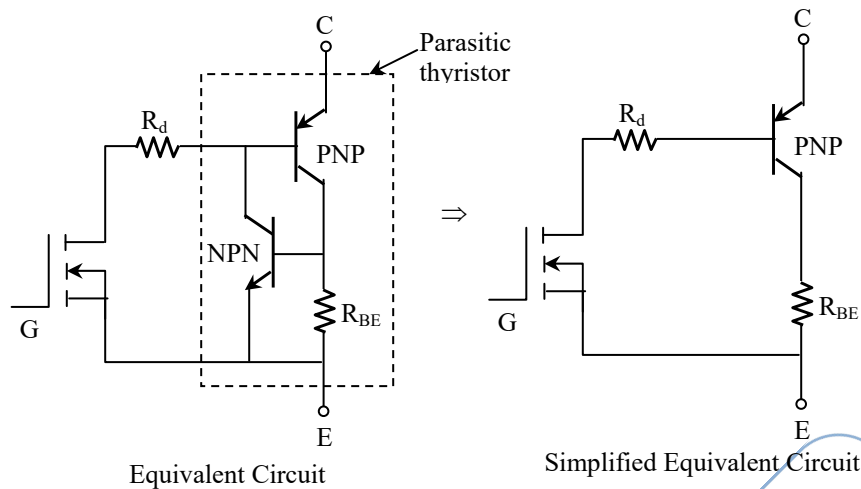

An IGBT is made of four alternate PNP layers and could latch like a thyristor given the necessary condition  $(\alpha_{NPN} + \alpha_{PNP}) > 1$ . Two transistor model of an IGBT provides a simplified representation of its internal structure and behavior. It combines a BJT and a MOSFET to explain how IGBT operates. This model helps to understand how the IGBT combines the advantages both transistor types: high input impedance and fast switching from the MOSFET and low on state voltage drop from the BJT.

**5[e] The overall transfer function of a unity feedback system is given by**

$$G_{CL}(s) = \frac{Ks + b}{s^2 + as + b}$$

- (i) Calculate the open loop transfer function of the system and its type.
- (ii) If the overall system with  $K=0$ , admits a unity normalized bandwidth, and a settling time of 4 seconds for 2% tolerance band, compute position, velocity and acceleration error constants. Assume unity DC gain.
- (iii) Compute the sensitivity and complimentary sensitivity function value at  $\omega = 1$  rad/sec. Consider  $K=1$ .
- (iv) Discuss the effect of having a non-zero value of  $K$  on the behavior of the system in comparison to that with  $K=0$ .

**[12M]**

**Solution:**

$$\text{Overall TF} \Rightarrow G_{CL}(s) = \left( \frac{Ks + b}{s^2 + as + b} \right)$$



$$\begin{aligned} \text{(i) OLTF} &= \frac{G_{CL}(s)}{1 - G_{CL}(s)} = \frac{\frac{Ks + b}{s^2 + as + b}}{1 - \left(\frac{Ks + b}{s^2 + as + b}\right)} \\ &= \frac{(Ks + b)}{(s^2 + as + b) - (Ks + b)} = \frac{(Ks + b)}{s^2 + s(a - K)} \\ \Rightarrow \text{OLTF} &= \frac{(Ks + b)}{s^1(s + (a - K))}, H(s) = 1 \end{aligned}$$

Type – 1 System

$$\text{(ii) } G_{CL}(s) = \frac{Ks + b}{s^2 + as + b}$$

$$\text{If } K = 0 \Rightarrow G_{CL}(s) = \frac{b}{s^2 + as + b}, t_s = 4 \text{ sec}(\pm 2\%)$$

$$\Rightarrow \text{Compare with standard form of second order system } \left( \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2} \right)$$

$$\omega_n = \sqrt{b} \text{ rad/sec}, 2\xi\omega_n = a$$

$$\pm 2\%: t_s = \frac{4}{\xi\omega_n} = 4 \text{ sec} \Rightarrow \xi\omega_n = 1$$

$$\Rightarrow \text{Unity normalized bandwidth } \omega_n = 1 \text{ rad/sec} \quad a = 2\xi\omega_n = 2 \text{ and } b = 1$$

**Error constants:**

$$\text{When } K = 0: \text{OLTF} = \frac{G_{CL}(s)}{1 - G_{CL}(s)} = \frac{\frac{b}{s^2 + as + b}}{1 - \frac{b}{s^2 + as + b}}$$

$$\text{OLTF} = \left( \frac{b}{s^2 + as + b - b} \right)$$

$$\text{OLTF} = \frac{b}{s^2 + as} = \frac{b}{s(s + a)}$$

$$G(s) = \text{OLTF} = \frac{b}{s(s + a)}, H(s) = 1$$

Position Error constant:

$$\Rightarrow K_p = \lim_{s \rightarrow 0} s G(s) = \lim_{s \rightarrow 0} \frac{b}{s + a} = \infty$$

Velocity error constant:

$$K_v = \lim_{s \rightarrow 0} s G(s) = \lim_{s \rightarrow 0} s \left( \frac{b}{s(s+a)} \right) = \frac{b}{a}$$

Acceleration Error Constant:

$$K_a = \lim_{s \rightarrow 0} s^2 G(s) = \lim_{s \rightarrow 0} s^2 \left( \frac{b}{s(s+a)} \right) = 0$$

$$(iii) G_{CL}(s) = \left( \frac{Ks + b}{s^2 + as + b} \right)$$

$$\text{When } K = 1 \rightarrow G_{CL}(s) = \frac{(s+b)}{(s^2 + as + b)}$$

$$\text{Sensitivity of CLTF with } G(s) \Rightarrow S_G^T = \frac{1}{1 + G(s)}$$

$$\text{OLTF} \rightarrow G(s) = \frac{(s+b)}{(s^2 + as + b) - (s+b)}$$

$$G(s) = \frac{(s+b)}{s^2 + as + b - s - b} = \frac{(s+b)}{s^2 + s(a-1)}$$

$$S_G^T = \frac{1}{1 + G(s)} = \frac{1}{1 + \left( \frac{(s+b)}{s^2 + s(a-1)} \right)}$$

$$S_G^T = \frac{s^2 + s(a-1)}{s^2 + as - s + s + b} \Rightarrow S_G^T = \frac{s^2 + s(a-1)}{s^2 + as + b}$$

$$S_G^T|_{s=j\omega} = \frac{-1 + j(a-1)}{-1 + aj + b} = \left( \frac{-1 + j(a-1)}{(b-1) + aj} \right)$$

**Complimentary sensitivity function :**

Sensitivity + Complementary sensitivity = 1

$$\text{Complimentary sensitivity} = (1 - \text{Sensitivity}) = 1 - \left[ \frac{-1 + j(a-1)}{(b-1) + aj} \right]$$

$$= \frac{(b-1) + aj + 1 - ja + j}{(b-1) + aj} = \left( \frac{b + j}{(b-1) + aj} \right)$$

(iv)  $K \neq 0$

$\Rightarrow$  If  $K$  is non-zero, then the damping ratio and natural frequency of oscillations are affected. Hence the transient response characteristics affected. Rise time, setting time, overshoot are affected.



**ACE<sup>®</sup>**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs





India's Leading Institute

**ESE, GATE, PSUs**  
SSC, RRB, BANKING & 30+ other exams


— USE CODE —  
**COLLEGE10**

Get **10% OFF**  
on all courses

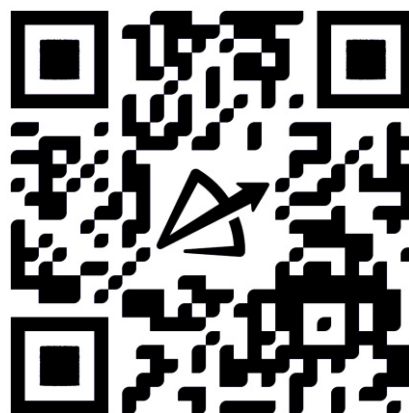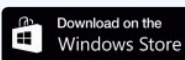

Scan QR & start your  
**7-DAY Free Trial!**

*#Let's ACE it!*

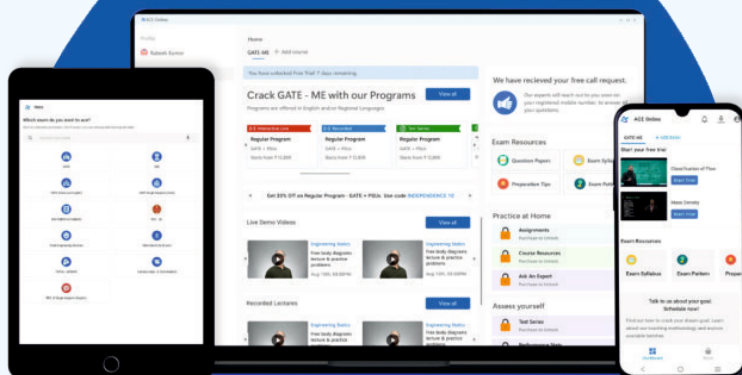

 **7799996602**

[www.ace.online](http://www.ace.online) | [www.aceenggacademy.com](http://www.aceenggacademy.com)

$\Rightarrow$  Error constants  $\Rightarrow K_p$  remains  $\infty$

$$\Rightarrow K_v = \lim_{s \rightarrow 0} sG(s) = \lim_{s \rightarrow 0} s \left( \frac{Ks + b}{s(s + (a - K))} \right)$$

$$K_v = \left( \frac{b}{a - K} \right)$$

$\Rightarrow K_a$  remains 0

6[a] A single phase AC controller operating on phase control is supplied from a 230 V, 50 Hz AC supply. If the controller is feeding a purely resistive load of  $10\Omega$  at a firing angle of  $45^\circ$ ; then determine

- (i) the RMS output voltage  $V_0$  rms (phase) of the phase controlled AC controller.
- (ii) the equivalent duty cycle (K) of an integral cycle AC controller that would produce the same RMS output voltage.
- (iii) If the integral cycle controller operates with a total of 100 cycles for one complete operation, determine the number of 'ON' cycles and 'OFF' cycles for the same as in (ii).
- (iv) The input power factor of the integral duty cycle AC controller operating at equivalent duty cycle.
- (v) The RMS Thyristor current  $I_{T, rms}$  for the integral cycle controller operating at this equivalent duty cycle.

Derive the formula used for integral cycle AC controllers as used in above parts.


[20M]

**Solution:**

**1- $\phi$  AC voltage controller:**

$$V_{S RMS} = 230 \text{ V}, R = 10 \Omega, \alpha = 45^\circ$$

(i) Phase control:

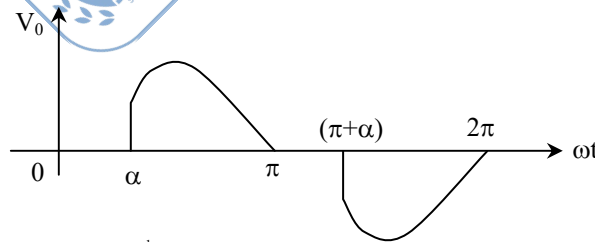

$$V_{0 RMS} = \left[ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2(\omega t) d\omega t \right]^{\frac{1}{2}}$$

$$= V_m \left[ \frac{1}{\pi} \int_{\alpha}^{\pi} \frac{1 - \cos(2\omega t)}{2} d\omega t \right]^{\frac{1}{2}}$$


$$= \frac{V_m}{\sqrt{2\pi}} \left[ \left\{ \omega t - \frac{\sin(2\omega t)}{2} \right\}^\pi_\alpha \right]^{\frac{1}{2}}$$

$$V_{0\text{ RMS}} = \frac{V_m}{\sqrt{2\pi}} \left[ (\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right]^{\frac{1}{2}}$$

$$\therefore V_{0\text{ RMS}} = \frac{230\sqrt{2}}{\sqrt{2\pi}} \left[ \left( \pi - \frac{\pi}{4} \right) + \frac{\sin(2 \times 45^\circ)}{2} \right]^{\frac{1}{2}}$$

$$V_{0\text{ RMS}} = 219.3 \text{ V}$$

(ii) Integral cycle control

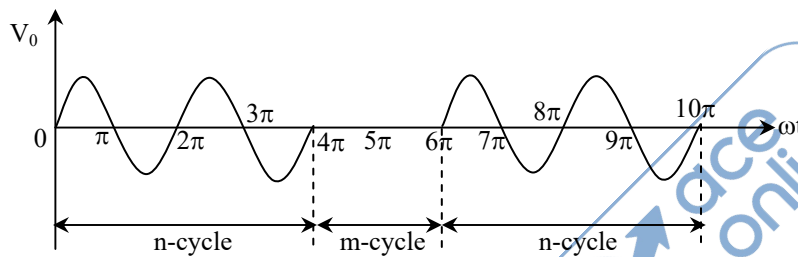

$$V_{0\text{ RMS}} = \left[ \frac{n}{(m+n)2\pi} \int_0^{2\pi} V_m^2 \sin^2(\omega t) d\omega t \right]^{\frac{1}{2}}$$

$$= \sqrt{\frac{n}{(m+n)}} V_{\text{SRMS}}$$

$$V_{0\text{ RMS}} = \sqrt{K} V_{\text{SRMS}} ; \text{ where } K = \frac{n}{m+n} \Rightarrow \text{Duty cycle}$$

$$219.3 = \sqrt{K} \times 230$$

$$\therefore K = 0.909$$

(iii)  $m + n = 100$

$$K = 0.909$$

$$\frac{n}{(m+n)} = 0.909$$

$$\frac{n}{100} = 0.909$$

$$n = 90.9 \approx 91$$

$$m + n = 100$$

$$m + 91 = 100$$

$$\therefore m = 9$$

$$\therefore \text{Number of ON cycles } n = 91$$

Number of OFF cycles  $m = 9$

(iv) Input power factor  $[\cos(\phi_s)]:$

$$P_{\text{input}} = P_{\text{output}}$$

$$V_{S\text{RMS}} \cdot i_{S\text{RMS}} \cos(\phi_s) = V_{0\text{RMS}} i_{0\text{RMS}}$$


$$\therefore \cos\phi_s = \frac{V_{0\text{RMS}}}{V_{S\text{RMS}}}$$

$$= \frac{\sqrt{K} V_{S\text{RMS}}}{V_{S\text{RMS}}}$$

$$\therefore \cos(\phi_s) = \sqrt{K}$$

$$\therefore \text{Input power factor} = \sqrt{0.909} = 0.9534 \text{ (lagging)}$$

(v)

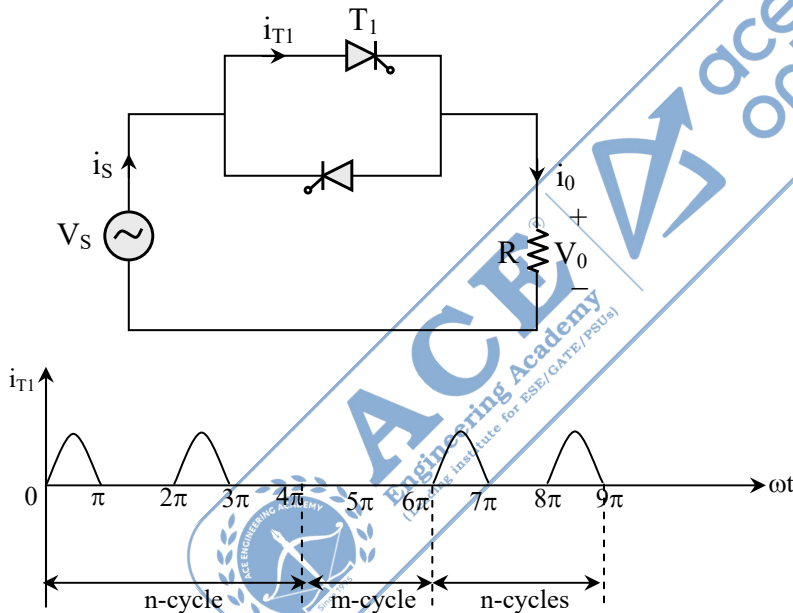

$$i_{\text{TRMS}} = \left[ \frac{n}{(m+n)} \cdot \frac{1}{2\pi} \int_0^\pi \frac{V_m^2 \sin^2(\omega t)}{R^2} d\omega t \right]^{\frac{1}{2}}$$

$$= \sqrt{\frac{n}{(m+n)}} \cdot \frac{V_m}{\sqrt{2\pi}} \times \frac{1}{R} \left[ \int_0^\pi \frac{1 - \cos(2\omega t)}{2} d\omega t \right]^{\frac{1}{2}}$$

$$= \sqrt{K} \frac{V_m}{\sqrt{\pi} \cdot 2R} \left[ \left( \omega t - \frac{\sin(2\omega t)}{2} \right) \right]_0^\pi^{\frac{1}{2}}$$

$$= \frac{\sqrt{K} \cdot V_m}{\sqrt{\pi} \cdot 2R} [\pi - 0]^{\frac{1}{2}}$$

$$i_{\text{TRMS}} = \frac{\sqrt{K} \cdot V_m}{2R} = \sqrt{0.9} \times \frac{230\sqrt{2}}{2 \times 10}$$

$$i_{\text{TRMS}} = 15.43 \text{ A}$$

**6[b] (i) Derive the even and odd decomposition of a general signal  $x(t)$  by applying the definitions of even and odd signals. [10M]**

**Solution:**

Any general signal  $x(t)$  can be expressed as sum of its even part and odd part.

$$x(t) = x_e(t) + x_o(t) \dots\dots\dots(1)$$

Where  $x_e(t)$  is even part of  $x(t)$

$x_o(t)$  is odd part of  $x(t)$

$$\text{Now, } x(-t) = x_e(-t) + x_o(-t)$$

From the definition of even and odd signals

$$x_e(-t) = x_e(t) \text{ and}$$

$$x_o(-t) = -x_o(t)$$

$$\text{So, } x(-t) = x_e(t) - x_o(t) \dots\dots\dots(2)$$

Add equation (1) & (2)

$$x(t) + x(-t) = 2x_e(t)$$


$$x_e(t) = \frac{x(t) + x(-t)}{2}$$

Subtract equation (1) & (2)

$$(1) - (2) \Rightarrow x(t) - x(-t) = 2x_o(t)$$

$$x_o(t) = \frac{x(t) - x(-t)}{2}$$

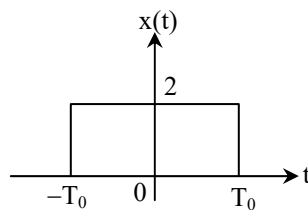**6[b] (ii) Find Fourier Transform of  $x(t)$ , which is given by following rectangular pulse, as shown in figure. [10M]**





**ACE<sup>®</sup>**  
Engineering Academy  
Leading Institute for ESE/GATE/PSUs

**ace  
online**  
(A Digital Initiative by ACE Engineering Academy)

# HEARTY CONGRATULATIONS TO OUR STUDENTS SELECTED IN **TGPSC-AEE (2022)**



Rank **1** (EE)

**KAVYA NALLA**  
CLASSROOM COACHING  
Selected in: **Transport,**  
**R&B Dept., Govt. of TG.**



**1** **CE**  
Venkat Reddy  
MEGA MOCK TEST  
Selected in Public Health,  
MA & UD Dept. Govt. of TG.



**3** **EE**  
Devarakonda Sathwik  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**4** **EE**  
Sangem Ravi Kumar  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**4** **CE**  
Makam Jeevan Kumar  
CLASSROOM COACHING  
Selected in **Public Health,**  
MA & UD Dept., Govt. of TG.



**6** **CE**  
Balraj Madgan  
MEGA MOCK TEST  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**7** **EE**  
Challabotta Saikiran  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**7** **ME**  
Vineetha Boddula  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



**7** **CE**  
Rama Krishna  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**8** **CE**  
Abhinav Karimilla  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**9** **EE**  
Ganapathi G  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**9** **CE**  
Pranay V  
CLASSROOM COACHING  
Selected in **Public Health,**  
MA & UD Dept., Govt. of TG.



**11** **EE**  
Sainath  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



**11** **CE**  
Bhugolla Surya Teja  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.



**12** **EE**  
Veligeti Umesh  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



**12** **CE**  
Puli Naveen Reddy  
CLASSROOM COACHING  
Selected in **Transport,**  
R&B Dept., Govt. of TG.




**14** **ME**  
Ravi Teja  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



**15** **ME**  
M Dheeraj Reddy  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



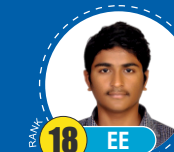**16** **EE**  
Jangili Rajashekar  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



**18** **EE**  
Maika Kiran  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.



**19** **EE**  
Sowmya  
CLASSROOM COACHING  
Selected in **Irrigation**  
& CAD Dept., Govt. of TG.




**20** **CE**  
Md. Azmatullah  
MEGA MOCK TEST  
Selected in **Transport,**  
R&B Dept., Govt. of TG.

AND MANY MORE..

**500+ SELECTIONS**  
**CE : 434 | EE : 61 | ME : 20**



**Solution:**

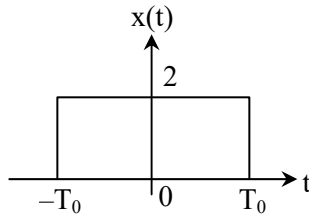

The F.T of  $x(t)$  is  $X(\omega) = \int_{-\infty}^{\infty} x(t)e^{-j\omega t} dt$

$$\text{So, } X(\omega) = \int_{-T_0}^{T_0} 2e^{-j\omega t} dt$$

$$X(\omega) = \frac{2e^{-j\omega t}}{-j\omega} \Big|_{-T_0}^{T_0}$$

$$X(\omega) = -\frac{2}{j\omega} [e^{-j\omega T_0} - e^{j\omega T_0}]$$

$$X(\omega) = -\frac{2}{j\omega} [-2j\sin(\omega T_0)]$$

$$X(\omega) = \frac{4}{\omega} \sin(\omega T_0)$$

$$X(\omega) = \frac{4}{\omega} \left[ \frac{\sin(\omega T_0)}{\omega T_0} \right] \omega T_0$$

$$X(\omega) = 4T_0 \left[ \frac{\sin(\omega T_0)}{\omega T_0} \right]$$

We know that  $\text{Sa}(x) = \frac{\sin(x)}{x}$

$$\text{So, } X(\omega) = 4T_0 \text{Sa}[\omega T_0]$$

**6[c] A unity feedback system has open loop transfer function.**

$$G(s) = \frac{K.e^{-0.5s}}{(s^2 + \alpha s + \beta)}$$

**$G(s)$  has a DC gain of  $K/16$ , and has a decay rate of 2 nepers per second. Using first-order Pade approximation for the delay, sketch the root locus plot of  $G(s)$  and find the range of  $K$  for which the unity feedback system remains stable. [20M]**

**Solution:**

$$G(s) = \frac{K.e^{-0.5s}}{(s^2 + \alpha s + \beta)}$$

$$\Rightarrow \text{Given DC gain} \Rightarrow \frac{K}{16}$$

Decay rate = 2 nepers/second

$$\Rightarrow \text{DC gain of } G(s)_{s=0} = \frac{K.e^0}{0+0+\beta} = \frac{K}{\beta} = \frac{K}{16}$$

$$\beta = 16$$

 $\rightarrow$  Decay rate gives real part of pole  $\Rightarrow$  That is  $-2$ .

$$\xrightarrow{\text{CE}} s^2 + \alpha s + \beta = 0$$

$$s_1, s_2 = \frac{-\alpha \pm \sqrt{\alpha^2 - 4 \times 1 \times \beta}}{2 \times 1}$$

$$= \left( \frac{-\alpha}{2} \pm \frac{\sqrt{\alpha^2 - 4\beta}}{2} \right)$$

$$\text{Real part of pole} = -\frac{\alpha}{2} = -2 \Rightarrow \alpha = 4$$

 $\Rightarrow$  First-order padé approximation for  $e^{-0.5s}$ ,

$$e^{-0.5s} \approx \frac{\left(1 - \frac{0.5s}{2}\right)}{\left(1 + \frac{0.5s}{2}\right)} = \frac{(1 - 0.25s)}{(1 + 0.25s)}$$

$$\Rightarrow \text{Substitute all the values, then } G(s) = \frac{K \left( \frac{1 - 0.25s}{1 + 0.25s} \right)}{(s^2 + 4s + 16)}$$

$$\Rightarrow G(s) = \frac{K(1 - 0.25s)}{(1 + 0.25s)(s^2 + 4s + 16)} = \frac{K(4 - s)}{(4 + s)(s^2 + 4s + 16)}$$

$$\xrightarrow{\text{Poles}} (s + 4)(s^2 + 4s + 16) = 0$$


$$s = -4, s = \frac{-4 \pm \sqrt{16 - 4 \times 1 \times 16}}{2}$$

$$s = -4, s = -2 \pm j2\sqrt{3}$$

$$\xrightarrow{\text{Zero}} (4 - s) = 0 \Rightarrow s = +4$$

$$G(s) = \frac{-K(s-4)}{(s+4)(s+2-j2\sqrt{3})(s+2+j2\sqrt{3})}, H(s) = 1$$

Real axis root locus:

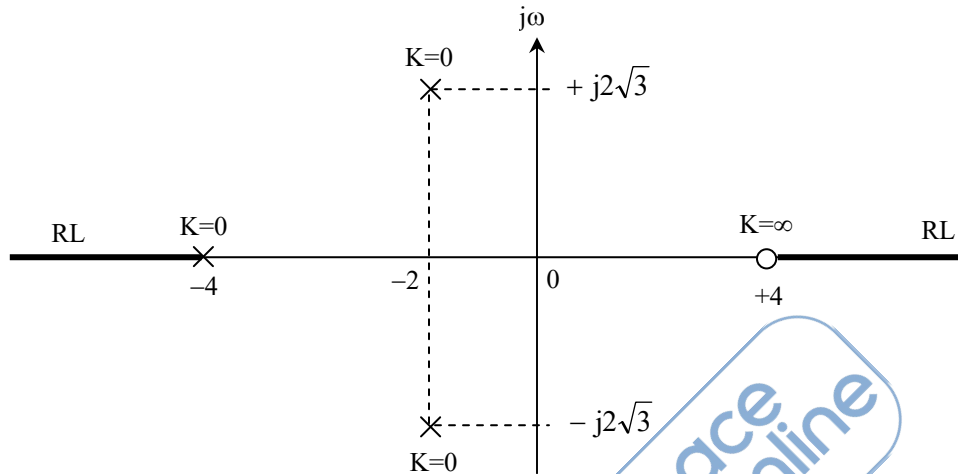

Number of Asymptotes:

$$N = (P - Z)$$

$$= 3 - 1 = 2$$

$$\theta = \frac{(2q)180^\circ}{(P - Z)} \Rightarrow q = 0 \Rightarrow \theta = 0^\circ$$

$$\Rightarrow q = 1 \Rightarrow \theta = \frac{2 \times 180^\circ}{2} = 180^\circ$$

**Break Point:**

$$\xrightarrow{\text{CE}} (s+4)(s^2 + 4s + 16) + K(4-s) = 0$$

$$\xrightarrow{\text{CE}} (s^3 + 8s^2 + 32s + 64) + K(4-s) = 0$$

$$K = \frac{(s^3 + 8s^2 + 32s + 64)}{(s-4)}$$

$$\xrightarrow{\text{BP}} \frac{dK}{ds} = 0$$

$$\frac{dK}{ds} = \frac{(3s^2 + 16s + 32)(s-4) - (s^3 + 8s^2 + 32s + 64)1}{(s-4)^2} = 0$$

$$\Rightarrow 2s^3 - 4s^2 - 64s - 192 = 0$$

$$\Rightarrow s = 7.72, -2 \pm j2.04$$

Valid BP is 7.72

**Intersection point with Imaginary axis:**

$$\xrightarrow{CE} 1 + G(s) = 0$$

$$\xrightarrow{CE} s^3 + 8s^2 + s(32 - K) + (64 + 4K) = 0$$

Routh Array:

$s^3$	1	$(32 - K)$
$s^2$	8	$(64 + 4K)$
$s^1$	$\frac{(256 - 8K - 64 - 4K)}{8}$	
$s^0$	$(32 - K)$	

$\Rightarrow$  For marginal stability

$$(256 - 8K - 64 - 4K) = 0$$


$$\Rightarrow (192 - 12K) = 0 \Rightarrow K_{\text{mar}} = 16$$

$$\Rightarrow \xrightarrow{AE} 8s^2 + (64 + 4 \times 16) = 0$$

$$8s^2 + 128 = 0$$

$$s^2 + 16 = 0$$

$$s = \pm j4$$

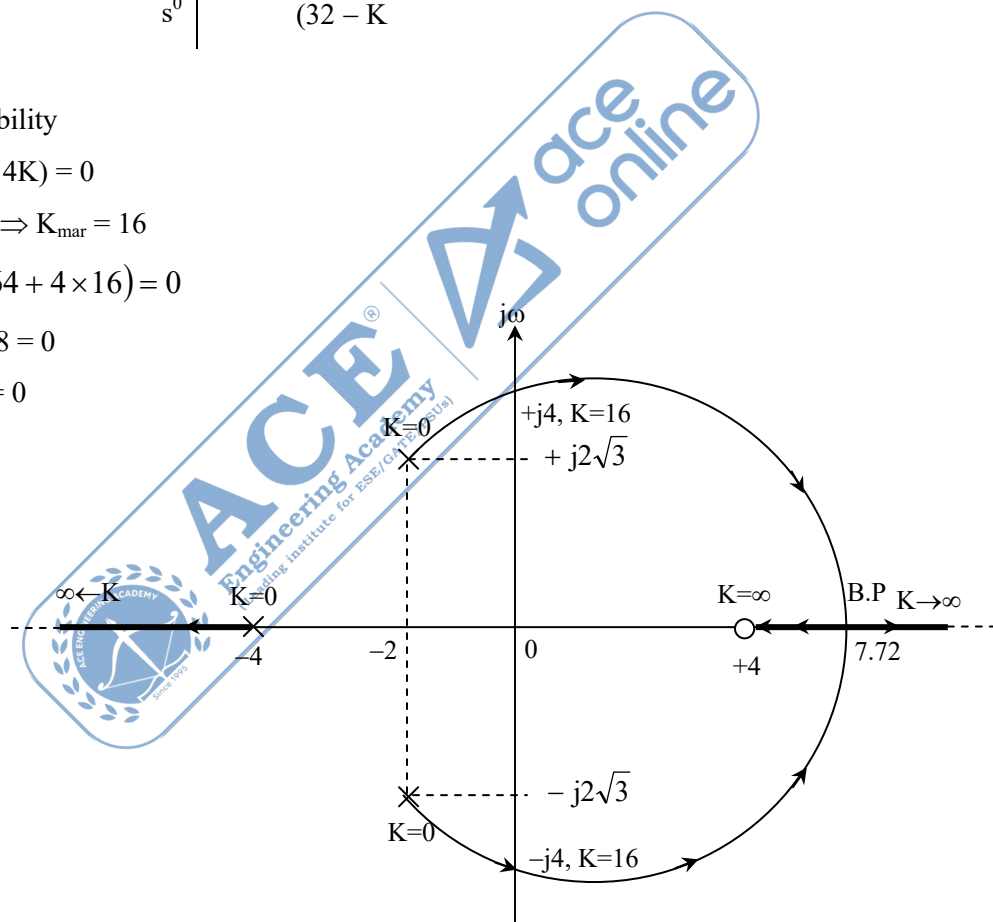

$\Rightarrow$  Condition for CL stability

$$0 < K < 16$$

$\Rightarrow K = 16$  closed loop system is marginal stable

$\Rightarrow$  When  $K = 16$ , the frequency of oscillations  $\omega_n = 4$  rad/sec

# Hearty Congratulations

To our students **CIVIL ENGINEERING**  
Selected in **SSC JE - 2024**



**HARSHIT KHARE**  
Roll No. **3008100089**  
Selected in: **CPWD**



**RAMSWRUP**  
Roll No. **2404100567**  
Selected in: **CPWD**



**LAKSHIT BHARDWAJ**  
Roll No. **3206106390**  
Selected in: **CPWD**



**M V SIVA RAM REDDY**  
Roll No. **8008101372**  
Selected in: **CPWD**



**RAVINDRA DHAKAD**  
Roll No. **6005100485**  
Selected in: **CPWD**



**RAHUL KUMAWAT**  
Roll No. **2401100340**  
Selected in: **CPWD**



**VISHAL SINGH**  
Roll No. **3013105309**  
Selected in: **MES**



**S R JAFFER SHARIEF**  
Roll No. **8006102160**  
Selected in: **MES**



**BEHARA SRIKANTH**  
Roll No. **8007102883**  
Selected in: **MES**



**ANIRUDH KOTIYAL**  
Roll No. **2003101448**  
Selected in: **MES**



**FAIZAN AHMAD**  
Roll No. **3010108428**  
Selected in: **MES**



**AMBATI NAGA SRI SAI**  
Roll No. **8601105973**  
Selected in: **MES**



**BHASKAR SHARMA**  
Roll No. **2201112287**  
Selected in: **MES**



**SRINI VASA RAO**  
Roll No. **8601101840**  
Selected in: **MES**



**PIJUSH AKHULI**  
Roll No. **4426100222**  
Selected in: **MES**



**ABHIMANU KUMAR**  
Roll No. **3205100298**  
Selected in: **MES**



**NIMESH SINGH**  
Roll No. **2201114868**  
Selected in: **MES**



**LALAM RAMU NAIDU**  
Roll No. **8601102319**  
Selected in: **MES**



**GYANENDRA KUMAR**  
Roll No. **2201110803**  
Selected in: **CWC**



**ADARSH AGRAHARI**  
Roll No. **3003100031**  
Selected in: **BRO**



**REDDI SANNIBABU**  
Roll No. **8007102353**  
Selected in: **MES**



**KONAPALA MANOJ**  
Roll No. **2201109855**  
Selected in: **MES**



**SUNIL SHARMA**  
Roll No. **4415100648**  
Selected in: **MES**



**RINKESH KUMAR**  
Roll No. **6204103361**  
Selected in: **MES**

& many more..


**Total 150+ Selections**

**CE-98**

**EE-29**

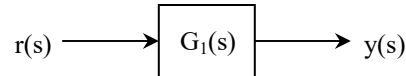**ME-24**


7[a] A second order system  $G_1(s)$  as shown in figure has no zeros, and has unity DC gain.



The unit step response of  $G_1(s)$  has a decay rate of 2.5 nepers/sec and has undamped natural frequency of  $\sqrt{6}$  rad/sec

(i) Compute the observable canonical state representation of  $G_1(s)$  and obtain its state transition matrix using Cayley-Hamilton approach.

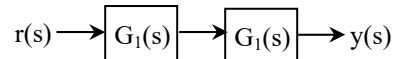(ii) Now another identical  $G_1(s)$  is placed in cascade with earlier  $G_1(s)$ , as shown below.



Obtain the state space representation of overall cascaded system using previously computed observable canonical representation of  $G_1(s)$  [20M]

**Solution:**

Given Decay rate = 2.5 nepers/sec, unity dc gain

Decay rate for second order system =  $\xi\omega_n = 2.5$

$$= \omega_n = \sqrt{16} \text{ rad/sec}$$

$$\text{Second order TF} \Rightarrow G_1(s) = \frac{K\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$G(s) = \left( \frac{K6}{s^2 + 5s + 6} \right)$$

$$\text{Unity dc gain} \Rightarrow G_1(s) \Big|_{s=0} = \frac{K6}{6} = 1 \Rightarrow K = 1$$

$$G_1(s) = \left( \frac{6}{s^2 + 5s + 6} \right)$$

$$G_1(s) = \frac{Y(s)}{R(s)} = \left( \frac{6}{s^2 + 5s + 6} \right)$$


Divide numerator & denominator with  $\left( \frac{1}{s^2} \right)$

$$\frac{Y(s)}{R(s)} = \left( \frac{6/s^2}{1 + 5/s + 6/s^2} \right) \Rightarrow \text{Compare with mason's gain formula } P_1 = 6/s^2$$

$$L_1 = -5/s$$

$$L_2 = -6/s^2$$

State diagram of OCF:

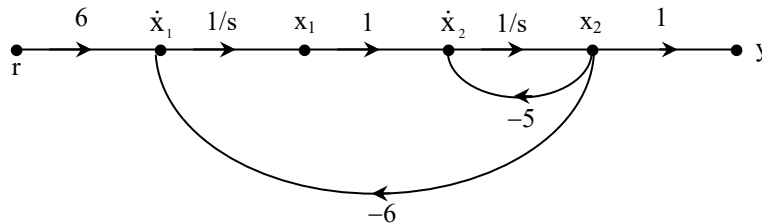

$$\dot{x}_1 = 6r - 6x_2 \dots\dots(1)$$

$$\dot{x}_2 = x_1 - 5x_2 \dots\dots(2)$$

$$y = x_2 \dots\dots(3)$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -6 \\ 1 & -5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 6 \\ 0 \end{bmatrix} [r], \quad [y] = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

Cayley – Hamilton Approach for state transition matrix

$$\xrightarrow{\text{CE}} |\lambda I - A| = \begin{vmatrix} \lambda & 6 \\ -1 & \lambda + 5 \end{vmatrix} = 0$$

$$\lambda(\lambda + 5) + 6 = 0$$

$$\xrightarrow{\text{CE}} \lambda^2 + 5\lambda + 6 = 0 \Rightarrow (\lambda + 2)(\lambda + 3) = 0$$

$$\lambda_1 = -2, \lambda_2 = -3$$

$\Rightarrow$  By Cayley-Hamilton theorem

$$\Rightarrow A^2 + 5A + 6I = 0$$

The state transition matrix

$$\phi(t) = e^{At} = \alpha_0 I + \alpha_1 A$$

In terms of eigen value  $\Rightarrow e^{-\lambda t} = \alpha_0 + \alpha_1 \lambda$

Substituting eigen values  $\Rightarrow e^{-2t} = (\alpha_0 - 2\alpha_1) \dots\dots(4)$

$$e^{-3t} = (\alpha_0 - 3\alpha_1) \dots\dots(5)$$

Solve equation (4) & (5)

$$\alpha_1 = (e^{-2t} - e^{-3t})$$

$$\alpha_0 = (3e^{-2t} - 2e^{-3t})$$

$$\phi(t) = \alpha_0 I + \alpha_1 A$$

$$= (3e^{-2t} - 2e^{-3t}) \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} + (e^{-2t} - e^{-3t}) \begin{bmatrix} 0 & -6 \\ 1 & -5 \end{bmatrix}$$

$$\phi(t) = \begin{bmatrix} 3e^{-2t} - 2e^{-3t} & 0 \\ 0 & 3e^{-2t} - 2e^{-3t} \end{bmatrix} + \begin{bmatrix} 0 & -6e^{-2t} + 6e^{-3t} \\ e^{-2t} - e^{-3t} & -5e^{-2t} + 5e^{-3t} \end{bmatrix}$$

$$\phi(t) = \begin{bmatrix} 3e^{-2t} - 2e^{-3t} & -6e^{-2t} + 6e^{-3t} \\ e^{-2t} - e^{-3t} & -2e^{-2t} + 3e^{-3t} \end{bmatrix}$$

$$(ii) \frac{Y(s)}{r(s)} = G_1(s) \cdot G_1(s)$$

$$= \left( \frac{6}{s^2 + 5s + 6} \right) \left( \frac{6}{s^2 + 5s + 6} \right)$$


$$\frac{Y(s)}{r(s)} = \frac{36}{(s^4 + 10s^3 + 37s^2 + 60s + 36)}$$

Divide numerator & denominator with  $\left( \frac{1}{s^4} \right)$

$$\frac{Y(s)}{r(s)} = \frac{36/s^4}{\left( 1 + \frac{10}{s} + \frac{37}{s^2} + \frac{60}{s^3} + \frac{36}{s^4} \right)}$$

Compare with mason's gain formula
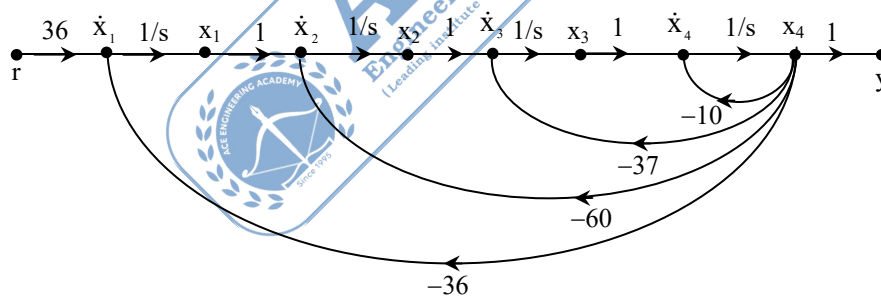
$$P_1 = \frac{36}{s^4}, L_1 = -\frac{10}{s}, L_2 = -\frac{37}{s^2}, L_3 = -\frac{60}{s^3}, L_4 = -\frac{36}{s^4}$$



$$\dot{x}_1 = 36 - 36x_4$$

$$\dot{x}_2 = x_1 - 60x_4$$

$$\dot{x}_3 = x_2 - 37x_4$$

$$\dot{x}_4 = x_3 - 10x_4$$

$$y = x_4$$



# Hearty Congratulations to our students GATE - 2025

**84** TIMES  
AIR 1<sup>st</sup>  
IN GATE

AIR  
**1**



**PI** Devendra Umbrajkar

AIR  
**1**



**EE** Pradip Chauhan

AIR  
**1**



**IN** Kailash Goyal

AIR  
**2**



**EE** Kailash Goyal

AIR  
**2**



**ME** Gollangi Sateesh

AIR  
**2**



**ES** Jitesh Choudhary

AIR  
**3**



**ME** Nimesh Chandra

AIR  
**3**



**ME** Sanket Tupkar

AIR  
**3**



**PI** Sadhan Anumala

AIR  
**3**



**XE** Rohan Biswal

AIR  
**3**



**PI** Aditya Kumar Prasad

AIR  
**4**



**CE** Harshil Maheshwari

AIR  
**5**



**EC** Mohammed Nafeez

AIR  
**5**



**IN** Sachin Yadav

AIR  
**5**



**ME** Uday G.

AIR  
**5**



**PI** Kuldeep Singh naruka

AIR  
**6**



**CE** Nimish Upadhyay

AIR  
**6**



**CE** Shivanand Chaurasia

AIR  
**6**



**EE** Shivam Kumar Gupta

AIR  
**6**



**EE** Puneet Soni

AIR  
**6**



**EC** P Jaswanth Bhavani

AIR  
**6**



**PI** Kaushal Kumar Kaushik

AIR  
**7**



**EC** Subhadip Dey

AIR  
**7**



**ME** Abhinav Srivastava

AIR  
**7**



**IN** Dev Jignesh Patel

AIR  
**7**



**DA** Sairam Gudla

AIR  
**7**



**CS** Hemanth Reddu P

AIR  
**7**



**PI** Waleed Shaikh

AIR  
**7**



**XE** Sanket Tupkar

AIR  
**8**



**ME** Goutam Kumar

AIR  
**8**



**IN** Pushpendra Payal

AIR  
**8**



**CS** Rishi Sharma

AIR  
**9**



**EC** Sai Charan Chilukuri

AIR  
**9**



**ME** Rahul Paliwal

AIR  
**9**



**PI** Anish Vanapalli

AIR  
**10**



**EE** Neelava Mukherjee

AIR  
**10**



**ME** Ashutosh kumar

AIR  
**10**



**ME** Jetty Ganateja

AIR  
**10**



**ME** Pitchika Kumar Vasu

AIR  
**10**




**CE** Adnan Quasain

& many more....

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \\ \dot{x}_4 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & -36 \\ 1 & 0 & 0 & -60 \\ 0 & 1 & 0 & -37 \\ 0 & 0 & 1 & -10 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 36 \\ 0 \\ 0 \\ 0 \end{bmatrix} [r]$$


$$[y] = \begin{bmatrix} 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix}$$

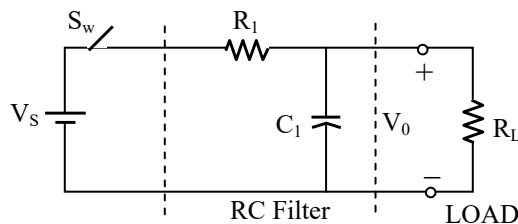**7[b] A buck converter with RC filter is shown in figure with a load resistance  $R_L$ .**




**The switch  $S_w$  is operated with  $DT_s$  time ON and  $(1 - D) T_s$  time OFF, cyclically with a time period of  $T_s$ . Draw the relevant waveforms and derive the expression for output voltage  $V_0$  as a function of duty ratio 'D'. Assume the switching frequency to be high. [20M]**

**Solution:**

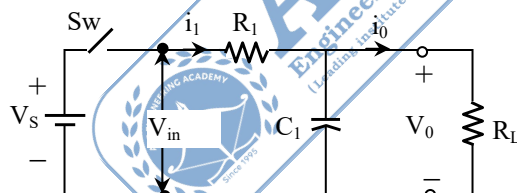


**Assumption:**

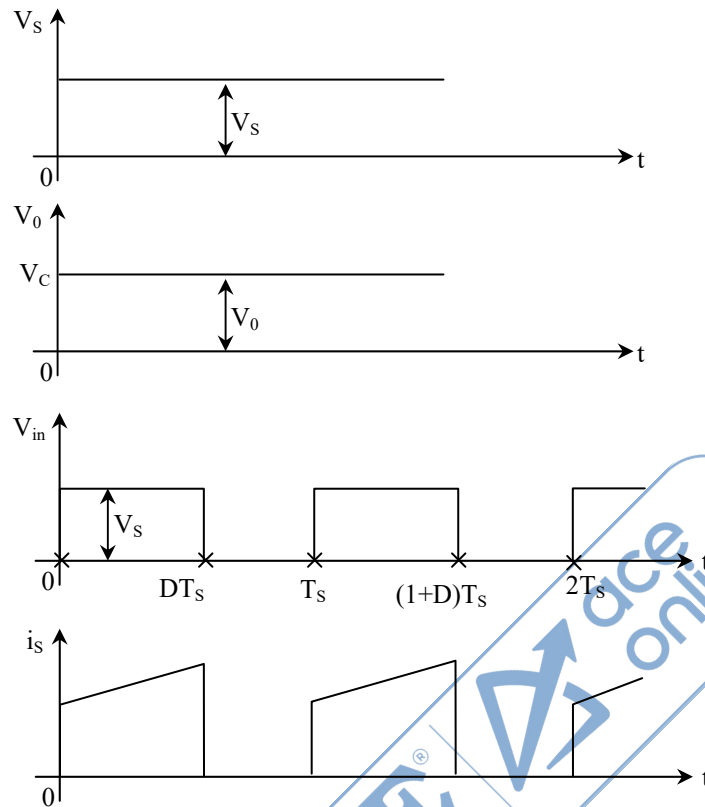1. Capacitor value is high
2. Due to high switching frequency and high capacitor ripple in output voltage is neglected.
3.  $V_0$  and  $i_0$  are ripple free constant.



**During  $t = 0$  to  $DT_s$ :**

SW – ON, C – Charges

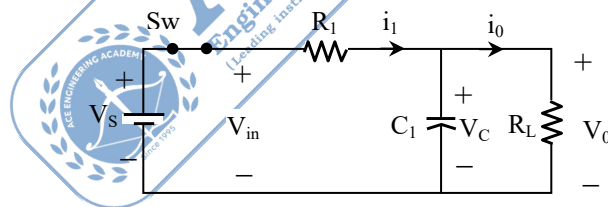


$V_{in} = V_s \Leftarrow$  Input voltage to filter

Current through  $R_1$  increases, capacitor charging and supplying  $R_L$

**During  $t = DT_s$  to  $T$ :**

SW-OFF, C – Discharging through load

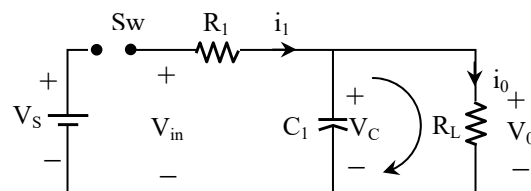

Input voltage to filter

$$V_{in} = 0, i_1 = 0$$

Average voltage at input of RC filter

$$V_{in\ avg} = \frac{DT_s \cdot V_s}{T_s}$$

$$V_{in\ avg} = DV_s$$

As the RC filter averages this pulsating input voltage and provides DC output voltage

∴ We can write


$$V_0 = V_{in\ avg} = DV_s$$

**7[c] Consider a single  $x(t)$  shown in following figure. Sketch and describe mathematically the signal  $x(t)$**

**(i) If time-compressed by factor 5**


**(ii) Repeat the problem for same signal time-expanded by factor 3.**

**[10+10M]**

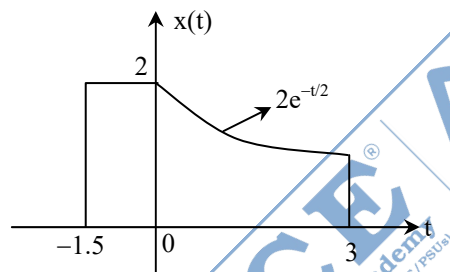


**Solution:**

Given

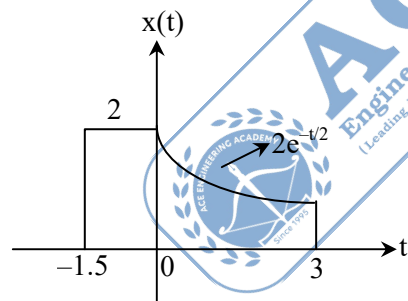

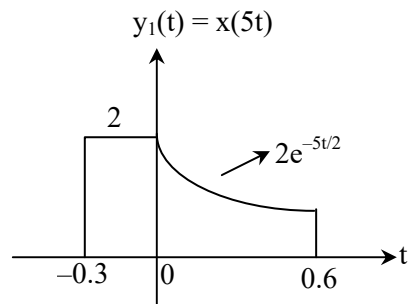(i) Time compressed by a factor of '5'

The resultant signal is  $y_1(t) = x(5t)$



# Hearty Congratulations to our students ESE - 2024



**Rohit Dhondge**



**Himanshu T**



**Rajan Kumar**



**Munish Kumar**



**HARSHIT PANDEY**



**SATYAM CHANDRAKANT**



**RAJESH KASANIYA**



**LAXMIKANT**



**UNNATI CHANSORIA**



**PRIYANSHU MUDGAL**



**GOLLANGI SATEESH**



**MADHAN KUMAR**



**RAJIV RANJAN MISHRA**



**AJINKYA DAGDU**



**AMAN PRATAP SINGH**



**PARAG SAROHA**



**MAYANK KUMAR S**




**BANKURU NAVEEN**



**SANCHIT GOEL**



**CHANDRIKA GADGIL**

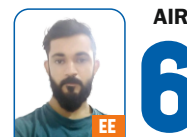

**RITVIK KOK**



**CHANDAN JOSHI**



**DEBARGHYA CH**



**MANTHAN SHARMA**



**DINESH KUMAR S**




**ROHIT KUMAR**



**VIDHU SHREE**



**MAYANK JAIMAN**

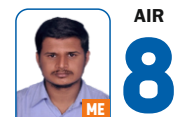

**SHAILENDRA SINGH**



**ANKIT MEENA**



**T PIYUSH DAYANAND**



**ANMOL SINGH**



**KRISHNA KUMAR D**



**RAJESH BADUGU**



**RAJVARDHAN SHARMA**



**AKSHAY VIDHATE**

**TOTAL 36 SELECTIONS IN TOP 10** CE: 09 | ME: 10 | EE: 08 | E&T: 09


$$y_1(t) = 2 \quad -0.3 < t < 0$$

$$= 2e^{-\frac{5t}{2}} \quad 0 < t < 0.6$$

$$= 0 \quad \text{Otherwise}$$

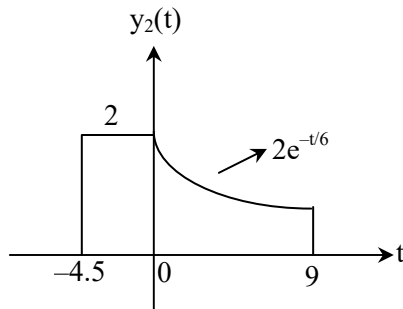(ii) Time expanded by factor '3'.

The resultant signal is  $y_2(t) = x(t/3)$



$$y_2(t) = 2 \quad -4.5 < t < 0$$

$$= 2e^{-t/6} \quad 0 < t < 9$$

$$= 0 \quad \text{Otherwise}$$

**8[a] Find the solution of following second order differential equation by using Transform method. The differential equation is**

$$\frac{d^2 y(t)}{dt^2} + 7 \frac{dy(t)}{dt} + 12y(t) = \frac{dx(t)}{dt} + x(t)$$

**with initial conditions  $y(0^-) = 2$  and  $\dot{y}(0^-) = 1$  and  $x(t) = e^{-5t}u(t)$  and  $x(0^-) = 0$**

**[20M]**

**Solution:**

$$\text{Given} \quad \frac{d^2 y(t)}{dt^2} + 7 \frac{dy(t)}{dt} + 12y(t) = \frac{dx(t)}{dt} + x(t)$$

$$\Rightarrow y''(t) + 7y'(t) + 12y(t) = x'(t) + x(t)$$

$$L\{y''(t)\} + 7L\{y'(t)\} + 12L\{y(t)\} = L\{x'(t)\} + L\{x(t)\}$$

$$\Rightarrow \{s^2 y(s) - sy(0^-) - y'(0^-)\} + 7\{sy(s) - y(0^-)\} + 12y(s) = sx(s) - x(0^-) + x(s) \dots\dots (1)$$

$$L\{x(t)\} = L\{e^{-5t}u(t)\} = \frac{1}{s+5}$$

$$x(s) = \frac{1}{s+5}$$

$$(1) \Rightarrow (s^2 y(s) - 2(s) - 1) + 7\{sy(s) - 2\} + 12y(s) = \frac{s}{s+5} + \frac{1}{s+5}$$

$$\Rightarrow (s^2 + 7s + 12)y(s) - 2s - 1 - 14 = \frac{s+1}{s+5}$$

$$\Rightarrow (s^2 + 7s + 12)y(s) = (2s + 15) + \frac{s+1}{s+5}$$

$$\Rightarrow (s+3)(s+4)y(s) = 2s + 15 + \frac{s+1}{s+5}$$

$$\Rightarrow y(s) = \frac{2s+15}{(s+3)(s+4)} + \frac{s+1}{(s+3)(s+4)(s+5)} \quad \dots\dots\dots (2)$$

$$\frac{2s+15}{(s+3)(s+4)} = \frac{A}{s+3} + \frac{B}{s+4}$$

$$A = \frac{2(-3)+15}{(-3+4)} = 9$$

$$B = \frac{2(-4)+15}{(-4+3)} = -7$$

$$\frac{2s+15}{(s+3)(s+4)} = \frac{9}{s+3} + \frac{7}{s+4}$$

$$\text{Now, } \frac{s+1}{(s+3)(s+4)(s+5)} = \frac{A}{s+3} + \frac{B}{s+4} + \frac{C}{s+5}$$

$$A = \frac{-3+1}{(-3+4)(-3+5)} = -1$$

$$B = \frac{-4+1}{(-4+3)(-4+5)} = 3$$

$$C = \frac{-5+1}{(-5+3)(-5+4)} = -2$$

$$\frac{s+1}{(s+3)(s+4)(s+5)} = \frac{-1}{s+3} + \frac{3}{s+4} - \frac{2}{s+5}$$

Substituting in eqn. (2)

$$y(s) = \frac{9}{s+3} + \frac{7}{s+4} - \frac{1}{s+3} + \frac{3}{s+4} - \frac{2}{s+5}$$

$$y(s) = \frac{8}{s+3} + \frac{10}{s+4} - \frac{2}{s+5}$$

$$L^{-1}\{y(s)\} = L^{-1}\left(\frac{8}{s+3} + \frac{10}{s+4} - \frac{2}{s+5}\right)$$

$$y(t) = 8e^{-3t} + 10e^{-4t} - 2e^{-5t}$$

**8[b] The open-loop transfer function of a unity feedback system is given as**

$$G(s) = \frac{10}{(s-1)(s+5)}$$

**Sketch the Bode plot for the system and calculate Gain and Phase margins**

**[20M]**

**Solution:**

$$G(s) = \frac{10}{(s-1)(s+5)}, \quad H(s) = 1$$

$$G(s) = -\frac{2}{(1-s)\left(1+\frac{s}{5}\right)}$$

Corner frequencies are (1, 5) rad/sec

$$s \rightarrow j\omega \Rightarrow G(j\omega) = \frac{-2}{(1-j\omega)\left(1+\frac{j\omega}{5}\right)}$$

Magnitude:

$$|G(j\omega)| = \frac{2}{\sqrt{1+(\omega)^2} \sqrt{1+\left(\frac{\omega}{5}\right)^2}} \Rightarrow M(\text{dB}) = 20\log|G(j\omega)|$$

$$\Rightarrow M_{\omega=0.1} = 20\log 2 \approx 6\text{dB}$$

Phase:

$$\Rightarrow \angle G(j\omega) = \frac{\angle -2}{\angle(1-j\omega)\angle(1+j\omega/5)}$$


$$\angle \phi = \angle G(j\omega) = -180^\circ - (-\tan^{-1}(\omega) - \tan^{-1}(\omega/5))$$

$$\angle \phi = -180^\circ + \tan^{-1}(\omega) + \tan^{-1}\left(\frac{\omega}{5}\right) \Rightarrow \phi|_{\omega=0.1} = -175^\circ$$

$$\phi|_{\omega=1} = 146^\circ$$

$$\phi|_{\omega=1.6} = -140^\circ$$



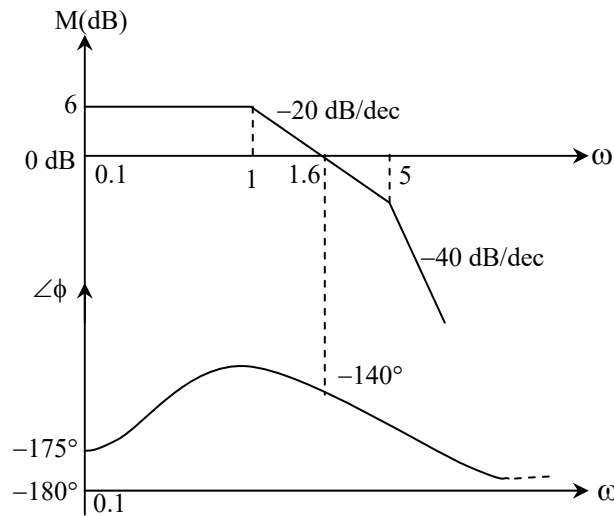

From Plot,

$$\Rightarrow \omega_{pc} = \infty$$

$$M(dB)|_{\omega_{pc}} = -\infty \text{ dB}$$

$$GM = -20 \log(M)|_{\omega_{pc}} = -(M(dB))|_{\omega_{pc}} = -(-\infty) = \infty \text{ dB}$$

$$\Rightarrow \omega_{gc} = 1.6 \text{ rad/sec}$$

$$\Rightarrow PM = 180^\circ + \angle \phi|_{\omega_{gc}}$$

$$\Rightarrow PM = 180^\circ + \left[ -180^\circ + \tan^{-1}(\omega_{gc}) - \tan^{-1}\left(\frac{\omega_{gc}}{5}\right) \right]$$

$$PM = \tan^{-1}(1.6) - \tan^{-1}\left(\frac{1.6}{5}\right)$$

$$PM = +40^\circ$$

**8[c] Design a UJT triggering circuit for a 220 V, 50 Hz ac source fed single phase half controlled rectifier using BT 151 – 500 R SCR and 2N2646 UJT having following parameters:**

**2N2646 UJT:  $\eta = 0.65$ ,  $R_{BB} = 7 \text{ k}\Omega$ ,  $I_P = 5 \text{ }\mu\text{A}$ ,  $V_V = 3 \text{ V}$ ,  $I_V = 4 \text{ mA}$**

**BT 151 – 500 R SCR:  $V_{GT} = 0.8 \text{ V}$  (typical),  $1.5 \text{ V}$  (max)**

**$I_{GT} = 5 \text{ mA}$  (typical,  $15 \text{ mA}$ )**

**$V_{DRM} = 500 \text{ V}$**

**Assume the triggering circuit be fed from 24 V DC**

**Take  $V_{BB}$  of 20 V for design and pulse width of triggering pulse of  $30 \text{ }\mu\text{s}$ . Draw relevant circuits and show the component values with power ratings** **[20M]**

**Solution:**


Given,

UJT:  $\eta = 0.65$ ,  $R_{BB} = 7 \text{ k}\Omega$ ,  $I_P = 5 \text{ }\mu\text{A}$ ,  $V_V = 3 \text{ V}$ ,  $I_V = 4 \text{ mA}$

SCR:  $V_{GT} = 0.8 \text{ V}$

$I_{GT} = 5 \text{ mA}$

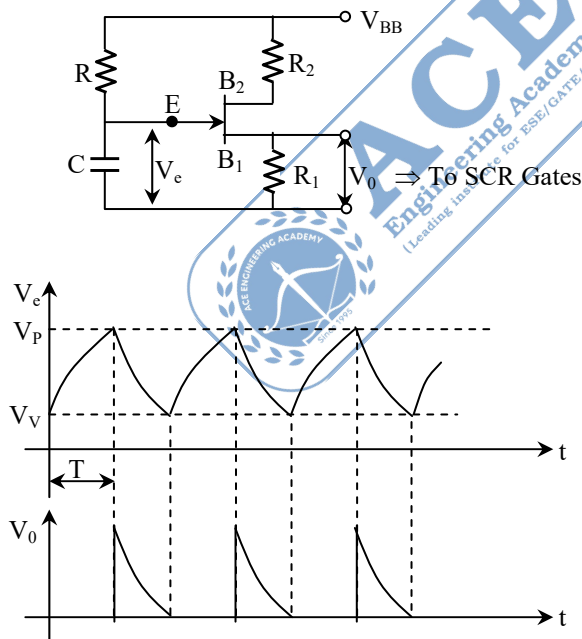$V_{BB} = 20 \text{ V}$ ,  $T = 30 \text{ }\mu\text{sec}$



$$V_P = \eta V_{BB} + V_D$$

Assume  $V_D = 0 \text{ V}$

$$\therefore V_P = \eta V_{BB} = 0.65 \times 20 = 13 \text{ V}$$

$$R_2 = \frac{10^4}{\eta \cdot V_{BB}} = \frac{10^4}{0.65 \times 20} = 769.23 \, \Omega$$

$$\frac{V_{BB} \cdot R_1}{(R_{BB} + R_1 + R_2)} < V_{GT}$$

$$\frac{20 \times R_1}{(7000 + R_1 + 769.23)} < 0.8$$

$$\therefore 20R_1 < 0.8(7000 + R_1 + 769.23)$$

$$\frac{20R_1}{0.8} < (7000 + R_1 + 769.23)$$

$$25R_1 < (7769.23 + R_1)$$

$$24R_1 < 7769.23$$

$$\therefore R_1 < \frac{7769.23}{24}$$

$$\therefore R_1 < 323.71 \, \Omega$$

Maximum value of 'R' is

$$R_{\max} = \frac{V_{BB} - V_P}{I_P} = \frac{20 - 13}{5 \times 10^{-6}} = 1.4 \, \text{M}\Omega$$

Minimum value of 'R' is


$$R_{\min} = \frac{V_{BB} - V_V}{I_V} = \frac{2 - 3}{4 \times 10^{-3}} = 4.25 \, \text{k}\Omega$$

Taking  $R = R_{\min} = 4.25 \, \text{k}\Omega$

$$R = \frac{T}{C \cdot \ln \left[ \frac{1}{1 - \eta} \right]}$$

$$4.25 \times 10^3 = \frac{30 \times 10^{-6}}{C \cdot \ln \left[ \frac{1}{1 - 0.65} \right]}$$
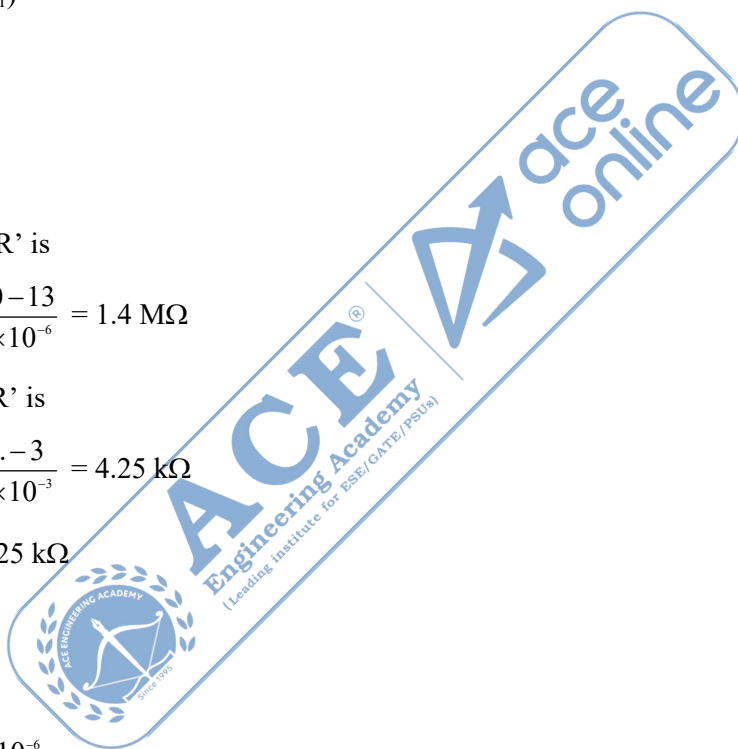
$$\therefore C = 6.72 \times 10^{-9} \, \text{F}$$



## FOLLOW US ON **SOCIAL MEDIA**



### WHY SHOULD YOU FOLLOW OUR SOCIAL MEDIA PLATFORMS?

- **Expert Guidance:** Access tips and strategies from experienced mentors.
- **Content:** Get exclusive notes, questions, and mock tests.
- **Interactive Learning:** Participate in live doubt-solving sessions and quizzes.
- **Exam & Job Updates:** Stay updated with the latest notifications and news.
- **Community Support:** Connect with peers and share resources.
- **Free:** All benefits are absolutely free!

**JOIN US NOW AND BOOST YOUR EXAM PREPARATIONS!**