



ESE – 2025

MAINS EXAMINATION

QUESTIONS WITH DETAILED SOLUTIONS

ELECTRONICS & TELECOMMUNICATION ENGINEERING

(Paper-1)

ACE Engineering Academy has taken utmost care in preparing the **ESE-2025** Examination solutions. Discrepancies, if any, may please be brought to our notice. ACE Engineering Academy do not owe any responsibility for any damage or loss to any person on account of error or omission in these solutions. ACE Engineering Academy is always in the fore front of serving the students, irrespective of the examination type (**GATE/ESE/IRMS/SSC/RRB/PSUs/PSC/GENCO/TRANSCO etc.,**).

All Queries related to **ESE-2025** Solutions are to be sent to the following email address **help@ace.online**

ELECTRONICS & TELECOMMUNICATION ENGINEERING

ESE MAINS 2025 PAPER – I


Questions with Detailed Solutions

SUBJECT WISE WEIGHTAGE

S.No	NAME OF THE SUBJECT	Marks
01	BASIC ELECTRICAL ENGINEERING	20
02	BASIC ELECTRONICS ENGINEERING	32
03	MATERIALS SCIENCE	54
04	ELECTRONIC MEASUREMENTS & INSTRUMENTATION	72
05	NETWORK THEORY	124
06	ANALOG ELECTRONICS	106
07	DIGITAL ELECTRONICS	52
08	CONTROL SYSTEMS	20
Total Marks		480


SECTION - A

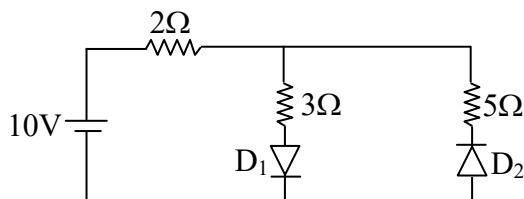01. (a) Find the current flowing in the circuit as given in the figure, where two ideal diodes are connected in parallel :



(12 M)

Sol:

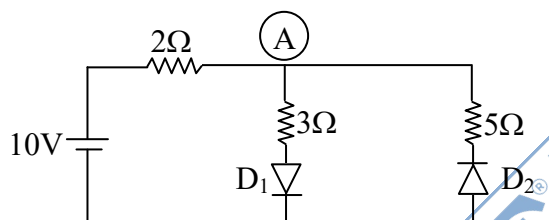

Very Clear $\rightarrow D_1$ ON

D_2 OFF

$$\Rightarrow \frac{10 - V_A}{2} = \frac{1V_A - 0}{3} \Rightarrow V_A = 6V$$

$$\Rightarrow I_{D1} = I_{3\Omega} = \frac{6 - 0}{3} = 2 \text{ Amp}$$

$$I_{D2} = I_{5\Omega} = 0$$

$$\therefore I_{2\Omega} = \frac{10 - V_A}{2} = 2 \text{ Amp}$$

ONLINE



PROGRAMMES OFFERED



Self-Paced Learning Program

Immerse yourself in a personalized and enriching learning experience, with high-quality video content delivered by India's most esteemed and highly accomplished faculty members.

Enjoy the freedom of unlimited access, allowing you to study at your convenience from any location. Take advantage of complimentary live doubt clearing sessions and an extensive online test series to elevate your exam readiness.



LIVE

Exclusive Online Live Classes

Engage in our exclusive live classes, offering an interactive learning experience from any location nationwide. Benefit from real-time guidance and the opportunity to resolve doubts directly with our esteemed faculty. Additionally, access recorded videos of the live sessions for convenient review before exams or to catch up on missed classes at your own pace.

0%
No-Cost
EMI
Available

ESE | GATE | PSUs | SSC | RRB & 30+ Other Exams

Streams: **CE | ME | EE | EC | CS | IN | DA**



Experienced
Faculty



Ask an
Expert



Live Doubt
Clearance




Learn with
2D & 3D
Animations



Free Online
Test Series



Full Set of
Study Material

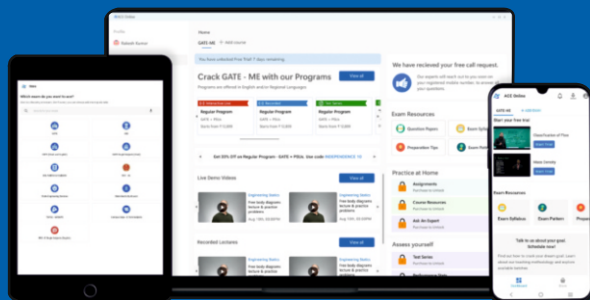

Scan QR
& start your
**7-DAY
Free Trial!**



Download on the
App Store

Get it on
Google play

Download on the
Windows Store

01. (b) A certain d.c. motor has $R_A = 1.3 \Omega$, $I_A = 10 \text{ A}$, and produces a back e.m.f. $E_A = 240 \text{ V}$, while operating at a speed of 1200 r.p.m. Determine the voltage applied to the armature, the developed torque and the developed power. (12 M)

Sol: DC Motor:

$$R_a = 1.3 \Omega; I_a = 10 \text{ A}$$

$$E_b = 240 \text{ V}, N = 1200 \text{ rpm}$$

$$V = E_b + I_a R_a = 240 + 10(1.3) = 253 \text{ V}$$

Torque developed

$$T = 9.55 \left(\frac{E_b I_a}{N} \right)$$

$$T = 9.55 \left(\frac{240 \times 10}{1200} \right) = 19.1 \text{ N-m}$$

$$P_{\text{developed}} = E_b I_a = 240 \times 10 = 2400 \text{ W}$$

01. (c) Consider a unit cell of simple cubic structure. Find the angle between the normals to pair of planes whose Miller indices are (i) $[1 \ 0 \ 1]$ and $[0 \ 1 \ 0]$, and (ii) $[2 \ 1 \ 1]$ and $[1 \ 0 \ 1]$. (12 M)

Sol: Given data, simple cubic structure

The angle between two crystallographic plane

$$\cos \theta = \frac{h_1 h_2 + k_1 k_2 + l_1 l_2}{\sqrt{h_1^2 + k_1^2 + l_1^2} \sqrt{h_2^2 + k_2^2 + l_2^2}}$$

(i) $[1 \ 0 \ 1]$ and $[0 \ 1 \ 0]$

$$\cos \theta = \frac{(1)(0) + (0)(1) + (1)(0)}{\sqrt{1^2 + 0^2 + 1^2} \sqrt{0^2 + 1^2 + 0^2}} = 0$$

$$\theta = 90^\circ$$

(ii) $[2 \ 1 \ 1]$ and $[1 \ 0 \ 1]$


$$\cos \theta = \frac{(2)(1) + (1)(0) + (1)(1)}{\sqrt{2^2 + 1^2 + 1^2} \sqrt{1^2 + 0^2 + 1^2}} = \frac{2+1}{\sqrt{6} \cdot \sqrt{2}} = \frac{3}{\sqrt{12}}$$

$$\cos \theta = \frac{3}{\sqrt{3} \cdot 2} = \frac{\sqrt{3}}{2}$$

$$\theta = 30^\circ$$


01. (d) For the circuit shown in the figure, calculate the value of the voltage V which gives

$V_0 = 5\angle 0^\circ$ volts:

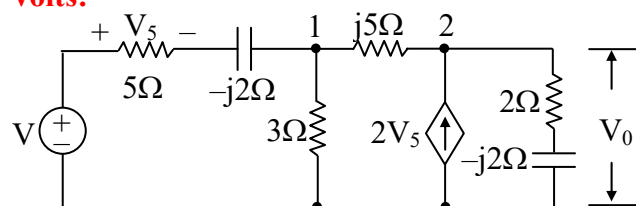

(12 M)

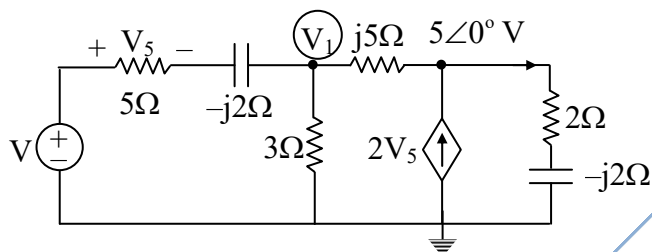Sol: Since given $V_0 = 5\angle 0^\circ$ V, then



Using Nodal Analysis

$$\frac{[V_1 - V]}{(5 - j2)} + \frac{V_1}{3} + \frac{[V_1 - 5]}{j5} = 0$$

$$\frac{[V_1 - V][5 + j2]}{29} + \frac{V_1}{3} + \frac{-j[V_1 - 5]}{5} = 0$$

$$\frac{[V_1 - V][75 + j30] + 145V_1 - j87[V_1 - 5]}{29 \times 3 \times 5} = 0$$

$$75V_1 + j30V_1 - 75V - j30V + 145V_1 - j87V_1 + j435 = 0$$

$$V_1[220 - j57] - V[75 + j30] = -j435 \quad \text{---- (1)}$$

Also Voltage division Rule

$$V_5 = [V - V_1] \left[\frac{5}{5 - j2} \right]$$

$$V_5 = [V - V_1] \left[\frac{25 + j10}{29} \right] \quad \text{---- (2)}$$

Also KCL

$$\frac{[V_1 - 5]}{j5} + 2V_5 = \frac{5}{(2 - j2)}$$

$$\frac{-j[V_1 - 5]}{5} + 2V_5 = \frac{5}{2 - j2} \times \frac{2 + j2}{2 + j2} = \frac{5}{8}[2 + j2]$$

$$2V_5 = \frac{[10 + j10]}{8} + \frac{j[V_1 - 5]}{5}$$

$$V_5 = \frac{5 + j5}{8} + \frac{j[V_1 - 5]}{10} \quad \text{---- (3)}$$

Sub (3) in (2)

$$\left[\frac{5 + j5}{8} \right] + \frac{j[V_1 - 5]}{10} = [V - V_1] \left[\frac{25 + j10}{29} \right]$$

$$\left[\frac{5 + j5}{8} \right] + \frac{jV_1}{10} - \frac{j5}{10} = V \left[\frac{25 + j10}{29} \right] - V_1 \left[\frac{25 + j10}{29} \right]$$

$$V_1 \left[\frac{j}{10} + \frac{25 + j10}{29} \right] - V \left[\frac{25 + j10}{29} \right] = \frac{j}{2} - \frac{[5 + j5]}{8}$$

$$V_1 \left[\frac{j29 + 250 + j100}{10 \times 29} \right] - \frac{V[25 + j10]}{29} = \frac{j8 - 10 - j10}{2 \times 8}$$

$$V_1 \left[\frac{250}{290} + \frac{j129}{290} \right] - V \left[\frac{25}{29} + j \frac{10}{29} \right] = \left[\frac{-5}{8} - \frac{j}{8} \right]$$

$$V_1[0.862 + j0.445] - V[0.862 + j0.345] = [-0.625 - j0.125] \quad \text{---- (4)}$$

Now solve (1) & (4)

$$(1) \times [0.862 + j0.445]$$

$$[215 + j48.766]V_1 - [51.3 + j59.235]V = [193.575 - j374.97] \quad \text{---- (5)}$$

$$(4) \times [220 - j57]$$

$$[215 + j48.766]V_1 - [209.3 + j26.766]V = [-144.625 + j8.125] \quad \text{---- (6)}$$

$$(5) - (6)$$

$$[158 - j32.469]V = [338.2 - j383.0]$$

OFFLINE



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



Classroom Coaching **@ Kothapet & Abids, Hyd**

GATE | PSUs -2026

06th Aug 2025

21st Aug 2025

Achievers Batches TARGET - 2027

06th Aug 2025

03rd Sep 2025

Foundation Batch TARGET - 2028

03rd Sep 2025

SPECIAL CONCESSIONS

Available for IITs/NITs/IIITs & Govt. College Students

50% Concession for ACE old students



📍 **Kothapet Address: 2nd Floor, BAHETI SPECTRUM, Beside: Kinara Grand, Near Victoria Memorial Metro Station, Metro Pillar No: CHPNP-32, 33, Margadarshi Colony, Kothapet, Hyderabad, Telangana – 500035.**

📍 **Abids Address: #3rd Floor, Suryalok Complex, Rosary Convent School Road, Gun Foundry, Basheer Bagh, Hyderabad, Telangana – 500001.**


Finally

$$V = \frac{[338.2 - j383]}{[158 - j32.469]}$$

$$V = [2.532 - j1.904]$$

$$V = 3.2 \angle -37.46^\circ \text{ V}$$

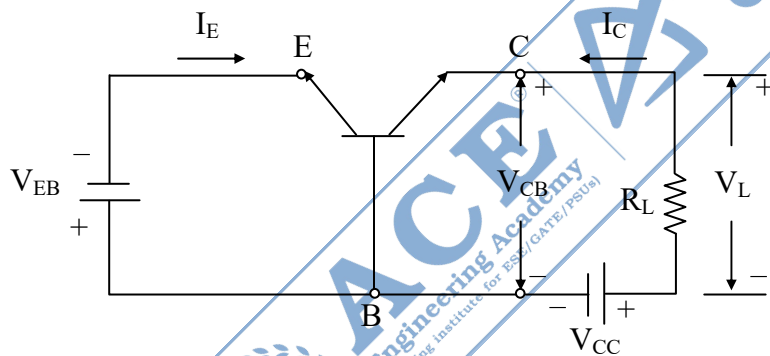01. (e) Shown below is an n-p-n transistor biased in the active region :



Assume that the emitter is much more heavily doped than the base.

- (i) Plot the potential variation across the emitter and collector junction**
- (ii) Plot the minority carrier concentration in each section of the transistor**
- (iii) Show how this transistor configuration works as an amplifier**
- (iv) Plot the collector current against base to emitter voltage for a silicon transistor when it is varied from -0.4 V to $+0.8 \text{ V}$. Indicate the cutoff, active and saturation regions.**
- (v) From the transistor characteristics, write the analytical expressions for the collector current and the emitter current.**
- vi) Show how these equations are used to replace the n-p-n transistor with two back diodes in shunt with two dependent current Sources.**

(12 M)

Sol:

- (i) Since $[E-B]_J$ is f, biased $\Rightarrow (V_0)_{EB_J}$ is low ($\cong 0.6V \rightarrow 0.8V$)


Also base is light doping than emitter and thin base

\Rightarrow Potential is nearly uniform (or) has only a slight slope as concentration of carriers is changing slowly

Also as base collector junction is Reverse biased

\Rightarrow Potential increases sharply at B.C junction (depletion region).

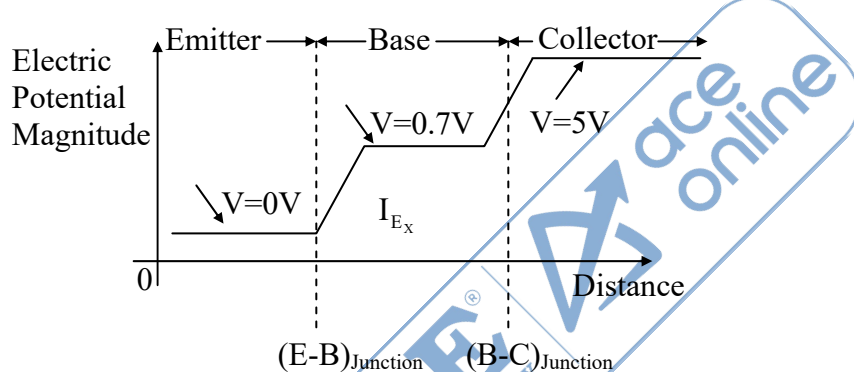Hence, variation of potential across n-p-n transistor (active region)




IF $V_E \rightarrow$ Grounded

$\Rightarrow V_{BE} = 0.7V \Rightarrow V_B = 0.7V$ (F. bias)

If $V_C = 5V \Rightarrow V_{CB} = V_C - V_B = 4.3V$ (R.Bias)

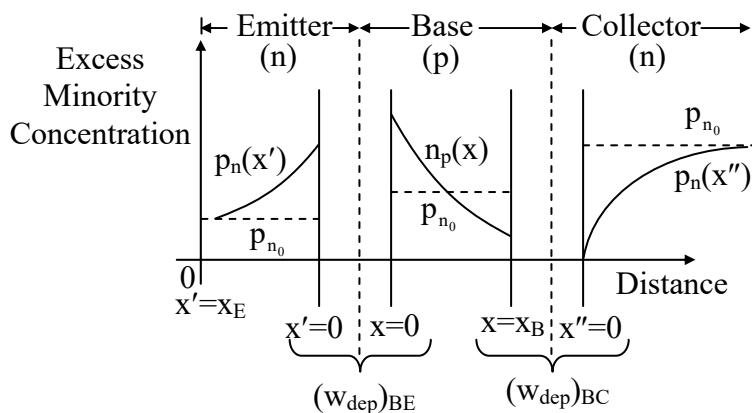- (ii) Minority (or) excess minority carrier profile in forward active \rightarrow



(iii) Clearly given npn transistor,

$$\left. \begin{aligned} (E-B)_J &\rightarrow \text{F.Bias} \\ (C-B)_J &\rightarrow \text{R.Bias} \end{aligned} \right\} \text{F.Active}$$

↓

Small AC signal + DC bias applied at the BE

↓

Small V_{BE} change will give large I_C change [$\because I_C = \beta_F I_B$]

↓

Due to E_J F.bias and C_J R.Bias \Rightarrow most of injected electrons from E reach B then to collector,

$$\alpha_{dc} = \alpha_F = \gamma \beta^{**}$$

↓

Now as $V_L = I_C R_L$, where as $V_C = V_{CC} - V_L$

\Rightarrow Output voltage at the collector varies in the opposite phase $\Rightarrow 180^\circ$ phase shift if input is given at the base.

↓

Now transistor produces as voltage gain,

$$A_v \cong \frac{-\beta R_L}{r_e}$$

$$\text{Where } r_e \cong \frac{26\text{mV}}{I_{EQ}}$$

Hence the above flow chart gives an idea that how above design could be used for amplification.

(iv) Let $I_S \cong 10^{-15} \text{ A}$

$$V_T = 26\text{mV}$$


$$\beta_F = 100 \text{ and } V_{CC} = 5\text{V}$$

$$R_L = 2\text{k}$$

$$\Rightarrow (V_{CE})_{\text{sat}} = 0.2\text{V}$$

$$I_{C_{\text{max}}} = \frac{5 - 0.2}{2000} \cong 2.4 \times 10^{-3} \text{ amp}$$

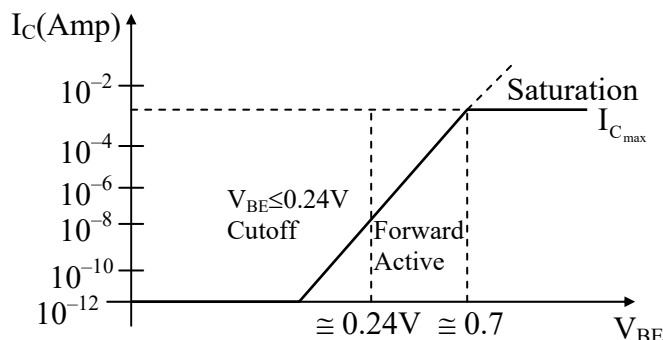Since $I_C \cong \beta I_S \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] + I_{CE0}$



Under cutoff only leakage currents pass in the device

Under active region, the step nearly straight line on a log plot, where transistor acts as an amplifier.

In saturation I_C cannot grow beyond, it is limited by supply and resistor.

(v) As active mode $\Rightarrow I_C = \beta_F I_B + I_{CEO}$ (or) $I_C = \alpha_{FE} I_E + I_{CBO}$

Also, $I_C = I_{C0} \exp\left(\frac{V_{BE}}{V_T}\right) \rightarrow$ by Ebers-Moll equation

$I_C = I_{C0} \exp\left(\frac{V_{BE}}{V_T}\right) (1 + \lambda V_{CE}) \rightarrow$ In C.Emitter

$I_C = I_{C0} \exp\left(\frac{V_{BE}}{V_T}\right) (1 + \lambda V_{CB}) \rightarrow$ In C.Base

With early effect.

As $I_E = I_B + I_C$ and $I_B = \frac{I_C}{\beta_F} \Rightarrow I_E = I_C \left(1 + \frac{1}{\beta_F} \right)$

\Rightarrow without early effect,


$I_E = I_{C0} \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{1}{\beta_F} \right)$

With early effect,

$$I_E = I_{C_0} \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{1}{\beta_F}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

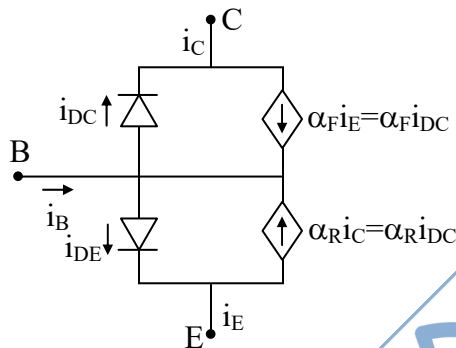(vi) Since two diodes connected back to back is ebers moll model

$\alpha_F I_{SE} = I_S = \alpha_R I_{SC}$ where $I_S \rightarrow 10^{-12}$ to 10^{-18} Amp



KCL at the E $\rightarrow i_E = i_{DE} - \alpha_R i_C$, where $i_{DE} = i_{SE} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right]$
 $i_{DC} = i_{SC} \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right]$

$$\begin{aligned} \therefore i_E &= i_{SE} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - i_{SC} \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right] \alpha_R \\ &= \frac{I_S}{\alpha_F} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\alpha_R} \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right] \alpha_R \\ \therefore i_E &= \frac{I_S}{\alpha_F} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - I_S \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right] \text{----- (1)} \end{aligned}$$

For forward active, $V_{BE} = (+) V_e$, $V_{BC} = (-) V_e$

$$\therefore i_E = \frac{I_S}{\alpha_F} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] + I_S$$

$$\therefore I_E = \frac{I_S}{\alpha_F} \exp\left[\frac{V_{BE}}{V_T}\right] - \frac{I_S}{\alpha_F} + I_S$$

$$\therefore I_E = \frac{I_S}{\alpha_F} \exp\left[\frac{V_{BE}}{V_T}\right] + I_S \left(1 - \frac{1}{\alpha_F}\right)$$

$$\alpha_F \rightarrow 0.95 \rightarrow 0.98$$

$$\alpha_R \rightarrow 0.01 \rightarrow 0.5$$

$$\beta_F \rightarrow 49 \rightarrow 300$$

$$\beta_R \rightarrow 0.01 \rightarrow 1$$

KCL at the C \rightarrow


$$i_C = \alpha_F I_{DE} - i_{DC}$$

$$= \alpha_F \cdot \frac{I_S}{\alpha_F} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\alpha_R} \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right]$$

$$\therefore i_C = I_S \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\alpha_R} \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right] \quad (2)$$

At the forward active, $V_{BE} = (+)Ve$, $V_{BC} = (-)Ve$
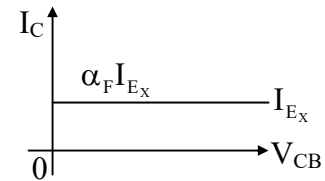
$$\Rightarrow i_C = I_S \exp\left[\frac{V_{BE}}{V_T}\right] + I_S \left[\frac{1}{\alpha_R} - 1 \right] \Rightarrow 'I_C' \text{ is independent of } V_{BC}.$$



Commonly neglected as I_S is very very small

* Now in sat region,

$$V_{CB} = (-)Ve \Rightarrow C B_J \rightarrow F_B \rightarrow V_{CB} \text{ knee} = 0.4V \rightarrow 0.5V$$

\Rightarrow from (2),

$$i_C = I_S \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - \left[\frac{I_S}{\alpha_R} \right] \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right]$$

$$\therefore i_C \approx I_S \exp\left(\frac{V_{BE}}{V_T}\right) - \left[\frac{I_S}{\alpha_R} \right] \left[\exp\left(\frac{V_{BC}}{V_T}\right) - 1 \right]$$

As $V_{BC} \uparrow \uparrow$ at the $V_{BE} = \text{constant} \rightarrow i_C \downarrow \downarrow$ exponentially in SAT region.

$$\therefore i_{C_{SAT}} < i_{C_{F.Active}} \Rightarrow i_{C_{SAT}} < \alpha_F i_E.$$

ONLINE



Upcoming Live Batches

GATE | PSUs -2026

06th Aug 2025

21st Aug 2025

Achievers Batches TARGET - 2027

06th Aug 2025

21st Aug 2025

Foundation Batch TARGET - 2028

03rd Sep 2025



**Experienced
Faculty**



**Ask an
Expert**



**Live Doubt
Clearance**



**Online
Test Series**




**Full Set of
Study Material**

- Freedom of Unlimited Access
- No-Cost EMI Available
- Backup Recorded Sessions

SPECIAL CONCESSIONS

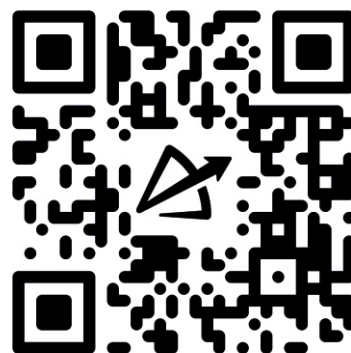Available for: IITs/NITs/IIITs & Govt. College Students
25% Off for ACE old students



Scan QR Code for more details

02. (a) (i) The magnetic field of the earth is approximately 3×10^{-5} T (tesla). At what distance from a long-distance wire carrying a steady current of 10 A is the field equal to 10 percent of the earth's field? Suggest at least two ways to help reduce the effect of electric circuits on the navigation compass in a boat or an airplane. (12 M)

Sol: Given data

$$B = 3 \times 10^{-5} \text{ T}$$

$$I = 10 \text{ A}$$

Magnetic field due to long straight rod

$$B = \frac{\mu_0 I}{2\pi r} \quad B = 10\% \text{ of earth} = 0.1 \times 3 \times 10^{-5} = 3 \times 10^{-6}$$

$$3 \times 10^{-6} = \frac{4\pi \times 10^{-7} \times 10}{2\pi r}$$

$$r = 0.67 \text{ m}$$

Methods of reducing effects on navigation compass

- (1) use magnetic shielding
- (2) Increase physical separation from electrical circuits
- (3) Use twisted wires cancel field

02. (a) (ii) A typical deep cycle battery (used for electric trolling motors for fishing boats) is capable of delivering 12.6 V and 10 A for a period of 10 hours. How much charge flows through the battery in this interval? How much energy does the battery deliver? (8 M)

Sol: $V_d = 12.6 \text{ V}$

$$I_d = 10 \text{ A}$$

$$T_d = 10 \text{ hours}$$

$$Q = I_d T_d = 10 \times 10 = 100 \text{ Ah} = (100 \text{ A}) (3600 \text{ sec}) = 36 \times 10^4 \text{ A sec}$$

$$\begin{aligned} E_d &= V_d I_d T_d \\ &= 12.6 \times 10 \times 10 \\ &= 1260 \text{ Wh} \end{aligned}$$

02. (b) During a laboratory experiment, a student tried to build an inverting amplifier as shown in Fig. (i). The student accidentally reversed the connection of the two input terminals and obtained the circuit of Fig. (ii). The student was greatly surprised that the circuit no longer behaved as expected. Calculate the gain in both the cases and explain the stability of both the circuits. Assume open-loop gain of op-amp as 2×10^5 , $R_i = \infty$, $R_o = 0$ and stray capacitance of 1 pF across the input terminals:

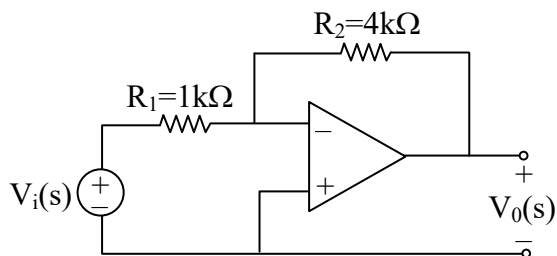


Fig. (i)


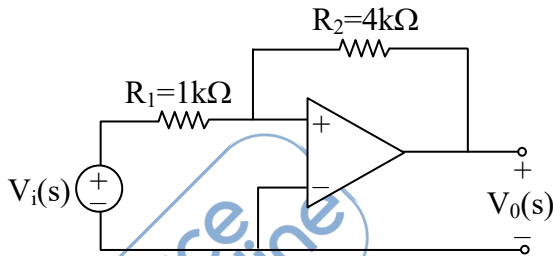


Fig. (ii)

(20 M)

Sol:

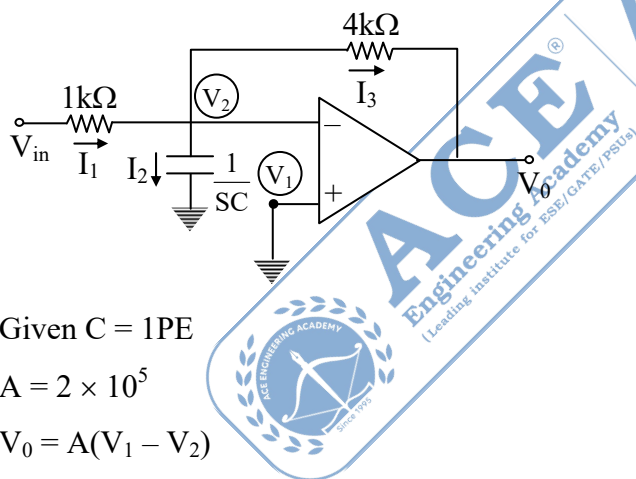

Given $C = 1\text{pF}$

$$A = 2 \times 10^5$$

$$V_0 = A(V_1 - V_2)$$

$$= 2 \times 10^5 (0 - V_2)$$

$$V_0 = -2 \times 10^5 V_2 \quad (1)$$

KCL at the V_2

$$I_1 = I_2 + I_3$$

$$\frac{V_{in} - V_2}{1k} = V_2(SC) + \frac{V_2 - V_0}{4k}$$

$$\frac{4V_{in} - 4V_2}{4k} = \frac{V_2(4k)SC + V_2 - V_0}{4k}$$

$$V_2 (1 + (4k)CS + 4) = 4V_{in} + V_0$$


$$V_2 = \frac{4V_{in} + V_0}{5 + (4k)CS} \quad (2)$$

Sub (2) in (1)

$$V_0 = -2 \times 10^5 \left[\frac{4V_{in} + V_0}{5 + (4k)CS} \right] \quad \because [C = 1\text{pF}]$$

$$\frac{V_0}{V_{in}} = \frac{-8 \times 10^5}{(2 \times 10^5 + 5) + (4k)(1\text{pF})s}$$
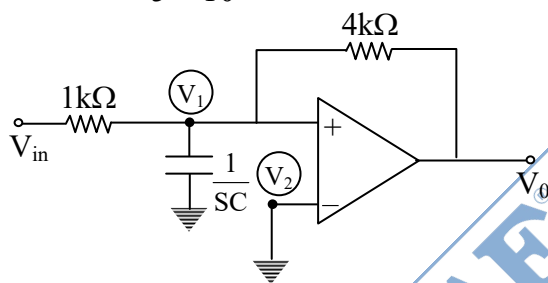
$$\frac{V_0}{V_{in}} = \frac{-4}{1 + \frac{s}{5 \times 10^{13}}} = \frac{k}{1 + s\tau} \quad (\text{low pass filter})$$



$$V_0 = A(V_1 - V_2)$$

$$= 2 \times 10^5 V_1 \quad (3)$$

$$\text{Similarly, } V_1 = \frac{4V_{in} + V_0}{5 + (4k)CS} \quad (4) \text{ from equation (2)}$$

Sub (4) in (3)

$$\frac{V_0}{V_{in}} = \frac{-4}{1 - \frac{s}{5 \times 10^{13}}} = \frac{k}{1 - s\tau}$$

The transfer function in the first case $\frac{k}{1 + s\tau}$ is stable.

But the transfer function is the second case $\frac{k}{1 - s\tau}$ is unstable.

The stability of the feedback system is determined by the location of poles of its closed loop transfer function.

02. (c) The state equation of a linear time-invariant system is expressed by

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} [r(t)]$$

(i) Calculate the state transition matrix.

(ii) Find the state vector $x(t)$ for $t \geq 0$, when $r(t) = u(t)$.

Assume the initial state to be zero.

(10 + 10 = 20 M)

Sol:

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} r(t)$$

$$\Rightarrow A = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \Rightarrow [sI - A] = \begin{bmatrix} s & -1 \\ +1 & s+2 \end{bmatrix}$$

(i) State transition matrix:

$$\phi(t) = e^{At} = L^{-1} \left[[sI - A]^{-1} \right] = L^{-1} \left[\frac{\text{Adj}[sI - A]}{|sI - A|} \right]$$

$$\phi(t) = L^{-1} \begin{bmatrix} \frac{s+2}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s}{(s+1)^2} \end{bmatrix} = L^{-1} \begin{bmatrix} \frac{s+1}{(s+1)^2} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s+1-1}{(s+1)^2} \end{bmatrix}$$

$$\phi(t) = L^{-1} \begin{bmatrix} \frac{1}{s+1} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{1}{s+1} + \frac{-1}{(s+1)^2} \end{bmatrix} = \begin{bmatrix} e^{-t} + te^{-t} & te^{-t} \\ -te^{-t} & e^{-t} - te^{-t} \end{bmatrix}$$

$$\Rightarrow \text{State transition matrix } \phi(t) = \begin{bmatrix} e^{-t} + te^{-t} & te^{-t} \\ -te^{-t} & e^{-t} - te^{-t} \end{bmatrix}$$

(ii) State Vector :

$$x(t) = e^{At} X(0) + L^{-1} [\phi(s) B U(s)]$$

$$X(0) = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \text{ initial condition are zero [given]}$$

$$x(t) = L^{-1} [\phi(s) B U(s)]$$

OFFLINE



Classroom Coaching

- Engaging in classroom coaching provides a transformative and engaging learning experience that deeply encourages interactive student-faculty relationships within an ideal educational environment.
- By participating in our extensive classroom sessions, students not only acquire knowledge but also develop crucial skills and enhanced confidence levels that are pivotal for their success.
- ACE provides classroom coaching by experienced educators to support increased competition and participation in competitive exams.



→ **Smart Classrooms**

→ **Library/Reading Rooms**

→ **Calm Study Environment**

→ **Near to Metro Station**

→ **Centralized AC Classrooms**

→ **No-Cost EMI available**



H.O. @ Abids # 3rd Floor, Suryalok Complex, Rosary Convent School Road, Gun Foundry, Basheer Bagh, Hyderabad, Telangana – 500001.



B.O. @ Kothapet # 2nd floor, BAHETI SPECTRUM, Beside: Kinara Grand, Near Victoria Memorial Metro Station, Pillar No: CHPNP-32, 33, Kothapet, Hyderabad, Telangana.

$$= L^{-1} \left[\begin{bmatrix} \frac{(s+2)}{(s+1)^2} & \frac{1}{(s+1)^2} \\ -1 & s \\ \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} \begin{bmatrix} \frac{1}{s} \end{bmatrix} \right]$$


$$x(t) = L^{-1} \left[\begin{bmatrix} \frac{1}{(s+1)^2} \\ \frac{s}{(s+1)^2} \end{bmatrix} \begin{bmatrix} \frac{1}{s} \end{bmatrix} \right] = L^{-1} \left[\begin{bmatrix} \frac{1}{s(s+1)^2} \\ \frac{1}{(s+1)^2} \end{bmatrix} \right]$$

$$x(t) = L^{-1} \left[\begin{bmatrix} \frac{1}{s} - \frac{1}{s+1} - \frac{1}{(s+1)^2} \\ \frac{1}{(s+1)^2} \end{bmatrix} \right]$$

$$x(t) = \begin{bmatrix} 1 - e^{-t} - te^{-t} \\ te^{-t} \end{bmatrix} \Rightarrow x(t) = \begin{bmatrix} 1 - e^{-t}(1+t) \\ te^{-t} \end{bmatrix}$$

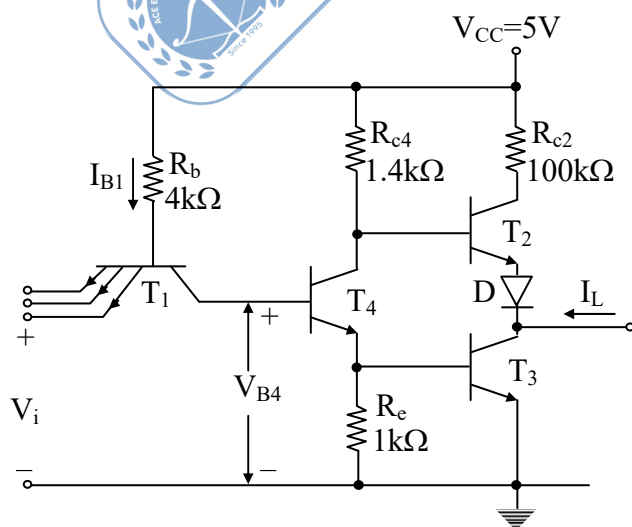
03. (a) Explain the operation of the TTL gate circuit shown below, clearly mentioning the roles of the transistors T_2 and T_4 , and the diode D .

Assume that when all the inputs are at logic 1, the transistors T_3 and T_4 are both in saturation:



(20 M)

Sol:

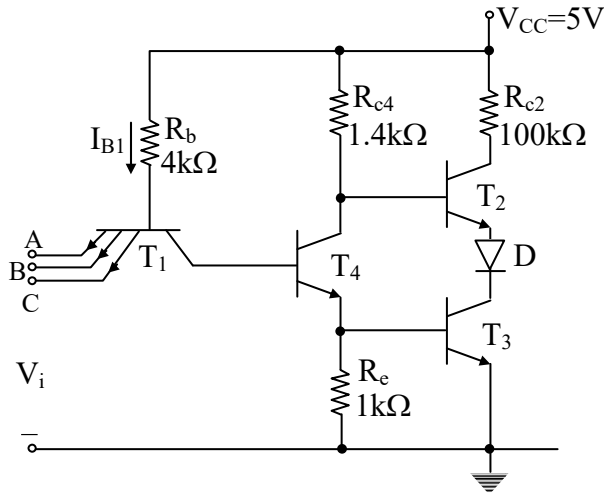

Transistor-transistor logic belongs to the digital logic family. It consists of transistor at both input and output side, diodes and few resistors. Unlike resistor-transistor logic and diode-transistor logic, both the logic function and amplifying function are performed by the transistors. In the given circuit of 3 input TTL NAND gate, it has four transistors T_1 , T_2 , T_3 and T_4 . Transistor T_1 has 3 inputs on the emitter side. Transistors T_2 and T_3 form the output side, called totem pole output.

When all the three inputs A, B and C are low, the three diodes are forward biased. So the current due to the supply $V_{CC} = 5V$ will go to the ground through R_b and it will not be sufficient to turn ON the transistor T_4 , with T_4 open, the transistor T_3 will also cutoff. But the transistor T_2 is pulled high. Since T_2 is an emitter follower, the output will also be HIGH i.e., logic 1.

When any one input is low, the diode with low input will be forward biased. The same operation will take place as explained above. In this case output is high.

When all the inputs A, B and C are HIGH then all the three diodes at the emitter base junction will be reverse biased. The diode at collector base junction is forward biased. It will turn on the transistor T_4 . with T_4 turned ON, transistor T_3 will also be turned ON. So the output will be logic low which is considered as logic 0.

In the circuit shown the transistors T_2 , T_3 , diode D and current limiting resistor R_{C2} from the totem-pole output configuration of TTL.

There are few advantages of this configuration, when the output switches from low the HIGH state, the output transistor T_3 goes from saturation to cutoff. During this transition the load capacitance across T_2 charges exponentially from low to high.

Due to the low output impedance of both T_2 and T_3 , the output voltage can change quickly from Low to HIGH as the capacitance charge and discharge quickly.

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

03. (b) (i) A thermistor, having $\beta = 3100\text{K}$, has a resistance of $1050\ \Omega$ at 20°C .

The thermistor is used for the measurement of temperature and the resistance measured is $2300\ \Omega$. Find the measured temperature if the thermistor is described by

the relation $R = R_0 \exp\left[\beta\left(\frac{1}{T} - \frac{1}{T_0}\right)\right]$ where the symbols have their standard meanings.

(10 M)

(ii) The following are the data for a Hay's bridge :

$R_1 = 1\text{ k}\Omega \pm 1\text{ part in } 10\text{ K}$, $R_2 = 16.8\text{ k}\Omega \pm 1\text{ part in } 10\text{ K}$,

$R_3 = 833 \pm 0.25\ \Omega$, $C = 1.43\ \Omega \pm 0.001\ \mu\text{F}$

The supply frequency is $50 \pm 01\text{ Hz}$ and the bridge's balanced conditions are

$$L = \frac{CR_1R_2}{1 + \omega^2C^2R_3^2} \quad \text{and} \quad R = \frac{R_1R_2R_3C^2\omega^2}{1 + \omega^2C^2R_3^2}$$

Calculate the values of L and R of the coil, and their limits of error.

(10 M)

Sol:

(i) $\beta = 3100\text{K}$

$$R_0 = 1050\ \Omega \text{ at } 20^\circ\text{C} \Rightarrow T_0 = 273 + 20 = 293$$

$$R_t = 2300\ \Omega$$

$$R_t = R_0 e^{\beta\left(\frac{1}{T} - \frac{1}{T_0}\right)}$$

$$\frac{R_t}{R_0} = e^{\beta\left(\frac{1}{T} - \frac{1}{T_0}\right)}$$

$$\ln\left(\frac{R_t}{R_0}\right) = \beta\left(\frac{1}{T} - \frac{1}{T_0}\right)$$

$$\ln\left(\frac{2300}{1050}\right) = 3100\left(\frac{1}{T} - \frac{1}{293}\right)$$

$$2.529 \times 10^{-4} = \frac{1}{T} - \frac{1}{293}$$

$$\frac{1}{T} = 3.6659 \times 10^{-3}$$

$$T = 272.78 \text{ k}$$

(ii) $R_1 = 1000 \pm 0.1 = 1000 \pm 0.01\%$

$$R_2 = 16800 \pm 0.01\%$$

$$R_3 = 833 \pm 0.25 \Omega = 833 \pm 0.03\%$$

$$C = 1.43 \pm 0.001 \mu\text{F} = 1.43 \mu\text{F} \pm 0.07\%$$


$$f = 50 \pm 0.1 \text{ Hz} = 50 \pm 0.2\%$$

$$\begin{aligned} R &= \frac{R_1 R_2 R_3 C^2 \omega^2}{1 + \omega^2 C^2 R_3^2} \\ &= \frac{(1000 \pm 0.01\%)(16800 \pm 0.01\%)(833 \pm 0.03\%)(1.43 \times 10^{-6} \pm 0.07\%)^2 [4\pi^2 (50 \pm 0.2\%)^2]}{1 + 4\pi^2 (50 \pm 0.2\%)^2 (1.43 \times 10^{-6} \pm 0.07\%)^2 (833 \pm 0.03\%)^2} \\ &= \frac{2824.39 \pm 0.59\%}{1 + 0.13998 \pm 0.6\%} \\ &= \frac{2824.39 \pm 0.59\%}{1.13998 \pm 0.0736\%} \\ &= 2477.57 \pm 0.6636\% \\ &= 2477.57 \pm 16.44 \end{aligned}$$

$$\begin{aligned} L_1 &= \frac{CR_1 R_2}{1 + \omega^2 C^2 R_3^2} = \frac{(1.43 \times 10^{-6} \pm 0.07\%)(1000 \pm 0.01\%)(16800 \pm 0.01\%)}{1.13998 \pm 0.0736\%} \\ &= \frac{24 \pm 0.09\%}{1.13998 \pm 0.0736\%} \\ &= 21.05 \pm 0.1636\% \\ &= 21.05 \pm 0.0344 \end{aligned}$$

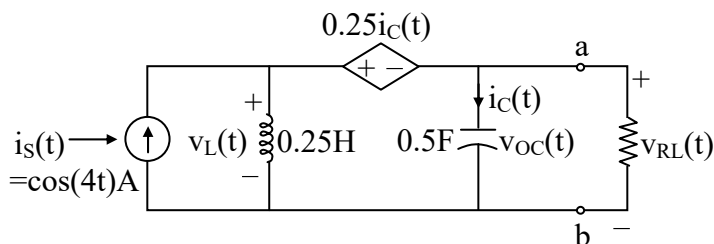
03. (c) Find the Thevenin's equivalent of the circuit shown in the figure if $\omega = 4 \text{ rad/s}$.

Also determine the voltage $V_{R_L}(t)$, when a 1.2Ω load is connected to terminals a-b:



(20 M)

Sol: V_{oc} :

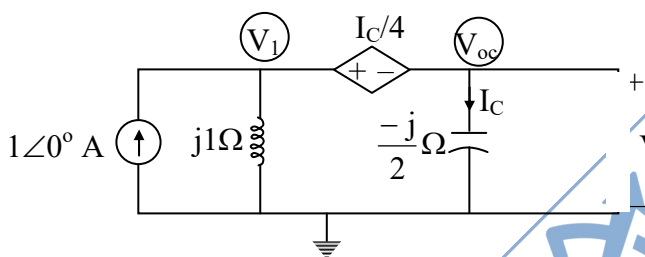

$$-[1\angle 0^\circ] + \frac{V_1}{j1} + \frac{V_{oc}}{-j/2} = 0$$

$$-jV_1 + j2V_{oc} = 1 \quad \text{---- (1)}$$

$$[V_1 - V_{oc}] = \frac{I_c}{4} \quad \text{---- (2)}$$

$$I_c = \frac{V_{oc}}{-j/2} = +j2V_{oc} \quad \text{---- (3)}$$

(3) in (2)

$$V_1 - V_{oc} = +\frac{j2V_{oc}}{4}$$

$$V_1 - V_{oc} = +\frac{j}{2}V_{oc} \quad \text{---- (4)}$$

Equation (4) $\times j$, we get

$$+jV_1 - jV_{oc} = -\frac{V_{oc}}{2} \quad \text{---- (5)}$$


(1) + (5)

$$jV_{oc} = 1 - \frac{V_{oc}}{2} \Rightarrow V_{oc} \left[\frac{1}{2} + j \right] = 1$$


$$V_{oc} = \left[\frac{2}{1 + j2} \right] V = [0.4 - j0.8] V = 0.894 \angle -63.43^\circ V$$

$$= 0.894 \cos(4t - 63.43^\circ) V$$

S-II: I_{sc}

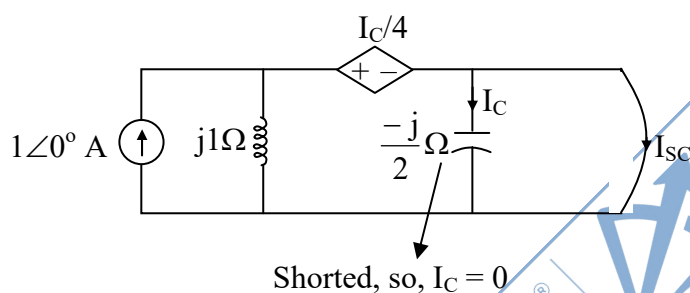


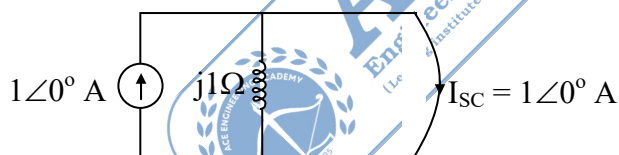Then dependent voltage source is also zero, so short it




$$Z_{TH} = \frac{V_{oc}}{I_{sc}} = \left[\frac{2}{1 + j2} \right] \Omega = [0.4 - j0.8] \Omega$$

Thevenin's Equivalent Circuit becomes

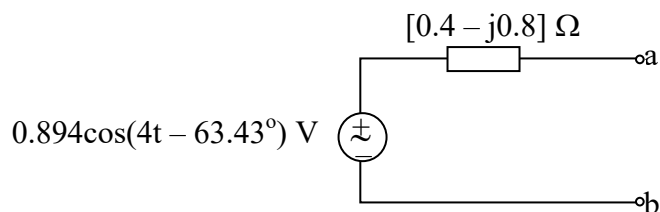

Also

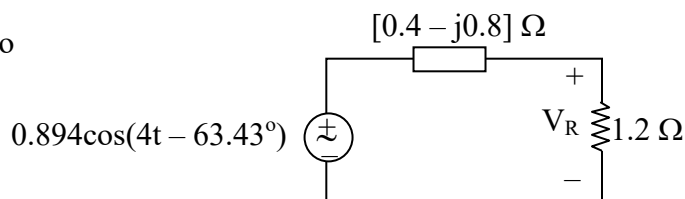

$$V_R = [0.894 \angle -63.43^\circ] \left[\frac{1.2}{1.6 - j0.8} \right]$$

$$V_R = [0.894 \angle -63.43^\circ] [0.6 + j0.3]$$

$$V_R = [0.894 \angle -63.43^\circ] [0.67 \angle 26.56^\circ]$$

$$V_R = 0.6 \angle -36.87^\circ$$

$$V_R = 0.6 \cos(4t - 36.87^\circ) \text{ V}$$

04. (a) Consider that a double-heterojunction LED emitting at a peak wavelength 1400 nm has radiative and non-radiative recombination times of 20 ns and 80 ns respectively. The drive current is 30 mA and the refractive index of the light source material is 3.0. Calculate the power emitted from the device. (20 M)

Sol: Given Peak wave length, $\lambda = 1400 \text{ nm}$

$$\tau_{\text{rad}} = 20 \text{ ns}$$

$$\tau_{\text{non-rad}} = 80 \text{ ns}$$

Drive current, $I = 30 \text{ mA}$

Refractive Index, $n = 3.0$

$$\text{Since internal quantum efficiency, } \eta_e = \theta_e = \frac{\tau_{\text{non-rad}}}{\tau_{\text{rad}} + \tau_{\text{non-rad}}} = \frac{80 \text{ ns}}{20 \text{ ns} + 80 \text{ ns}} = 0.8$$

$$\text{Now, to calculate internal optical power, } P_{\text{internal}} = \eta_e \times I \times \frac{hc}{q\lambda} \cong 11.3 \text{ mW}$$

$$\text{Now emitter power, } P_{\text{Emitted}} = \frac{P_{\text{internal}}}{n^2} = \frac{11.3 \text{ mW}}{(3)^2} = \frac{11.3 \text{ mW}}{9} \cong 1.2 \text{ mW}$$

$$\Rightarrow \text{Power Emitter} \cong 1.2 \text{ mW}$$



ACE Interview Guidance Program

Empowering Job Seekers to Succeed

- Job seekers confront a variety of challenges on their path to securing a job. Our ACE Interview Guidance programme has been carefully designed to provide thorough assistance in overcoming these challenges.
- With a team of seasoned experts at the helm, our focus is on empowering individuals with the intricate skills and extensive knowledge required to fully shine during interviews.
- Whether it's perfecting your presentation strategies or fine-tuning your overall interview skills, we are completely committed to improving your prospects of securing desired positions.
- ACE conducts comprehensive mock interviews with expert panel members, both in person and virtually. These simulations are designed to thoroughly prepare individuals for college admissions or job interviews.

ACE YOUR INTERVIEWS WITH OUR EXPERT GUIDANCE!



Our Social Links



aceonlineprep



aceonlineprep



aceonline



@aceengacademy



aceacademyindia_official

04. (b) A spherical nanoparticle has diameter of 10 nm. Determine the surface area to volume ratio and explain how this property affects the behaviour of nanomaterials compared to bulk materials. (20 M)

Sol: Calculate Surface Area to Volume Ratio

For a sphere:

- **Surface Area** $A=4\pi r^2$
- **Volume** $V=4\pi r^3/3$

So, the surface area to volume ratio is:

$$A/V = 3/r = 3/5\text{nm} = 6 \times 10^8$$

At the nanoscale, the surface area to volume ratio is extremely high. This has significant consequences:

◆ **Increased Reactivity**

- More atoms are exposed at the surface.
- Surface atoms are less tightly bound → more reactive.

◆ **Enhanced Mechanical Properties**

- Higher surface energy contributes to strength and hardness.

◆ **Changes in Electrical & Thermal Properties**

- Electron transport may occur via surface or quantum effects.
- Thermal conductivity can decrease due to boundary scattering.

◆ **Quantum Confinement**

- Electrons are confined in small volumes → changes in optical/electronic properties.
- Example: Quantum dots emitting different colors based on size.

04. (c) (i) A CR tube has an anode-screen distance of 30 cm. The accelerating potential is 1 kV. The tube is placed with its axis vertical. Find the maximum deflection of the spot due to the earth's magnetic field having $B = 0.018 \times 10^{-3} \text{ Wb/m}^2$. (10 M)

Sol: Speed of Electron beam

$$v = \sqrt{\frac{2qV}{m}} = \sqrt{\frac{2ev}{m}} = \sqrt{\frac{2 \times 1.602 \times 10^{-19} \times 1000}{9.1 \times 10^{-31}}}$$

$$v = 1.8755 \times 10^7 \text{ m/s}$$


Radius of curvature of magnitude field

$$r = \frac{mv}{eB} = \frac{9.1 \times 10^{-31} \times 1.8755 \times 10^7}{1.602 \times 10^{-19} \times 1.8 \times 10^{-5}} = 5.92 \text{ } \mu\text{m}$$

The beam follows a circular path of radius of arc length 'L'


$$y = \frac{L^2}{2r} = \frac{(0.3)^2}{2 \times 5.92 \text{ } \mu\text{m}} = 7.6 \text{ mm}$$

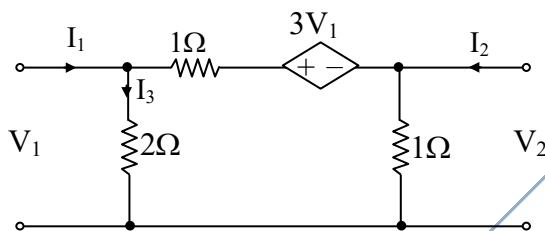04. (c) (ii) Calculate the Y-parameters for the network shown in the figure:



(10 M)

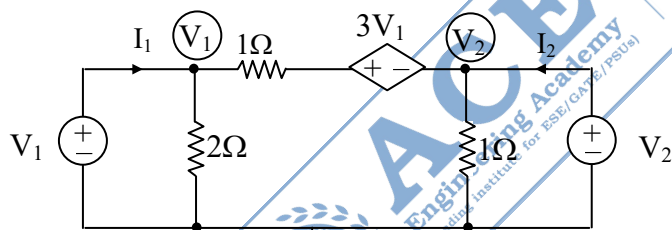Sol: Here for Y-parameters just write Nodal Equations



KCL at V_1

$$-I_1 + \frac{V_1}{2} + \frac{[V_1 - V_2 - 3V_1]}{1} = 0$$

$$-2I_1 + V_1 + 2V_1 - 2V_2 - 6V_1 = 0$$

$$-2I_1 - 3V_1 - 2V_2 = 0$$

$$-2I_1 = 3V_1 + 2V_2$$

$$I_1 = -\frac{3}{2}V_1 - V_2 \quad \text{---- (1)}$$

KCL at (V_2)

$$-I_2 + \frac{V_2}{1} + \frac{(V_2 - V_1 + 3V_1)}{1} = 0$$

$$I_2 = 2V_1 + 2V_2 \quad \text{--- (2)}$$

So, from (1) & (2)

$$I_1 = -\frac{3}{2}V_1 - V_2$$


$$I_2 = 2V_1 + 2V_2$$

$$\text{So, } [Y] = \begin{bmatrix} -\frac{3}{2} & -1 \\ 2 & 2 \end{bmatrix} \mathcal{U}$$

SECTION - B

05. (a) Derive a relation for the value of the capacitor for frequency error compensation of a moving-iron voltmeter in terms of its parameters and the series resistance. (12 M)

Sol:

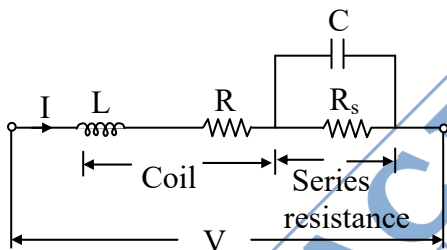

Frequency Compensation for M.I voltmeters

$$\text{Now } Z = j\omega L + \frac{R}{1 + j\omega CR_s} = j\omega L + \frac{R_s - j\omega CR_s^2}{1 + \omega^2 C^2 R_s^2}$$

Since $\omega CR_s \ll 1$, we can write

$$\begin{aligned} Z &= j\omega L + (R_s - j\omega CR_s^2)(1 - \omega^2 C^2 R_s^2) \\ &= j\omega L + R_s - j\omega CR_s^2 - \omega^2 C^2 R_s^3 + j\omega^3 C^3 R_s^4 \\ &= R_s - \omega^2 C^2 R_s^3 + j[\omega L - \omega CR_s^2(1 - \omega^2 C^2 R_s^2)] \\ &= R_s - \omega^2 C^2 R_s^2 + j[\omega L + \omega CR_s^2] \\ &= R_s(1 - \omega^2 C^2 R_s^2)^2 + j\omega(L - CR_s^2) \end{aligned}$$

Or

$$Z^2 = R_s^2(1 - \omega^2 C^2 R_s^2)^2 + \omega^2(L - CR_s^2)^2.$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs

 **ace**
online



Scan QR code for more details

GATE | ESE - 2026

Online Test Series

GATE - 2026

EC | EE | CE | ME | CS | IN | PI | DA

No. of Tests: **54**

+

FREE 54 Tests of
GATE - 2025

Total Tests: **108***

ESE (Prelims) 2026*

EC | EE | CE | ME

No. of Tests: **44**

+

FREE 30 Tests of
ESE (Prelims) 2025

Total Tests: **74***

**Losing Marks To
Poor Time Management?**
Solve with **ACE Test Series**

 **REAL-TIME MOCK TESTS**

 **SMART FEEDBACKS**

 **VIDEO SOLUTIONS**

GATE | ESE | PSUs | SSC | State AE | JE exams

GRAB FLAT

20% OFF

FREEDOM FESTIVAL

from **9th** to **17th** August

This must equal R_s^2 in order that the a.c. calibration at all frequencies and d.c calibration is the same.

$$\begin{aligned}\therefore R_s^2 &= R_s^2(1 - \omega^2 C^2 R_s^2)^2 + \omega^2 (L - C R_s^2)^2 \\ &= R_s^2(1 - 2\omega^2 C^2 R_s^2 + \omega^4 C^4 R_s^4) + \omega^2 (L - C R_s^2)^2 \\ &= R_s^2(1 - 2\omega^2 C^2 R_s^2) + \omega^2 (L - C R_s^2)^2\end{aligned}$$

$$\text{as } \omega^4 C^4 R_s^2 \ll 1$$

$$= R_s^2 - 2\omega^2 C^2 R_s^4 + \omega^2 L^2 + \omega^2 C^2 R_s^4 - 2\omega^2 L C R_s^2$$


$$\text{or } L^2 - 2LCR_s^2 - C^2 R_s^4 = 0 \quad \text{or } L = 2.41 C R_s^2$$

$$\therefore C = \frac{1}{2.41} \frac{L}{R_s^2} = 0.41 \frac{L}{R_s^2}$$

It should be understood that the above analysis is valid for a limited range of frequency which in practical cases is upto 125 Hz.

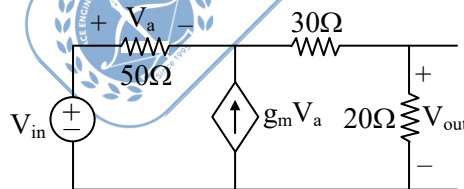
05. (b) For the circuit shown in the figure, find $\frac{V_{out}}{V_{in}}$ in terms of the parameter g_m .

Then find $\frac{V_{out}}{V_{in}}$, when $g_m = 2$:



(12 M)

Sol:

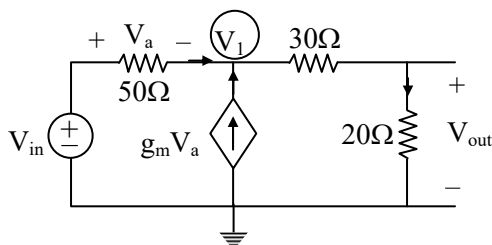

KCL + OHM'S LAW

$$V_{out} = 20 \left[g_m V_a + \frac{V_a}{50} \right]$$

$$V_{out} = 20 V_a \left[g_m + \frac{1}{50} \right] \quad \text{----- (1)}$$

$$\text{Also } V_a = [V_{in} - V_1] \quad \text{----- (2)}$$

$$\text{Also } V_{out} = V_1 \left[\frac{20}{20 + 30} \right] \Rightarrow V_{out} = \frac{2}{5} V_1 \quad \text{----- (3)}$$

Sub (2) in (1)

$$V_{out} = 20 [V_{in} - V_1] \left[g_m + \frac{1}{50} \right] \quad \text{----- (4)}$$

Sub (3) in (4)

$$V_{out} = 20 \left[V_{in} - \frac{5}{2} V_{out} \right] \left[g_m + \frac{1}{50} \right]$$

$$V_{out} = \left[20 V_{in} - 50 V_{out} \right] \left[\frac{50 g_m + 1}{50} \right]$$

$$V_{out} = \left[20 V_{in} \left[\frac{50 g_m + 1}{50} \right] - \left[50 V_{out} \left[\frac{50 g_m + 1}{50} \right] \right] \right]$$

$$V_{out} = \left[\frac{2}{5} V_{in} \right] \left[\frac{50 g_m + 1}{1} \right] - V_{out} [50 g_m + 1]$$

$$V_{out} [1 + 1 + 50 g_m] = \frac{2}{5} V_{in} [50 g_m + 1]$$

$$V_{out} = V_{in} \frac{2}{5} \left[\frac{[50 g_m + 1]}{[50 g_m + 2]} \right]$$

$$\frac{V_{out}}{V_{in}} = \frac{2}{5} \left[\frac{[50 g_m + 1]}{[50 g_m + 2]} \right]$$

if $g_m = 2$


$$\frac{V_{out}}{V_{in}} = \frac{2 [101]}{5 [102]} = 0.4 \times 0.9901$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = 0.396$$

05. (c) For the circuit shown in the figure, all the MOSFETs are identical. Assume

$\mu_n C_{ox} = 0.1 \text{ mA/V}^2$, $V_{tn} = 1 \text{ V}$, $\lambda = 0$ **and** $I_Q = 1 \text{ mA}$. **Calculate** $\frac{W}{L}$ **ratio and voltage gain**

$$A_d = \frac{V_0}{V_{s1} - V_{s2}} :$$

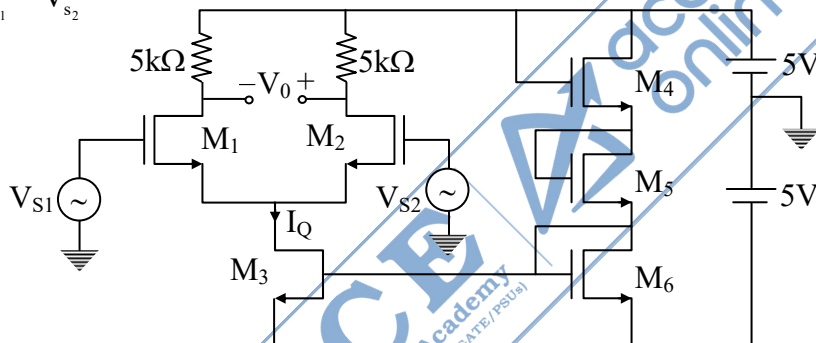

(12 M)

Sol: Given $I_Q = 1 \text{ mA}$ so $I_6 = I_5 = I_4 = 1 \text{ mA} \rightarrow V_{GS6} = V_{GS5} = V_{GS4}$ _____ (1)

$$\mu_n C_{ox} = 0.1 \text{ mA/V}^2$$

$$V_{GS4} + V_{GS5} + V_{GS6} = 5 - (-5) = 10 \text{ V} \text{ _____ (2)}$$


$$\therefore V_{GS4} = V_{GS5} = V_{GS6} = 3.33$$

Assuming MOS in saturation


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) [V_{GS} - V_{tn}]^2$$

$$\rightarrow \frac{1 \text{ m}}{2} = \frac{1}{2} 0.1 \text{ m} \left(\frac{W}{L} \right) [3.33 - 1]^2$$
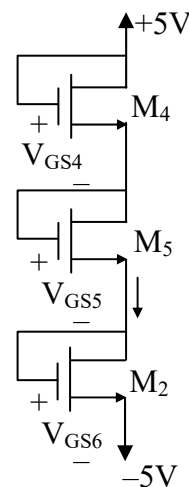
$$\rightarrow \left(\frac{W}{L} \right) = \frac{3.6745}{2} = 1.8367 \text{ (for } M_4, M_5, M_6 \text{)}$$



AC Equivalent

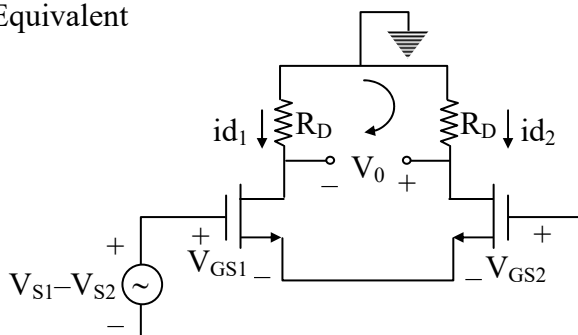

$$\text{KVL } V_{S1} = V_{S2} - V_{GS2} \quad (V_{GS1} = -V_{GS2} \text{ and } i_{d1} = -i_{d2} = i_d)$$

$$= 2V_{GS}$$

$$\text{KVL } i_{d2} R_D + V_0 - i_{d2} R_D = 0$$

$$V_0 = (i_{d1} - i_{d2}) R_D = 2i_d R_D$$

Differential gain

$$\frac{V_0}{V_d} = \frac{V_0}{V_{S1} - V_{S2}} = \frac{2i_d R_D}{2V_{GS}} = +g_m R_D$$

$$= (0.42856) 5k$$

$$= 2.1428$$

$$\text{Where } g_m = \sqrt{2kI_D}$$

$$= \sqrt{2(\mu_n C_{ox}) \left(\frac{W}{L} \right) [I_D]}$$

$$= \sqrt{2(0.1m) \frac{[3.6745]}{2} (0.5m)}$$

$$= \sqrt{0.2m(1.8367)(0.5m)}$$

$$= 0.42856$$

05. (d) Design a JK counter for states 1, 2, 4, 5, 7, 8, 10, 11, What would happen if the circuit were turned ON and the first state it entered was a don't care state? (12 M)

Sol:

	PS				NS				FF i/p's							
	Q ₃	Q ₁	Q ₂	Q ₀	Q ₃	Q ₁	Q ₂	Q ₀	J ₃ K ₃	J ₂ K ₂	J ₁ F ₁	J ₀ K ₀				
1	0	0	0	1	0	0	1	0	0 ×	0 ×	1 ×	× 1				
2	0	0	1	0	0	1	0	0	0 ×	1 ×	× 1	0 ×				
4	0	1	0	0	0	1	0	1	0 ×	× 0	0 ×	1 ×				
5	0	1	0	1	0	1	1	1	0 ×	× 0	1 ×	× 0				
7	0	1	1	1	1	0	0	0	1 ×	× 1	× 1	× 1				
8	1	0	0	0	1	0	1	0	× 0	0 ×	1 ×	0 ×				
10	1	0	1	0	1	0	1	1	× 0	0 ×	× 0	1 ×				
11	1	0	1	1	0	0	0	1	× 0	0 ×	× 1	× 0				

$$J_3 = \Sigma m(7) + d(0, 3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$K_3 = \Sigma m(11) + d(0, 1, 2, 3, 4, 5, 6, 7, 9, 12, 13, 14, 15)$$

$$J_2 = \Sigma m(2) + d(0, 3, 4, 5, 6, 7, 9, 12, 13, 14, 15)$$

$$K_2 = \Sigma m(7) + d(0, 1, 2, 3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$J_1 = \Sigma m(1, 5, 8) + d(0, 2, 3, 6, 7, 9, 10, 11, 12, 13, 14, 15)$$

$$K_1 = \Sigma m(2, 7, 11) + d(0, 1, 3, 4, 5, 6, 8, 9, 12, 13, 14, 15)$$

$$J_0 = \Sigma m(4, 10) + d(0, 1, 3, 5, 6, 7, 9, 11, 12, 13, 14, 15)$$

$$K_0 = \Sigma m(1, 7) + d(0, 2, 3, 4, 6, 8, 9, 10, 12, 13, 14, 15)$$

		Q ₁ Q ₀			
Q ₃ Q ₂		00	01	11	10
	00	×		×	
	01			1	×
	11	×	×	×	×
	10	×	×	×	×

$J_3 = Q_1 Q_0$

		Q ₁ Q ₀			
Q ₃ Q ₂		00	01	11	10
	00	×	×	×	×
	01	×	×	×	×
	11	×	×	×	×
	10		×	1	

$K_3 = Q_0$

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	x		x	1
01	x	x	x	x
11	x	x	x	x
10		x		

$$J_2 = \overline{Q_3}Q_1$$

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	×	×	×	×
	01			1	×
	11	×	×	×	×
	10	×	×	×	×

$$K_2 = Q_1$$

		$Q_1 Q_0$			
		00	01	11	10
$Q_3 Q_2$	00	×	1	×	×
	01		1	×	×
	11	×	×	×	×
	10	1	×	×	×

$$J_1 = Q_3 + Q_0$$

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	×	×	×	1
	01	×	×	1	×
	11	×	×	×	×
	10	×	×	1	×

$$K_1 = \overline{Q}_3 + Q_0$$


		Q_1Q_0			
Q_3Q_2		00	01	11	10
00		x	x	x	
01		1	x	x	
11		x	x	x	x
10			x	x	1

$$J_0 = Q_3 + Q_2$$

Q₃Q₂ \ Q₁Q₀


00	00	01	11	10
00	×	1	×	×
01	×		1	×
11	×	×	×	×
10	×	×		×
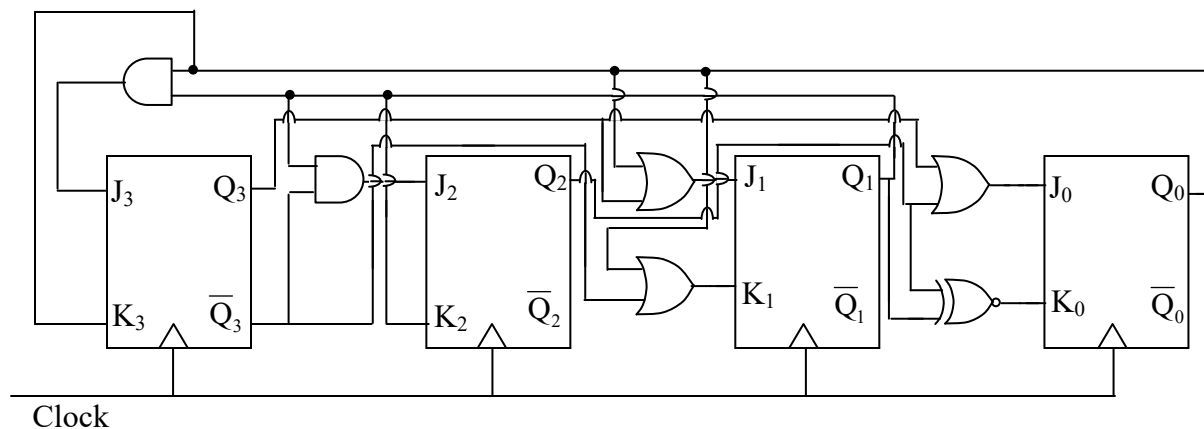
$$\dot{K}_0 = \dot{\overline{Q}}_2 \overline{Q}_1 + Q_2 Q_1 = Q_2 \odot Q_1$$



If a counter is entering into unused state and it is used as a don't care, then depending on utilization of don't cares in flip flop input expression may result input is 1 or 0. So the next state may be either used or unused state. Then there is a possibility for forming a loop in unused states only and it is called lockout.

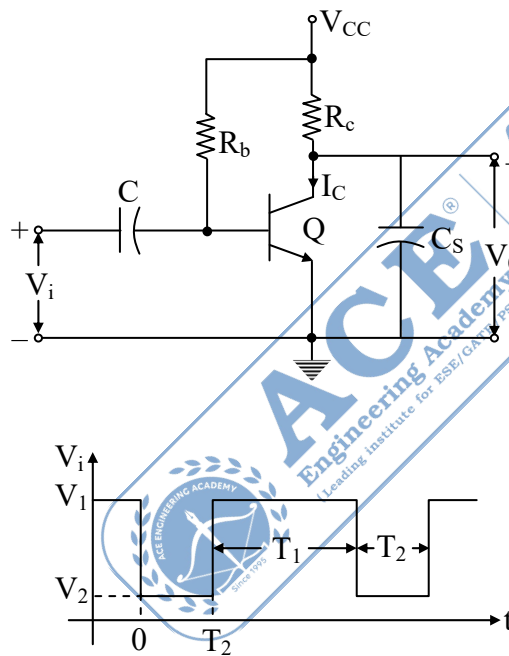05. (e) The transistor Q acts as a switch in the given circuit for the applied input V_i that varies with time as shown below:




Plot the variation of the collector current: I_c and the output voltage v_0 , assuming that the time constants are small compared to T_1 or T_2 . (12 M)

Sol: The given transistor acts as a switch. Consider the input V_1 is high and V_2 is low. The transitions are instantaneous as the time constants are negligible.



Case 1: Let $V_{in} = V_1$ (high), the BJT is ON and $I_C = \frac{V_{CC} - V_{CC(sat)}}{R_C} \approx \frac{V_{CC}}{R_C}$

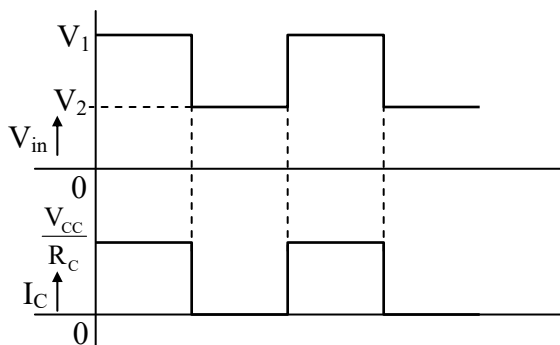Case 2: Let $V_{in} = V_2$ (low), the BJT is OFF and $I_C = 0$, $V_0 = V_{CC}$



The given transistor toggles between cutoff and saturation.

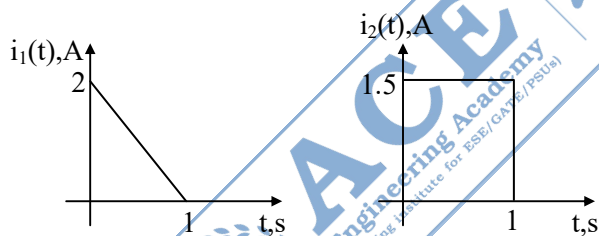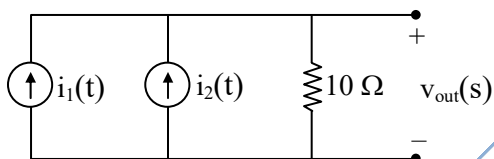06. (a) The circuit of the figure has two sources of excitation $i_1(t)$ and $i_2(t)$. Compute $v_{out}(s)$:



(20 M)

Sol: $V_{out} = [i_1(t) + i_2(t)] 10 \text{ Volts}$

At $t = 0$

$$i_1(t=0) = 2 \text{ A}$$

$$i_2(t=0) = 1.5 \text{ A}$$

$$i_1 + i_2 = 3.5 \text{ A}$$

$$\text{So, } V_{out}(t=0) = 3.5 \times 10 = 35 \text{ volts}$$

At $t = 1^-$

$$i_1(t=1^-) = 0 \text{ A}$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



**ace
online**



(A Digital Initiative by ACE Engineering Academy)

India's Leading Institute

ESE, GATE, PSUs
SSC, RRB, BANKING & 30+ other exams


— USE CODE —
COLLEGE10

Get **10% OFF**
on all courses

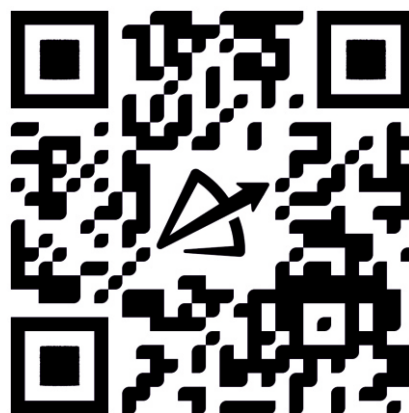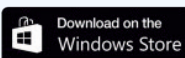

Scan QR & start your
7-DAY Free Trial!

#Let's ACE it!

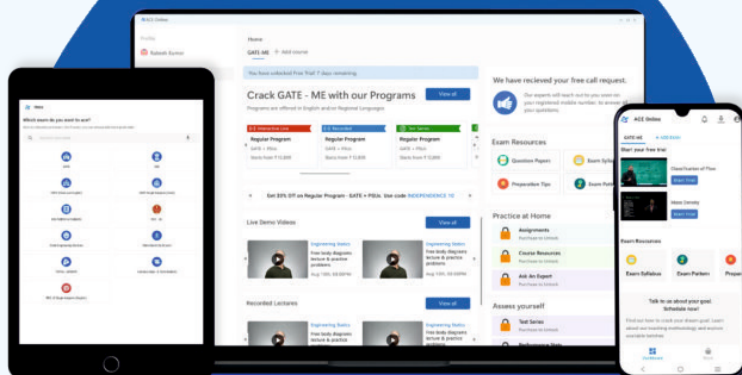

7799996602

www.ace.online | www.aceenggacademy.com

$$i_2(t=1^-) = 1.5 \text{ A}$$

$$i_1 + i_2 = 1.5 \text{ A}$$

$$\text{So, } V_{\text{out}}(t=1^-) = 1.5 \times 10 = 15 \text{ volts}$$


At $t = 1^+$

$$i_1(t=1^+) = 0 \text{ A}$$

$$i_2(t=1^+) = 0 \text{ A}$$

$$i_1 + i_2 = 0 \text{ A}$$
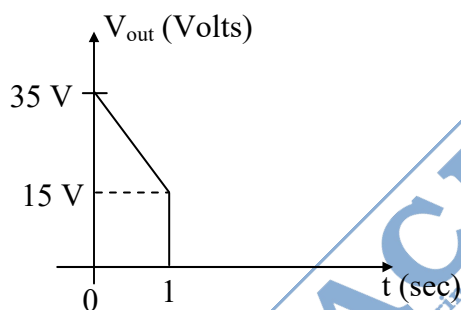
$$\text{So, } V_{\text{out}}(t=1^+) = 0 \text{ V}$$



Using Laplace Transform

$$i_1 = -2tu(t) + 2(t-1)u(t-1)$$

$$I_1(s) = -\frac{2}{s^2} - \frac{2}{s^2}e^{-s} = -\frac{2}{s^2}[1 + e^{-s}] \text{ A}$$

$$i_2(t) = 1.5tu(t) - 1.5u(t-1)$$

$$I_2(s) = \frac{1.5}{s} - \frac{1.5}{s}e^{-s} = \frac{1.5}{s}[1 - e^{-s}] \text{ A}$$

$$V_{\text{out}}(s) = [I_1(s) + I_2(s)]10$$

$$= 10 \left[-\frac{2}{s^2}[1 + e^{-s}] + \frac{1.5}{s}[1 - e^{-s}] \right] \text{ V}$$


06. (b) Consider the circuit given below with the following parameters:

$$R_{c_1} = 3K, R_{c_2} = 500\Omega, R_e = 50\Omega, R' = R_s = 1.2K, h_{fe} = 50, h_{ie} = 1.1K$$

and $h_{re} = h_{oe} = 0$


Analyze the circuit for —

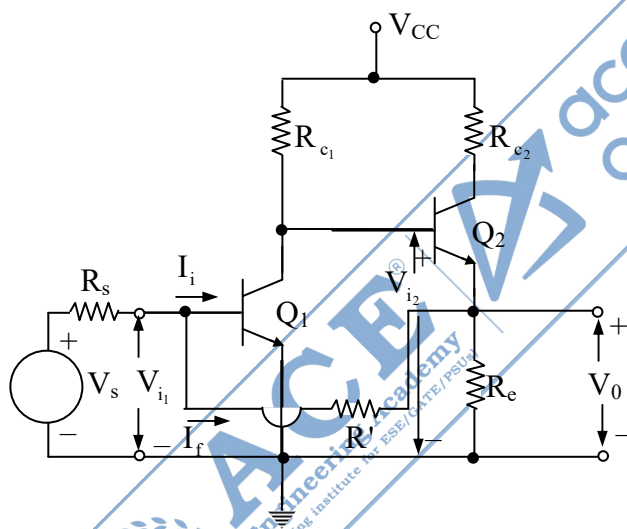- (i) reverse transmission factor, β ;**
- (ii) transfer gain;**
- (iii) voltage gain with feedback;**
- (iv) input resistance with feedback;**
- (v) output resistance with feedback.**



(20 M)

Sol:

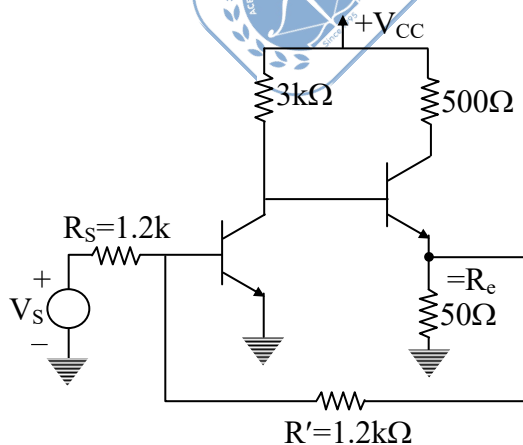


$$h_{fe} = \beta = 50$$

$$h_{ie} = r_{\pi} = 1.1k\Omega$$

$$h_{re} = h_{oe} = 0$$

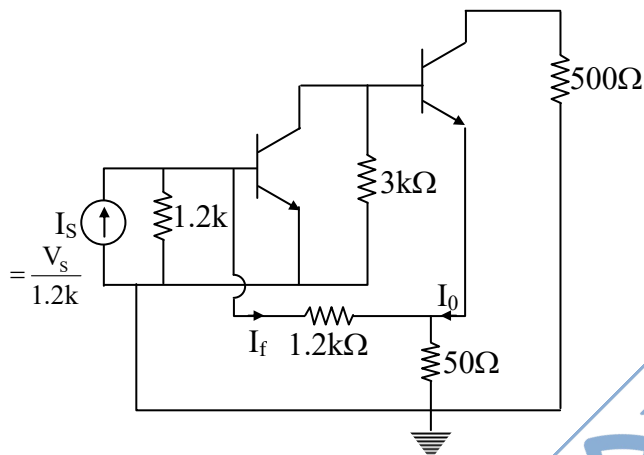The given amplifier is a current amplifier with shunt-series feedback



$$(i) \quad i_{b1} = \frac{I_s [612.244]}{612.244 + 110}$$

$$\frac{i_{b1}}{I_s} = \frac{612.244}{1712.244} = 0.357568$$

$$(ii) \quad A_{open} = \frac{i_0}{i_s} = \frac{i_0}{i_{b2}} \cdot \frac{i_{b2}}{i_{b1}} \cdot \frac{i_{b1}}{i_s}$$

$$= (51) (-22.9077) (0.357568)$$

$$= -417.7443$$

$$(iii) \quad \text{Desensitivity factor} = 1 + A_{open} \cdot \beta$$


$$= 1 + (-417.7443) (-0.04)$$

$$= 17.70977$$

$$(iv) \quad \text{Input resistance with feedback } R_{inf} = \frac{R_{inopen}}{1 + A_{open} \cdot \beta} = \frac{612.244 // 1.1k\Omega}{17.70977}$$

$$= \frac{393.325}{17.70977} = 22.2094\Omega$$

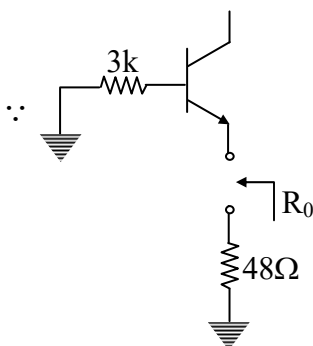(v) Output resistance with feedback $R_{of} = R_{0(\text{Basic Amp})} [1 + A\beta]$
 $= 128392 (17.7097)$
 $R_{of} = 2273.79\Omega$



$$R_{o(\text{Basic})} = \left(\frac{r_{\pi}}{1 + \beta} + \frac{3k}{1 + \beta} \right) + 48\Omega$$

$$= \frac{h_{ie}}{1 + h_{fe}} + \frac{3k}{1 + h_{fe}} + 48\Omega$$

$$= \frac{1.1k}{51} + \frac{3k}{51} + 48$$

$$= 21.568 + 58.82 + 48$$

$$= 128.392$$

Overall current gain with feedback

$$\left(\frac{i_o}{i_{in}} \right) = A_f = \frac{A}{1 + A\beta} = \frac{-417.7443}{17.70977} = -23.58835$$



ACE[®]
Engineering Academy
Leading Institute for ESE/GATE/PSUs



**ace
online**
(A Digital Initiative by ACE Engineering Academy)

HEARTY CONGRATULATIONS TO OUR STUDENTS SELECTED IN **TGPSC-AEE (2022)**



Rank **1** (EE)

KAVYA NALLA
CLASSROOM COACHING
Selected in: **Transport,**
R&B Dept., Govt. of TG.



1 **CE**
Venkat Reddy
MEGA MOCK TEST
Selected in Public Health,
MA & UD Dept. Govt. of TG.



3 **EE**
Devarakonda Sathwik
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



4 **EE**
Sangem Ravi Kumar
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



4 **CE**
Makam Jeevan Kumar
CLASSROOM COACHING
Selected in **Public Health,**
MA & UD Dept., Govt. of TG.



6 **CE**
Balraj Madgan
MEGA MOCK TEST
Selected in **Transport,**
R&B Dept., Govt. of TG.



7 **EE**
Challabotta Saikiran
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



7 **ME**
Vineetha Boddula
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



7 **CE**
Rama Krishna
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



8 **CE**
Abhinav Karimilla
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



9 **EE**
Ganapathi G
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



9 **CE**
Pranay V
CLASSROOM COACHING
Selected in **Public Health,**
MA & UD Dept., Govt. of TG.



11 **EE**
Sainath
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



11 **CE**
Bhugolla Surya Teja
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



12 **EE**
Veligeti Umesh
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



12 **CE**
Puli Naveen Reddy
CLASSROOM COACHING
Selected in **Transport,**
R&B Dept., Govt. of TG.



14 **ME**
Ravi Teja
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



15 **ME**
M Dheeraj Reddy
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



16 **EE**
Jangili Rajashekar
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



18 **EE**
Maika Kiran
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



19 **EE**
Sowmya
CLASSROOM COACHING
Selected in **Irrigation**
& CAD Dept., Govt. of TG.



20 **CE**
Md. Azmatullah
MEGA MOCK TEST
Selected in **Transport,**
R&B Dept., Govt. of TG.


AND MANY MORE..

500+ SELECTIONS

CE : 434 | EE : 61 | ME : 20


06. (c) Consider the circuit in which $v_{in}(t) = 5u(t) \text{ V}$, $v_{c_1}(0^-) = 3 \text{ V}$, $v_{c_2}(0^-) = 0 \text{ V}$ **and** $i_L(0^-) = 2 \text{ A}$.

Find $v_{out}(t)$:

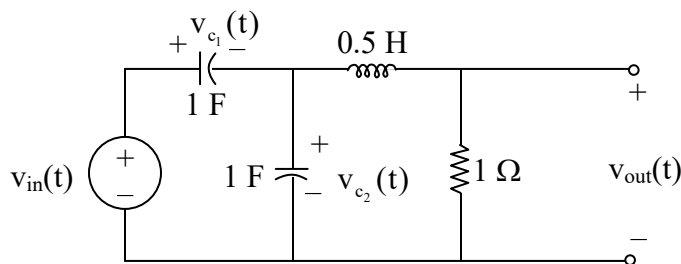

(20 M)

Sol: Using Laplace Transform

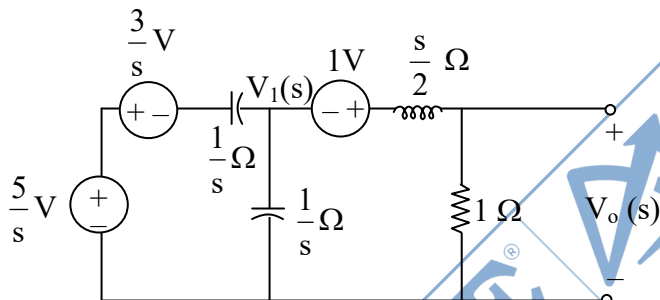

By Nodal

$$\left[\frac{V_1(s) - \frac{5}{s} + \frac{3}{s}}{\frac{1}{s}} \right] + \frac{V_1(s)}{\frac{1}{s}} + \frac{[V_1(s) + 1]}{\left[1 + \frac{s}{2} \right]} = 0$$

$$V_1(s) \left[s + s + \frac{2}{s+2} \right] = 5 - 3 - \frac{2}{(s+2)}$$

$$V_1(s) \left[\frac{s^2 + 2s + s^2 + 2s + 2}{s+2} \right] = 2 - \frac{2}{s+2} = \frac{2s+4-2}{s+2} = \frac{2s+2}{s+2}$$

$$V_1(s) = \frac{2(s+1)}{2s^2 + 4s + 2} = \frac{2(s+1)}{2(s^2 + 2s + 1)}$$

But

$$V_0(s) = [V_1(s) + 1] \left[\frac{1}{1 + \frac{s}{2}} \right] = [V_1(s) + 1] \left[\frac{2}{s+2} \right]$$

$$V_0(s) = \left[\frac{s+1}{s^2+2s+1} + 1 \right] \left[\frac{2}{s+2} \right]$$

$$V_0(s) = \left[\frac{s+1+s^2+2s+1}{s^2+2s+1} \right] \left[\frac{2}{s+2} \right]$$

$$V_0(s) = \frac{2(s^2+3s+2)}{(s+2)(s^2+2s+1)} = \frac{2(s+2)(s+1)}{(s+2)(s+1)^2} = \frac{2}{s+1}$$

Do Inverse Laplace transform to get

$$V_0(t) = L^{-1}[V_0(s)]$$

$$V_0(t) = 2e^{-t}u(t) \text{ Volts}$$

07. (a) (i) A first-order thermometer is used for the measurement of temperature of air cycling at a rate of 1 cycle every 5 minutes. The time constant of the thermometer is 20 seconds. Calculate the attenuation of the indicated temperature in percent. If the temperature undergoes a sinusoidal variation of 20 °C, calculate the indicated variation in temperature. (10 M)

Sol: $f = \frac{1}{5 \times 60} = \frac{1}{300} \text{ Hz}$

$$\omega = 2\pi f = 0.02094 \text{ rad/sec}$$

$$\tau = 20 \text{ sec}$$

$$(\text{AR}) \text{ ratio} = \frac{1}{\sqrt{1 + (\omega\tau)^2}} = 0.923$$

$$\therefore \text{Attenuation \%} = 0.923 \times 100 = 92.3 \%$$

$$\text{Indicated amplitude} = (\text{AR}) \times 20 = 0.923 \times 20 = 18.46 \text{ }^\circ\text{C}$$

07. (a) (ii) Compare and contrast Type-I and Type-II superconductors based on the following parameters:

(1) Magnetic field behaviour

(2) Critical magnetic field

(3) Material examples

(4) Meissner effect

(5) Applications.

(10 M)

Sol: Comparison: Type-I vs Type-II Superconductors

Parameter	Type-I Superconductors	Type-II Superconductors
1. Magnetic field behaviour	Exhibit perfect diamagnetism (complete expulsion of magnetic field) below critical field. Transition is abrupt.	Allow partial penetration of magnetic field through vortex state between two critical fields.
2. Critical magnetic field (B_c)	Have a single critical magnetic field (B_c). Superconductivity is lost completely above this value.	Have two critical fields: lower (B_{c1}) and upper (B_{c2}). Between B_{c1} and B_{c2} , mixed state exists.
3. Material examples	Elements like Lead (Pb), Mercury (Hg), Tin (Sn), Aluminium (Al).	Alloys and complex oxides like Niobium-Titanium (NbTi), YBCO (Yttrium Barium Copper Oxide).
4. Meissner effect	Show complete Meissner effect (perfect expulsion of magnetic field).	Show partial Meissner effect in the mixed state. Magnetic flux penetrates in quantized vortices.
5. Applications	Limited use due to low critical magnetic fields and current density.	Widely used in magnets, MRI, particle accelerators due to high critical fields and current capacity.

Hearty Congratulations

To our students **CIVIL ENGINEERING**
Selected in **SSC JE - 2024**



HARSHIT KHARE
Roll No. **3008100089**
Selected in: **CPWD**



RAMSWRUP
Roll No. **2404100567**
Selected in: **CPWD**



LAKSHIT BHARDWAJ
Roll No. **3206106390**
Selected in: **CPWD**



M V SIVA RAM REDDY
Roll No. **8008101372**
Selected in: **CPWD**



RAVINDRA DHAKAD
Roll No. **6005100485**
Selected in: **CPWD**



RAHUL KUMAWAT
Roll No. **2401100340**
Selected in: **CPWD**



VISHAL SINGH
Roll No. **3013105309**
Selected in: **MES**



S R JAFFER SHARIEF
Roll No. **8006102160**
Selected in: **MES**



BEHARA SRIKANTH
Roll No. **8007102883**
Selected in: **MES**



ANIRUDH KOTIYAL
Roll No. **2003101448**
Selected in: **MES**



FAIZAN AHMAD
Roll No. **3010108428**
Selected in: **MES**



AMBATI NAGA SRI SAI
Roll No. **8601105973**
Selected in: **MES**



BHASKAR SHARMA
Roll No. **2201112287**
Selected in: **MES**



SRINI VASA RAO
Roll No. **8601101840**
Selected in: **MES**



PIJUSH AKHULI
Roll No. **4426100222**
Selected in: **MES**



ABHIMANU KUMAR
Roll No. **3205100298**
Selected in: **MES**



NIMESH SINGH
Roll No. **2201114868**
Selected in: **MES**



LALAM RAMU NAIDU
Roll No. **8601102319**
Selected in: **MES**



GYANENDRA KUMAR
Roll No. **2201110803**
Selected in: **CWC**



ADARSH AGRAHARI
Roll No. **3003100031**
Selected in: **BRO**



REDDI SANNIBABU
Roll No. **8007102353**
Selected in: **MES**



KONAPALA MANOJ
Roll No. **2201109855**
Selected in: **MES**



SUNIL SHARMA
Roll No. **4415100648**
Selected in: **MES**



RINKESH KUMAR
Roll No. **6204103361**
Selected in: **MES**

& many more..



Total 150+ Selections

CE-98

EE-29

ME-24

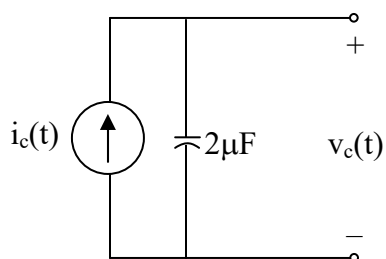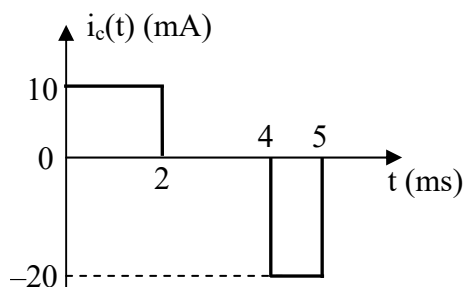07. (b) The current through a $2 \mu\text{F}$ capacitor is shown in the figure. At $t = 0$, the voltage is zero. Sketch the voltage and power waveform with respect to the time (scaled voltage and power):



(20 M)

Sol: $V_c(t) = V(0) + \frac{1}{C} \int i(t) dt$

$0 \leq t \leq 2 \text{ msec}$

$$V_c(t) = V(0) + \frac{1}{2\mu} \int_0^{2m} 10 \text{ m} dt$$

$$= 0 + \frac{10 \text{ m}}{2\mu} \cdot t \Big|_0^{2m}$$

So, at $t = 0 \rightarrow V_c = 0 \text{ V}$
 at $t = 2 \text{ m} \rightarrow V_c = 10 \text{ V}$ } Ramp Voltage

$2 \text{ m} \leq t \leq 4 \text{ m}$

$$V_c(t) = V(0) + \frac{1}{2\mu} \int_{2m}^{4m} 0 dt$$


Voltage remains at 10 Volts

$4 \text{ m} \leq t \leq 5 \text{ msec}$

$$V_c(t) = V(0) + \frac{1}{2\mu} \int_{4m}^{5m} -20 \text{ m} dt$$

$$= 10 - \frac{20 \text{ m}}{2\mu} \cdot t \Big|_{4m}^{5m}$$

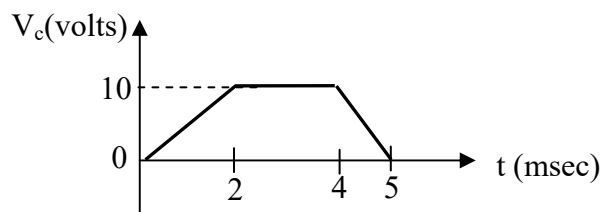So, at $t = 4\text{m} \rightarrow V_c = 10\text{ V}$
 at $t = 5\text{m} \rightarrow V_c = 0\text{ V}$ } Ramp function



$$P_c(t) = V_c(t)i_c(t) \text{ W}$$

$$0 \leq t \leq 2\text{ m}$$

$$\text{at } t = 0 \rightarrow 0\text{ W}$$

$$\text{at } t = 2\text{m} \rightarrow 10\text{ V} \times 10\text{mW} = 100\text{ mW}$$

} Ramp


$$2\text{m} \leq t \leq 4\text{ m}$$

$$\therefore i_c = 0 \rightarrow P = 0\text{ W}$$

$$4\text{m} \leq t \leq 5\text{ m}$$

$$\text{at } t = 4\text{m} \rightarrow 10\text{ V} \times -20\text{ m} = -200\text{ mW}$$
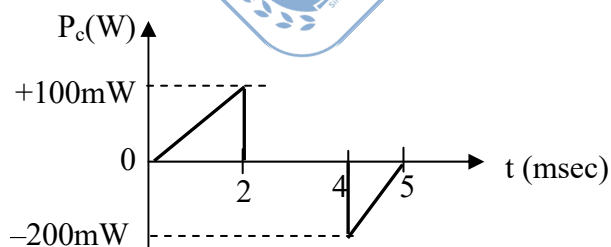
$$\text{at } t = 5\text{m} \rightarrow 0\text{ W}$$



Hearty Congratulations to our students GATE - 2025

84 TIMES
AIR 1st
IN GATE

AIR
1



PI Devendra Umbrajkar

AIR
1



EE Pradip Chauhan

AIR
1



IN Kailash Goyal

AIR
2



EE Kailash Goyal

AIR
2



ME Gollangi Sateesh

AIR
2



ES Jitesh Choudhary

AIR
3



ME Nimesh Chandra

AIR
3



ME Sanket Tupkar

AIR
3



PI Sadhan Anumala

AIR
3



XE Rohan Biswal

AIR
3



PI Aditya Kumar Prasad

AIR
4



CE Harshil Maheshwari

AIR
5



EC Mohammed Nafeez

AIR
5



IN Sachin Yadav

AIR
5



ME Uday G.

AIR
5



PI Kuldeep Singh naruka

AIR
6



CE Nimish Upadhyay

AIR
6



CE Shivanand Chaurasia

AIR
6



EE Shivam Kumar Gupta

AIR
6



EE Puneet Soni

AIR
6



EC P Jaswanth Bhavani

AIR
6



PI Kaushal Kumar Kaushik

AIR
7



EC Subhadip Dey

AIR
7



ME Abhinav Srivastava

AIR
7



IN Dev Jignesh Patel

AIR
7



DA Sairam Gudla

AIR
7



CS Hemanth Reddu P

AIR
7



PI Waleed Shaikh

AIR
7



XE Sanket Tupkar

AIR
8



ME Goutam Kumar

AIR
8



IN Pushpendra Payal

AIR
8



CS Rishi Sharma

AIR
9



EC Sai Charan Chilukuri

AIR
9



ME Rahul Paliwal

AIR
9



PI Anish Vanapalli

AIR
10



EE Neelava Mukherjee

AIR
10



ME Ashutosh kumar

AIR
10



ME Jetty Ganateja

AIR
10



ME Pitchika Kumar Vasu

AIR
10



CE Adnan Quasain

& many more....

07. (c) (i) A piezoelectric ceramic disc of thickness $t = 2\text{mm}$ and area $= 1.5 \times 10^{-4} \text{ m}^2$ is subjected to a compressive force of $F = 50\text{N}$ applied perpendicular to its faces. The material has the following properties:

- **Piezoelectric coefficient $= 300 \times 10^{-12} \text{ C/N}$**
- **Relative permittivity $= 1200$**
- **Volume permittivity $= 8.854 \times 10^{-12} \text{ F/m}$**

Determine the following :

(1) Charge generated on electrodes due to applied force

(2) Capacitance of the piezoelectric disc

(3) Voltage generated across the ceramic disc

(10 M)

Sol:

$$\text{Charge } Q = dF = 300 \times 10^{-12} \times 50 = 15 \times 10^{-9} \text{ col}$$

$$C = \frac{\epsilon_0 \cdot \epsilon_r \cdot A}{t} = \frac{8.854 \times 10^{-12} \times 1200 \times 1.5 \times 10^{-4}}{0.002} = 7.97 \times 10^{-10} \text{ F}$$

$$V = \frac{Q}{C} = \frac{15 \times 10^{-9}}{7.97 \times 10^{-10}} = 18.8 \text{ V}$$

(or)

$$V = \frac{d}{\epsilon_0 \epsilon_r} \frac{E}{A} t = \frac{300 \times 10^{-12}}{8.854 \times 10^{-12} \times 1200} \times \frac{50}{1.5 \times 10^{-4}} \times 2 \times 10^{-3} = 18.8 \text{ V}$$

07. (c) (ii) For a 2-port network, express Z-parameters in terms of inverse hybrid parameters.

(10 M)

Sol: g-parameters

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

Z-parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

For z_{11} & $z_{21} \Rightarrow I_2 = 0$

$I_2 = 0$:

$$I_1 = g_{11} V_1 \quad z_{11} = \frac{V_1}{I_1} = \frac{1}{g_{11}} \quad \text{---- (1)}$$

$$V_2 = g_{21} V_1 \quad z_{21} = \frac{V_2}{I_1} = \frac{g_{21}}{g_{11}} \quad \text{---- (2)}$$

For z_{22} & $z_{12} \Rightarrow I_1 = 0$

$I_1 = 0$:

$$g_{11} V_1 = -g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$V_2 = g_{21} \left[-\frac{g_{12}}{g_{11}} \right] I_2 + g_{22} I_2 = \frac{\Delta g}{g_{11}} I_2$$


$$z_{22} = \frac{V_2}{I_2} = \frac{\Delta g}{g_{11}}$$

$$z_{12} = \frac{V_1}{I_2} = -\frac{g_{12}}{g_{11}}$$

So,


$$[Z] = \begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{\Delta g}{g_{11}} \end{bmatrix}$$

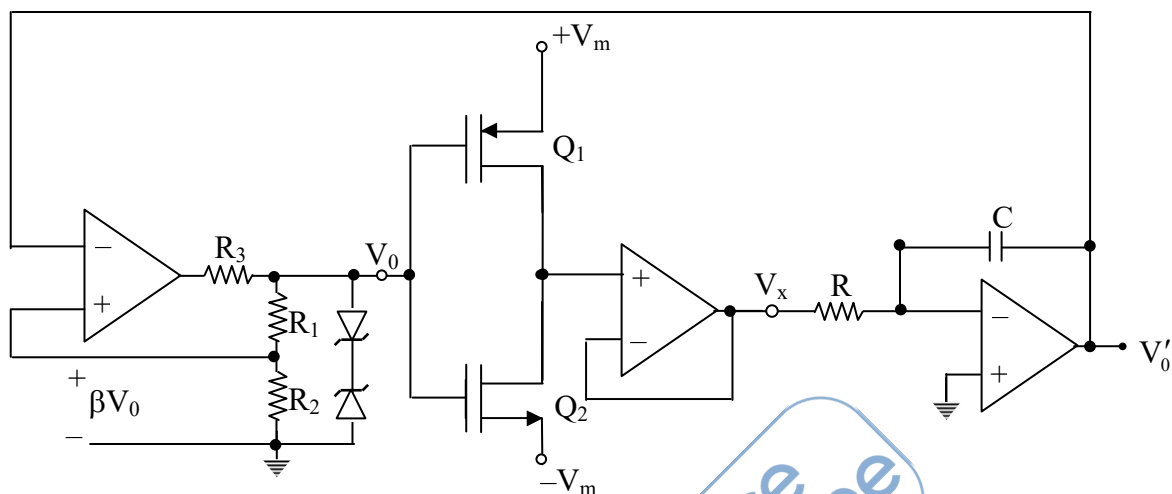08. (a) Explain the working of each stage of the voltage-controlled oscillator circuit shown below :



Evaluate the effect of change in modulating voltage V_m to the output frequency. (20 M)

Sol: **Stage 1: Schmitt trigger**

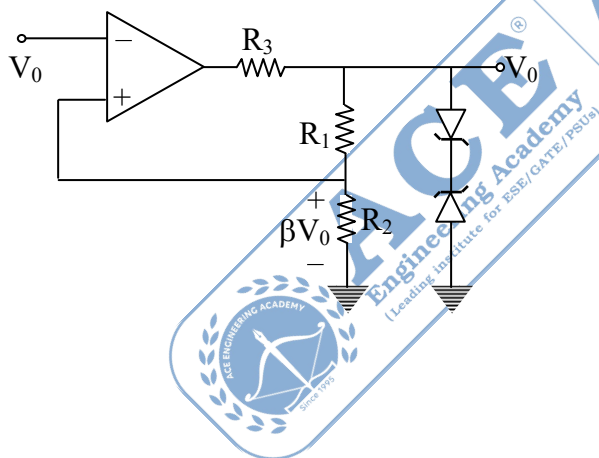

The given circuit is a Schmitt trigger with positive feedback. So the output V_0 can have two states, $V_z + V_{D_{ON}}$ or $-(V_z + V_{D_{ON}})$


$$\rightarrow \text{The feedback factor } \beta = \frac{R_2}{R_1 + R_2}$$

So a portion of V_0 which is βV_0 is fed back to the non inverting terminal for comparison

→ If $V_{01} > \beta V_0$ then $V_0 = -\left(V_z + V_{D_{ON}}\right)$

If $V_{01} < \beta V_0$ then $V_0 = +\left(V_z + V_{D_{ON}}\right)$

Stage 2:

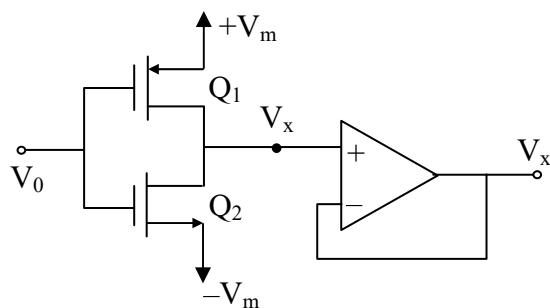


→ The given MOS in the above diagram as used as switch.

→ If $V_0 = V_z + V_{D_{ON}}$ then Q_2 is ON and $V_x = -V_m$

→ If $V_0 = -\left(V_z + V_{D_{ON}}\right)$ then Q_1 is ON and $V_x = +V_m$

→ The buffer (voltage follower) is used for Isolation as it has to drive the (inverting terminal) integrator


Stage 3: (Integrator)

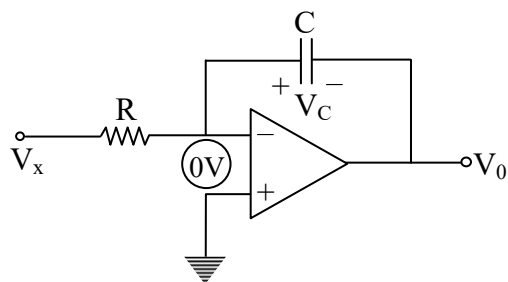

→ If $V_x = V_m$ then $V_{01} = \left(\frac{-V_m}{RC} \right) t$ and the output is a negative ramp

$$V_{01} = -V_c = -\frac{1}{C} \int I dt = -\left(\frac{I}{C} \right) t = \left(\frac{-V_m}{RC} \right) t$$

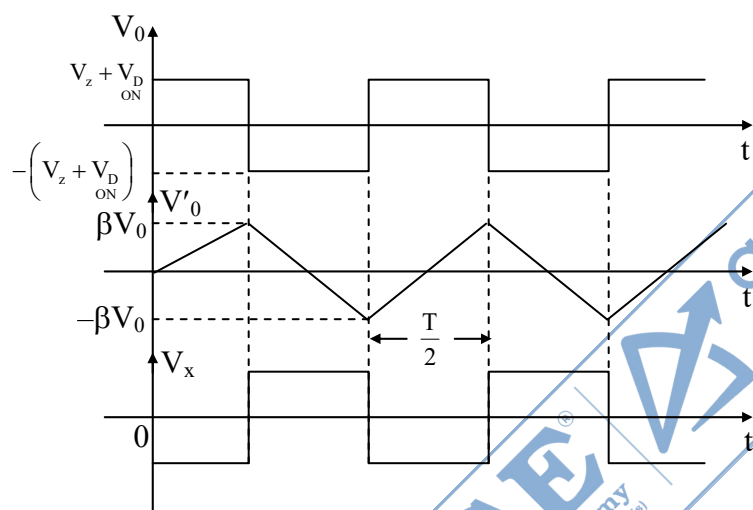→ If $V_x = -V_m$ then $V_{01} = \left(\frac{V_m}{RC} \right) t$ then output is a positive ramp



Calculation of frequency

$$\text{slope} = \frac{\Delta y}{\Delta x}$$

$$\frac{V_m}{RC} = \frac{\beta V_0 - (-\beta V_0)}{\left(\frac{T}{2} \right)}$$

$$\frac{V_m}{RC} = \frac{4\beta V_0}{T}$$

$$\rightarrow \frac{1}{T} = f = \frac{V_m}{4\beta V_0 RC}$$

$$\text{Sub } \beta = \frac{R_2}{R_1 + R_2} \text{ and } V_0 = V_z + V_{D_{ON}}$$

$$\therefore f = \frac{V_m (R_1 + R_2)}{4R_2 RC (V_z + V_{D_{ON}})}$$

Hearty Congratulations to our students ESE - 2024



Rohit Dhondge




Himanshu T



Rajan Kumar



Munish Kumar

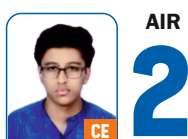

HARSHIT PANDEY



SATYAM CHANDRAKANT




RAJESH KASANIYA



LAXMIKANT



UNNATI CHANSORIA

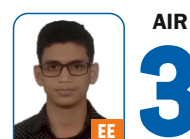

PRIYANSHU MUDGAL



GOLLANGI SATEESH



MADHAN KUMAR



RAJIV RANJAN MISHRA




AJINKYA DAGDU



AMAN PRATAP SINGH



PARAG SAROHA

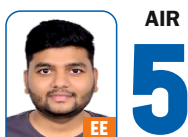

MAYANK KUMAR S




BANKURU NAVEEN



SANCHIT GOEL



CHANDRIKA GADGIL

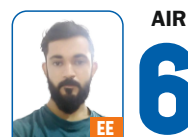

RITVIK KOK



CHANDAN JOSHI



DEBARGHYA CH



MANTHAN SHARMA



DINESH KUMAR S



ROHIT KUMAR



VIDHU SHREE



MAYANK JAIMAN



SHAILENDRA SINGH



ANKIT MEENA



T PIYUSH DAYANAND



ANMOL SINGH



KRISHNA KUMAR D



RAJESH BADUGU



RAJVARDHAN SHARMA




AKSHAY VIDHATE

TOTAL 36 SELECTIONS IN TOP 10 CE: 09 | ME: 10 | EE: 08 | E&T: 09

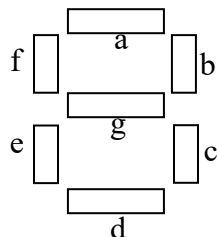08. (b) Use a decoder to design a binary-to-hexadecimal character generator. The outputs of the character generator are to be connected via current limiting resistors to a common anode seven-segment display. Assume that the inputs are positive logic signals. (20 M)

Sol: Binary to hexa character generation with 7 segment display.



	B ₃	B ₂	B ₁	B ₀	a b c d e f g
0	0	0	0	0	1 1 1 1 1 1 0
1	0	0	0	1	0 1 1 0 0 0 0
2	0	0	1	0	1 1 0 1 1 0 1
3	0	0	1	1	1 1 1 1 0 0 1
4	0	1	0	0	0 1 1 0 0 1 1
5	0	1	0	1	1 0 1 1 0 1 1
6	0	1	1	0	1 0 1 1 1 1 1
7	0	1	1	1	1 1 1 0 0 0 0
8	1	0	0	0	1 1 1 1 1 1 1
9	1	0	0	1	1 1 1 0 1 1 1
10	1	0	1	0	1 1 1 1 0 1 1
11	1	0	1	1	1 1 1 1 1 1 1
12	1	1	0	0	0 0 0 1 1 1 0
13	1	1	0	1	1 1 1 1 1 1 0
14	1	1	1	0	1 0 0 1 1 1 1
15	1	1	1	1	1 0 0 0 1 1 1

$$a = \Sigma m(0,2,3,5,6,7,8,9,10,11,13,14,15)$$

$$b = \Sigma m(0,1,2,3,4,7,8,9,10,11,13)$$


$$c = \Sigma m(0,1,3,4,5,6,7,8,9,10,11,13)$$

$$d = \Sigma m(0,2,3,5,6,8,10,11,12,13,14)$$


$$e = \Sigma m(0,2,6,8,9,11,12,13,14,15)$$

$$f = \Sigma m(0,4,5,6,8,9,10,11,12,13,14,15)$$

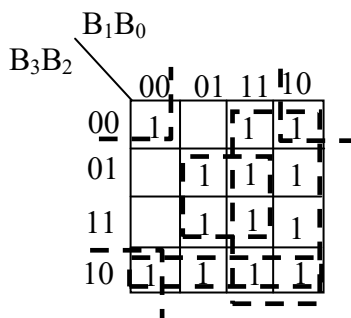
$$g = \Sigma m(2,3,4,5,6,8,9,10,11,14,15)$$



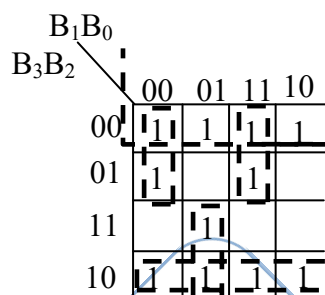
$$a = B_1 + B_2 B_0 + B_3 \bar{B}_2 + \bar{B}_2 \bar{B}_0$$



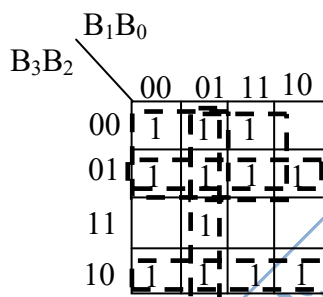
$$b = \bar{B}_2 + \bar{B}_3 \bar{B}_1 \bar{B}_0 + \bar{B}_3 B_1 B_0 + B_3 \bar{B}_1 B_0$$



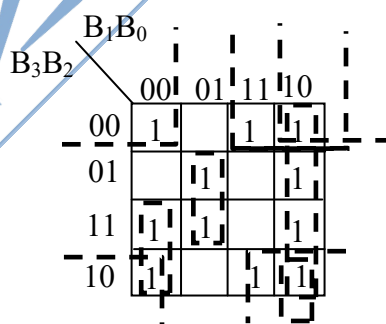
$$c = \bar{B}_3 B_2 + B_3 \bar{B}_2 + \bar{B}_3 \bar{B}_0 + \bar{B}_3 B_0 + B_1 \bar{B}_0$$


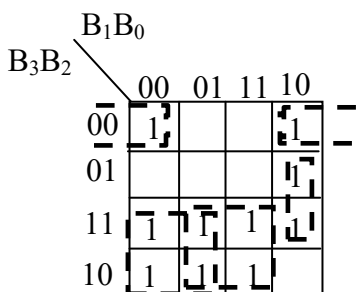
$$d = \bar{B}_1 \bar{B}_0 + \bar{B}_2 B_1 + \bar{B}_2 \bar{B}_0 + B_3 \bar{B}_1 \bar{B}_0 + B_2 \bar{B}_1 B_0$$


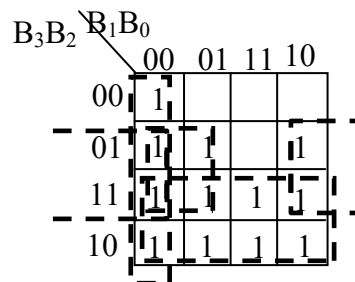
$$e = B_3 \bar{B}_1 + B_3 B_0 + B_2 B_1 \bar{B}_0 + \bar{B}_3 \bar{B}_2 \bar{B}_0$$




$$f = B_3 + B_1 \bar{B}_0 + B_2 \bar{B}_1 + B_2 \bar{B}_0$$

	B_1B_0			
B_3B_2	00	01	11	10
00			1	1
01	1	1		1
11			1	1
10	1	1	1	1


$$g = B_3\bar{B}_2 + B_1\bar{B}_0 + B_3B_1 + \bar{B}_2B_1 + \bar{B}_3B_2\bar{B}_1$$

08. (c) (i) A voltage $50 + 25\sin\omega t$ volts is applied to a series R-L circuit having a resistance of $10\ \Omega$ and inductance of 0.1 H . A wattmeter is connected in the circuit to measure power. Calculate the reading of the wattmeter if $\omega = 100\pi\text{ rad/s}$. (10 M)

Sol:

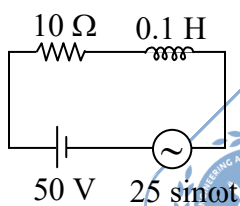


DC:

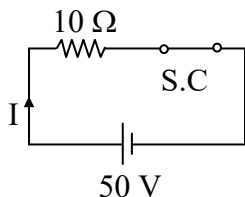

$$I = \frac{50}{10} = 5\text{ A}$$

$$P_{dc} = I^2R = (5)^2 10 = 250\text{ W}$$

AC:

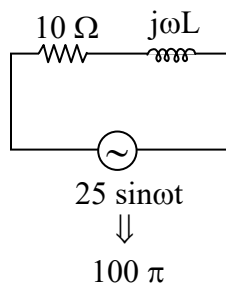

$$j\omega L = 100\pi (0.1) = 10\pi = 31.4 \Omega$$

$$I_{\text{rms}} = \frac{V_m / \sqrt{2}}{Z} = \frac{25 / \sqrt{2}}{10 + j31.4} = 0.5355 \angle -72.366^\circ \text{ A}$$


$$P_{\text{ac}} = (0.5355)^2 10 = 2.8676 \text{ W}$$

$$\therefore P_{\text{Total}} = P_{\text{dc}} + P_{\text{ac}} = 250 + 2.8676 = 252.8676 \text{ W}$$

08. (c) (ii) For the circuit shown in the figure, find I_{out} . Assume $\mu_n C_{\text{ox}} = 250 \mu\text{A} / \text{V}^2$ and

$V_{\text{tn}} = 0.4 \text{ V}$ for both the MOSFETs:

(10 M)

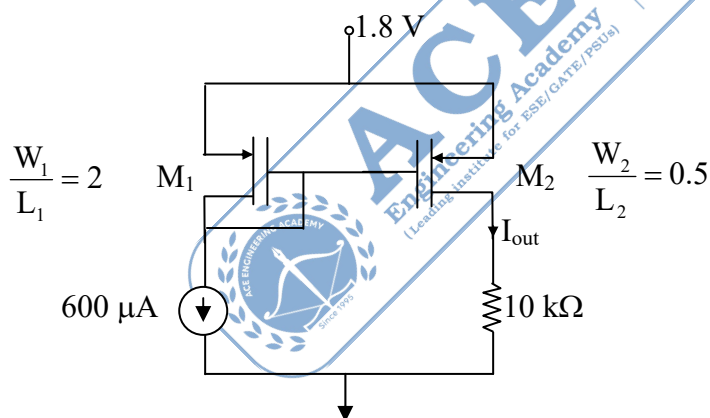

Sol: Circuit given is a current mirror

$$\frac{I_{\text{out}}}{\left(\frac{W}{L}\right)_2} = \frac{I_{\text{in}}}{\left(\frac{W}{L}\right)_1}$$

$$I_{\text{out}} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \cdot I_{\text{in}} = \left(\frac{0.5}{2}\right) 600 \mu = 150 \mu\text{A}$$

FOLLOW US ON SOCIAL MEDIA



WHY SHOULD YOU FOLLOW OUR SOCIAL MEDIA PLATFORMS?

- **Expert Guidance:** Access tips and strategies from experienced mentors.
- **Content:** Get exclusive notes, questions, and mock tests.
- **Interactive Learning:** Participate in live doubt-solving sessions and quizzes.
- **Exam & Job Updates:** Stay updated with the latest notifications and news.
- **Community Support:** Connect with peers and share resources.
- **Free:** All benefits are absolutely free!

JOIN US NOW AND BOOST YOUR EXAM PREPARATIONS!